



***Bode Plot Review***  
***High Frequency BJT Model***

## Logarithmic Frequency Response Plots (Bode Plots)

Generic form of frequency response *rational polynomial*, where we substitute  $j\omega$  for  $s$ :

$$H(s) = K \frac{s^m + a_{m-1}s^{m-1} + \cdots + a_1s + a_0}{s^n + b_{n-1}s^{n-1} + \cdots + b_1s + b_0}$$

$H(j\omega)$  can represent an impedance, an admittance, or a gain transfer function. If we are lucky, we can factor each of the polynomials as a product of first degree terms:

$$H(s) = K \frac{(s + z_1)(s + z_2) \cdots (s + z_m)}{(s + p_1)(s + p_2) \cdots (s + p_n)}$$

## *Logarithmic Frequency Response Plots (Bode Plots)*

Determination of a frequency response requires evaluating the complex number expression:

$$H(j\omega) = K \frac{(j\omega + z_1)(j\omega + z_2) \cdots (j\omega + z_m)}{(j\omega + p_1)(j\omega + p_2) \cdots (j\omega + p_n)}$$

Bode's approach was to simplify the calculations, using polar representation of the factors:

$$H(j\omega) = K \frac{z_1 * z_2 * \dots * z_m}{p_1 * p_2 * \dots * p_n} \frac{|j\frac{\omega}{z_1} + 1| e^{j\phi_1} |j\frac{\omega}{z_2} + 1| e^{j\phi_2} \cdots |j\frac{\omega}{z_m} + 1| e^{j\phi_m}}{|j\frac{\omega}{p_1} + 1| e^{j\theta_1} |j\frac{\omega}{p_2} + 1| e^{j\theta_2} \cdots |j\frac{\omega}{p_n} + 1| e^{j\theta_n}}$$

where

$$|j\frac{\omega}{z_k} + 1| = \sqrt{[(j\frac{\omega}{z_k} + 1)(-j\frac{\omega}{z_k} + 1)]} = \sqrt{(\frac{\omega}{z_k})^2 + 1} \quad \phi_k = \tan^{-1} \frac{\omega}{z_k}$$

## Bode Plot cont.

$$|j\frac{\omega}{z_k} + 1| = \sqrt{[(j\frac{\omega}{z_k} + 1)(-j\frac{\omega}{z_k} + 1)]} = \sqrt{(\frac{\omega}{z_k})^2 + 1}$$

- $\omega \ll z_k \Rightarrow |j\frac{\omega}{z_k} + 1| \approx 1$
- $\omega = z_k \Rightarrow |j\frac{\omega}{z_k} + 1| = \sqrt{2}$
- $\omega \gg z_k \Rightarrow |j\frac{\omega}{z_k} + 1| \approx \frac{\omega}{z_k}$

$$\phi_k = \tan^{-1} \frac{\omega}{z_k}$$

- $\omega \ll z_k \Rightarrow \tan^{-1} \frac{\omega}{z_k} \rightarrow 0^\circ$
- $\omega = z_k \Rightarrow \tan^{-1} \frac{\omega}{z_k} = 45^\circ$
- $\omega \gg z_k \Rightarrow \tan^{-1} \frac{\omega}{z_k} \rightarrow 90^\circ$

## *Bode Plots cont.*

$$G(\omega)e^{j\rho(\omega)} = K \frac{|j\omega + z_1|e^{j\phi_1}|j\omega + z_2|e^{j\phi_2}\cdots|j\omega + z_m|e^{j\phi_m}}{|j\omega + p_1|e^{j\theta_1}|j\omega + p_2|e^{j\theta_2}\cdots|j\omega + p_n|e^{j\theta_n}}$$

We can separate magnitude and phase angle calculations:

$$G(\omega) = |H(j\omega)| = K \frac{\prod_1^m z_i \left|j\frac{\omega}{z_1} + 1\right| \left|j\frac{\omega}{z_2} + 1\right| \cdots \left|j\frac{\omega}{z_m} + 1\right|}{\prod_1^n p_i \left|j\frac{\omega}{p_1} + 1\right| \left|j\frac{\omega}{p_2} + 1\right| \cdots \left|j\frac{\omega}{p_n} + 1\right|}$$

$$\rho(\omega) = (\phi_1 + \phi_2 + \cdots + \phi_m) - (\theta_1 + \theta_2 + \cdots + \theta_n)$$

where  $\phi_k = \tan^{-1} \frac{\omega}{z_k}$        $\theta_k = \tan^{-1} \frac{\omega}{p_k}$

## Bode Plots

$$G(\omega) = |H(j\omega)| = K_{dc} \frac{\left| j\frac{\omega}{z_1} + 1 \right| \left| j\frac{\omega}{z_2} + 1 \right| \cdots \left| j\frac{\omega}{z_m} + 1 \right|}{\left| j\frac{\omega}{p_1} + 1 \right| \left| j\frac{\omega}{p_2} + 1 \right| \cdots \left| j\frac{\omega}{p_n} + 1 \right|}$$

Where we define the *dc gain*, the value of the magnitude of  $H$  at  $\omega=0$ , as:

$$K_{dc} = K \frac{\prod_1^m z_i}{\prod_1^n p_i}$$

## Logarithmic Frequency Response Plots (Bode Plots)

$$G(\omega) = |H(j\omega)| = K_{dc} \frac{|j\frac{\omega}{z_1} + 1| |j\frac{\omega}{z_2} + 1| \cdots |j\frac{\omega}{z_m} + 1|}{|j\frac{\omega}{p_1} + 1| |j\frac{\omega}{p_2} + 1| \cdots |j\frac{\omega}{p_n} + 1|}$$

Another “simplification” converts the magnitude computation from multiplication to addition by working with its logarithm (in decibels):

$$G(\omega)_{dB} = \sum_1^m 20 \log_{10} |j\frac{\omega}{z_i} + 1| - \sum_1^n 20 \log_{10} |j\frac{\omega}{p_i} + 1|$$

## *Logarithmic Frequency Response Plots (Bode Plots)*

$$G(\omega)_{dB} = \sum_1^m 20 \log_{10} \left| j \frac{\omega}{z_i} + 1 \right| - \sum_1^n 20 \log_{10} \left| j \frac{\omega}{p_i} + 1 \right|$$

Let's calculate the frequency response for a simple transfer function and make some observations:

$$H(j\omega) = 10 \frac{j \frac{\omega}{1} + 1}{j \frac{\omega}{10} + 1}$$

## Simple Example

$$H(j\omega) = 10 \frac{j\frac{\omega}{1} + 1}{j\frac{\omega}{10} + 1} = 10 \frac{\sqrt{\left(\frac{\omega}{1}\right)^2 + 1}}{\sqrt{\left(\frac{\omega}{10}\right)^2 + 1}}$$

Working with logs:

$$|H_{dB}| = 20 \log_{10}|10| + 20 \log_{10} \left| j \frac{\omega}{1} + 1 \right| - 20 \log_{10} \left| j \frac{\omega}{10} + 1 \right|$$

Note:

1. if the **coefficient of  $j$** , i.e.  $\frac{\omega}{\omega_a} \leq 0.1$ , then  $\left| j \frac{\omega}{\omega_a} + 1 \right| \approx 1$  and  $\log_{10} \left| j \frac{\omega}{\omega_a} + 1 \right| = 0$ .
2. If the **coefficient of  $j$** , i.e.  $\frac{\omega}{\omega_a} \geq 10$ , then  $\left| j \frac{\omega}{\omega_a} + 1 \right| \approx \frac{\omega}{\omega_a}$  and  $\log_{10} \left| j \frac{\omega}{\omega_a} + 1 \right| = \log_{10} \frac{\omega}{\omega_a}$ .
3. When  $\omega = \omega_a$ ,  $\left| j \frac{\omega}{\omega_a} + 1 \right| = \sqrt{2}$  and  $\log_{10} \left| j \frac{\omega}{\omega_a} + 1 \right| = 0.15$ .

## *Simple Example*

$$|H_{dB}| = 20 \log_{10} |K_{dc}| + 20 \log_{10} \left| j \frac{\omega}{1} + 1 \right| - 20 \log_{10} \left| j \frac{\omega}{10} + 1 \right|$$

Applying the approximation on the previous slide:

$$\omega < 1 \Rightarrow |H_{dB}| = 20 \log_{10} K_{dc}$$

$$1 < \omega < 10 \Rightarrow |H_{dB}| = 20 \log_{10} K_{dc} + 20 \log_{10} \frac{\omega}{1}$$


$$\omega > 10 \Rightarrow |H_{dB}| = 20 \log_{10} K_{dc} + 20 \log_{10} \frac{\omega}{1} - 20 \log_{10} \frac{\omega}{10}$$



## *Scilab Simulation*

```
Kdc=10; //Example Bode Plot
KdB= 20*log10(Kdc);
omegaz=1;
fz=omegaz/(2*%pi);
omegap=10;
fp=omegap/(2*%pi);
f=0.01:0.01:100;
magnum=sqrt((f/fz)^2 + 1);
magden=sqrt((f/fp)^2 + 1);
FreqResp=KdB+20*(log10(magnum)-log10(magden));
plot(f,FreqResp)
term1=KdB*sign(f); //Create constant array of length len(f)
term2=max(0,20*log10(f/fz)); //Zero for f < fz;
term3=min(0,-20*log10(f/fp)); //Zero for f < fp;
BodePlot=term1+term2+term3;
plot(f,BodePlot);
err=BodePlot-FreqResp;
plot(f,err);
```

## Scilab Results

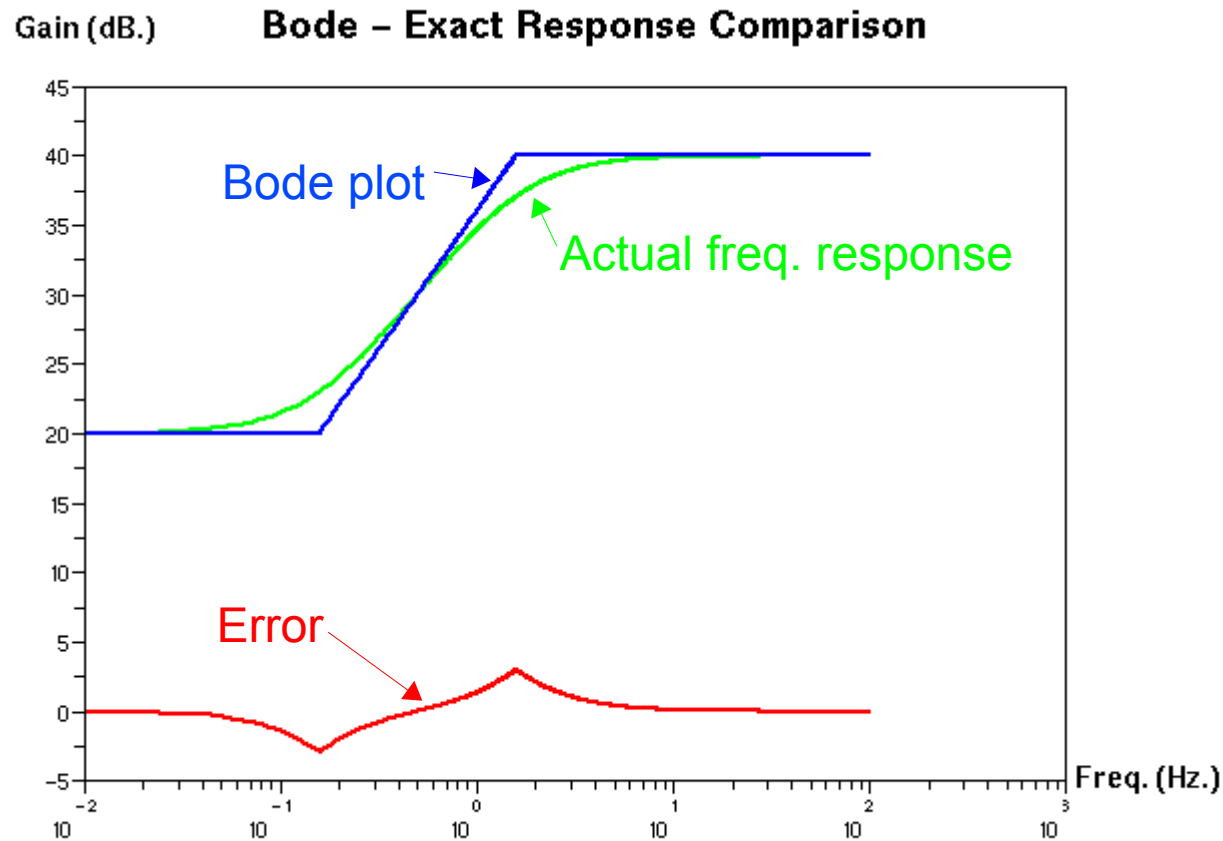


## *Observations*

The  $\omega/\omega_a$  ratio changes by 20 dB for each order of magnitude change in frequency ( $20\log_{10}(10) = 20$ ).


Our “rule of 10” scheme for using either 1, or  $\omega/\omega_a$  for magnitude estimation is quite accurate. This why the Bode plot is called an asymptotic plot.

We can plot a system transfer function, then position straight line segments of  $\pm x*20 \text{ dB/decade}$  on the Bode plot. The intersection of the lines occurs at the break frequencies.
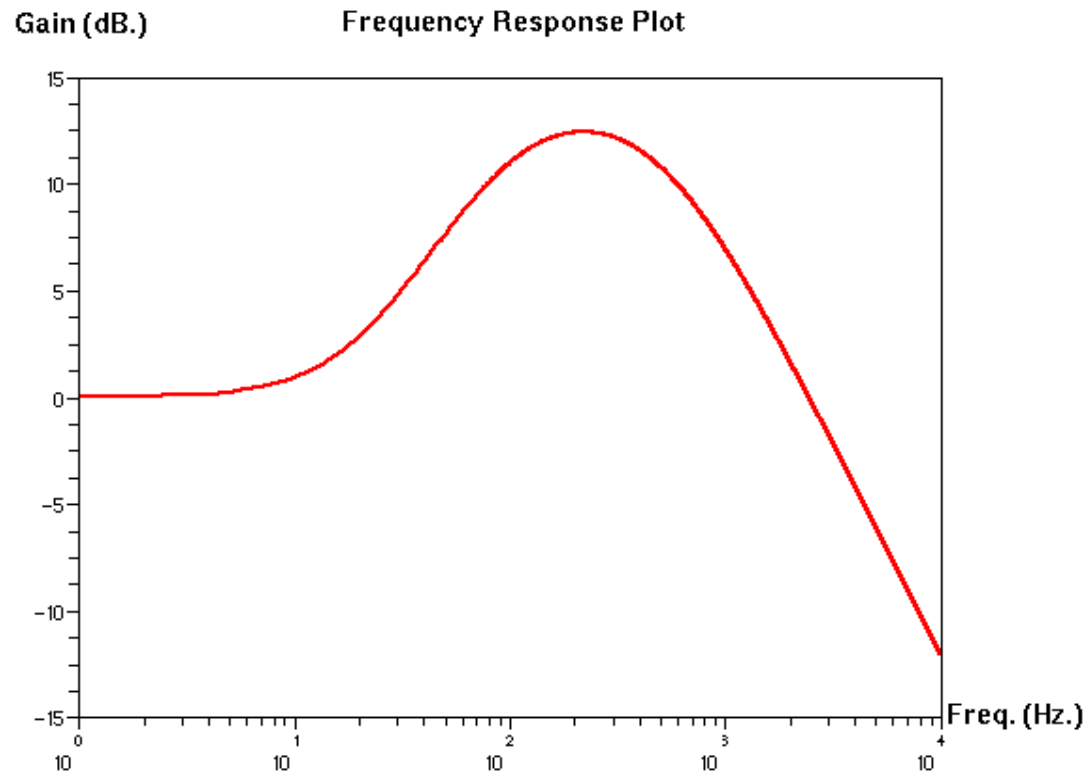
## *Bode Plot Used to Estimate Zeros & Poles*





## Bode Plot Superposition

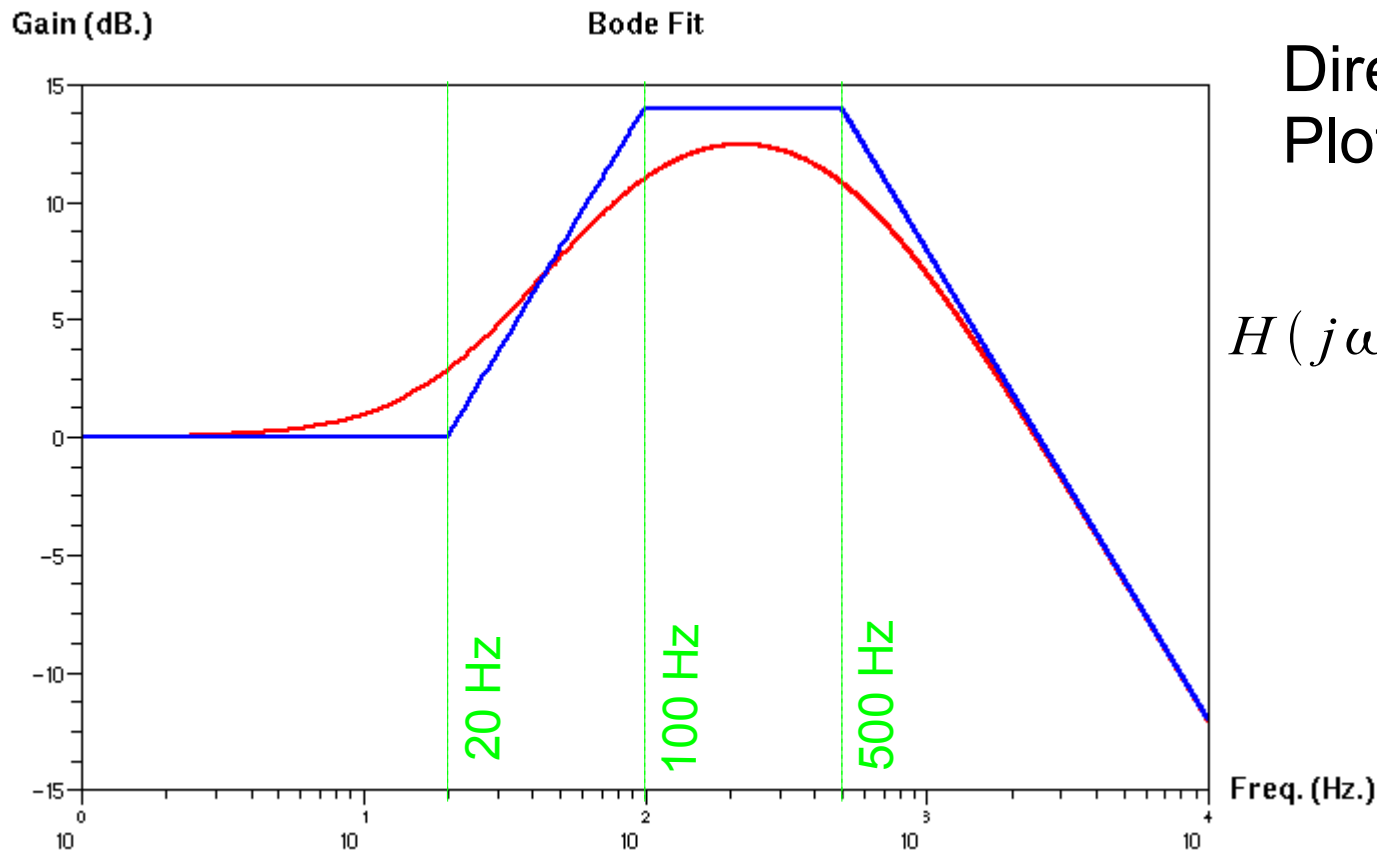

Directly from the Bode Plot!

$$H(j\omega) = \frac{\frac{j\omega}{20} + 1}{\left(\frac{j\omega}{100} + 1\right)\left(\frac{j\omega}{500} + 1\right)}$$
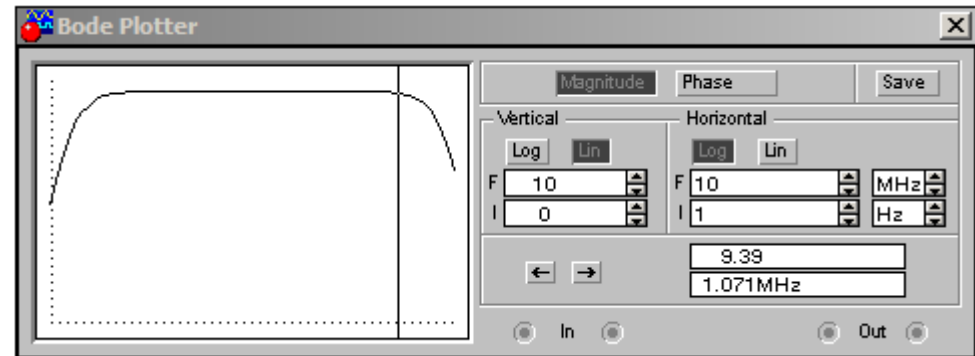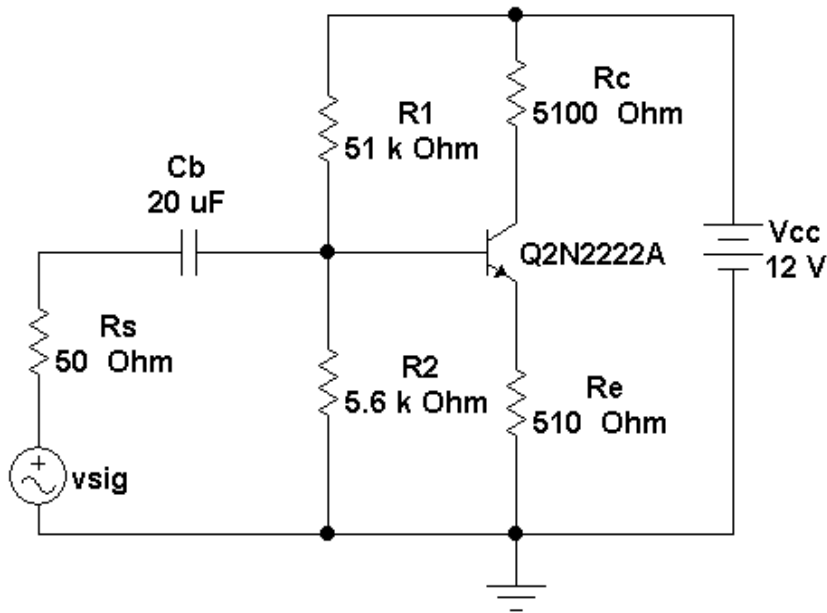
## Gain of 10 Amplifier – Non-ideal Transistor




Gain starts dropping at about 1MHz.


Why!

Because of internal transistor capacitances that we have ignored in our models.
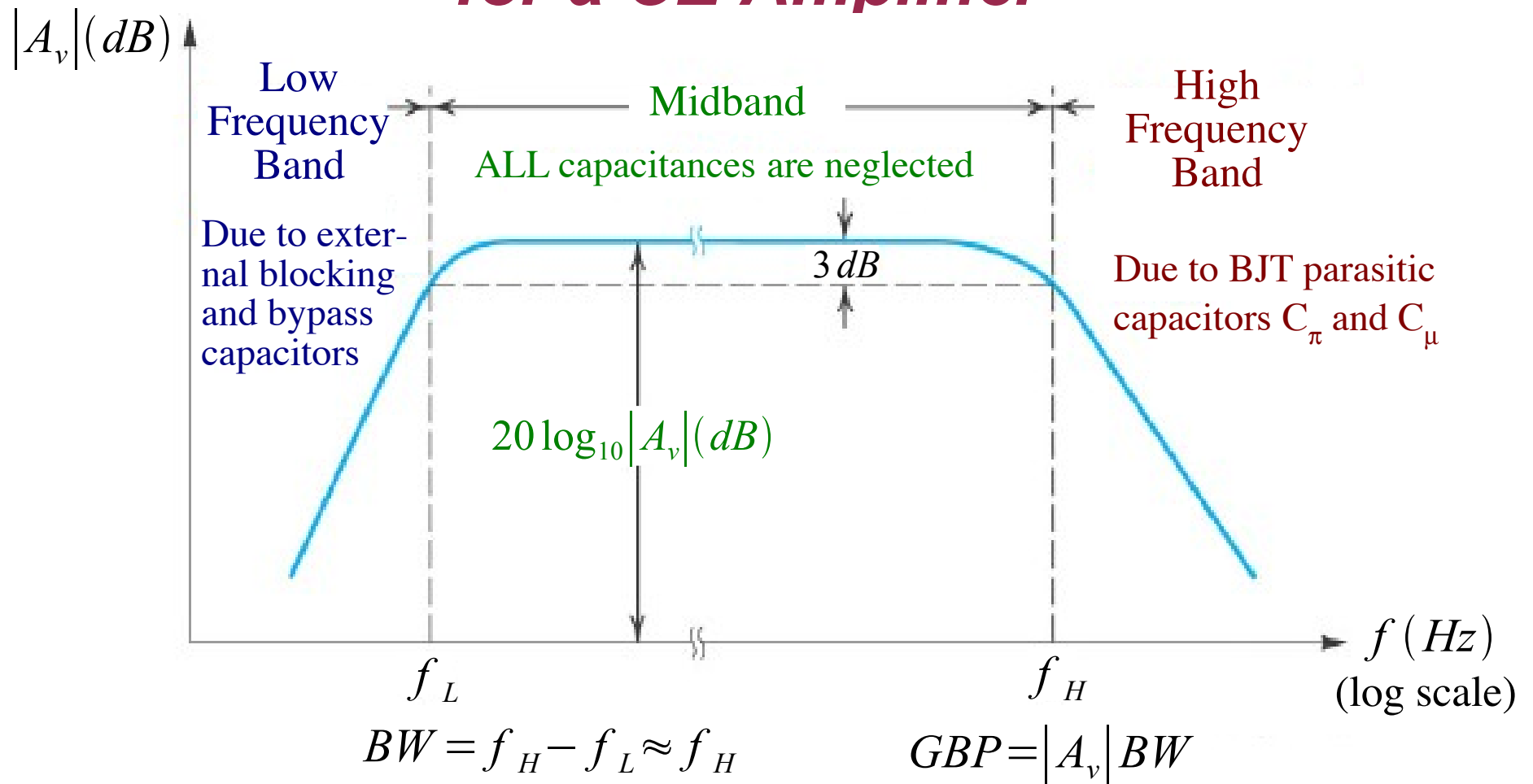
## Sketch of Typical Voltage Gain Response for a CE Amplifier



## High Frequency Small-signal Model

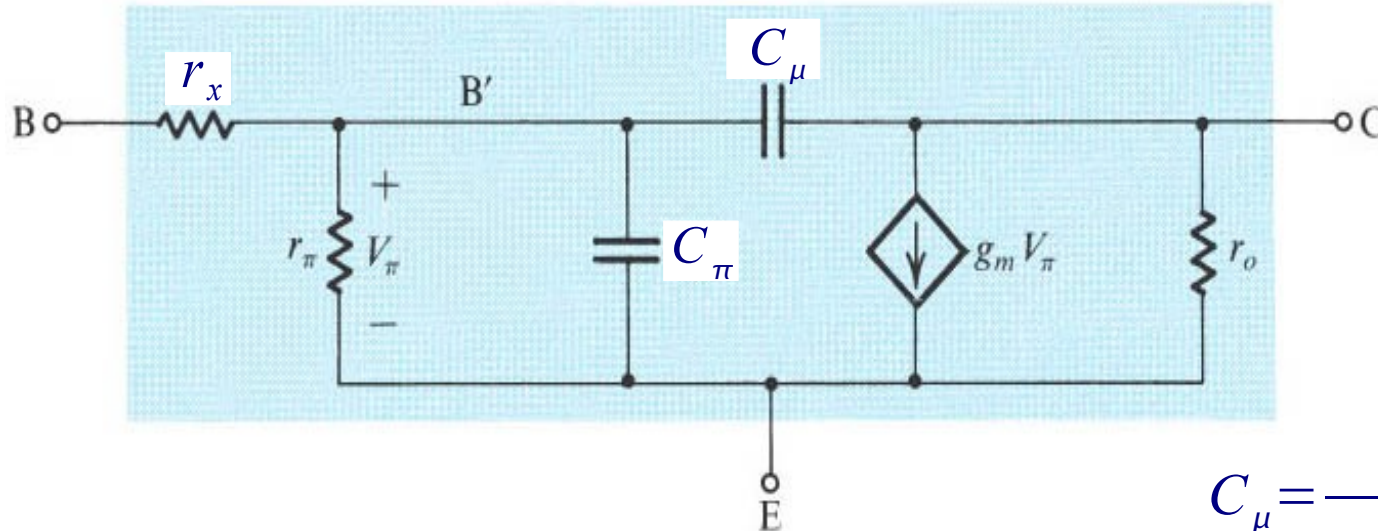

Two capacitors and a resistor added.

A base to emitter capacitor,  $C_{\pi}$

A base to collector capacitor,  $C_{\mu}$

A resistor,  $r_x$ , representing the base terminal resistance ( $r_x \ll r_{\pi}$ )

$$C_{\mu} = \frac{C_{\mu 0}}{\left(1 + \frac{V_{CB}}{V_{0c}}\right)^m}$$

$$C_{\pi} = C_{de} + \frac{C_{je0}}{\left(1 + \frac{V_{BE}}{V_{0e}}\right)^m}$$


## *High Frequency Small-signal Model*

The internal capacitors on the transistor have a strong effect on circuit high frequency performance! They attenuate base signals, decreasing  $v_{be}$  since their reactance approaches zero (short circuit) as frequency increases.

As we will see later  $C_{\mu}$  is the principal cause of this gain loss at high frequencies. At the base  $C_{\mu}$  looks like a capacitor of value  $k C_{\mu}$  connected between base and emitter, where  $k > 1$  and may be  $\gg 1$ .

This phenomenon is called the *Miller Effect*.

## Frequency-dependent “beta” $h_{fe}$

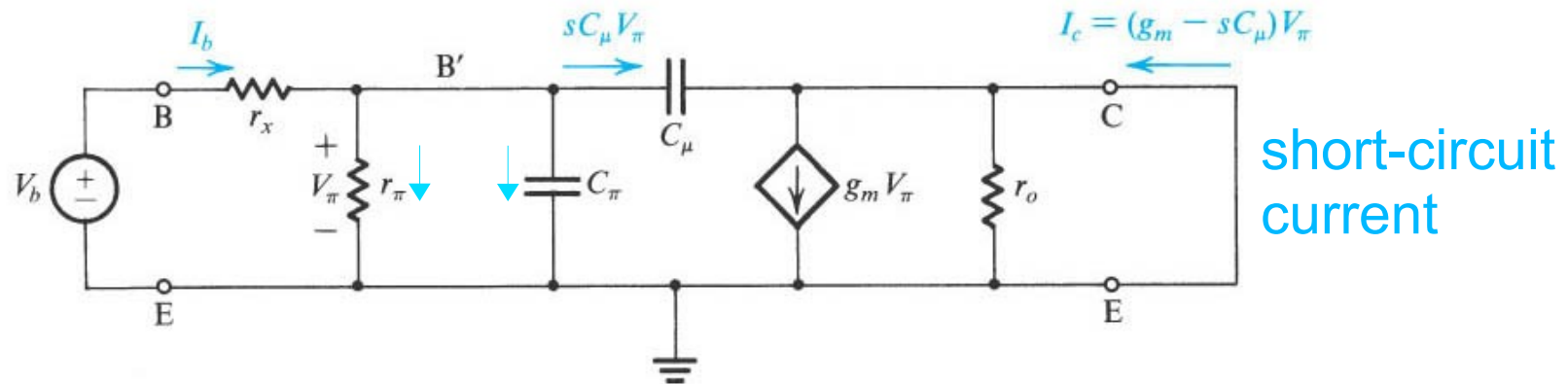


The relationship  $i_c = \beta i_b$  does not apply at high frequencies  $f > f_H$ !

Using the relationship  $-i_c = f(V_\pi)$  – find the new relationship between  $i_b$  and  $i_c$ . For  $i_b$  (using *phasor notation* ( $I_x$  &  $V_x$ ) for *frequency domain analysis*):

@ node B': 
$$I_b = \left( \frac{1}{r_\pi} + sC_\pi + sC_\mu \right) V_\pi \quad \text{where } r_x \approx 0 \quad (\text{ignore } r_x)$$
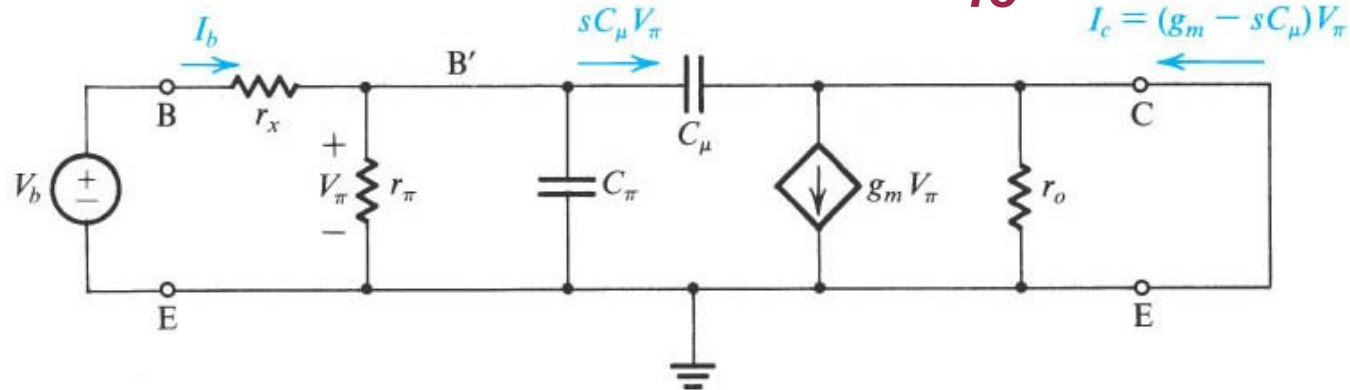
## Frequency-dependent $h_{fe}$ or “beta”



The ratio of the two equations:

$$I_b = \left( \frac{1}{r_\pi} + s C_\pi + s C_\mu \right) V_\pi \quad @ \text{ node C: } I_c = (g_m - s C_\mu) V_\pi \quad (\text{ignore } r_o)$$

Leads to a new relationship between the  $I_b$  and  $I_c$ :

$$h_{fe} = \frac{I_c}{I_b} = \frac{g_m - s C_\mu}{\frac{1}{r_\pi} + s C_\pi + s C_\mu}$$

## Frequency Response of $h_{fe}$

$$h_{fe} = \frac{g_m - sC_\mu}{\frac{1}{r_\pi} + sC_\pi + sC_\mu}$$

multiply N&D by  $r_\pi$

$$h_{fe} = \frac{(g_m - j\omega C_\mu)r_\pi}{1 + j\omega(C_\pi + C_\mu)r_\pi}$$

factor N to isolate  $g_m$

$$h_{fe} = \frac{\left(1 - j\omega \frac{C_\mu}{g_m}\right) \underbrace{g_m r_\pi}_\beta}{1 + j\omega(C_\pi + C_\mu)r_\pi}$$

$$g_m = \frac{I_C}{V_T} \quad r_\pi = \beta \frac{V_T}{I_C}$$

For small  $\omega = \omega_{low}$ :  $\omega_{low} \frac{C_\mu}{g_m} \ll 1 < \frac{1}{10}$

and:  $\omega_{low}(C_\pi + C_\mu)r_\pi \ll 1 < \frac{1}{10}$


Note:  $\omega_{low}(C_\pi + C_\mu)r_\pi = \omega_{low}(C_\pi + C_\mu) \frac{\beta}{g_m} \gg \omega_{low} \frac{C_\mu}{g_m}$

We have:

$$h_{fe} = g_m r_\pi = \beta$$
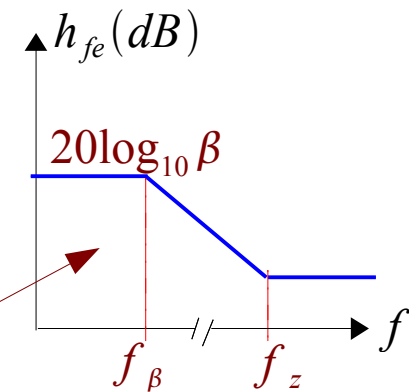
## Frequency Response of $h_{fe}$ cont.

$$h_{fe} = \frac{(1 - j\omega \frac{C_\mu}{g_m}) g_m r_\pi}{1 + j\omega (C_\pi + C_\mu) r_\pi} = \frac{\left(1 - j \frac{\omega}{\omega_z}\right) g_m r_\pi}{\left(1 + j \frac{\omega}{\omega_\beta}\right)} = \frac{\left(1 - j \frac{f}{f_z}\right)}{\left(1 + j \frac{f}{f_\beta}\right)} \beta$$



$$(C_\pi + C_\mu) r_\pi = (C_\pi + C_\mu) \frac{\beta}{g_m} \gg \frac{C_\mu}{g_m} \Rightarrow f_z \gg f_\beta$$

Hence, the lower break frequency or  $-3dB$  frequency is  $f_\beta$

$$f_\beta = \frac{1}{2\pi (C_\pi + C_\mu) r_\pi} = \frac{g_m}{2\pi (C_\pi + C_\mu) \beta} \quad \text{the upper:} \quad f_z = \frac{1}{2\pi C_\mu / g_m} = \frac{g_m}{2\pi C_\mu}$$

where  $f_z > 10 f_\beta$

## *Frequency Response of $h_{fe}$ cont.*

Using Bode plot concepts, for the range where:  $\omega < \omega_\beta$

$$h_{fe} = g_m r_\pi = \beta$$

For the range where:  $f_\beta < f < f_z$  s.t.  $|1 - j f / f_z| \approx 1$

We consider the frequency-dependent numerator term to be 1 and focus on the response of the denominator:

$$h_{fe} = \frac{g_m r_\pi}{\left(1 + j \frac{f}{f_\beta}\right)} = \frac{\beta}{\left(1 + j \frac{f}{f_\beta}\right)}$$

## Frequency Response of $h_{fe}$ cont.

Neglecting numerator term:

$$h_{fe} = \frac{g_m r_\pi}{\left(1 + j \frac{f}{f_\beta}\right)} = \frac{\beta}{\left(1 + j \frac{f}{f_\beta}\right)}$$

And for  $f/f_\beta \gg 1$  (but  $< f/f_z$ ):

$$|h_{fe}| \approx \frac{\beta}{\left(\frac{f}{f_\beta}\right)} = \beta \frac{f_\beta}{f}$$

Unity gain bandwidth:  $|h_{fe}| = 1 \Rightarrow \beta \frac{f_\beta}{f} = 1 \Rightarrow f_T = \beta f_\beta$

$$f_T = \frac{\omega_T}{2\pi} = \beta f_\beta$$

BJT unity-gain frequency or GBP

## Frequency Response of $h_{fe}$ cont.

$$\beta = 100 \quad r_{\pi} = 2500 \, \Omega \quad C_{\pi} = 12 \, pF \quad C_{\mu} = 2 \, pF \quad g_m = 40 \cdot 10^{-3} \, S$$

$$\omega_{\beta} = \frac{1}{(C_{\pi} + C_{\mu})r_{\pi}} = \frac{10^{12} \cdot 10^{-3}}{(12 + 2) \cdot 2.5} = 28.57 \cdot 10^6 \, rps$$

$$f_{\beta} = \frac{\omega_{\beta}}{2\pi} = \frac{28.57}{6.28} 10^6 \, Hz = 4.55 \, MHz \quad f_T = \beta f_{\beta} = 455 \, MHz$$


$$\omega_z = \frac{g_m}{C_{\mu}} = \frac{40 \cdot 10^{-3} \cdot 10^{12}}{2} \, Hz = 20 \cdot 10^9 \, rps$$

$$f_z = \frac{\omega_z}{2\pi} = 3.18 \cdot 10^9 \, Hz = 3180 \, MHz$$


## *Scilab $f_T$ Plot*

```
//fT Bode Plot
Beta=100;
KdB= 20*log10(Beta);
fz=3180;
fp=4.55;
f= 1:1:10000;
term1=KdB*sign(f); //Constant array of len(f)
term2=max(0,20*log10(f/fz)); //Zero for f < fz;
term3=min(0,-20*log10(f/fp)); //Zero for f < fp;
BodePlot=term1+term2+term3;
plot(f,BodePlot);
```

## $h_{fe}$ Bode Plot

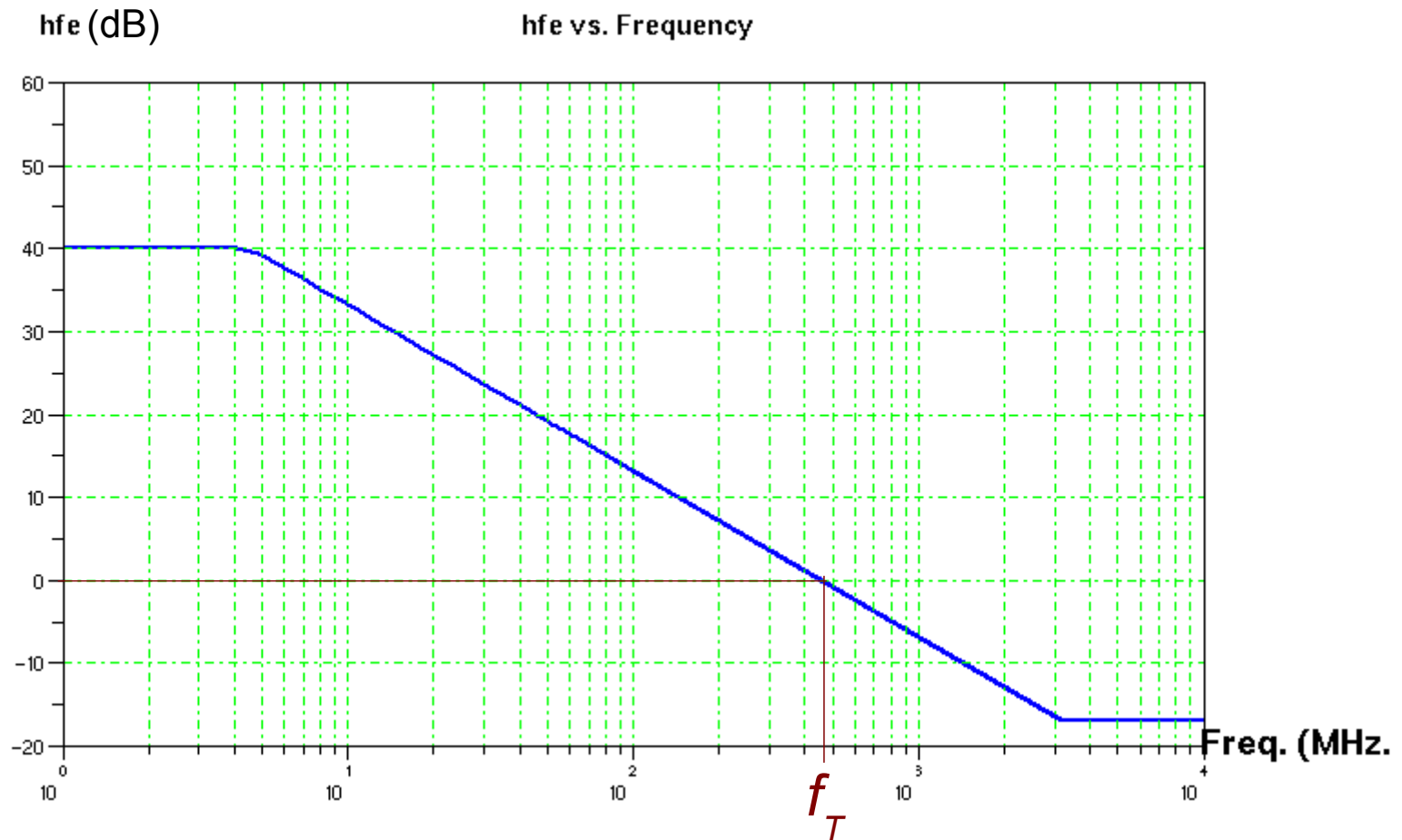


## Multisim Simulation

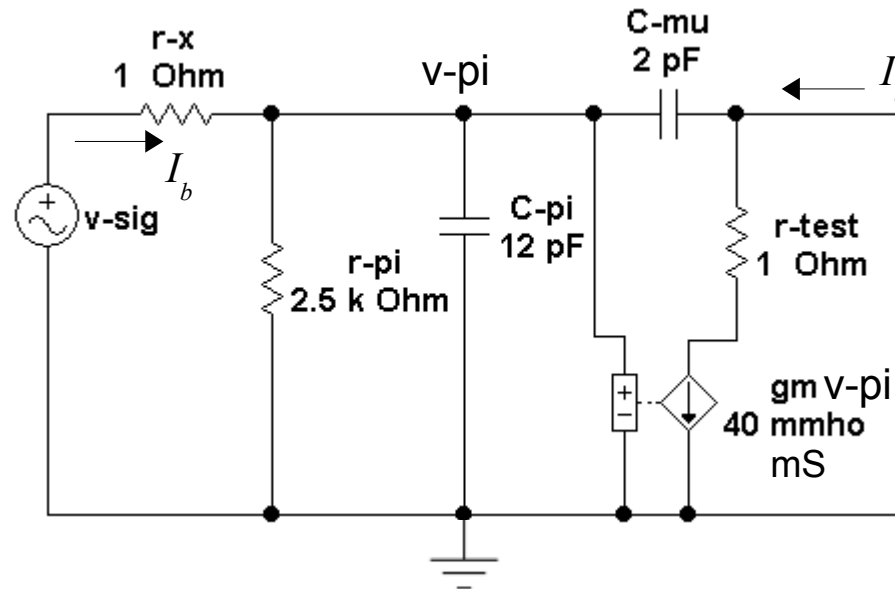


Insert 1 ohm resistors – we want to measure a current ratio.

$$h_{fe} = \frac{I_c}{I_b} = \frac{g_m - s C_\mu}{\frac{1}{r_\pi} + s(C_\pi + C_\mu)}$$

## Simulation Results

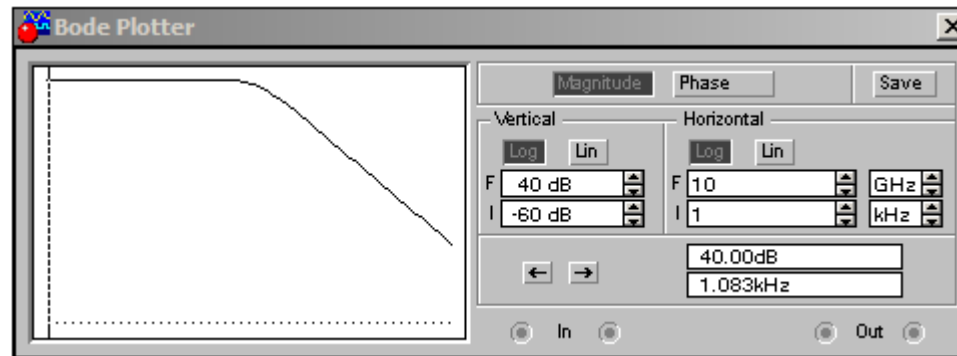

Low frequency  $|h_{fe}|$

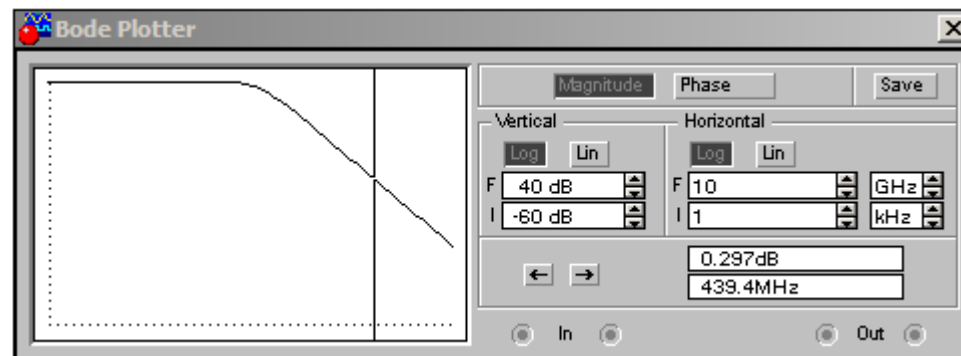

Unity Gain frequency about 440 MHz.