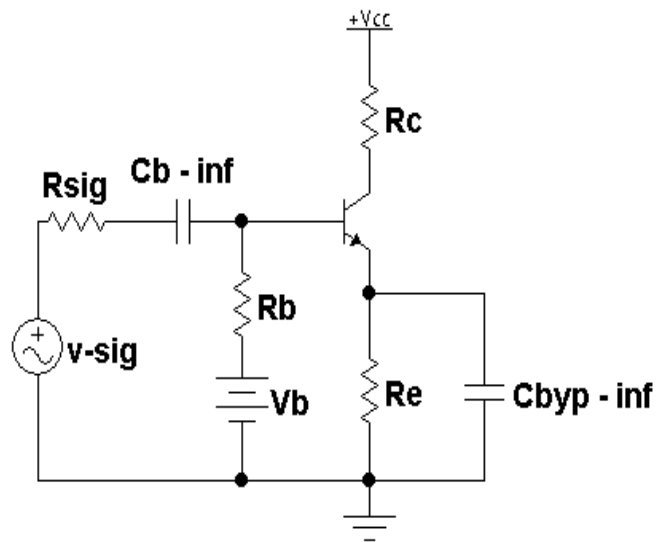





# *Miller Effect*

## *Cascode BJT Amplifier*

## Prototype Common Emitter Circuit





Ignore “low frequency” capacitors

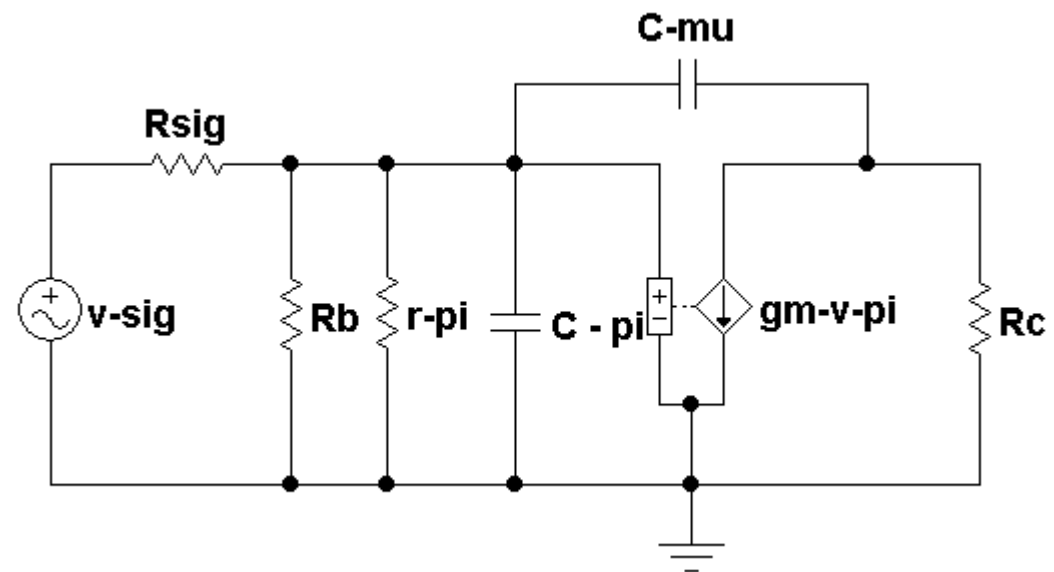


High frequency model

## Multisim Simulation

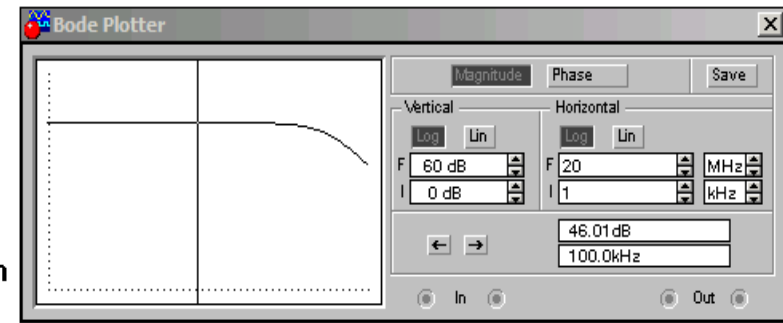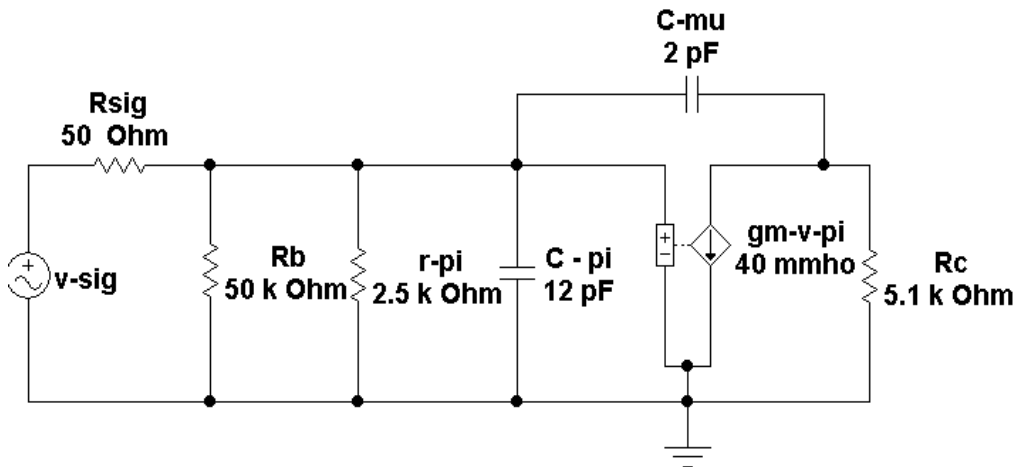


Mid-band gain

$$|A_v| = g_m R_C = (40 \text{ mS}) * (5.1 \text{ k} \Omega) = 204 (46.2 \text{ dB})$$

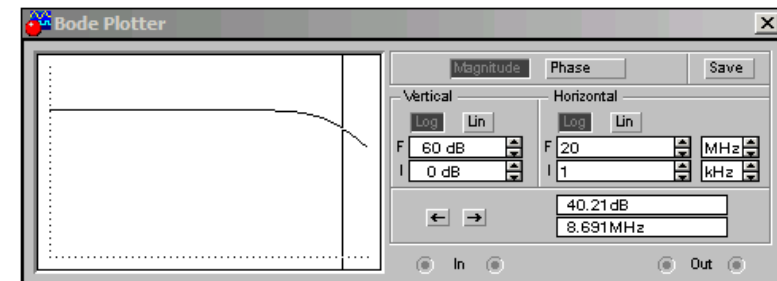

Half-gain point


## Introducing the Miller Effect

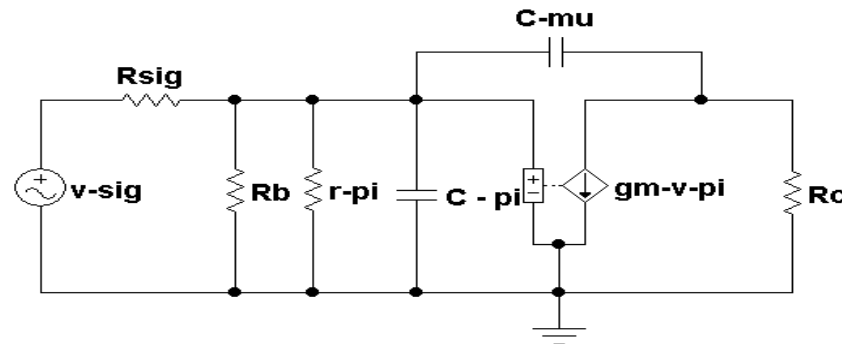

The feedback connection of  $C_{\mu}$  between base and collector causes it to appear to the amplifier like a large capacitor  $(1-K)C_{\mu}$  has been inserted between the base and emitter terminals. This phenomenon is called the “Miller effect” and the capacitive multiplier “ $1-K$ ” acting on  $C_{\mu}$  equals the **common emitter** amplifier mid-band gain, i.e.  $K = -g_m R_C$ .

Common base and common collector amplifiers do not suffer from the Miller effect, since in these amplifiers, one side of  $C_{\mu}$  is connected directly to ground.

## High Frequency CC and CB Models

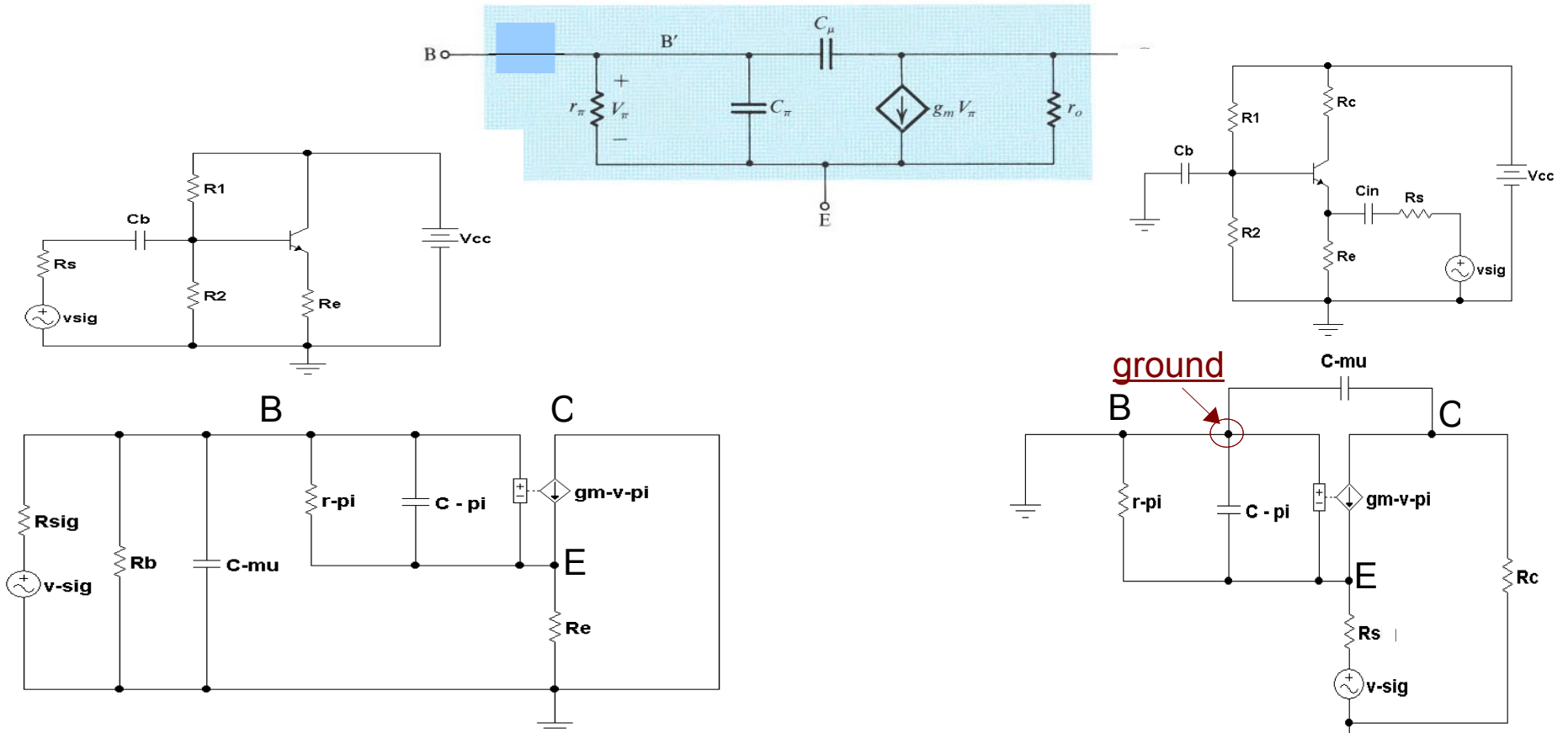


Common Collector

$C_{\mu}$  is in parallel with  $R_B$ .

Common Base

$C_{\mu}$  is in parallel with  $R_C$ .

## Miller's Theorem

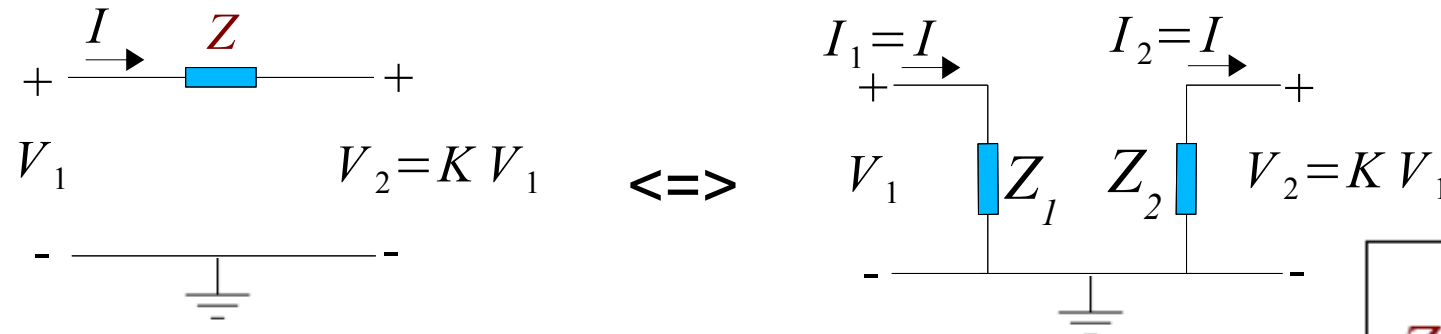

$$I = \frac{V_1 - V_2}{Z} = \frac{V_1 - K V_1}{Z} = \frac{V_1}{Z} \frac{1 - K}{1 - K} \Rightarrow Z_1 = \frac{V_1}{I_1} = \frac{V_1}{I} = \frac{Z}{1 - K}$$


$$Z = \frac{1}{j 2 \pi f C_\mu}$$

$$Z_1 \approx \frac{1}{j 2 \pi f C_\mu (1 - K)}$$

$$\Rightarrow Z_2 = \frac{V_2}{-I_2} = \frac{V_2}{-I} = -\frac{Z}{\frac{1}{K} - 1} = \frac{Z}{1 - \frac{1}{K}} \approx Z \text{ if } K \gg 1$$

Let's examine Miller's Theorem as it applies to the HF model for the BJT CE amplifier.

## Common Emitter Miller Effect Analysis

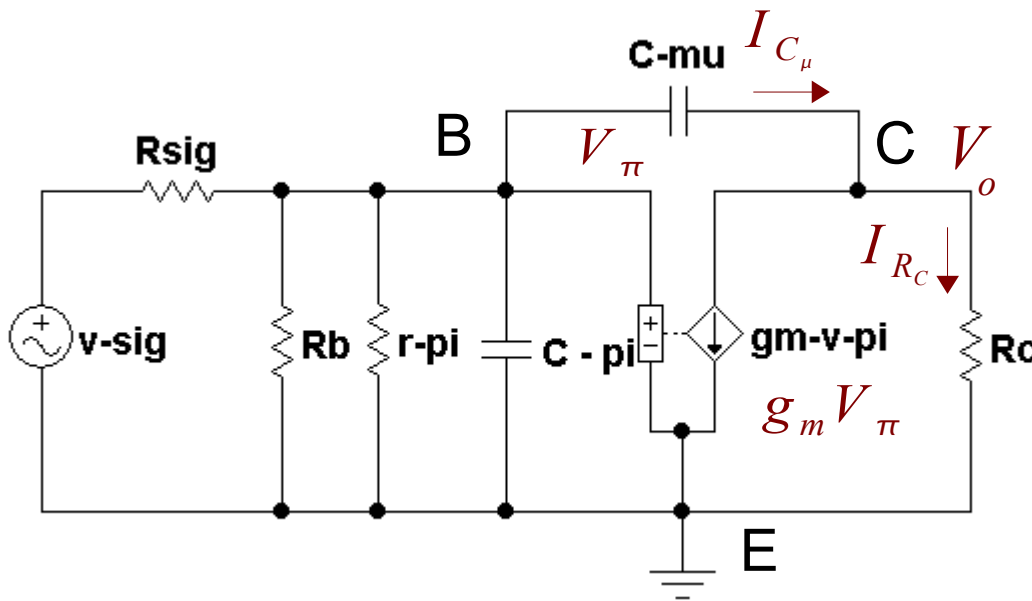

Note: The current through  $C_\mu$  depends only on  $V_\pi$ !

Determine effect of  $C_\mu$ :

Using phasor notation:

$$I_{R_C} = -g_m V_\pi + I_{C_\mu}$$

or

$$V_o = (-g_m V_\pi + I_{C_\mu}) R_C$$

where

$$I_{C_\mu} = (V_\pi - V_o) s C_\mu$$

$$I_{C_\mu} = \underbrace{(V_\pi + g_m V_\pi R_C - I_{C_\mu} R_C)}_{V_o} s C_\mu$$



## Common Emitter Miller Effect Analysis II

From slide 7:

$$I_{C_\mu} = (V_\pi + g_m V_\pi R_C - I_{C_\mu} R_C) s C_\mu$$

Collect terms for  $I_{C_\mu}$  and  $V_\pi$ :

$$(1 + s R_C C_\mu) I_{C_\mu} = (1 + g_m R_C) s C_\mu V_\pi$$

$$I_{C_\mu} = \frac{(1 + g_m R_C) s C_\mu}{(1 + s R_C C_\mu)} V_\pi = \frac{s(1 + g_m R_C) C_\mu}{(1 + s R_C C_\mu)} V_\pi$$

Miller Capacitance  $C_{eq}$  :  $C_{eq} = (1 - K) C_\mu = (1 + g_m R_C)$

## *Common Emitter Miller Effect Analysis III*


$$C_{eq} = (1 + g_m R_C) C_\mu$$

For our example circuit:

$$1 + g_m R_C = 1 + 0.040 \cdot 5100 = 205$$

$$C_{eq} = (205) \cdot 2 \text{ pF} \approx 410 \text{ pF}$$
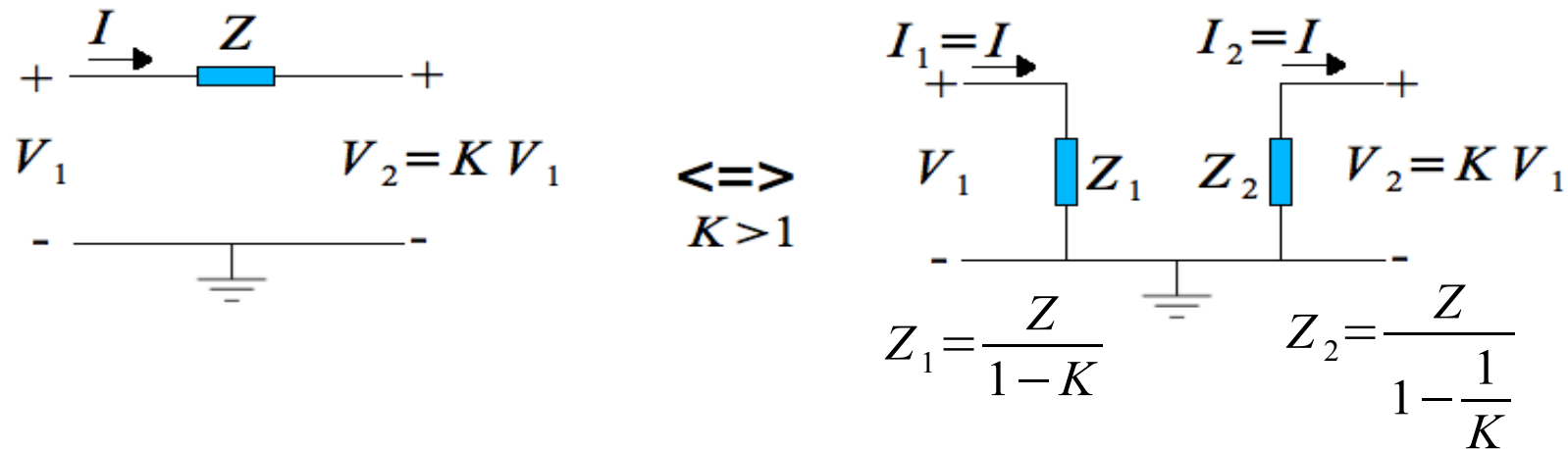
## Apply Miller's Theorem to BJT CE Amplifier




For the BJT CE Amplifier:  $Z = \frac{1}{j\omega C_\mu}$  and  $K = -g_m R_C$

$$\Rightarrow Z_1 = \frac{1}{j\omega(1 + g_m R_C)C_\mu} \quad \text{and} \quad Z_2 = \frac{1}{j\omega(1 + \frac{1}{g_m R_C})C_\mu} \approx \frac{1}{j\omega C_\mu}$$

$$C_{eq} = (1 + g_m R_C)C_\mu$$


Miller's Theorem  $\Rightarrow$  important simplification to the HF BJT CE Model

## Simplified HF Model

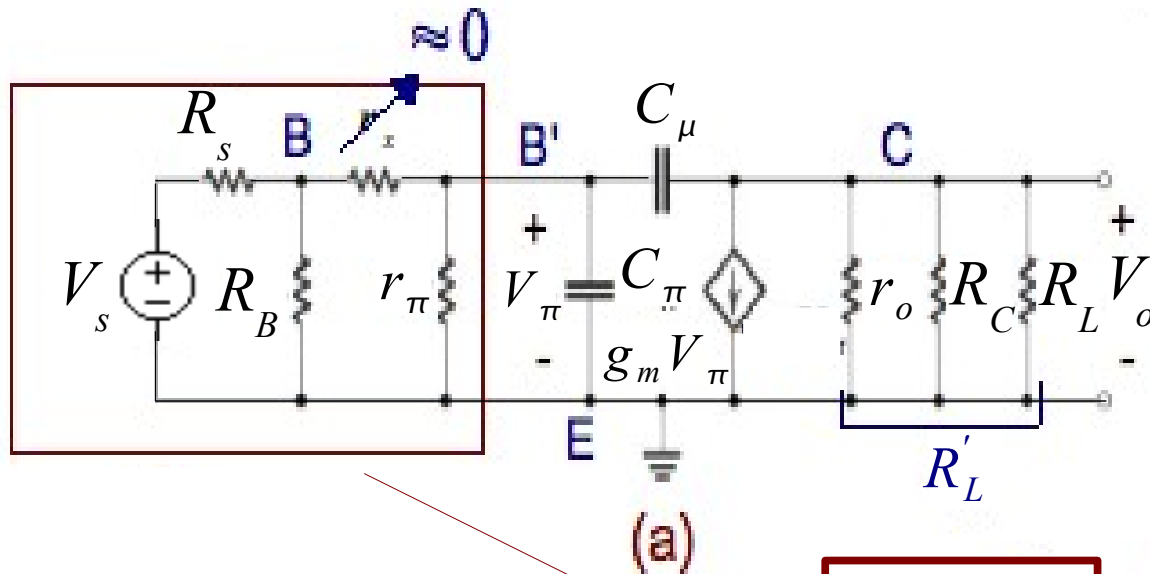


$$V'_s = V_s \frac{R_B \parallel r_\pi}{R_B \parallel r_\pi + R_{sig}}$$
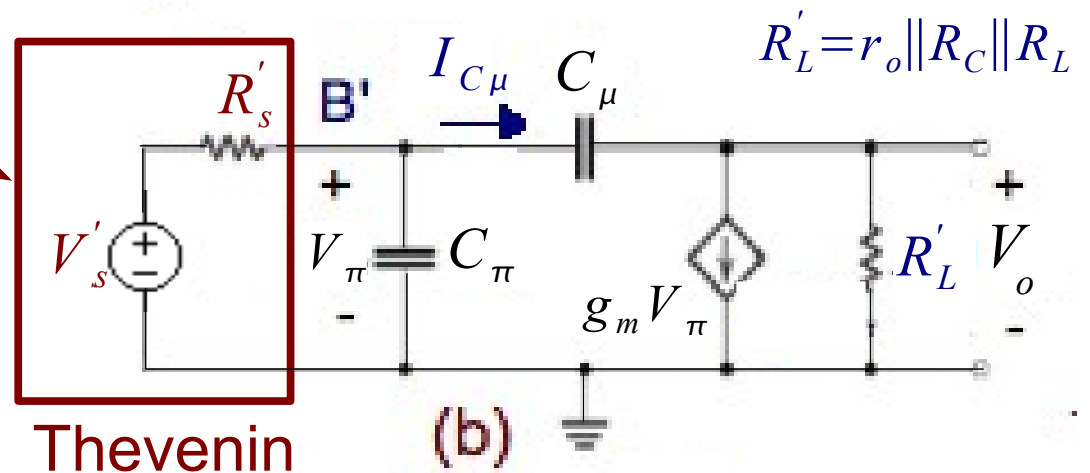
$$R'_s = r_\pi \parallel (R_B \parallel R_s)$$




## Simplified HF Model

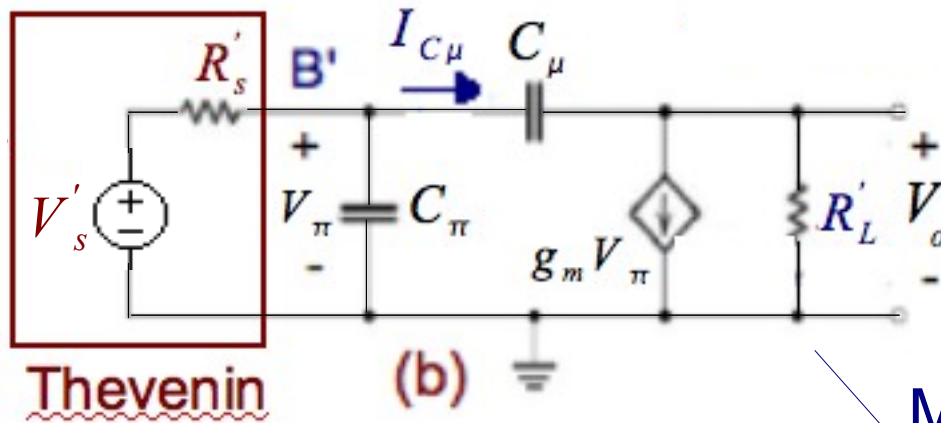


Miller's Theorem

$$C_{in} = C_{\pi} + C_{eq}$$

$$= C_{\pi} + C_{\mu} (1 + g_m R'_L)$$

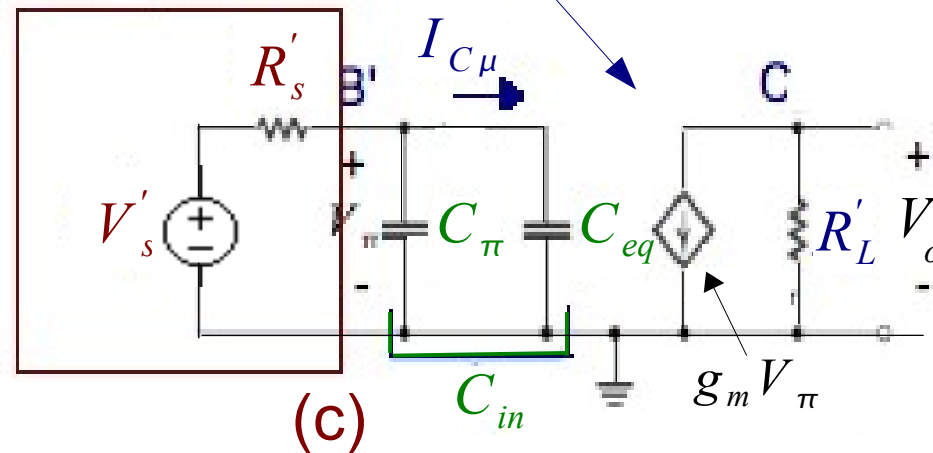


## Simplified HF Model

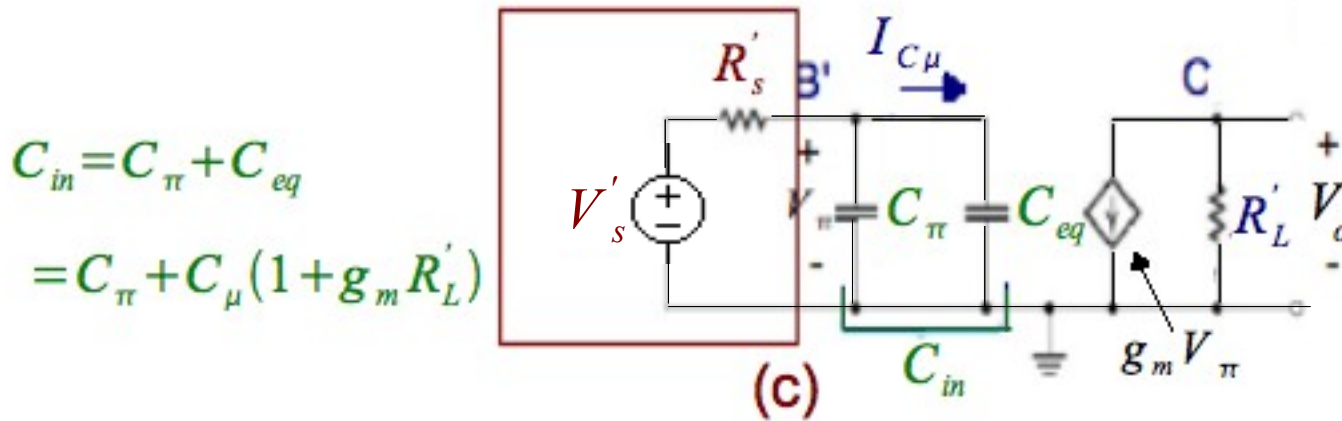

$$A_v(f) = \frac{V_o}{V_s} \approx \frac{-g_m R'_L}{1 + j2\pi f C_{in} R'_s}$$

$$f_H = \frac{1}{2\pi C_{in} R'_s}$$

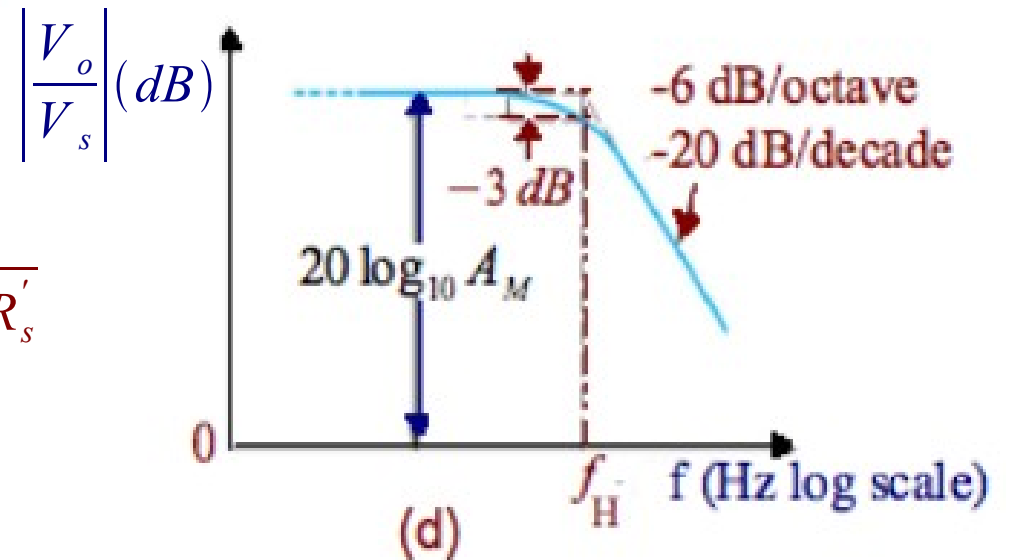



## *The Cascode Amplifier*

A two transistor amplifier used to obtain simultaneously:

1. Reasonably high input impedance.
2. Reasonable voltage gain.
3. Wide bandwidth.

None of the conventional single transistor designs will meet all of the criteria above. The cascode amplifier will meet all of these criteria. a cascode is a combination of a common emitter stage cascaded with a common base stage. (In “olden days” the cascode amplifier was a cascade of *grounded cathode* and *grounded grid* vacuum tube stages – hence the name “cascode,” which has persisted in modern terminology.


## The Cascode Circuit

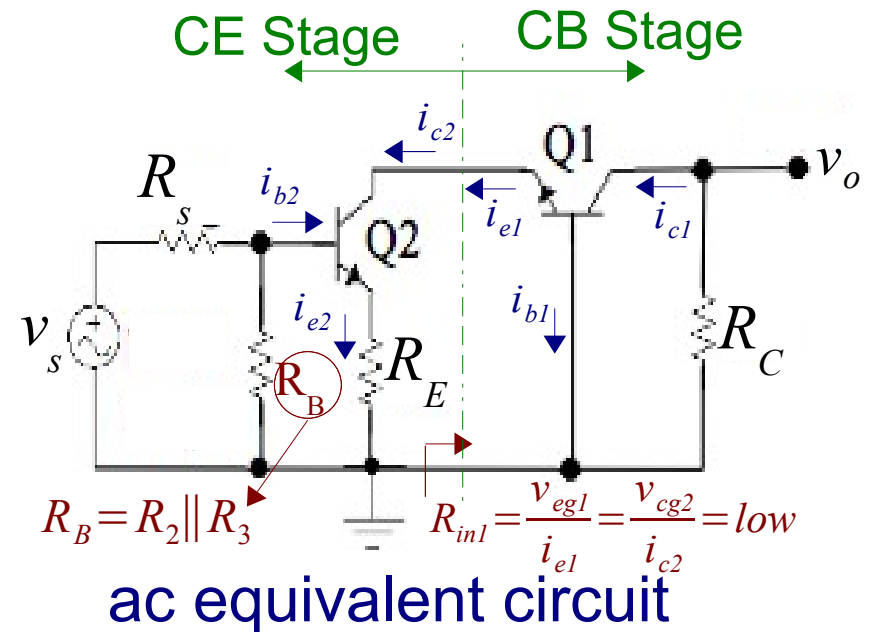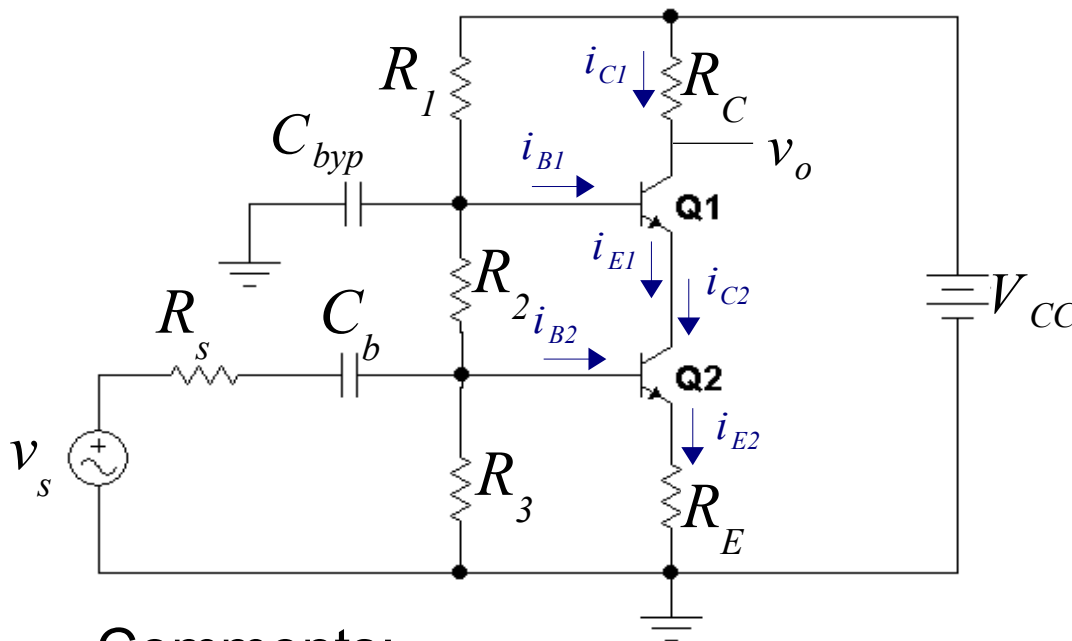

Comments:

1.  $R_1$ ,  $R_2$ ,  $R_3$ , and  $R_C$  set the bias levels for both Q1 and Q2.
2. Determine  $R_E$  for the desired voltage gain.
3.  $C_b$  and  $C_{byp}$  are to act as “open circuits” at dc and act as “short circuits” at all operating frequencies of interest, i.e.  $f > f_{min}$ .

## Cascode Mid-Band Small Signal Model

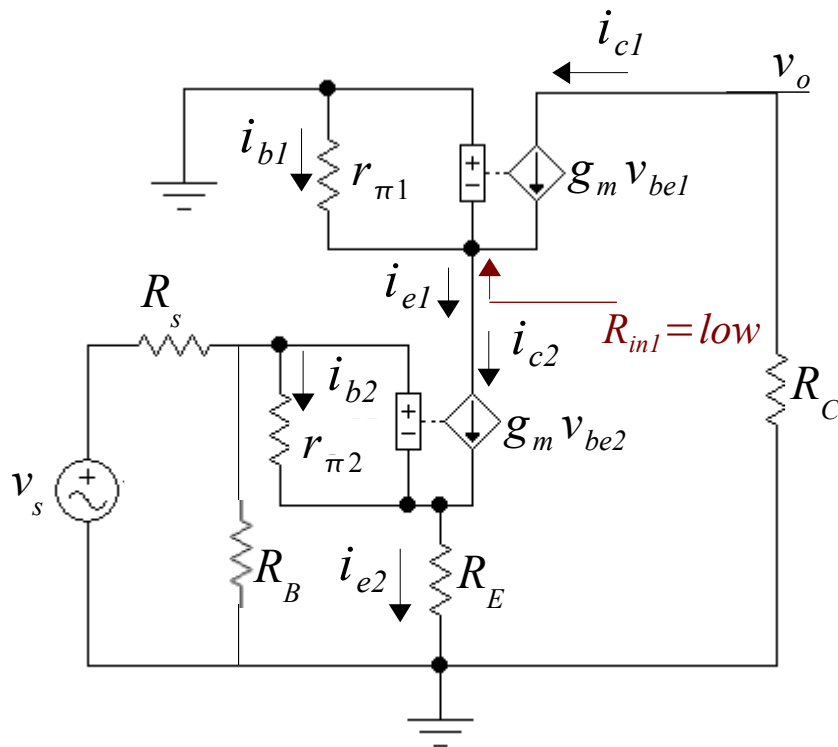

$$g_{m1} = g_{m2} = g_m$$

$$r_{e1} = r_{e2} = r_e$$

$$r_{\pi 1} = r_{\pi 2} = r_{\pi}$$

1. Show reduction in Miller effect
2. Evaluate small-signal voltage gain

### OBSERVATIONS

a. The emitter current of the CB stage is the collector current of the CE stage. (This also holds for the dc bias current.)


$$i_{e1} = i_{c2}$$

b. The base current of the CB stage is:

$$i_{b1} = \frac{i_{e1}}{\beta + 1} = \frac{i_{c2}}{\beta + 1}$$

c. Hence, both stages have about same collector current  $i_{c1} \approx i_{c2}$  and same  $g_m, r_e, r_{\pi}$ .

## Cascode Small Signal Analysis cont.

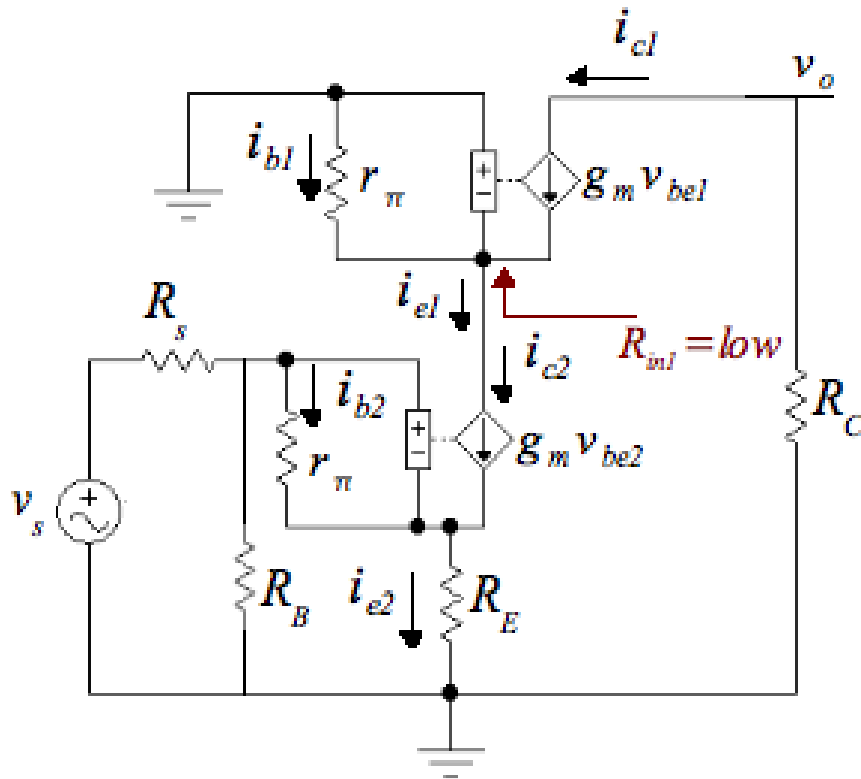

The input resistance  $R_{in1}$  to the CB stage is the small-signal “ $R_C$ ” for the CE stage

$$i_{b1} = \frac{i_{e1}}{\beta + 1} = \frac{i_{c2}}{\beta + 1}$$

The CE output voltage, the voltage drop from Q2 collector to ground, is:


$$v_{cg2} = v_{eg1} = -r_{\pi 1} i_{b1} = -\frac{r_{\pi 1}}{\beta + 1} i_{c2} = -\frac{r_{\pi 1}}{\beta + 1} i_{e1}$$

Therefore, the CB Stage input resistance is:

$$R_{in1} = \frac{v_{eg1}}{-i_{e1}} = \frac{r_{\pi 1}}{\beta + 1} = r_{e1}$$

$$A_{vCE-Stage} = \frac{v_{cg2}}{v_{sig}} \approx -\frac{R_{in1}}{R_E} = -\frac{r_e}{R_E} < 1 \Rightarrow C_{eq} = \left(1 + \frac{r_e}{R_E}\right) C_{\mu} < 2 C_{\mu}$$

## Cascode Small Signal Analysis - cont.

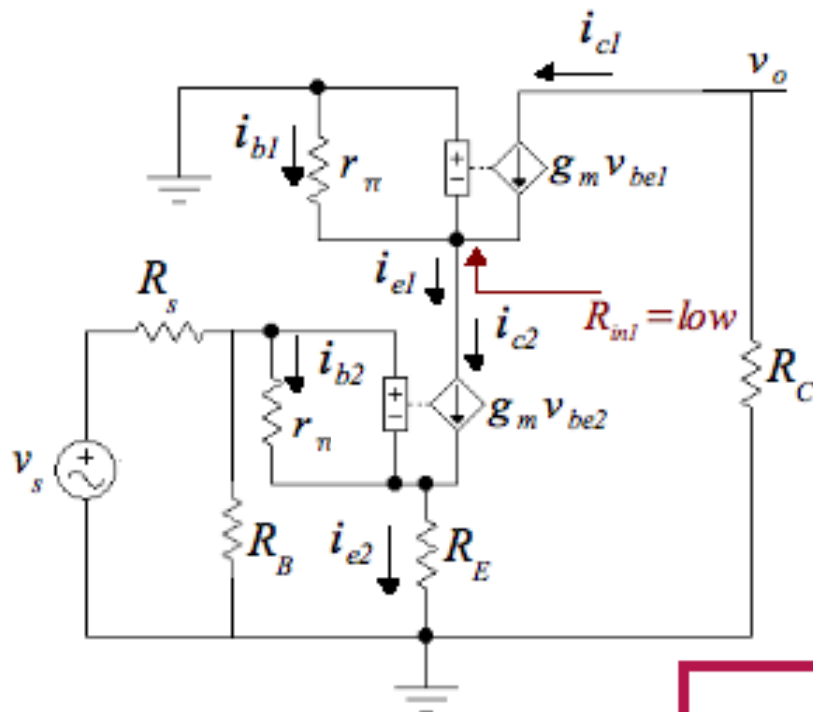

Now, find the CE collector current in terms of the input voltage  $v_s$ : **Recall**  $i_{c1} \approx i_{c2}$

$$i_{b2} \approx \frac{v_s}{R_s \parallel R_B + r_{\pi 2} + (\beta + 1) R_E}$$

$$i_{c2} = \beta i_{b2} \approx \frac{\beta v_s}{R_s \parallel R_B + r_{\pi 2} + (\beta + 1) R_E} \approx \frac{\beta v_s}{(\beta + 1) R_E}$$

for bias insensitivity:  $(\beta + 1) R_E \gg R_s \parallel R_B + r_{\pi}$

$$i_{c2} \approx \frac{v_s}{R_E}$$

$$v_o = -i_{c2} R_C$$

$$\Rightarrow A_v = \frac{V_{out}}{V_{sig}} = -\frac{R_C}{R_E}$$

### OBSERVATIONS:

1. Voltage gain  $A_v$  is about the same as a stand-alone CE Amplifier.
2. HF cutoff is much higher than a CE Amplifier due to the reduced  $C_{eq}$ .


## Approximate Cascode HF Voltage Gain

$$A_v(f) = \frac{V_o(f)}{V_s(f)} \approx \frac{-\frac{R_C}{R_E}}{1 + j2\pi f C_{in} R'_s}$$

where

$$C_{in} = C_{\pi} + C_{eq} = C_{\pi} + \left(1 + \frac{r_e}{R_E}\right) C_{\mu} < C_{\pi} + 2C_{\mu}$$
$$R'_s = R_s \parallel R_B \approx R_s$$

## Cascode Biasing

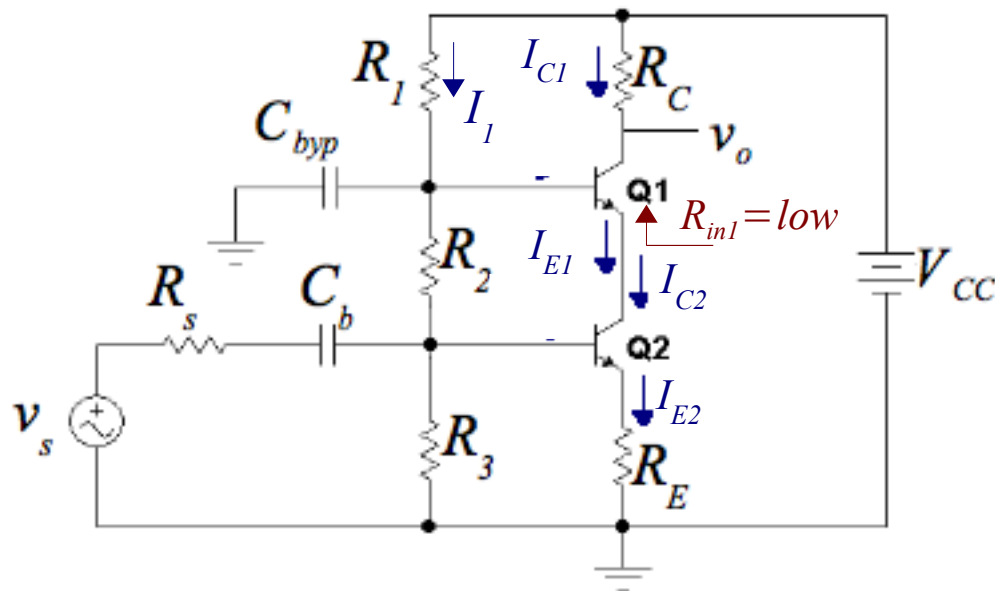

1. Choose  $I_{E1}$  – make it relatively large to reduce  $R_{in1} = r_{e1} = V_T / I_{E1}$  to push out HF break frequencies.

2. Choose  $R_C$  for suitable voltage swing  $V_{C1G}$  and  $R_E$  for desired gain.

3. Choose bias resistor string such that its current  $I_1$  is about 0.1 of the collector current  $I_{C1}$ .

4. Given  $R_E$ ,  $I_{E2}$  and  $V_{BE2} = 0.7 V$  calculate  $R_3$ .

## Cascode Biasing - cont.


- Since the CE-Stage gain is very small:
- The collector swing of Q2 will be small.
  - The Q2 collector bias  $V_{C2} = V_{B1} - 0.7 V$ .
5. Set  $V_{B1} - V_{B2} \approx 1 V \Rightarrow V_{CE2} \approx 1 V$

This will limit  $V_{CB2} = V_{CE2} - V_{BE2} = 0.3 V$  which will keep Q2 forward active.

6. Next determine  $R_2$ . Its drop  $V_{R2} = 1 V$  with the known current.

$$R_2 = \frac{V_{B1} - V_{B2}}{I_1}$$


7. Then calculate  $R_1$ .
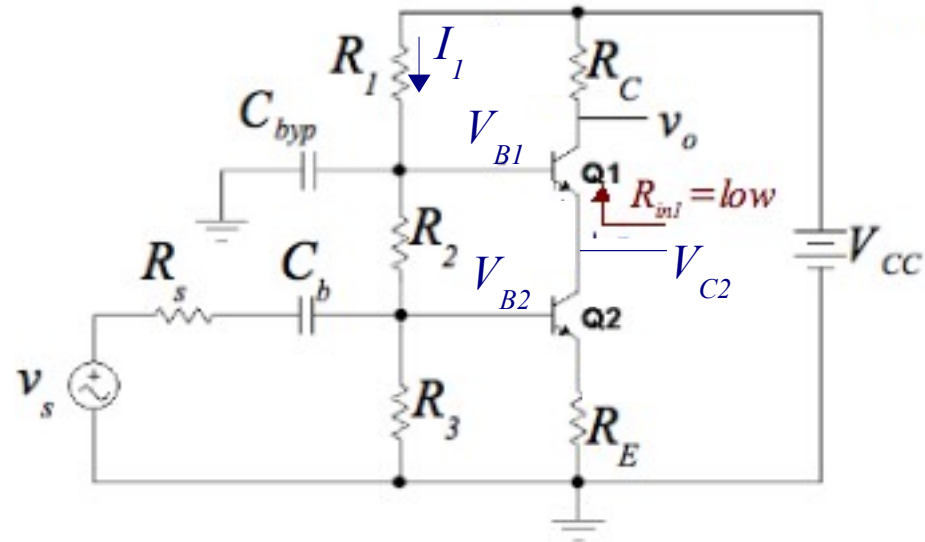
$$R_1 = \frac{V_{CC} - V_{B1}}{I_1}$$


$$\begin{aligned} V_{CE2} &= V_{C2} - V_{Re} = V_{C2} - (V_{B2} - 0.7 V) \\ &= V_{B1} - V_{BE1} - V_{B2} + V_{BE2} \\ &\approx V_{B1} - 0.7 V - V_{B2} + 0.7 V \\ &= V_{B1} - V_{B2} \end{aligned}$$




## Cascode Bias Example cont.

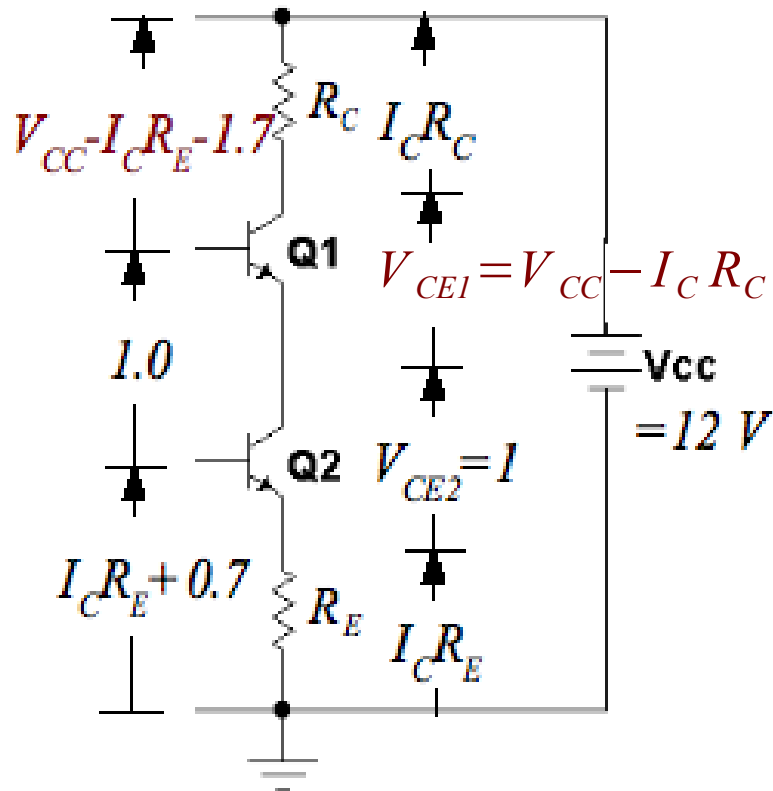

1. Choose  $I_{E1}$  – make it a bit high to lower  $r_e$  or  $r_\pi$ . Try  $I_{E1} = 5 \text{ mA} \Rightarrow r_e = 0.025 \text{ V} / I_E = 5 \Omega$ .
2. Set desired gain magnitude. For example if  $A_V = -10$ , then  $R_C / R_E = 10$ .
3. Since the CE stage gain is very small,  $V_{CE2}$  can be small. Use  $V_{CE2} = V_{B1} - V_{B2} = 1 \text{ V}$ .

## Cascode Bias Example cont.

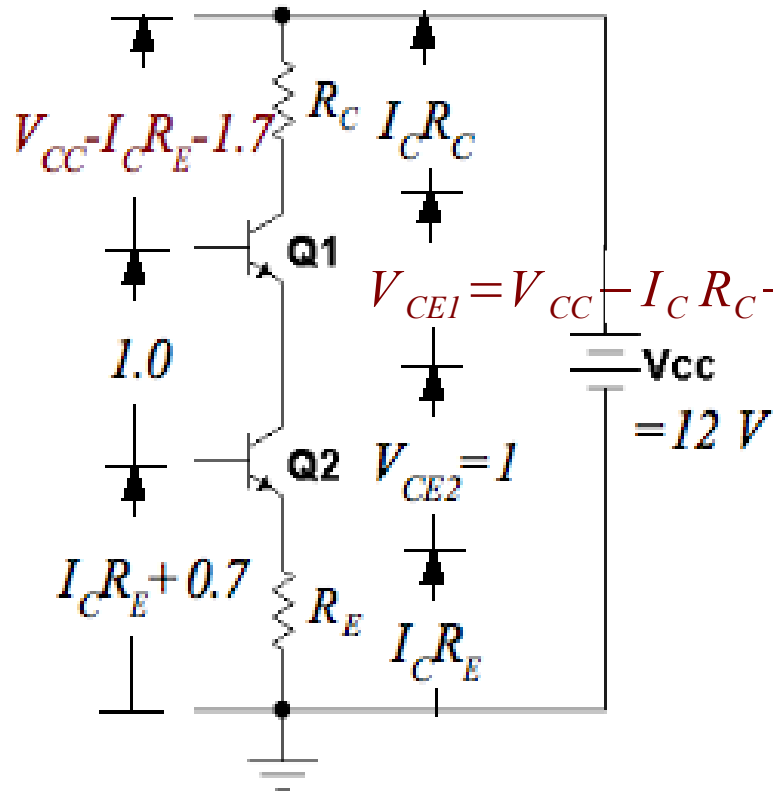


$$V_{CC} = 12 \quad I_C = 5 \text{ mA} \quad |A_v| = \frac{R_C}{R_E} = 10$$

Determine  $R_C$  for a 5 V drop across  $R_C$ .

$$R_C = \frac{5 \text{ V}}{5 \cdot 10^{-3} \text{ A}} = 1000 \Omega$$

$$R_E = \frac{R_C}{|A_v|} = \frac{R_C}{10} = 100 \Omega$$

## Cascode Bias Example cont.

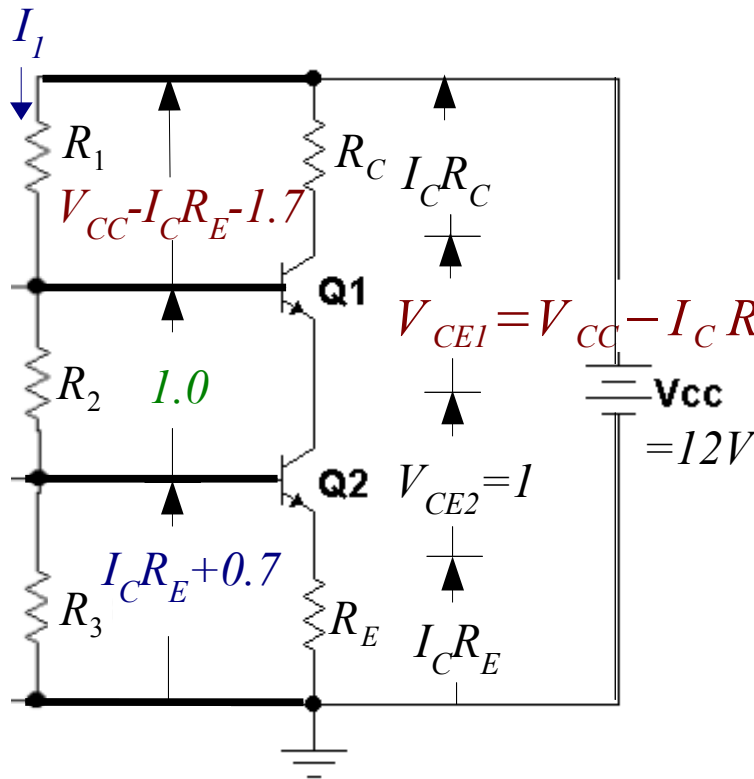

$$V_{CC} = 12 \quad R_C = 1k\Omega \quad I_C = 5mA. \quad R_E = 100\Omega$$

Make current through the string of bias resistors  $I_1 = 1mA$ .

$$R_1 + R_2 + R_3 = \frac{V_{CC}}{I_1} = \frac{12}{1 \cdot 10^{-3}} = 12k\Omega$$


We now calculate the bias voltages:

$$V_{CC} - I_C R_E - 1.7V = 12V - 0.5V - 1.7V = 9.8V$$

$$V_{B1B2} = V_{B1} - V_{B2} = 1.0V$$

$$V_{B2} = I_C R_E + 0.7 = 5 \cdot 10^{-3} \cdot 100 + 0.7 = 1.2V$$

## Cascode Bias Example cont.

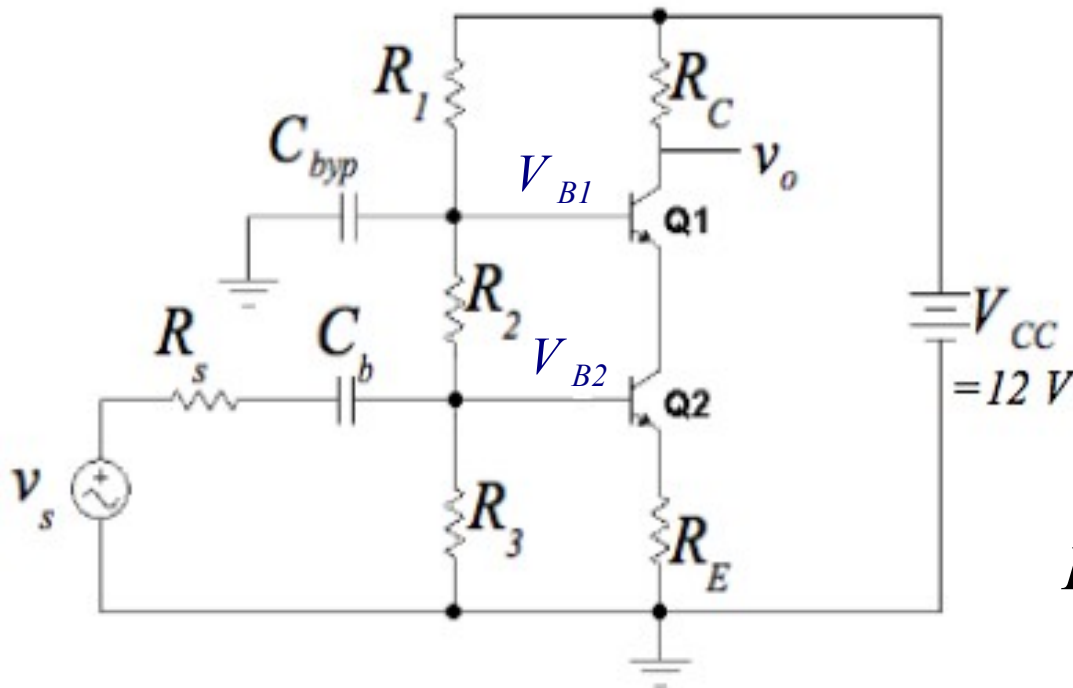

$$V_{B2} = 10^{-3} R_3 = 1.2 V$$

$$R_3 = 1.2 k \Omega$$

$$V_{B1} - V_{B2} = 1 \cdot 10^{-3} R_2 = 1.0 V$$

$$R_2 = 1 k \Omega$$


$$R_1 = 12000 - 1200 - 1000 = 9.8 k \Omega$$

$$R_1 = 10 k \Omega$$

$$V_{CC} = 12 \quad R_C = 1 k \Omega \quad V_{B2} = 1.2 V$$

$$I_C = 5 mA. \quad R_E = 100 \Omega \quad V_{B1} - V_{B2} = 1.0 V$$

## Multisim Results – Bias Example

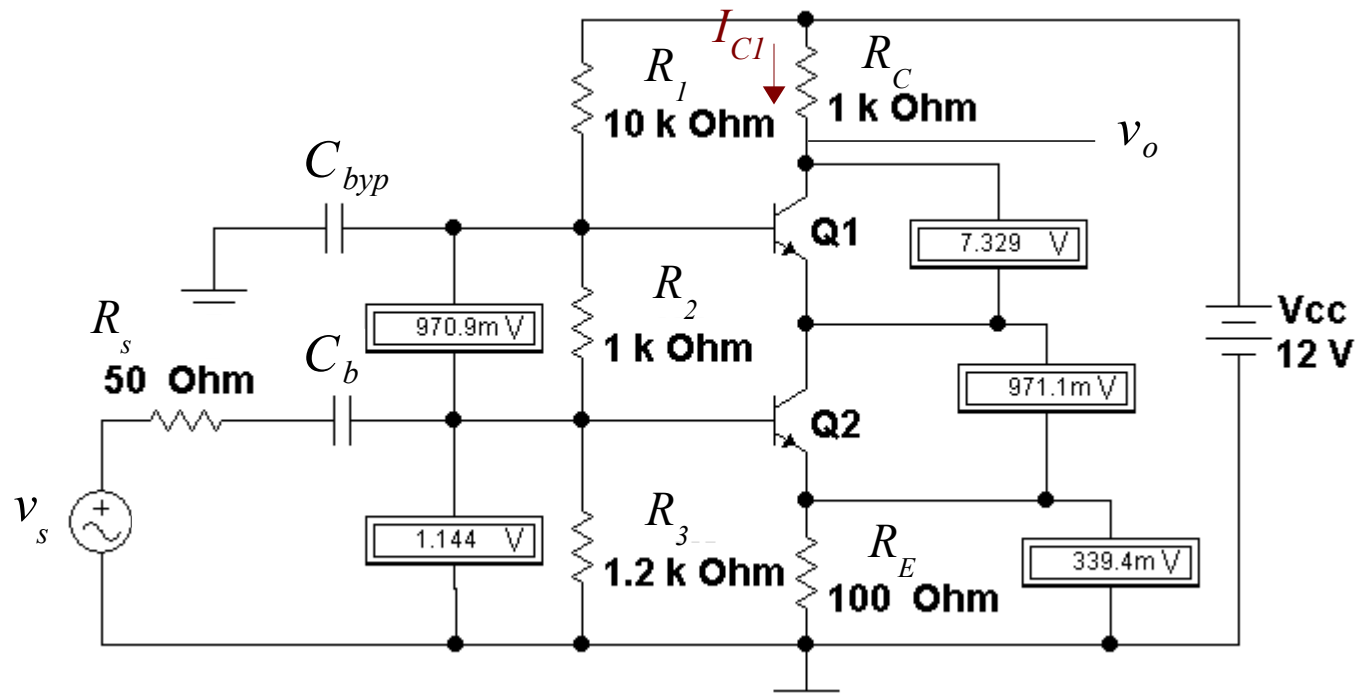


Check  $I_{C1}$ : 
$$I_{C1} = \frac{V_{CC} - (7.329 + 0.971 + 0.339)}{R_C} = \frac{12V - 8.639V}{1000\Omega} = 3.36mA$$

$I_{C1}$  about 3.4 mA. That's a little low.

Increase  $R_3$  to 1.5 k Ohms and re-simulate.


## Improved Biasing

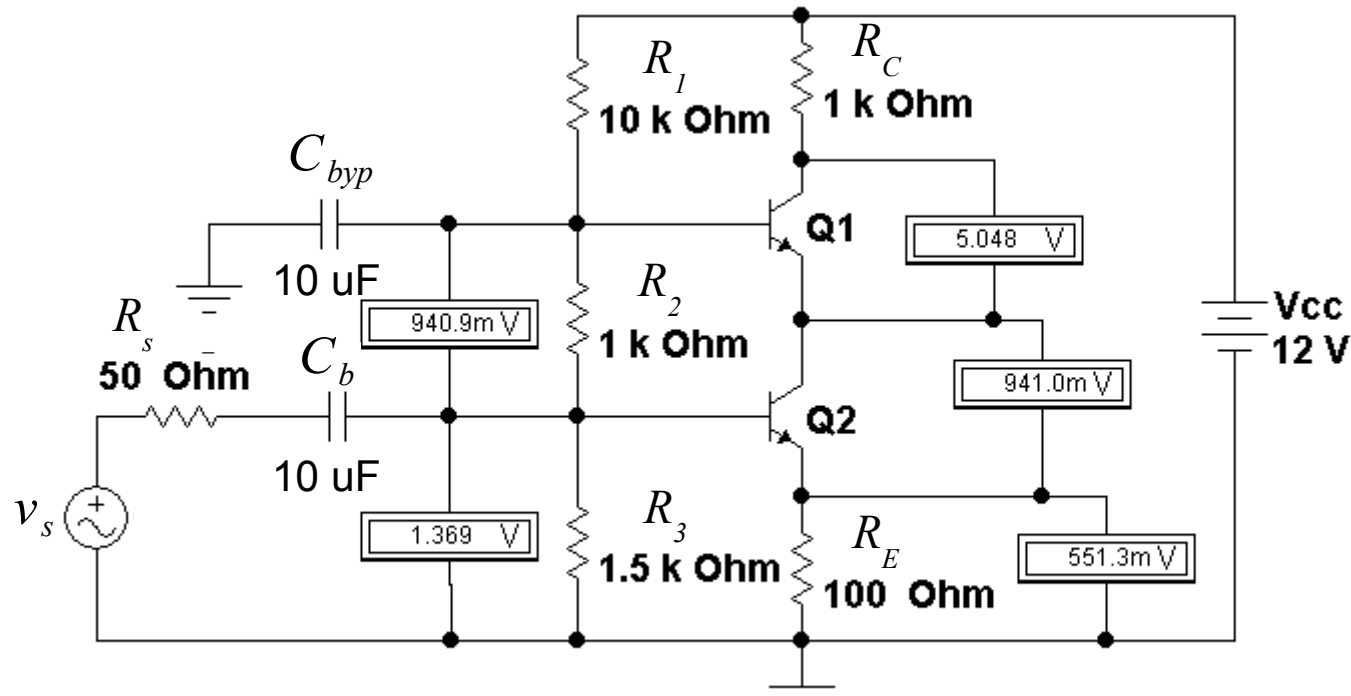

$$\text{Check } I_{C1}: I_{C1} = \frac{V_{CC} - (5.048 + 0.941 + 0.551)}{R_C} = \frac{12\text{ V} - 6.540\text{ V}}{1000\ \Omega} = 5.46\text{ mA}$$


That's better! Now measure the gain at a mid-band frequency with some “large” coupling capacitors, say  $10\ \mu\text{F}$  inserted.

## Single Frequency Gain

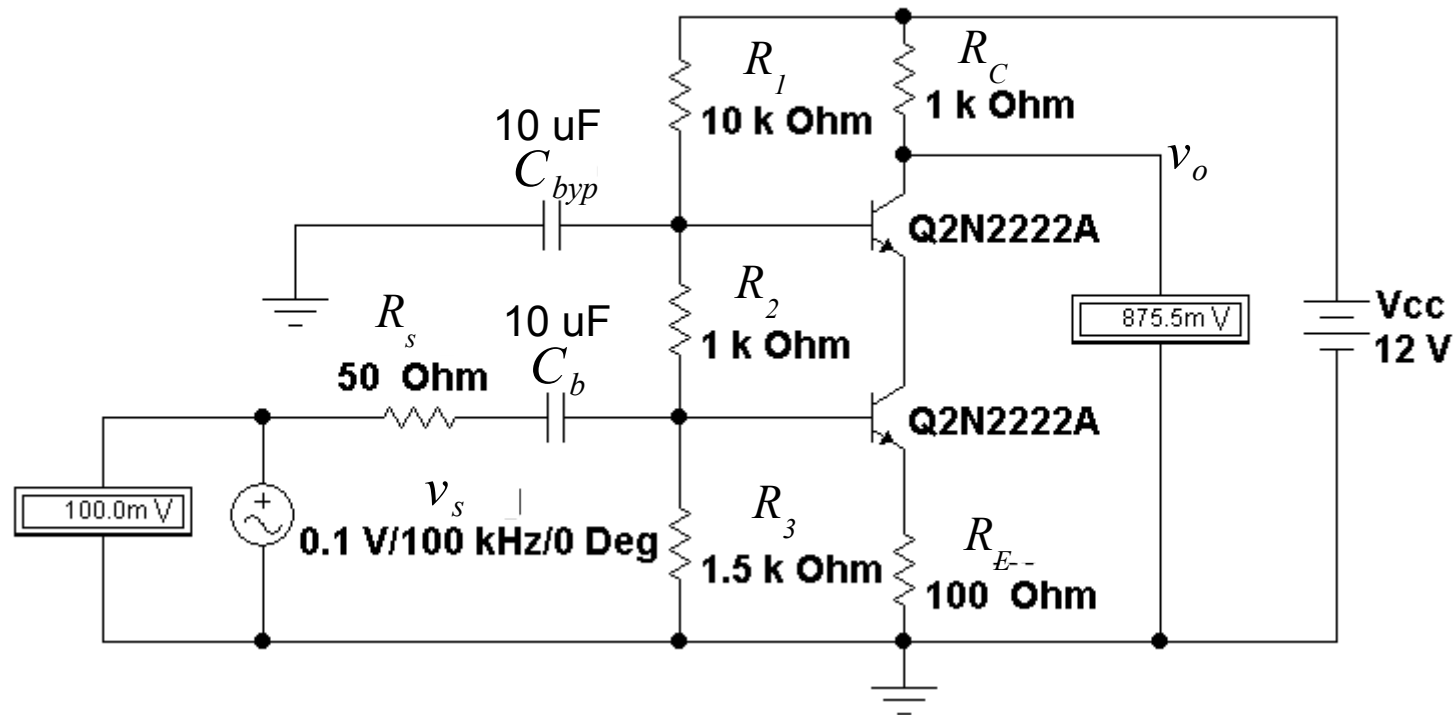


Gain  $|A_v|$  of about 8.75 at 100 kHz - OK for rough calculations. Some attenuation from low CB input impedance ( $R_B = R_2 || R_3$ ) and some from  $5\Omega r_e$ .

## *Bode Plot for the Amplifier*

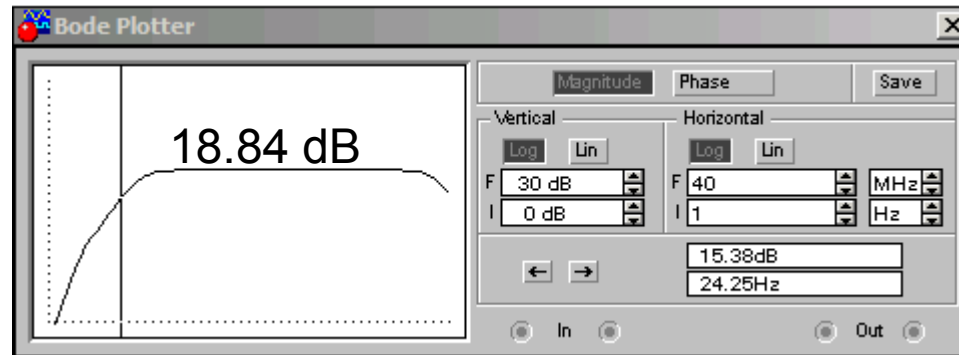


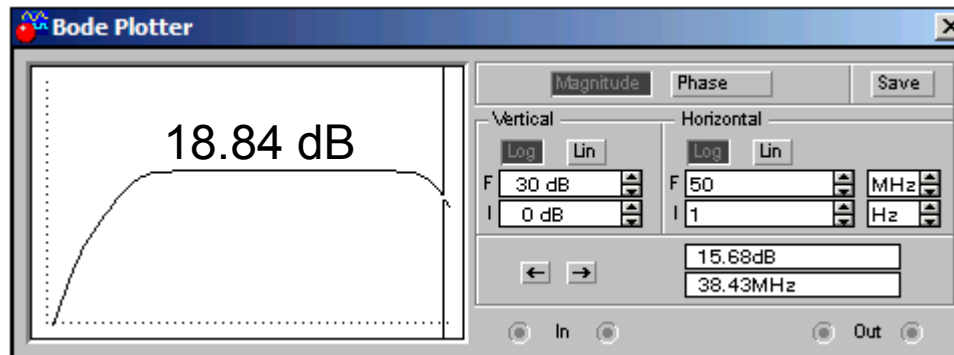Low frequency break point with 10  $\mu$ F. capacitors




High frequency break point – internal capacitances only

## Scope Plot – Near 5 V Swing on Output

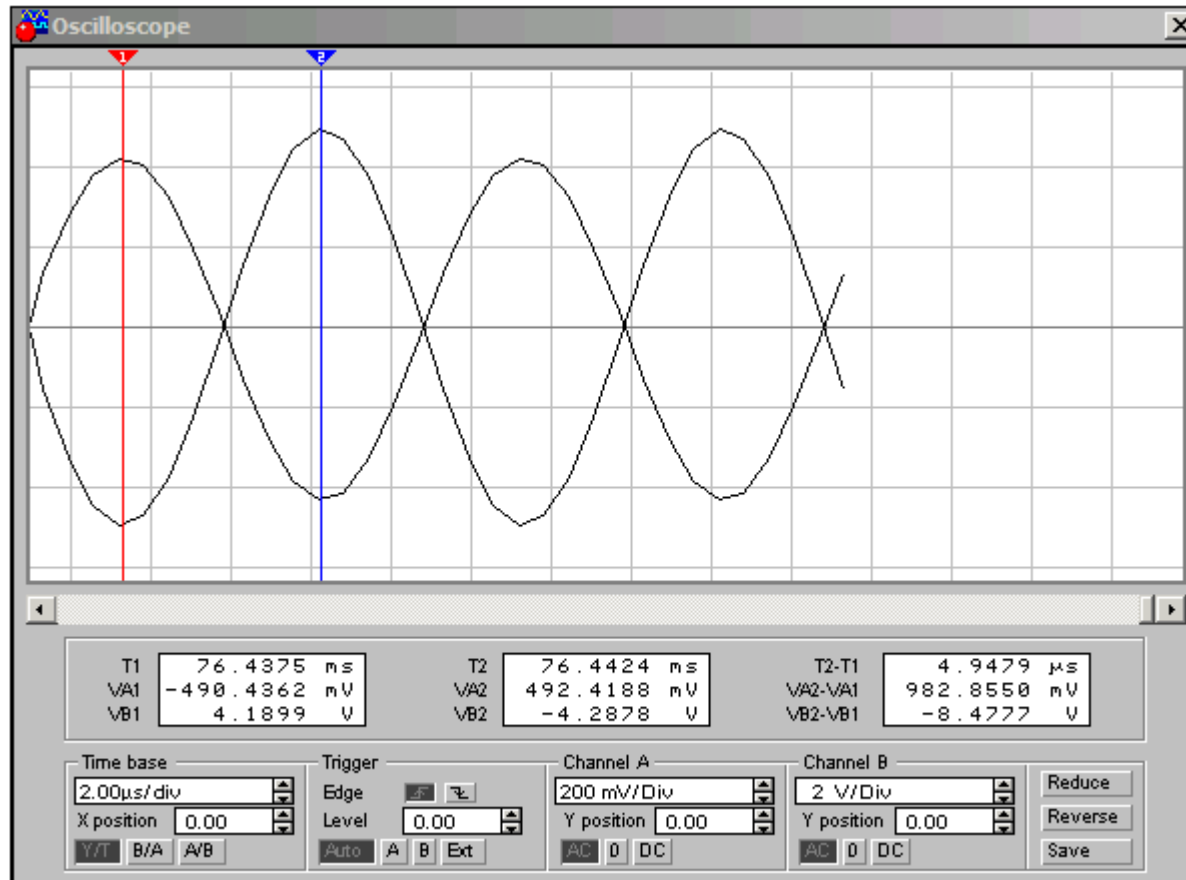

## Determine Bypass Capacitors

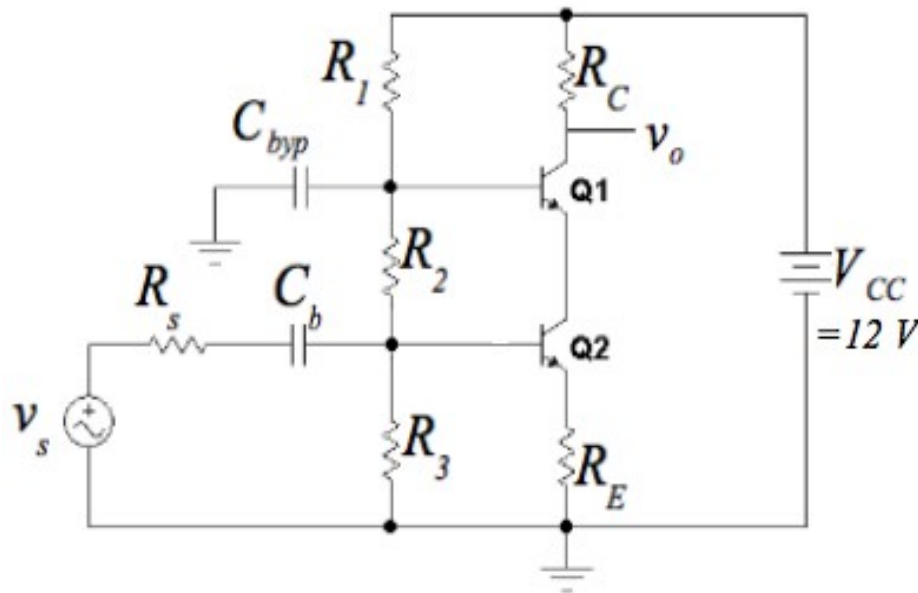

Low Frequency  $f \leq f_{min}$

From CE stage determine  $C_b$

$$C_b \geq \frac{10}{2\pi f_{min} R_B \parallel r_{bg}} \approx \frac{10}{2\pi f_{min} R_B \parallel (\beta + 1) R_E} F$$

$$R_B = R_2 \parallel R_3$$

From CB stage determine  $C_{byp}$

$$C_{byp} \geq \frac{10}{2\pi f_{min} ((\beta + 1) R_E + r_{\pi})} F$$

where  $R_S \rightarrow R_E$