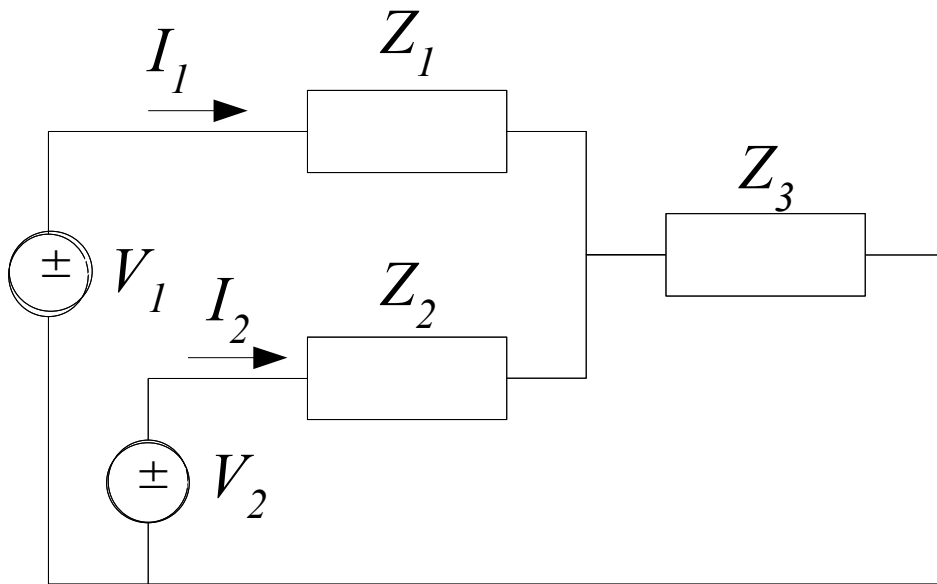


# *Differential Amplifier Common & Differential Modes*

- Common & Differential Modes
- BJT Differential Amplifier
- Diff. Amp Voltage Gain and Input Impedance
- Small Signal Analysis – Differential Mode
- Small Signal Analysis – Common Mode

## Common and Differential Modes

Consider a circuit with the *two-port* configuration shown



Define (convention) the voltages:


$$V_c = \frac{V_1 + V_2}{2} \quad V_d = V_1 - V_2$$

$V_c$  = “common mode voltage”

$V_d$  = “differential mode voltage”

1. Let  $V_1 = V_2 = V \Rightarrow V_c = V$  &  $V_d = 0$
2. Let  $V_1 = -V_2 = V \Rightarrow V_c = 0$  &  $V_d = 2V$
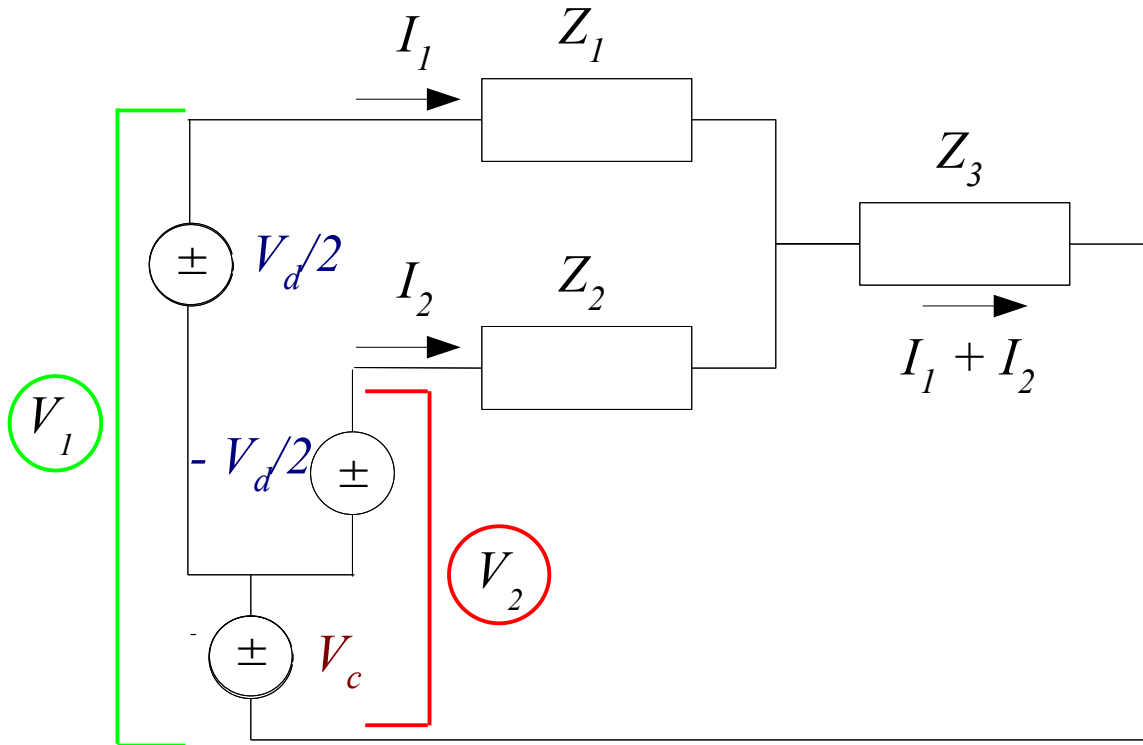
## Replace $V_1$ , $V_2$ with CM and DM Sources



Simultaneous Equations:

$$V_1 + V_2 = 2V_c$$

$$V_1 - V_2 = V_d$$

Adding:  $2V_1 = 2V_c + V_d$


$$V_1 = V_c + V_d/2$$

Subtracting:  $2V_2 = 2V_c - V_d$

$$V_2 = V_c - V_d/2$$

Definition  $V_c = \frac{V_1 + V_2}{2}$      $V_d = V_1 - V_2$

## Common and Differential Mode Currents

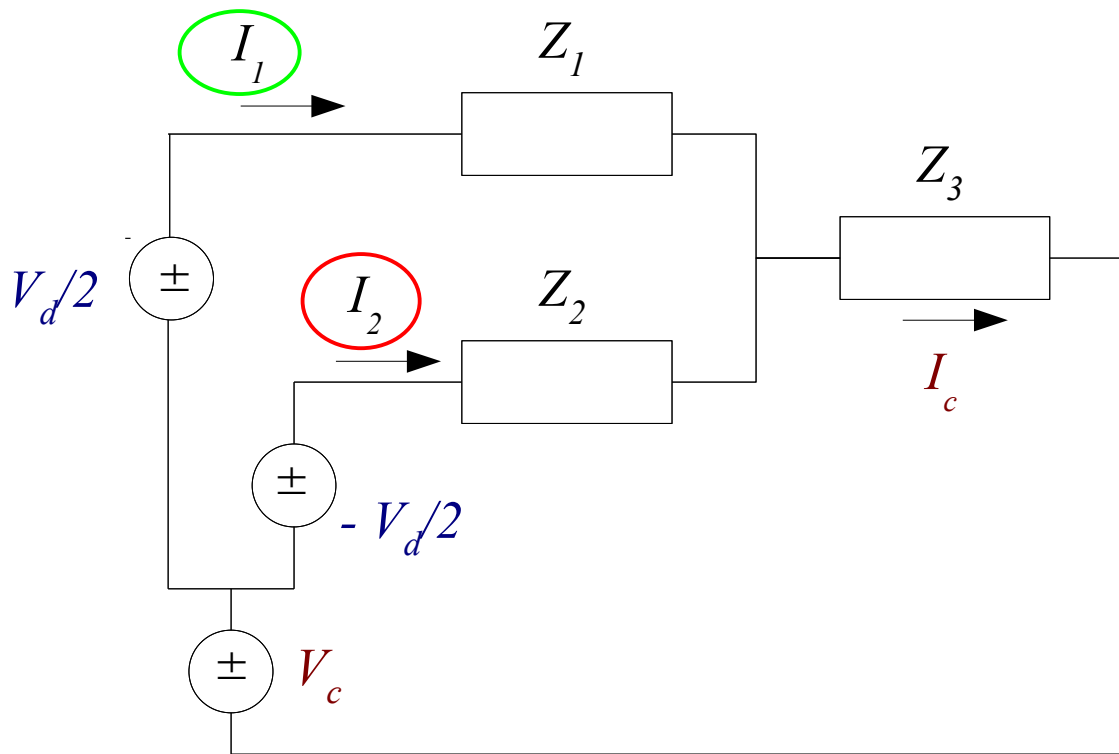

Define (convention):  $I_c = I_1 + I_2$   $I_d = \frac{I_1 - I_2}{2}$

Simultaneous Equations:

$$I_1 + I_2 = I_c$$

$$I_1 - I_2 = 2I_d$$

Adding:

$$2I_1 = I_c + 2I_d$$


$$I_1 = I_c/2 + I_d$$

Subtracting:

$$2I_2 = I_c - 2I_d$$

$$I_2 = I_c/2 - I_d$$

## CM-DM Circuit Description

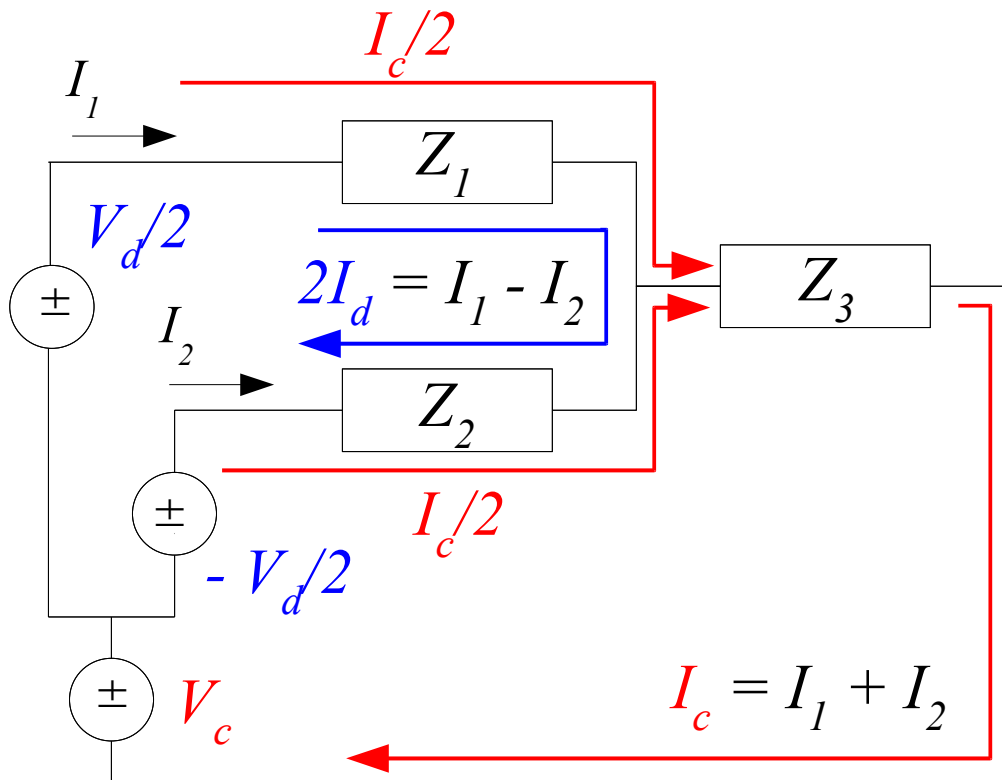


1. Voltage sources redefined as common and differential mode quantities.
2. Differential mode currents take “blue” path.
3. Common mode current takes “red” path.

$$I_1 = I_c/2 + I_d \quad I_2 = I_c/2 - I_d$$


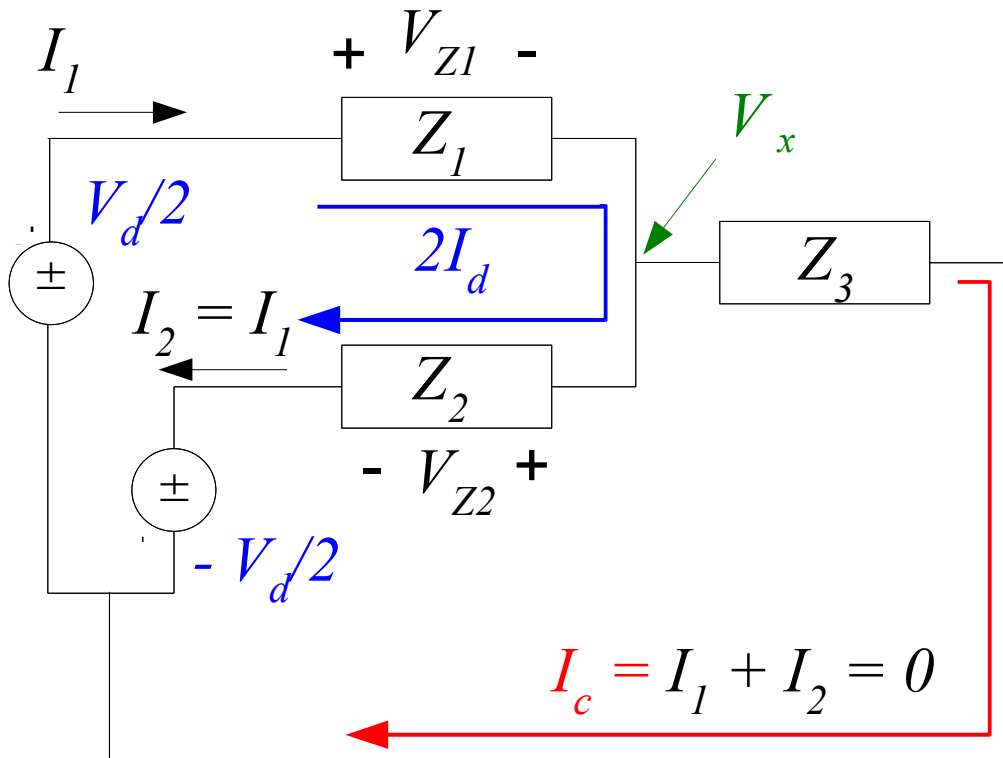
# Analyze Circuits by Superposition Balanced Circuit Differential Mode ( $V_C = 0$ )



$$I_c = I_1 + I_2 = I_d - I_d = 0$$

$$I_c = I_1 + I_2 = \frac{\frac{V_d}{2} - V_x}{Z_1} + \frac{-\frac{V_d}{2} - V_x}{Z_2} = \frac{-2V_x}{Z} = 0$$

$$I_c = 0 \Rightarrow V_x = 0$$

$$2I_d = \frac{\frac{V_d}{2} - (-\frac{V_d}{2})}{Z_1 + Z_2} = \frac{V_d}{2Z}$$


$$Z_{in-dm} = \frac{V_d}{2I_d} = 2Z$$

balanced circuit  $\Rightarrow Z_1 = Z_2 = Z$

NOTE: If  $Z_2 = Z_1 + \delta Z$ , then  $I_c \neq 0 \Rightarrow V_x \neq 0$ .


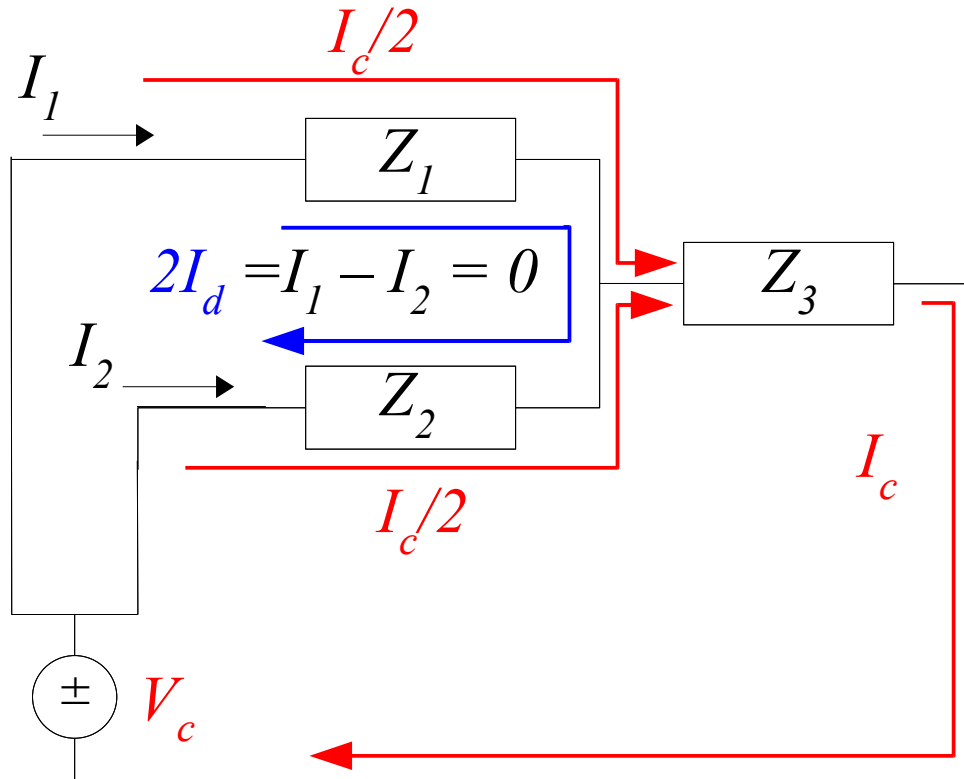
# Analyze Circuits by Superposition Balanced Circuit Common Mode ( $V_d = 0$ )



$$I_c = \frac{V_c}{Z_1 || Z_2 + Z_3} = \frac{V_c}{\frac{Z}{2} + Z_3}$$

$$2I_d = I_1 - I_2 = \frac{I_c}{2} - \frac{I_c}{2} = 0 \Rightarrow I_d = 0$$

$$Z_{in-cm} = \frac{V_c}{I_c} = \frac{Z}{2} + Z_3$$

balanced circuit  $\Rightarrow Z_1 = Z_2 = Z$

## Summary

In a **balanced differential circuit** ( $Z_1 = Z_2 = Z$ ):

1. Differential mode voltages result in differential mode currents.
2. Common mode voltages result in common mode currents.


The *differential mode input impedance* of a balanced circuit is:

$$Z_{in-dm} = 2Z$$

The *common mode input impedance* of a balanced circuit is:

$$Z_{in-cm} = \frac{Z}{2} + Z_3$$
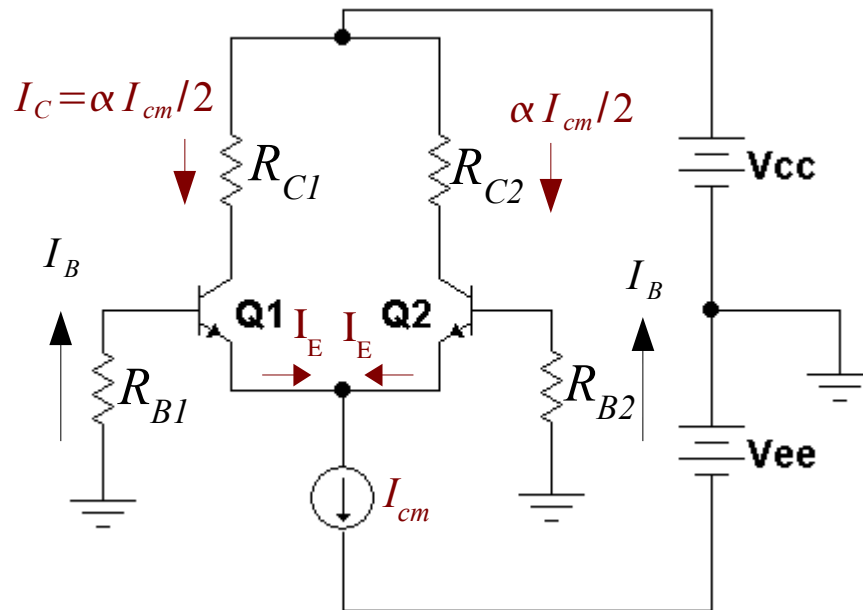
## BJT Differential Amplifier – Bias View



$$Q1 = Q2$$

$$R_{C1} = R_{C2} = R_C$$

$$R_{B1} = R_{B2} = R_B$$

balanced  
circuit


Collector bias path inherently common mode.

Choose  $I_{cm}$  and  $R_C$  for approximate  $\frac{1}{2} V_{CC}$  drop across  $R_C$ .

$$I_E = \frac{I_{cm}}{2}$$

$$I_B = \frac{I_{cm}}{2(\beta + 1)} \quad I_C = \alpha \frac{I_{cm}}{2} \approx \frac{I_{cm}}{2}$$


## Voltage Gain & Input Impedance

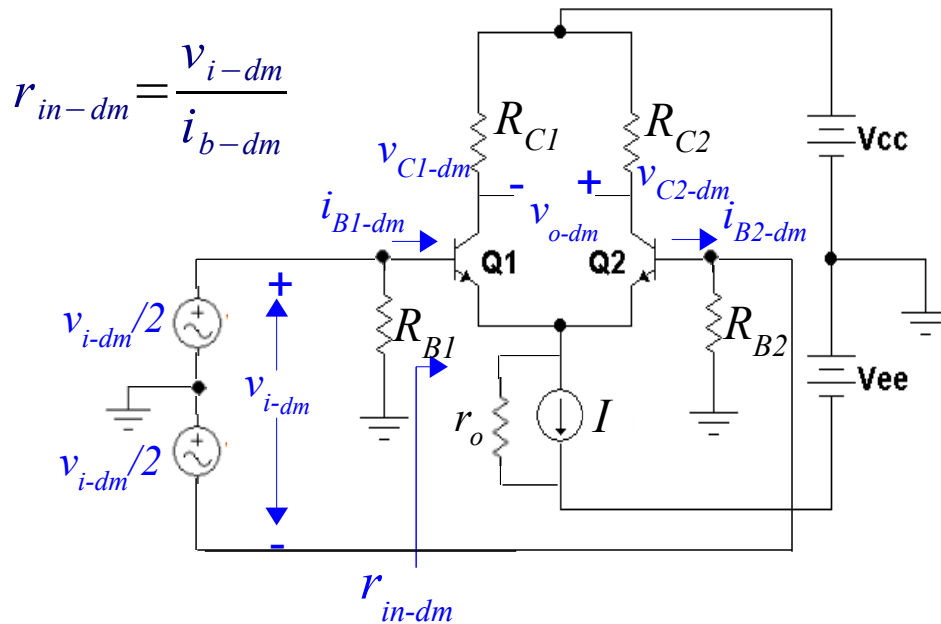

Single-ended outputs:  $v_{c1-dm}$ ,  $v_{c2-dm}$

Differential output:  $v_{o-dm} = v_{c2-dm} - v_{c1-dm}$
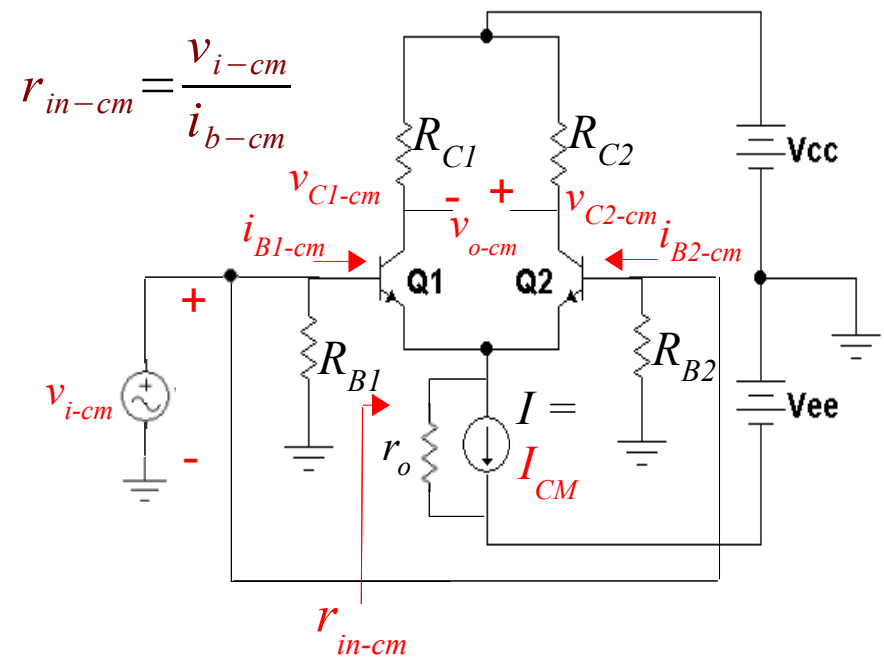
$$\begin{aligned} \text{(diff)} \quad A_{v-dm} &= \frac{v_{o-dm}}{v_{i-dm}} & \text{(se)} \quad A_{v-dm1,2} &= \frac{v_{c1,2-dm}}{v_{i-dm}} \end{aligned}$$




Single-ended outputs:  $v_{c1-cm}$ ,  $v_{c2-cm}$

Differential output:  $v_{o-cm} = v_{c2-cm} - v_{c1-cm}$

$$\begin{aligned} \text{(diff)} \quad A_{v-cm} &= \frac{v_{o-cm}}{v_{i-cm}} & \text{(se)} \quad A_{v-cm1,2} &= \frac{v_{c1,2-cm}}{v_{i-cm}} \end{aligned}$$

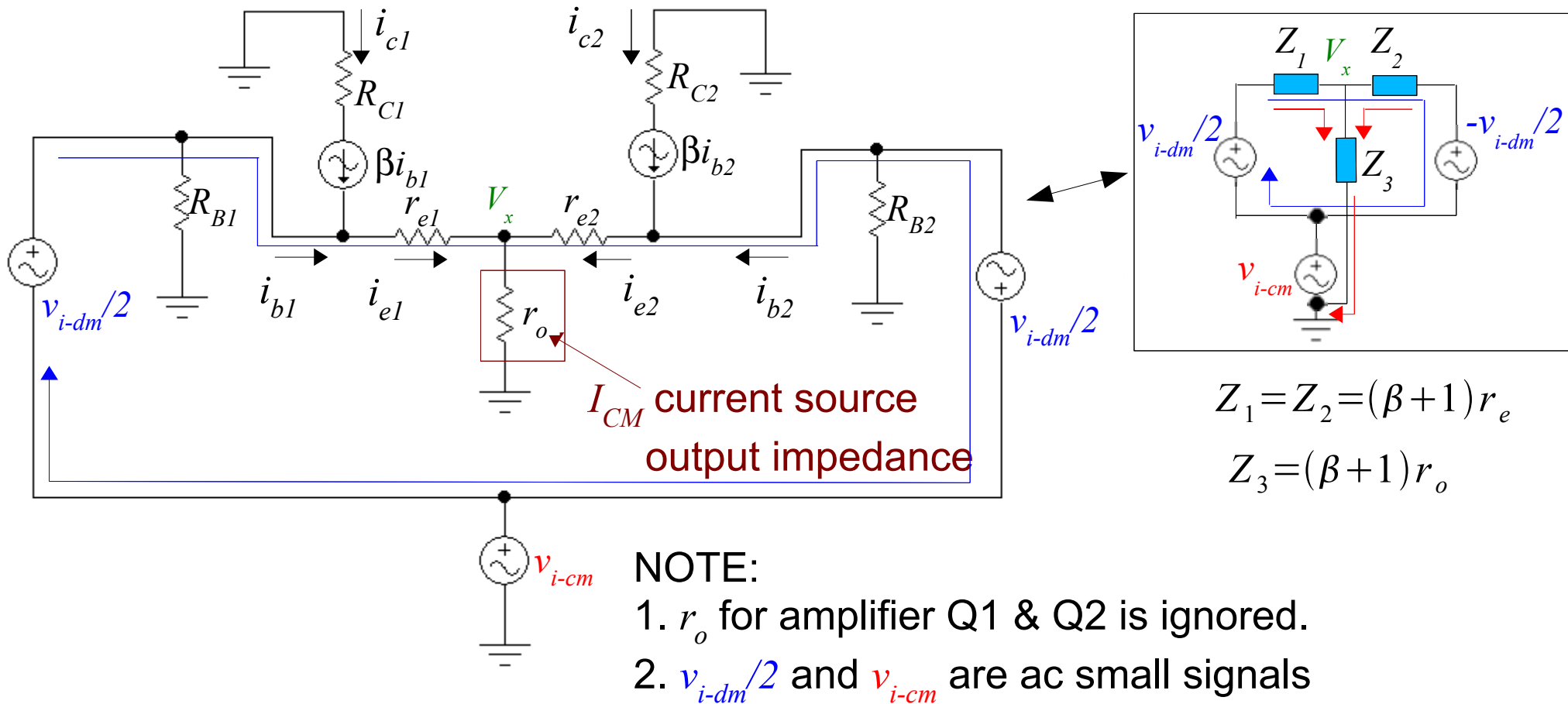
## BJT Differential Amplifier – Small-signal View


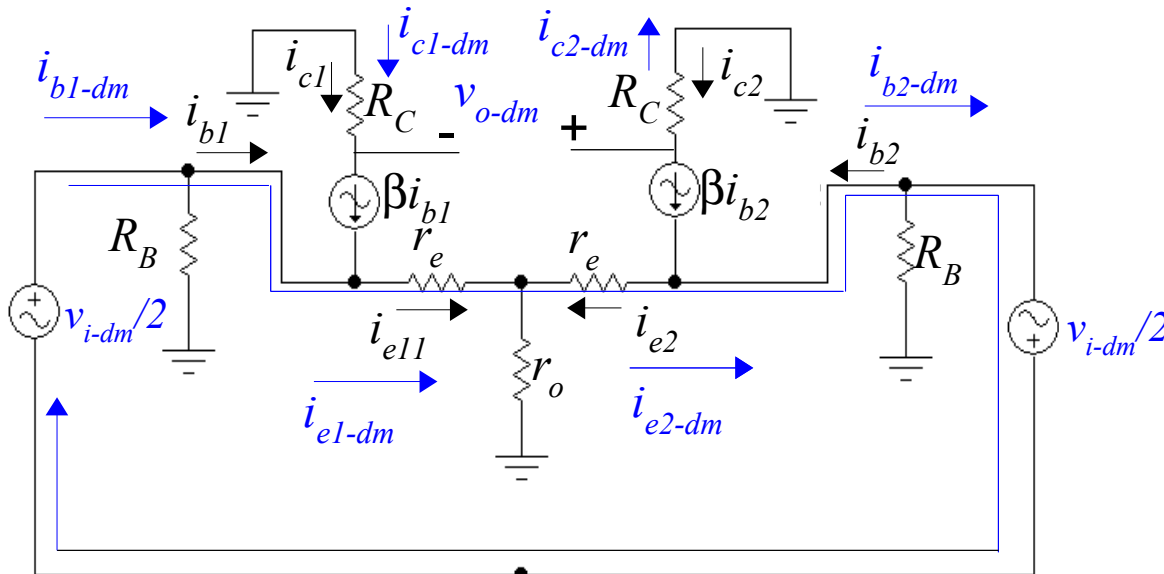
## Superposition Small-signal Analysis Differential Mode ( $v_{i-cm} = 0$ )

Balanced circuit  $\Rightarrow R_{C1} = R_{C2} = R_C, R_{B1} = R_{B2} = R_B, r_{e1} = r_{e2} = r_e, \beta_1 = \beta_2 = \beta$

$$\Rightarrow i_{e1} = i_{e2} = i_e, i_{b1} = i_{b2} = i_b, i_{c1} = i_{c2} = i_c$$



DM Path (ignoring both  $R_B$ ):

$$\frac{v_{i-dm}}{2} = i_{e-dm} r_e + i_{e-dm} r_e - \frac{v_{i-dm}}{2}$$

$$v_{i-dm} = 2 r_e i_{e-dm} = 2(\beta + 1) r_e i_{b-dm}$$

$$= r_{in-dm} i_{b-dm}$$

$$r_{in-dm} = 2(\beta + 1) r_e$$

Recall:  $Z_{in-dm} = 2Z$

$$Z_1 = Z_2 = (\beta + 1) r_e$$

$$Z_3 = (\beta + 1) r_o$$

$$i_{e1-dm} = i_{e-dm} = i_{e1} = i_e$$

$$i_{e2-dm} = i_{e-dm} = -i_{e2} = -i_e$$

$$i_{b1-dm} = i_{b-dm} = i_{b1} = i_b$$

$$i_{b2-dm} = i_{b-dm} = -i_{b2} = -i_b$$


$$i_{c1-dm} = i_{c-dm} = i_{c1} = i_c$$

$$i_{c2-dm} = i_{c-dm} = -i_{c2} = -i_c$$



# Superposition Small-signal Analysis Differential Mode ( $v_{i-cm} = 0$ ) cont.

Balanced circuit

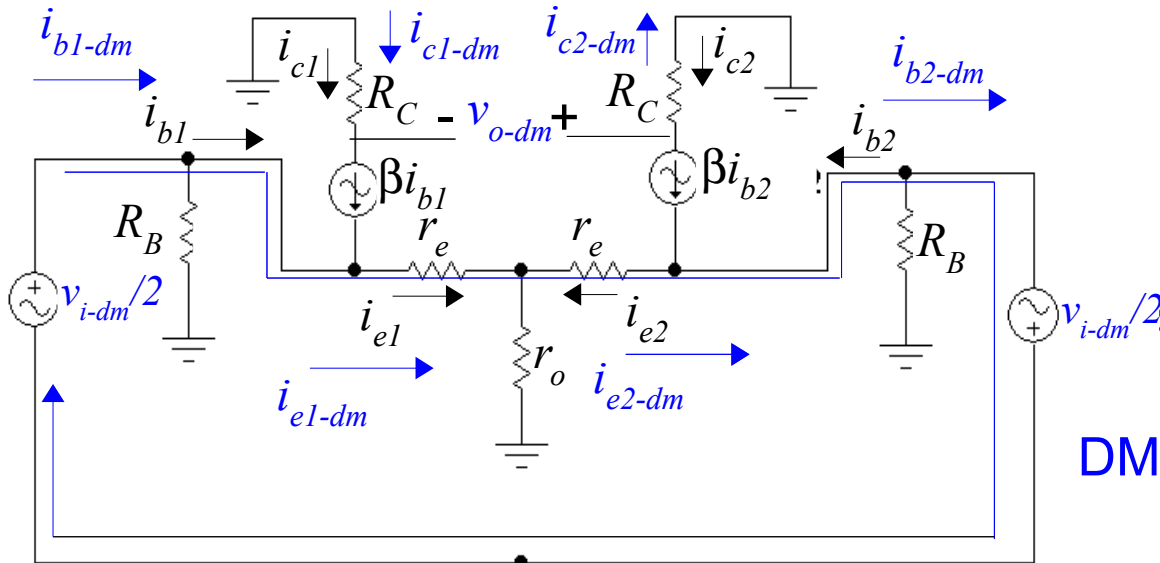

$$i_{e1-dm} = i_{e-dm} = i_{e1} = i_e$$

$$i_{e2-dm} = i_{e-dm} = -i_{e2} = -i_e$$

$$i_{b1-dm} = i_{b-dm} = i_{b1} = i_b$$

$$i_{b2-dm} = i_{b-dm} = -i_{b2} = -i_b$$

$$i_{c1-dm} = i_{c-dm} = i_{c1} = i_c$$

$$i_{c2-dm} = i_{c-dm} = -i_{c2} = -i_c$$

$$i_{c-dm} = \beta i_{b-dm}$$

$$v_{o-dm} = v_{c2-dm} - v_{c1-dm}$$

$$v_{o-dm} = \underbrace{-R_C \beta (-i_{b-dm})}_{v_{c2-dm}} - \underbrace{(-R_C \beta i_{b-dm})}_{v_{c1-dm}}$$

$$i_{b-dm} = \frac{v_{i-dm}}{2(\beta+1)r_e}$$

$$v_{o-dm} = 2 \frac{R_C \beta}{2(\beta+1)r_e} v_{i-dm}$$

DM Differential voltage gain:

$$A_{v-dm} = \frac{v_{o-dm}}{v_{i-dm}} = \frac{R_C \beta}{(\beta+1)r_e} \approx \frac{R_C}{r_e}$$


DM Single-ended voltage gains:

$$A_{v-dm2} = -A_{v-dm1} = \frac{v_{c2-dm}}{v_{i-dm}} = \frac{\beta R_C}{2(\beta+1)r_e} \approx \frac{R_C}{2r_e}$$



# Superposition Small-signal Analysis Common Mode ( $v_{i-dm} = 0$ )

Balanced circuit

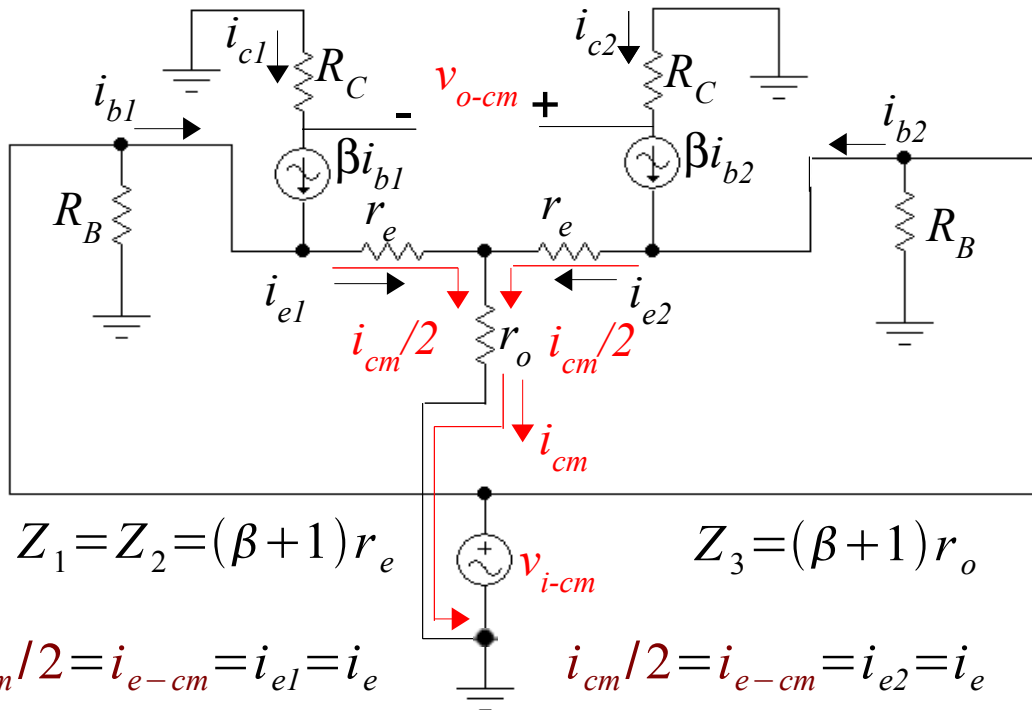

$$Z_1 = Z_2 = (\beta + 1)r_e$$

$$Z_3 = (\beta + 1)r_o$$

$$i_{cm}/2 = i_{e-cm} = i_{e1} = i_e$$

$$i_{cm}/2 = i_{e-cm} = i_{e2} = i_e$$

$$i_{b1-cm} = i_{b-cm} = i_{b1} = i_b$$

$$i_{b2-cm} = i_{b-cm} = i_{b2} = i_b$$

$$i_{c1-cm} = i_{c-cm} = i_{c1} = i_c$$

$$i_{c2-cm} = i_{c-cm} = i_{c2} = i_c$$

CM path: both  $r_e$  are in parallel

$$v_{i-cm} = [r_e \parallel r_e + r_o] i_{cm}$$

$$i_{cm} = \frac{v_{i-cm}}{\frac{r_e}{2} + r_o} \approx \frac{v_{i-cm}}{r_o}$$

$$i_{cm} = 2i_{e-cm} = (\beta + 1)2i_{b-cm}$$

$$v_{i-cm} = 2i_{b-cm}(\beta + 1)\left(\frac{r_e}{2} + r_o\right)$$


$$r_{in-cm} = \frac{v_{i-cm}}{2i_{b-cm}} = (\beta + 1)\left(\frac{r_e}{2} + r_o\right) \approx (\beta + 1)r_o$$

Recall:  $Z_{in-cm} = \frac{Z}{2} + Z_3$



# Superposition Small-signal Analysis Common Mode ( $v_{i-dm} = 0$ )

Balanced circuit

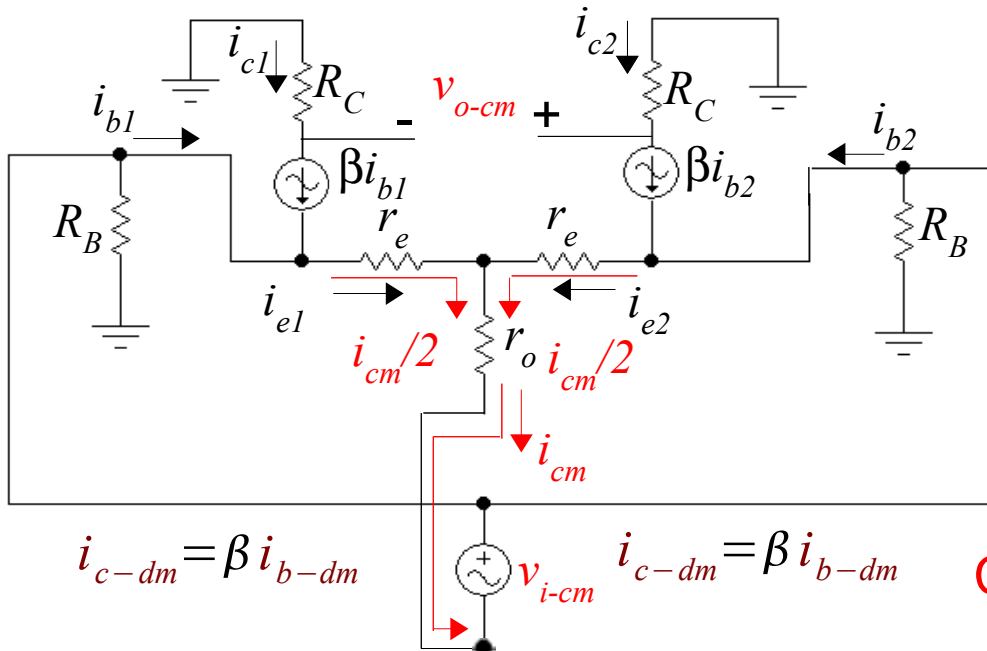

$$v_{o-cm} = v_{c2-cm} - v_{c1-cm}$$

$$v_{o-cm} = -R_C \beta i_{b-cm} - (-R_C \beta i_{b-cm}) = 0$$

$$i_{b-cm} = \frac{v_{i-cm}}{(\beta+1)(r_e + 2r_o)} \approx \frac{v_{i-cm}}{(\beta+1)2r_o}$$

$$v_{c2-cm} = v_{c1-cm} = -R_C \beta i_{b-cm} = \frac{-R_C \beta}{(\beta+1)2r_o} v_{i-cm}$$

CM Differential voltage gain:  $A_{v-cm} = \frac{v_{o-cm}}{v_{i-cm}} = 0$

CM Single-ended voltage gains:

$$A_{v-cm2} = A_{v-cm1} = \frac{v_{c1-cm}}{v_{i-cm}} = -\frac{R_C \beta}{(\beta+1)2r_o} \approx -\frac{R_C}{2r_o}$$

$$\begin{aligned} i_{cm}/2 &= i_{e-cm} = i_{e1} = i_e & i_{cm}/2 &= i_{e-cm} = i_{e2} = i_e \\ i_{b1-cm} &= i_{b-cm} = i_{b1} = i_b & i_{b2-cm} &= i_{b-cm} = i_{b2} = i_b \\ i_{c1-cm} &= i_{c-cm} = i_{c1} = i_c & i_{c2-cm} &= i_{c-cm} = i_{c2} = i_c \end{aligned}$$

## Summary

Differential mode:

$$r_{in-dm} = 2(\beta + 1)r_e$$

Differential DM Voltage gain:

$$A_{v-dm} = \frac{v_{o-dm}}{v_{i-dm}} \approx \frac{R_C}{r_e}$$

Single-Ended DM Voltage gain:

$$A_{v-dm1} = -A_{v-dm2} = \frac{v_{cl-dm}}{v_{i-dm}} \approx -\frac{R_C}{2r_e}$$

Common mode:

$$r_{in-cm} = (\beta + 1) \left( \frac{r_e}{2} + r_o \right) \approx (\beta + 1)r_o$$

Differential CM Voltage gain:

$$A_{v-cm} = \frac{v_{o-cm}}{v_{i-cm}} = 0$$

Single-Ended CM Voltage gain:

$$A_{v-cm1} = A_{v-cm2} = \frac{v_{cl-cm}}{v_{i-cm}} \approx -\frac{R_C}{2r_o}$$