



Differential Amplifier Design

- Design with ideal current source bias.
- Differential and common mode gain results
- Add finite output resistance to current source.
- Replace ideal current source with current mirror.

Quick Amplifier Design

By inspection DC bias ($v_{i-dm} = v_{i-cm} = 0$) for Q1 & Q2 is **common mode**:

$$I_E = \frac{I}{2} = 5 \text{ mA}$$


Neglecting I_B :

$$I_C = I_E = 5 \text{ mA}$$

$$V_{R_c} = 5 \text{ V} \Rightarrow V_{C1} = V_{CC} - V_{R_c} = 7 \text{ V}$$

$$V_E = -V_{BE} = -0.7 \text{ V}$$

$$V_{CE} = V_C - V_E = 7.7 \text{ V}$$

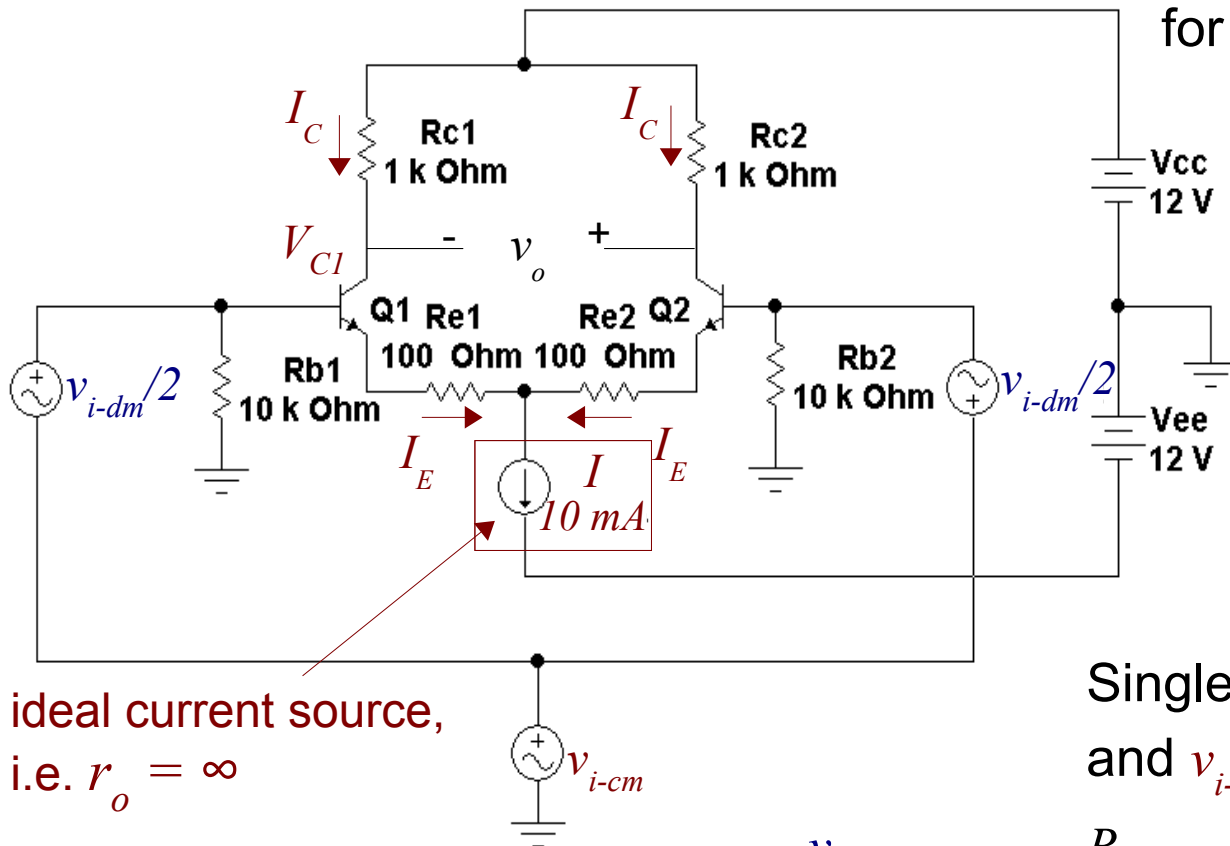


ideal current source,
i.e. $r_o = \infty$

Single-ended voltage gains w.r.t. $v_{i-dm}/2$ and v_{i-cm} (for Q1 side):

$$A'_{v-dm1} = \frac{v_{c1-dm}}{v_i = v_{i-dm}/2} \approx \frac{-R_C}{R_E} = -10$$

$$A_{v-cm1} = \frac{v_{c1-cm}}{v_{cm}} \approx -\frac{R_C}{2r_o} = 0$$

Differential- Mode AC Gain Results

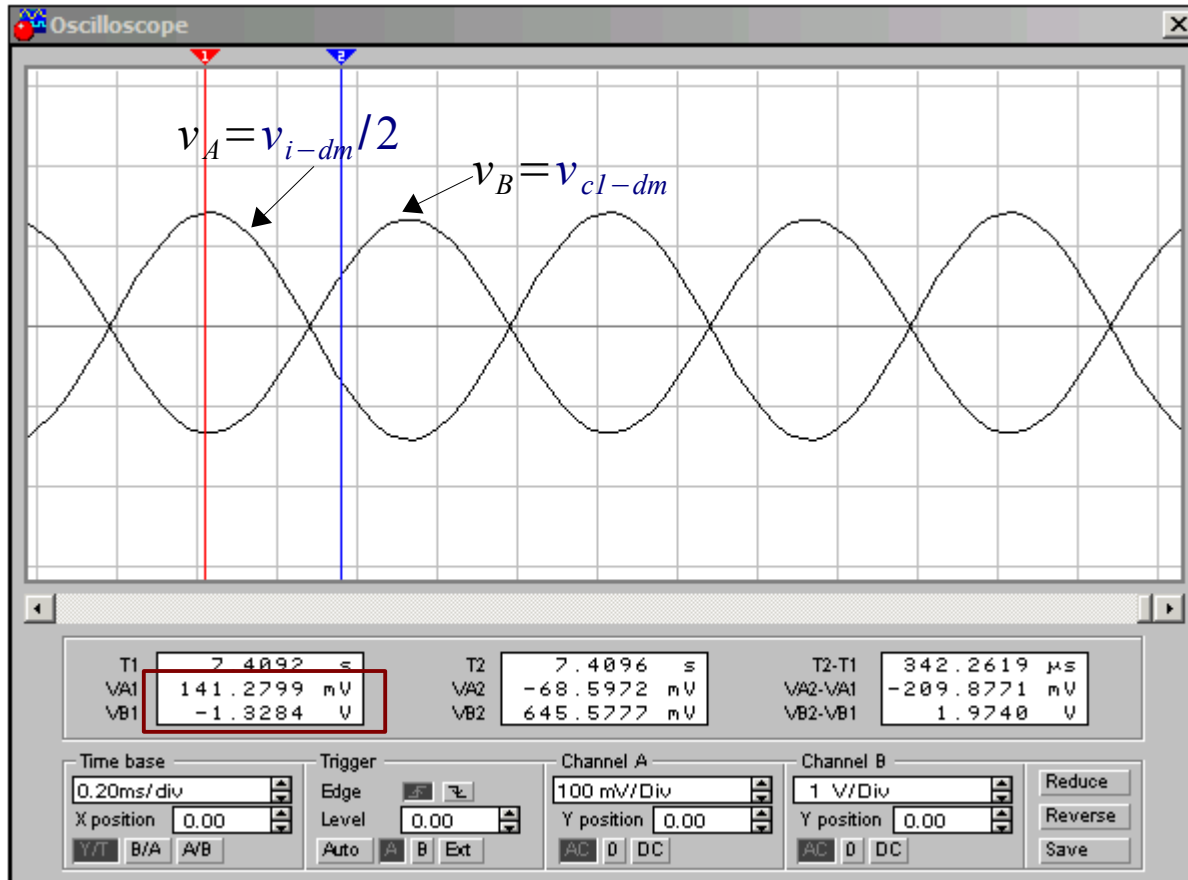

“Scope” output B at collector of Q1, i.e. $v_B = v_{cl-dm}$.


Input voltage $v_A = v_i = v_{i-dm}/2$
 $0.14 V_{peak} \arg(0^\circ)$ at $f = 1 \text{ kHz}$.

Output voltage $v_B = v_{cl-dm}$
 $1.33 V_{peak} \arg(180^\circ)$.

Measured gain:

$$A'_{v-dm1} = \frac{v_B}{v_A} = \frac{v_{cl-dm}}{v_i} = \frac{-1.33 V}{0.14 V} = -9.5$$

Common Mode AC Results

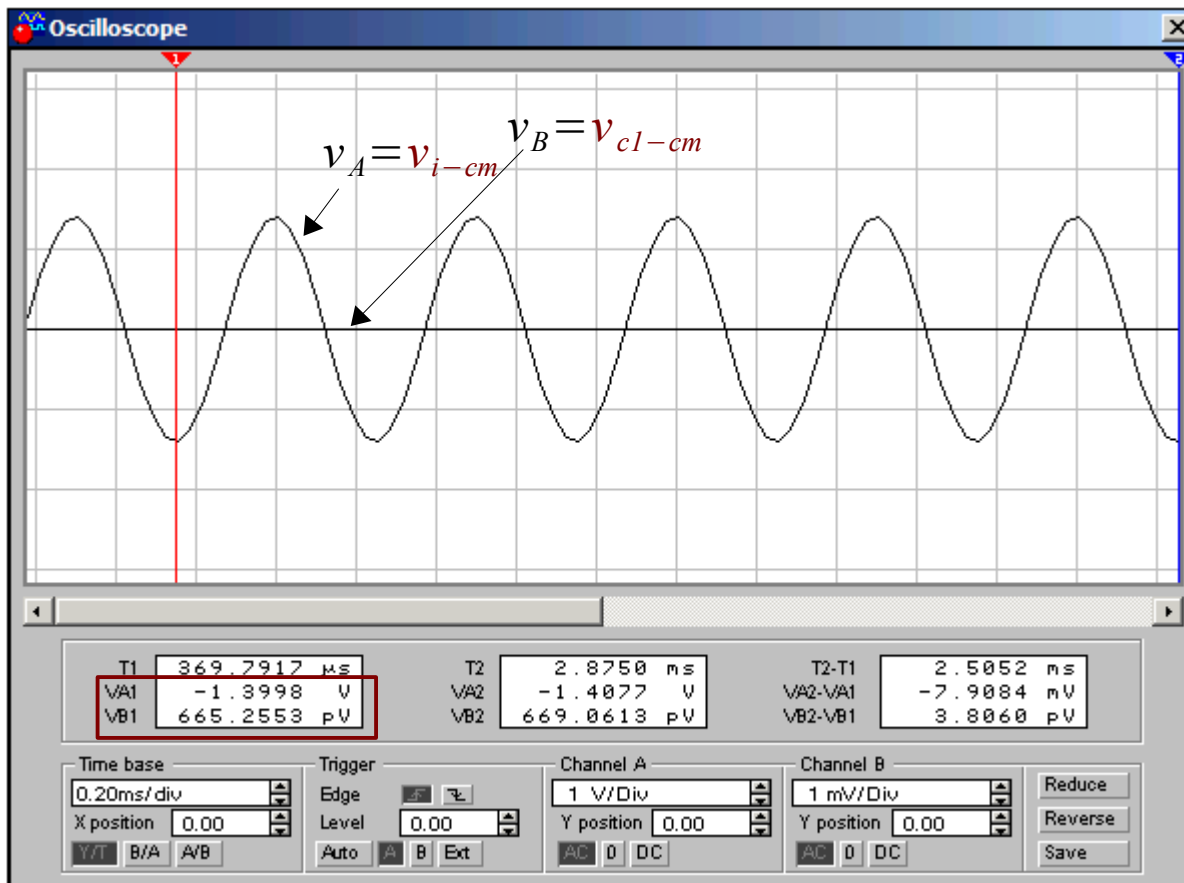

“Scope” output B at collector of Q1, i.e. $v_B = v_{cl-cm} = 0 V$.

Input voltage $v_A = v_{i-cm}$
 $0.14 V_{peak} \arg(0^\circ)$ at $f = 1 \text{ kHz}$.



Since I is an ideal current source $r_o = \infty \Rightarrow A_{v-cm1} = 0$.

No common mode signal current ($i_{cm} = 0 \Rightarrow i_{e-cm} = 0$)

$$\Rightarrow v_{cl-cm} = 0 V_{peak}$$

$$CMRR \approx 20 \log_{10} \left| \frac{-9.5}{0} \right| = \infty$$

Common Mode AC Results - II

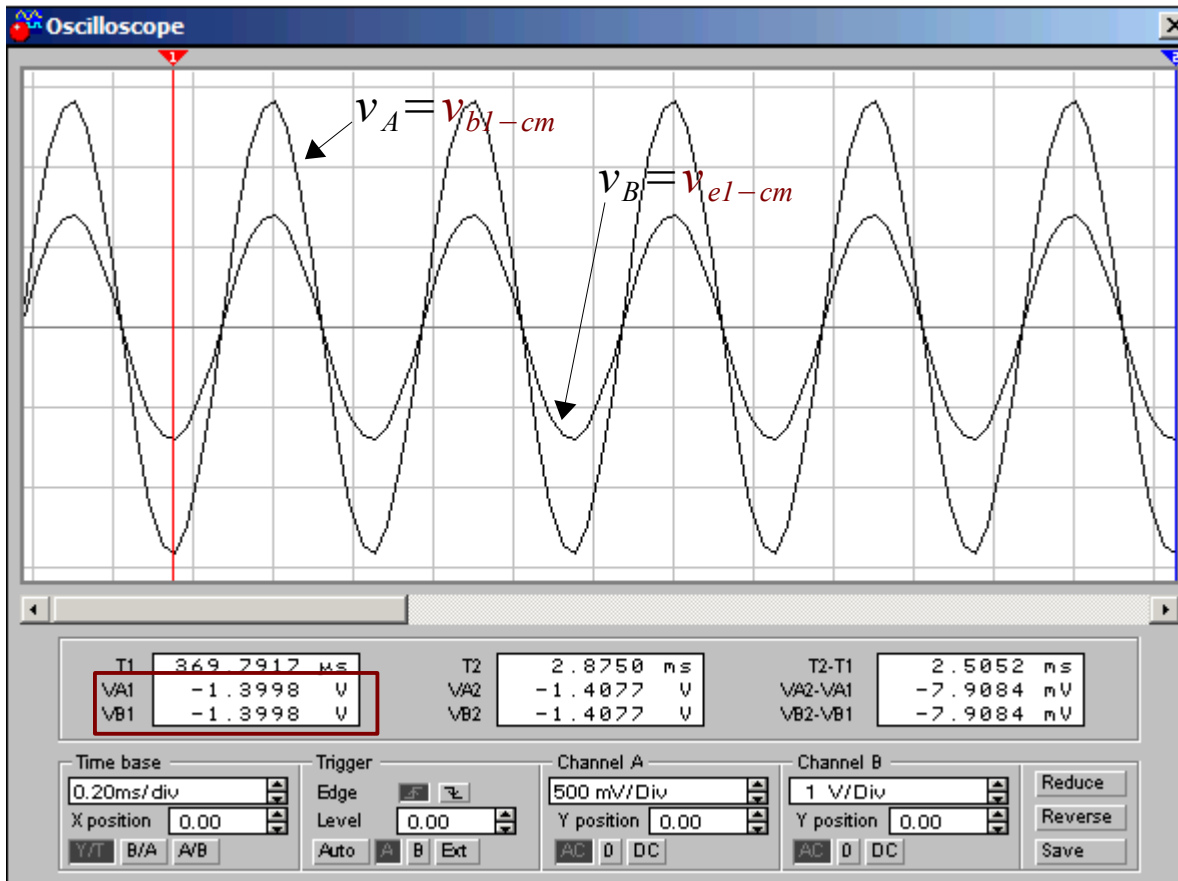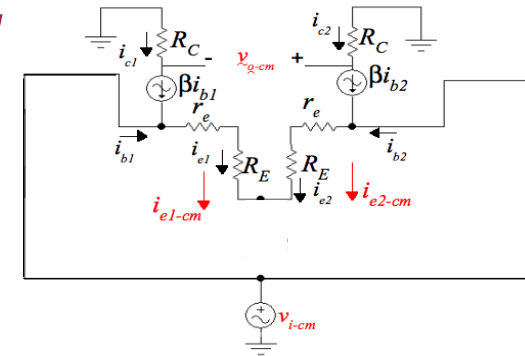

Comparing ac base and emitter voltages to ground for Q1, i.e. v_{b1-cm} , v_{e1-cm} .


$$v_{b1-cm} = v_{e1-cm} = 1.4 V_{peak}$$

$$\Rightarrow v_{be-cm} = 0 V_{peak}$$

Since $i_{e-cm} = 0$, we expect

$v_{be-cm} = 0 V_{peak}$, i.e. all base voltage appears at emitter.


Common Mode Results - Add r_o to Model

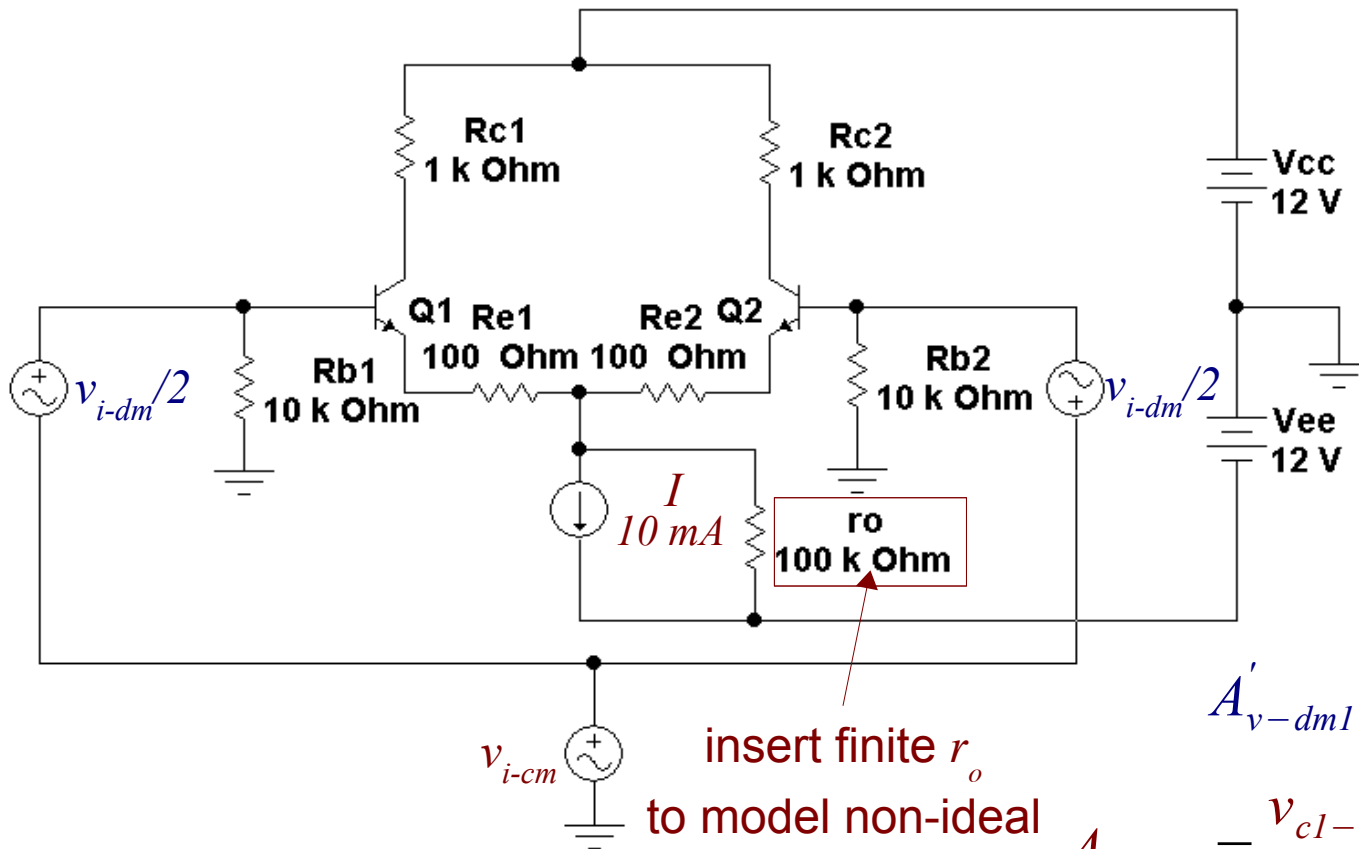

$$A'_{v-dm1} = \frac{v_{cl-dm}}{v_i} \approx \frac{-R_C}{R_E} = -10$$

$$A_{v-cm1} = \frac{v_{cl-cm}}{v_{i-cm}} \approx -\frac{R_C}{2r_o} = \frac{-1}{200} = -0.005$$

Common Mode Results - Add Finite r_o

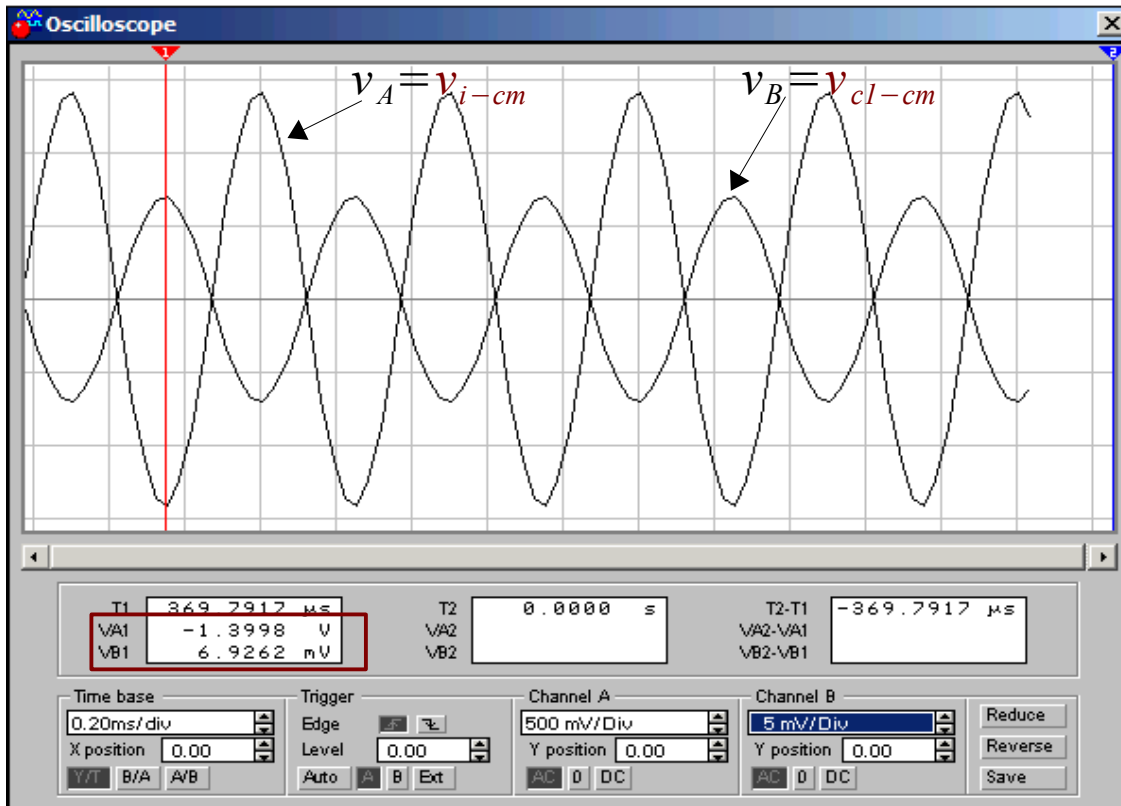

$$r_o = 100 k \Omega$$

“Scope” output B at collector of Q1, i.e. $v_B = v_{cl-cm}$.

Input voltage $v_A = v_{i-cm}$
 $1.4 V_{peak} \arg(0^\circ)$ at $f = 1 \text{ kHz}$.


Output voltage $v_B = v_{cl-cm}$
 $0.007 V_{peak} \arg(180^\circ)$.

$$A_{v-cm1} \approx \frac{-0.007}{1.4} = -0.005$$

$$A'_{v-dm1} = -9.5 \text{ (unchanged)}$$

$$CMRR \approx 20 \log_{10} \left(\frac{9.5}{0.005} \right) \approx 66 \text{ dB}$$

Simulation with Current Mirror

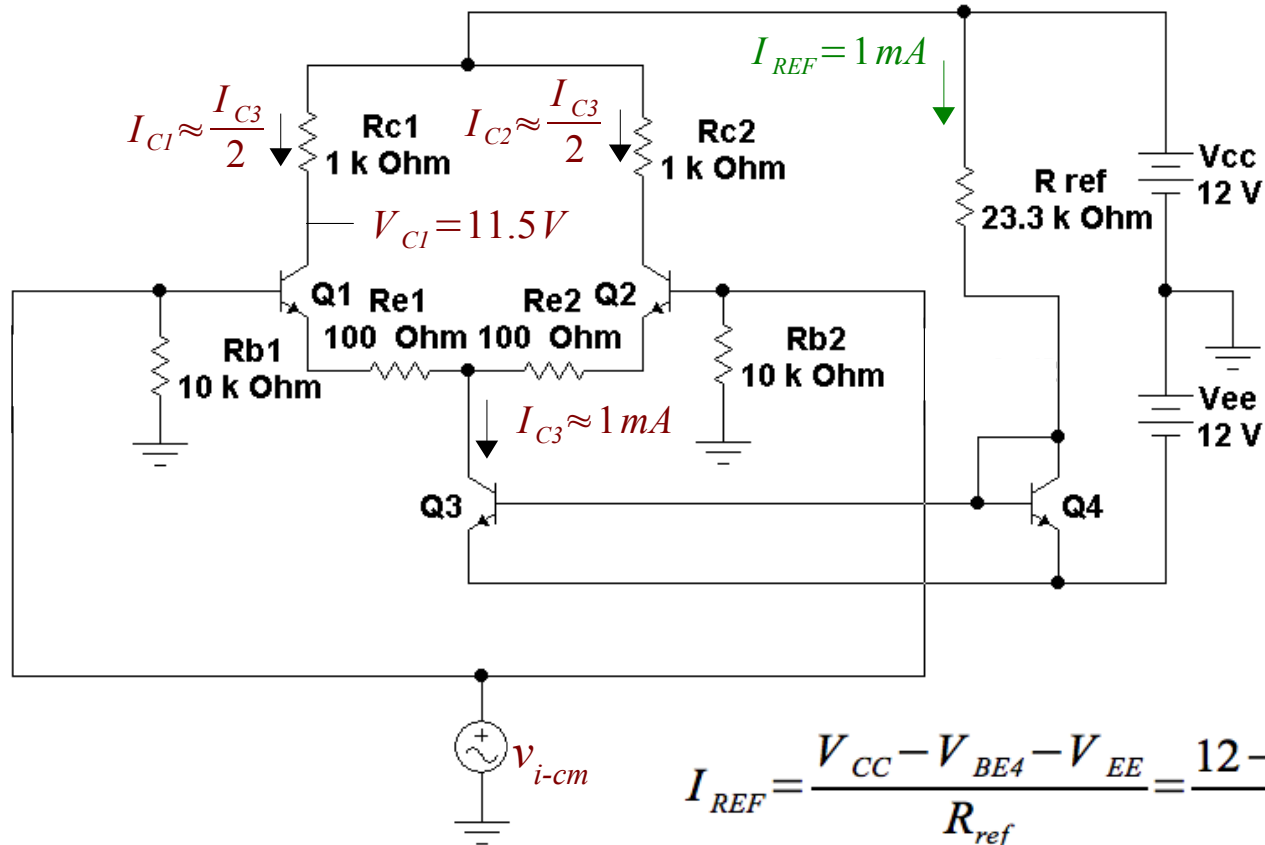

Matched 2N2222 BJTs (Q1, Q2, Q3 and Q4).

$$I_{C3} \approx 1 \text{ mA}$$


$$\Rightarrow I_{C1} = I_{C2} \approx 0.5 \text{ mA}$$

$$R_{ref} = 23.3 \text{ k} \Omega$$

$$I_{REF} = \frac{V_{CC} - V_{BE4} - V_{EE}}{R_{ref}} = \frac{12 - 0.7 - (-12\text{V})}{23.3} \text{ mA} \approx 1 \text{ mA}$$

NOTE: - The zero-to-peak ac voltage swing across each R_C now only 0.5 V !

Simulation with Current Mirror - II

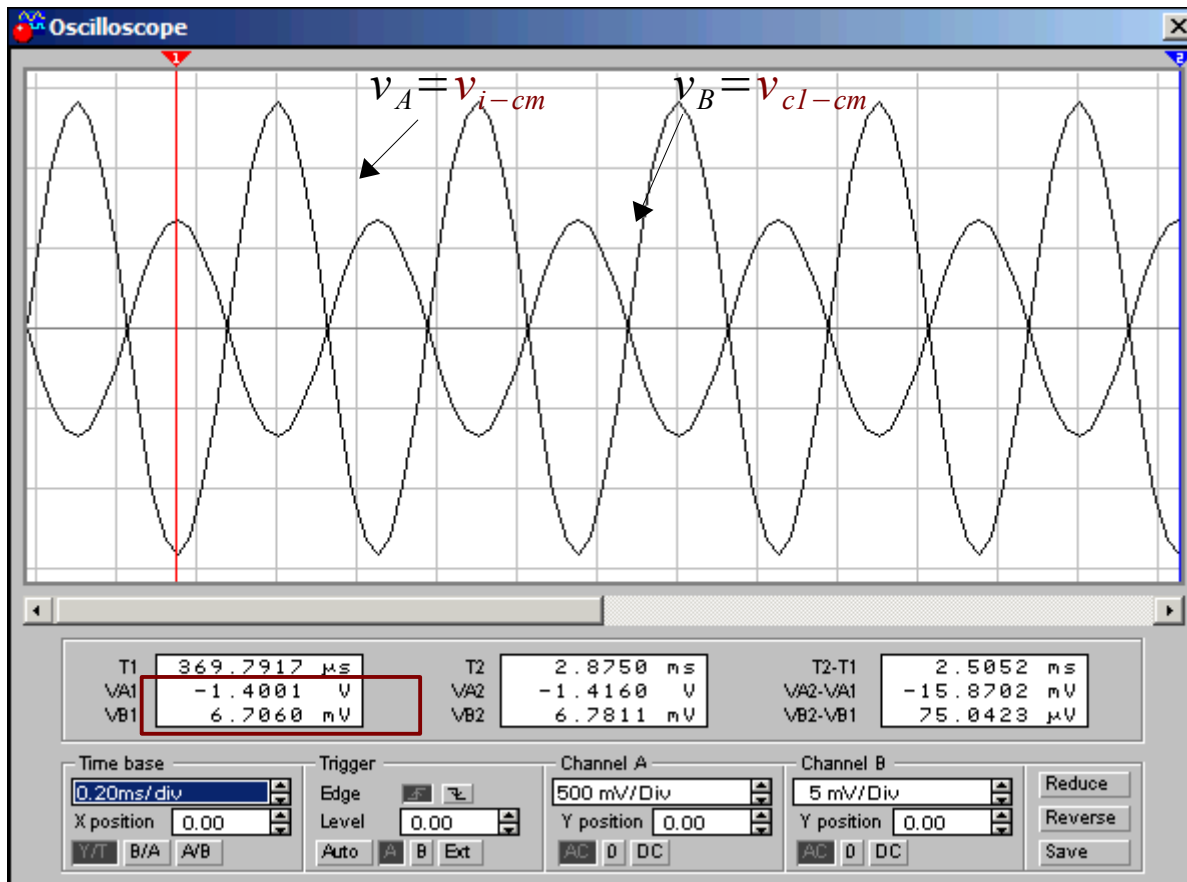

“Scope” output B at collector of Q1, i.e. $v_B = v_{c1-cm}$.


Input voltage $v_A = v_{i-cm}$
 $1.4 V_{peak} \arg(0^\circ)$ at $f = 1 \text{ kHz}$.

Output voltage $v_B = v_{c1-cm}$
 $7 \text{ mV}_{peak} \arg(180^\circ)$.

$$A_{v-cm1} \approx \frac{-0.007}{1.4} = -0.005$$

1 kHz common mode results almost exactly same as those for $r_o = 100 \text{ k}\Omega$ model.

Simulation with Current Mirror - III

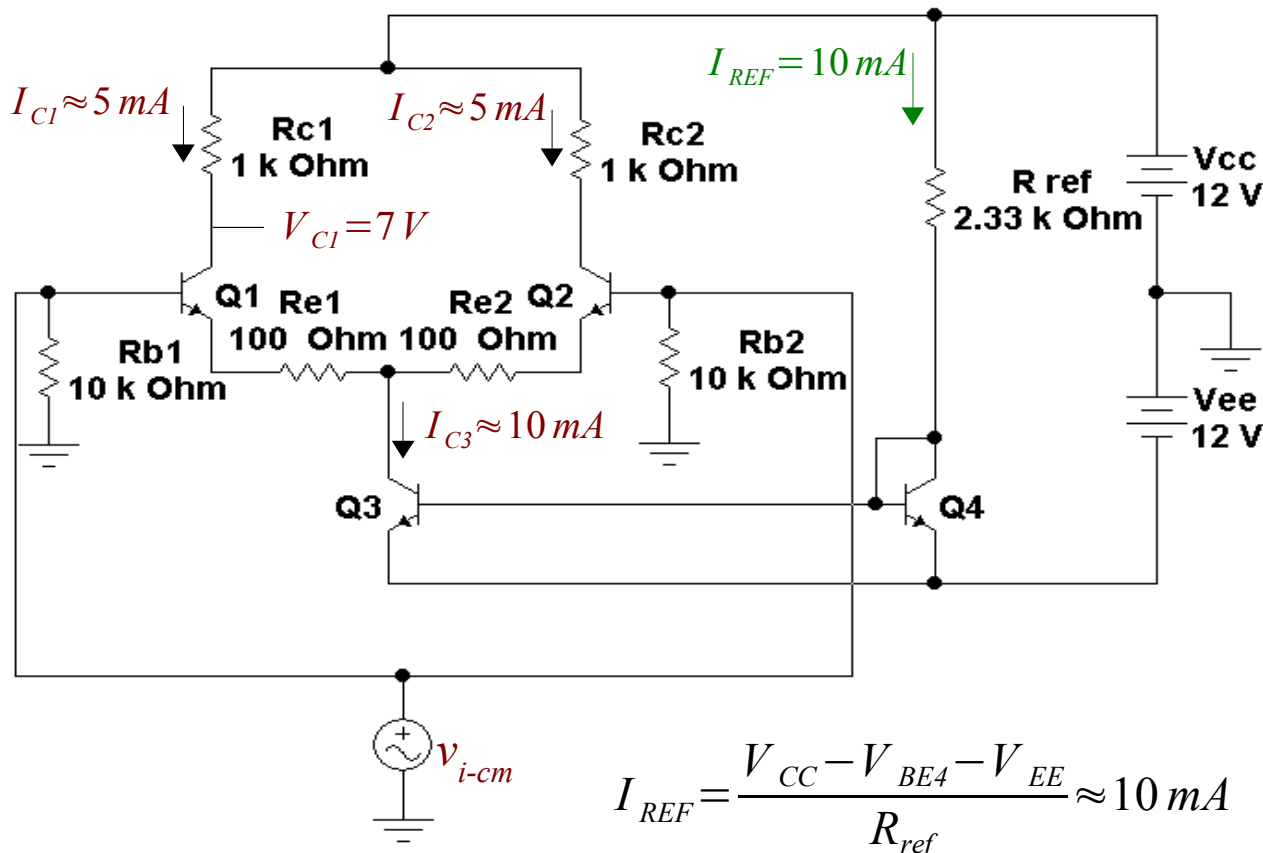

Matched 2N2222 BJTs
(Q1, Q2, Q3 and Q4).


$$I_{C3} \approx 10 \text{ mA}$$

$$\Rightarrow I_{C1} = I_{C2} \approx 5 \text{ mA}$$

$$R_{ref} = 2.33 \text{ k } \Omega$$

NOTE: - The zero-to-peak ac voltage swing across each R_C increased to 5 V !

Simulation with Current Mirror - III

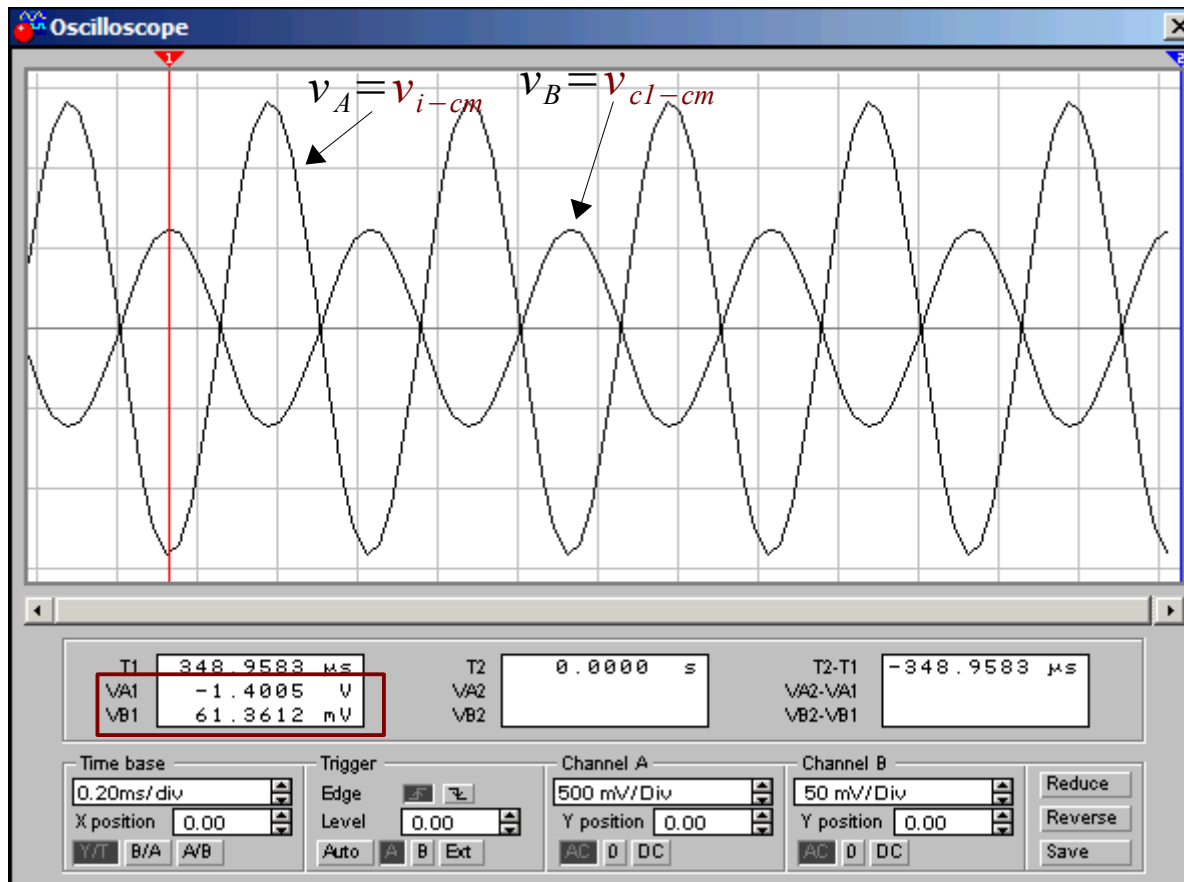

Input voltage $v_A = v_{i-cm}$
 $1.4 V_{peak} \arg(0^\circ)$ at $f = 1 \text{ kHz}$.

Output voltage $v_B = v_{cl-cm}$
 $60 mV_{peak} \arg(180^\circ)$.

$$A_{v-cm1} \approx -0.043$$

Common mode output now about $10X$ its previous value with 0.5 mA collector current.


Why? Early effect!

$$r_o = \frac{V_A}{I_C} \approx 10 \text{ k}\Omega$$


10 times the current means $1/10$ the value of r_o !

$$A_{v-cm1} \approx \frac{-0.06}{1.4} = -0.043$$

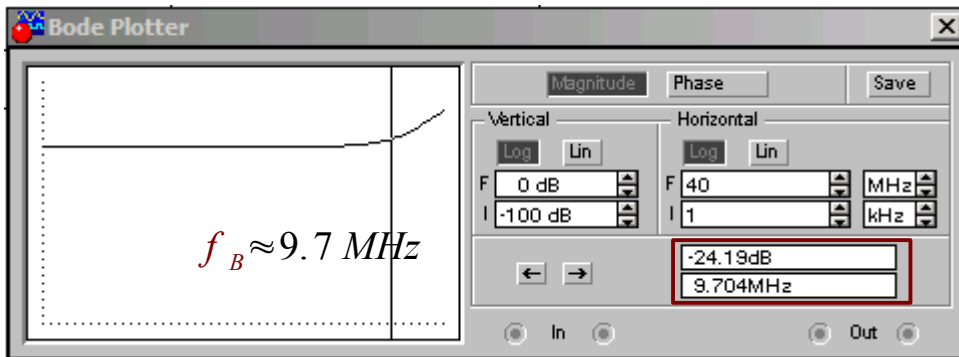Simulation with Current Mirror - Bode Plots



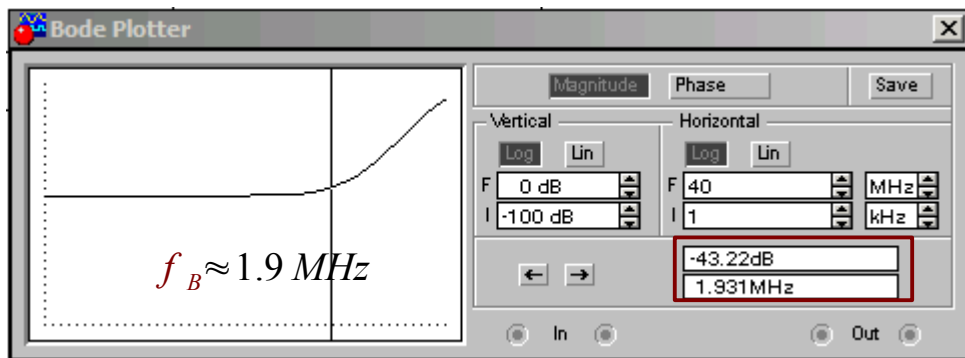5 mA current: $A_{v-cm1(dB)} + 3 \text{ dB}$ frequency



0.5 mA current: $A_{v-cm1(dB)} + 3 \text{ dB}$ frequency

$$r_o \approx 10 \text{ k}\Omega \quad (I_{REF} = 10 \text{ mA})$$

$$A_{v-cm1(dB)}(f = 1 \text{ kHz}) \approx 20 \log_{10}\left(\frac{0.06}{1.4}\right) = -27.3 \text{ dB}$$

$$A_{v-cm1(dB)}(f = 9.7 \text{ MHz}) = -24.2 \text{ dB} (+ 3 \text{ dB})$$

$$f_B \approx \frac{1}{2\pi r_o C_o} \Rightarrow$$

theory $\frac{f_{B(1mA)}}{f_{B(10mA)}} \approx \frac{r_{o(10mA)}}{r_{o(1mA)}} = \frac{10\text{k}}{100\text{k}} = 0.1$

simulation $\frac{f_{B(1mA)}}{f_{B(10mA)}} = \frac{1.9 \text{ MHz}}{9.7 \text{ MHz}} = 0.2$

$$r_o \approx 100 \text{ k}\Omega \quad (I_{REF} = 1 \text{ mA})$$

$$A_{v-cm1(dB)}(f = 1 \text{ kHz}) \approx 20 \log_{10}\left(\frac{0.007}{1.4}\right) = -46 \text{ dB}$$

$$A_{v-cm1(dB)}(f = 1.9 \text{ MHz}) = -43.2 \text{ dB} (+ 3 \text{ dB})$$



Summary & Comparison

$$I_{REF} = 1 \text{ mA}$$

$$V_{RCI} \approx \frac{I_{REF}}{2} R_{CI} = 0.5 \text{ V}$$

$$r_o \approx \frac{V_A}{I_{REF}/2} = 100 \text{ k}\Omega$$

$$A_{v-cm1} = \frac{-R_{CI}}{2r_o} \approx \frac{-0.007}{1.4} = -0.005$$

$$f_B \approx 1.9 \text{ MHz}$$

$$A'_{v-dm1} = -9.5$$

$$I_{REF} = 10 \text{ mA}$$

$$V_{RCI} \approx \frac{I_{REF}}{2} R_{CI} = 5 \text{ V}$$

$$V_{RCI} \approx \frac{I_{REF}}{2} R_{CI} = 5 \text{ V}$$


$$A_{v-cm1} = \frac{-R_{CI}}{2r_o} \approx \frac{-0.06}{1.4} = -0.043$$

$$f_B \approx 9.7 \text{ MHz}$$

$$A'_{v-dm1} = -9.5$$

Try Redesign for Reasonable Differential Mode Voltage Swing & large r_o
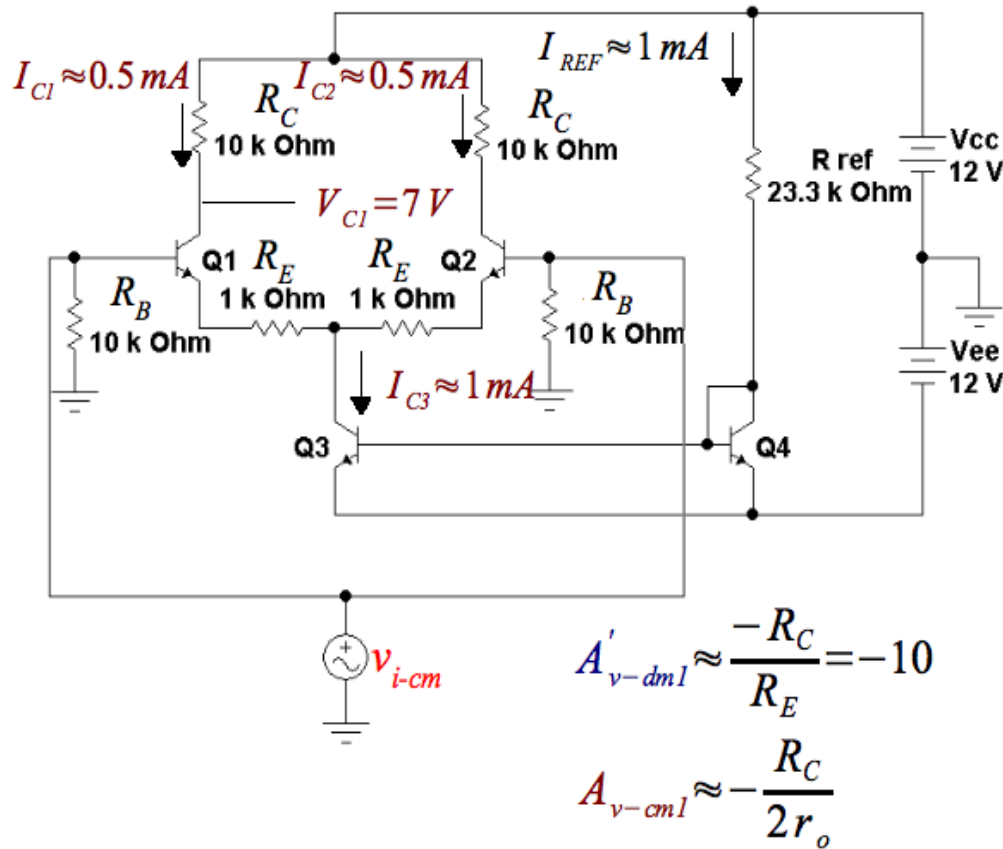
$$I_{C3} = 1 \text{ mA} \Rightarrow r_o \approx 100 \text{ k}\Omega$$



Can we beat the r_o trade-off?

IDEA:

1. Reduce I_{REF} to increase r_o .

$$r_o \approx \frac{V_A}{I_{REF}}$$

2. Increase R_C to increase V_{RC1} .

$$V_{RC1} = R_C \frac{I_{REF}}{2}$$



3. Increase R_E to retain desired A'_{v-dm1} .

$$A'_{v-dm1} = \frac{R_C}{R_E}$$

$$A_{v-cm1} \approx -\frac{R_C}{2r_o} = -\frac{V_{RC1}}{I_{REF}/2} \frac{I_{REF}}{2V_A} = -\frac{V_{RC1}}{V_A}$$

RESULT: No help!

Simulations with Parasitic Caps

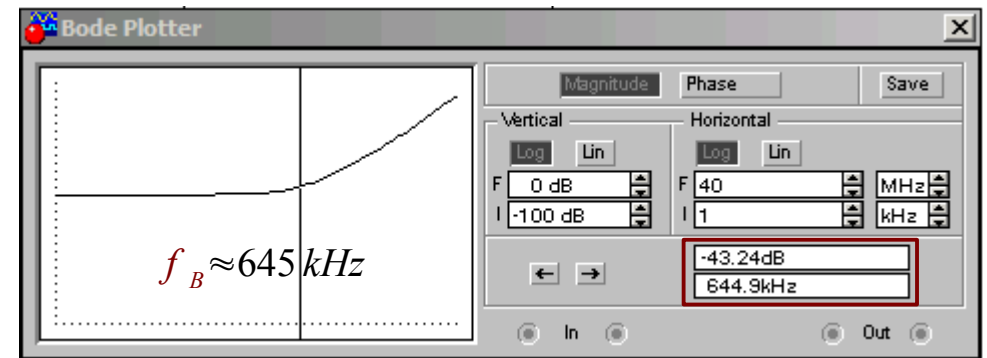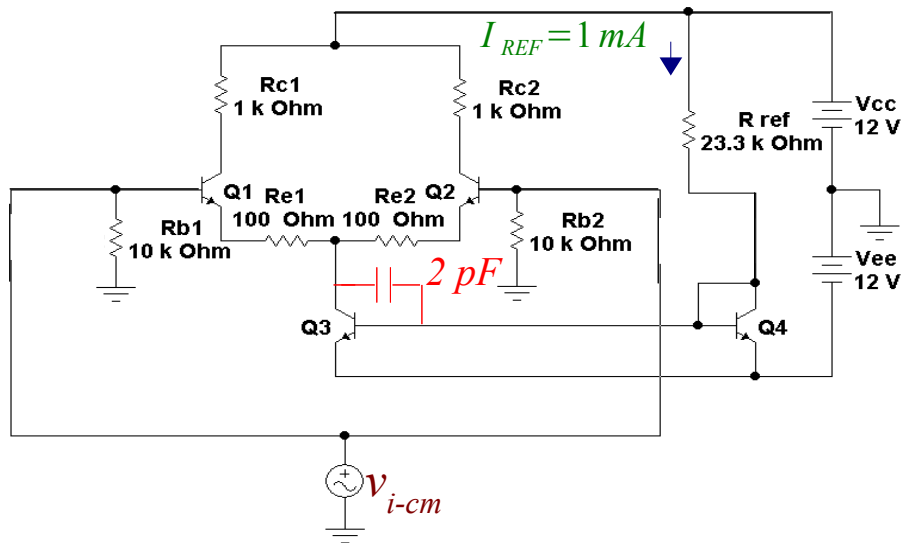



$$A_{v-cm1(dB)}(f = 1 \text{ kHz}) \approx 20 \log_{10}\left(\frac{0.007}{1.4}\right) = -46 \text{ dB}$$

$$A_{v-cm1(dB)}(f = 645 \text{ kHz}) = -43.2 \text{ dB}$$

Results with 2 pF capacitance added from collector-to-base of mirror transistor in the " $I_{C1} = I_{C2} = 0.5 \text{ mA}$ amplifier" emitter return path.

This drops the amplifier $A_{v-cm1(dB)} + 3 \text{ dB}$ frequency from 1.9 MHz to about 645 kHz !

Simulations with Parasitic Caps - cont.

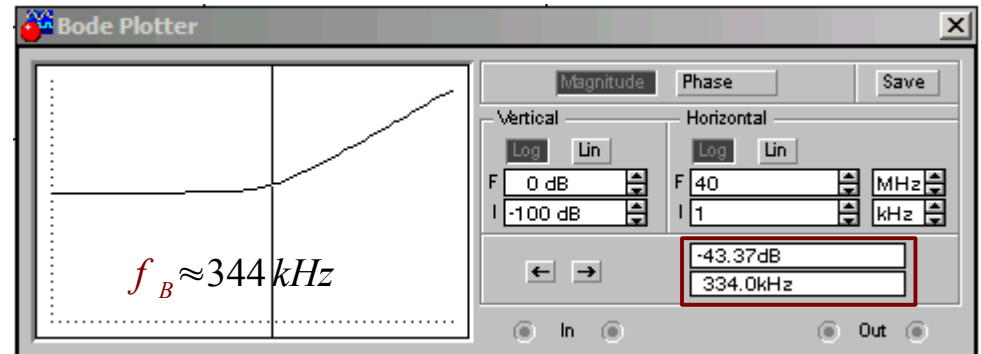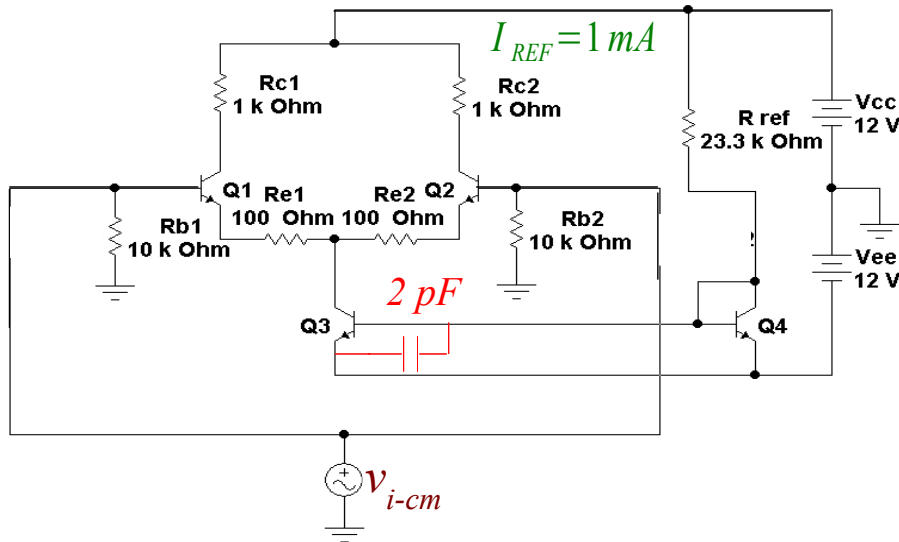

$$A_{v-cm1(dB)}(f = 1 \text{ kHz}) \approx 20 \log_{10}\left(\frac{0.007}{1.4}\right) = -46 \text{ dB}$$



$$A_{v-cm1(dB)}(f = 334 \text{ kHz}) = -43.2 \text{ dB}$$

Results with 2 pF capacitance added from base-to-emitter of mirror transistor.

This drops the amplifier $A_{v-cm1(dB)} + 3 \text{ dB}$ frequency from 1.9 MHz to about 334 kHz !

RECALL: 2 pF is about the capacitance between 2 rows of Protoboard pins!

Simulations with Parasitic Caps - cont.

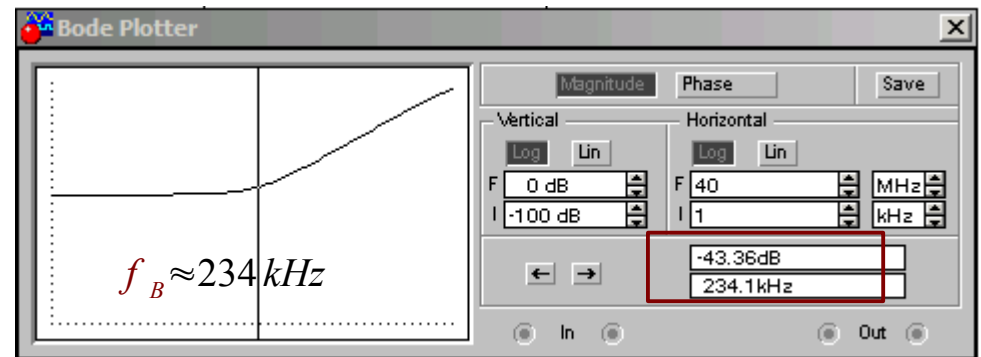
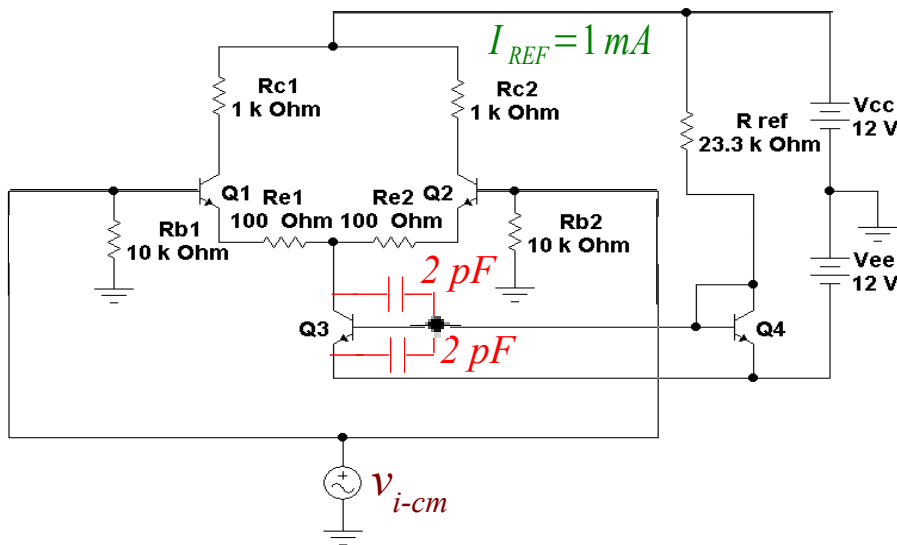


$$A_{v-cm1(dB)}(f = 1 \text{ kHz}) \approx 20 \log_{10} \left(\frac{0.007}{1.4} \right) = -46 \text{ dB}$$

$$A_{v-cm1(dB)}(f = 234 \text{ kHz}) = -43.2 \text{ dB}$$

Drops amplifier $A_{v-cm1(dB)}$ break frequency from 1.9 MHz to about 234 kHz !

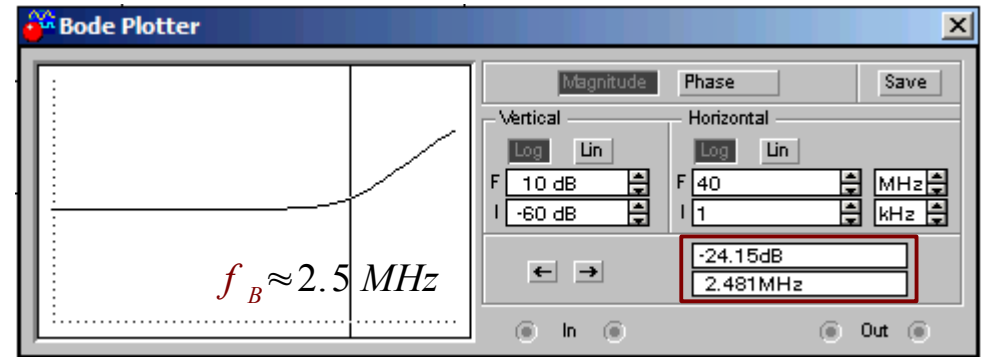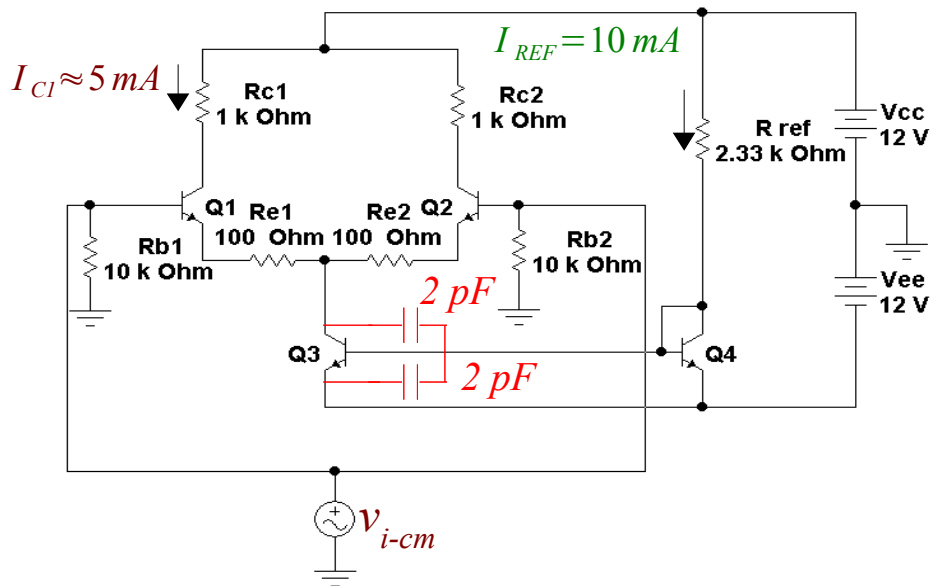Simulate the 5 mA Design with 2 pF Parasitics



$$A_{v-cm}(dB)(f = 1 \text{ kHz}) \approx -27 \text{ dB}$$

$$A_{v-cm}(dB)(f = 2.5 \text{ MHz}) = -24.2 \text{ dB}$$

3dB common mode bandwidth with 2 pF base-emitter and base collector capacitances.

About 10X the bandwidth as the $I_{REF} = 1 \text{ mA}$ design.

Parasitic caps drop amplifier $A_{v-cm}(dB)$ break frequency from 9.7 MHz to about 2.5 MHz!

	$I_{REF} = 10 \text{ mA}$	$I_{REF} = 1 \text{ mA}$
f_B	2.5 MHz	234 kHz
$A_{v-cm}(dB)(f = 1 \text{ kHz})$	-27 dB	-46 dB
$A'_{v-dm}(dB)(f = 1 \text{ kHz})$	+20 dB	+20 dB

Observations

- 1). For best common mode rejection use small collector currents i.e. increase r_o .
- 2). For best bandwidth use large collector currents, i.e. decrease r_o .
- 3). Minimize parasitic capacitance around mirror transistor to increase common mode rejection bandwidth.
- 4). Since no differential mode current flows through the mirror transistor (Q3, i.e. r_o), it should have no effect on differential mode performance.
- 5). Observations 1) and 2) force a trade-off in selecting the bias current.

