


## *Feedback Basics*

- Stability
- Feedback concept
- Feedback in emitter follower
- One-pole feedback and root locus
- Frequency dependent feedback and root locus
- Gain and phase margins
- Conditions for closed loop stability
- Frequency compensation

## *Circuit/System Stability*


1. Simply put, a linear system such as an electronic circuit is “stable” if it has no poles (denominator roots or zeros) in the right-half of the complex  $s$ -plane.
2. Right-half plane poles correspond to growing exponential terms in the solution of the system/circuit differential equation.
3. To determine stability, we need to check for RH plane poles. This requires either factoring the denominator polynomial or employing a number of other techniques developed to assist in the pencil and paper design of linear systems.
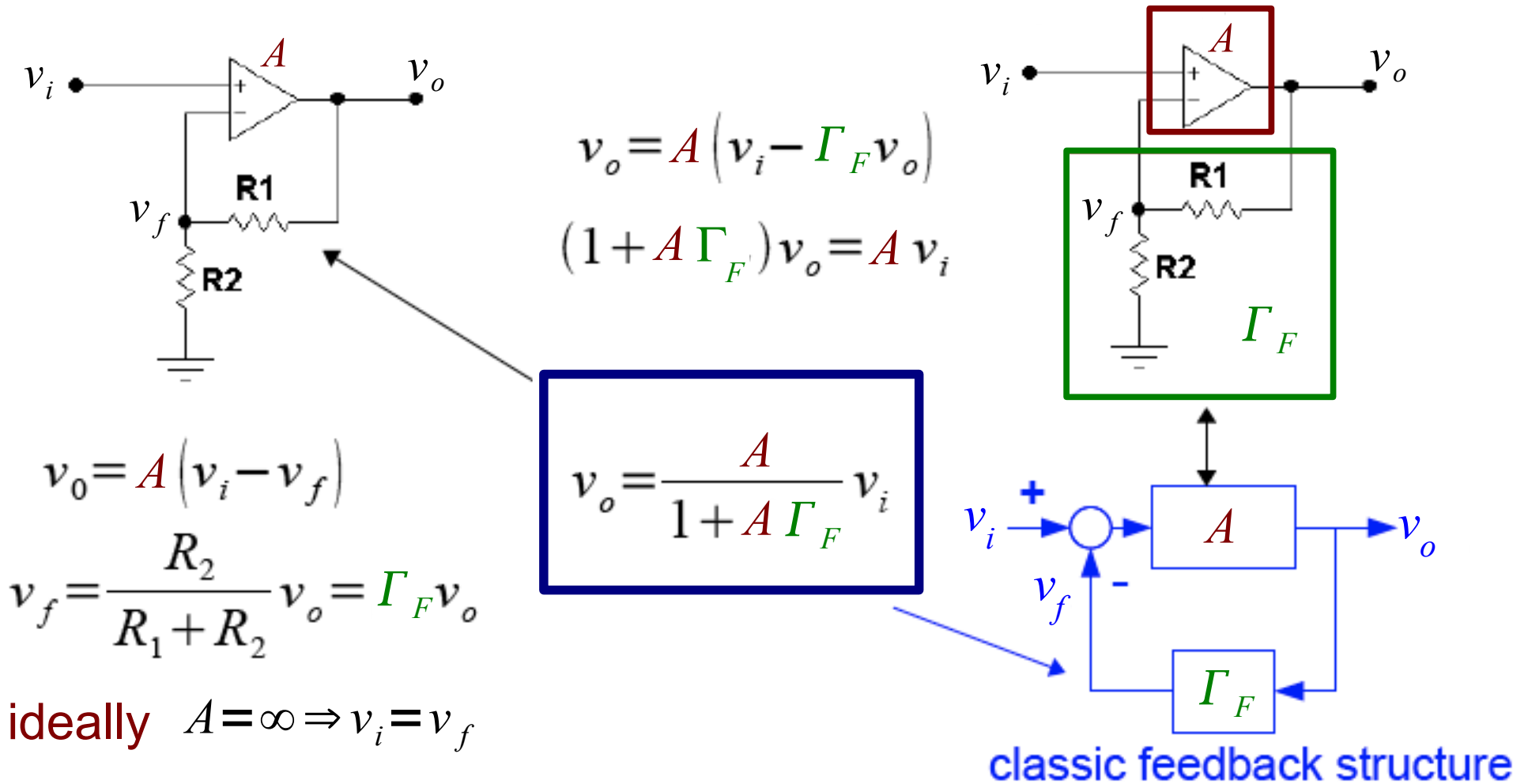
## Operational Amplifier From Another View



## Feedback Block Diagram Point of View

Fundamental block diagram

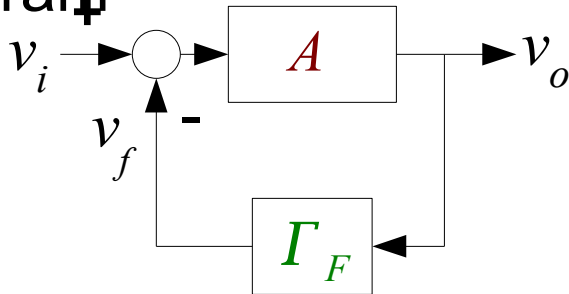


Fundamental feedback equation

$$v_o = \frac{A}{1 + A\Gamma_F} v_i$$

We can split the ideal op amp  $A$  and resistive divider  $\Gamma_F$  into 2 separate blocks because they *do not interact with*, or “load,” each other.

1. The op amp output is an ideal voltage source.
2. The op amp input draws no current.

## Comments on the Feedback Equation

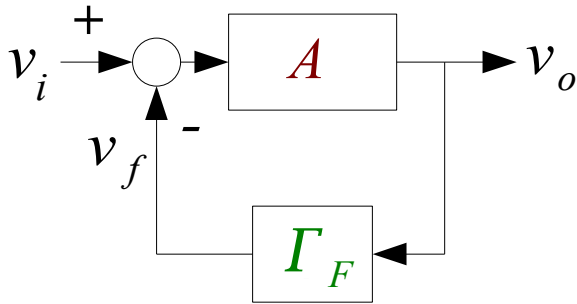

The quantity  $A\Gamma_F = \text{loop-gain}$  and  $A_{cl} = \text{closed-loop gain}$ .

The quantity  $A = \text{open-loop gain}$  and  $\Gamma_F = \text{feedback gain}$ .

If the loop gain is much greater than one, i.e.

$$A_{cl} = \frac{v_o}{v_i} = \frac{A}{1 + A\Gamma_F}$$

$$A\Gamma_F \gg 1$$


(and the system is stable – a topic to be discussed later!) the *closed-loop gain* approximates  $1/\Gamma_F$ , and is independent of “A”!

$$A = \left. \frac{v_o}{v_i} \right|_{v_f=0}$$

$$\Gamma_F = \frac{v_f}{v_o}$$

$$\boxed{A_{v-cl} = \frac{v_o}{v_i} \approx \frac{1}{\Gamma_F}} \quad \Gamma_F = \frac{R_2}{R_1 + R_2} \Rightarrow \boxed{\frac{1}{\Gamma_F} = 1 + \frac{R_1}{R_2}}$$


## Feedback in the Emitter Follower

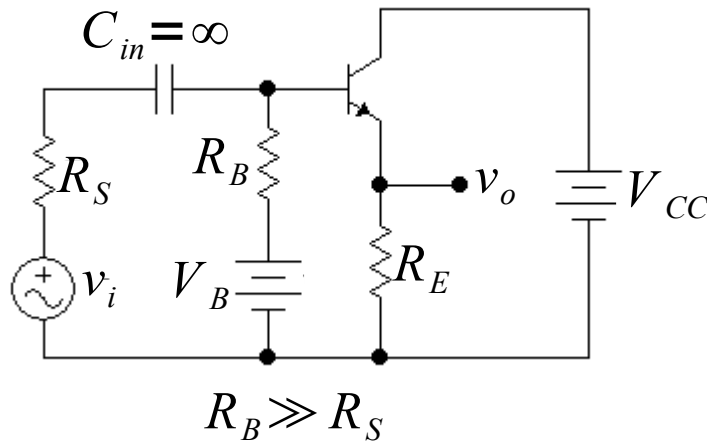

Small-signal ac emitter current equation:

$$i_e = \frac{1}{\frac{R_S}{\beta+1} + r_e + R_E} v_i$$

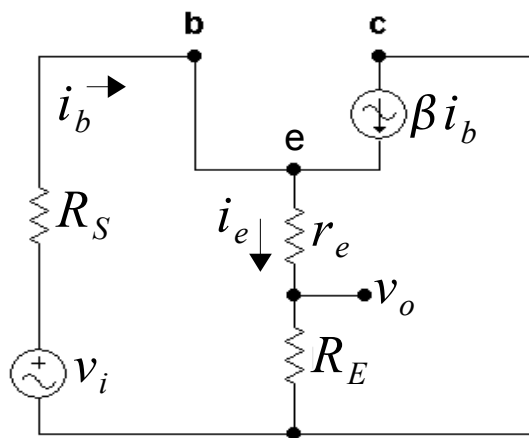
$$v_o = R_E i_e = \frac{R_E}{\frac{R_S}{\beta+1} + r_e + R_E} v_i$$



Create an “artificial” feedback equation, multiply “num” & “denom” by  $(\beta+1)/R_S$  and multiply “denom” by  $R_E/R_E$ :

$$v_o = \frac{\frac{R_E(\beta+1)}{R_S}}{1 + \frac{R_E(\beta+1)}{R_S} \frac{(r_e + R_E)}{R_E}} v_i = \frac{A}{1 + A\Gamma_F} v_i$$

## Emitter Follower Emitter Current

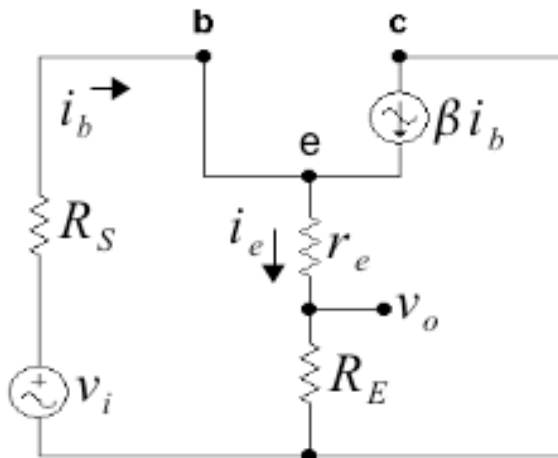

$$v_o = \frac{\frac{R_E(\beta+1)}{R_S}}{1 + \frac{R_E(\beta+1)}{R_S} \frac{(r_e + R_E)}{R_E}} v_i = \frac{A}{1 + A\Gamma_F} v_i$$

The forward gain open-loop term,  $A$ :

$$A = \frac{R_E(\beta+1)}{R_S}$$

The feedback term,  $\Gamma_F$ :

$$\Gamma_F = \frac{r_e + R_E}{R_E}$$

$$A\Gamma_F = \frac{R_E(\beta+1)}{R_S} \frac{r_e + R_E}{R_E} = (\beta+1) \frac{r_e + R_E}{R_S} \gg 1$$

If the “loop gain” is large,  $A\Gamma_F \gg 1$

$$v_o \approx \frac{1}{\Gamma_F} v_i = \frac{R_E}{r_e + R_E} v_i$$

Dependence on  $\beta$  is eliminated.



## Loop Gain Sensitivities For:

$$A_{cl} = \frac{A}{1 + A\Gamma_F}$$

calculus  $\frac{d f(x)g(x)}{d x} = g(x)\frac{d f(x)}{d x} + f(x)\frac{d g(x)}{d x}$

Open-loop gain:

$$\frac{dA_{cl}}{dA} = \frac{1}{(1 + A\Gamma_F)^2}$$

$$\frac{dA_{cl}}{A_{cl}} = \frac{1}{(1 + A\Gamma_F)^2} \frac{1 + A\Gamma_F}{A} dA$$

$$\frac{dA_{cl}}{A_{cl}} = \frac{1}{(1 + A\Gamma_F)} \frac{dA}{A} \rightarrow 0 \quad \text{as } A\Gamma_F \rightarrow \infty$$

Feedback gain:


$$\frac{dA_{cl}}{d\Gamma_F} = \frac{-A^2}{(1 + A\Gamma_F)^2}$$

$$\frac{dA_{cl}}{A_{cl}} = \frac{-A^2}{(1 + A\Gamma_F)^2} \frac{1 + A\Gamma_F}{A} d\Gamma_F$$

$$\frac{dA_{cl}}{A_{cl}} = \frac{-A\Gamma_F}{(1 + A\Gamma_F)} \frac{d\Gamma_F}{\Gamma_F} \rightarrow -\frac{d\Gamma_F}{\Gamma_F} \quad \text{as } A\Gamma_F \rightarrow \infty$$

High loop gain makes system insensitive to  $A$ , but sensitive to  $\Gamma_F$  !

## Feedback - One-pole $A(s)$

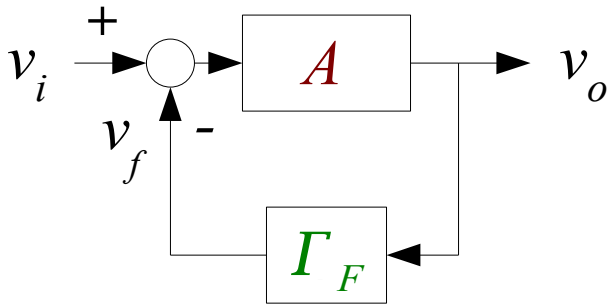

$$A_{cl}(s, \Gamma_F) = \frac{v_o}{v_i} = \frac{A(s)}{1 + A(s)\Gamma_F}$$


pole(s) of  $A_{cl}(s)$  are the roots of  $1 + A\Gamma_F = 0$ , or

$$A(s)\Gamma_F = -1 = 1 * e^{j\pi \pm 2k\pi} \text{ for } k = 0, 1, \dots$$

Consider the case where:

$$A(s) = \frac{a K_0}{s + a} \text{ open-loop pole}$$
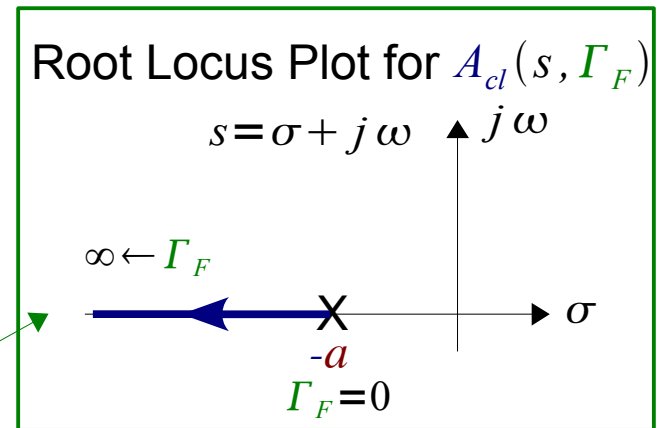
$$A_{cl}(s, \Gamma_F) = \frac{\frac{a K_0}{s + a}}{1 + \Gamma_F a K_0 \frac{1}{s + a}} = \frac{a K_0}{s + a(1 + \Gamma_F K_0)}$$



closed-loop pole

stable for all  $\Gamma_F$ !

Where  $a$ ,  $\Gamma_F$  and  $K_0$  are positive real quantities.



## Feedback - One-pole $A(s)$ cont.


$$A(s) = \frac{a K_0}{s + a}$$

open-loop (OL)

$$A_{cl}(s) = \frac{a K_0}{s + a(1 + \Gamma_F K_0)} = \frac{N(s)}{D(s)}$$


closed-loop (CL)

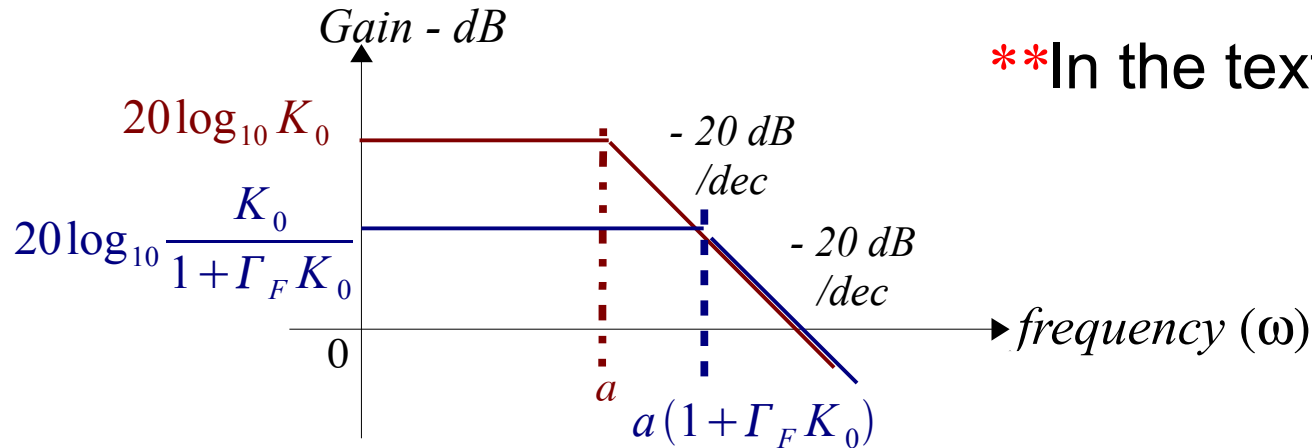**\*\*In the text  $\beta = \Gamma_F$  \*\***



$$GBW_{OL} = GBW_{CL} = a K_0$$

## Quick Review

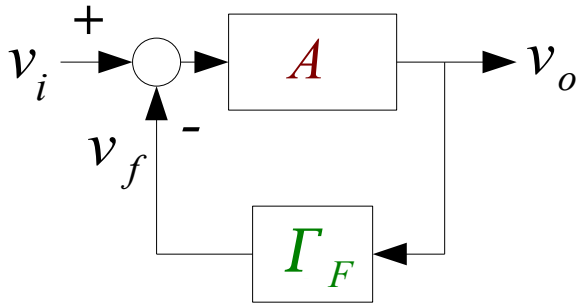


The quantity  $A = ?$  and  $\Gamma_F = ?$

The *loop-gain* = ?

The *closed-loop gain* = ?

If the *loop gain*  $\gg 1$  what is the *closed-loop gain* ?

## Quick Review

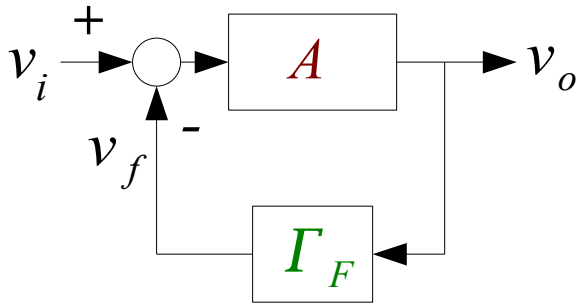

The quantity  $A = \text{open-loop gain}$  and  $\Gamma_F = \text{feedback gain}$ .

$$A = \left. \frac{v_o}{v_i} \right|_{v_f=0} \quad \Gamma_F = \frac{v_f}{v_o}$$


The *loop-gain* =  $A\Gamma_F$

The *closed-loop gain* =  $A_{cl} = \frac{v_o}{v_i} = \frac{A}{1 + A\Gamma_F}$

If the *loop gain*  $\gg 1$  what is the *closed-loop gain* ?

$$A_{v-cl} = \frac{v_o}{v_i} \approx \frac{1}{\Gamma_F} \quad A\Gamma_F \gg 1$$

## Quick Review

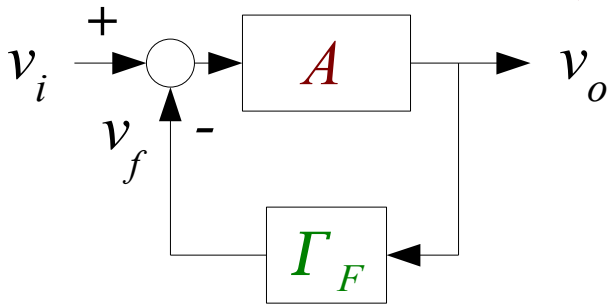

$$A_{cl}(s, \Gamma_F) = \frac{v_o}{v_i} = \frac{A(s)}{1 + A(s)\Gamma_F}$$


$$A(s) = \frac{a K_0}{s + a}$$

$a$ ,  $K_0$  and  $\Gamma_F$  are positive real.

### QUESTIONS:

1.  $A_{cl}(s, \Gamma_F)$  ?
2. What is a test of the stability of  $A_{cl}(s, \Gamma_F)$  ?
3. Is  $A_{cl}(s, \Gamma_F)$  **stable**? **absolutely stable**?

## Quick Review

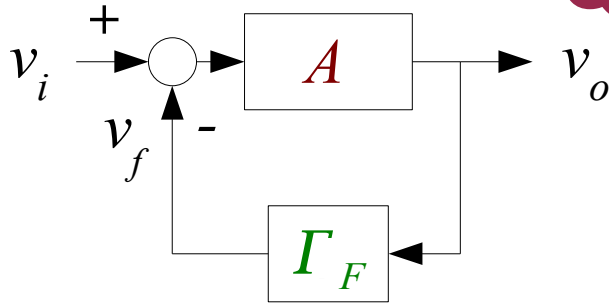

$$A_{cl}(s, \Gamma_F) = \frac{v_o}{v_i} = \frac{A(s)}{1 + A(s)\Gamma_F}$$

$$A(s) = \frac{aK_0}{s+a}$$

$a, K_0$  and  $\Gamma_F$  are positive real.

QUESTIONS:

1.  $A_{cl}(s, \Gamma_F)$  ?


$$A_{cl}(s, \Gamma_F) = \frac{\frac{aK_0}{s+a}}{1 + \Gamma_F a K_0 \frac{1}{s+a}} = \frac{aK_0}{s+a(1 + \Gamma_F K_0)}$$

2. What is a test of the stability of  $A_{cl}(s, \Gamma_F)$  ?

Poles of  $A_{cl}(s, \Gamma_F)$  in LHP for each or all  $\Gamma_F$ .

3. Is  $A_{cl}(s, \Gamma_F)$  **stable**? Yes;

**absolutely stable**? Yes

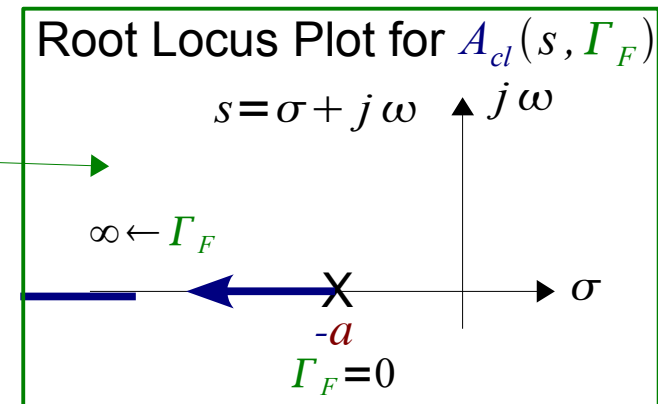



## One-pole Feedback - Root Locus

$$A(s) = \frac{a K_0}{s+a} \quad A_{cl}(s) = \frac{N(s)}{D(s)} = \frac{A(s)}{1 + A(s)\Gamma_F} = \frac{a K_0}{s+a(1 + \Gamma_F K_0)}$$

Pole of  $A_{cl}(s)$ :  $D(s) = 1 + A(s)\Gamma_F = s + a(1 + \Gamma_F K_0) = 0 \Rightarrow s = -a(1 + \Gamma_F K_0)$

ALTERNATIVELY

$$s + a(1 + \Gamma_F K_0) = 0 \Rightarrow \frac{a \Gamma_F K_0}{s+a} = -1 = 1 * e^{j\pi \pm 2k\pi} \text{ for } k = 0, 1, \dots$$

$s = r_1$  is a root of  $D(s) = 0$  or  $A(s)\Gamma_F = -1$  iff

$$\phi_{(r_1+a)} = \pi \pm 2k\pi$$

and  $\frac{a \Gamma_{F1} K_0}{|r_1+a|} = 1$  for p.r.  $a, K_0$  and  $\Gamma_{F1}$

Root locus algorithm  
for 1-pole Amplifier

$a, K_0$  and  $\Gamma_F$  being positive-real  $\Rightarrow r_1$  is positive-real





## One-pole Feedback - Root Locus

$$A_{cl}(s) = \frac{N(s)}{D(s)} = \frac{A(s)}{1 + A(s)\Gamma_F} = \frac{aK_0}{s + a(1 + \Gamma_F K_0)}$$

$s = r_l$  is a root of  $D(s) = 0$  or  $A(s)\Gamma_F = -1$  iff

$$\phi_{(r_1+a)} = \pi \pm 2k\pi \quad \text{and} \quad \frac{a\Gamma_{F1}K_0}{|r_1+a|} = 1$$

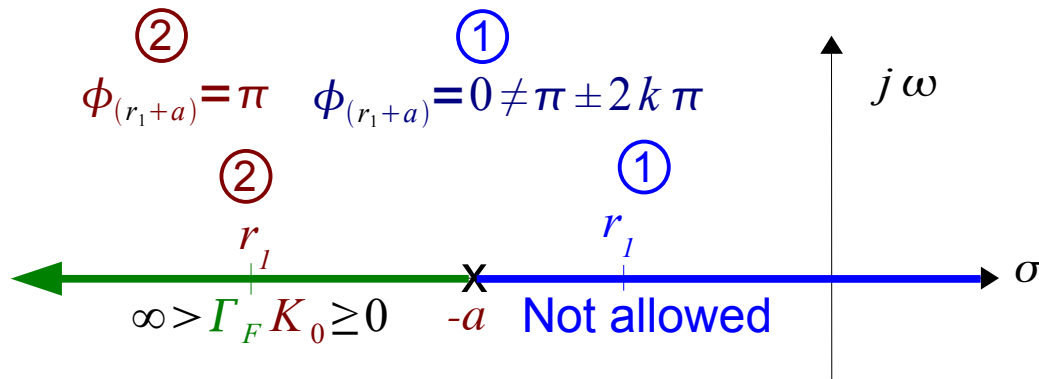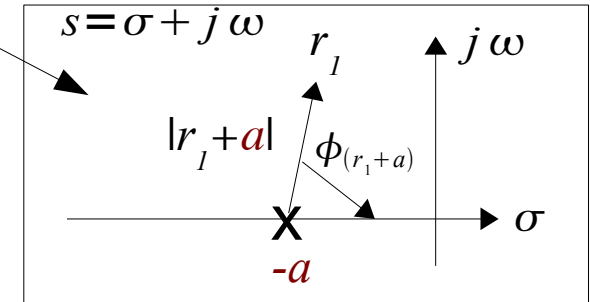$a, K_0$  and  $\Gamma_F$  being positive-real  $\Rightarrow r_l$  is positive-real




## Frequency-Dependent Feedback

Consider the case where the open-loop gain is:

$$A(s) = K \frac{(s+a)}{(s+b)(s+c)} \quad a < b < c$$

dc Gain:  $A(s)_{s=0} = K \frac{(0+a)}{(0+b)(0+c)} = K \frac{a}{bc} = K_0$

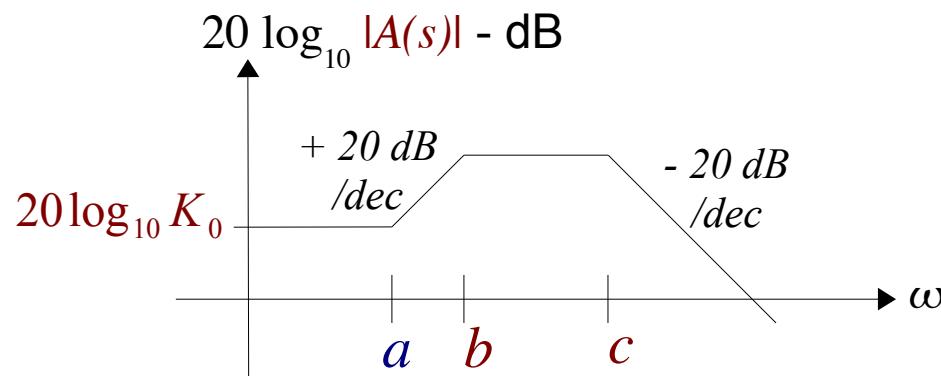A sketch of the Bode plot would look something like:



open-loop (OL)

$$A(s) = K \frac{(s+a)}{(s+b)(s+c)} \quad a < b < c$$



## Frequency-Dependent Feedback

$$A_{cl}(s) = \frac{A(s)}{1 + \Gamma_F A(s)} = \frac{K_0 \frac{(s+a)}{(s+b)(s+c)}}{1 + \Gamma_F K_0 \frac{(s+a)}{(s+b)(s+c)}} \quad \text{where } a, b, c, K_0 \text{ \& } \Gamma_F \text{ are p.r.}$$

Rationalizing this expression leads to:

$$A_{cl}(s) = \frac{K_0(s+a)}{(s+b)(s+c) + \Gamma_F K_0(s+a)} = \frac{N(s)}{D(s)}$$

The numerator is factored, but the denominator is not. We have a new quadratic polynomial  $D(s)$  for  $A_{cl}(s)$ .  $D(s)$  can be factored using the quadratic formula.

$$D(s) = (s+b)(s+c) + \Gamma_F K_0(s+a) = (s+r_1)(s+r_2) = 0$$

where  $r_1$  and  $r_2$  are either real or complex-conjugate roots




**What's the Root Locus for  $A_{cl}(s)$ ?**

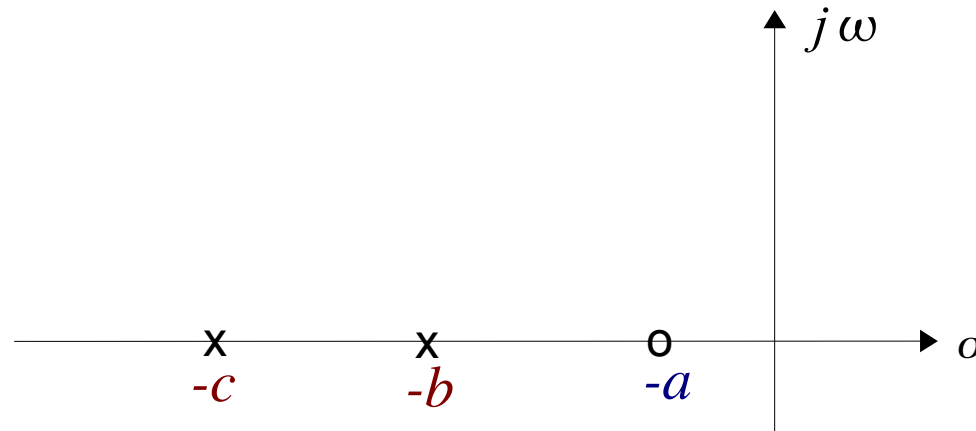**Is  $A_{cl}(s)$  Stable for all  $\Gamma_F$ ?**

$$A_{cl}(s) = \frac{K_0 \frac{(s+a)}{(s+b)(s+c)}}{1 + \Gamma_F K_0 \frac{(s+a)}{(s+b)(s+c)}} = K_0 \frac{(s+a)}{(s+b)(s+c) + \Gamma_F K_0 (s+a)} \quad a < b < c$$

for p.r.  $a, b, c,$   
 $K_0$  and  $\Gamma_F$



**What's the Root Locus for  $A_{cl}(s)$ ?**

**Is  $A_{cl}(s)$  Stable for all  $\Gamma_F$ ?**

$$(s+b)(s+c) + \Gamma_F K_0 (s+a) = 0$$

Since the poles of  $A_{cl}(s)$  will not equal any of the poles of  $A(s)$ , we can divide by  $(s+b)(s+c)$  and obtain:

$$1 + \boxed{\Gamma_F K_0 \frac{(s+a)}{(s+b)(s+c)}} = 0$$

← loop-gain

$$\Gamma_F K_0 \frac{(s+a)}{(s+b)(s+c)} = \Gamma_F K_0 f(s) = -1 = 1 * e^{j\pi \pm 2k\pi} \quad \text{for } k = 0, 1, \dots$$

The “loop-gain” terms,  $\Gamma_F$  and  $K_0$ , are positive-real numbers, so for a root  $s = r_i$  to exist, the value of  $f(s)$  must be negative-real when evaluated at  $s = r_i$ , where  $r_i$  is in general complex.

**What's the Root Locus for  $A_{cl}(s)$ ?**

**Is  $A_{cl}(s)$  Stable for all  $\Gamma_F$ ?**


$$\Gamma_F K_0 \frac{(s+a)}{(s+b)(s+c)} = -1 = 1 * e^{j\pi \pm 2k\pi} \quad \text{where } k = 0, 1, \dots$$

Working with the complex numbers in polar form:

$$\phi_{(r_i+a)} - \phi_{(r_i+b)} + \phi_{(r_i+c)} = \pi \pm 2k\pi$$

and

$$\frac{\Gamma_F K_0 a \left| \frac{r_i+a}{r_i+b} \right|}{\left| \frac{r_i+c}{r_i+c} \right|} = 1 \quad \text{for p.r. } a, b, c, K_0 \text{ and } \Gamma_F$$

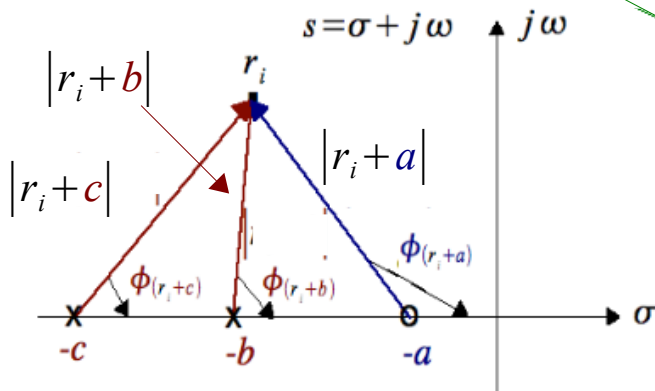

To test a potential root at say  $s = r_i$ , we first add the angles for zeros to the point " $r_i$ " in the complex s-plane and subtract the angles for poles (open-loop).

## What's the Root Locus for $A_{cl}(s)$ ?

### Is $A_{cl}(s)$ Stable for all $\Gamma_F$ ?

Only  $D(s)$  root locations where the angles with respect to open-loop pole/zero locations of  $A(s)$  are odd multiples of  $\pm 180^\circ$  are candidates.

$$D(s = -r_i) = (r_i + b)(r_i + c) + \Gamma_F (r_i + a) = 0 \quad \text{for } i = 1, 2$$


$$\phi_{tot} = \phi_{(r_i+a)} - \phi_{(r_i+b)} - \phi_{(r_i+c)} = \pi \pm 2k\pi$$

①  $\phi_{(r_{i1}+a)} = 0; \phi_{(r_{i1}+b)} = 0; \phi_{(r_{i1}+c)} = 0 \Rightarrow \phi_{tot} = 0 \neq \pi \pm 2k\pi$

②  $\phi_{(r_{i2}+a)} = \pi; \phi_{(r_{i2}+b)} = 0; \phi_{(r_{i2}+c)} = 0 \Rightarrow \phi_{tot} = \pi$

③  $\phi_{(r_{i3}+a)} = \pi; \phi_{(r_{i3}+b)} = \pi; \phi_{(r_{i3}+c)} = 0 \Rightarrow \phi_{tot} = 0 \neq \pi \pm 2k\pi$

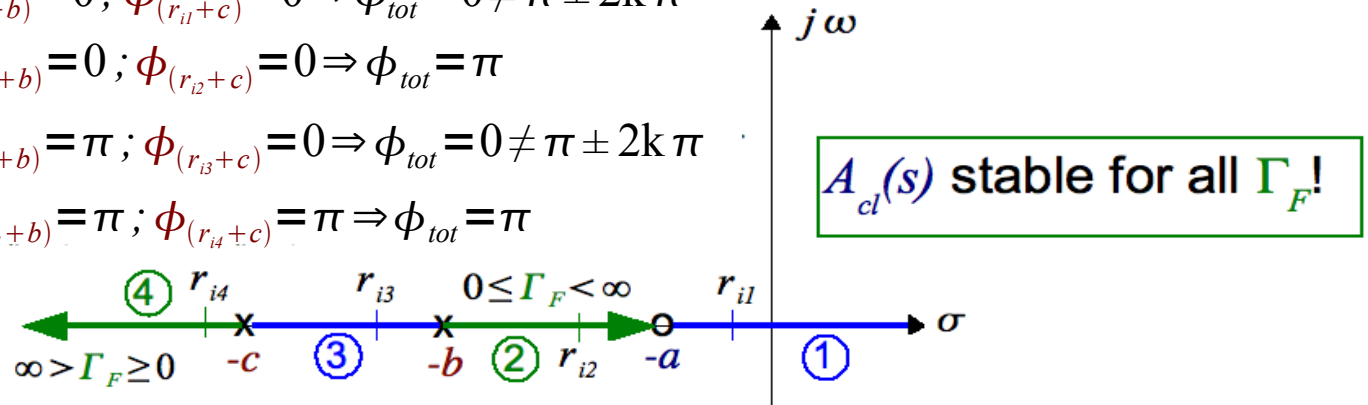④  $\phi_{(r_{i4}+a)} = \pi; \phi_{(r_{i4}+b)} = \pi; \phi_{(r_{i4}+c)} = \pi \Rightarrow \phi_{tot} = \pi$




1. All roots of  $D(s)$  must lie along the "green" loci.
2. Bandwidth of  $A_{cl}(s) >$  bandwidth of  $A(s)$
3. If an  $r_i = -a$  there is a zero/pole cancellation

**What's the Root Locus for  $A_{cl}(s)$ ?**

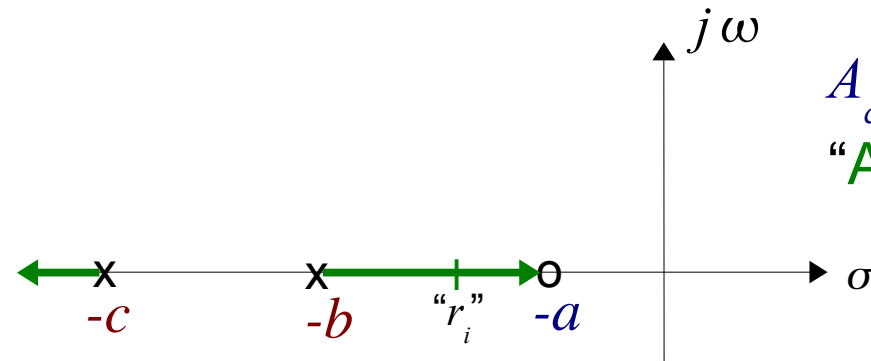**Is  $A_{cl}(s)$  Stable for all  $\Gamma_F$ ?**

$$A_{cl}(s) = \frac{K_0 \frac{(s+a)}{(s+b)(s+c)}}{1 + \Gamma_F K_0 \frac{(s+a)}{(s+b)(s+c)}} = K_0 \frac{(s+a)}{(s+b)(s+c) + \Gamma_F K_0 (s+a)} \quad a < b < c$$



$A_{cl}(s)$  IS stable for all  $\Gamma_F$ !  
“ABSOLUTELY STABLE”

1. zeros of  $A_{cl}(s)$  = zeros of  $A(s)$  and are independent of feedback
2. poles of  $A_{cl}(s) \neq$  poles of  $A(s)$  are a function of the feedback





# What's the Root Locus for $A_{cl}(s)$ ?
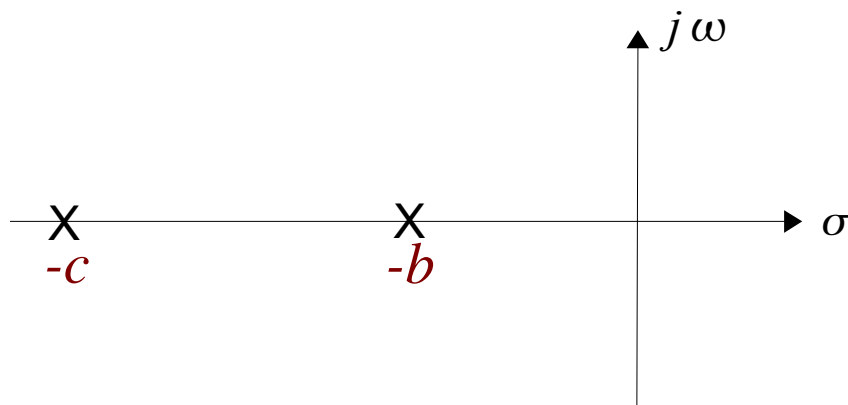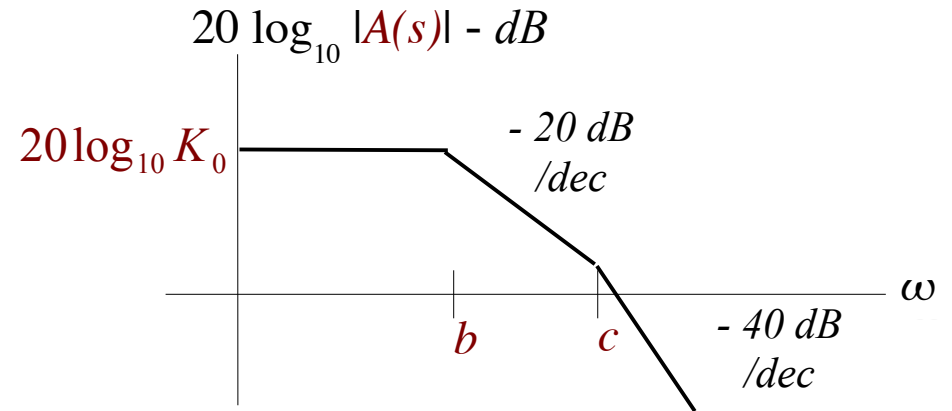
## Is $A_{cl}(s)$ Stable for all $\Gamma_F$ ?

$$A(s) = \frac{K_0 bc}{(s+b)(s+c)} \quad \text{two-pole } b < c$$

$$A_{cl}(s) = \frac{K_0 bc}{(s+b)(s+c) + \Gamma_F K_0 bc} = \frac{N(s)}{D(s)}$$




**What's the Root Locus for  $A_{cl}(s)$ ?**

**Is  $A_{cl}(s)$  Stable for all  $\Gamma_F$ ?**

$$A(s) = \frac{K_0 bc}{(s+b)(s+c)} \quad A_{cl}(s) = \frac{K_0 bc}{(s+b)(s+c) + \Gamma_F K_0 bc} = \frac{N(s)}{D(s)} \quad b < c$$

where  $b, c, K_0$  &  $\Gamma_F$  are p.r.

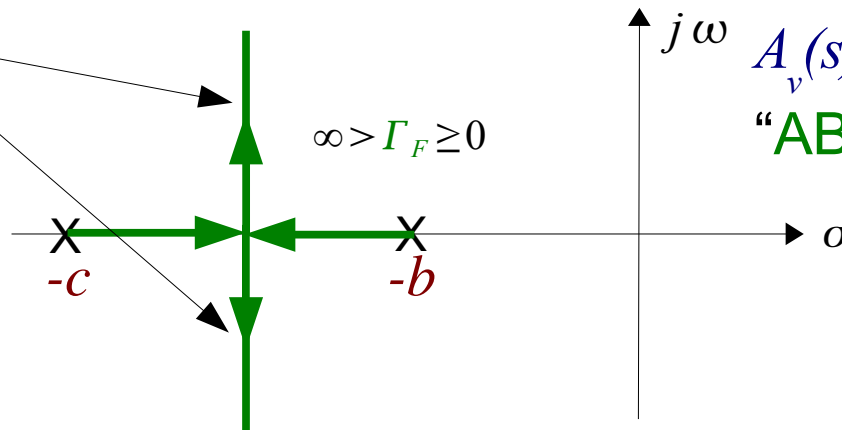complex conjugate  
poles of  $A_{cl}(s)$



$A_v(s)$  IS stable for all  $\Gamma_F$ !  
"ABSOLUTELY STABLE"


**What's the Root Locus for  $A_{cl}(s)$ ?**

**Is  $A_{cl}(s)$  Stable for all  $\Gamma_F$ ?**

$$A(s) = \frac{K_0 bcd}{(s+b)(s+c)(s+d)}$$

$$b < c < d$$
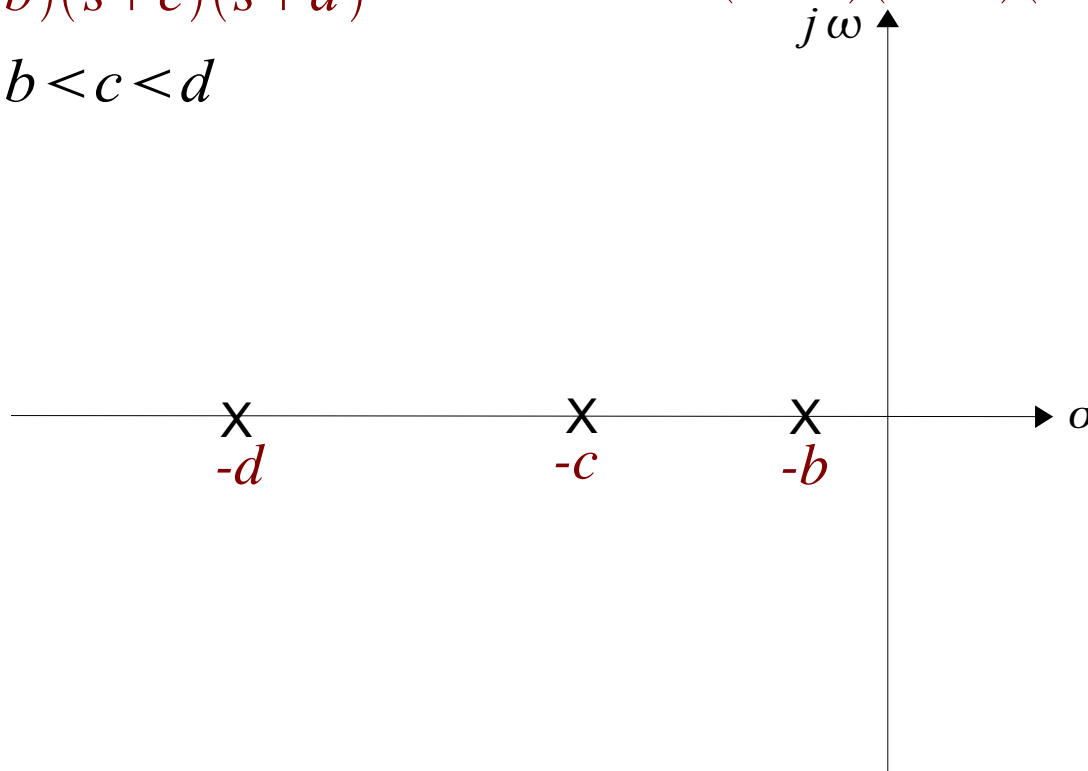
$$A_{cl}(s) = \frac{K_0 bcd}{(s+b)(s+c)(s+d) + \Gamma_F K_0 bcd} = \frac{N(s)}{D(s)}$$




## What's the Root Locus for $A_{cl}(s)$ ?

Is  $A_{cl}(s)$  Stable for all  $\Gamma_F$ ?

$$A(s) = \frac{K_0 bcd}{(s+b)(s+c)(s+d)}$$

$$b < c < d$$
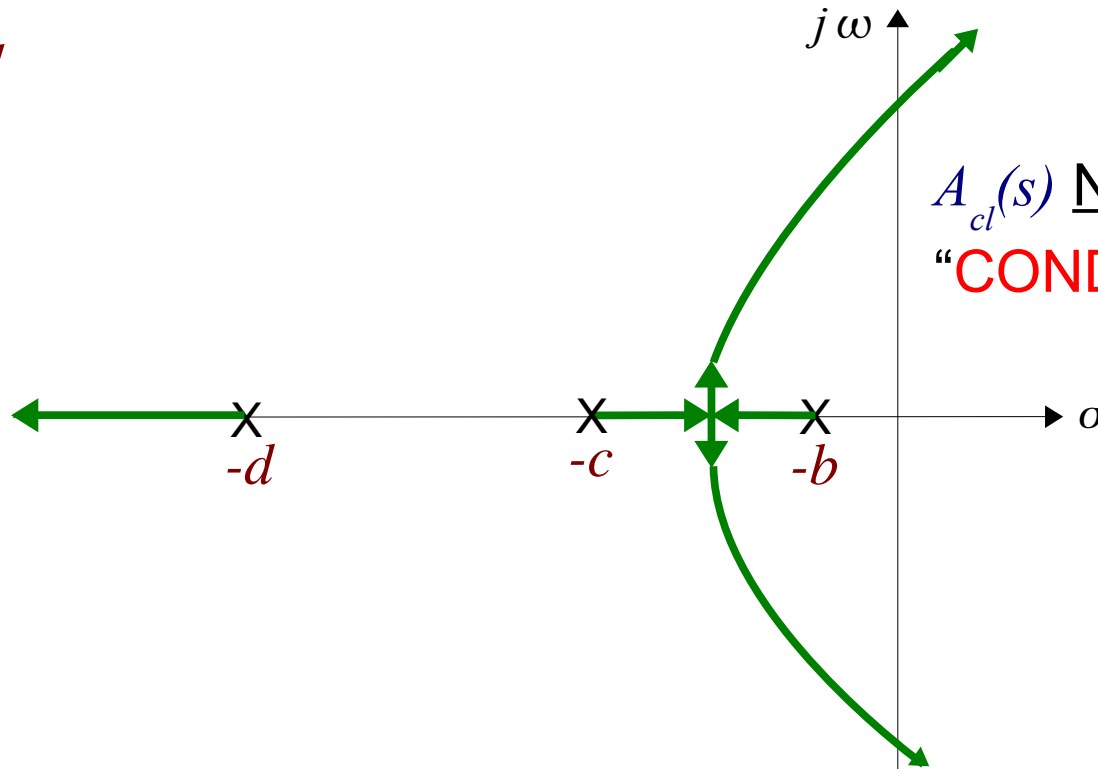
$$A_{cl}(s) = \frac{K_0 bcd}{(s+b)(s+c)(s+d) + \Gamma_F K_0 bcd} = \frac{N(s)}{D(s)}$$



$A_{cl}(s)$  NOT stable for all  $\Gamma_F$ !  
“**CONDITIONALLY STABLE**”


## *The Root Locus Method*

This graphical method for finding the roots of a polynomial is known as the *root locus method*. It was developed before computers were available. It is still used because it gives valuable insight into the behavior of feedback systems as the loop gain is varied. Matlab (control systems toolbox) will plot root loci.


In the frequency-dependent feedback (two-pole & one-zero) example, we noted that increasing feedback increases the CL bandwidth – i.e. the low & high frequency break points moved in opposite directions as  $\Gamma_F$  increases. Higher  $\Gamma_F$ , as a trade-off, reduces the closed-loop mid-band gain.

## Quick Review

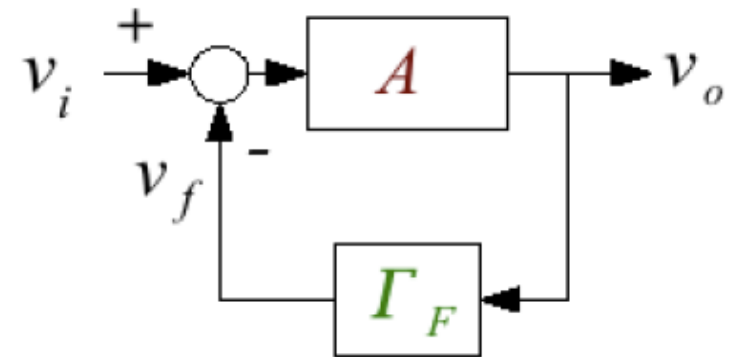
1.  $s = r_i$  is a pole of  $A_{cl}(s)$  iff ?



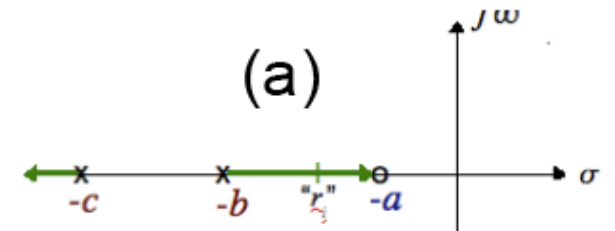2. Let  $s = r_i$  is a pole of  $A_{cl}(s)$ . What insight does the root-locus provide?



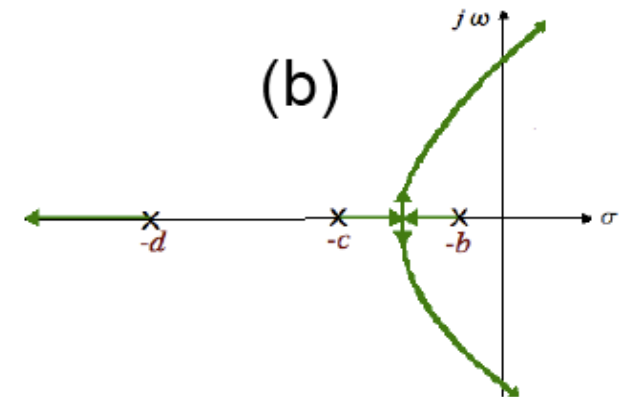3. What can be concluded from the root-locus (a); from root-locus (b)?





## Quick Review



1.  $s = r_i$  is a pole of  $A_{cl}(s)$  iff ?

$$\text{Loop-gain} = A(s)\Gamma_F \Big|_{s=r_i} = -1 = 1 * e^{j\pi \pm 2k\pi}$$

2. Let  $s = r_i$  is a pole of  $A_{cl}(s)$ . What insight does the root-locus provide?

The trajectories of this and all other poles of  $A_{cl}(s)$  for values of  $0 \leq \Gamma_F < \infty$ . Stability for any or all values of  $\Gamma_F$ .

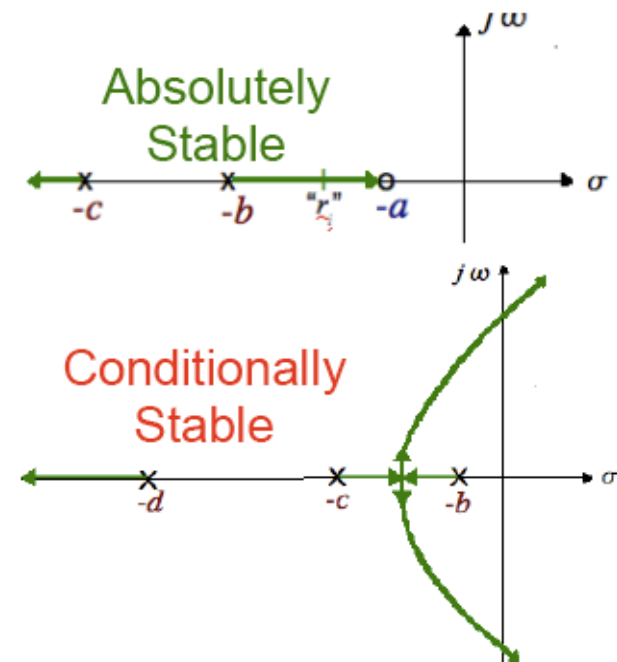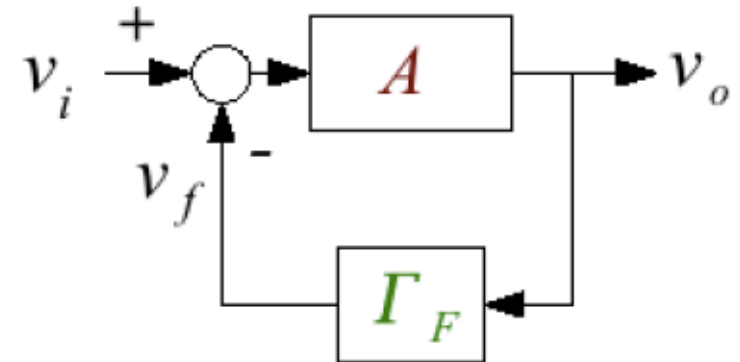
3. What can be concluded from the root-locus (a); from root locus (b)?



## Stability – Gain and Phase Margins

$s = r_i$  is a root of  $A_{cl}(s)$  iff

$$A(s)G_F \Big|_{s=r_i} = -1 = 1 * e^{j\pi \pm 2k\pi}$$

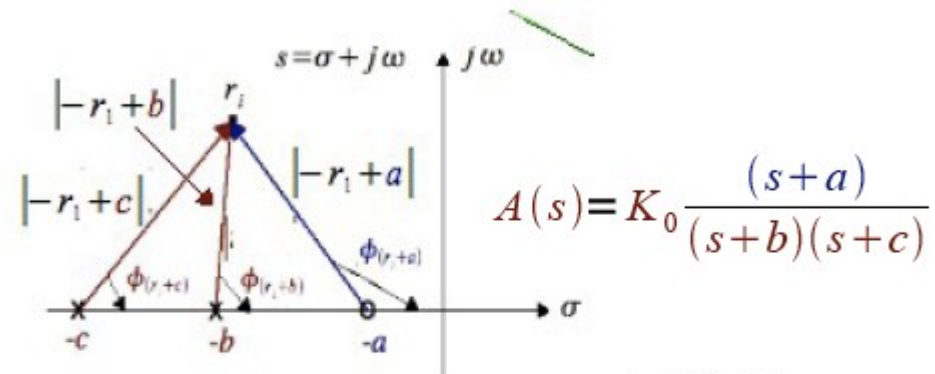

If the root  $s = r_i$  is a stable root, what is the margin for the stability?

◆ Root-Locus provides qualitative insight, but little if any quantitative information.

◆ Designers need both!

◆ Root-locus is tedious to determine in general, i.e. one must know the location of all open-loop poles and zeros.

## Stability – Gain and Phase Margins

Stability can also be determined quantitatively by plotting the gain and phase of the loop-gain =  $A(s = j\omega_i)\Gamma_F$ , i.e.


$$A_{cl}(j\omega) = \frac{V_o(j\omega)}{V_i(j\omega)} = \frac{A(j\omega)}{1 + A(j\omega)\Gamma_F}$$

Let's test for roots on the  $j\omega$  axis, i.e.  $r_i = j\omega_i$

$$A(j\omega_k)\Gamma_F = -1 = 1 e^{j\pi \pm 2k\pi} \Rightarrow \text{oscillation or instability}$$

Does  $A(j\omega_i)\Gamma_F = 1 e^{j\pi \pm 2k\pi}$  for any values of  $\omega_i$ ?

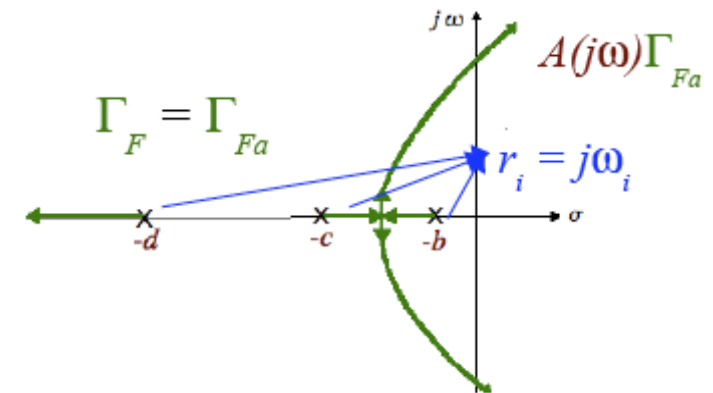$A(j\omega_i)\Gamma_F$  for particular  $\Gamma_F = \Gamma_{Fa}$  and all  $\omega_i$  is obtained from theory, sim or experiment.





## Stability - Gain and Phase Margins

Since  $A(j\omega_k)\Gamma_F = -1 = 1 e^{j\pi \pm 2k\pi} \Rightarrow$  instability

stable close-loop amplifier  $\Rightarrow |A(j\omega_{180})\Gamma_{Fa}| < 1$



$20 \log  A(j\omega_{180})\Gamma_{Fa}  < 0 \text{ dB} \Rightarrow GM > 0 \text{ dB}$ $\phi(\omega_1) = \arg [A(j\omega_1)\Gamma_{Fa}] > -180^\circ \Rightarrow PM > 0^\circ$
--


mutually consistent stability conditions


$\arg[A(j\omega_k)\Gamma_{Fa}] = -180^\circ @ \omega_k = \omega_{180}$  180° phase-crossover freq.

$20 \log_{10} |A(j\omega_k)\Gamma_{Fa}| = 0 \text{ dB} @ \omega_k = \omega_1$  Unity gain-crossover freq.




## Stability - Gain and Phase Margins

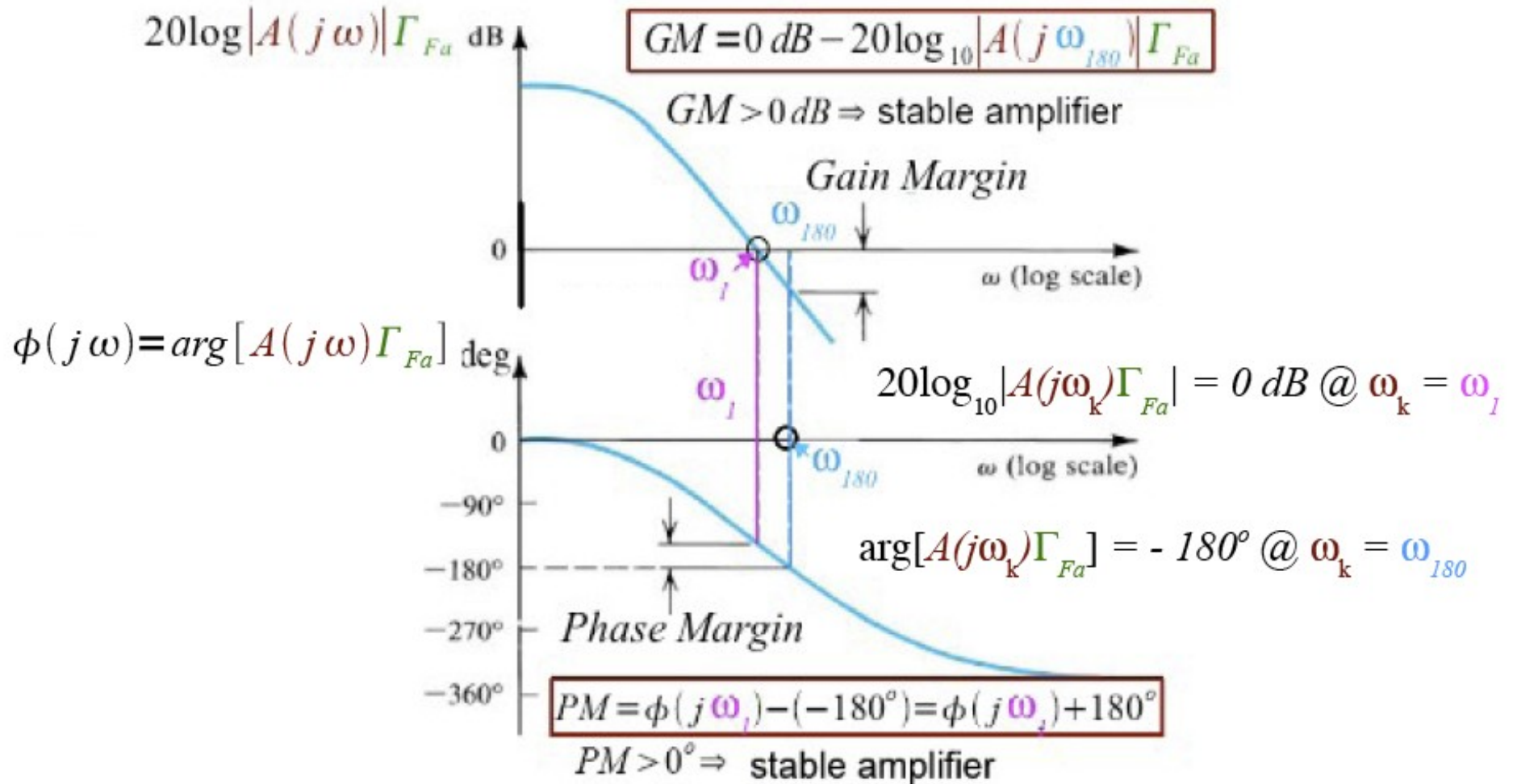

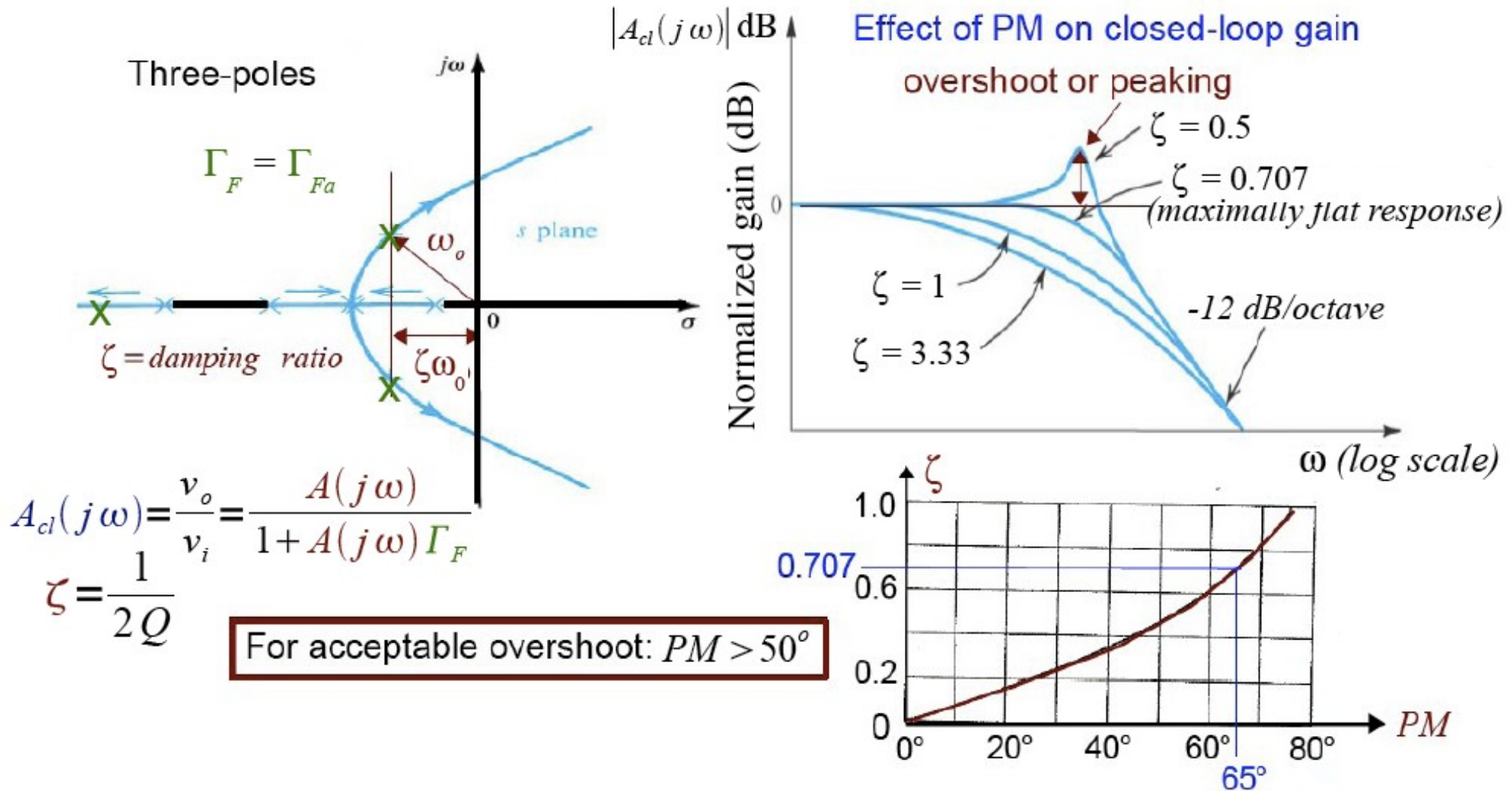

## Frequency-Domain

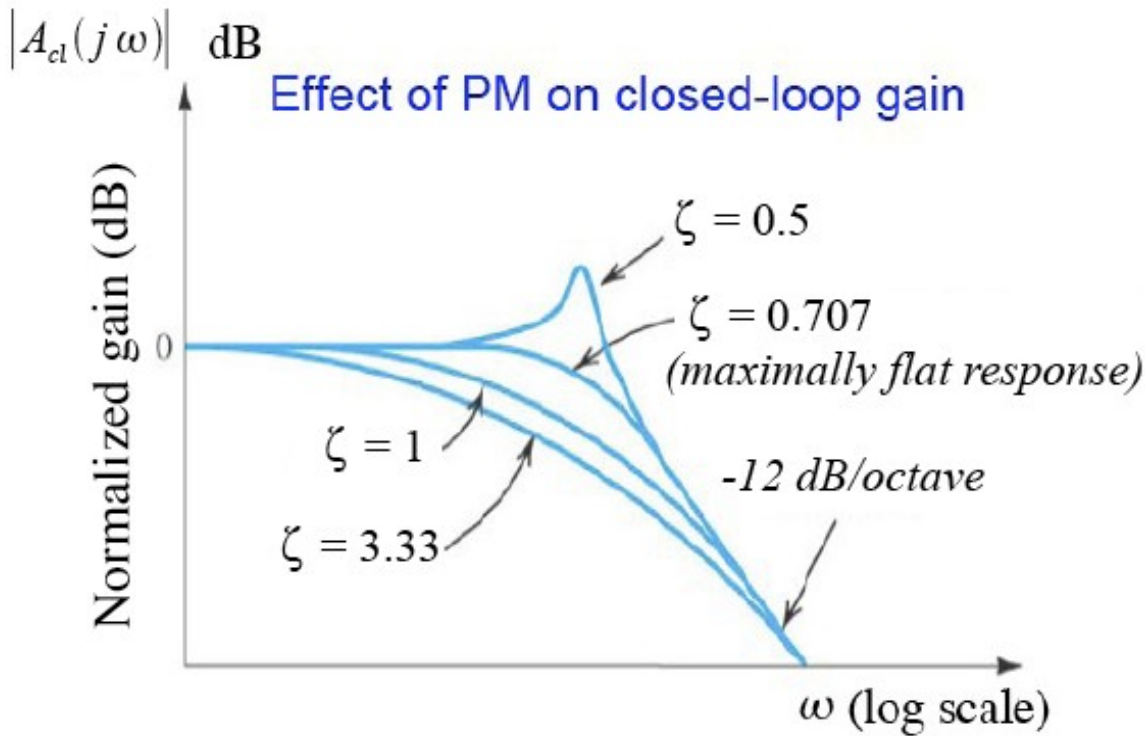


$$70^\circ > PM > 55^\circ$$

For best compromise of overshoot vs.  $t_{rise}$  &  $t_{settle}$ .

## Time-Domain


ideal unit step  $u(t)$

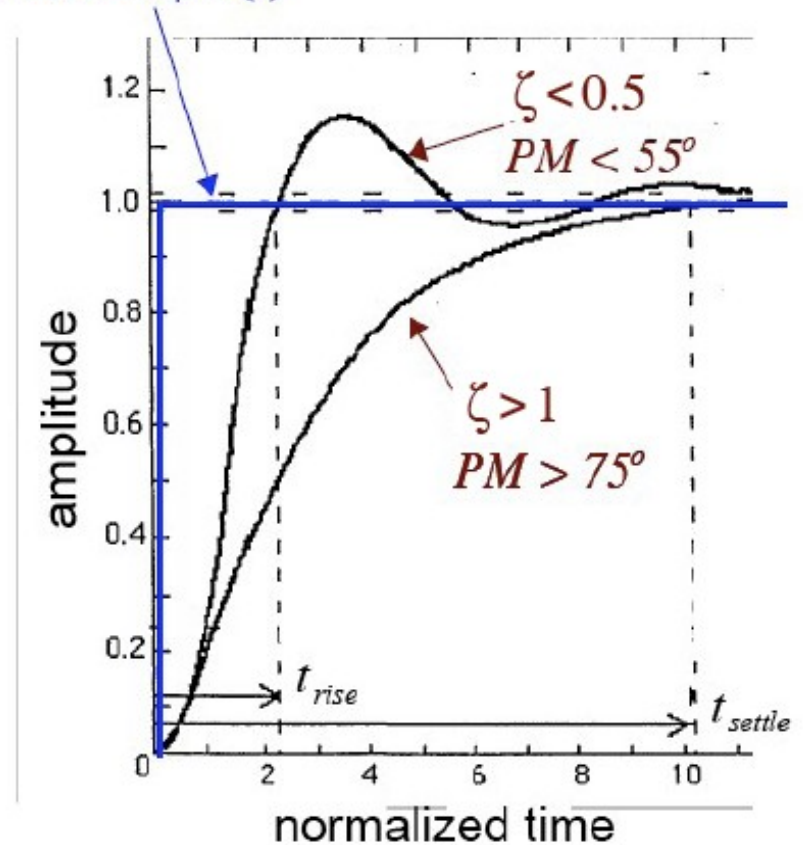

## Quick Review

3.  $GM = ?$  definition

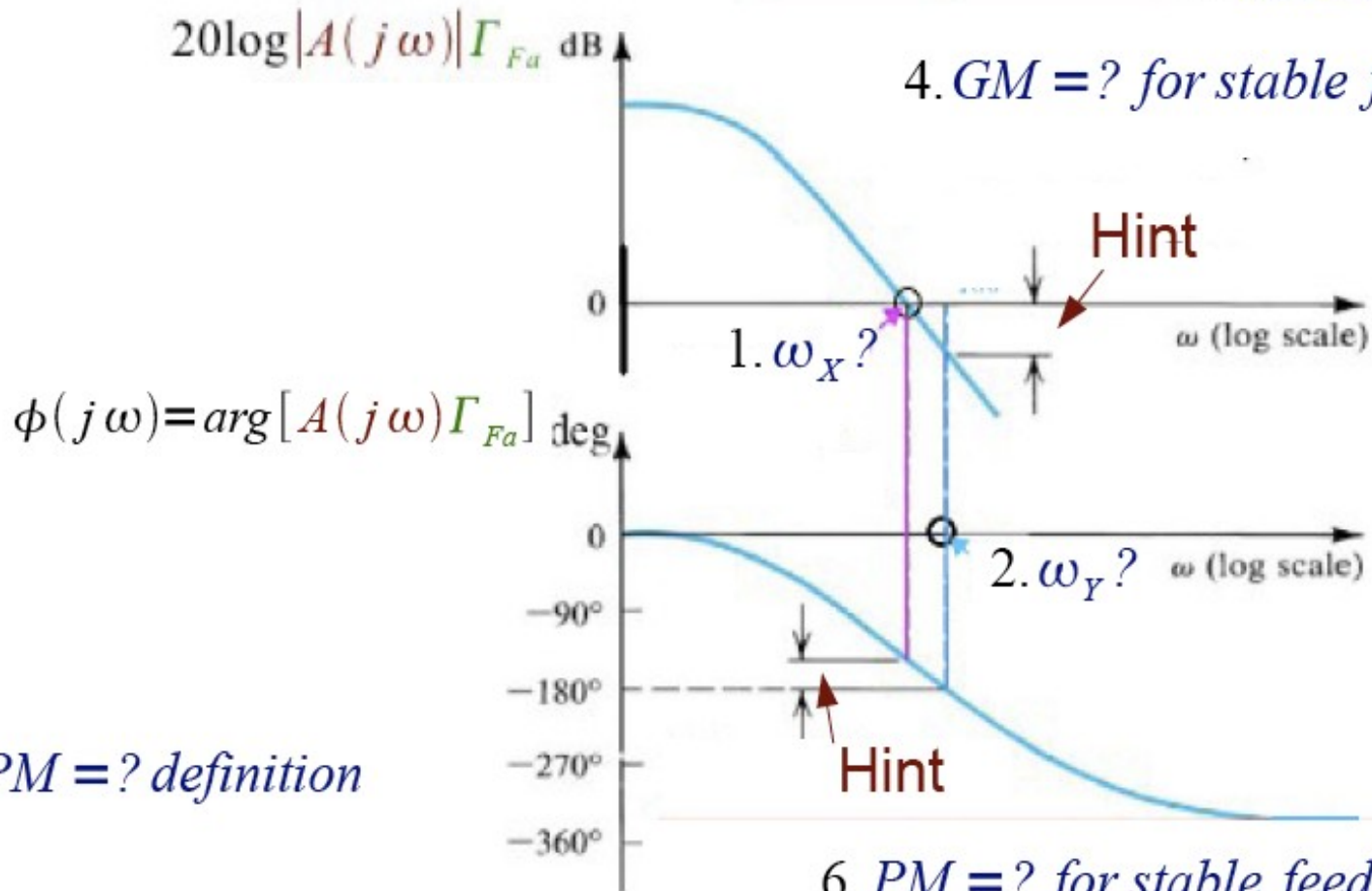4.  $GM = ?$  for stable feedback amplifier




5.  $PM = ?$  definition

6.  $PM = ?$  for stable feedback amplifier



## Quick Review

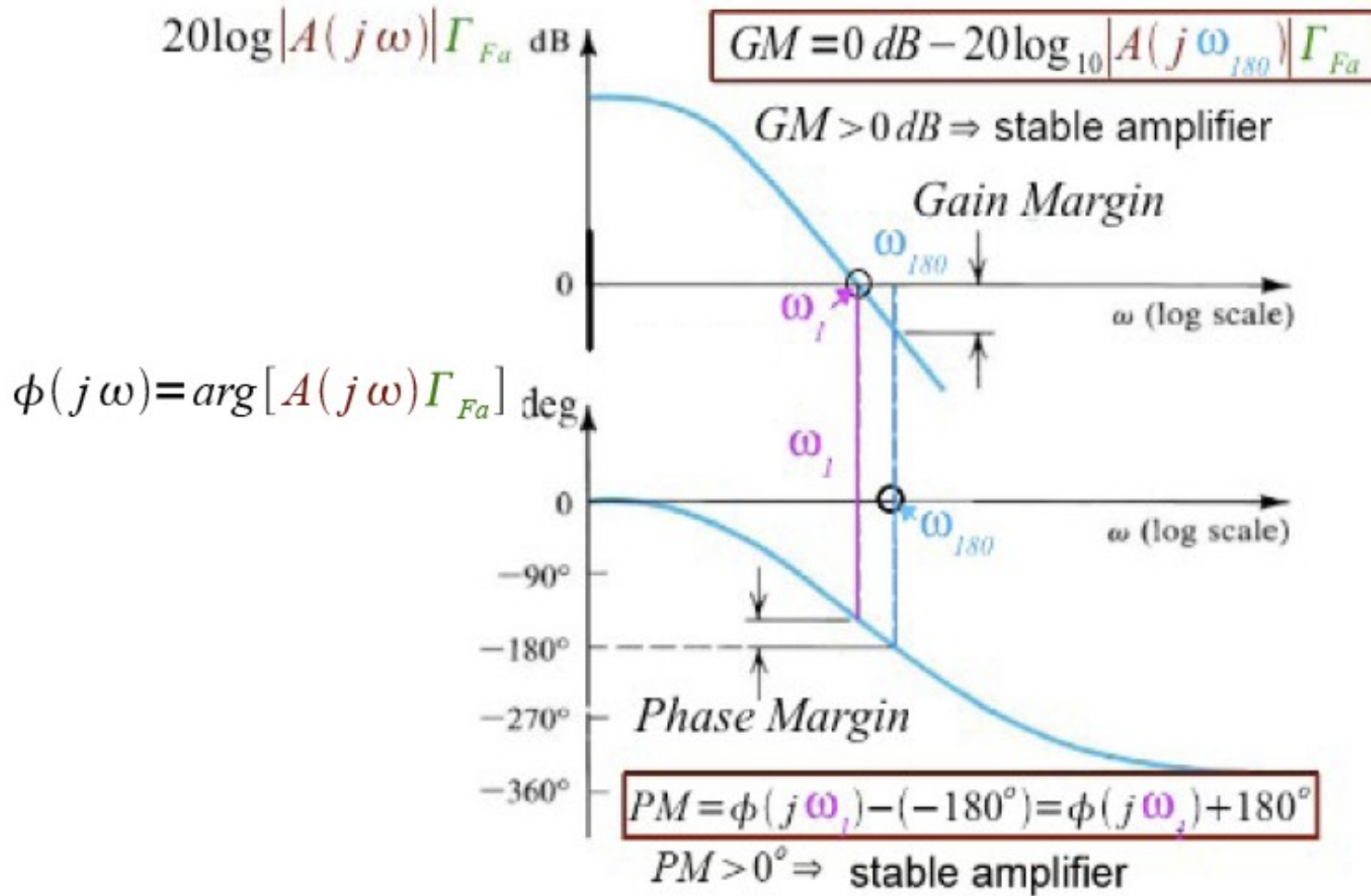

## Alternative Stability Analysis

1. Investigating stability for a variety of feedback gains  $\Gamma_F$  by constructing Bode plots for the loop-gain  $A(j\omega)\Gamma_F$  can be tedious and time consuming.

2. A simpler approach involves constructing Bode plots for  $A(j\omega)$  and  $\Gamma_F$  (or  $1/\Gamma_F$ ) separately.

$$20 \log |A(j\omega)\Gamma_F| = 20 \log |A(j\omega)| - 20 \log \frac{1}{\Gamma_F}$$


$20 \log \Gamma_F = -20 \log \frac{1}{\Gamma_F}$

when

$$20 \log |A(j\omega)| = 20 \log \frac{1}{\Gamma_F} \Rightarrow 20 \log |A(j\omega)\Gamma_F| = 0 \text{ dB} \Rightarrow \omega = \omega_1$$

gain cross-over frequency
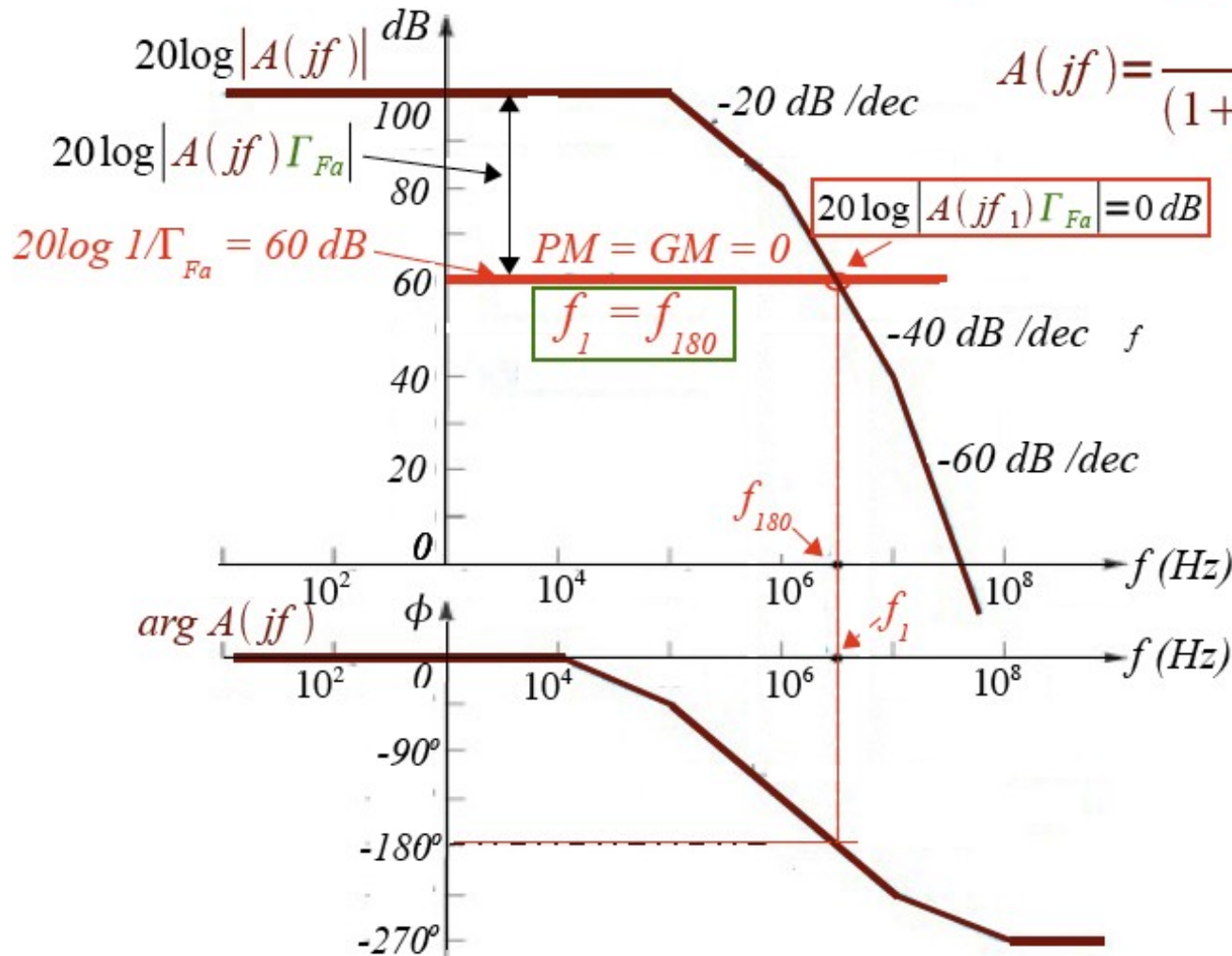
## Alternative Stability Analysis - cont.




$$A(jf) = \frac{10^5}{(1 + jf/10^5)(1 + jf/10^6)(1 + jf/10^7)}$$

### Basic Relation


$$\begin{aligned}
 &20 \log |A(jf) \Gamma_F| \\
 &= 20 \log |A(jf)| - 20 \log \frac{1}{\Gamma_F}
 \end{aligned}$$
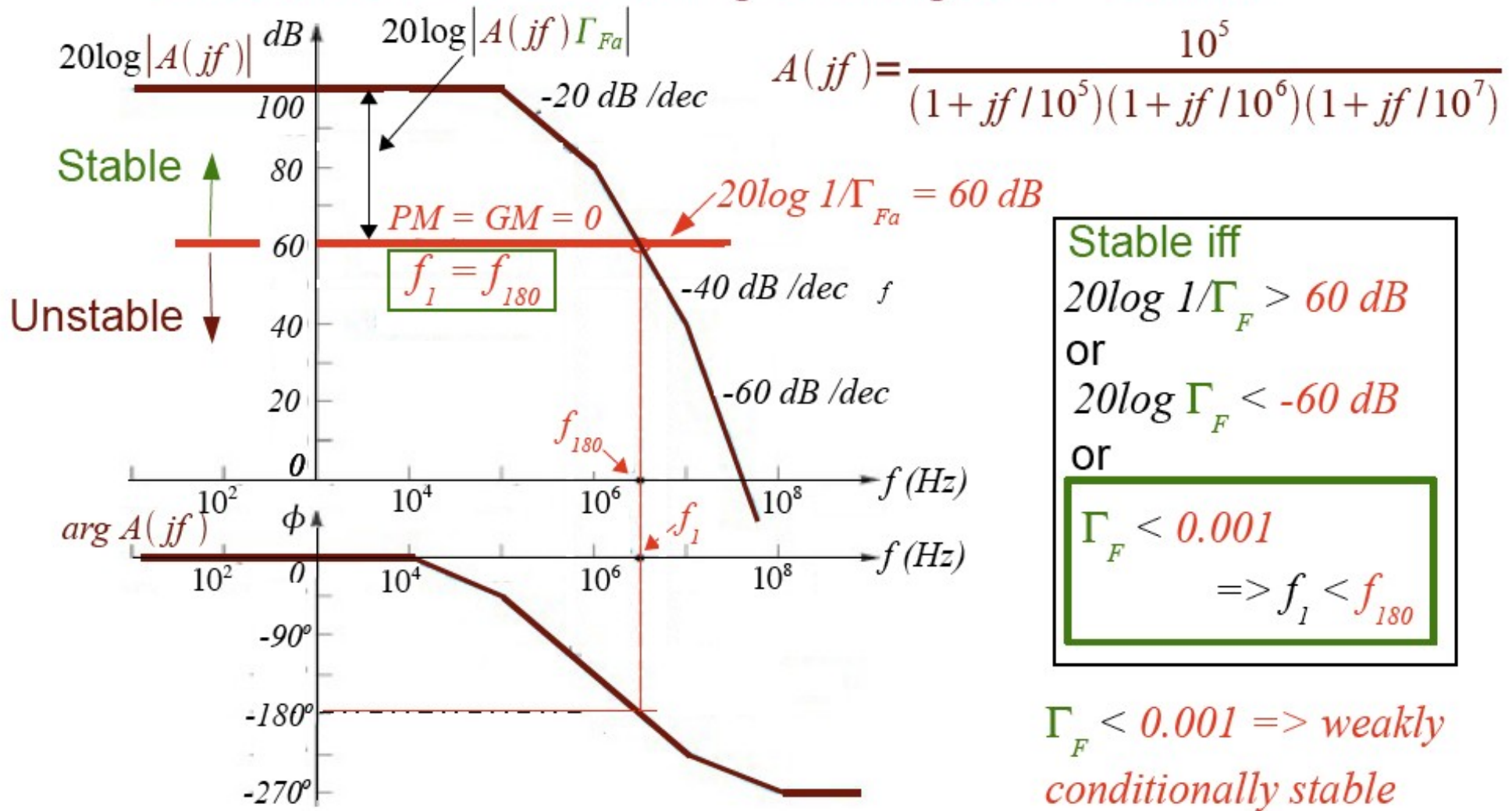
## Alternative Stability Analysis - cont.




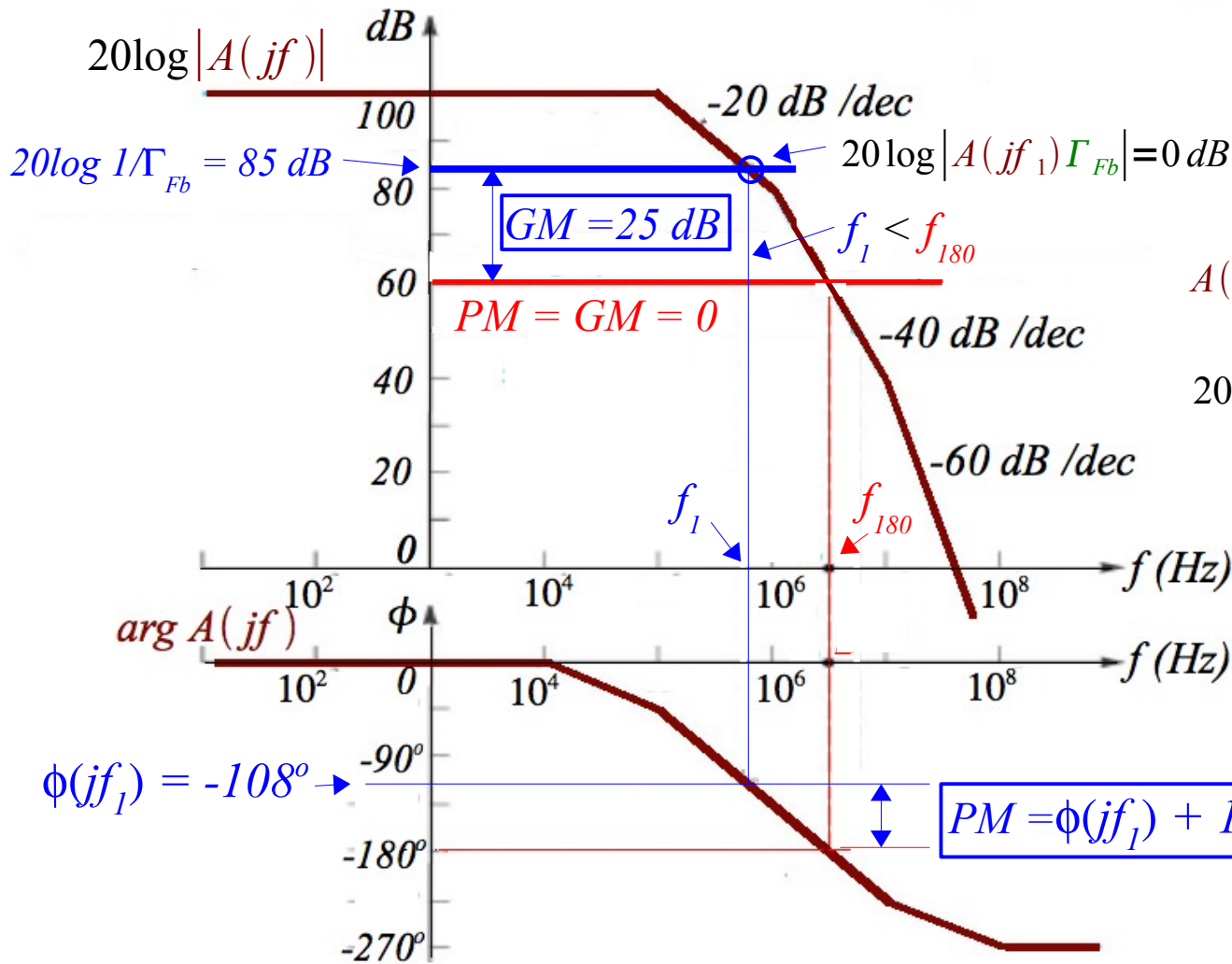
## Alternative Stability Analysis - cont.




$$A(jf) = \frac{10^5}{(1 + jf/10^5)(1 + jf/10^6)(1 + jf/10^7)}$$

$$20\log|A(jf)\Gamma_F| = 20\log|A(jf)| - 20\log\frac{1}{\Gamma_{Fb}}$$


$$\phi(jf_1) = \arg[A(jf_1)\Gamma_{Fb}] > -180^\circ$$

$PM = \phi(jf_1) + 180^\circ = 72^\circ$  *stable!*

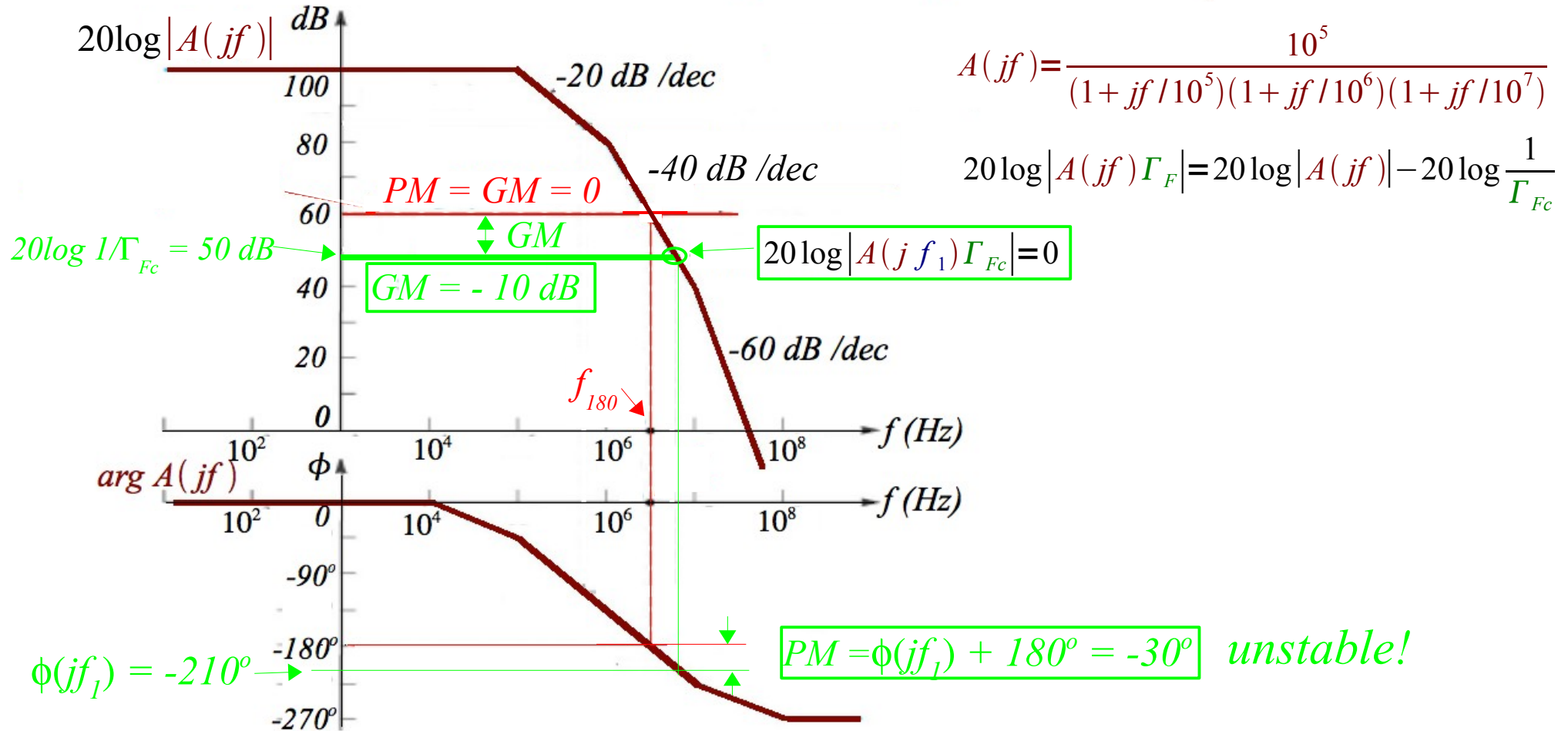
## Alternative Stability Analysis - cont.


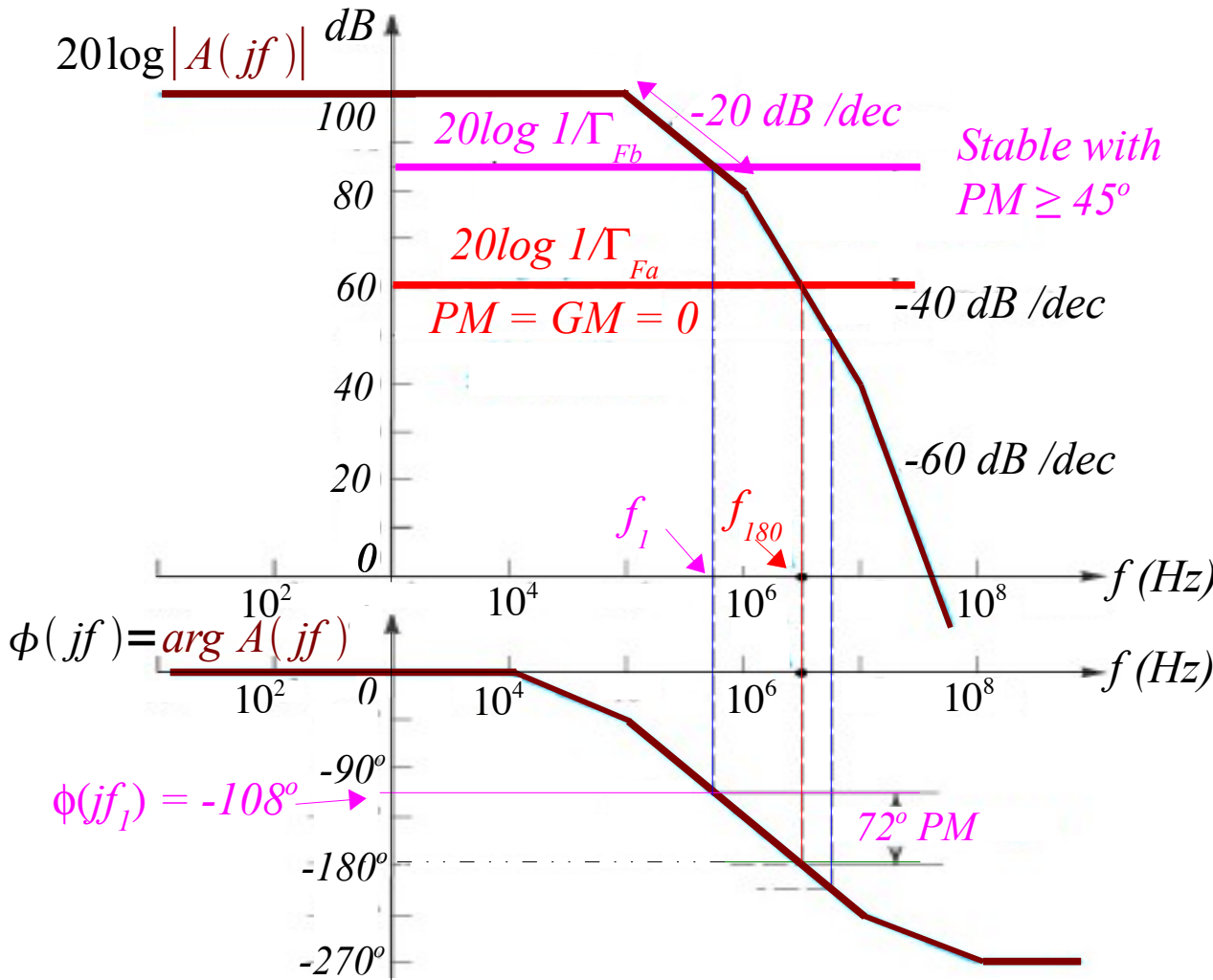
## Alternative Stability Analysis - cont.



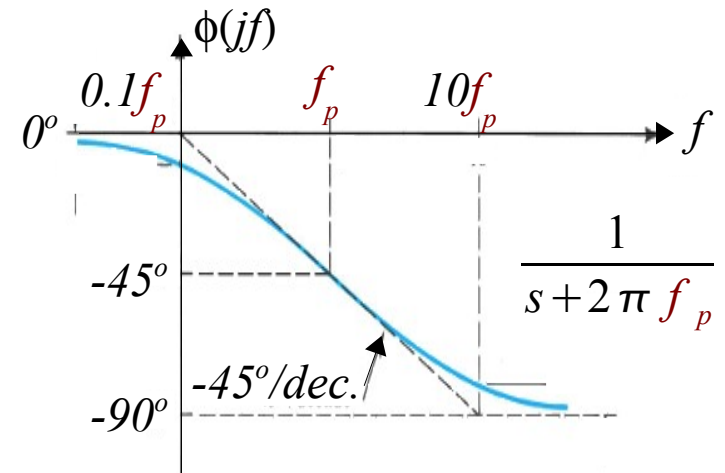
$$A(jf) = \frac{10^5}{(1 + jf/10^5)(1 + jf/10^6)(1 + jf/10^7)}$$



Hence, over  $-20\text{dB/dec.}$   
 Segment of  $20 \log |A(jf)|$   
 $-45^\circ \geq \phi(jf) \geq -135^\circ$   
 $\Rightarrow PM = \phi(jf) + 180^\circ \geq 45^\circ$
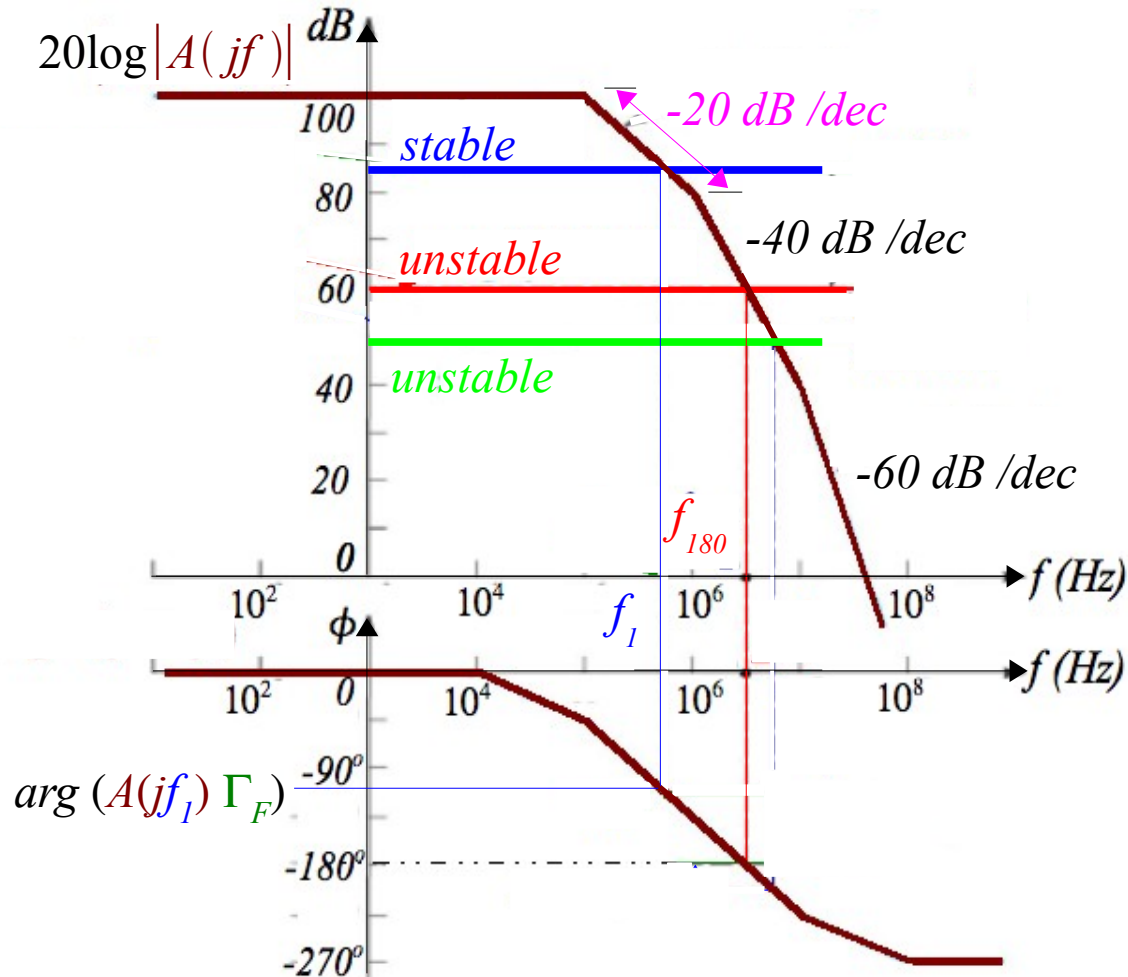
## Alternative Stability Analysis - cont.



$$A(jf) = \frac{10^5}{(1 + jf/10^5)(1 + jf/10^6)(1 + jf/10^7)}$$


$$20 \log |A(jf) \Gamma_F| = 20 \log |A(jf)| - 20 \log \frac{1}{\Gamma_F}$$

“Rule of Thumb” – Closed-loop amplifier will be stable if the  $20 \log 1/\Gamma_F$  line intersects the  $20 \log |A(jf)|$  curve on the  $-20 \text{ dB/dec}$  segment.

Using “Rule of Thumb”:

$$\arg(A(jf_1) \Gamma_F) > -135^\circ$$

$$\Rightarrow \boxed{PM \geq 45^\circ}$$

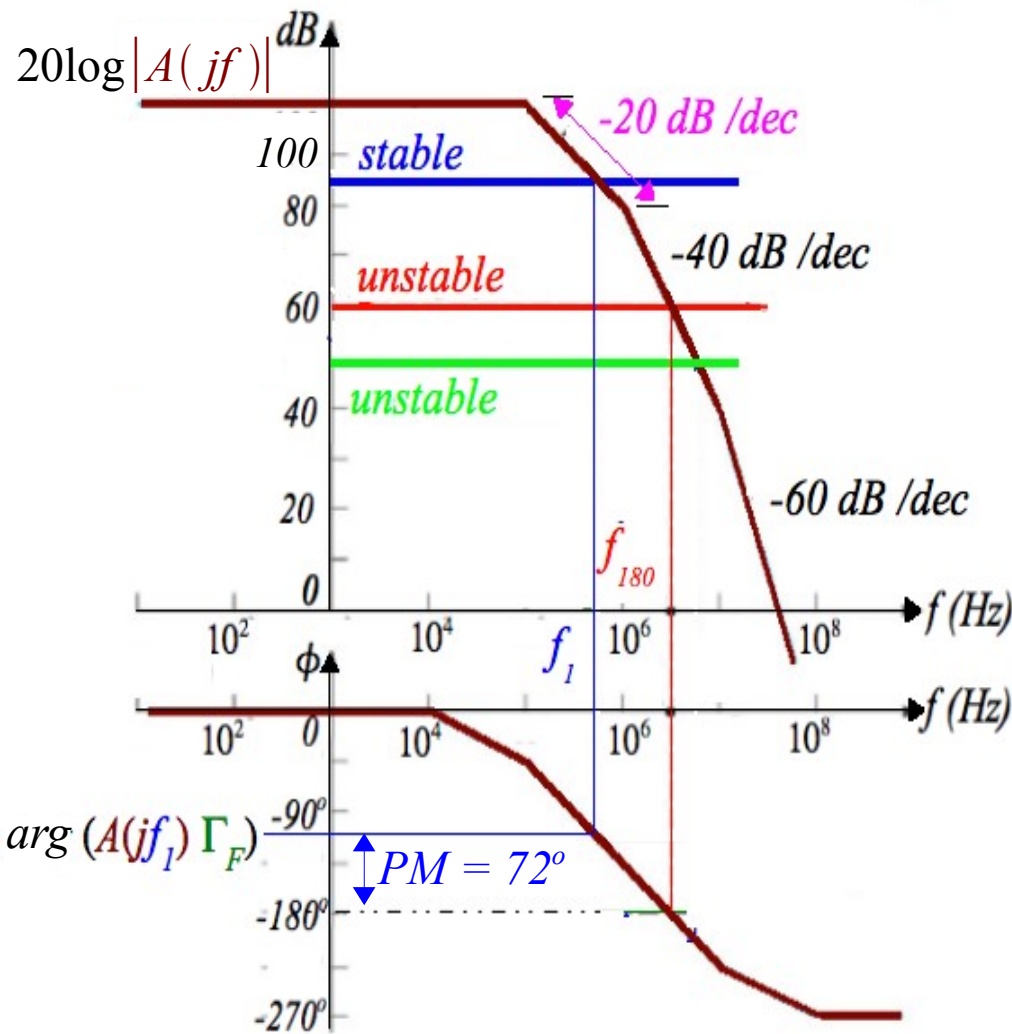

## Rate of Closure (RC)

$$RC = \text{slope } A(j2\pi f)_{dB/dec} - \text{slope} \left( \frac{1}{\Gamma_F} \right)_{dB/dec}$$

$$RC = -20 \text{ dB/dec} - 0 \text{ dB/dec} = -20 \text{ dB/dec}$$

$$RC = -40 \text{ dB/dec} - 0 \text{ dB/dec} = -40 \text{ dB/dec}$$

$$RC = -40 \text{ dB/dec} - 0 \text{ dB/dec} = -40 \text{ dB/dec}$$


From previous slide:

“Rule of Thumb” – Closed-loop amplifier will be stable if  $20\log 1/\Gamma_F$  line intersects  $20\log|A(jf)|$  curve on the  $-20 \text{ dB/dec}$  segment.

“Equivalent Rule of Thumb” – Closed-loop amplifier will be stable if

$$RC = -20 \text{ dB/dec}$$

## Frequency Dependent Feedback

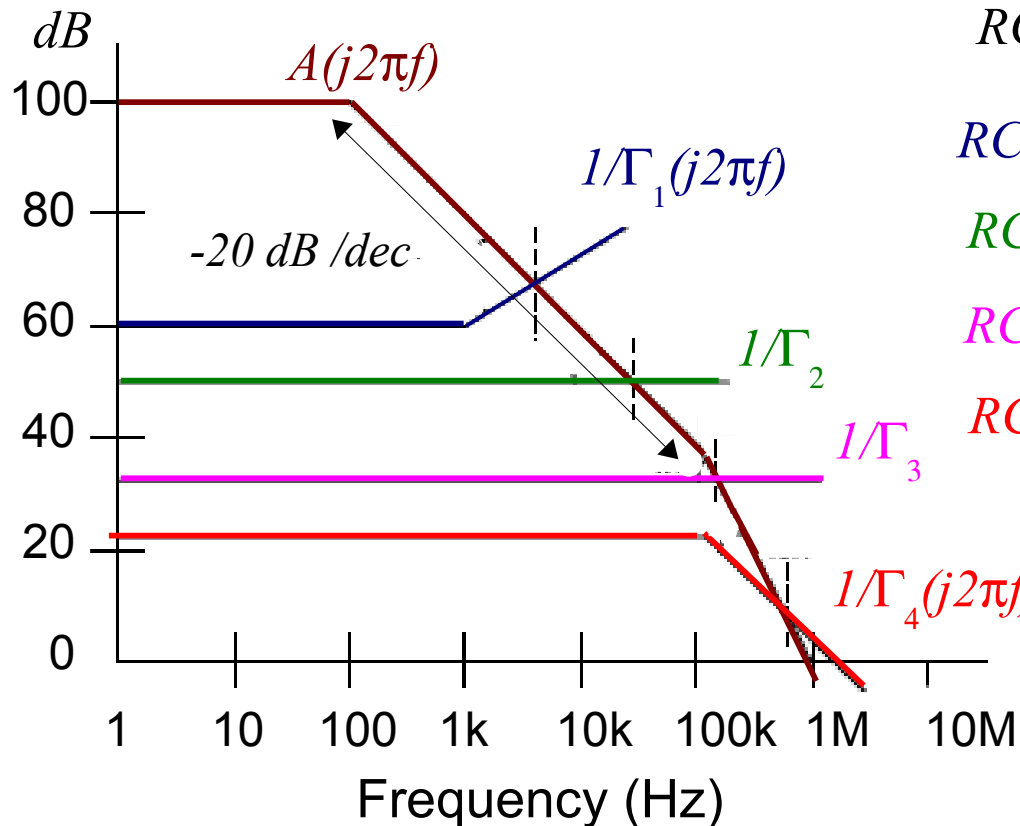

$$RC = \text{slope } A(j2\pi f)_{\text{dB/dec}} - \text{slope} \left( \frac{1}{\Gamma_F} \right)_{\text{dB/dec}}$$

$$RC_1 = -20 \text{ dB/dec} - (+20 \text{ dB/dec}) = -40 \text{ dB/dec}$$

$$RC_2 = -20 \text{ dB/dec} - (0 \text{ dB/dec}) = -20 \text{ dB/dec}$$

$$RC_3 = -40 \text{ dB/dec} - (0 \text{ dB/dec}) = -40 \text{ dB/dec}$$

$$RC_4 = -40 \text{ dB/dec} - (-20 \text{ dB/dec}) = -20 \text{ dB/dec}$$

“Equivalent Rule of Thumb” –  
Closed-loop amplifier will be  
stable with  $PM \geq 45^\circ$  if

$$RC = -20 \text{ dB/dec}$$

## Quick Review

$$A_{cl}(s) = \frac{A(s)}{1 + \Gamma_F A(s)}$$


### Gain & Phase Margins

A. What are the two methods for determining stability of closed loop amplifier?

B. What is the “Rule of thumb”?

## Quick Review cont.

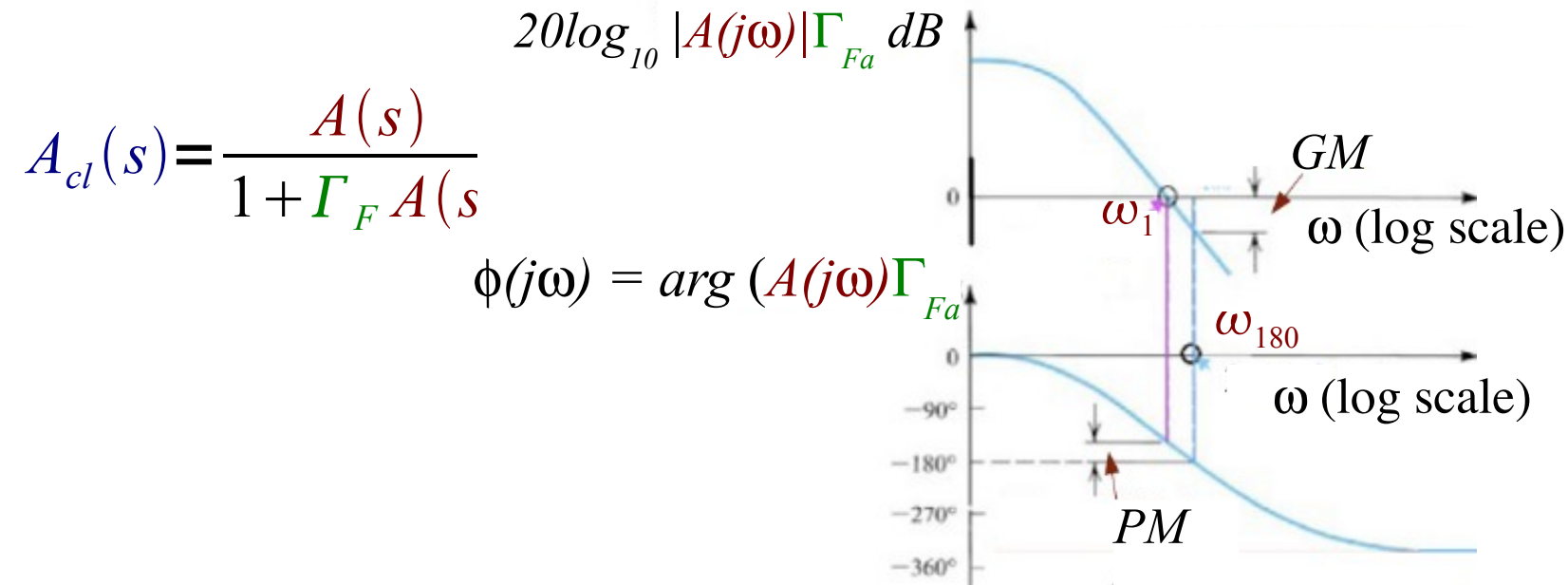A. What are the two methods for determining stability of closed loop amplifier?



$$(1) \quad A(j\omega) \Gamma_F = -1 = 1 e^{j\pi \pm 2k\pi}$$


$$GM = 0 \text{ dB} - 20 \log_{10} |A(j\omega_{180})| \Gamma_{Fa} > 0$$

$$PM = \arg(A(j\omega_1) \Gamma_{Fa}) - (-180^\circ)$$

## Quick Review cont.

$$A_{cl}(s) = \frac{A(s)}{1 + \Gamma_F A(s)}$$

$$\phi(j\omega) = \arg(A(j\omega))$$

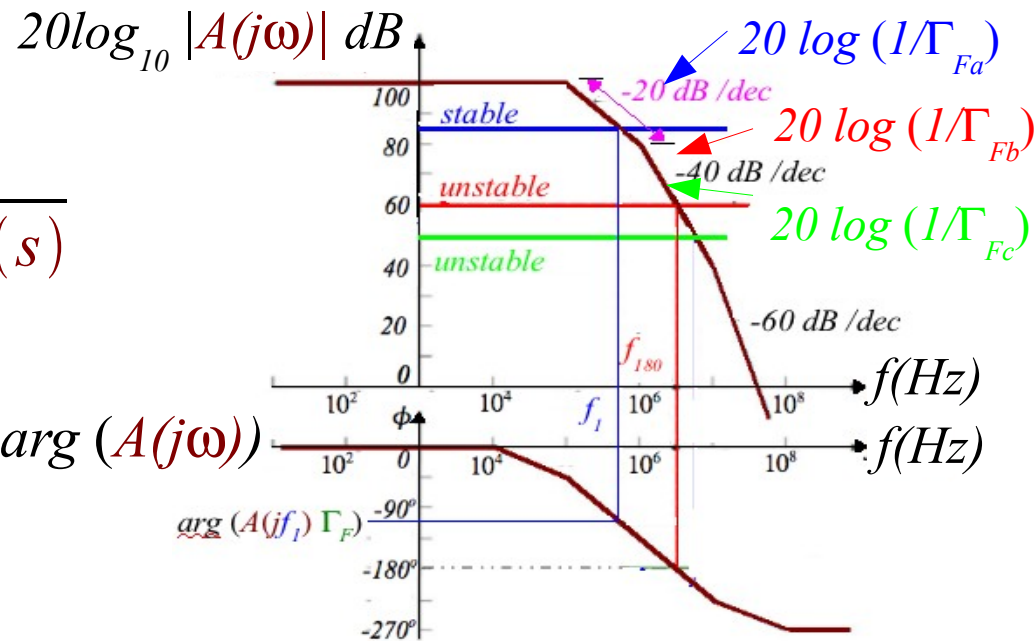


$$(2) \quad 20 \log |A(j\omega) \Gamma_F| = 20 \log |A(j\omega)| - 20 \log \frac{1}{\Gamma_F} \quad \text{where } \Gamma_F = \Gamma_{Fa}$$

$$20 \log |A(j\omega_1)| = 20 \log \frac{1}{\Gamma_{Fa}}$$

## Quick Review cont.


“Rule of Thumb” – Closed -loop amplifier will be stable if the  $20\log 1/\Gamma_F$  line intersects the  $20\log|A(jf)|$  curve on the  $-20\text{ dB/dec}$  segment and  $PM \geq 45^\circ$ .

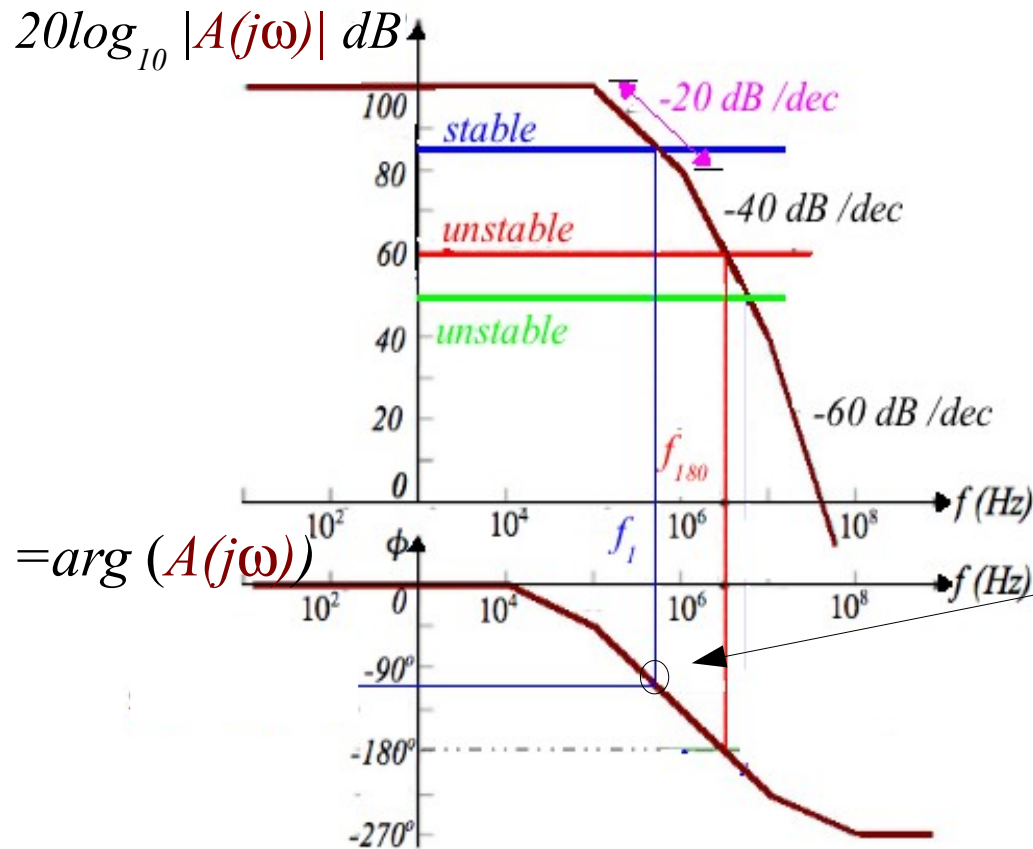

over  $-20\text{ dB/dec. segment}$   
 $-45^\circ \geq \arg(A(jf_1)\Gamma_F) \geq -135^\circ$   
 $\Rightarrow PM = \phi(jf) + 180^\circ \geq 45^\circ$



# Frequency Compensation

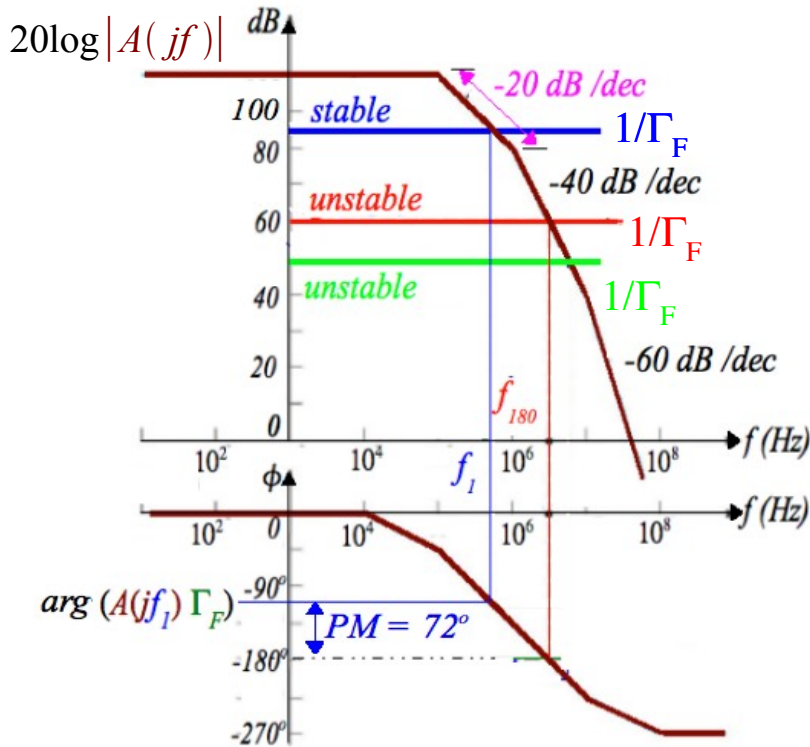

“Rule of Thumb” – Closed-loop amplifier will be stable if the  $20\log 1/\Gamma_F$  line intersects the  $20\log|A(jf)|$  curve on the -20 dB/dec segment.

Using “Rule of Thumb”:

$$\arg(A(jf_1)\Gamma_F) > -135^\circ$$



$$\Rightarrow PM \geq 45^\circ$$

Ex: LM 741 op amp is frequency compensated to be stable with  $60^\circ PM$  for  $20\log|A_{cl}(jf)| = 20\log 1/\Gamma_F = 0\text{ dB}$ .

frequency compensation – modifying the open-loop  $A(s)$  so that the closed-loop  $A_{cl}(s)$  is stable for any desired value of  $|A_{cl}(jf)|$  by extending the -20 dB/dec segment.

desired implementation - minimum on-chip or external components.

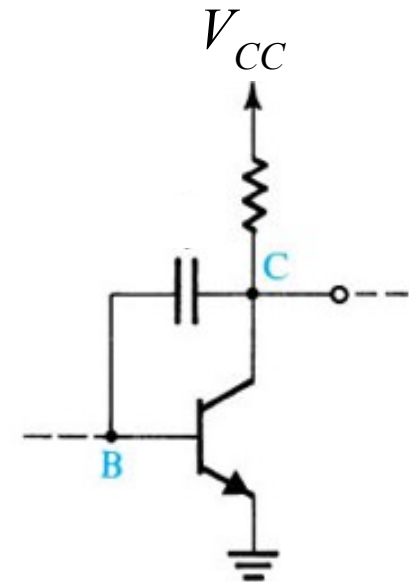
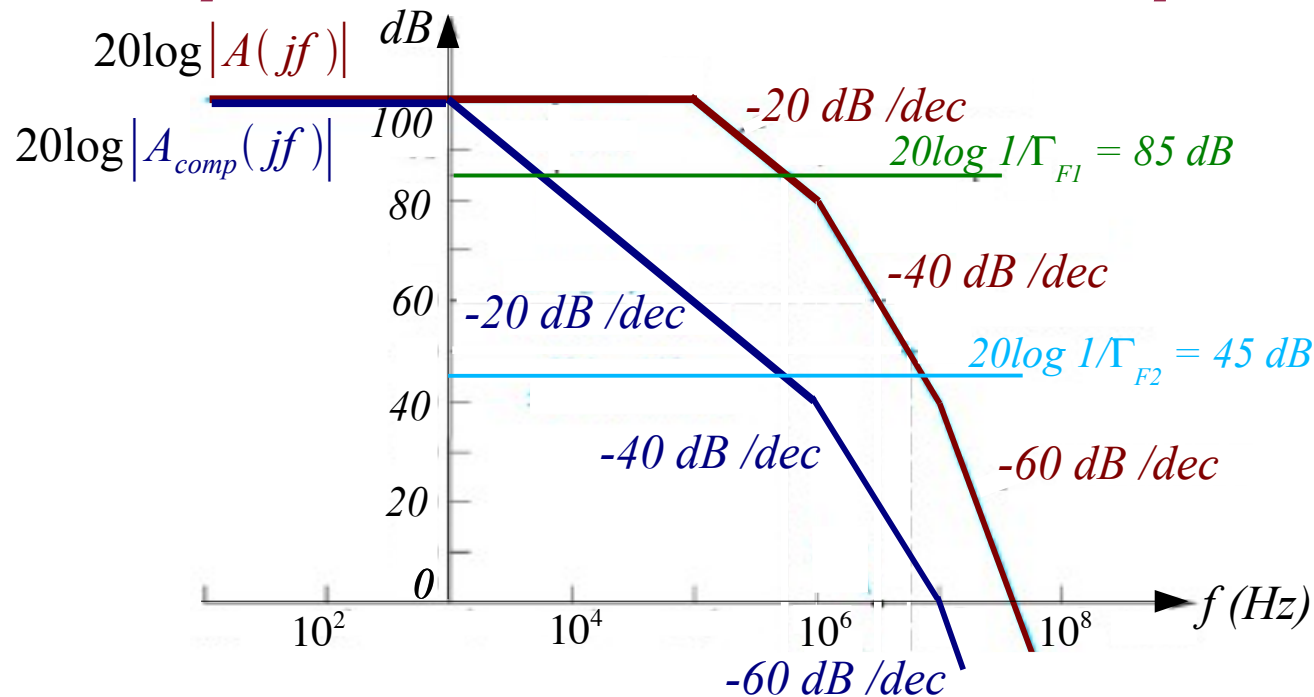
## Compensation – What if 1st pole is shifted lower?



$$A(jf) = \frac{10^5}{(1 + jf/10^5)(1 + jf/10^6)(1 + jf/10^7)}$$

$$A_{comp}(jf) \approx \frac{10^5}{(1 + jf/10^3)(1 + jf/10^6)(1 + jf/10^7)}$$
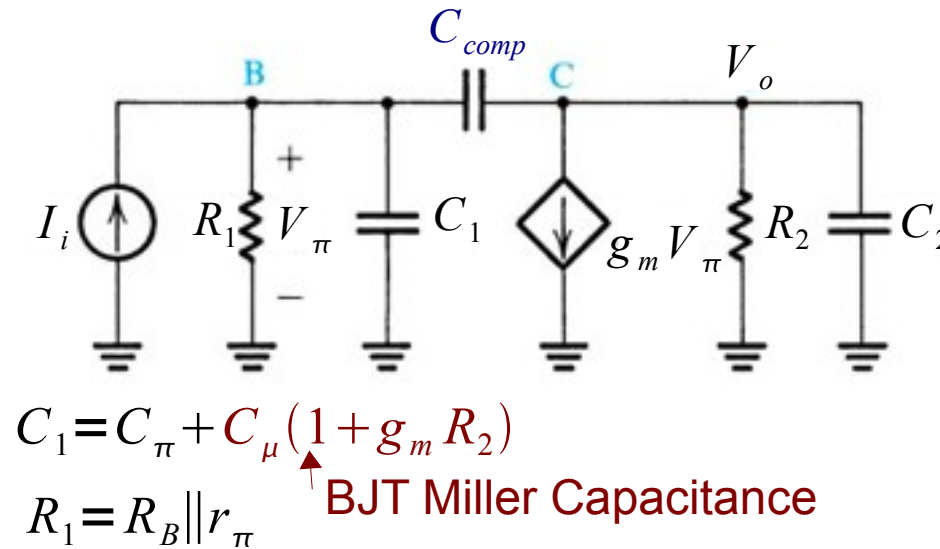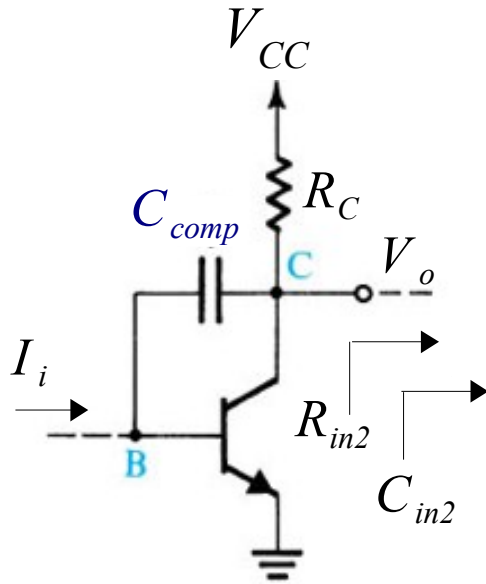
## Frequency Compensation Using Miller Effect



with  $C_{comp} = 0$

$$\omega_{p1} = \frac{1}{R_1 C_1}$$

$$\omega_{p2} = \frac{1}{R_2 C_2}$$

$$R_2 = R_C \parallel r_o \parallel R_{in2}$$

$$C_2 = C_\mu + C_{in2}$$

$$\frac{V_o}{I_i} = \frac{(s C_{comp} - g_m) R_1 R_2}{1 + s [C_1 R_1 + C_2 R_2 + C_{comp} (g_m R_1 R_2 + R_1 + R_2)] + s^2 [C_1 C_2 + C_{comp} (C_1 + C_2)] R_1 R_2}$$

$$= \frac{(s C_{comp} - g_m) R_1 R_2}{\left(1 + \frac{s}{\omega_{plc}}\right) \left(1 + \frac{s}{\omega_{p2c}}\right)} = \frac{(s C_{comp} - g_m) R_1 R_2}{1 + s \left(\frac{1}{\omega_{plc}} + \frac{1}{\omega_{p2c}}\right) + \frac{s^2}{\omega_{plc} \omega_{p2c}}}$$

where  $\omega_{p2c} \gg \omega_{plc}$



# Compensation Using Miller Effect - cont.

$$\frac{V_o}{I_i} = \frac{(sC_{comp} - g_m) R_1 R_2}{1 + s\left(\frac{1}{\omega_{plc}} + \frac{1}{\omega_{p2c}}\right) + \frac{s^2}{\omega_{plc} \omega_{p2c}}} \approx \frac{(sC_{comp} - g_m) R_1 R_2}{1 + s\left(\frac{1}{\omega_{plc}}\right) + s^2\left(\frac{1}{\omega_{plc} \omega_{p2c}}\right)}$$

assumption  
 If  $\omega_{p2c} \gg \omega_{plc}$   
 pole-splitting

and

$$\frac{V_o}{I_i} = \frac{(sC_{comp} - g_m) R_1 R_2}{1 + s[C_1 R_1 + C_2 R_2 + C_{comp}(g_m R_1 R_2 + R_1 + R_2)] + s^2[C_1 C_2 + C_{comp}(C_1 + C_2)] R_1 R_2}$$

$$\omega_{plc} = \frac{1}{C_1 R_1 + C_2 R_2 + C_{comp}(g_m R_1 R_2 + R_1 + R_2)} \approx \frac{1}{C_{comp} g_m R_2 R_1}$$

Compensation Miller Capacitance

$$\omega_{p2c} = \frac{\omega_{plc} \omega_{p2c}}{\omega_{plc}} = \frac{C_1 R_1 + C_2 R_2 + C_{comp}(g_m R_1 R_2 + R_1 + R_2)}{[C_1 C_2 + C_{comp}(C_1 + C_2)] R_1 R_2} \approx \frac{C_{comp} g_m R_1 R_2}{C_{comp}(C_1 + C_2) R_1 R_2} \approx \frac{g_m}{C_1 + C_2}$$

If  $C_{comp}(C_1 + C_2) \gg C_1 C_2$

## Compensation Using Miller Effect - cont.

$$A(jf) = \frac{10^5}{\left(1 + \frac{jf}{10^5}\right)\left(1 + \frac{jf}{10^6}\right)\left(1 + \frac{jf}{10^7}\right)} = \frac{10^5}{\left(1 + \frac{jf}{f_{p1}}\right)\left(1 + \frac{jf}{f_{p2}}\right)\left(1 + \frac{jf}{f_{p3}}\right)}$$

$$f_{p1} = \frac{\omega_{p1}}{2\pi} = \frac{1}{R_1 C_1}$$

$$f_{p2} = \frac{\omega_{p2}}{2\pi} = \frac{1}{R_2 C_2}$$

Using Miller effect compensation:  $f_{p1} \rightarrow f_{p1c} \ll f_{p1}$  and  $f_{p2} \rightarrow f_{p2c} \gg f_{p2}$  (pole-splitting)

Also  $f_{p3}$ , determined by another stage, is unaffected by the compensation  $\Rightarrow f_{p3c} = f_{p3}$

$$A_{comp}(jf) = \frac{10^5}{\left(1 + \frac{jf}{f_{p1c}}\right)\left(1 + \frac{jf}{f_{p2c}}\right)\left(1 + \frac{jf}{f_{p3}}\right)}$$

$$f_{p1c} = \frac{\omega_{p1c}}{2\pi} \approx \frac{1}{2\pi [C_{comp} g_m R_1 R_2]}$$

$$f_{p2c} = \frac{\omega_{p2c}}{2\pi} \approx \frac{g_m}{2\pi [C_1 + C_2]}$$

## Miller Compensation Example

Given:

$$A(jf) = \frac{10^5}{\left(1 + \frac{jf}{R_1 C_1}\right) \left(1 + \frac{jf}{R_2 C_2}\right) \left(1 + \frac{jf}{10^7}\right)} = \frac{10^5}{\left(1 + \frac{jf}{f_{p1}}\right) \left(1 + \frac{jf}{f_{p2}}\right) \left(1 + \frac{jf}{10^7}\right)} = \frac{10^5}{\left(1 + \frac{jf}{10^5}\right) \left(1 + \frac{jf}{10^6}\right) \left(1 + \frac{jf}{10^7}\right)}$$

where  $C_1 = 20 \text{ pF}$ ,  $C_2 = 5 \text{ pF}$ ,  $g_m = 40 \text{ mS}$ ,  $R_1 = 100/2\pi \text{ k}\Omega$  and  $R_2 = 200/2\pi \text{ k}\Omega$


Design Objective: determine  $C_{comp}$  s.t.  $f_{p1c} = 100 \text{ Hz}$  and compute  $f_{p2c}$ .

$$A_{comp}(jf) = \frac{10^5}{\left(1 + \frac{jf}{10^2}\right) \left(1 + \frac{jf}{f_{p2c}}\right) \left(1 + \frac{jf}{10^7}\right)} = \frac{10^5}{\left(1 + \frac{jf}{f_{p1c}}\right) \left(1 + \frac{jf}{f_{p2c}}\right) \left(1 + \frac{jf}{10^7}\right)}$$

$$f_{p1c} = 100 \text{ Hz} \approx \frac{1}{2\pi [C_{comp} g_m R_1 R_2]} = \frac{(2\pi)^2}{2\pi [C_{comp} (40 \times 10^{-3}) (10^5) (2 \times 10^5)]} \Rightarrow C_{comp} = 78.5 \text{ pF}$$

$$f_{p2c} = \frac{g_m}{2\pi (C_1 + C_2)} \approx 61 \text{ MHz}$$
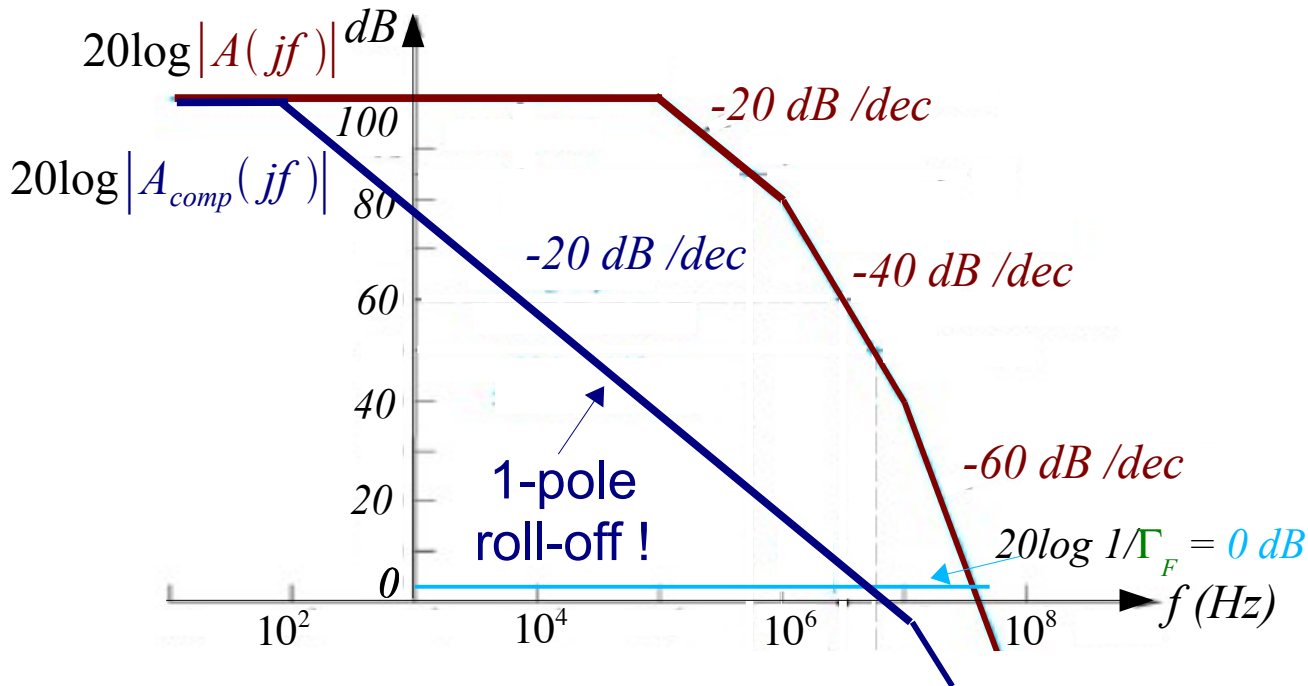
## Compensation Using Miller Effect - cont.



$$A_{comp}(jf)$$

$$PM > 45^\circ \text{ for } |A_{cl}(jf)| = \frac{1}{\Gamma_F} \geq 1$$

$$A(jf) = \frac{10^5}{\left(1 + \frac{jf}{10^5}\right)\left(1 + \frac{jf}{10^6}\right)\left(1 + \frac{jf}{10^7}\right)}$$

$$A_{comp}(jf) \approx \frac{10^5}{\left(1 + \frac{jf}{10^2}\right)\left(1 + \frac{jf}{6.1 \cdot 10^7}\right)\left(1 + \frac{jf}{10^7}\right)}$$

## *Summary*

Feedback has many desirable features, but it can create unexpected - undesired results if the full frequency-dependent nature (phase-shift with frequency) of the feedback circuit is not taken into account.

Feedback can be used to convert a well-behaved stable circuit into an oscillator. Sometimes, due to parasitics, feedback in amplifiers results in unexpected oscillations.

The root-locus method was used to show how feedback can create the conditions for oscillation and instability.