



## ***Class AB Output Stage***

- Class AB amplifier Operation
- Multisim Simulation - VTC
- Class AB amplifier biasing
- Widlar current source
- Multisim Simulation - Biasing



## Class AB Operation

**Class AB – Amplifier** transistor conducts for positive  $v_I$  swing + part of negative  $v_I$  swing

s.t.:

$$v_I + V_B \geq 0.7V \quad \text{where} \quad V_B < \max(v_I)$$
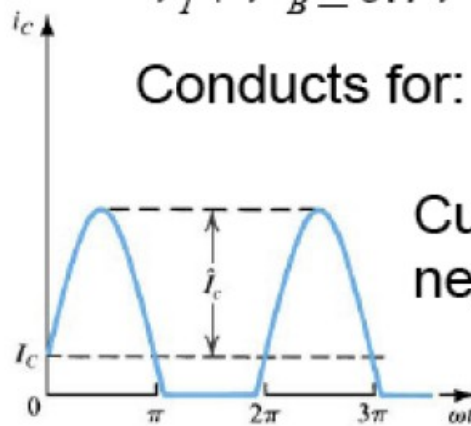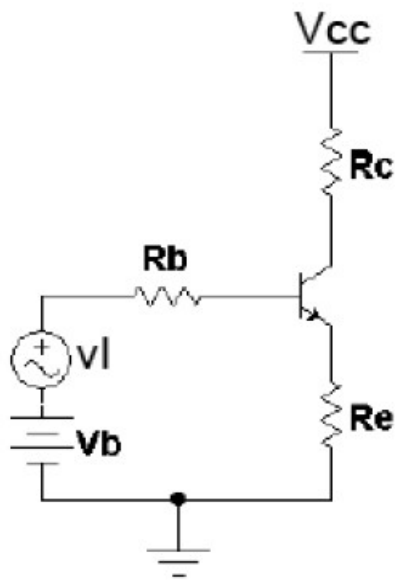
$$\text{Conducts for:} \quad v_I \geq 0.7 - V_B$$



Cut-off for rest of negative  $v_I$  swing:


Transistor cut-off ( $i_C = 0$ ) if:

$$v_I + V_B < 0.7V$$

NOTE: 1. when  $v_I = 0$ ,  $i_C = I_C$

2. a 2<sup>nd</sup> class AB BJT is needed to conduct for interval slightly larger than the negative  $v_I$  cycle.

## Basic Class AB Amplifier Circuit

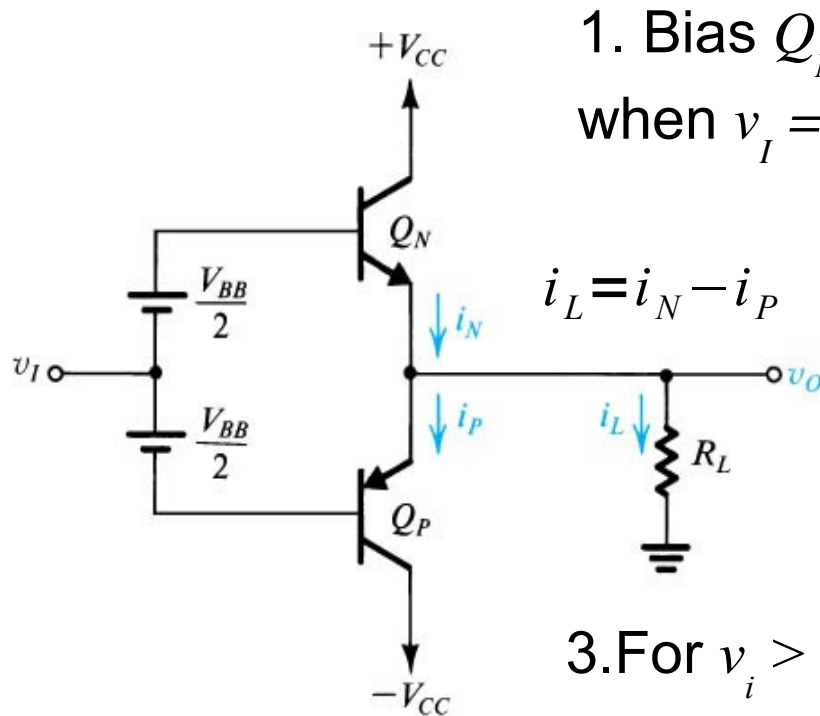

1. Bias  $Q_N$  and  $Q_P$  into slight conduction (fwd. act.)  
when  $v_I = 0$ :  $i_N = i_P$ .

2 Ideally  $Q_N$  and  $Q_P$  are:

- Matched (unlikely with discrete transistors and challenging in IC).
- Operate at same ambient temperature.


3. For  $v_i > 0$ :  $i_N > i_P$  i.e.  $Q_N$  most cond. (like Class B).

4. For  $v_i < 0$ :  $i_P > i_N$  i.e.  $Q_P$  most cond. (like Class B).

**NOTE. This is base-voltage biasing with all its stability problems!**

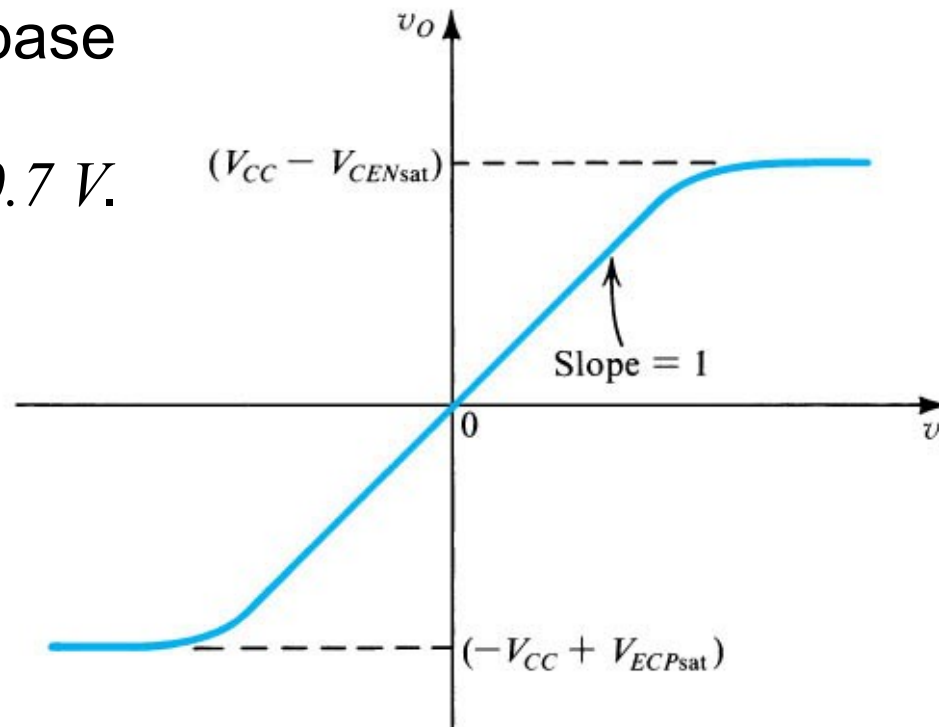
## Class AB VTC Plot

Requires the two DC base voltage sources to be matched and  $V_{BB}/2 = 0.7 V$ .




Amplitude: 20 V<sub>p</sub>  
Frequency: 1 kHz

## Class AB VTC Simulation

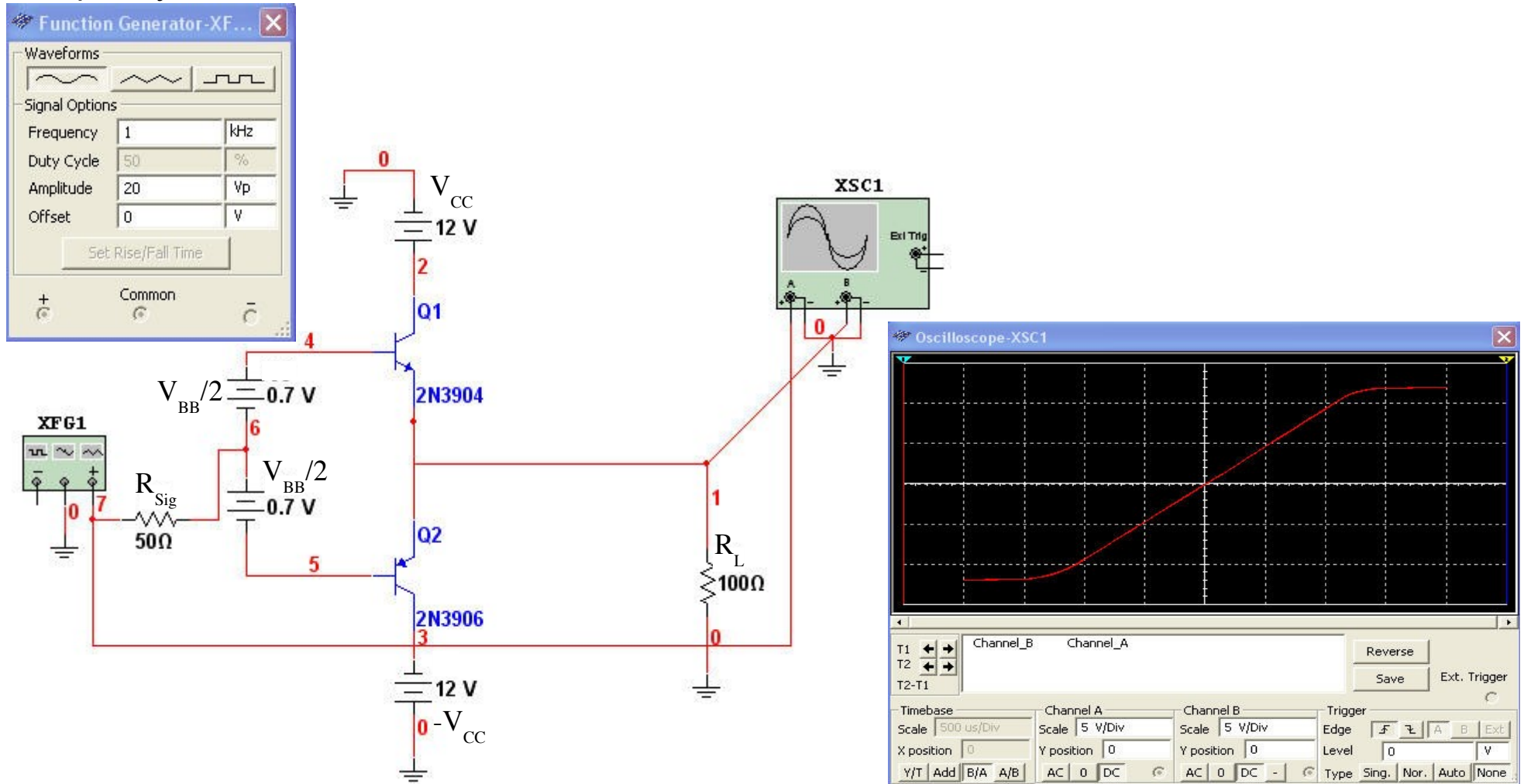


## Class AB VTC Simulation - cont.



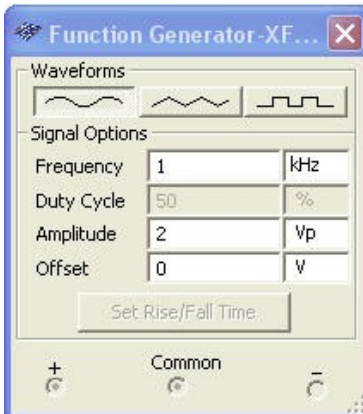


Amplitude: 2 V<sub>p</sub>  
Frequency: 1 kHz

$$\frac{V_{BB}}{2} = 0.5 V$$

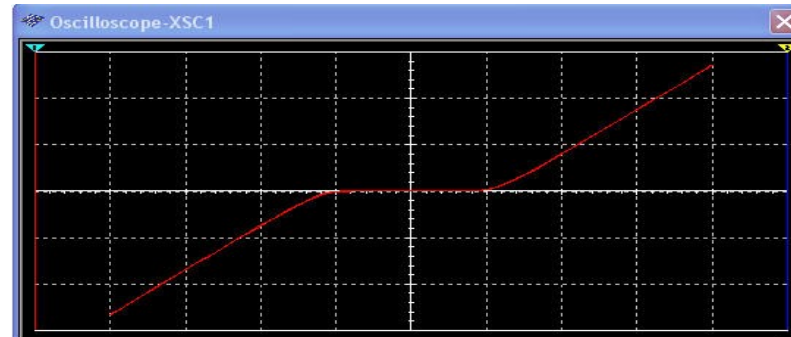


$$\frac{V_{BB}}{2} = 0.1 V$$

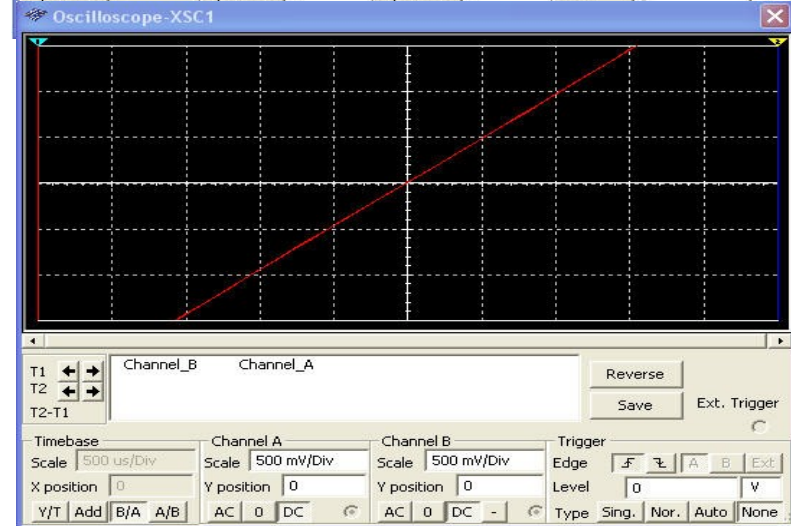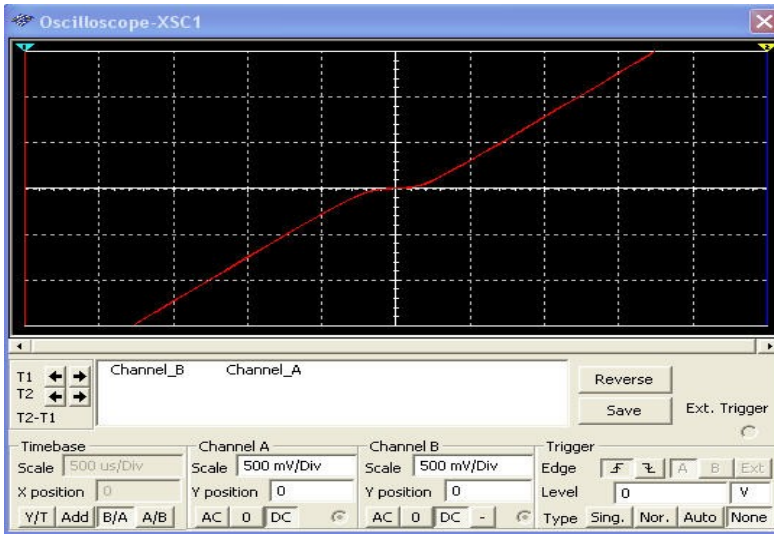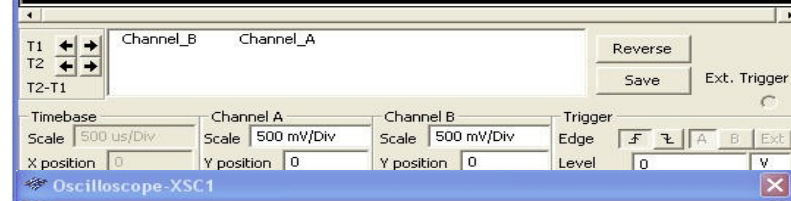

$$\frac{V_{BB}}{2} = 0.7 V$$

## Class AB Circuit Operation - cont.

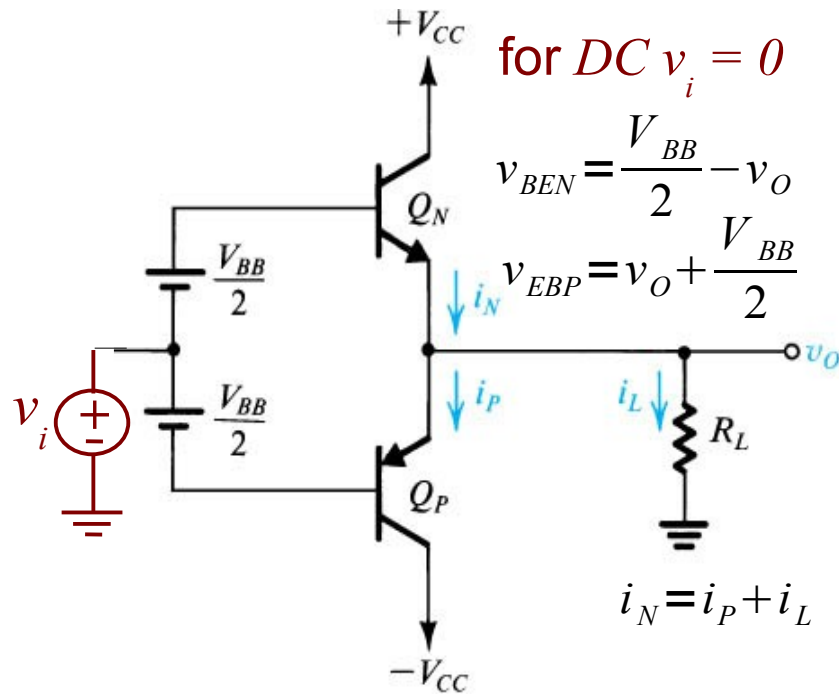

Output voltage for  $v_i \neq 0$ :

$$\text{for } v_i > 0 \quad v_o = v_i + \frac{V_{BB}}{2} - v_{BEN} \Rightarrow v_o \approx v_i$$

$$\text{for } v_i < 0 \quad v_o = v_i - \frac{V_{BB}}{2} + v_{EBP} \Rightarrow v_o \approx v_i$$

Base-to base voltage is constant!

$$v_{BEN} + v_{EBP} = V_{BB} \quad \text{for all } v_i$$

Bias ( $Q_N$  &  $Q_P$  matched):

$$I_N = I_P = I_Q = I_S e^{\frac{V_{BB}}{2V_T}}$$

## Class AB Circuit Operation - cont.

$$\begin{aligned} \text{for } v_i > 0 \quad v_o &= v_i + \frac{V_{BB}}{2} - v_{BEN} \Rightarrow v_{BEN} = v_i - v_o + \frac{V_{BB}}{2} \\ \text{for } v_i < 0 \quad v_o &= v_i - \frac{V_{BB}}{2} + v_{EBP} \Rightarrow v_{EBP} = v_o - v_i + \frac{V_{BB}}{2} \end{aligned}$$


ADD

$$v_{BEN} + v_{EBP} = V_{BB} \quad \text{for all } v_i \quad \text{Note for Class B } V_{BB} = 0$$

Using the currents

$$\begin{aligned} i_N = I_S e^{\frac{v_{BEN}}{V_T}} \Rightarrow v_{BEN} &= V_T \ln \left( \frac{i_N}{I_S} \right) & i_P = I_S e^{\frac{v_{EBP}}{V_T}} \Rightarrow v_{EBP} &= V_T \ln \left( \frac{i_P}{I_S} \right) \\ I_N = I_P = I_Q = I_S e^{\frac{V_{BB}}{2V_T}} \Rightarrow V_{BB} &= 2V_T \ln \left( \frac{I_Q}{I_S} \right) \\ V_T \ln \left( \frac{i_N}{I_S} \right) + V_T \ln \left( \frac{i_P}{I_S} \right) &= 2V_T \ln \left( \frac{I_Q}{I_S} \right) \quad \text{for all } v_i \end{aligned}$$

## Class AB Circuit Operation - cont.

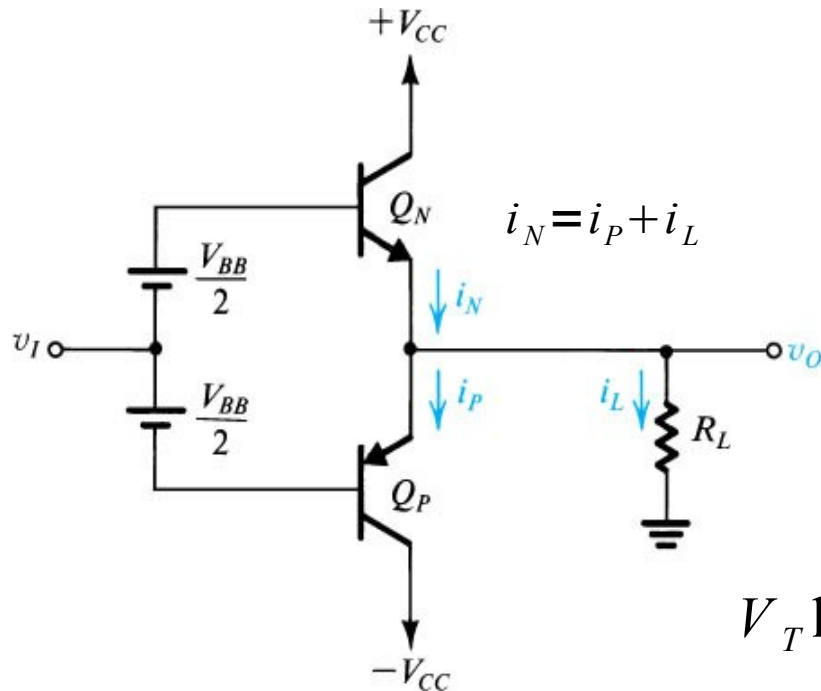

from the previous slide

$$V_T \ln \left( \frac{i_N}{I_S} \right) + V_T \ln \left( \frac{i_P}{I_S} \right) = 2 V_T \ln \left( \frac{I_Q}{I_S} \right)$$

$$V_T \ln \left( \frac{i_N i_P}{I_S^2} \right) = 2 V_T \ln \left( \frac{I_Q}{I_S} \right)$$

$$V_T \ln(i_N i_P) - V_T \ln(I_S^2) = 2 V_T \ln(I_Q) - 2 V_T \ln(I_S)$$

$$\ln(i_N i_P) = \ln(I_Q^2) \quad \text{or} \quad i_N i_P = I_Q^2$$

Constant base voltage condition:

$$v_{BEN} + v_{EBP} = V_{BB} \Rightarrow i_N i_P = I_Q^2$$

## Class AB Circuit Operation – VTC cont.

The constant base voltage condition  $i_P i_N = I_Q^2$  where  $I_Q$  is typically small.

For example let  $I_Q = 1 \text{ mA}$  and  $i_N = 10 \text{ mA}$ .

$$i_P = \frac{I_Q^2}{i_N} = \frac{1 \cdot 10^{-6}}{10 \cdot 10^{-3}} = 0.1 \text{ mA} = \frac{1}{100} i_N$$


The Class AB circuit, over most of its input signal range, operates as if either the  $Q_N$  or  $Q_P$  transistor is conducting and the  $Q_P$  or  $Q_N$  transistor is cut off.

For small values of  $v_I$  both  $Q_N$  and  $Q_P$  conduct, and as  $v_I$  is increased or decreased, the conduction of  $Q_N$  or  $Q_P$  dominates, respectively.

Using this approximation we see that a class AB amplifier acts much like a class B amplifier; but without the dead zone.
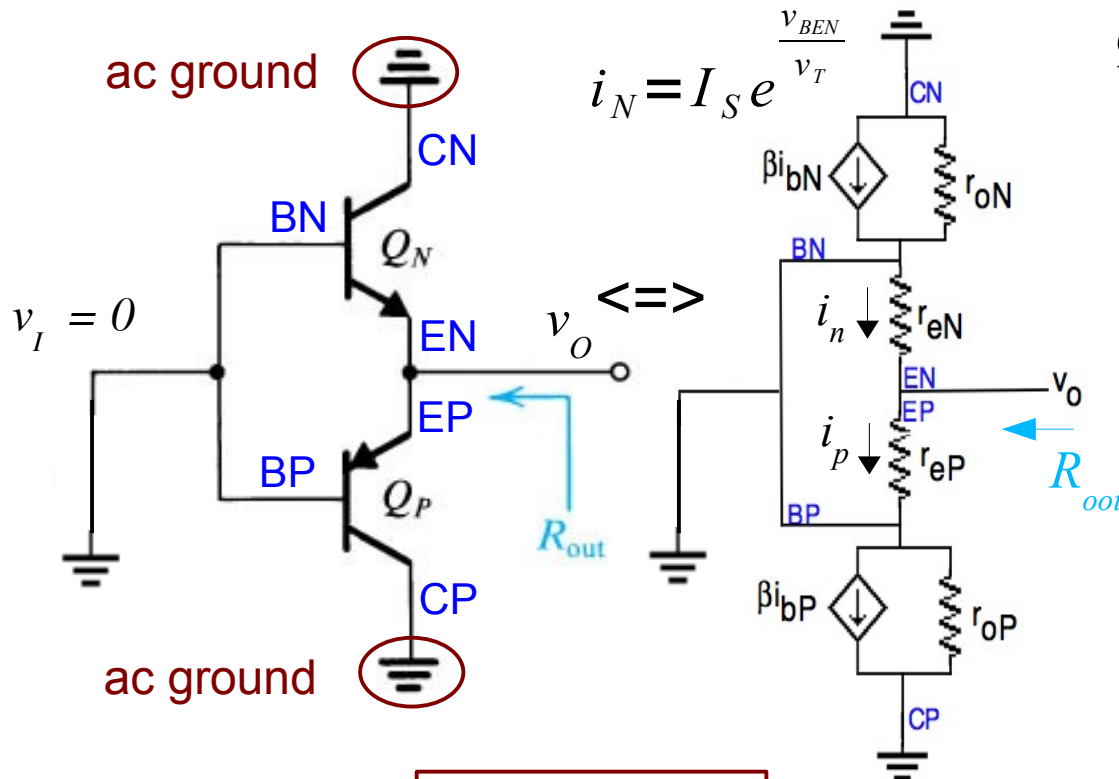
## Class AB Small-Signal Output Resistance

Instantaneous resistance for the  $Q_N$  transistor - assume  $\alpha = 1$ :



$$v_I = 0$$

$$R_{out} = r_{eN} \parallel r_{eP}$$

$$v_I > 0 V: i_N > i_P \Rightarrow R_{out} \approx r_{eN}$$

$$v_I < 0 V: i_P > i_N \Rightarrow R_{out} \approx r_{eP}$$

$$\frac{di_N}{dv_{BEN}} = \frac{I_S e^{\frac{v_{BEN}}{V_T}}}{V_T} = \frac{i_N}{V_T}$$

For the  $Q_P$  transistor:

$$\frac{di_P}{dv_{EBP}} = \frac{i_P}{V_T}$$

Hence:

$$r_{eN} = \frac{V_T}{i_N} \quad \text{and} \quad r_{eP} = \frac{V_T}{i_P}$$

## Small-Signal Output Resistance - cont.

The two emitter resistors are in parallel:

$$R_{out} = r_{eN} \parallel r_{eP} = \frac{\frac{V_T^2}{i_N i_P}}{\frac{V_T}{i_N} + \frac{V_T}{i_P}} = \frac{V_T}{i_N i_P \left( \frac{1}{i_N} + \frac{1}{i_P} \right)} = \frac{V_T}{i_N + i_P} \quad \text{and} \quad i_L = \frac{v_O}{R_L} = i_N - i_P$$


At  $i_N = i_P$  (the no-signal condition i.e.  $v_O = 0 \Rightarrow i_L = 0$ ):  $i_N = i_P = I_Q$

$$R_{out} = \frac{V_T}{2I_Q}$$


So, for small signals, a small load current  $I_Q$  flows  $\Rightarrow$  no dead-zone!


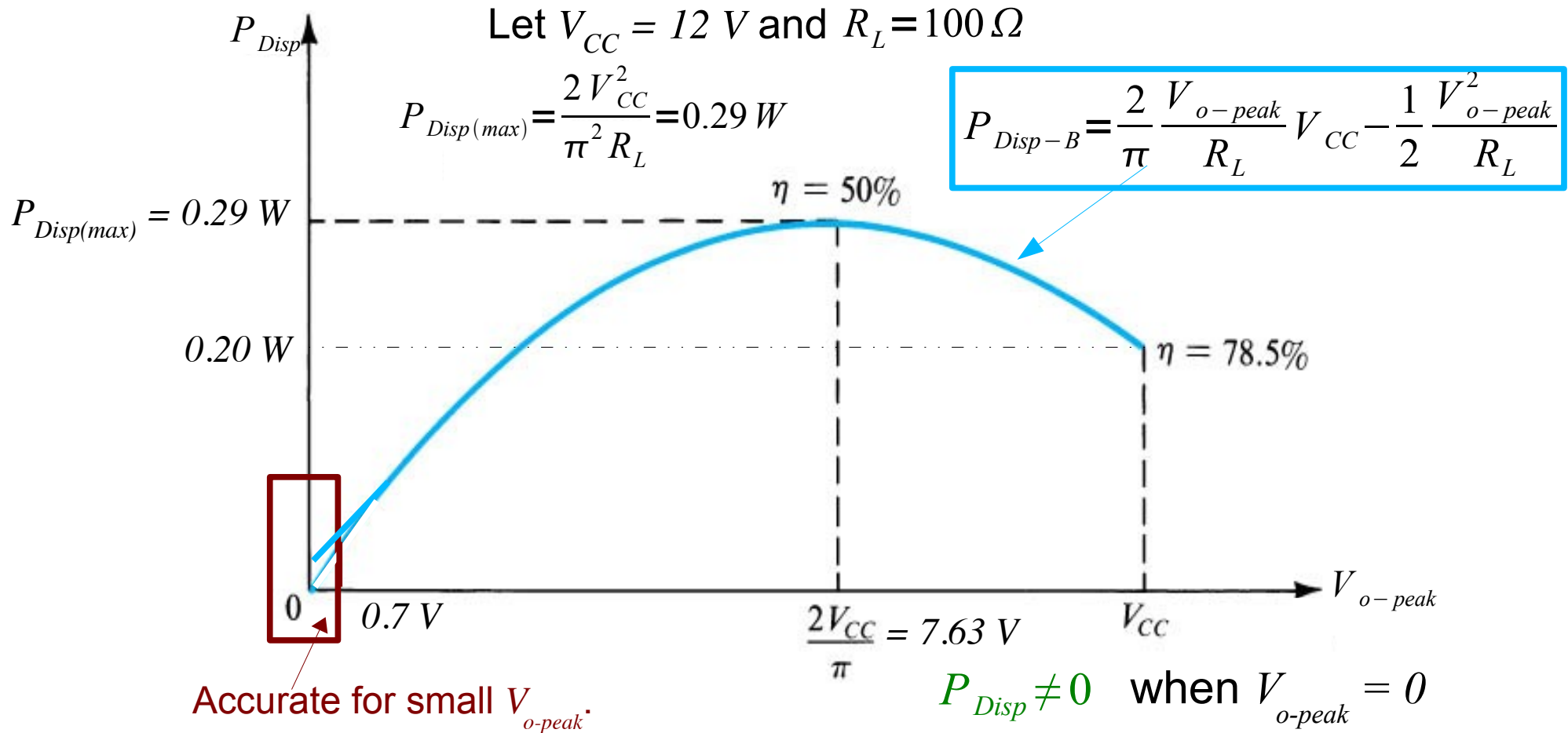
# Class AB Power Conversion Efficiency & Power Dissipation Similar to Class B



## Class AB Amplifier Biasing

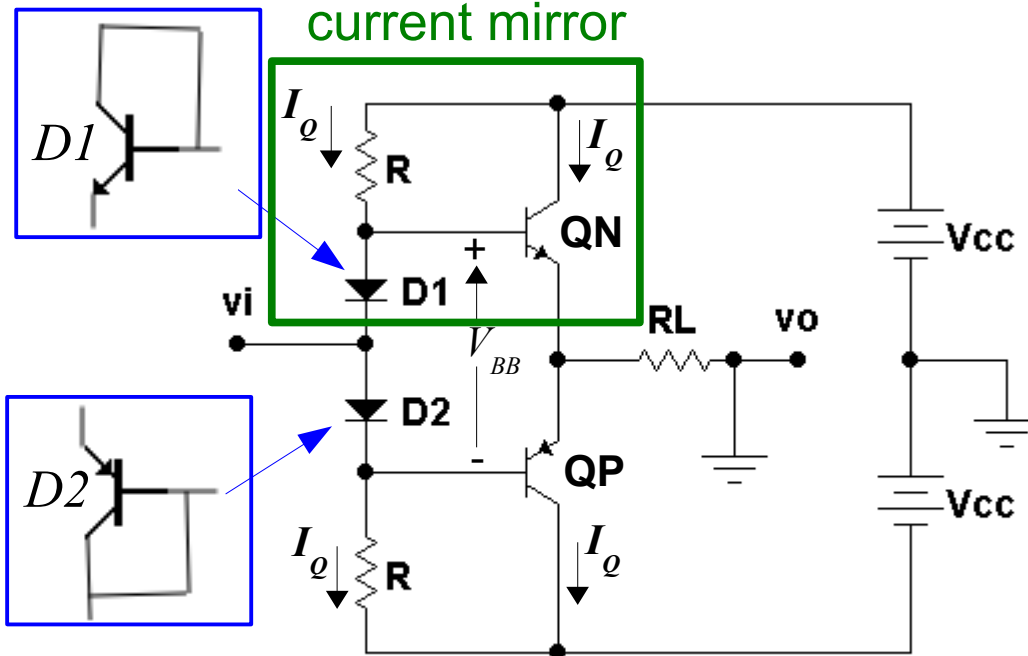

A straightforward biasing approach:  $D1$  and  $D2$  are diode-connected transistors **identical to  $QN$  and  $QP$** , respectively.

They form mirrors with the quiescent currents  $I_Q$  set by matched  $R$ 's:

$$I_Q = \frac{2V_{CC} - 1.4}{2R} = \frac{V_{CC} - 0.7}{R}$$


or:

$$R = \frac{V_{CC} - 0.7}{I_Q}$$

Recall: With mirrors, the ambient temperature for all transistors needs to be matched!
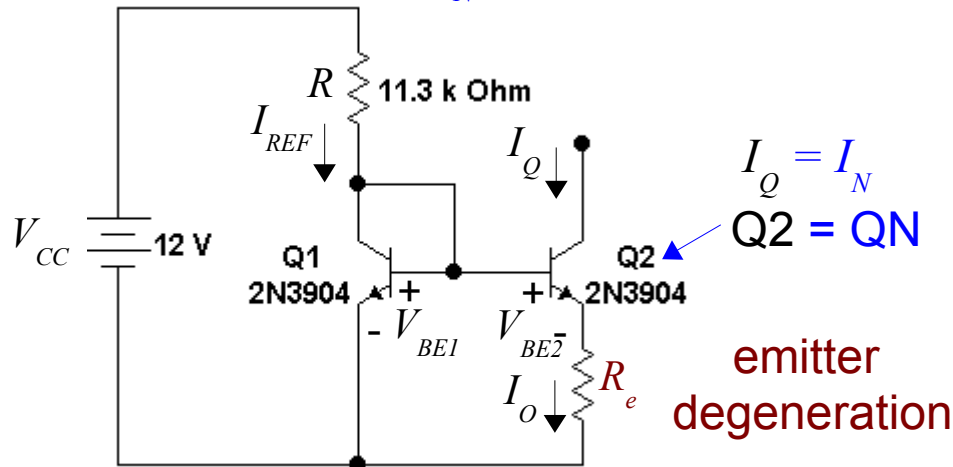
## Widlar Current Source

$I_N$  = bias current for Class AB amplifier NPN



$$V_{BE1} = V_T \ln \left( \frac{I_{REF}}{I_S} \right)$$

$$V_{BE2} = V_T \ln \left( \frac{I_Q}{I_S} \right)$$

$$V_{BE1} - V_{BE2} = V_T \ln \left( \frac{I_{REF}}{I_S} \frac{I_S}{I_Q} \right) = V_T \ln \left( \frac{I_{REF}}{I_Q} \right)$$

$$V_{BE1} = V_{BE2} + I_Q R_e$$


$$I_Q R_e = V_T \ln \left( \frac{I_{REF}}{I_Q} \right)$$

Note  $R_e > 0$  iff  $I_Q < I_{REF}$

$$I_{REF} = \frac{V_{CC} - V_{BE1}}{R} = \frac{12V - 0.7V}{11.3k\Omega} = 1mA$$

Note: Pages 543-546 in Sedra & Smith Text.

## Widlar Current Source - cont.

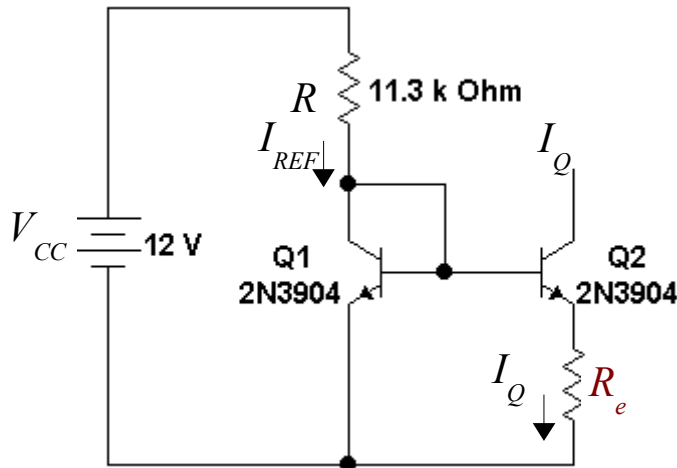

$$I_Q R_e = V_T \ln\left(\frac{I_{REF}}{I_Q}\right)$$

If  $R_e$  specified and  $I_{REF}$  chosen by the designer:

$$I_Q = \frac{V_T}{R_e} \left( \ln(I_{REF}) - \ln(I_Q) \right)$$

Solve for  $I_Q$  graphically.

If  $I_Q$  specified and  $I_{REF}$  chosen by designer:

$$R_e = \frac{V_T}{I_Q} \ln\left(\frac{I_{REF}}{I_Q}\right)$$


**Example** Let  $I_Q = 10 \mu A$  & choose  $I_{REF} = 10 mA$ , determine  $R$  and  $R_e$ :

$$R = \frac{V_{CC} - V_{BE1}}{I_{REF}} = \frac{12V - 0.7V}{10mA} = 1.13k\Omega$$

$$R_e = \frac{V_T}{I_Q} \ln\left(\frac{I_{REF}}{I_Q}\right) = \frac{0.025V}{10\mu A} \ln\left(\frac{10mA}{10\mu A}\right) = 2500 \ln(1000) = 17.27k\Omega$$

$$R = 1.13k\Omega \quad R_e = 17.27k\Omega$$
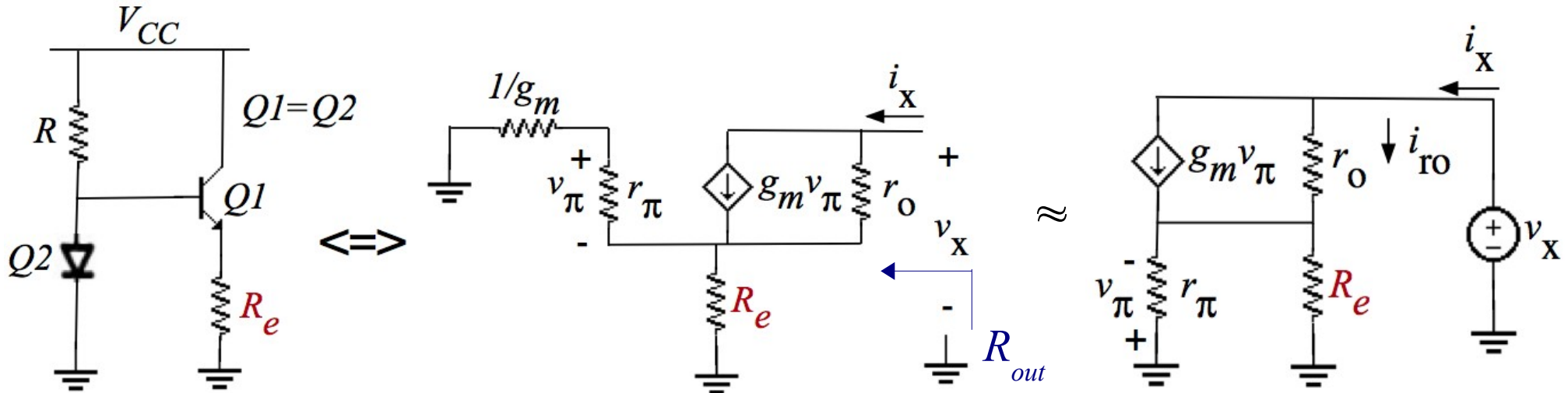
## Widlar Current Mirror Small-Signal Analysis



$$i_x = g_m v_\pi + i_{ro} = g_m v_\pi + \frac{v_x - (-v_\pi)}{r_o}$$

$$v_\pi = -r_\pi \parallel R_e i_x$$

$$i_x = -g_m r_\pi \parallel R_e i_x + \frac{v_x}{r_o} - \frac{r_\pi \parallel R_e i_x}{r_o}$$


$$\approx -g_m r_\pi \parallel R_e i_x + \frac{v_x}{r_o}$$

$R_{out}$  is greatly enhanced by adding emitter degeneration.

$$\Rightarrow R_{out} = \frac{v_x}{i_x} = r_o (1 + g_m (R_e \parallel r_\pi))$$



$$g_m (R_e \parallel r_\pi) \gg 1$$

## Quick Review

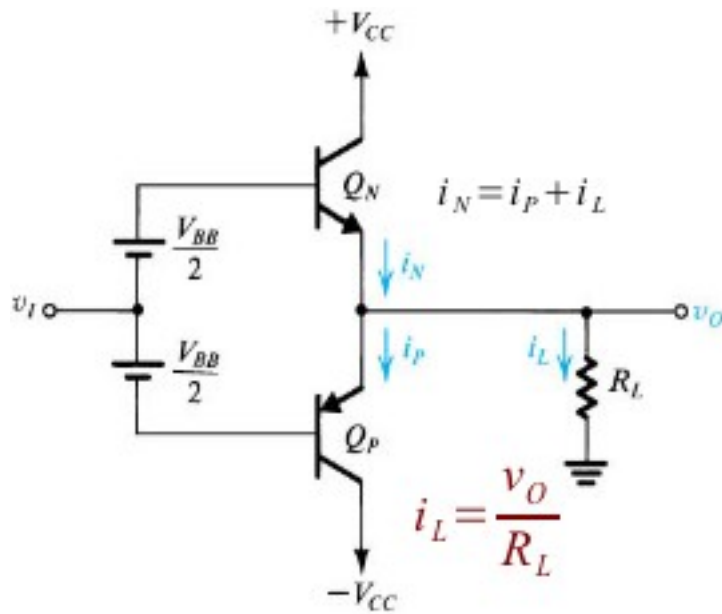

$$i_L = i_N - i_P$$
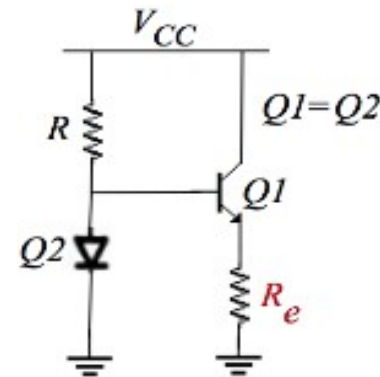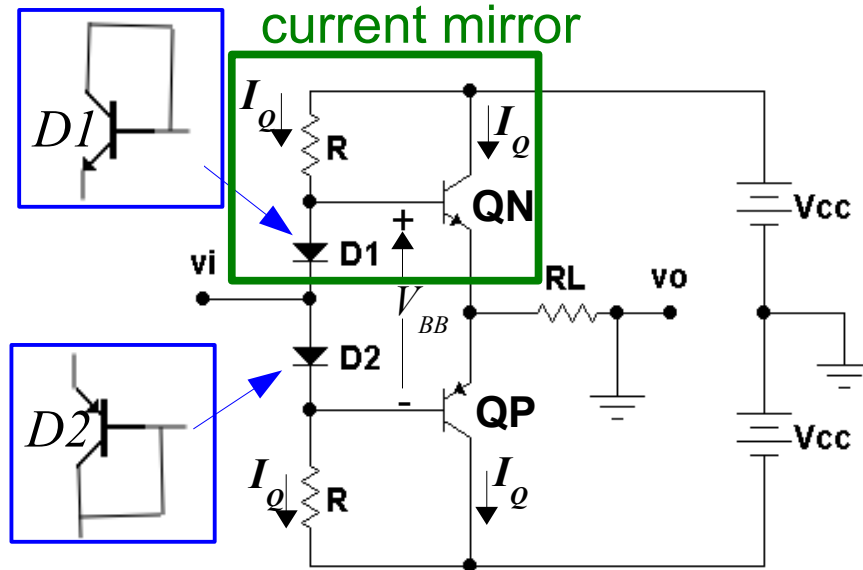
$$v_{BEN} + v_{EBP} = V_{BB} \Rightarrow i_N i_P = I_Q^2$$



Widlar Current Mirror

$$R_e = \frac{V_T}{I_Q} \ln \left( \frac{I_{REF}}{I_Q} \right)$$


## Class AB Current Biasing Simulation

Bias currents set at  $I_{REF}$  and  $I_Q$  by  $R$  and emitter resistor(s)  $R_e$ .


$$I_{REF} \approx 4 \text{ mA}$$

$$I_Q = I_{QN} = I_{QP} \approx 2 \text{ mA}$$

NPN Widlar current mirror

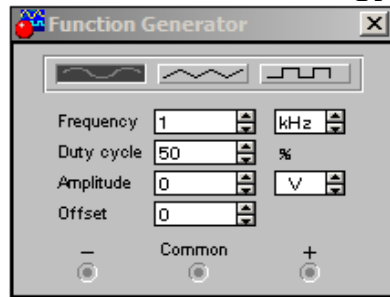

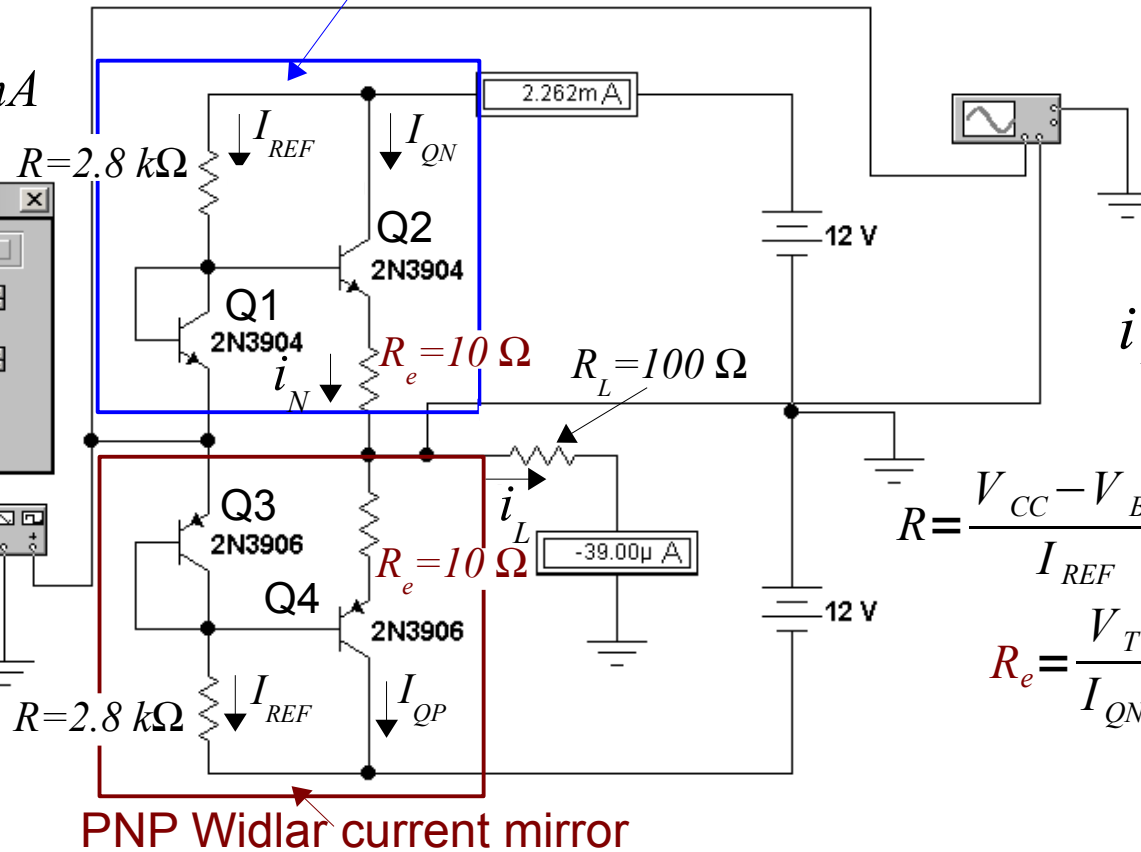Amplitude:  $0 \text{ V}_p$   
Frequency:  $1 \text{ kHz}$



$$i_L = i_N - i_P$$

$$R = \frac{V_{CC} - V_{BE1}}{I_{REF}} = \frac{V_{CC} - V_{EB3}}{I_{REF}} \approx 2.8 \text{ k}\Omega$$

$$R_e = \frac{V_T}{I_{QN}} \ln \left( \frac{I_{REF}}{I_{QN}} \right) \approx 10 \Omega$$

## *Conclusions*

### ADVANTAGE:

Class AB operation improves on Class B linearity.  
Power conversion efficiency similar to Class B

### DISADVANTAGES:

1. Emitter resistors absorb output power.
2. Power dissipation for low signal levels higher than Class B.
3. Temperature matching will be needed – more so.  
if emitter degeneration resistors are not used.