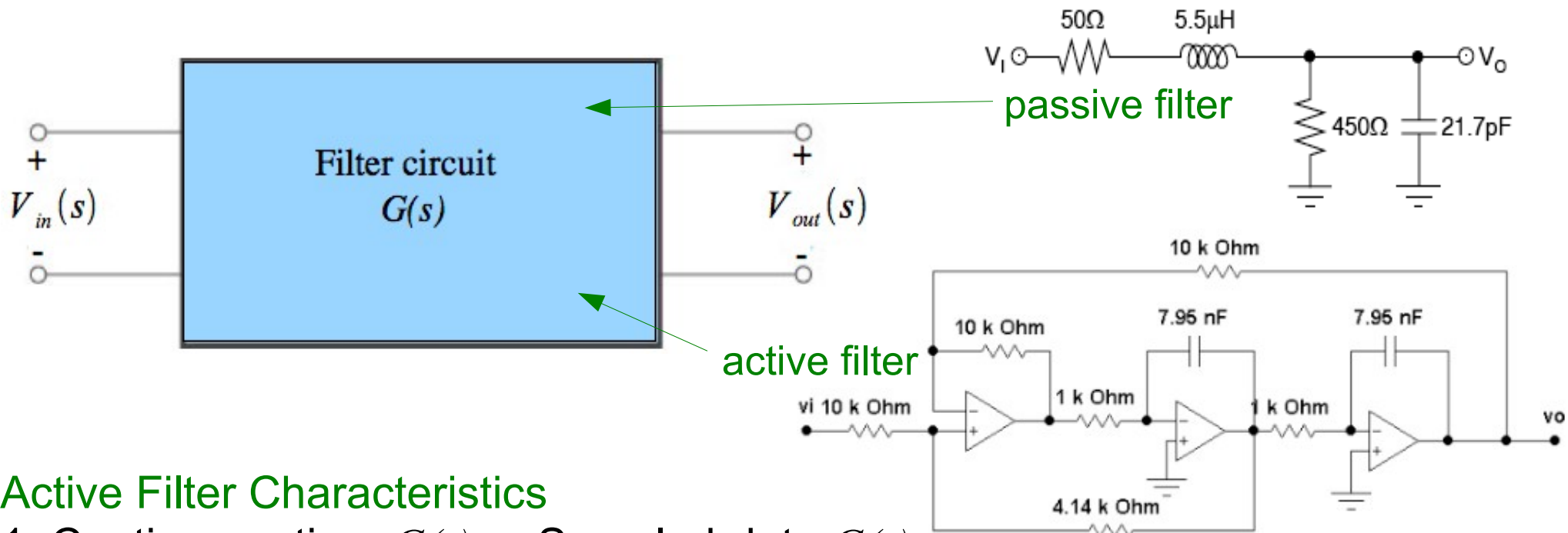



Active Filters – an Introduction



Active Filter Characteristics

1. Continuous-time $G(s)$ or Sampled-data $G(z)$
2. Employ active elements (e.g. transistors, amplifiers, op-amps)
 - a. inductor-less (continuous-time)
 - b. inductor-less & resistor-less (sample-data)
 - c. $|G(jf)| \geq 1$ in passband

Active Filters – an Introduction

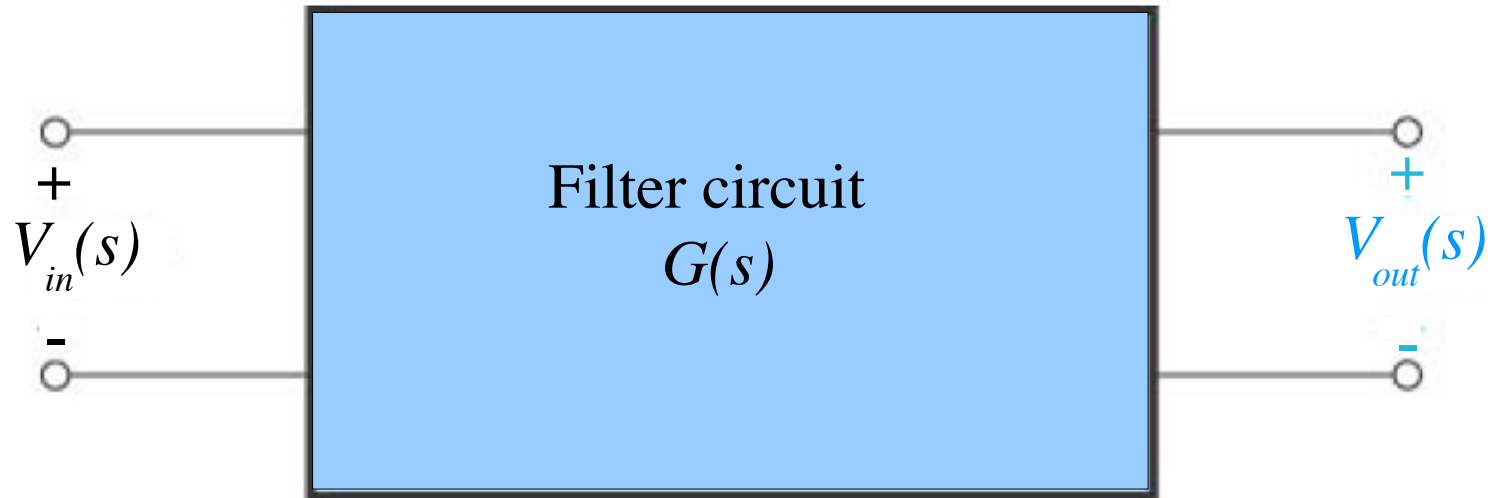

$$G(s) = \frac{V_{out}(s)}{V_{in}(s)} = \frac{a_M s^M + a_{M-1} s^{M-1} + \dots + a_1 s + a_0}{s^N + b_{N-1} s^{N-1} + \dots + b_1 s + b_0}$$

a_k = real

b_k = positive real

$$G(s) = \frac{a_M (s + z_1)(s + z_2) \dots (s + z_M)}{(s + p_1)(s + p_2) \dots (s + p_N)}$$

z_k = real or complex


p_k = r.h.p. real of complex

$$M \leq N$$


Filter Order = N




Ideal Filter Response Characteristics

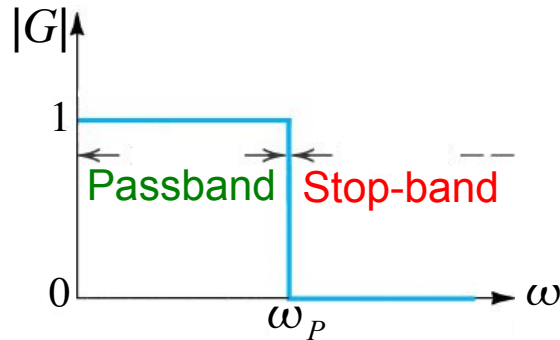


Low-pass (LP)

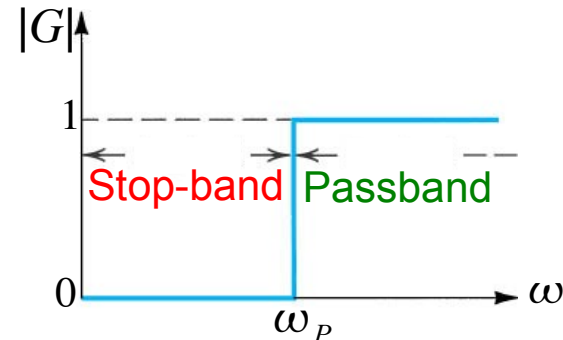

High-pass (HP)

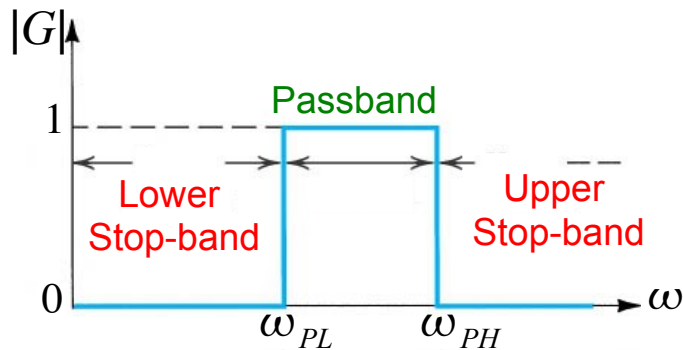


Bandpass (BP)

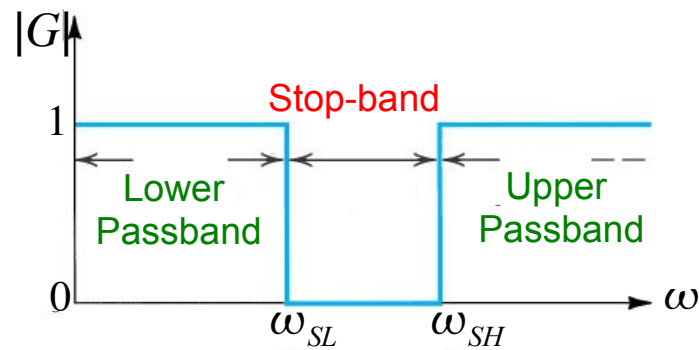

Bandstop (BS)

$$|G| = |G(j\omega)| = \left| \frac{V_{out}(j\omega)}{V_{in}(j\omega)} \right|$$

Practical Lowpass Filter Specification

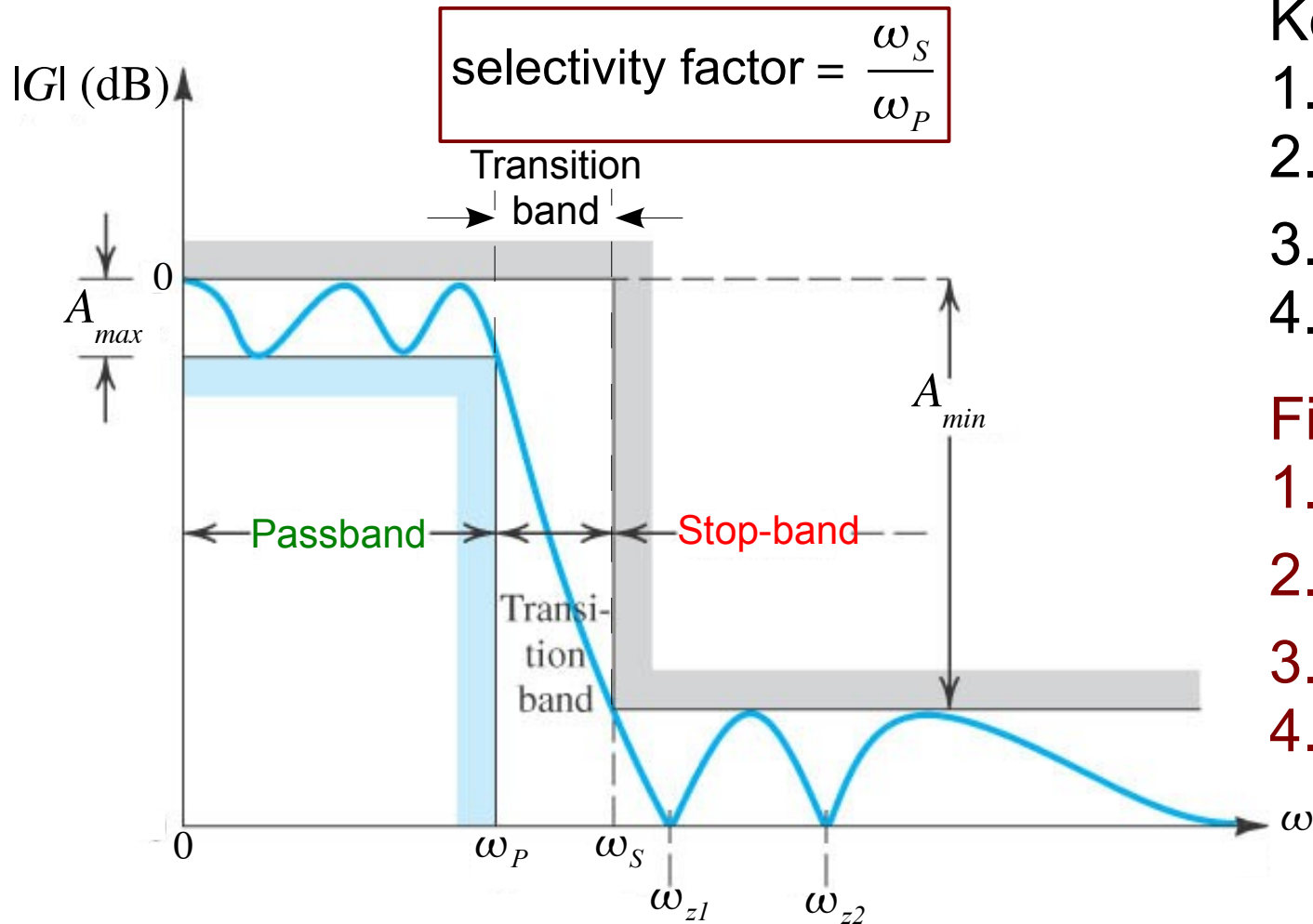

Key specs:

1. $f_B = \omega_P / 2\pi$

2. A_{max}

3. $f_S = \omega_S / 2\pi$

4. A_{min}

Filter cost increases!


1. $A_{max} \rightarrow$ lower

2. $A_{min} \rightarrow$ larger

3. $\omega_P \rightarrow$ larger

4. $\omega_S / \omega_P \rightarrow 1$


Filter Approximation – Design $G(s)$

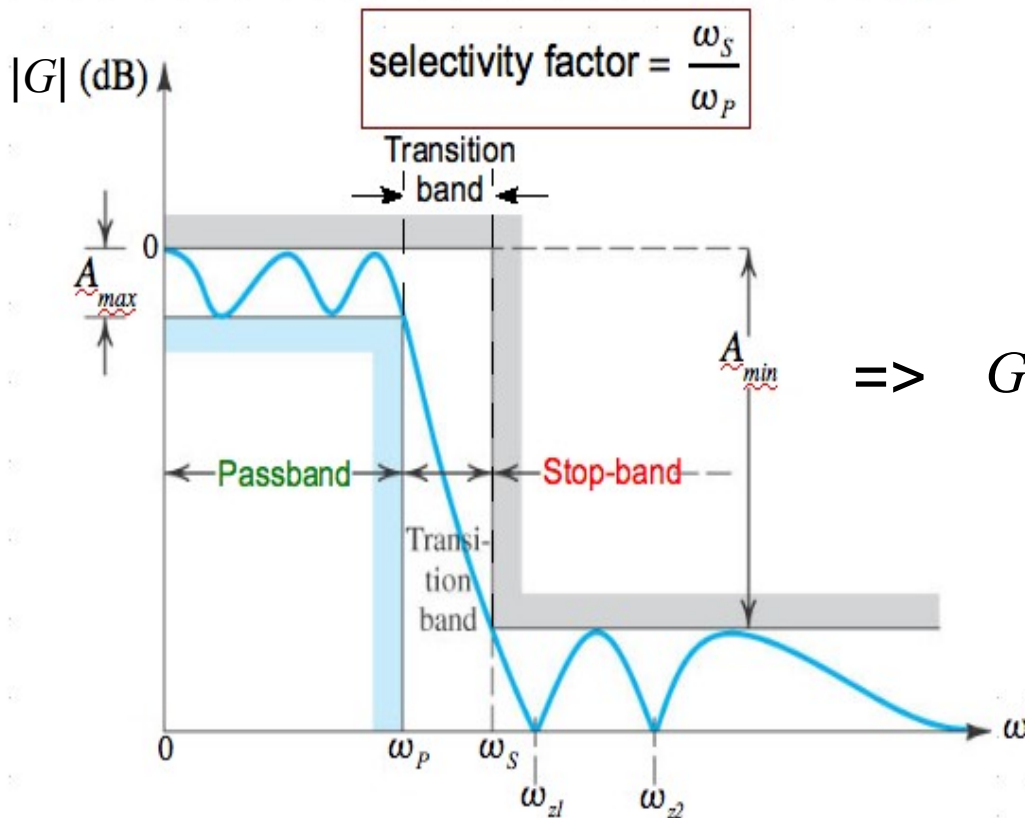

$$\Rightarrow G(s) = \frac{a_M (s + z_1)(s + z_2) \dots (s + z_M)}{(s + p_1)(s + p_2) \dots (s + p_N)}$$

MatLab is a good tool for this task.

Practical Bandpass Filter Specification

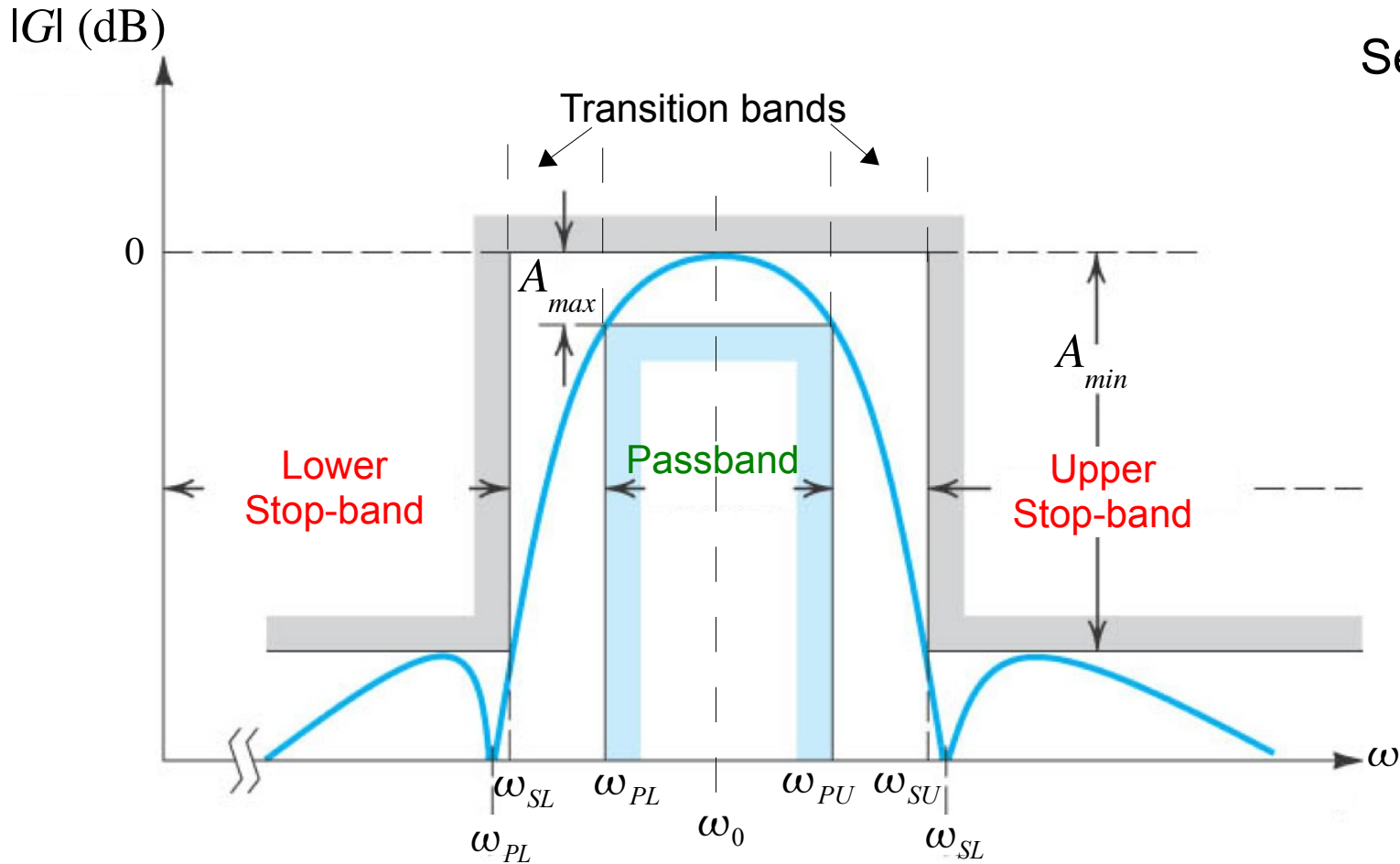

Selectivity factors


$$\frac{\omega_{SL}}{\omega_{PL}} \neq \frac{\omega_{SU}}{\omega_{PU}}$$

Symmetric bandpass filter

$$\frac{\omega_{SL}}{\omega_{PL}} = \frac{\omega_{SU}}{\omega_{PU}}$$

$$Q = \frac{\omega_{PU} - \omega_{PL}}{\omega_0}$$

Cascade Filter Design

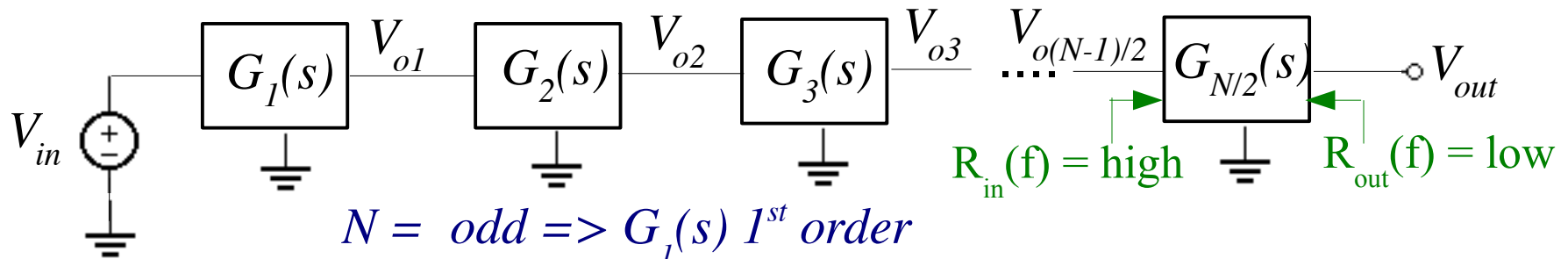

$N = \text{odd} \Rightarrow G_1(s)$ 1st order

$N = \text{even} \Rightarrow G_1(s)$ 2nd order

$$G(s) = \frac{V_{out}}{V_{in}} = \frac{a_M s^M + a_{M-1} s^{M-1} + \dots + a_1 s + a_0}{s^N + b_{N-1} s^{N-1} + \dots + b_1 s + b_0} = \prod_{i=1}^{N/2} G_i(s)$$

If $N = \text{even}$ $G_i(s) = \frac{a_{2i} s^2 + a_{1i} s + a_{0i}}{s^2 + b_{1i} s + b_{0i}}$ for $1 \leq i \leq N/2$

If $N = \text{odd}$ $G_1(s) = \frac{a_{10} s + a_{00}}{s + b_{10}}$ $G_i(s) = \frac{a_{2i} s^2 + a_{1i} s + a_{0i}}{s^2 + b_{1i} s + b_{0i}}$ for $2 \leq i \leq N/2$

The factorization of $G(s)$ into $G_i(s)$ can be done with Matlab.

2nd Order (Biquadratic) Filter Section

$$G_i(s) = \frac{a_{2i}s^2 + a_{1i}s + a_{0i}}{s^2 + b_{1i}s + b_{0i}}$$

1. $G_i(s)$ is the most important active-filter building block.
2. Numerous realizations of $G_i(s)$, most using op-amp based circuits.
 - a. Multiple Op-amp Circuits with R's & C's (i.e. no L's)
 - b. Single Op-amp Circuits with R's & C's (i.e. no L's)
 - c. Cost advantage depends on how the filter is fabricated.





Filter Type	s-plane zeros/poles	$ G $
<p>2nd order low-pass (LP)</p> $G(s) = \frac{a_0}{s^2 + s \frac{\omega_0}{Q} + \omega_0^2}$ $ G(j\omega) = \frac{a_0}{\omega_0^2 \sqrt{1 - \frac{1}{4Q^2} + \frac{\omega^2}{\omega_0^2}}}$	<p>$z_2 = \infty$ $z_1 = \infty$</p>	<p>$G_{max} = G(j\omega_0) = \frac{a_0 Q}{\omega_0^2}$ $\omega_1 = \omega_0 \sqrt{1 - \frac{1}{4Q^2}}$</p>
<p>2nd order high-pass (HP)</p> $G(s) = \frac{a_2 s^2}{s^2 + s \frac{\omega_0}{Q} + \omega_0^2}$ $ G(j\infty) = a_2$	<p>$z_1 = 0$ $z_2 = 0$</p>	<p>$G_{max} = G(j\omega_0) = a_2 Q$ $\omega_1 = \omega_0 \sqrt{1 - \frac{1}{4Q^2}}$</p>
<p>2nd order bandpass (BP)</p> $G(s) = \frac{a_1 s}{s^2 + s \frac{\omega_0}{Q} + \omega_0^2}$ $ G(j\omega_0) = \frac{a_1 Q}{\omega_0}$	<p>$z_1 = 0$ $z_2 = \infty$</p>	<p>$G_{max} = G(j\omega_0) = \frac{a_1 Q}{\omega_0}$ $\omega_1 = \omega_0 \sqrt{1 - \frac{1}{4Q^2}} \approx \omega_0$ as $Q \rightarrow \text{large}$</p>



Filter Type	s-plane zeros/poles	$ G $
<p>2nd order Notch (N)</p> $G(s) = a_2 \frac{s^2 + \omega_N^2}{s^2 + s \frac{\omega_0}{Q} + \omega_0^2}$ <p>$\omega_N = \omega_0$</p>		<p>$G(j0) = G(j\infty) = a_2$</p>
<p>2nd order LP Notch (LPN)</p> $G(s) = a_2 \frac{s^2 + \omega_N^2}{s^2 + s \frac{\omega_0}{Q} + \omega_0^2}$ <p>$\omega_N > \omega_0$</p>		<p>$G(j0) = a_2 \frac{\omega_N^2}{\omega_0^2}$</p> <p>$G(j\infty) = a_2$</p>
<p>2nd order HP Notch (HPN)</p> $G(s) = a_2 \frac{s^2 + \omega_N^2}{s^2 + s \frac{\omega_0}{Q} + \omega_0^2}$ <p>$\omega_N < \omega_0$</p>		<p>$G(j0) = a_2 \frac{\omega_N^2}{\omega_0^2}$</p> <p>$G(j\infty) = a_2$</p>



Delay Equalization Concept

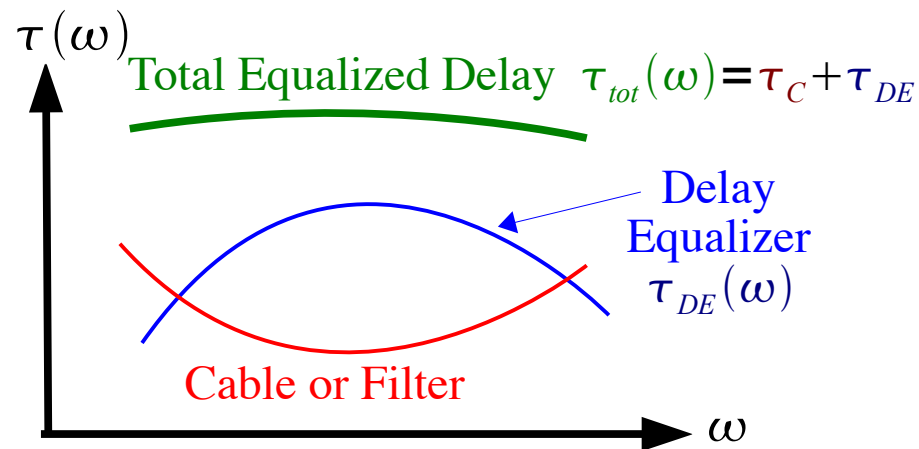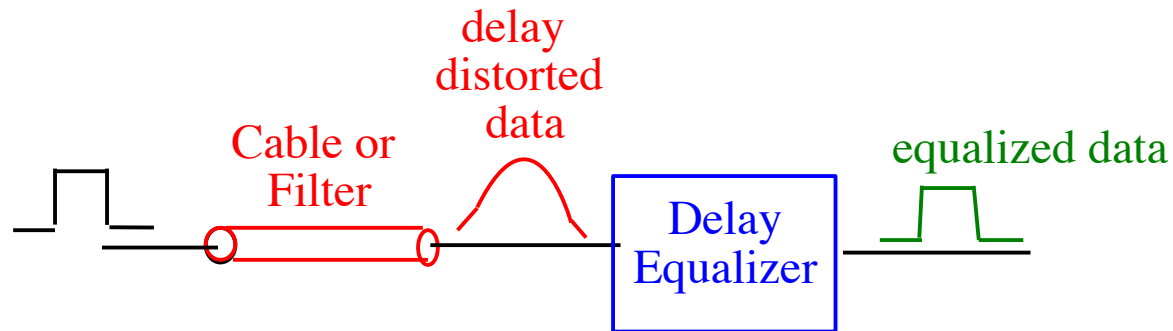

2nd order All-Pass (AP)

$$G(s) = a_2 \frac{s^2 - s \frac{\omega_0}{Q} + \omega_0^2}{s^2 + s \frac{\omega_0}{Q} + \omega_0^2}$$

$$|G(j0)| = |G(j\infty)| = |a_2|$$

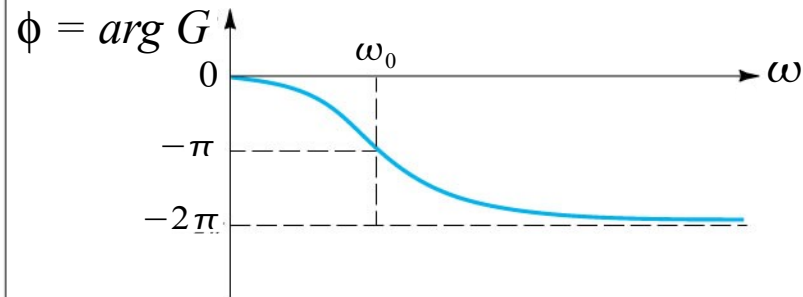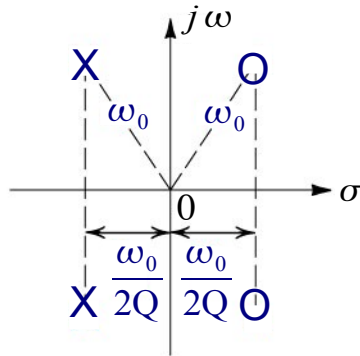

Ideal transmission:

$$v_O(t) = K v_I(t - t_d) \Rightarrow G(j\omega) = |G(j\omega)| e^{j\omega t_d}$$

$$|G(j\omega)| = K$$


$$\phi(j\omega) = -\omega t_d$$

Group Delay

$$\tau(\omega) = \frac{-d\phi(j\omega)}{d\omega} = t_d$$



Quick Review

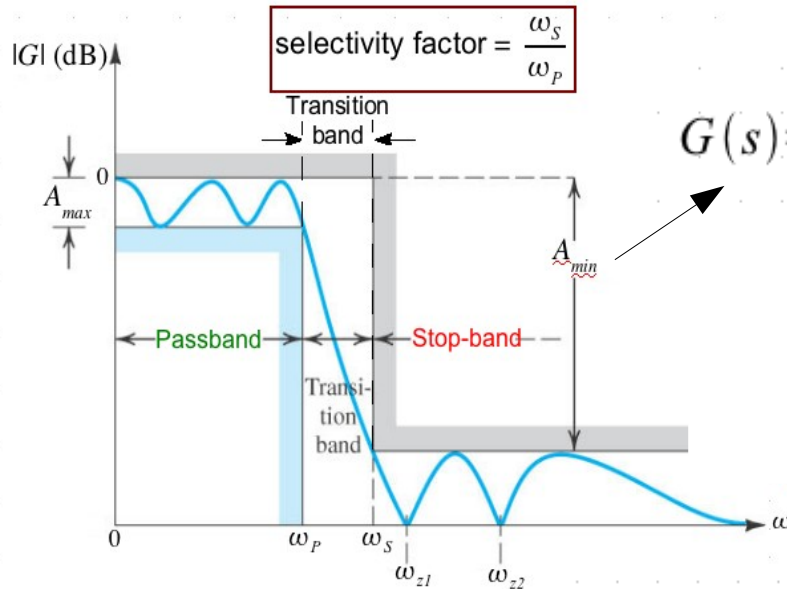


$$G(s) = \frac{V_{out}}{V_{in}} = \frac{a_M s^M + a_{M-1} s^{M-1} + \dots + a_1 s + a_0}{s^N + b_{N-1} s^{N-1} + \dots + b_1 s + b_0} = \prod_{i=1}^{N/2} G_i(s)$$


$$G(s) = a_2 \frac{s^2 + \omega_N^2}{s^2 + s \frac{\omega_0}{Q} + \omega_0^2}$$

$$G(s) = \frac{a_1 s}{s^2 + s \frac{\omega_0}{Q} + \omega_0^2}$$
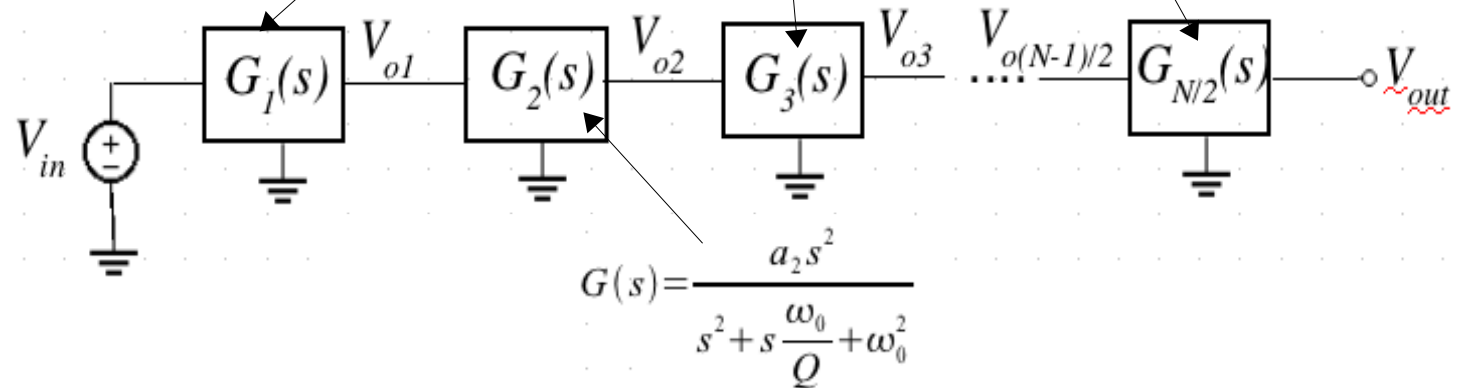
$$G(s) = \frac{a_0}{s^2 + s \frac{\omega_0}{Q} + \omega_0^2}$$



Multiple Op-Amp Biquadratic Circuits

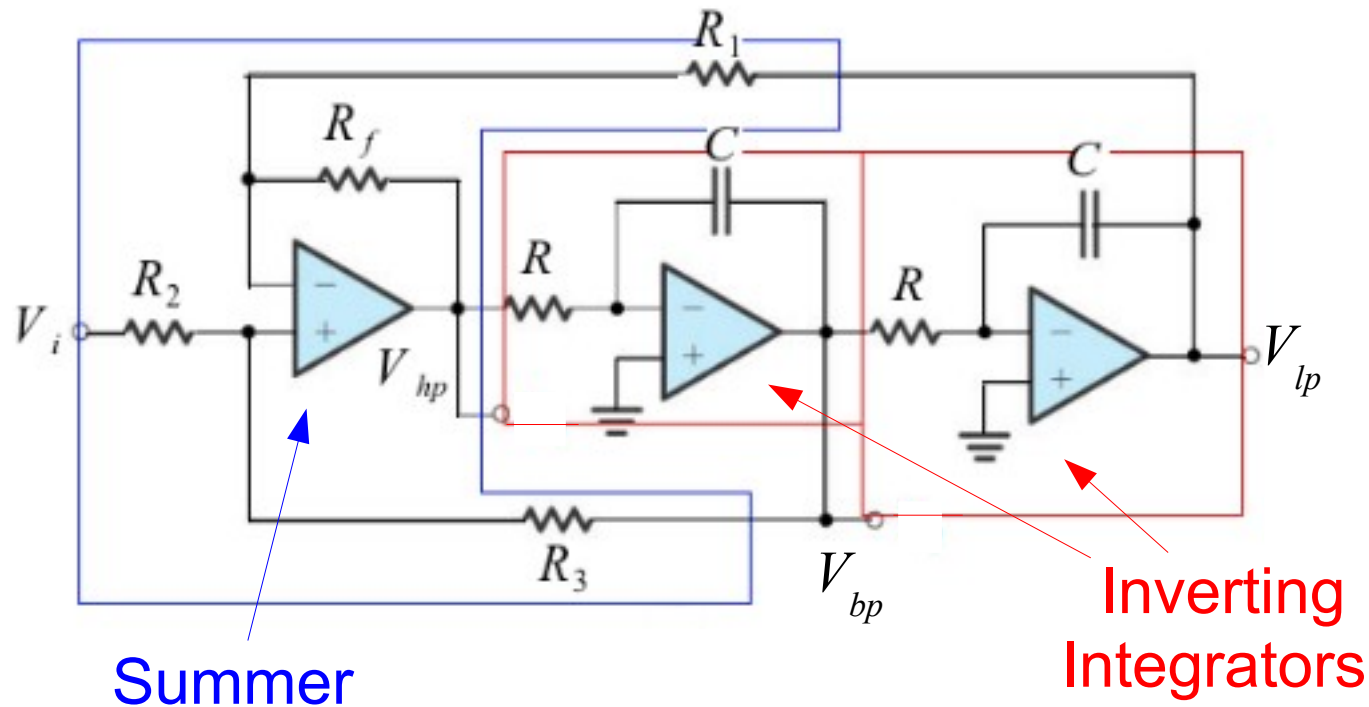


Two-Integrator-Feedback-Loop



OP Amp Circuit Building Blocks


Inverting Integrator
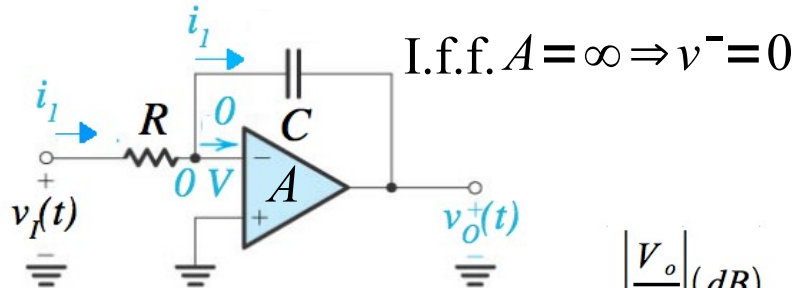
$$v_o(t) = \frac{-1}{CR} \int_0^t v_I(t) dt$$




$$\frac{V_o(s)}{V_i(s)} = -\frac{1}{sCR} = -\frac{\omega_0}{s}$$

$$\omega_0 = \frac{1}{CR}$$

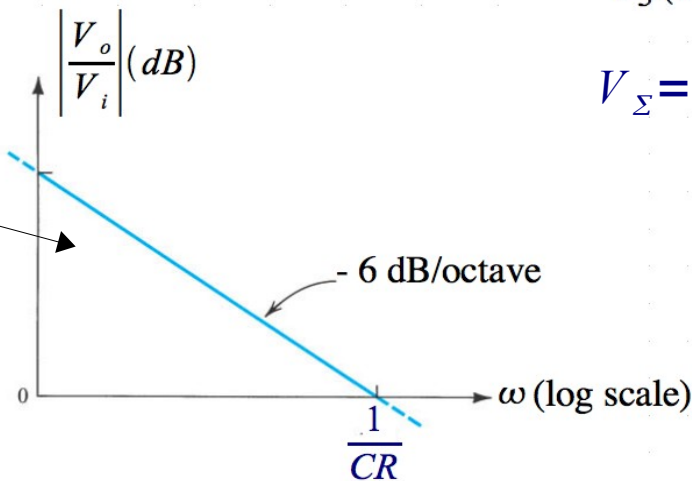

I.f.f. $A = \infty \Rightarrow v^- = v^+$

Summer

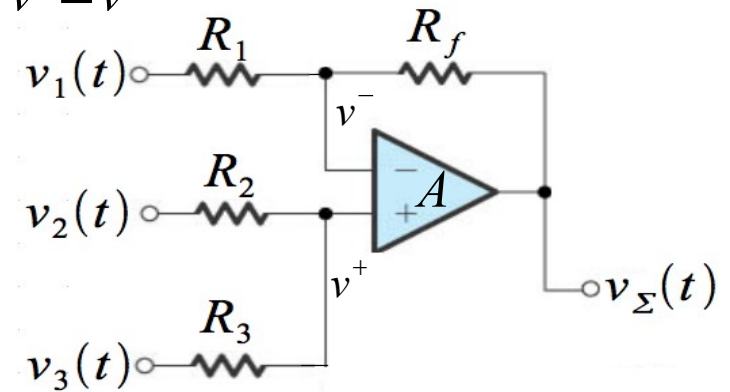

$$V_{\Sigma} = -\frac{R_f}{R_1} V_1 + \frac{R_3}{R_2 + R_3} \left(1 + \frac{R_f}{R_1}\right) V_2 + \frac{R_2}{R_2 + R_3} \left(1 + \frac{R_f}{R_1}\right) V_3$$

Two-Integrator-Feedback-Loop Active Filter

Let's start with $V_{hp}(s) = \frac{K s^2}{s^2 + s \frac{\omega_0}{Q} + \omega_0^2} V_i(s)$

OBJECTIVE: realize $V_{hp}(s)$ using a two-integrator cascade (loop).

1. Divide numerator and denominator of $V_{hp}(s)$ by s^2 , i.e.

$$V_{hp}(s) = \frac{K}{1 + \frac{1}{Q} \frac{\omega_0}{s} + \frac{\omega_0^2}{s^2}} V_i(s)$$

2. Multiply both sides of $V_{hp}(s)$ by $1 + \frac{1}{Q} \frac{\omega_0}{s} + \frac{\omega_0^2}{s^2}$, i.e.

$$V_{hp}(s) \left[1 + \frac{1}{Q} \frac{\omega_0}{s} + \frac{\omega_0^2}{s^2} \right] = K V_i(s) \Rightarrow \underbrace{V_{hp}(s)}_{\text{HP}} + \underbrace{\frac{1}{Q} \frac{\omega_0}{s} V_{hp}(s)}_{\text{BP}} + \underbrace{\frac{\omega_0^2}{s^2} V_{hp}(s)}_{\text{LP}} = K V_i(s)$$


?
?

Two-Integrator-Feedback-Loop Active Filter



From previous slide

$$V_{hp}(s) + \frac{1}{Q} \frac{\omega_0}{s} V_{hp}(s) + \frac{\omega_0^2}{s^2} V_{hp}(s) = K V_i(s)$$


3. Rearrange terms

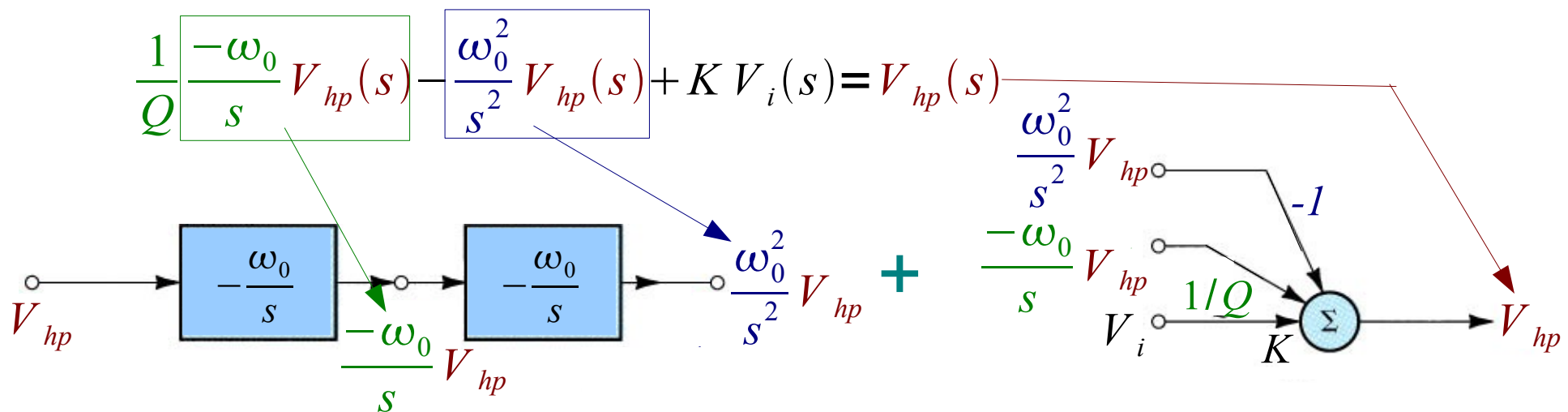

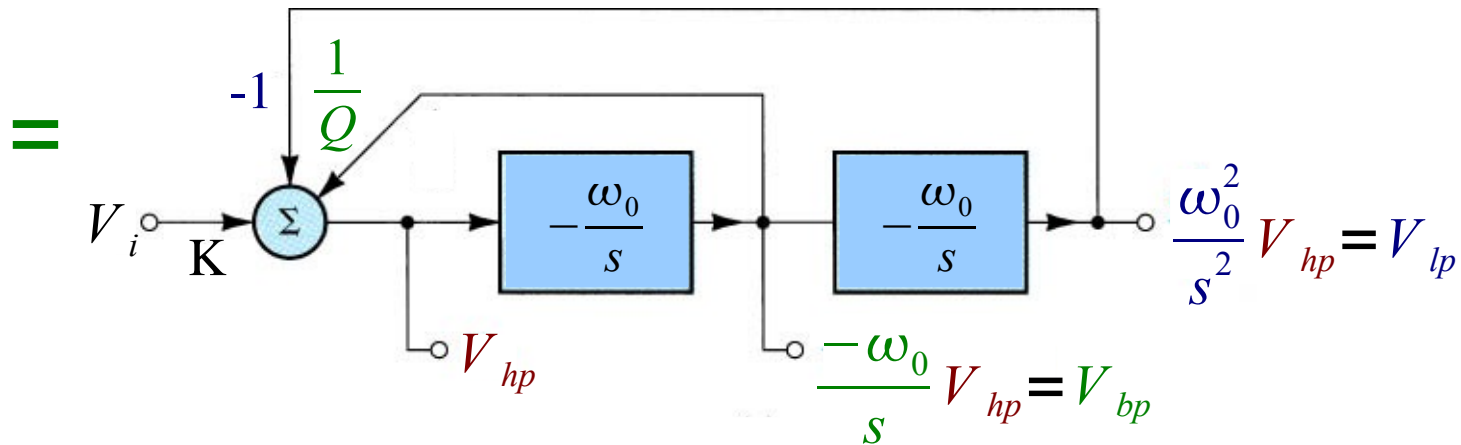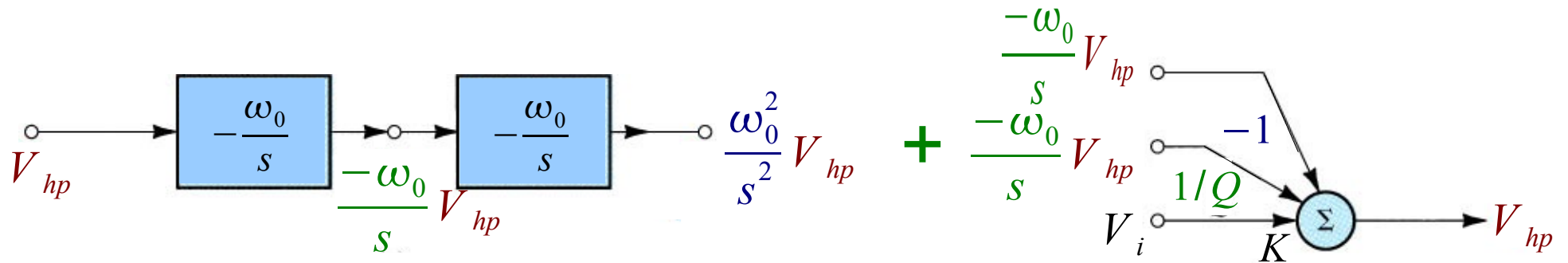Two-Integrator-Feedback-Loop Active Filter




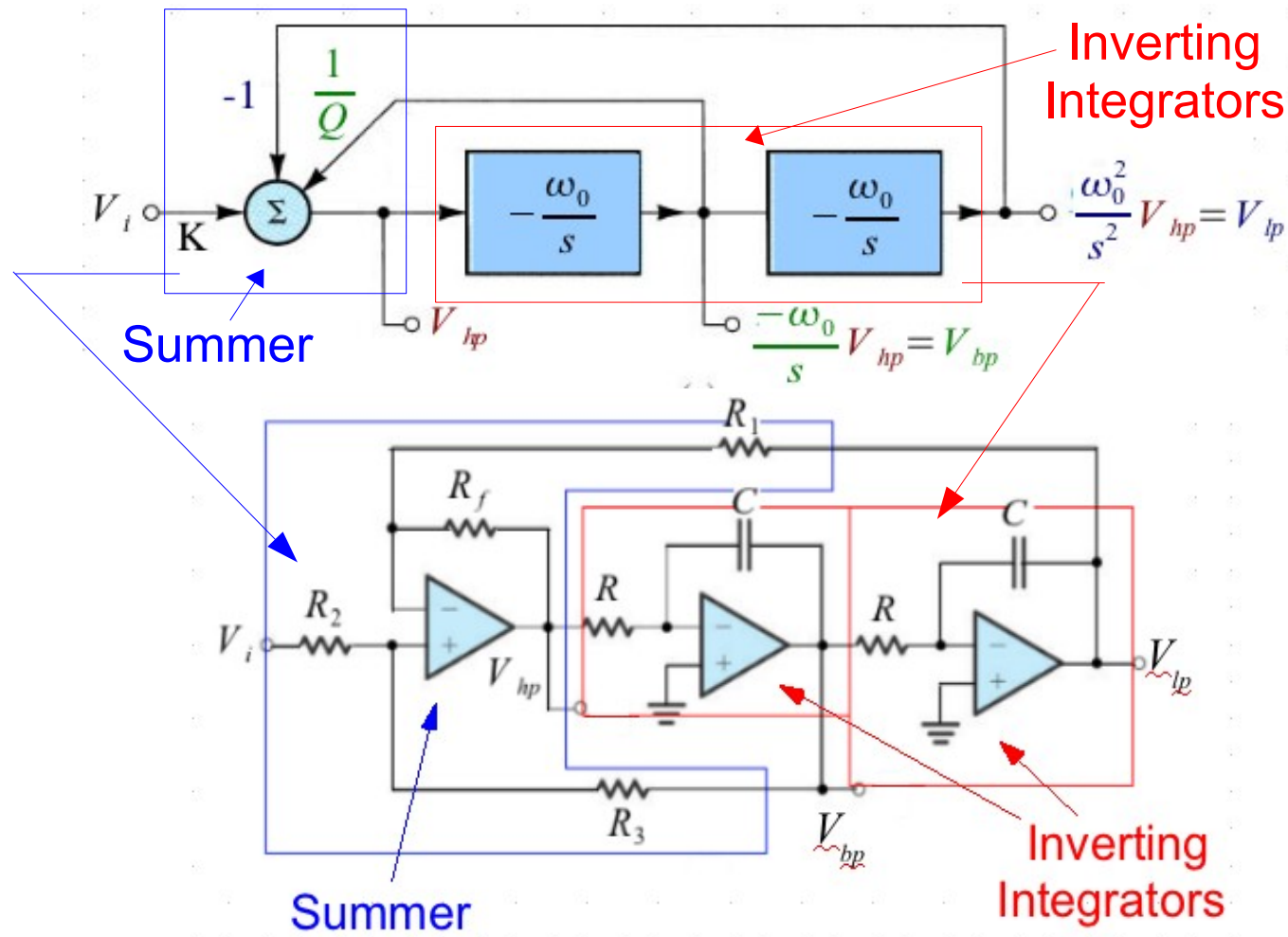Two-Integrator-Feedback-Loop Active Filter





Two Integrator Loop cont.

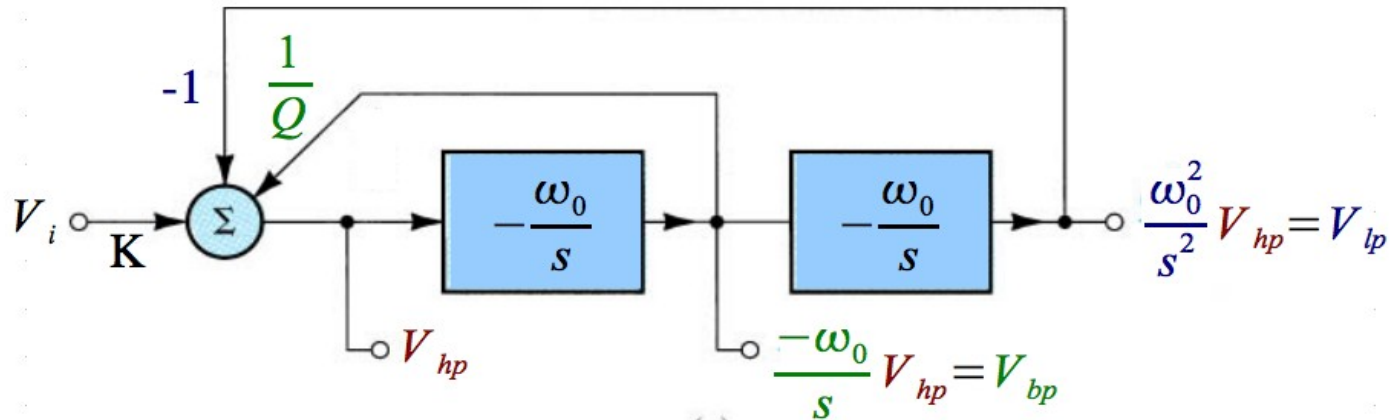

$$V_{hp} = -V_{lp} + \frac{1}{Q} V_{bp} + K V_i \Rightarrow V_{hp} = -\frac{\omega_0^2}{s^2} V_{hp} - \frac{1}{Q} \frac{\omega_0}{s} V_{hp} + K V_i$$

$$\Rightarrow G_{hp}(s) = \frac{V_{hp}}{V_i} = \frac{K}{1 + \frac{1}{Q} \frac{\omega_0}{s} + \frac{\omega_0^2}{s^2}} = \frac{K s^2}{s^2 + \frac{\omega_0}{Q} s + \omega_0^2}$$

Numeric (Spec) Eqs.

Specs: ω_0 or f_0 , Q & K

$G_{bp}(s)$ and $G_{lp}(s)$ are also available.


Two Integrator Loop cont.

High Pass Output:
$$G_{hp}(s) = \frac{V_{hp}}{V_i} = \frac{K s^2}{s^2 + \frac{\omega_0}{Q} s + \omega_0^2}$$

Bandpass Output:
$$G_{bp}(s) = \frac{V_{bp}}{V_i} = \frac{-\omega_0}{s} \frac{V_{hp}}{V_i} = \frac{-K \omega_0 s}{s^2 + \frac{\omega_0}{Q} s + \omega_0^2}$$

Lowpass Output:
$$G_{lp}(s) = \frac{V_{lp}}{V_i} = \frac{-\omega_0}{s} \frac{V_{bp}}{V_i} = \frac{K \omega_0^2}{s^2 + \frac{\omega_0}{Q} s + \omega_0^2}$$

Implementation

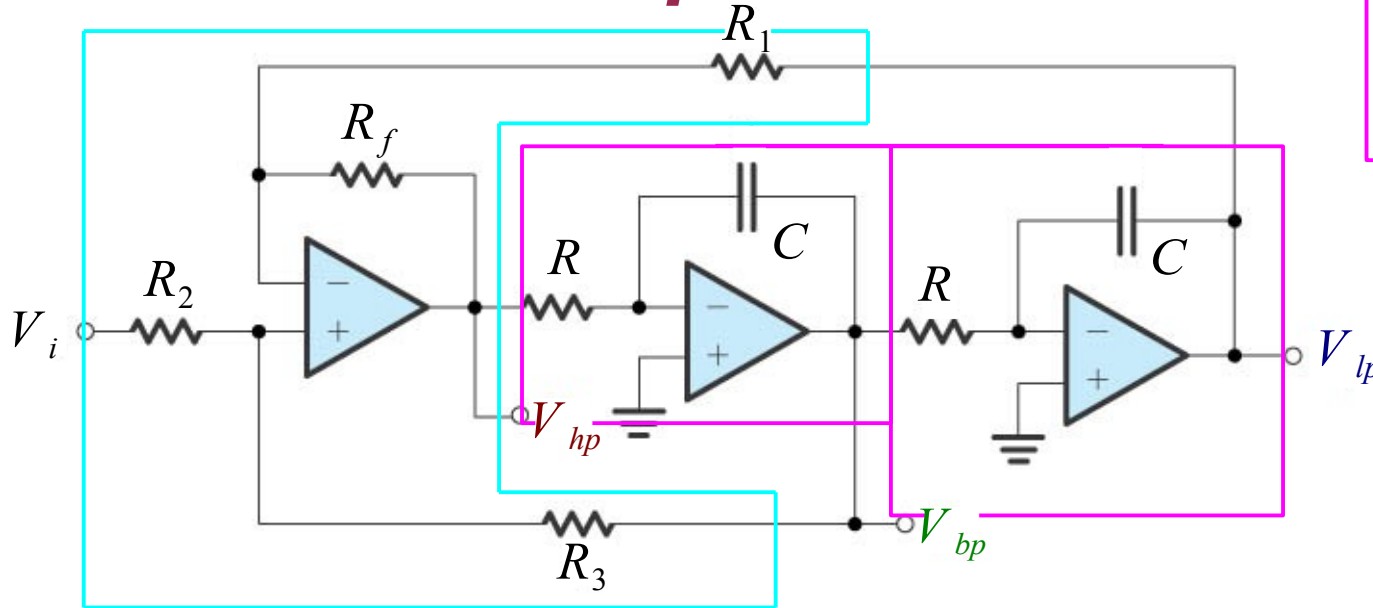

Inverting Integrators $\omega_0 = \frac{1}{CR}$

Summing Amp

$$V_{bp} = -\frac{\omega_0}{s} V_{hp}$$

$$V_{lp} = \frac{\omega_0^2}{s^2} V_{hp}$$

$$V_{hp} = \left[\frac{R_f}{R_1} \right] V_{lp} + \left[\frac{R_2}{R_2 + R_3} \left(1 + \frac{R_f}{R_1} \right) \right] V_{bp} + \left[\frac{R_3}{R_2 + R_3} \left(1 + \frac{R_f}{R_1} \right) \right] V_i$$

Symbolic Eq.

Numeric Eq. $V_{hp} = (-1) V_{lp} + \frac{1}{Q} V_{bp} + K V_i$

Numeric Specs: ω_0 or f_0 , Q & K

Numeric Eq. = Symbolic Eq.

Implementation cont.

$$V_{hp} = -\frac{R_f}{R_1} V_{lp} + \frac{R_2}{R_2 + R_3} \left(1 + \frac{R_f}{R_1} \right) V_{bp} + \frac{R_3}{R_2 + R_3} \left(1 + \frac{R_f}{R_1} \right) V_i$$

Set: $R_f = R_1$ And compare terms:

$$V_{hp} = (-1) V_{lp} + \frac{2R_2}{R_2 + R_3} V_{bp} + \frac{2R_3}{R_2 + R_3} V_i \quad \text{Symbolic Eq.}$$

$$V_{hp} = (-1) V_{lp} + \frac{1}{Q} V_{bp} + K V_i \quad \text{Numeric Eq.}$$

$$Q = \frac{R_2 + R_3}{2R_2} \Rightarrow Q = \frac{1}{2} \left(1 + \frac{R_3}{R_2} \right) \Rightarrow$$

$$\frac{R_3}{R_2} = 2Q - 1 = \frac{2}{K} - 1 \Rightarrow K = 2 - \frac{1}{Q}$$

$$K = \frac{2R_3}{R_2 + R_3} \Rightarrow \frac{1}{K} = \frac{1}{2} \left(1 + \frac{R_2}{R_3} \right)$$

$$\frac{1}{CR} = \omega_0$$

Design Eqs.

Design Equations

$$RC = \frac{1}{\omega_0} \quad \text{Given } \omega_0 = 2\pi f_0, \text{ choose } C, \text{ calculate } R$$


$$R_f = R_1 \quad \text{Choose } R_f, \text{ Calculate } R_1 \text{ or vice-versa.}$$

$$\frac{R_3}{R_2} = 2Q - 1 \quad \text{Given } Q, \text{ choose } R_2, \text{ calculate } R_3 \text{ or vice-versa.}$$

$$K = 2 - \frac{1}{Q} \quad K \text{ is fixed by choice of } Q.$$

- 2 independent requirements (ω_0 and Q)
- 3 independent components (C , R_f , and R_2)
- 3 dependent components (R , R_1 , and R_3)

MFM LP Example

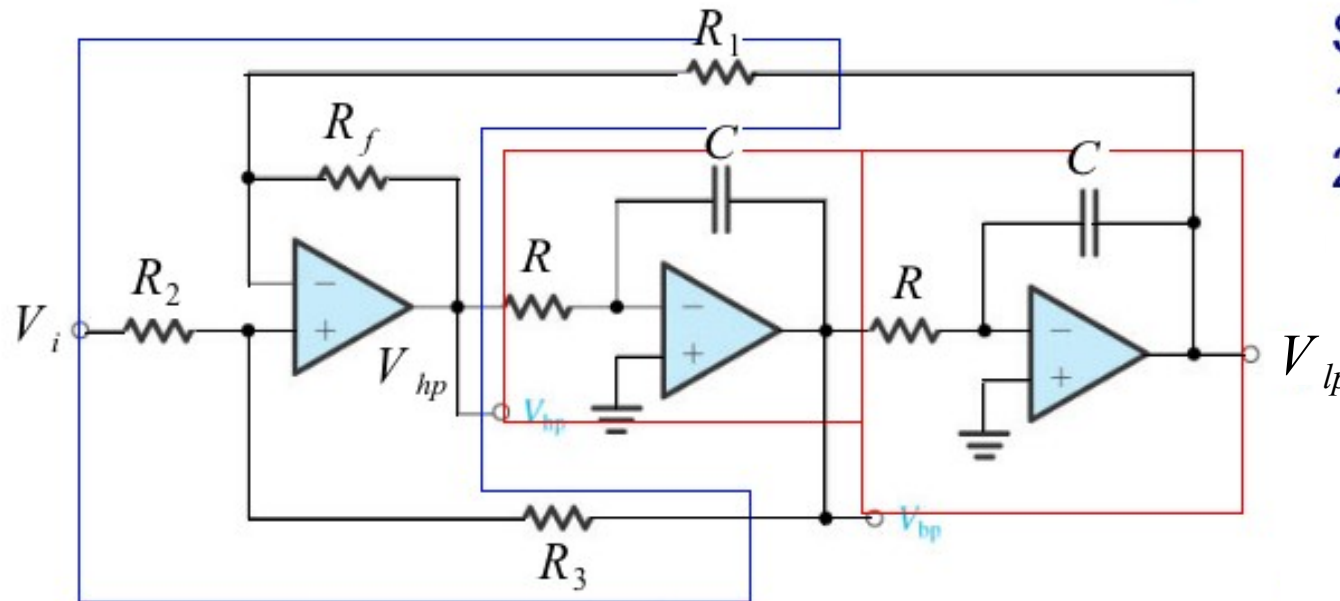

Specifications:

1. MFM 2nd Order LP
2. $f_p = f_0 = 20 \text{ kHz}$

symbolic $G_{lp}(s)$

$$G_{lp}(s) = \frac{V_{lp}}{V_i} = \frac{\frac{R_3}{R_2 + R_3} \left(1 + \frac{R_f}{R_1}\right) \omega_0^2}{s^2 + s \frac{R_2}{R_2 + R_3} \left(1 + \frac{R_f}{R_1}\right) \left(\frac{1}{RC}\right) + \frac{R_f}{R_1} \left(\frac{1}{RC}\right)^2} = \frac{K \omega_0^2}{s^2 + s \sqrt{2} \omega_0 + \omega_0^2}$$

specification $G_{lp}(s)$

MFM LP Example - cont.

Choosing $R_f = R_1 = R_2 = 10\text{ k}\Omega \Rightarrow \frac{R_f}{R_1} = 1$

$$G_{lp}(s) = \frac{V_{lp}}{V_i} = \frac{\frac{R_3}{R_2 + R_3} \left(1 + \frac{R_f}{R_1}\right) \omega_0^2}{s^2 + s \frac{R_2}{R_2 + R_3} \left(1 + \frac{R_f}{R_1}\right) \left(\frac{1}{RC}\right) + \frac{R_f}{R_1} \left(\frac{1}{RC}\right)^2} = \frac{K \omega_0^2}{s^2 + s \sqrt{2} \omega_0 + \omega_0^2}$$

$$RC = RC = \omega_0 = 2\pi f_0$$

$$\frac{2R_2}{R_2 + R_3} = \sqrt{2} \Rightarrow \frac{R_3}{R_2} = \frac{2}{\sqrt{2}} - 1 = \sqrt{2} - 1 = 0.414$$

$$\frac{2R_3}{R_2 + R_3} = K \Rightarrow \frac{R_2}{R_3} = \frac{2}{K} - 1 \Rightarrow K = 2 \frac{\sqrt{2} - 1}{\sqrt{2}} = 0.586$$

MFM LP Example - cont.

Design Eqs.

Choose $R_2 = R_f = R_1 = 10\text{ k}\Omega$
 $C = 7.95\text{ nF}$

$$\frac{1}{RC} = \omega_0 = 2\pi f_0 = 125.66\text{ k rad/sec}$$

$$R = \frac{1}{C(125.66\text{ k rad/sec})} = \frac{1}{7.95 \cdot 10^{-9} (125.66\text{ k rad/sec})} = 1\text{ k}\Omega$$

$$\frac{2R_2}{R_2 + R_3} = \sqrt{2} \Rightarrow \frac{R_3}{R_2} = 0.414 \Rightarrow R_3 = 4.14\text{ k}\Omega$$

$$\frac{2R_3}{R_2 + R_3} = K \Rightarrow K = 0.586$$

Final Design

$$R_2 = R_f = R_1 = 10\text{ k}\Omega$$


$$R_3 = 4.14\text{ k}\Omega$$

$$R = 1\text{ k}\Omega$$

$$C = 7.95\text{ nF}$$

$$K = 0.586$$


MFM LP Example - cont.

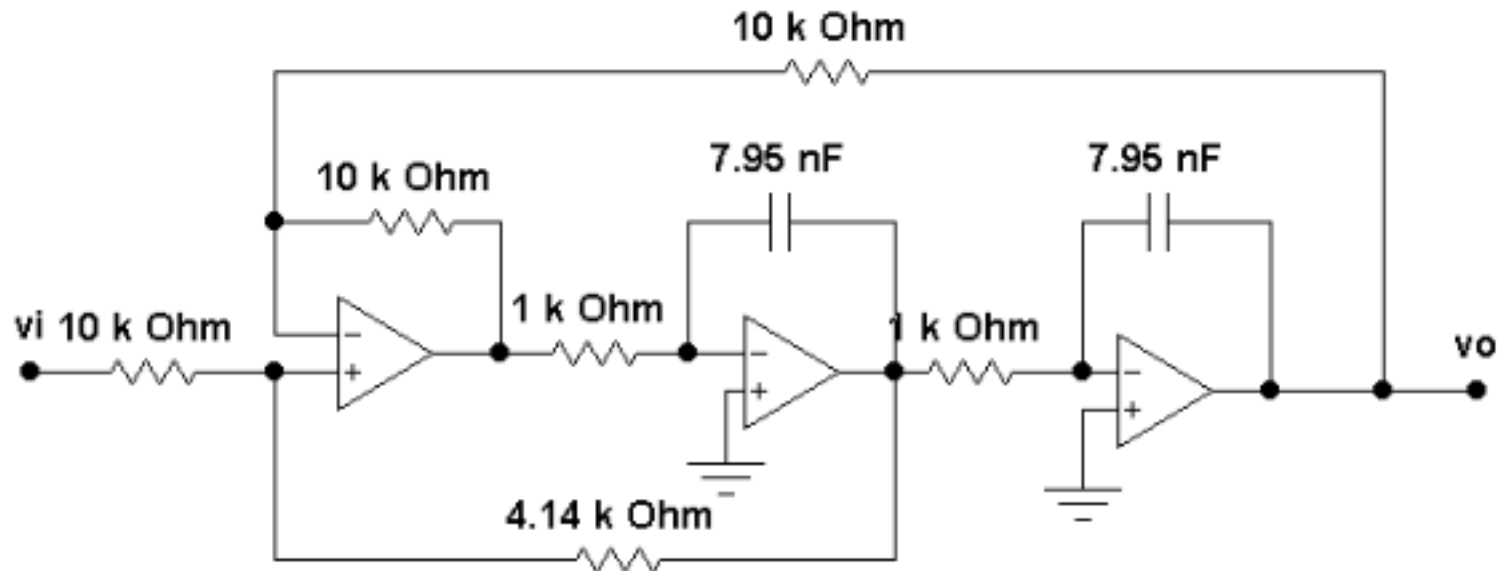


$$K = 0.586$$

$$G_{lp}(j0) = 20 \log_{10}(0.586) = -4.64 \text{ dB}$$

MFM LP Example - Bode Plots

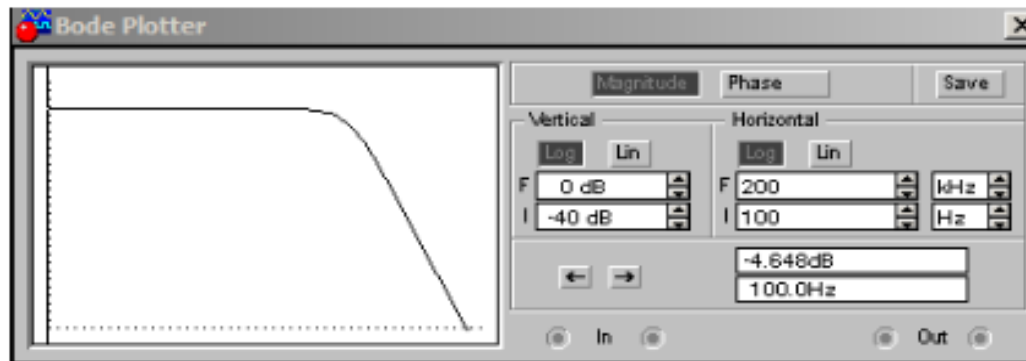


Passband Gain

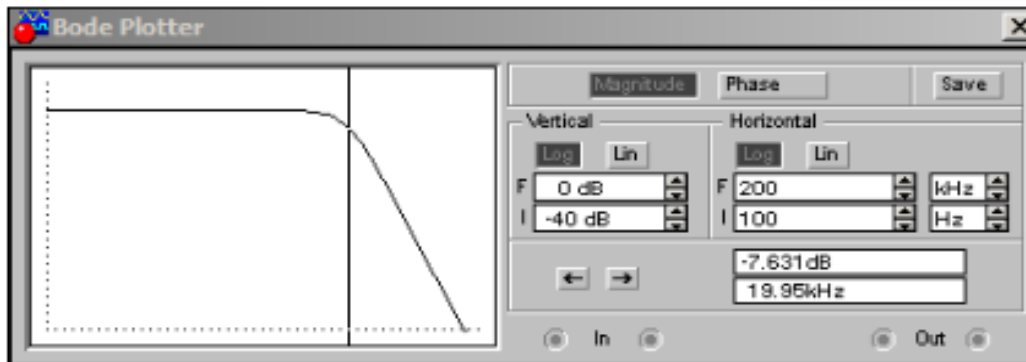

3dB Frequency

Adding Finite Zeros – (Notches)

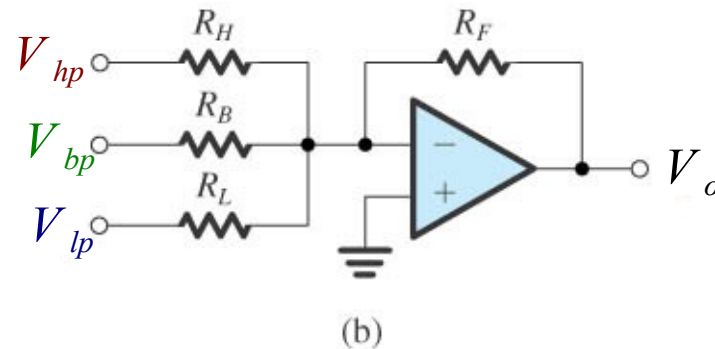To be able to create notches in the response, we need a second summing amplifier:




Where the weighted inputs come from the highpass, bandpass, and lowpass outputs of the feedback circuit.



Filter Type	s-plane zeros/poles	$ G $
<p>2nd order Notch (N)</p> $G(s) = a_2 \frac{s^2 + \omega_N^2}{s^2 + s \frac{\omega_0}{Q} + \omega_0^2}$ <p>$\omega_N = \omega_0$</p>		<p>$G(j0) = G(j\infty) = a_2$</p>
<p>2nd order LP Notch (LPN)</p> $G(s) = a_2 \frac{s^2 + \omega_N^2}{s^2 + s \frac{\omega_0}{Q} + \omega_0^2}$ <p>$\omega_N > \omega_0$</p>		<p>$G(j0) = a_2 \frac{\omega_N^2}{\omega_0^2}$</p> <p>$G(j\infty) = a_2$</p>
<p>2nd order HP Notch (HPN)</p> $G(s) = a_2 \frac{s^2 + \omega_N^2}{s^2 + s \frac{\omega_0}{Q} + \omega_0^2}$ <p>$\omega_N < \omega_0$</p>		<p>$G(j0) = a_2 \frac{\omega_N^2}{\omega_0^2}$</p> <p>$G(j\infty) = a_2$</p>

Notch Creation

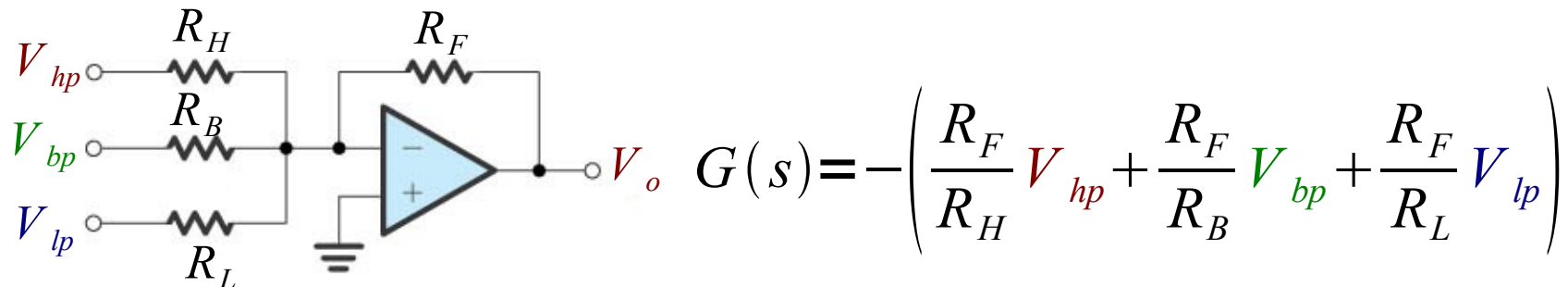All the output point transfer functions contain the same denominator, so only the numerator terms will be affected:



$$G(s) = -K \frac{(R_F/R_H)s^2 - (R_F/R_B)\omega_0 s + (R_F/R_L)\omega_0^2}{s^2 + (\omega_0/Q)s + \omega_0^2}$$

For a notch at $\omega = \omega_N$, no connection is made to V_{bp} , i.e. $R_B = \infty$

“Big Picture” Filter Design Tasks

1. Design $G(s)$ from filter specs.
2. Determine filter structure (block diagram) to realize $G(s)$.
3. Determine filter circuit(s) to implement structure.
4. Determine component values.


Filter Design CAD Tools on the Market

1. MatLab - Mathworks
2. FILTER PRO – Texas Instruments
3. Aktiv Filter – New Wave Instruments
4. Filter Lab – Microchip
5. Filter Wiz Pro – Schematica
6. FilterCAD – Linear Technology

Butterworth (MFM)

Matlab:

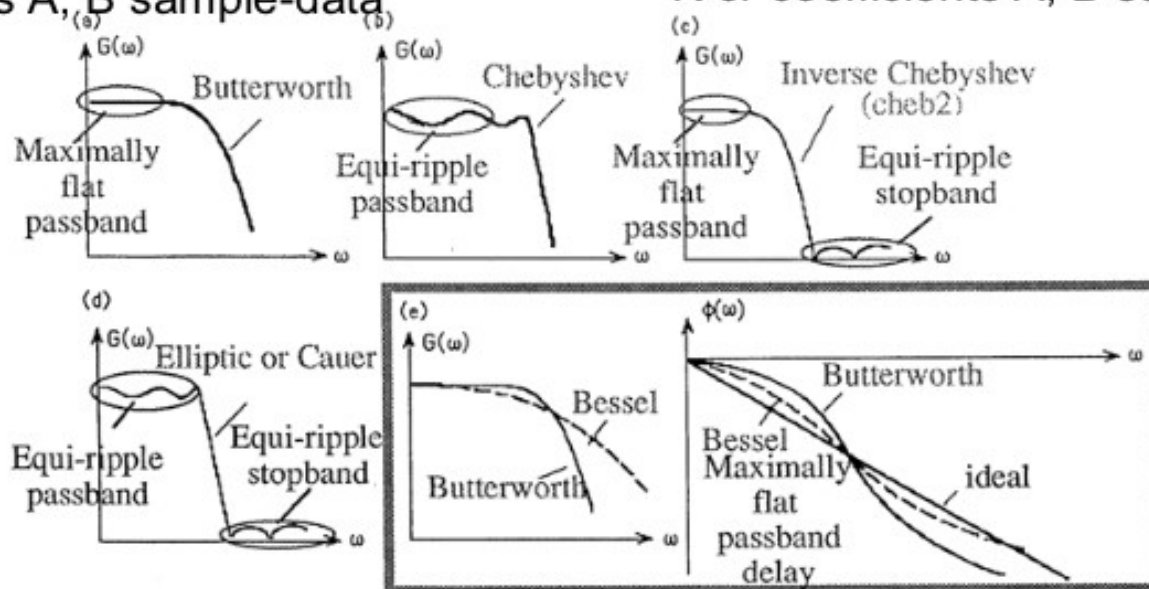1. buttord (W_p, W_s, R_p, R_s) $\Rightarrow n$
2. buttap (n) \Rightarrow poles, zeros, K cont-time
3. butter ($n, W_n, ftype$) \Rightarrow poles, zeros, K or coefficients A, B sample-data



Elliptic

Matlab:

1. ellipord (W_p, W_s, R_p, R_s) $\Rightarrow n$
2. ellipap (n, R_p, R_s) \Rightarrow poles, zeros, K cont-time
3. ellip ($n, R_p, W_n, ftype$) \Rightarrow poles, zeros, K or coefficients A, B sample-data