




Penn
UNIVERSITY of PENNSYLVANIA


ESE319 Introduction to Microelectronics

Common Emitter BJT Amplifier

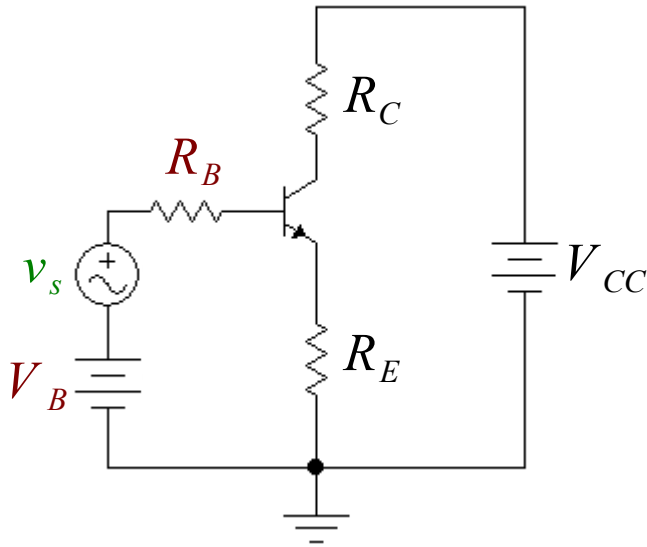Adding a signal source to the single power supply bias amplifier




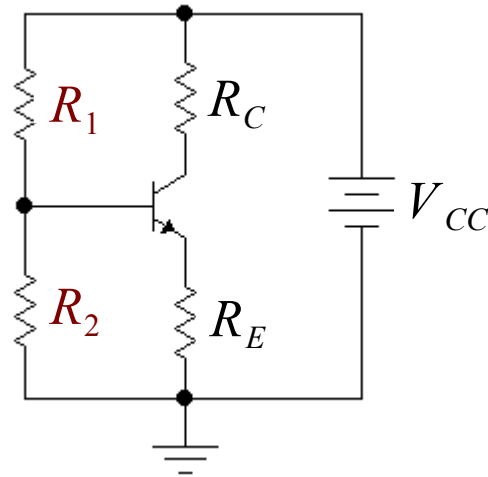Desired effect – addition of bias and signal sources




Starting point - single dc source

Wrong Way to Combine Sources

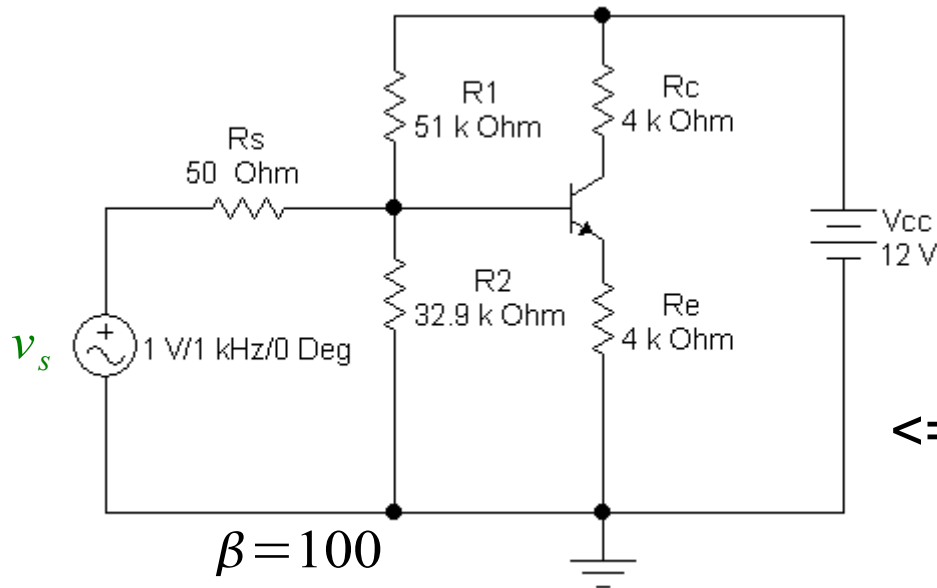


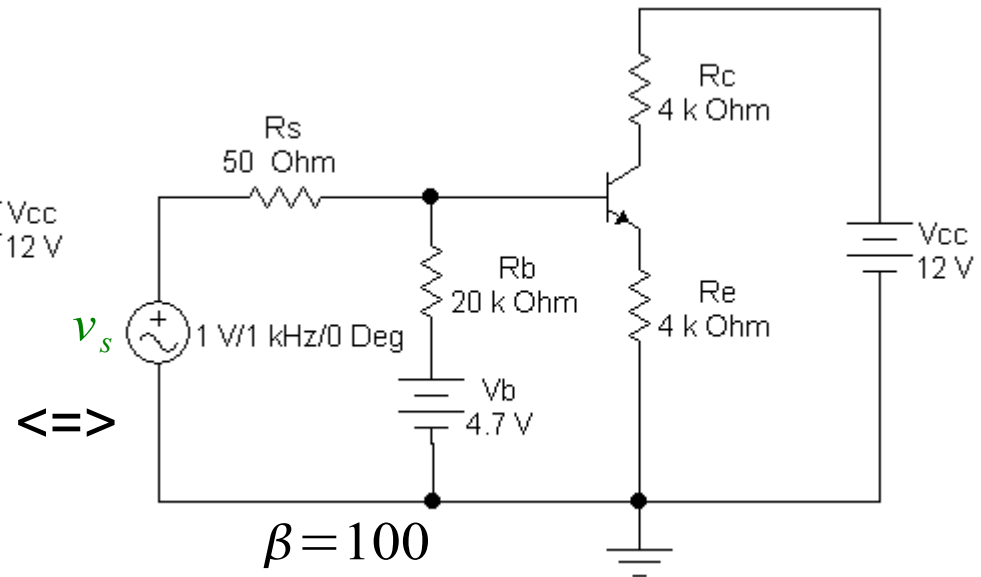Source with low output impedance upsets bias.



Thevenin equivalent at base:

Wrong Way - Continued

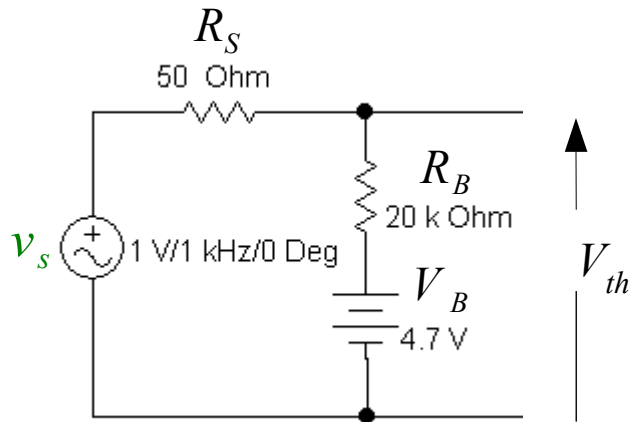

$$V_{th} = \frac{50}{20000 + 50} V_B \approx \frac{5}{2000} V_B \quad (v_s = 0)$$

$$R_{th} = R'_B = R_B \parallel R_S = \frac{50 \cdot 20000}{50 + 20000} \approx 50 \Omega$$


The signal source effectively “shorts out” the bias source!

The signal source v_s is essentially unaffected by the bias source V_B . (Why? What is its Thevenin equivalent?)

To analyze,

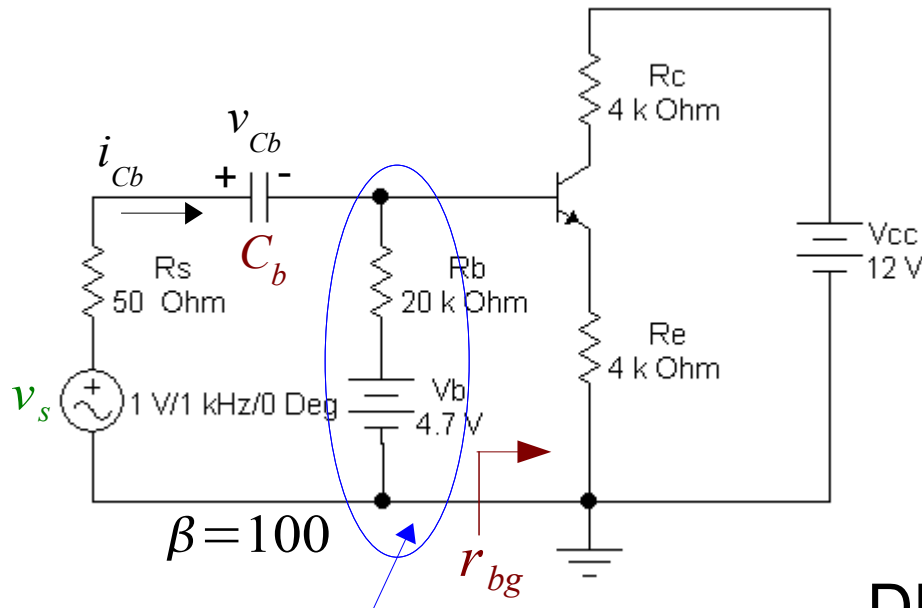1. Isolate base circuit,
2. Use superposition,
3. Find Thevenin equivalent for the base bias source, V_B :

The Right Way – Use a “Blocking” Capacitor





For convenience lets continue to use the “base bias Thevenin equiv”.

1. Capacitor C_b is an OPEN at dc and R_S does not affect the bias!
2. C_b charges to the dc bias source, V_B , to satisfy Kirchoff's voltage law.
3. The dc bias is in series with the signal source v_s , i.e. $v_S = V_B + v_s$

DESIGN GOAL: for $f \geq f_{min1}$, set the value of C_b so that its ac voltage drop v_{Cb} is negligible at and above the low frequency cutoff at say f_{min1} .

Blocking Capacitor Selection

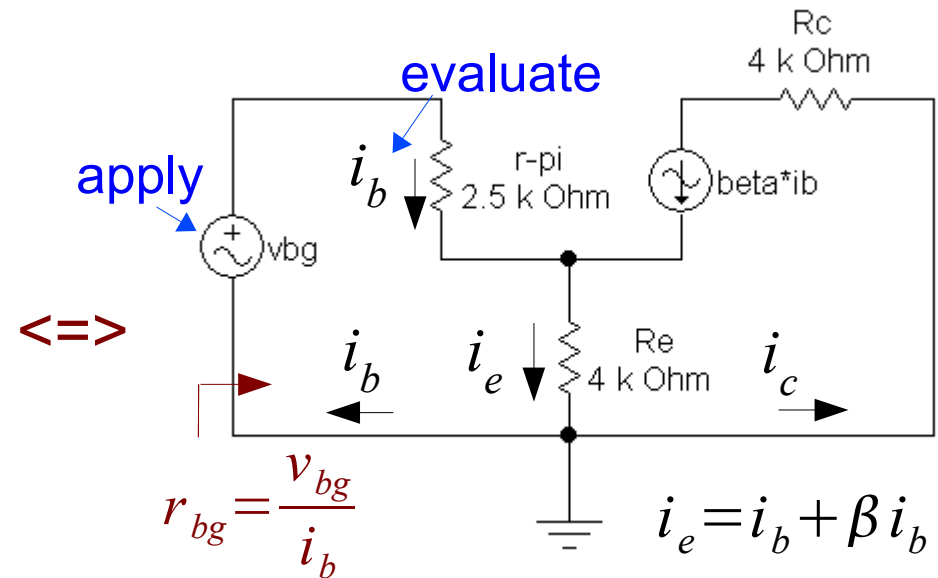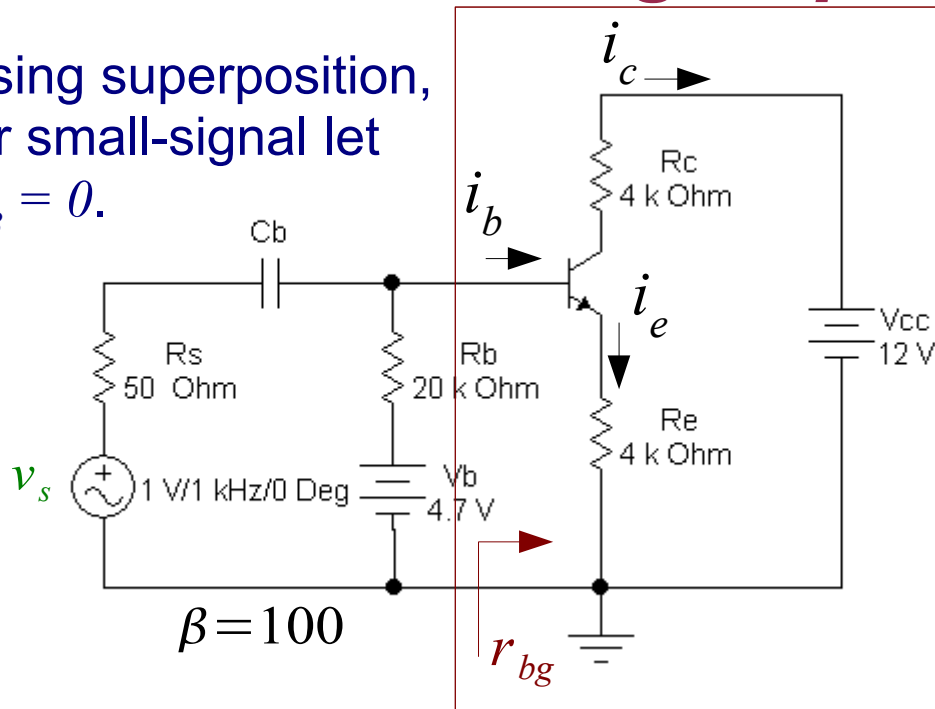Using superposition, for small-signal let $V_B = 0$.




Use the small signal equivalent circuit and superposition to estimate the input resistance of the *transistor*.

$$v_{bg} = i_b r_{\pi} + i_e R_E = i_b r_{\pi} + i_b (\beta + 1) R_E$$

$$r_{bg} = \frac{v_{bg}}{i_b} = r_{\pi} + (\beta + 1) R_E \approx \beta R_E$$

Capacitor Selection- continued

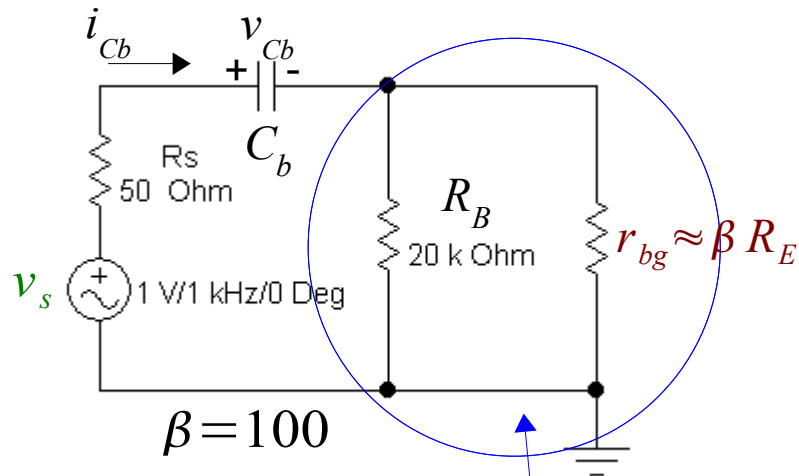The signal source “sees” the $20\text{ k}\Omega$ bias source resistance in parallel with . So the signal source equivalent circuit is:



$$r_{bg} \approx 100 R_E = 400\text{ k}\Omega$$

Therefore:

$$R_B \parallel r_{BG} = \frac{400}{420} 20 \approx 20\text{ k}\Omega = R_B$$

The capacitor voltage drop is:

$$v_{Cb} = \frac{1}{j\omega C_b} i_{Cb}$$


Where the capacitor current is:

$$v_s = i_{Cb} \left(R_S + R_B \parallel r_{bg} + \frac{1}{j\omega C_b} \right)$$

$$i_{Cb} \approx \frac{v_s}{R_B + \frac{1}{j\omega C_b}} \Rightarrow v_{Cb} \approx \frac{v_s}{j\omega C_b R_B + 1}$$

Goal: $\omega C_b R_B \gg 1$

Capacitor Selection - continued

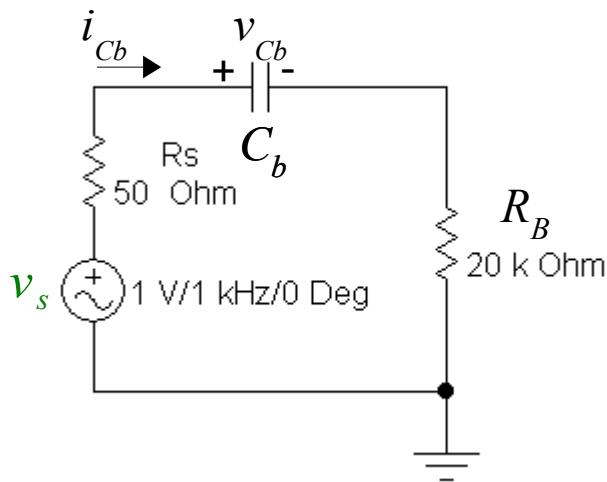

$$|v_{Cb}| \approx \frac{v_s}{|j\omega C_b R_B + 1|} \quad \text{or} \quad f_{R_B C_b} = \frac{1}{2\pi C_b R_B}$$

CONSERVATIVE DESIGN GOAL: Choose C_b for negligible voltage drop at v_{Cb} for $f \geq f_{min1}$, i.e.

$$|v_{Cb}| \approx \frac{v_s}{|j\omega C_b R_B + 1|} \leq \frac{v_s}{10} \quad \text{for } f \geq f_{min1}$$


$$|v_{Cb}| \leq \frac{v_s}{10} \Rightarrow 2\pi f_{min1} C_b R_B \geq 10 \Rightarrow C_b \geq \frac{10}{2\pi f_{min1} R_B}$$

OR

DESIGN GOAL: Choose C_b so that $f_{R_B C_b} = 0.1 f_{min1}$,

$$\text{i.e.} \quad f_{Cb} = \frac{1}{2\pi C_b R_B} = 0.1 f_{min1} \Rightarrow C_b = \frac{10}{2\pi f_{min1} R_B}$$

Capacitor Selection - continued

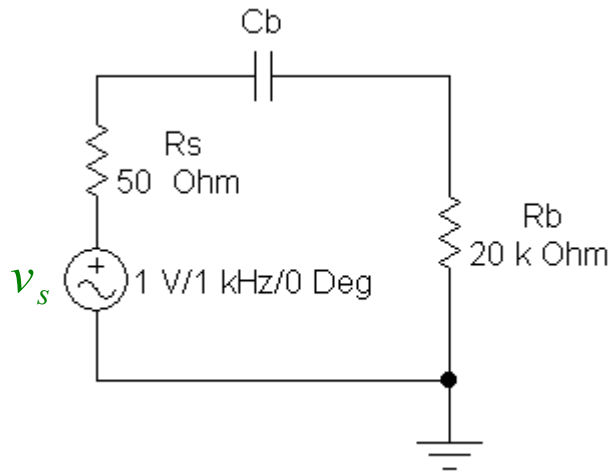

Select the LOWEST frequency of interest. This sets the lower bound on C_b . Using $f_{min1} = 20 \text{ Hz}$ frequency for our example circuit:

$$2\pi f_{min1} = 2\pi \cdot 20 \approx 6.28 \cdot 20 = 125.6 \text{ sec}^{-1}$$


$$C_b \geq \frac{10}{2\pi f_{min1} R_B}$$

$$C_{b-min} = \frac{10}{125.6 \cdot 20 \cdot 10^3} = \frac{10^{-6}}{0.25} = 4 \mu F$$

$$C_{b-min} = \frac{10}{2\pi f_{min1} R_B}$$

ANY capacitor larger than $4 \mu F$ will also do the job!

Common Emitter Unity Gain Amplifier

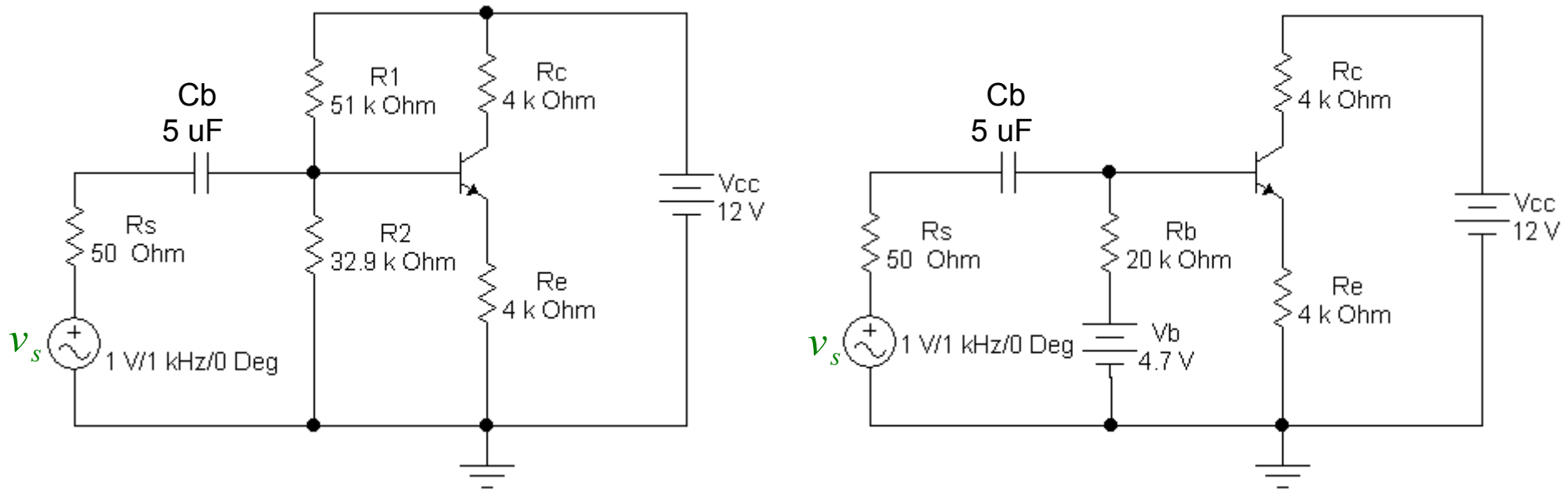


Equivalent circuits

How can we achieve reasonable gain with this circuit?

Solution: Split R_E and use *capacitor bypassing*.

Bypass for Gain

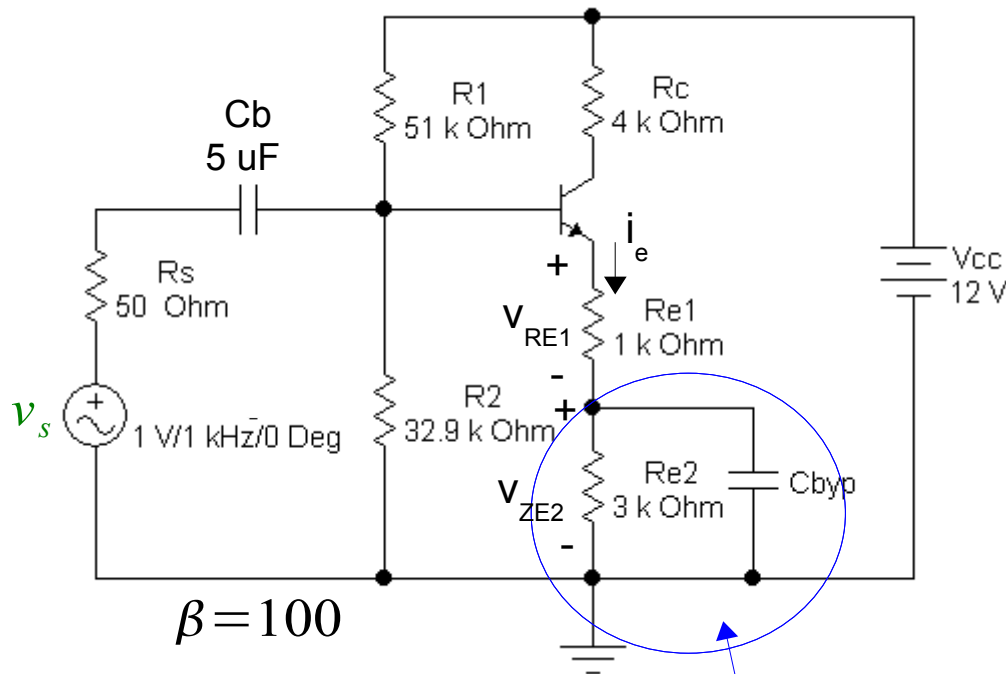

$$Z_{E2} = R_{E2} \parallel \frac{1}{j\omega C_{byp}}$$

Procedure:


1. Split the emitter resistor in two. Later, we will show that the voltage gain will be close to $-R_C/R_{E1}$.

2. Bypass R_{E2} with a capacitor C_{byp} that looks like a near “short circuit” at some suitable low frequency ($f_{min2} \geq f_{min1}$).


i.e. $|v_{ZE2}| \ll |v_{RE1}|$ for $f \geq f_{min2}$

$$v_{RE1} = i_e R_{E1} \quad \& \quad v_{ZE2} = i_e Z_{E2}$$

Bypass for Gain - continued

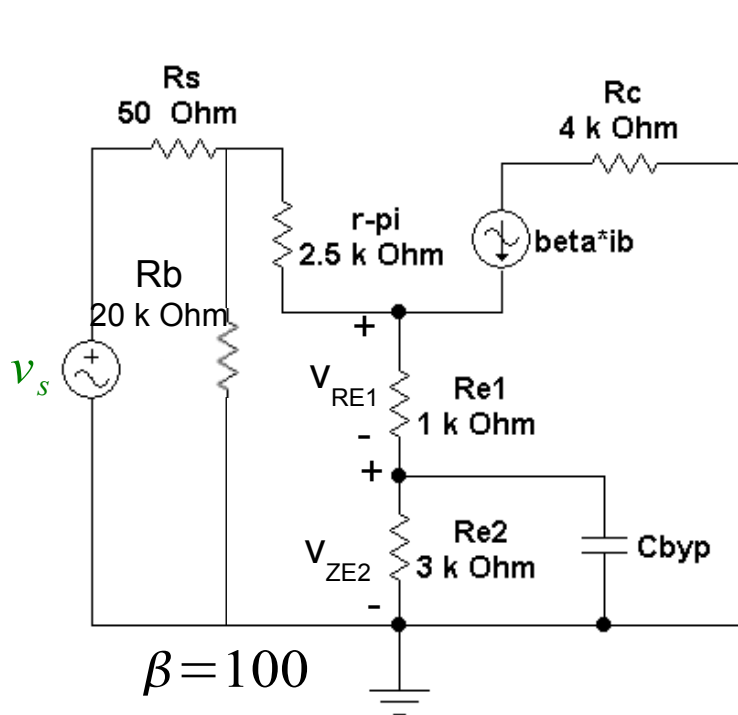


Small signal circuit

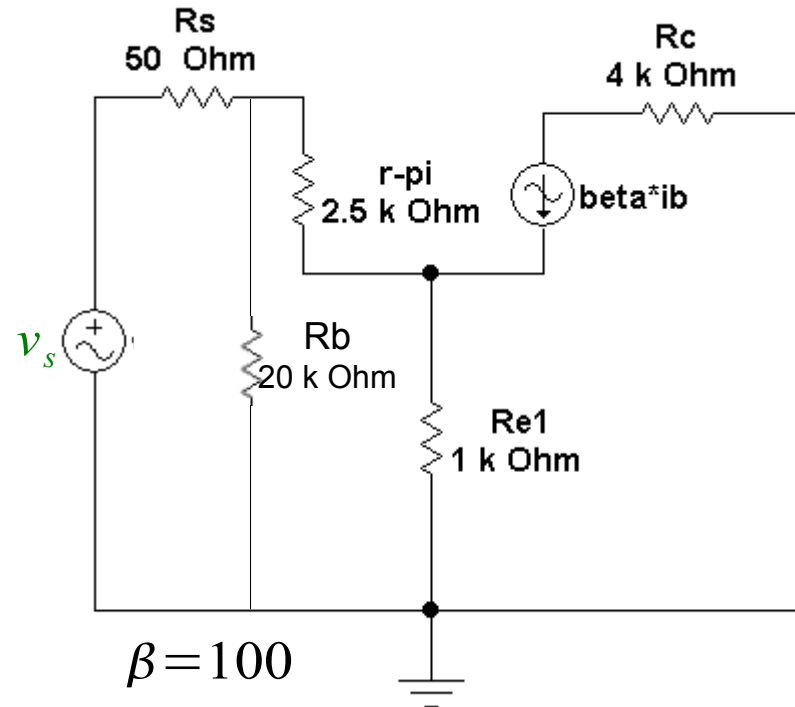

Desired circuit for $f \geq f_{min2}$

i.e. CONSERVATIVE DESIGN GOAL:
Choose C_{byp} s.t. $|v_{ZE2}| \ll |v_{RE1}|$ for $f \geq f_{min2}$

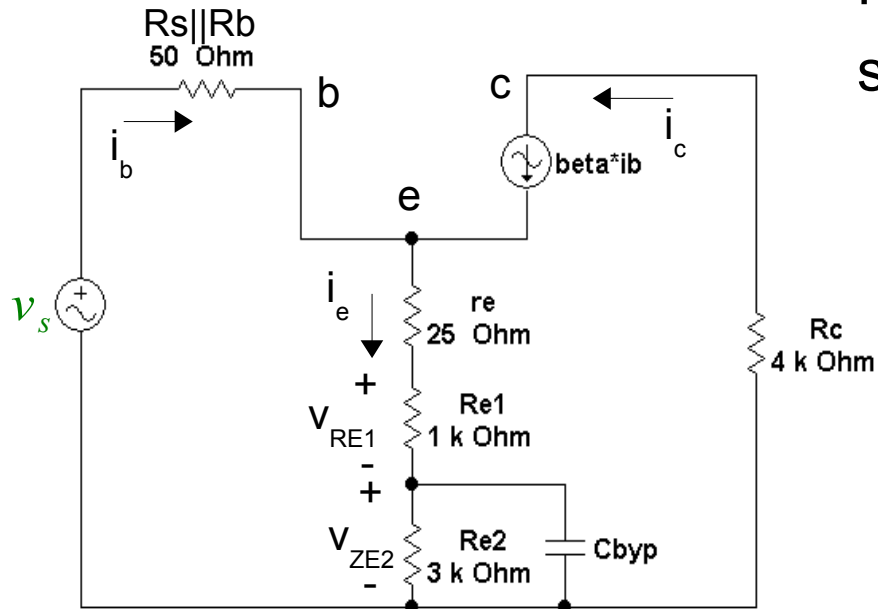

Need to develop a design equation for C_{byp}
 s.t. DESIGN GOAL: $|v_{ZE2}| \ll |v_{RE1}|$

where $Z_{E2} = \frac{R_{E2}}{j\omega C_{byp} R_{E2} + 1}$

$$\left| \frac{v_{ZE2}}{v_{RE1}} \right| = \left| \frac{Z_{E2} i_e}{R_{E1} i_e} \right| = \left| \frac{R_{E2}/R_{E1}}{j\omega C_{byp} R_{E2} + 1} \right| \leq \frac{1}{10}$$

or

$$\left| j2\pi f_{min2} C_{byp} R_{E2} + 1 \right| \geq 10 \frac{R_{E2}}{R_{E1}} \gg 1$$

$$C_{byp} \geq 10 \frac{R_{E2}}{R_{E1}} \frac{1}{2\pi f_{min2} R_{E2}} = \frac{10}{2\pi f_{min2} R_{E1}}$$

$$C_{byp} = \frac{10}{2\pi f_{min2} R_{E1}}$$

$$i_e = (\beta + 1) i_b$$

$$\beta = 100$$

$$r_e \ll R_{E1}$$

$$v_{RE1} = i_e R_{E1} \quad \& \quad v_{ZE2} = i_e Z_{E2}$$

In Lab 2

$$C_b = \frac{10}{2\pi f_{min1} R_B}$$

Choose C_b s.t. $\frac{1}{2\pi f_{min1} C_b} = R_{in} = R_B \parallel r_{bg} \approx R_B$

$$f_{min1} = 10\text{Hz}$$

$$C_b = \frac{1}{2\pi f_{min1} R_B} = \frac{1}{20\pi R_B}$$

$$C_{byp} = \frac{10}{2\pi f_{min2} R_{E1}}$$

Choose C_{byp} s.t. $\frac{1}{2\pi f_{min2} C_{byp}} = \frac{R_E}{2}$


$$f_{min2} = 100\text{Hz}$$

$$C_{byp} = \frac{1}{2\pi f_{min2} R_E/2} = \frac{1}{100\pi R_E}$$


$$C_{byp} = \frac{10}{2\pi f_{min} R_{E1}} = \frac{10}{2\pi \times 20 \times 1000} F = 79.6 \mu F$$

You may choose $C_{byp} = 100 \mu F$

Final Design

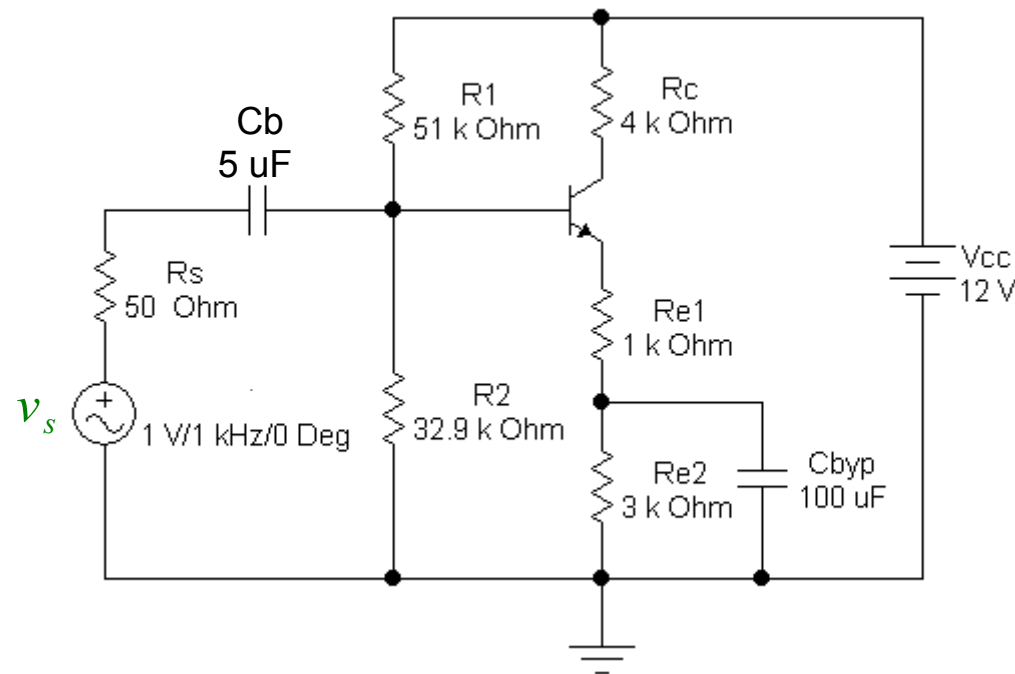

Gain Calculation in Passband

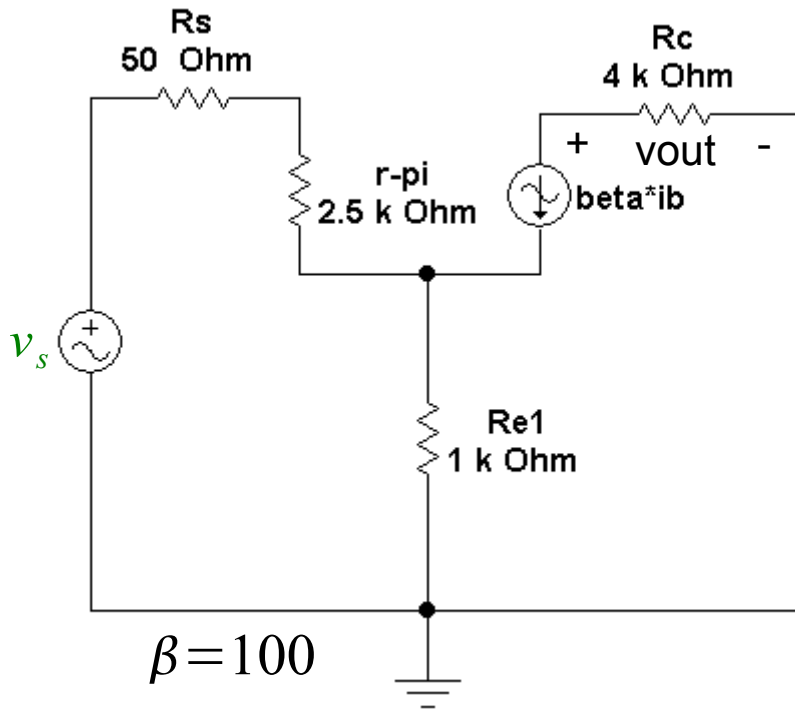

Passband model

Simple gain calculation:


$$i_b = \frac{v_s}{R_s + r_\pi + (\beta + 1)R_{E1}} \approx \frac{v_s}{(\beta + 1)R_{E1}}$$

$$v_{out} = -R_C i_c = -R_C \beta i_b$$


$$v_{out} = \frac{-\beta R_C}{(\beta + 1)R_{E1}} v_s$$

$$A_v = \frac{v_{out}}{v_s} \approx -\frac{R_C}{R_{E1}} = -4$$

Multisim Simulation

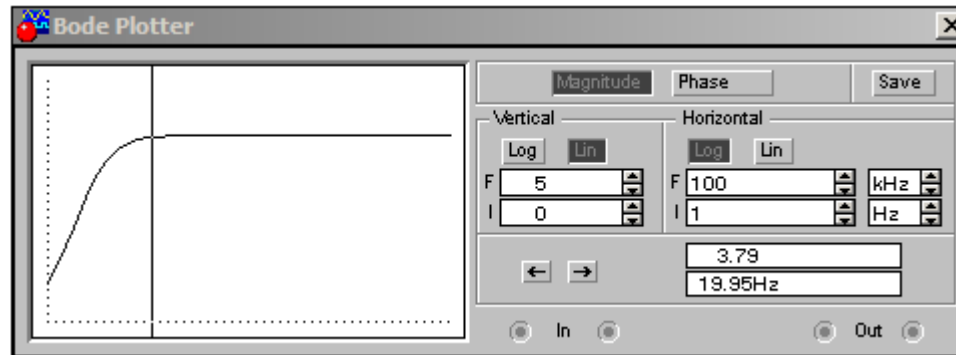

20 Hz Gain

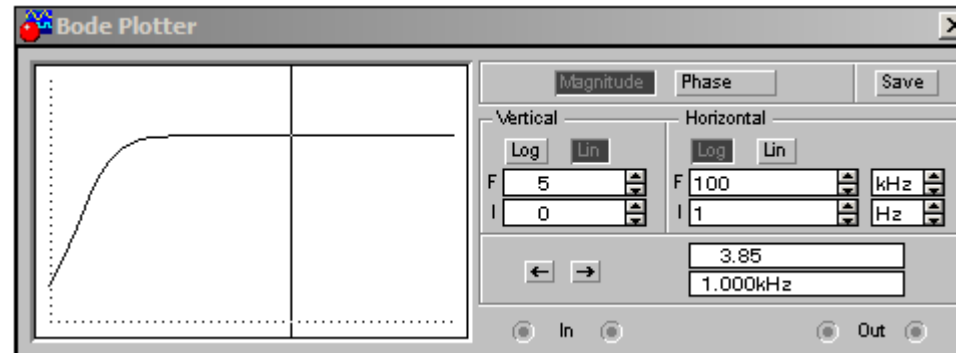


1 kHz Gain



What if R_E is Fully Bypassed?

$$A_v = \frac{v_{out}}{v_s} \approx -\frac{R_C}{\cancel{R_E}} = \infty ?$$

What if R_E is Fully Bypassed?

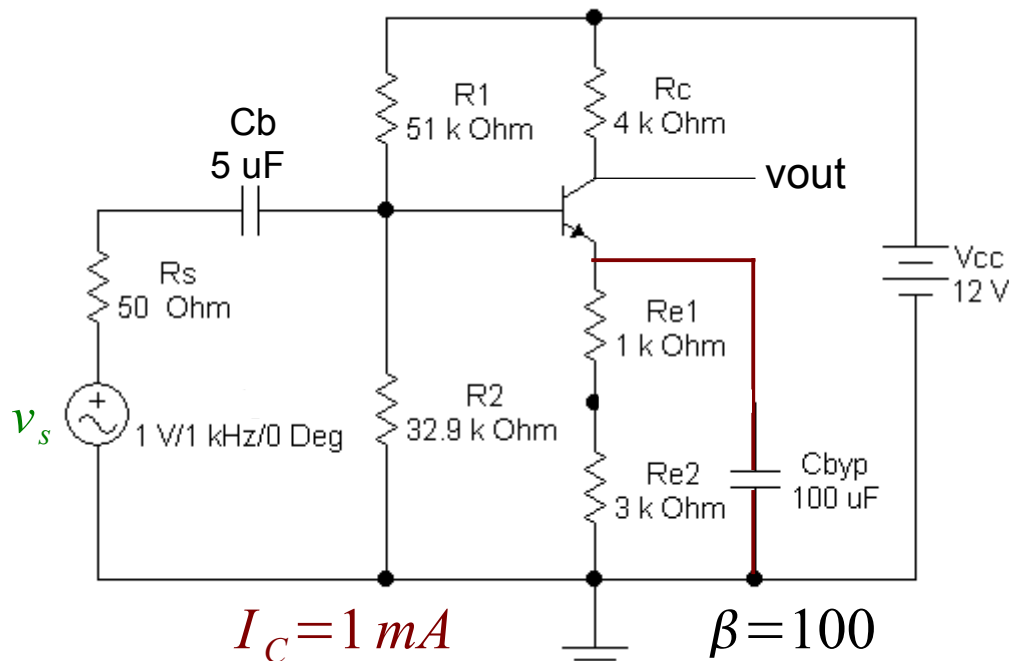

$$g_m = I_C / V_T = 0.04 \text{ S}$$

$$r_\pi = \beta / g_m = 2.5 \text{ k} \Omega$$

$$i_b = \frac{v_s}{R_s + r_\pi + (\beta + 1) R_E} = \frac{v_s}{R_s + r_\pi}$$

$$v_{out} = -R_C i_c = -R_C \beta i_b$$

$$v_{out} = \frac{-\beta R_C}{R_s + r_\pi} v_s \approx \frac{-\beta R_C}{r_\pi} v_s$$

$$= \frac{-\beta R_C}{\beta / g_m} v_s = -g_m R_C v_s$$

$$A_v = \frac{v_{out}}{v_s} \approx -g_m R_C = -160$$