

Common Base BJT Amplifier

Common Collector BJT Amplifier

- Common Collector (Emitter Follower) Configuration
- Common Base Configuration
- Small Signal Analysis
- Design Example
- Amplifier Input and Output Impedances

Basic Single BJT Amplifier Features

| | <u>CE Amplifier</u> | <u>CC Amplifier</u> | <u>CB Amplifier</u> |
|------------------------|-------------------------|--------------------------|---------------------|
| Voltage Gain (A_V) | moderate ($-R_C/R_E$) | low (about 1) | high |
| Current Gain (A_I) | moderate (β) | moderate ($\beta + 1$) | low (about 1) |
| Input Resistance | high | high | low |
| Output Resistance | high | low | high |


VCVS
CCCS

CE BJT amplifier => CS MOS amplifier


CC BJT amplifier => CD MOS amplifier

CB BJT amplifier => CG MOS amplifier

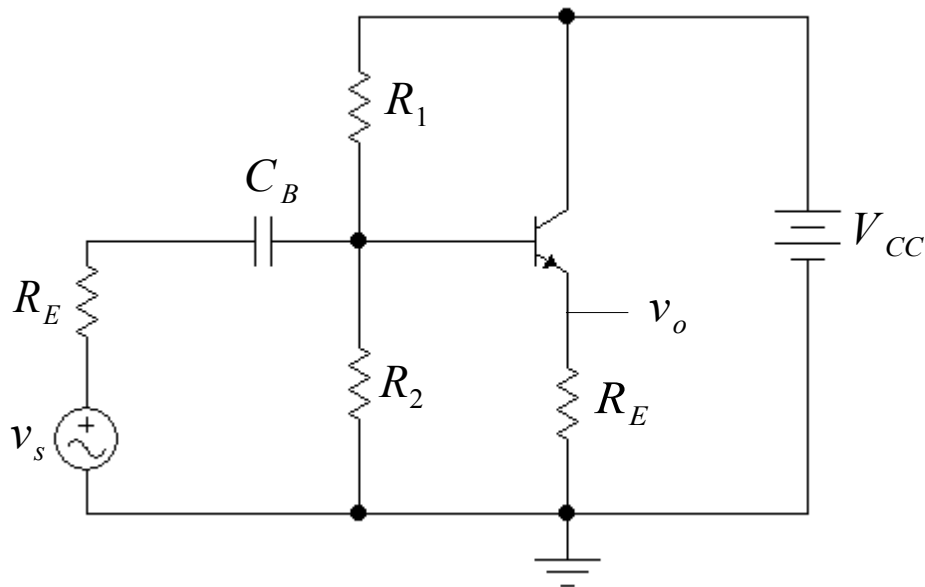Common Collector (Emitter Follower) Amplifier




Voltage Bias Design

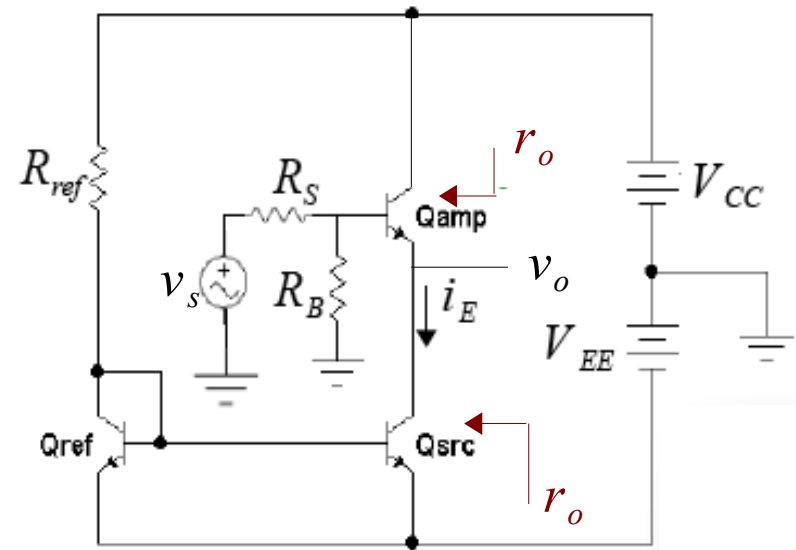

Current Bias Design

In the emitter follower, the output voltage is taken between emitter and ground. The voltage gain of this amplifier is nearly one – the output “follows” the input - hence the name: emitter “follower.”

Emitter Follower Biasing

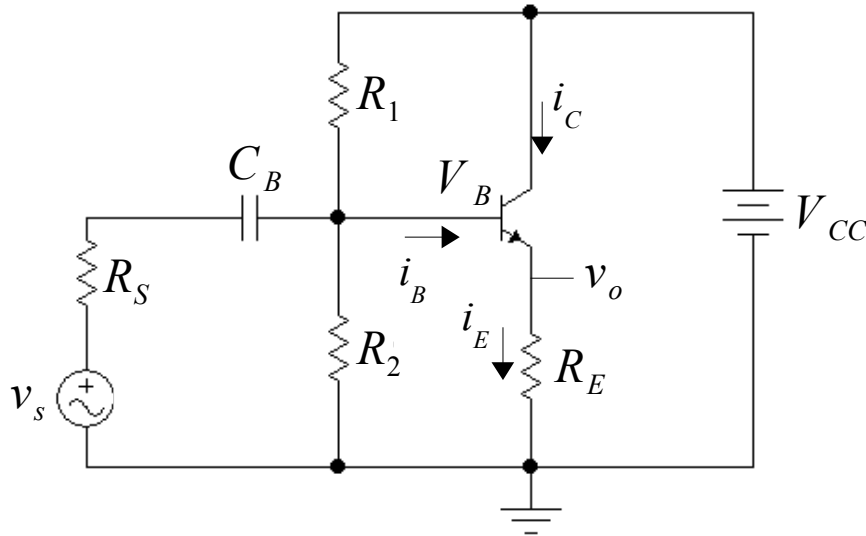

Split bias voltage drops about equally across the transistor V_{CE} (or V_{CB}) and V_{Re} (or V_B).

For simplicity, choose:

$$V_B = \frac{V_{CC}}{2} \Rightarrow R_1 = R_2$$

Then, choose/specified I_E , and the rest of the design follows:

$$R_E = \frac{V_E}{I_E} = \frac{V_{CC}/2 - 0.7}{I_E}$$

For an assumed $\beta = 100$:

As with CE bias design, stable op. pt. $\Rightarrow R_B \ll (\beta + 1) R_E$, i.e.

$$R_B = R_1 \parallel R_2 = \frac{R_1}{2} = (\beta + 1) \frac{R_E}{10} \approx 10 R_E$$

$$R_1 = R_2 = 20 R_E$$

Typical Design

Choose: $I_E = 1 \text{ mA}$

$$V_{CC} = 12 \text{ V}$$


And the rest of the design follows immediately:

$$R_E = \frac{V_E}{I_E} = \frac{12/2 - 0.7}{10^{-3}} = 5.3 \text{ k}\Omega$$


Use standard sizes:

$$R_E = 5.1 \text{ k}\Omega$$


$$R_1 = R_2 = 100 \text{ k}\Omega$$

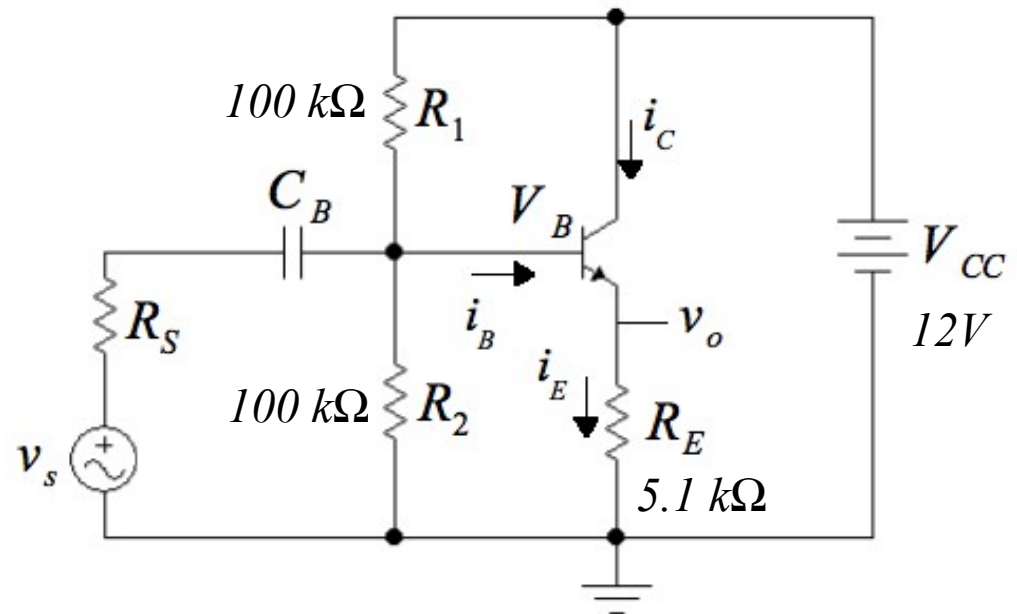

Equivalent Circuits

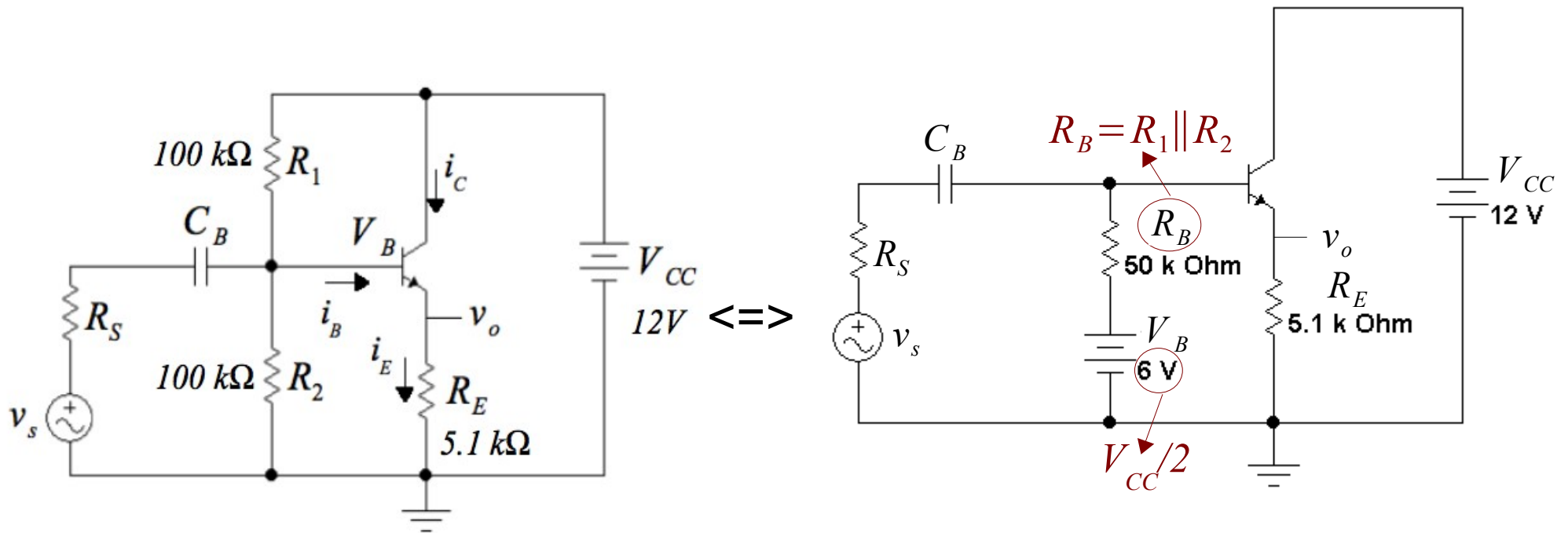

Multisim Bias Check

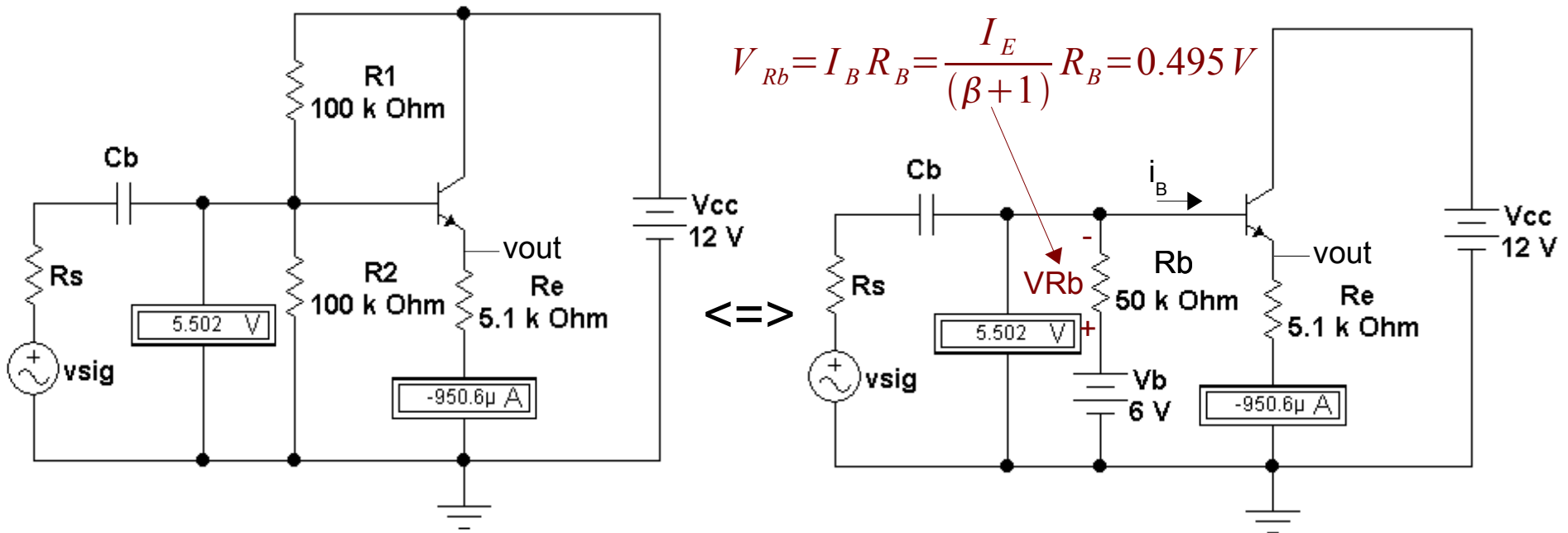


Identical results – as expected!

Emitter Follower Small Signal Circuit

Mid-band equivalent circuit:

$$v_s' = \frac{R_B}{R_B + R_S} v_s = \frac{50}{50.05} v_s \approx v_s$$
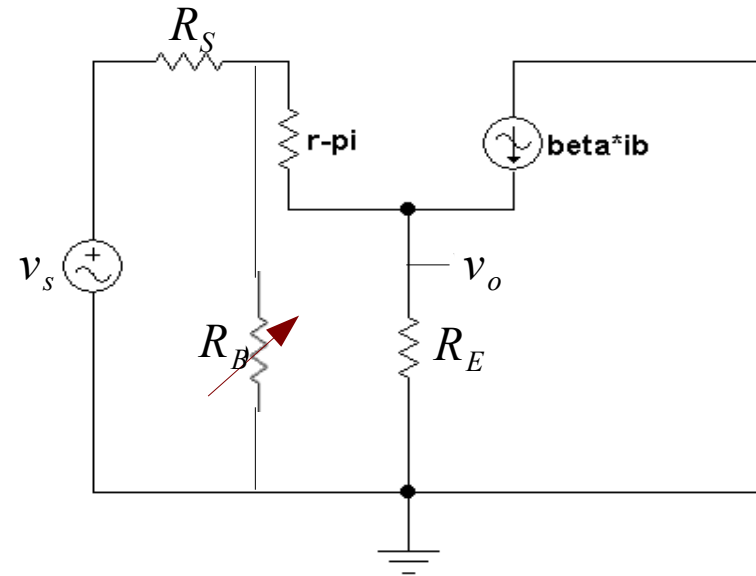
$$R_{TH} = R_S \parallel R_B = \frac{50}{50.05} R_S \approx R_S$$



Small signal mid-band circuit - where C_B has negligible reactance (above f_{min}). Thevenin circuit consisting of R_S and R_B shows effect of R_B negligible, since it is much larger than R_S .

Follower Small Signal Analysis - Voltage Gain

Circuit analysis:



$$v_s = (R_S + r_\pi + (\beta + 1)R_E) i_b$$

Solving for i_b

$$i_b = \frac{v_s}{R_S + r_\pi + (\beta + 1)R_E}$$

$$v_o = R_E i_e = R_E (1 + \beta) i_b$$

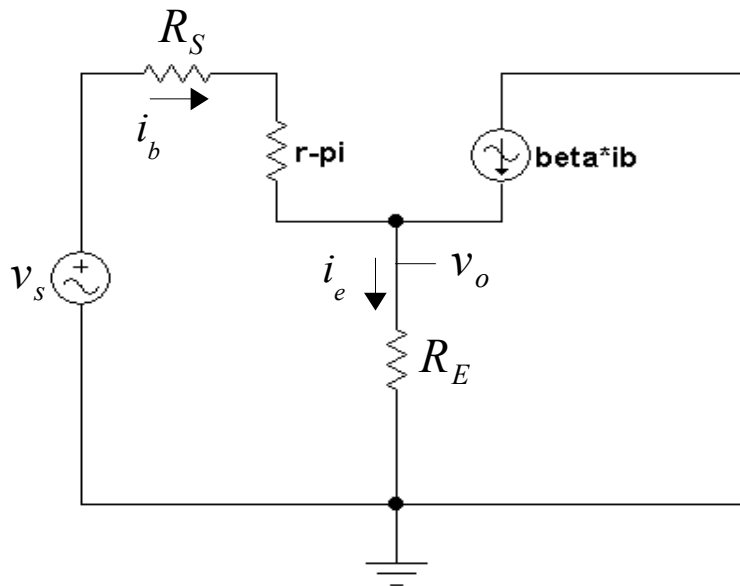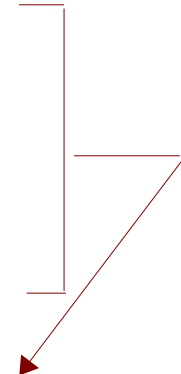
$$v_o = \frac{R_E (\beta + 1) v_s}{R_S + r_\pi + (\beta + 1)R_E}$$



for Current Bias Design
replace R_E with $r_o \parallel r_o = r_o/2 \gg R_E$

$$A_V = \frac{v_o}{v_s} = \frac{R_E \cancel{r_o} \parallel r_o}{\frac{R_S + r_\pi}{(\beta + 1)} + R_E \cancel{r_o} \parallel r_o} \approx 1$$

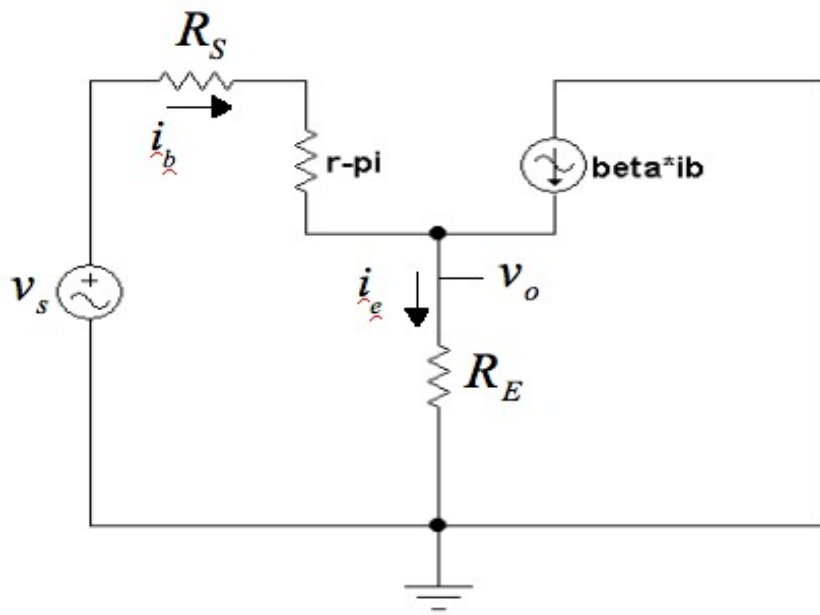Small Signal Analysis – Voltage Gain - cont.



$$\frac{v_o}{v_s} = \frac{R_E}{\frac{R_S + r_{\pi}}{(\beta + 1)} + R_E}$$


Since, typically:

$$\frac{R_S + r_{\pi}}{(\beta + 1)} \ll R_E \quad (\text{or } r_o || r_o = r_o/2)$$

$$A_V = \frac{v_o}{v_s} \approx \frac{R_E}{R_E} = 1$$

Note: A_V is non-inverting

Blocking Capacitor - C_B - Selection

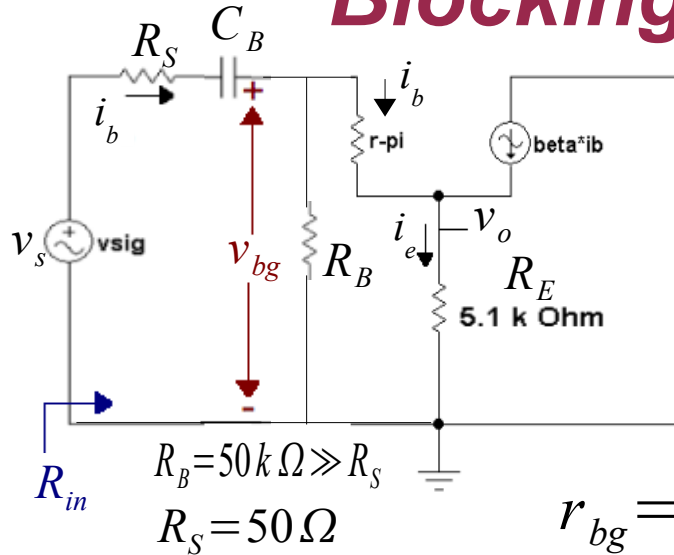

Use the base current expression:

$$v_{bg} = r_{\pi} i_b + R_E i_E = (r_{\pi} + (\beta + 1)) i_b$$

$$i_b = \frac{v_{bg}}{r_{\pi} + (\beta + 1) R_E}$$

$$r_{bg} = \frac{v_{bg}}{i_b} = r_{\pi} + (\beta + 1) R_E \approx (\beta + 1) R_E = 101 \cdot 5.1\text{ k} = 515\text{ k}\ \Omega$$

To obtain the base to ground resistance of the transistor:

This transistor input resistance is in parallel with the $50\text{ k}\ \Omega$ R_B , forming the total amplifier input resistance:

$$R_{in} = R_S + R_B \parallel r_{bg} \approx R_B \parallel r_{bg} = \frac{515}{(515 + 50)} 50\text{ k}\ \Omega = 45.6\text{ k}\ \Omega \approx R_B = 50\text{ k}\ \Omega$$

C_B – Selection cont.

Choose C_B such that its reactance is $\leq 1/10$ of R_{in} at f_{min} :

$$\frac{1}{2\pi f C_B} = \frac{R_{in}}{10}$$

$$C_B \geq \frac{10}{2\pi f_{min} R_{in}}$$


Assume $f_{min} = 20 \text{ Hz}$

with $R_{in} \approx 50 \text{ k}\Omega$


$$C_B \geq \frac{10}{2\pi \cdot 20 \cdot 50 \cdot 10^3} \approx 1.59 \mu\text{F}$$

Pick $C_B = 2 \mu\text{F}$ (two $1 \mu\text{F}$ caps in parallel), the nearest standard value in the RCA Lab. We could be (unnecessarily) more precise and include R_s as part of the total resistance in the loop. It is very small compared to R_{in} .


Final Design

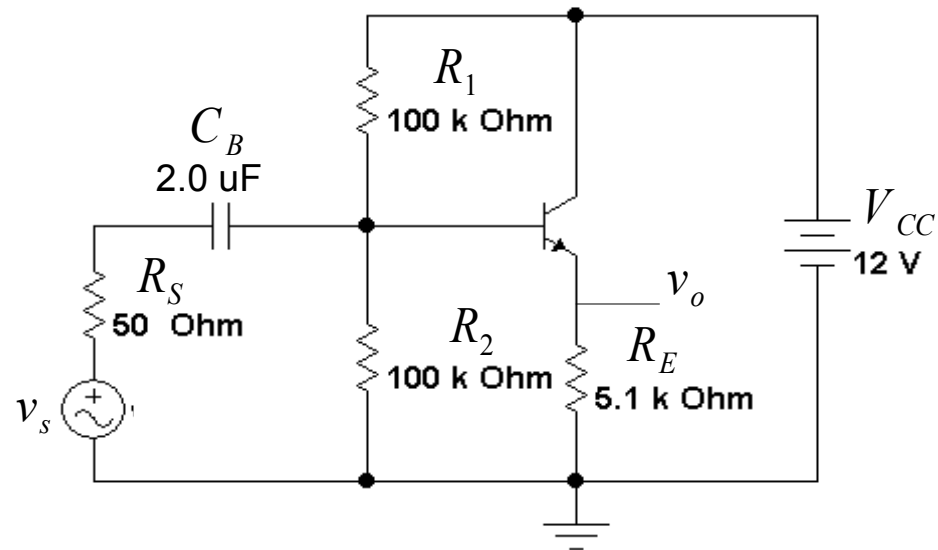

Multisim Simulation Results

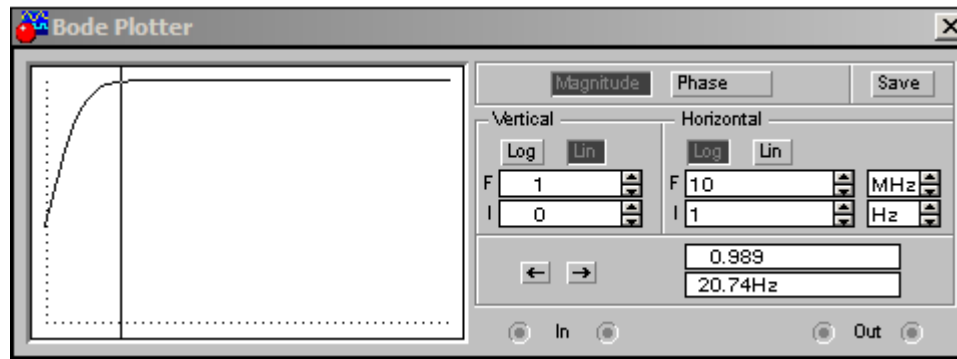


20 Hz Data

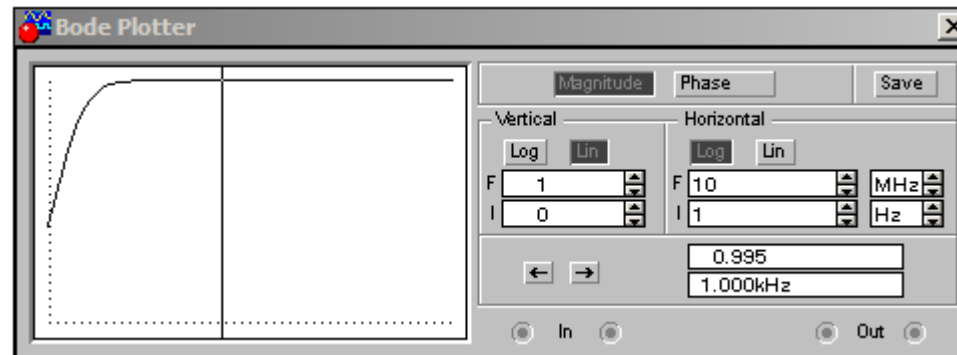


1 kHz Data

Of What value is a Unity Gain Amplifier?

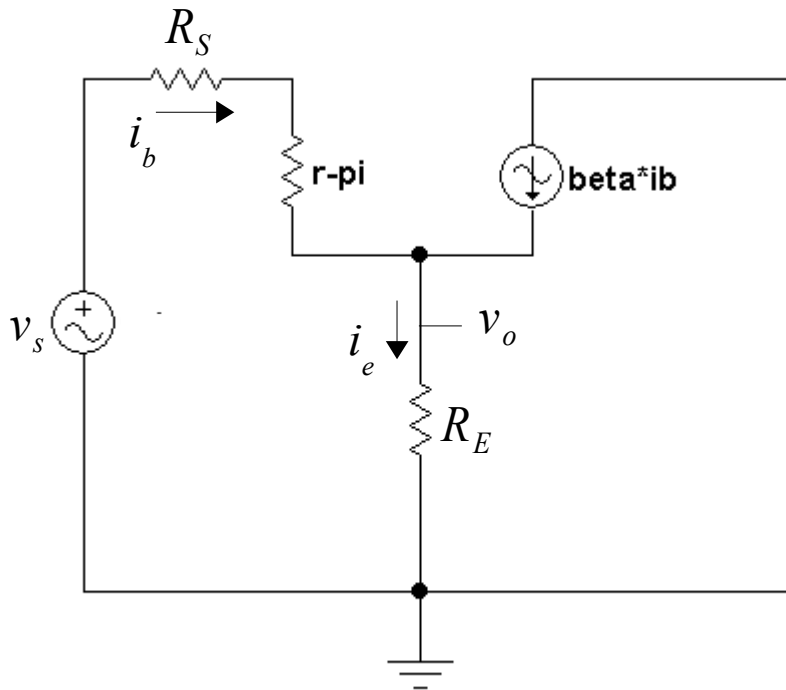

To answer this question, we must examine the small-signal *output impedance* of the amplifier and its *power gain*.

Emitter Follower Output Resistance

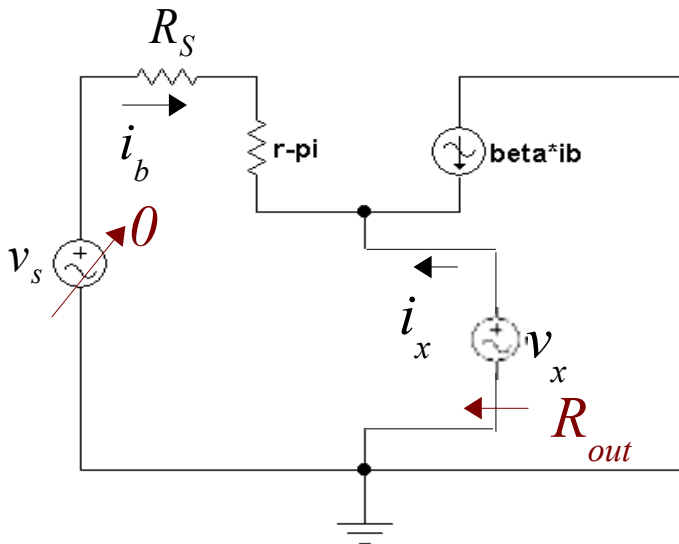

$$R_B = 50\text{ k}\Omega \gg R_S$$

$$i_x = -i_b - \beta i_b = -(1 + \beta) i_b \Rightarrow i_b = \frac{-i_x}{(1 + \beta)}$$

$$v_x = -i_b (R_S + r_\pi) = \frac{R_S + r_\pi}{1 + \beta} i_x$$

$$R_{out} = \frac{v_x}{i_x} = \frac{R_S + r_\pi}{1 + \beta} \approx \frac{r_\pi}{1 + \beta} = r_e$$

R_{out} is the Thevenin resistance looking into the open-circuit output.


Assume:

$$I_C = 1\text{ mA} \Rightarrow r_\pi = \frac{V_T}{I_B} = \beta \frac{V_T}{I_C} = 2500\ \Omega$$

$$\beta = 100 \quad R_S = 50\ \Omega$$

$$R_{out} \approx \frac{2550}{100} = 25.5\ \Omega$$


Multisim Verification of R_{out}

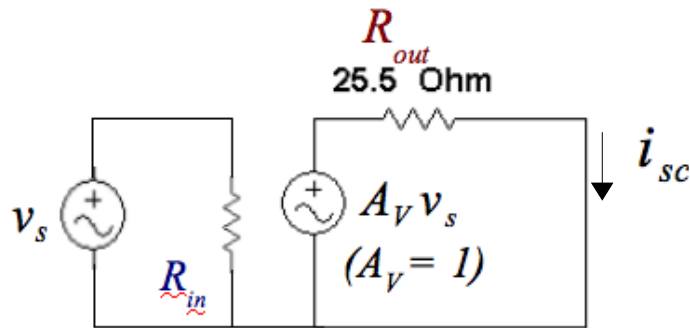

$$R_{in} = R_S + r_{\pi} + (\beta + 1)R_E \approx (\beta + 1)R_E$$

Thevenin equivalent for the short-circuited emitter follower.

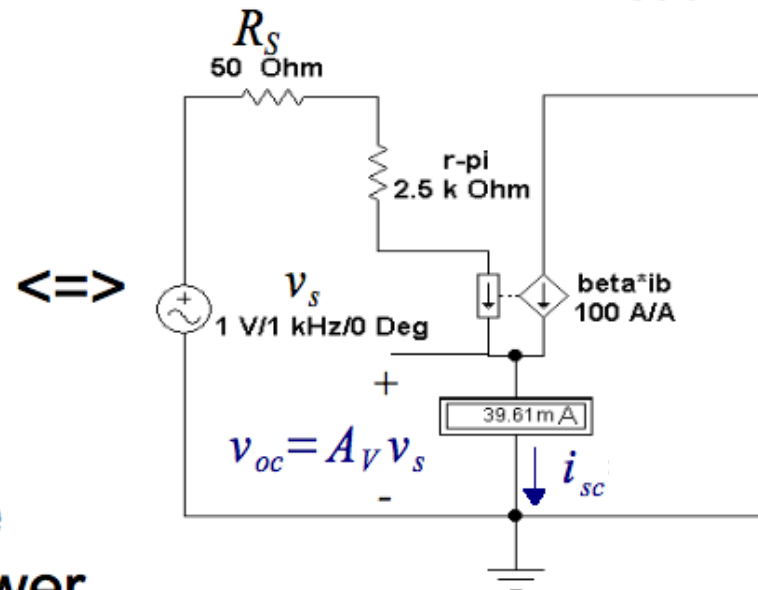If $\beta = 200$, as for most good NPN transistors, R_{out} would be lower - close to 12Ω .



$$R_{out} = \frac{v_{oc}}{i_{sc}}$$

$$i_{sc} = (1 + \beta)i_b$$

$$v_{sig} = R_S i_b + r_{\pi} i_b$$

$$R_{out} = \frac{A_V v_{sig}}{i_{sc}} = \frac{R_S + r_{\pi}}{1 + \beta}$$



$$\beta = 100$$

Multisim short circuit check

($\beta = 100, v_o = v_s$):

$$R_{out} = \frac{v_{oc}}{i_{sc}} = \frac{A_V v_{s(rms)}}{i_{sc(rms)}} = \frac{1}{0.0396} = 25.25 \Omega$$

Equivalent Circuits with Load R_L

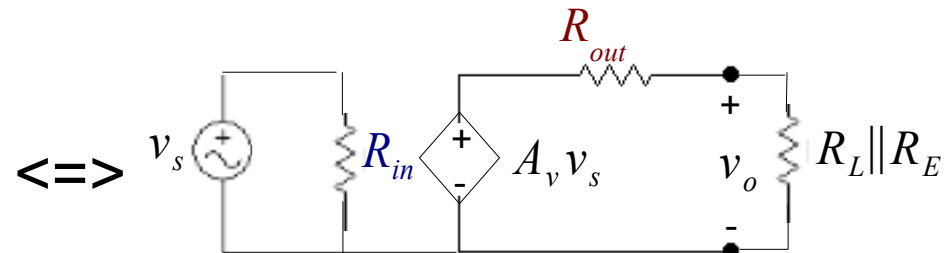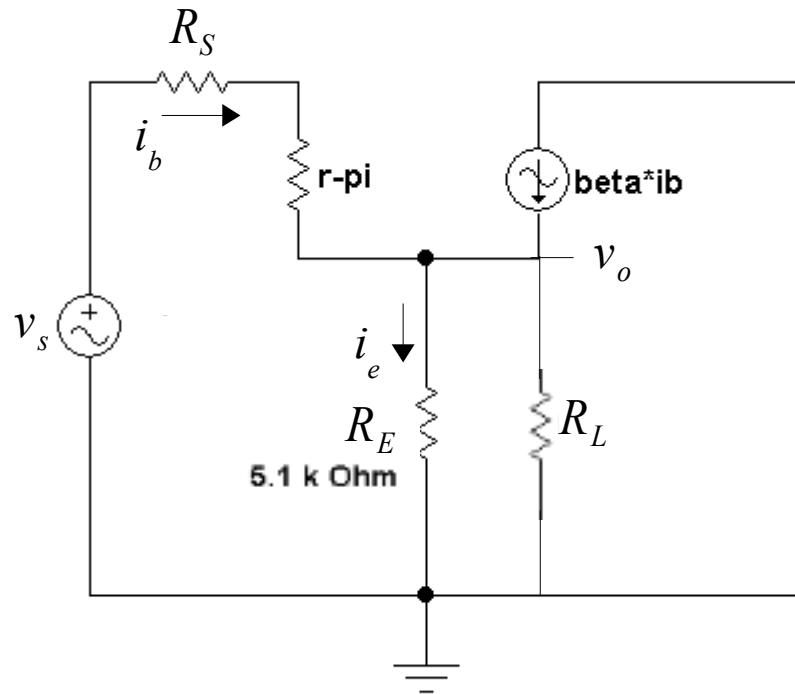


$$R_{out} = \frac{v_{s(rms)}}{i_{sc(rms)}} = \frac{1}{0.0396} = 25.25 \Omega$$

$$R_{in} = R_S + r_{\pi} + (\beta + 1) R_E \parallel R_L \approx (\beta + 1) R_L$$

Emitter Follower Power Gain

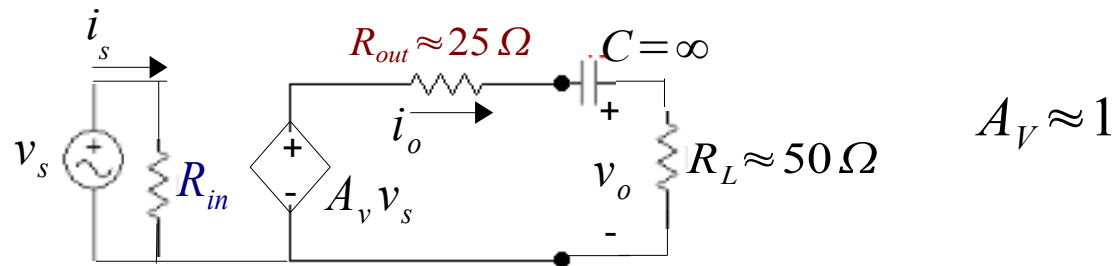Consider the case where a $R_L = 50\Omega$ load is connected through an infinite capacitor to the emitter of the follower we designed. Using its Thevenin equivalent:



$$v_o = \frac{R_L A_V v_s}{R_L + R_{out}} = \frac{50}{75} v_s = \frac{2}{3} v_s$$

$$i_o = \frac{A_V v_s}{R_{out} + R_L} = \frac{v_s}{75}$$

$$p_o = v_o i_o = \frac{2}{225} v_s^2$$


$$R_E \parallel R_L = 5.1 k\Omega \parallel 50\Omega \approx 50\Omega$$

$$i_s = i_b = \frac{v_s}{R_{in}} \approx \frac{v_s}{(\beta + 1) R_E \parallel R_L} \approx \frac{v_s}{101 \cdot 50} \approx \frac{v_s}{5000}$$


$$p_s = v_s i_s \approx \frac{1}{5000} v_s^2$$

$$A_{pwr} = \frac{p_o}{p_s} = \frac{2(5000)}{225} = 44.4 \gg 1$$

The Common Base Amplifier

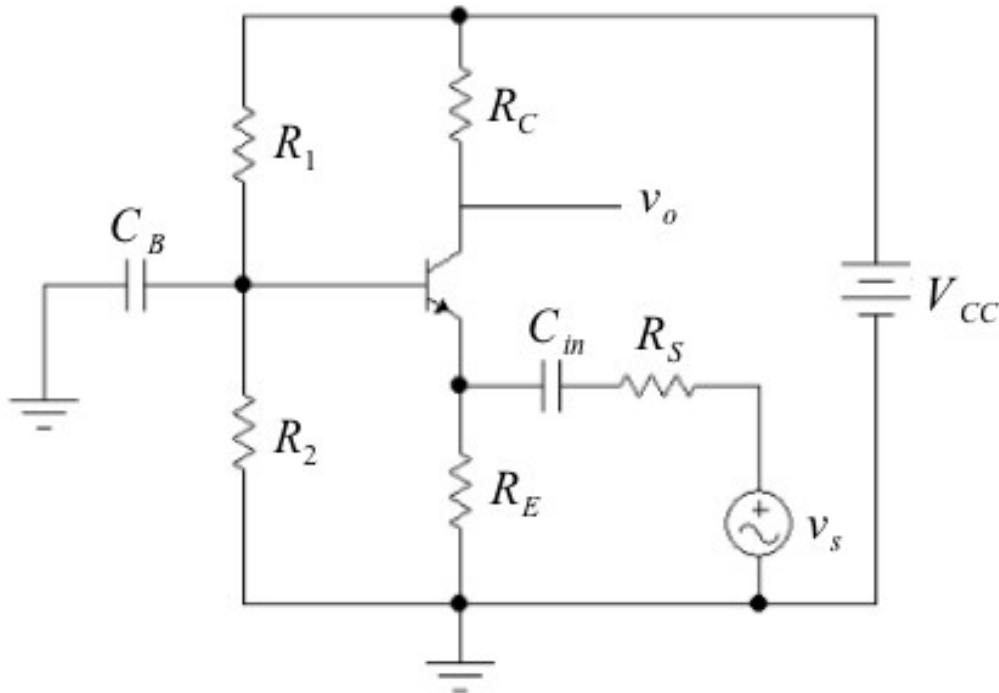

Voltage Bias Design

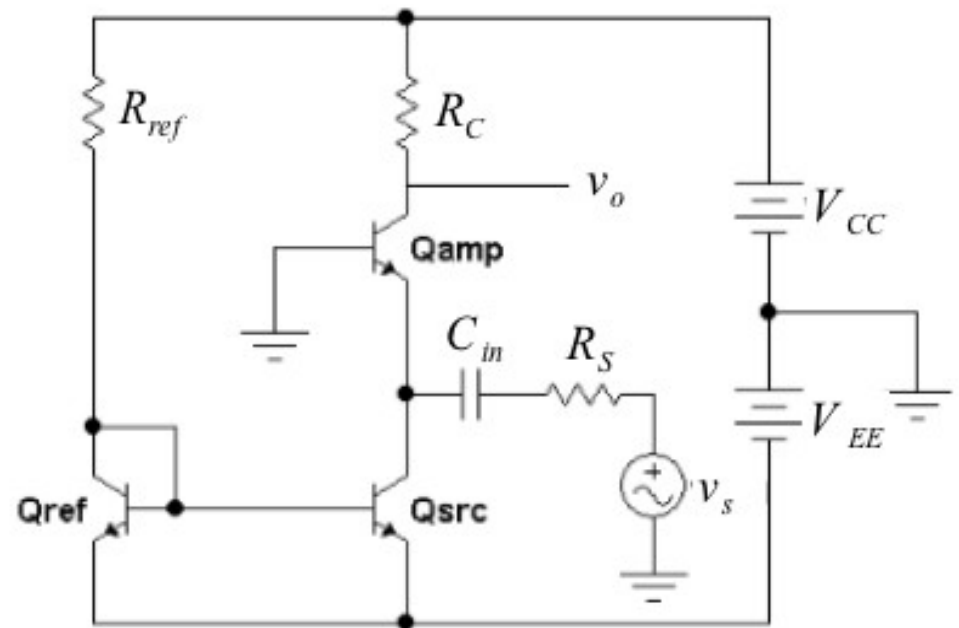

Current Bias Design

Common Base Configuration


Both voltage and current biasing follow the same rules as those applied to the common emitter amplifier.

As before, insert a blocking capacitor in the input signal path to avoid disturbing the dc bias.

The common base amplifier uses a bypass capacitor – or a direct connection from base to ground to hold the base at ground *for the signal only!*


The common emitter amplifier (except for intentional R_E feedback) holds the emitter at signal ground, while the common collector circuit does the same for the collector.

Voltage Bias Common Base Design

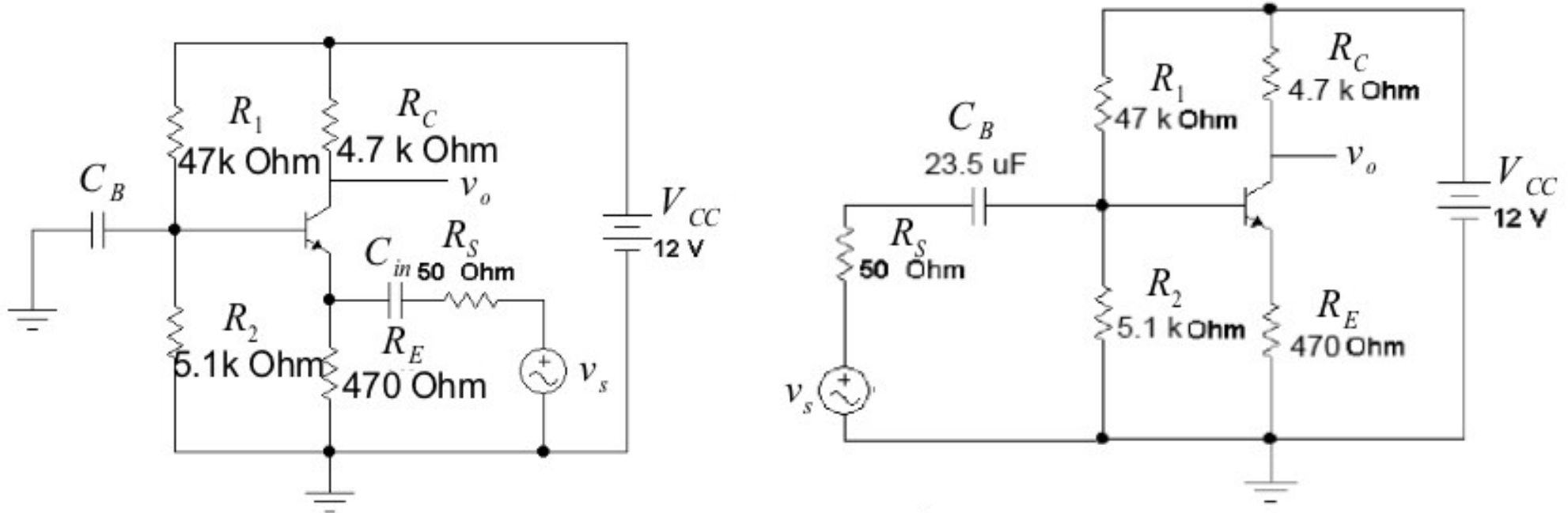

- ◆ We keep the same bias that we established for the gain of 10 common emitter amplifier.
- ◆ All that we need to do is pick the capacitor values and calculate the circuit gain.

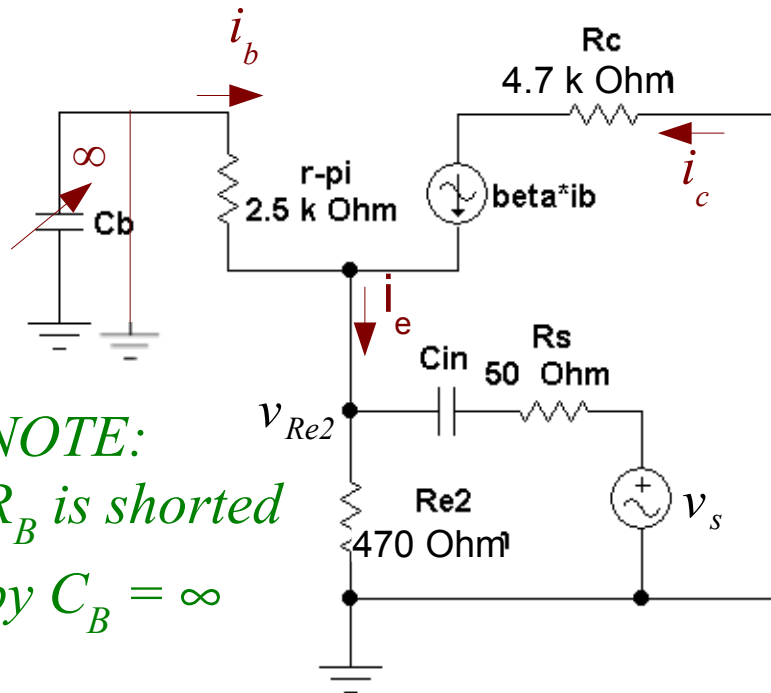Common Base Small Signal Analysis - C_{IN}



NOTE:
 R_B is shorted
by $C_B = \infty$

Determine C_{IN} : (let $C_B = \infty$)

Find an equivalent impedance for the input circuit, R_S , C_{in} , and R_{E2} :

$$v_{Re2} = \frac{R_{E2} \parallel r_e}{R_{E2} \parallel r_e + R_S + \frac{1}{j2\pi f C_{in}}} v_s$$

$r_e = \frac{r_\pi}{1 + \beta}$

ideally $v_{Re2} = \frac{R_{E2} \parallel r_e}{R_{E2} \parallel r_e + R_S} v_s$ for $f \geq f_{min}$

$$\frac{1}{2\pi f_{min} C_{in}} \ll R_S + R_{E2} \parallel r_e \Rightarrow \frac{1}{2\pi f_{min} C_{in}} = \frac{R_S + r_e}{10} \Rightarrow C_{in} = \frac{10}{2\pi f_{min} (R_S + r_e)}$$

Determine C_{IN} cont.

A suitable value for C_{in} for a 20 Hz lower frequency:

$$2\pi f_{min} C_{in} (R_S + r_e) \gg 1 \Rightarrow C_{in} \geq \frac{10}{2\pi f_{min} (R_S + r_e)} = \frac{10}{2\pi \cdot 20 \cdot 75} F$$

$$C_{in} = \frac{10}{125.6 \cdot 75} \approx 1062 \mu F !$$

Not too Practical!


Must choose smaller value of C_{in} .

1. Choose: $2\pi f_{min} C_{in} (R_S + r_e) = 1$

or

2. Choose larger f_{min}

Small-signal Analysis - C_B

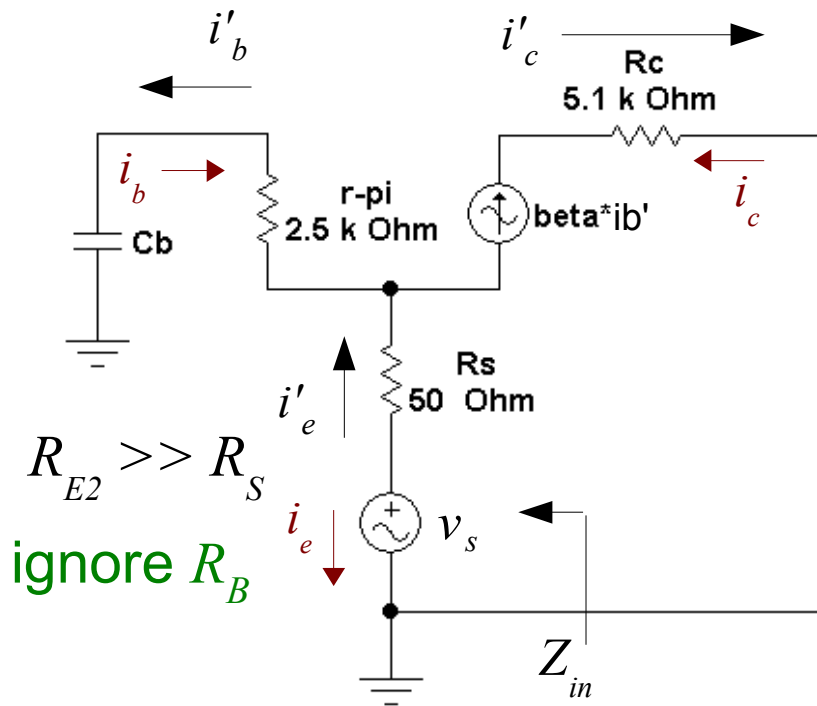

Determine $Z_{in} = \frac{v_s}{i_e'}$

Determine C_B : (let $C_{in} = \infty$)


Note the ac reference current reversals (due to v_s polarity)!

$$v_s = R_S i_e' + \left(r_\pi + \frac{1}{j\omega C_B} \right) i_b'$$

$$v_s = R_S i_e' + \left(r_\pi + \frac{1}{j\omega C_B} \right) \frac{i_e'}{\beta + 1}$$

$$i_e' = \frac{\beta + 1}{(\beta + 1) R_S + r_\pi + \frac{1}{j\omega C_B}} v_s$$

Determine – C_B

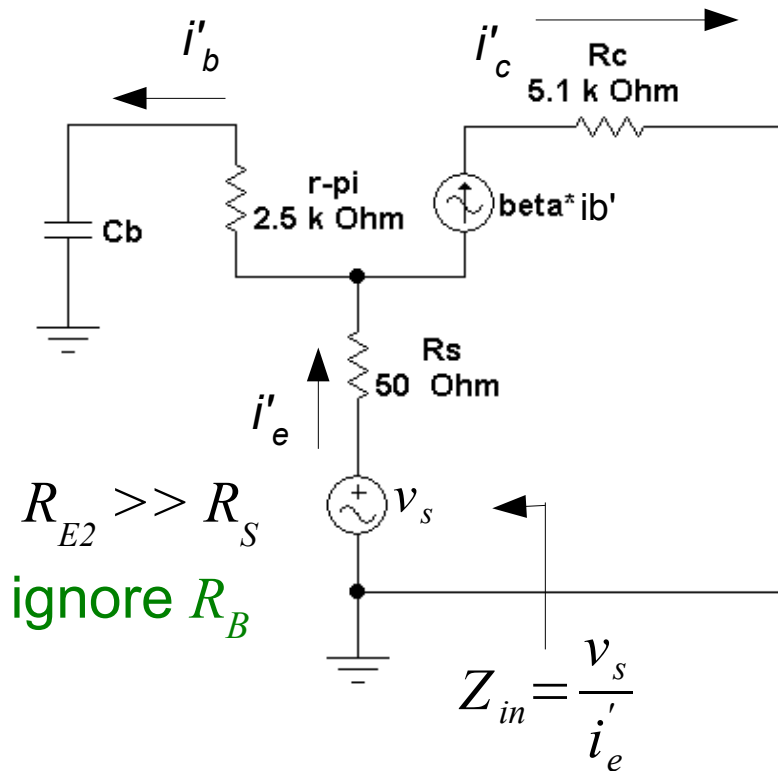

$$i'_e = \frac{\beta + 1}{(\beta + 1)R_S + r_\pi + \frac{1}{j2\pi f C_B}} v_s$$


ideally $Z_{in} \approx \frac{(\beta + 1)R_S + r_\pi}{\beta + 1} = R_S + \frac{r_e}{\beta + 1} \quad f \geq f_{min}$

or $\frac{1}{2\pi f C_B} \ll (\beta + 1)R_S + r_\pi \quad f \geq f_{min}$

Choose (conservatively):

$$C_B \geq \frac{10}{2\pi f_{min} ((\beta + 1)R_S + r_\pi)} F$$

Determine - C_B cont.

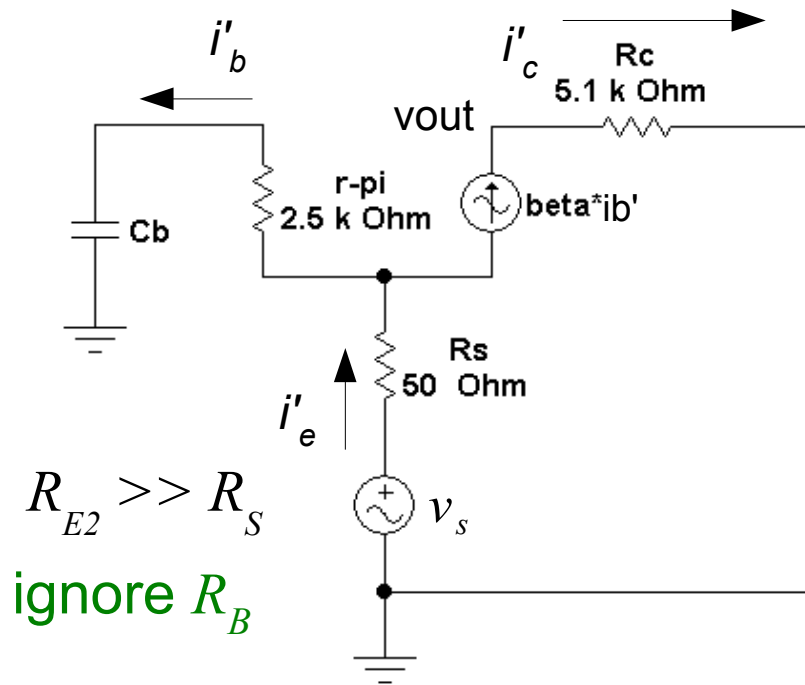

Choosing (conservatively):

$$C_B \geq \frac{10}{2\pi f_{min} ((\beta + 1) R_S + r_{\pi})} F$$


for $f_{min} = 20 \text{ Hz}$

i.e.
$$C_B \geq \frac{10}{2\pi 20 ((100) 50 + 2500)} = 10.6 \mu F$$

Choose (less conservatively):

$$C_B \geq \frac{1}{2\pi 20 ((100) 50 + 2500)} = 1.06 \mu F$$

Small-signal Analysis – Voltage Gain

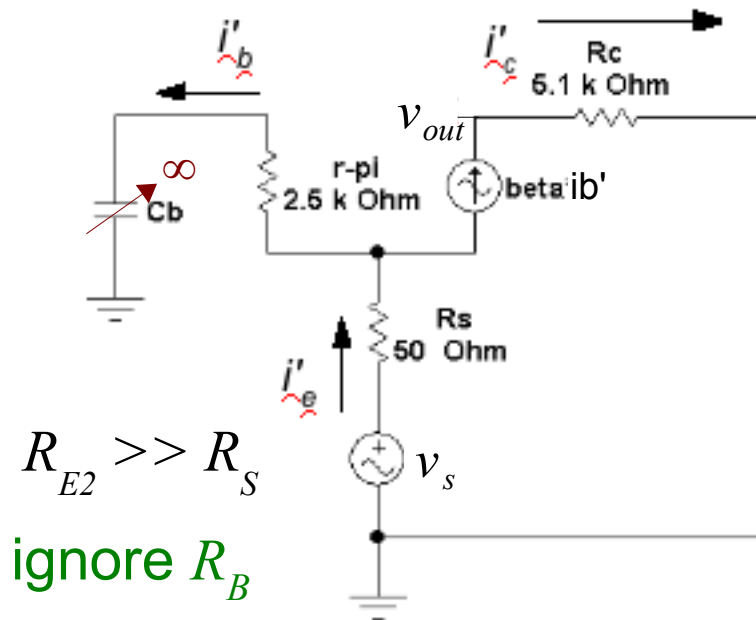


Assume: $C_B = C_{in} = \infty$

$$i'_e \approx \frac{1}{R_S + \frac{r_\pi}{\beta + 1}} v_s = \frac{1}{(R_S + r_e)} v_s$$


$$v_{out} = R_C i'_c = \alpha R_C i'_e = \frac{\beta}{\beta + 1} \frac{R_C}{R_S + r_e} v_s$$

$$A_V = \frac{v_{out}}{v_s} = \frac{\beta}{\beta + 1} \frac{R_C}{R_S + r_e} = \frac{100}{101} \frac{5100}{50 + 25} \approx 67$$


Multisim Simulation

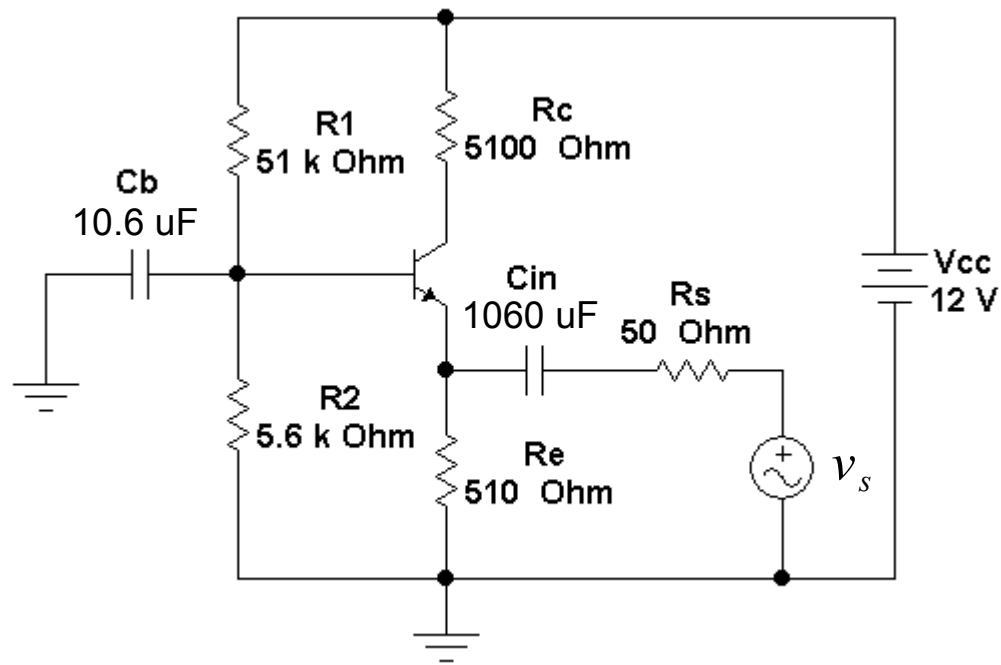

Multisim Frequency Response

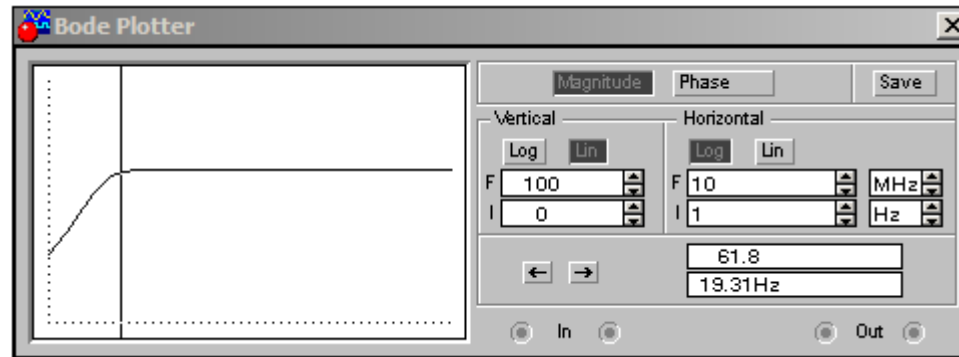

20 Hz response

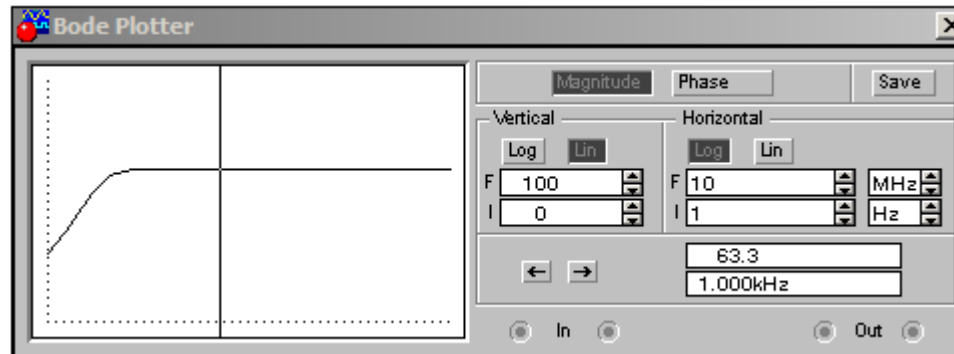

1 kHz Response