

ESE 3400: Medical Devices Lab

Lec 12: October 24, 2022
Data Converters Pt 2




Lecture Outline

- ❑ SQNR
- ❑ Oversampling
- ❑ Nyquist ADCs
- ❑ Flash ADCs
- ❑ SAR ADCs

Ideal B-bit Quantizer

- ❑ Practical quantizers have a limited input range and a finite set of output codes
- ❑ E.g. a 3-bit quantizer can map onto $2^3=8$ distinct output codes
- ❑ Quantization error grows out of bounds beyond code boundaries
- ❑ We define the full scale range (FSR) as the maximum input range that satisfies $|e_q| \leq \Delta/2$
 - Implies that $FSR = 2^B \cdot \Delta$

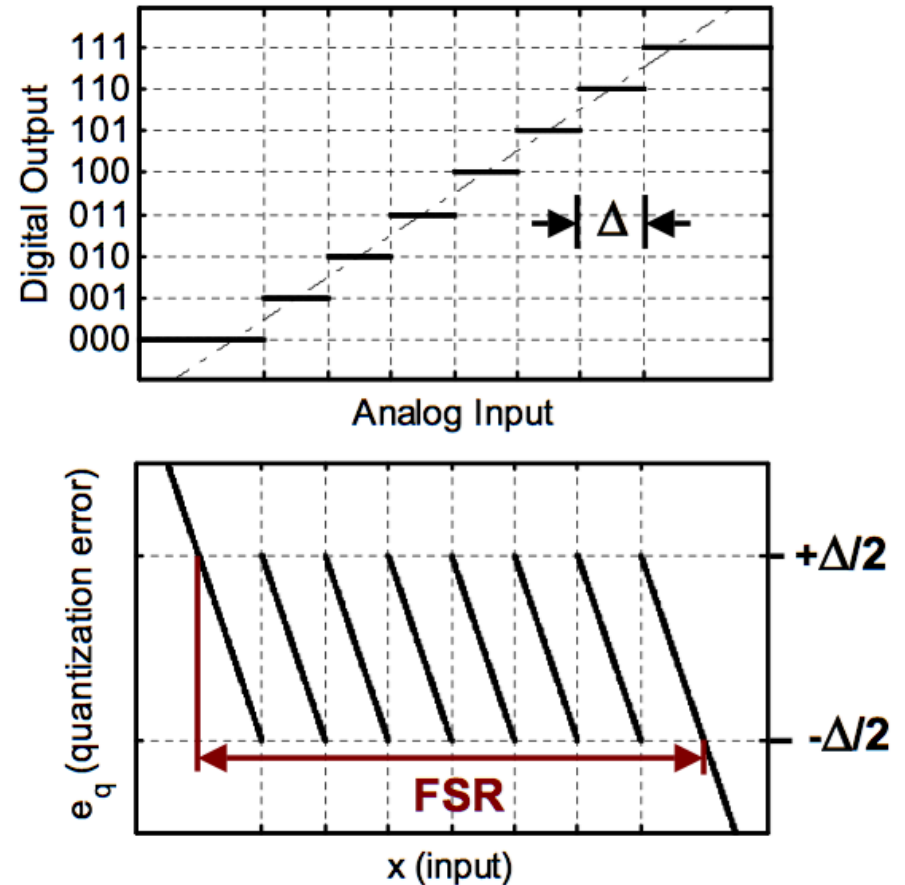




Effect of Quantization Error on Signal

- ❑ Quantization error is a deterministic function of the signal
 - Consequently, the effect of quantization strongly depends on the signal itself
- ❑ Unless, we consider fairly trivial signals, a deterministic analysis is usually impractical
 - More common to look at errors from a statistical perspective
 - "Quantization noise"

Quantization Error Statistics

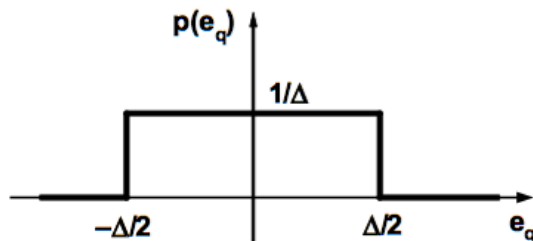- ❑ Crude assumption: $e_q(x)$ has uniform probability density
- ❑ This approximation holds reasonably well in practice when
 - Signal spans large number of quantization steps
 - Signal is "sufficiently active"
 - Quantizer does not overload



Mean

$$\bar{e} = \int_{-\Delta/2}^{+\Delta/2} \frac{e}{\Delta} de = 0$$


Variance

$$\overline{e^2} = \int_{-\Delta/2}^{+\Delta/2} \frac{e^2}{\Delta} de = \frac{\Delta^2}{12}$$



Quantization Noise

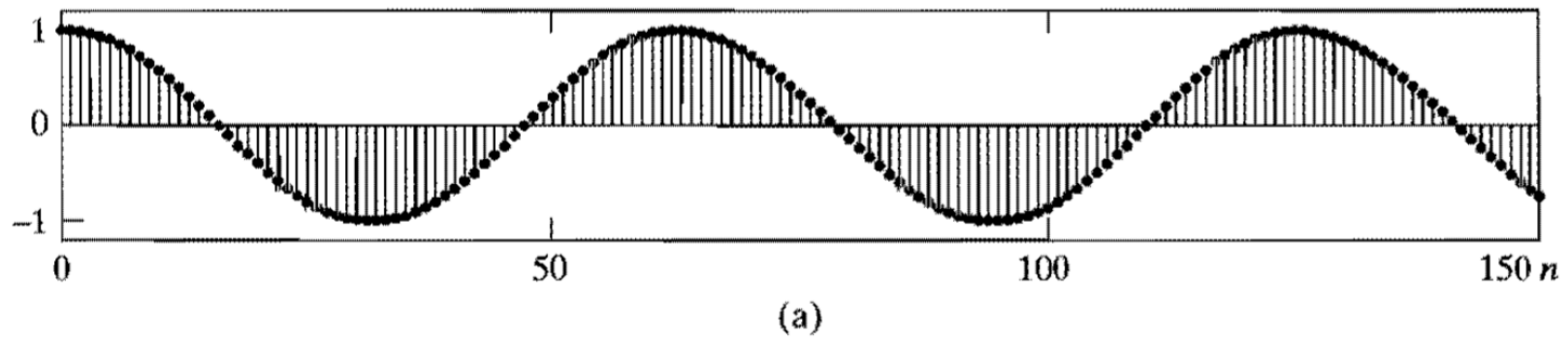
- **Figure 4.57** Example of quantization noise. (a) Unquantized samples of the signal $x[n] = 0.99\cos(n/10)$.





Quantization Noise

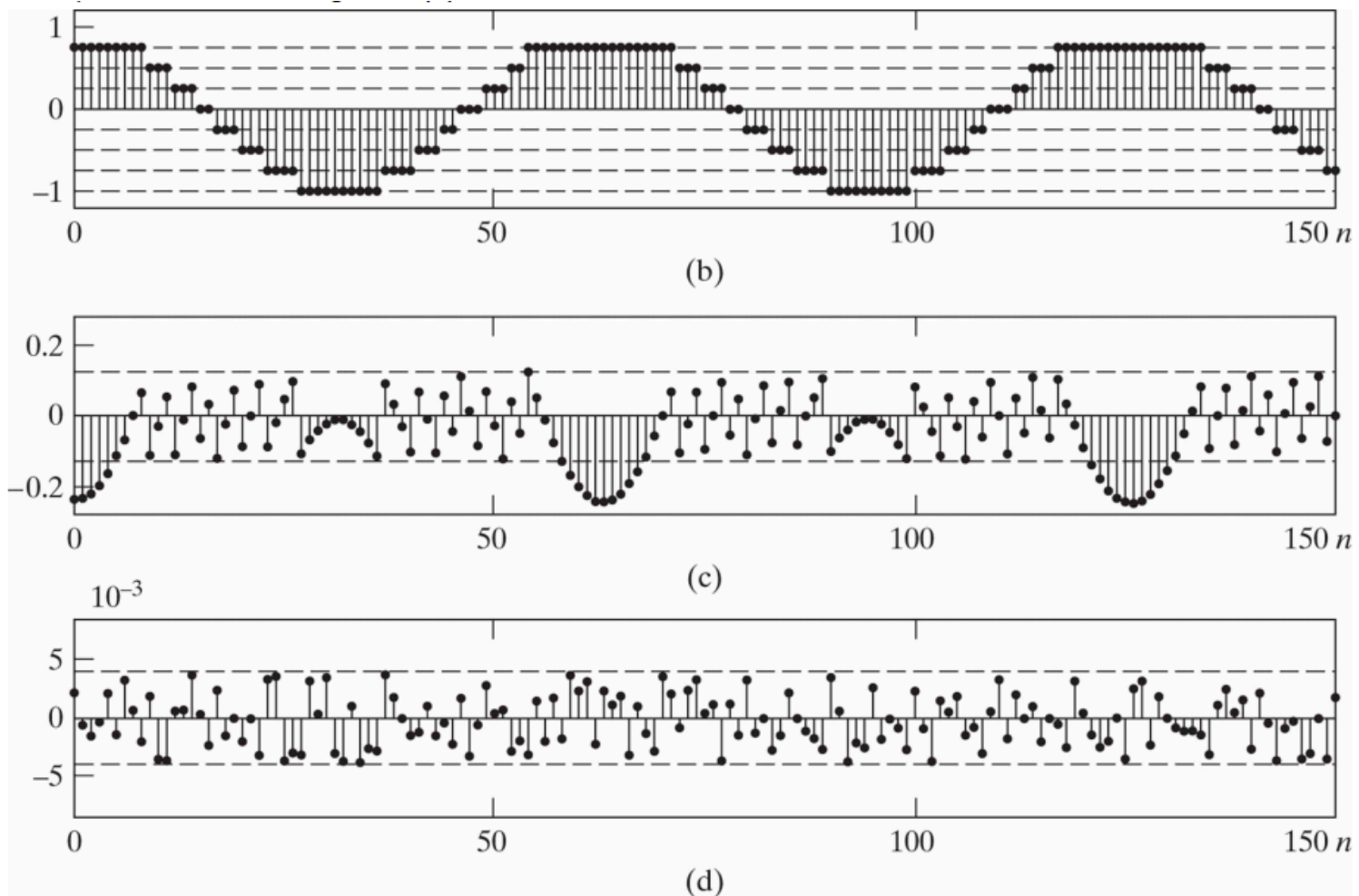- Figure 4.57(continued) (b) Quantized samples of the cosine waveform in part (a) with a 3-bit quantizer. (c) Quantization error sequence for 3-bit quantization of the signal in (a). (d) Quantization error sequence for 8-bit quantization of the signal in (a).





Signal-to-Quantization-Noise Ratio

- Assuming full-scale sinusoidal input, we have

$$\text{SNR}_Q = 6.02B + 1.76 \text{ dB}$$

B (Number of Bits)	SQNR
8	50dB
12	74dB
16	98dB
20	122dB



Signal-to-Quantization-Noise Ratio

- For uniform B bits quantizer

$$SNR_Q = 10 \log_{10} \left(\frac{\sigma_x^2}{\sigma_e^2} \right)$$

Signal-to-Quantization-Noise Ratio

- For uniform B bits quantizer

$$\begin{aligned} SNR_Q &= 10 \log_{10} \left(\frac{\sigma_x^2}{\sigma_e^2} \right) \\ &= 10 \log_{10} \left(\frac{12 \cdot 2^{2B} \sigma_x^2}{FSR^2} \right) \end{aligned}$$

$$SNR_Q = 6.02B + 10.8 - 20 \log_{10} \left(\frac{FSR}{\sigma_x} \right) \begin{matrix} \text{Quantizer range} \\ \text{rms of amp} \end{matrix}$$



Signal-to-Quantization-Noise Ratio

$$\text{SNR}_Q = 6.02B + 10.8 - 20 \log_{10} \left(\frac{\text{Quantizer range}}{\sigma_x \text{ rms of amp}} \right)$$

- ❑ Improvement of 6dB with every bit
- ❑ The range of the quantization must be adapted to the rms amplitude of the signal
 - Tradeoff between clipping and noise!
 - Often use pre-amp
 - Sometimes use analog auto gain controller (AGC)



Signal-to-Quantization-Noise Ratio

- Assuming full-scale sinusoidal input, we have

$$\text{SNR}_Q = 6.02B + 10.8 - 20 \log_{10} \left(\frac{\text{Quantizer range}}{\sigma_x \text{ rms of amp}} \right)$$



Signal-to-Quantization-Noise Ratio


- Assuming full-scale sinusoidal input, we have

$$\text{SNR}_Q = 6.02B + 1.76 \text{ dB}$$

B (Number of Bits)	SQNR
8	50dB
12	74dB
16	98dB
20	122dB

Quantization Noise Spectrum

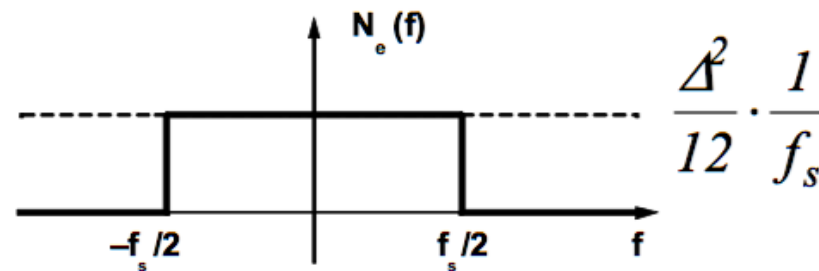
- If the quantization error is "sufficiently random", it also follows that the noise power is uniformly distributed in frequency



- References


- W. R. Bennett, "Spectra of quantized signals," Bell Syst. Tech. J., pp. 446-72, July 1988.
- B. Widrow, "A study of rough amplitude quantization by means of Nyquist sampling theory," IRE Trans. Circuit Theory, vol. CT-3, pp. 266-76, 1956.

Non-Ideal Anti-Aliasing Filter


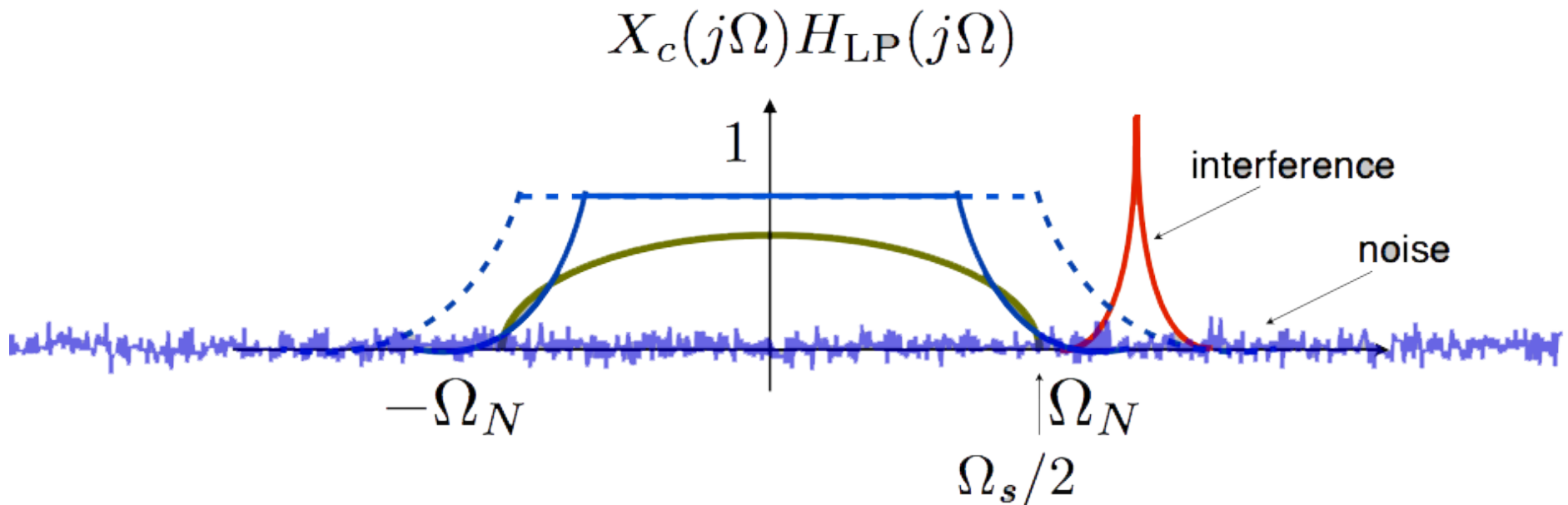


- ❑ Problem: Hard to implement sharp analog filter
- ❑ Consequence: Crop part of the signal and suffer from noise and interference

Oversampled ADC

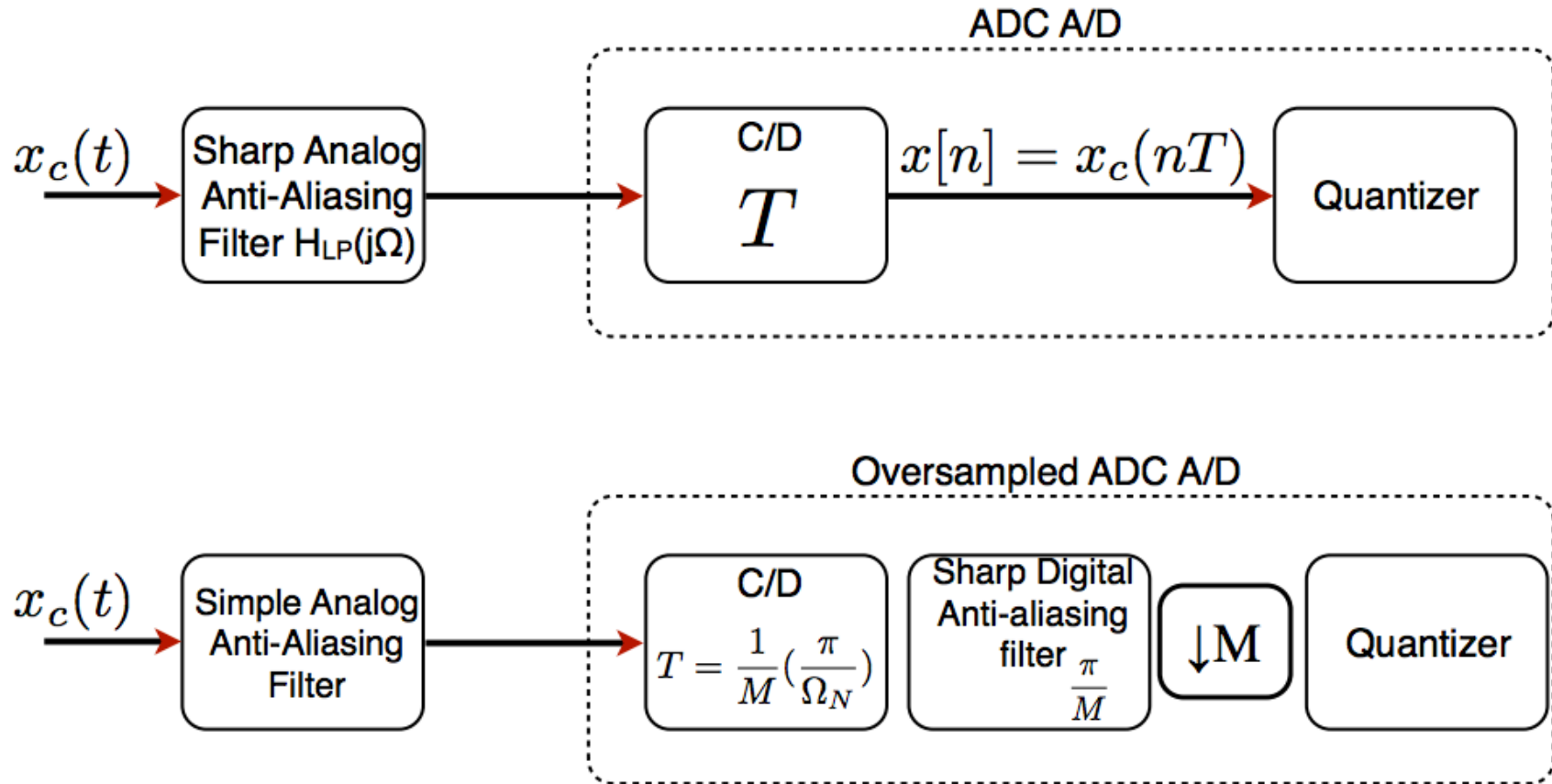

Quantization Noise with Oversampling

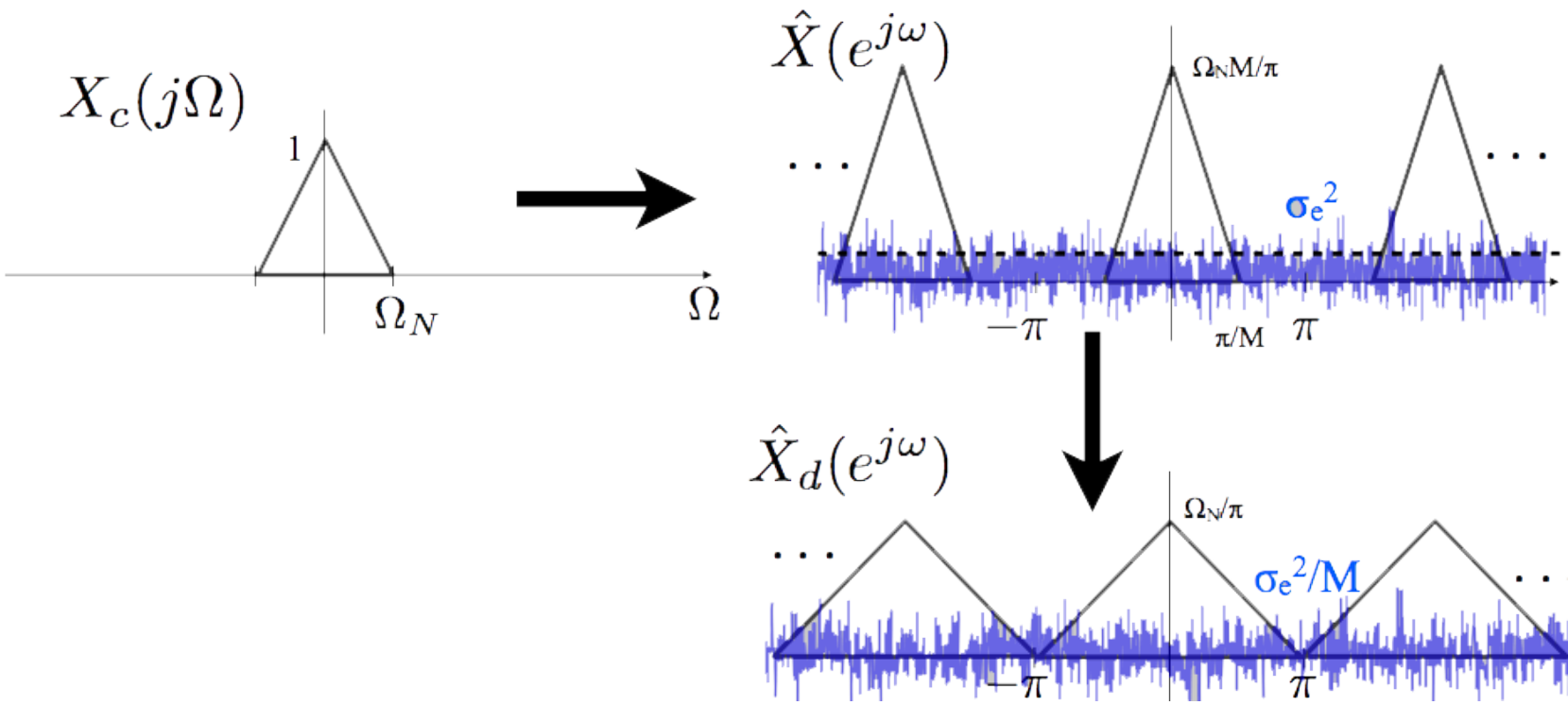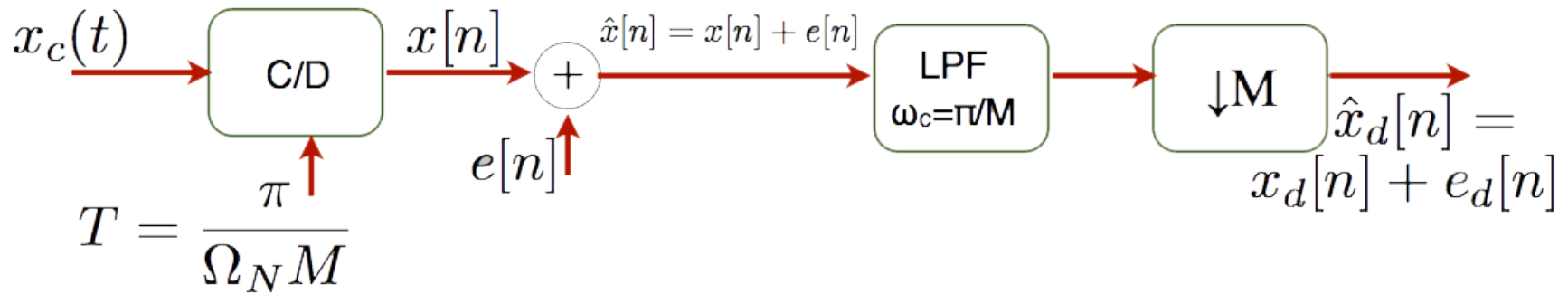


ADC Architectures



Nyquist ADC Architectures

 
- ❑ Word-at-a-time
 - E.g. flash ADC
 - Instantaneous comparison with 2^B-1 reference levels
- ❑ Multi-step
 - E.g. pipeline ADCs
 - Coarse conversion, followed by fine conversion of residuals
- ❑ Bit-at-a-time
 - E.g. successive approximation ADCs
 - Conversion via a binary search algorithm



speed

ADC Survey (ISSCC & VLSI 1997-2013)

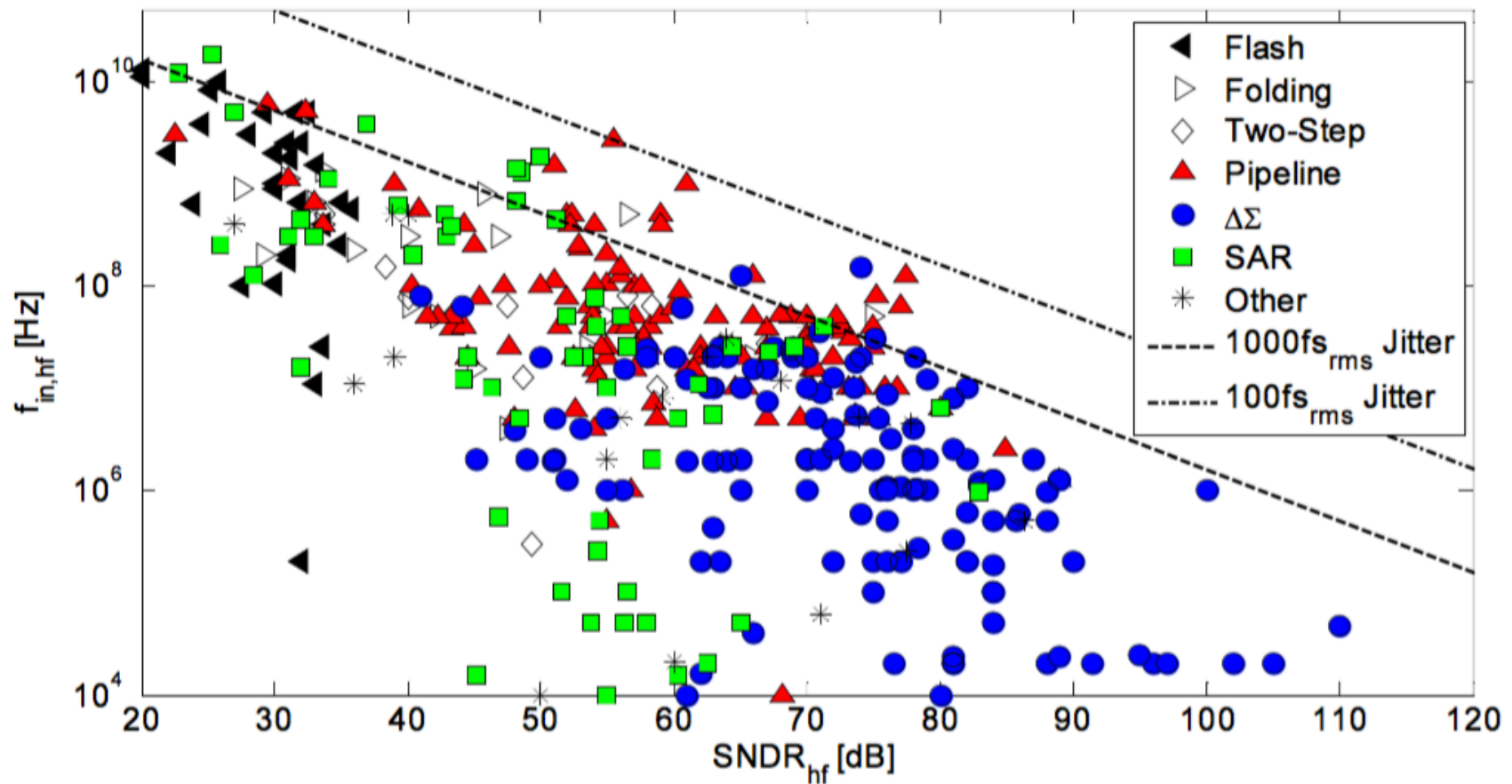Data: <http://www.stanford.edu/~murmman/adcsurvey.html>




Flash ADCs



Flash ADC

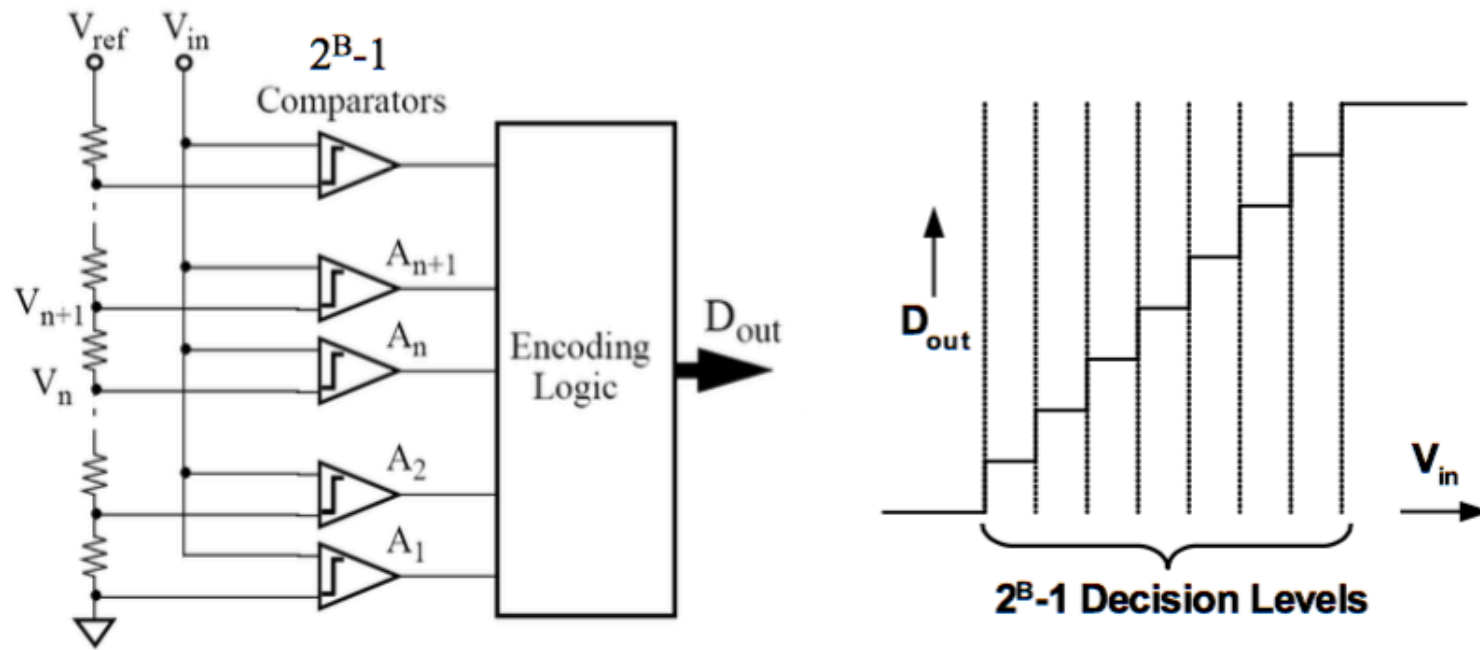
- ❑ Fast
 - Speed limited by single comparator plus encoding logic
- ❑ High circuit complexity (2^B-1 comparators), high input capacitance
 - Typically only use for resolution up to 6...8 bits




Flash ADC

□ B-bit flash ADC:


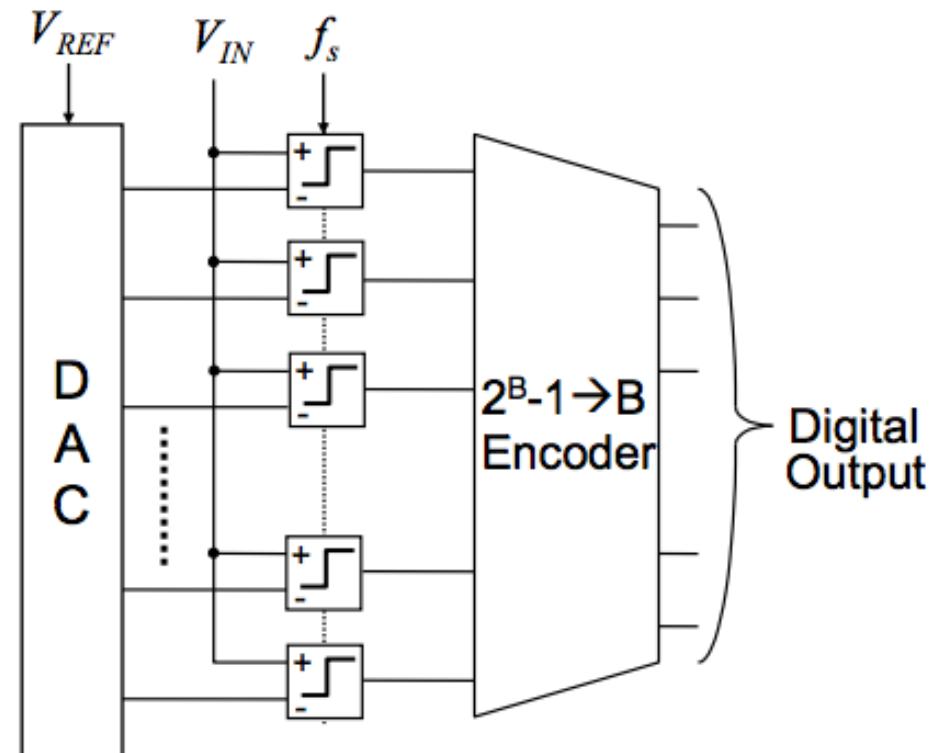
- DAC generates all possible 2^B-1 levels
- 2^B-1 comparators compare V_{IN} to DAC outputs
- Comparator output:
 - If $V_{DAC} < V_{IN} \rightarrow 1$
 - If $V_{DAC} > V_{IN} \rightarrow 0$
- Comparator outputs form thermometer code
- Encoder converts thermometer to binary code




Multi-channel Bio-potential Recording

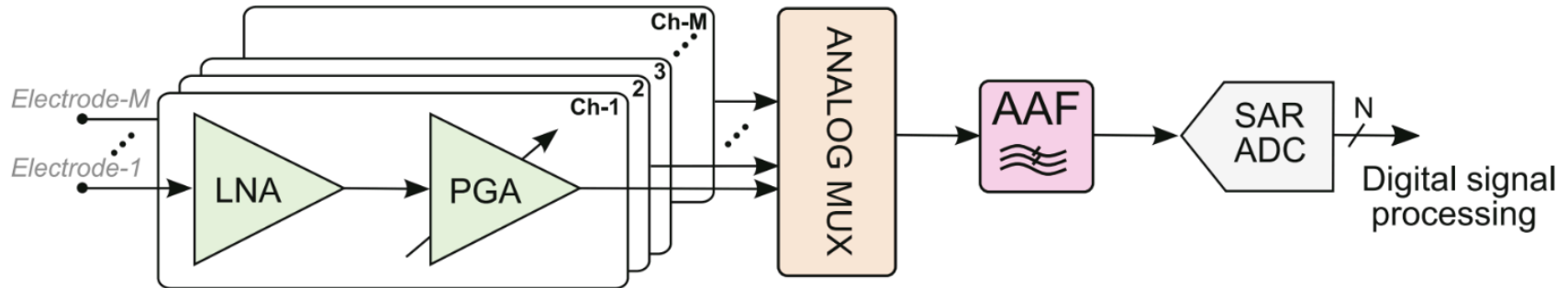

Multi-channel Bio-potential Recording

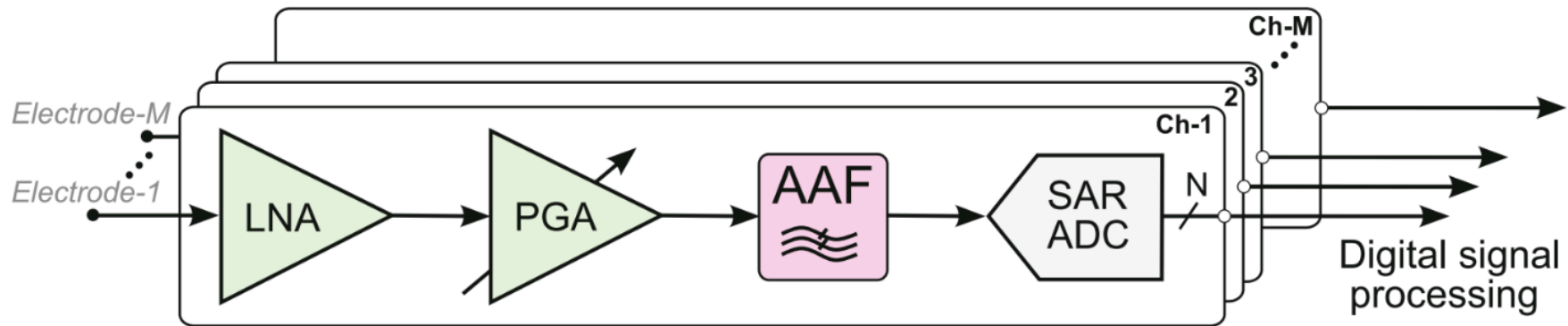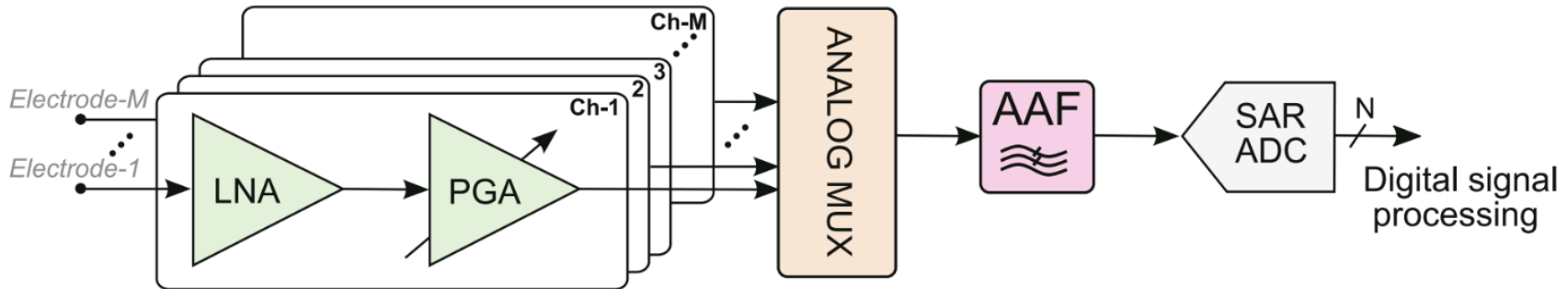


SAR ADC Architectures

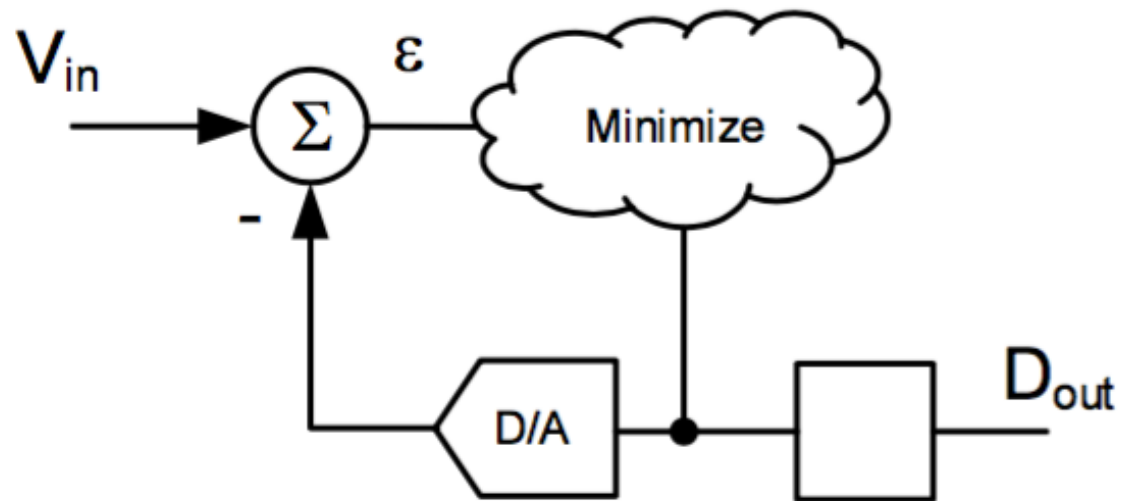


- ❑ Most ADC architectures (other than flash) are based on minimizing (reducing) the error between input and a D/A signal approximation
 - Pipeline uses distributed DAC
 - SAR ADC uses comparator to sense error
 - Sigma-delta ADC minimizes error via integration and feedback

SAR ADC

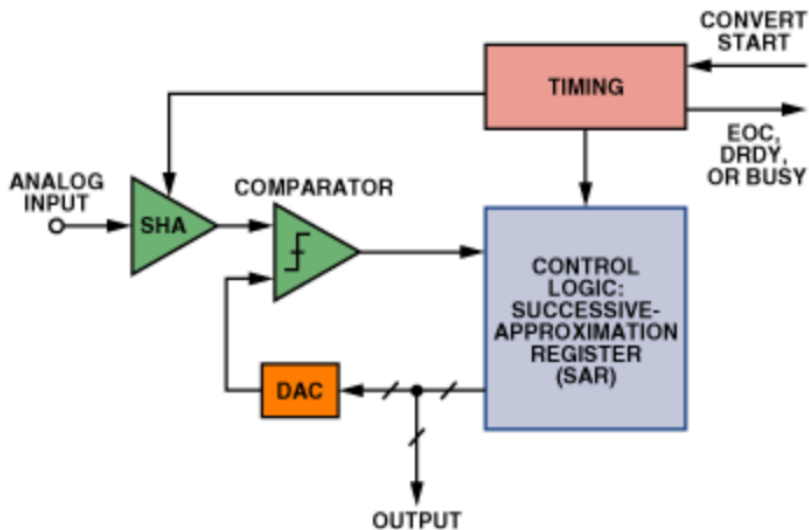



- ❑ Key features:
- ❑ High resolution
- ❑ Fast response and low latency
- ❑ Power varies with sample rate

Pulse Oximetry Example

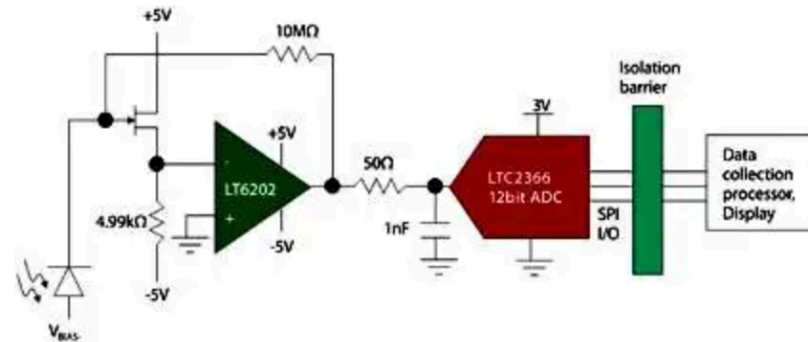


- ❑ LTC2366 is part of a family of tiny ADCs sampling from 100KSps to 3MSps
- ❑ ADCs dissipate only 7.8mW at 3MSps, 1.5mW at 100KSps and 0.3 microwatts in sleep mode
- ❑ LTC2366 features no data latency through the ADC

Successive Approximation Algorithm

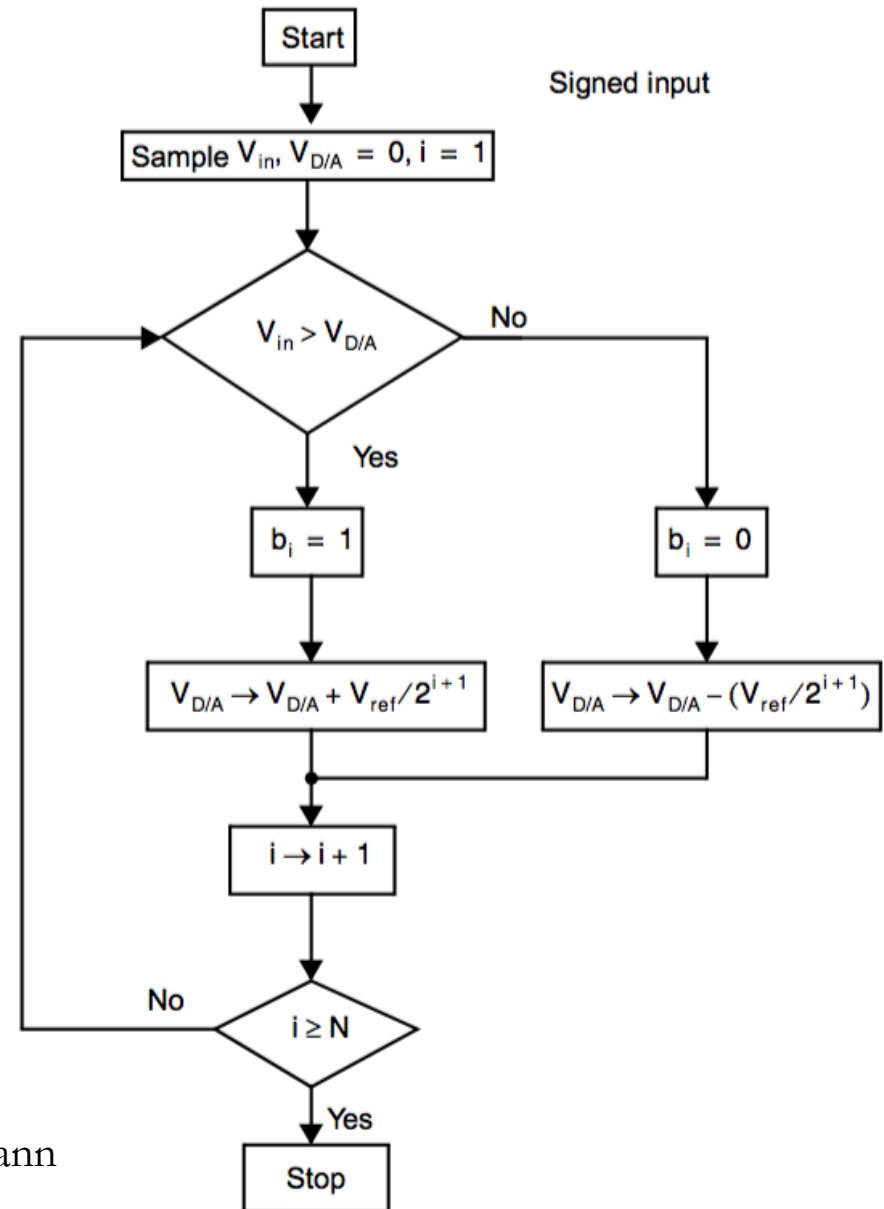
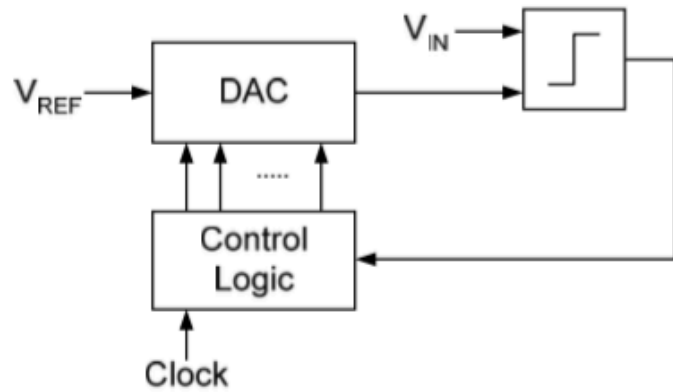


Successive Approximation Register ADC

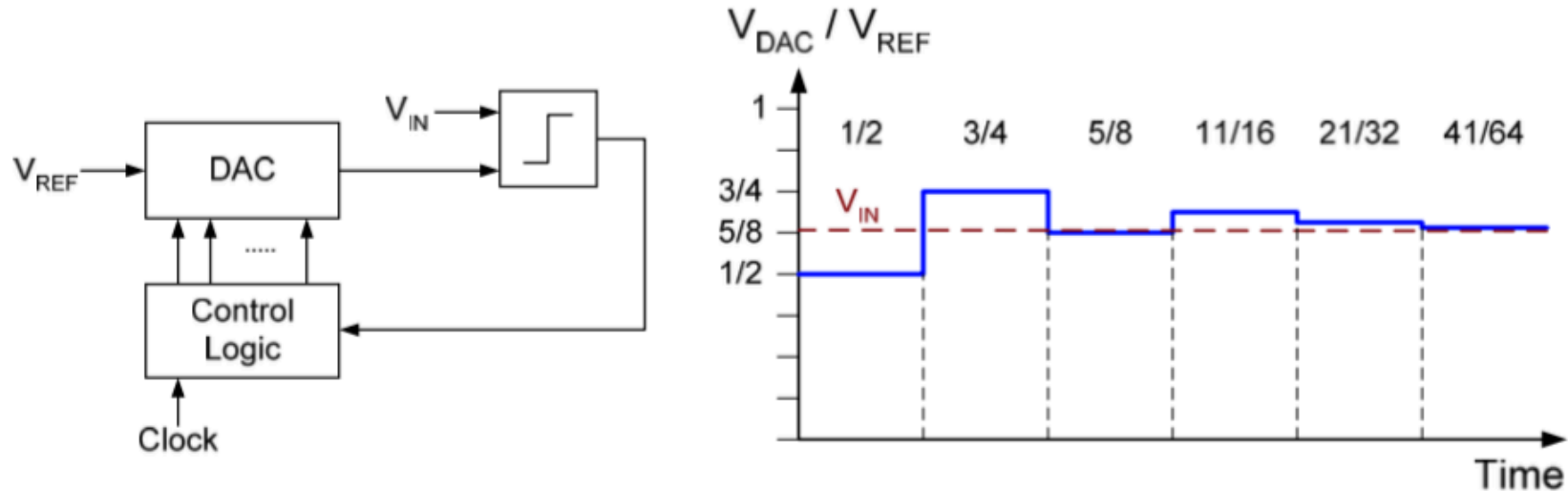



- ❑ Binary search over DAC output
- ❑ High accuracy achievable (16+ bits)
 - Relies on highly accurate comparator
- ❑ Moderate speed (1+ Mhz)

SAR ADC Block Diagram

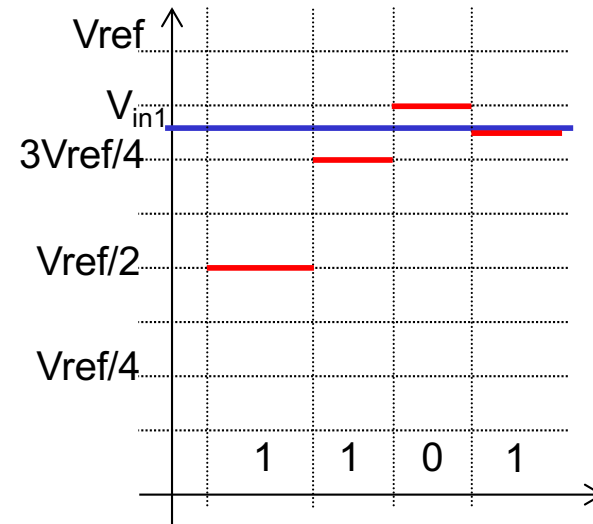
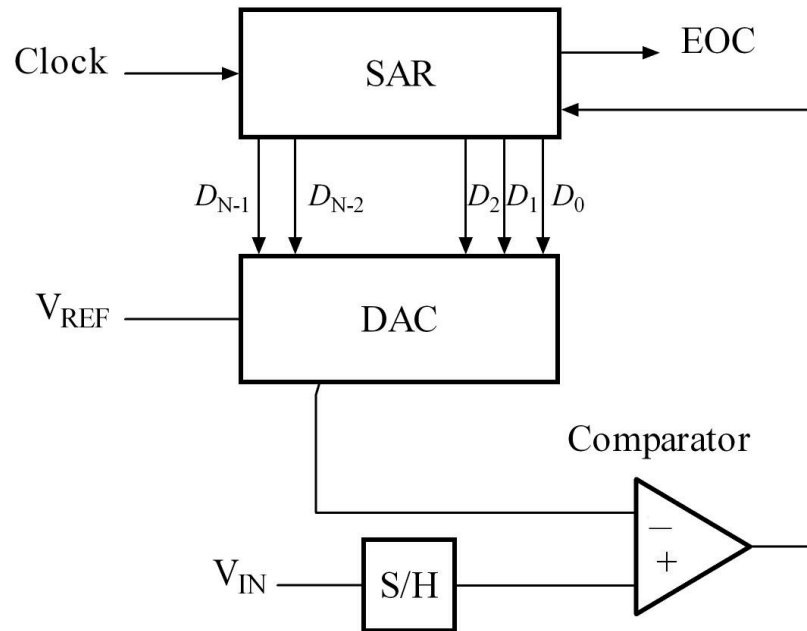


- ❑ Sampling phase: Sample input with Sample-and-Hold
- ❑ Bit-cycling: Compare with DAC output, adjusting the SAR with each clock cycle as bits are determined

Charge Redistribution ADC

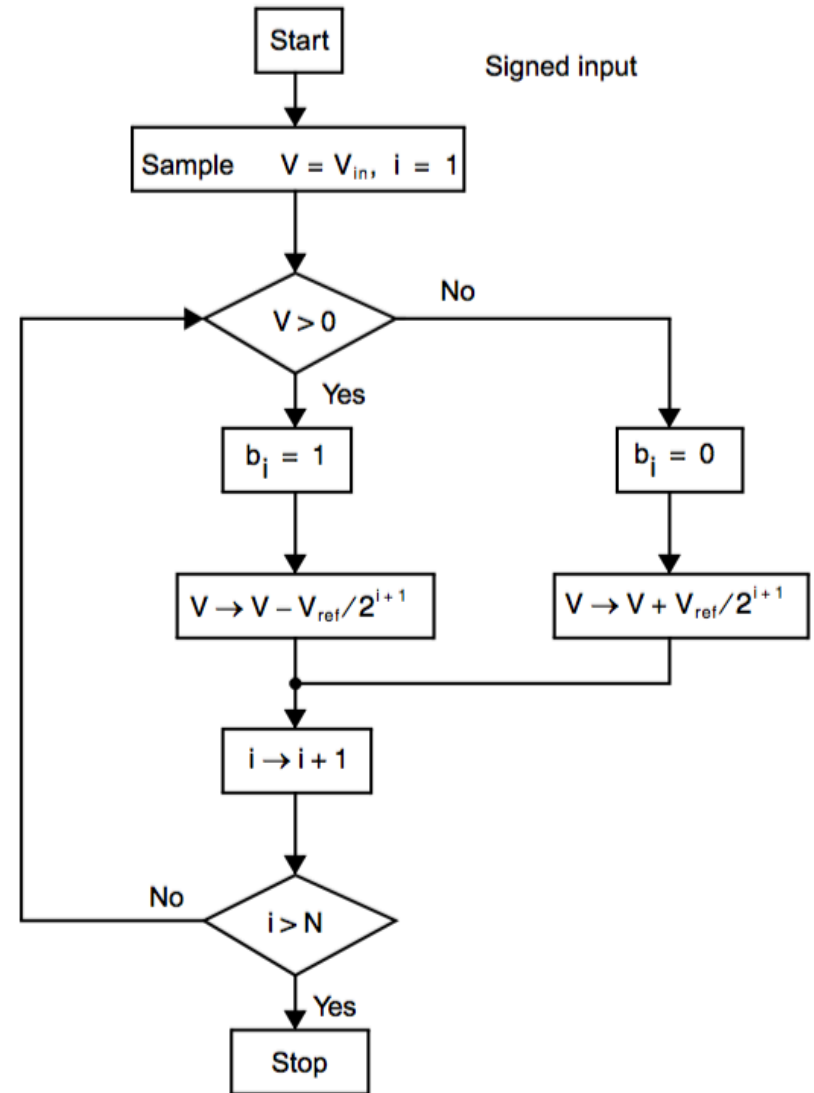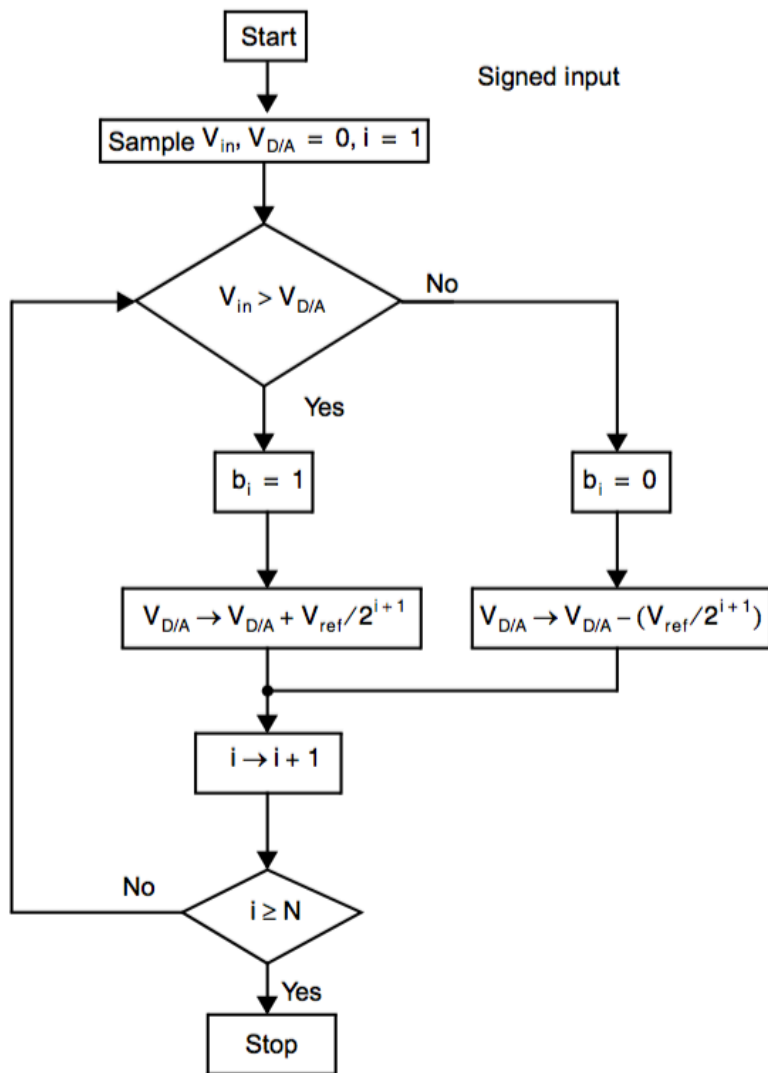

Multi-channel Bio-potential Recording

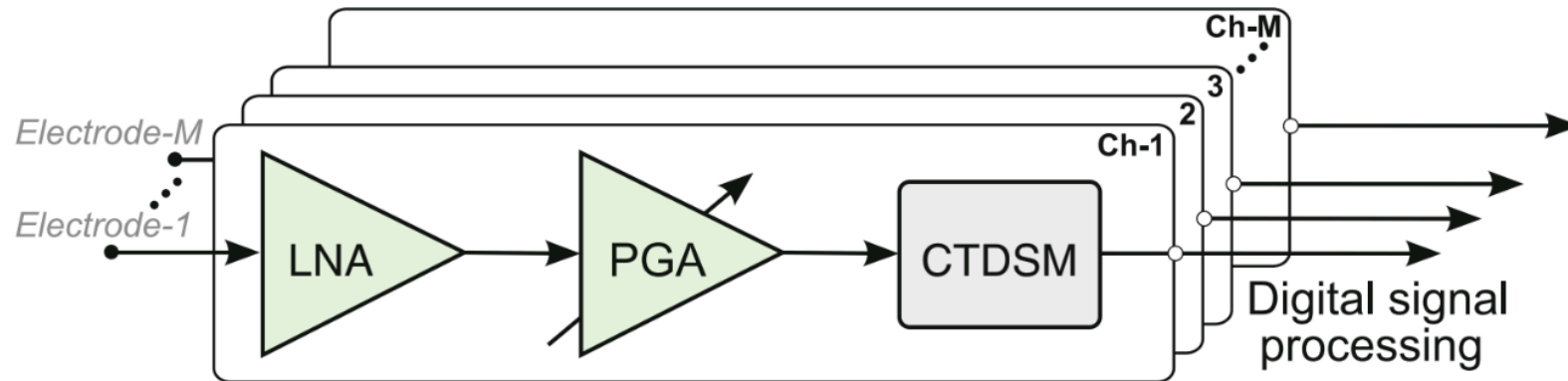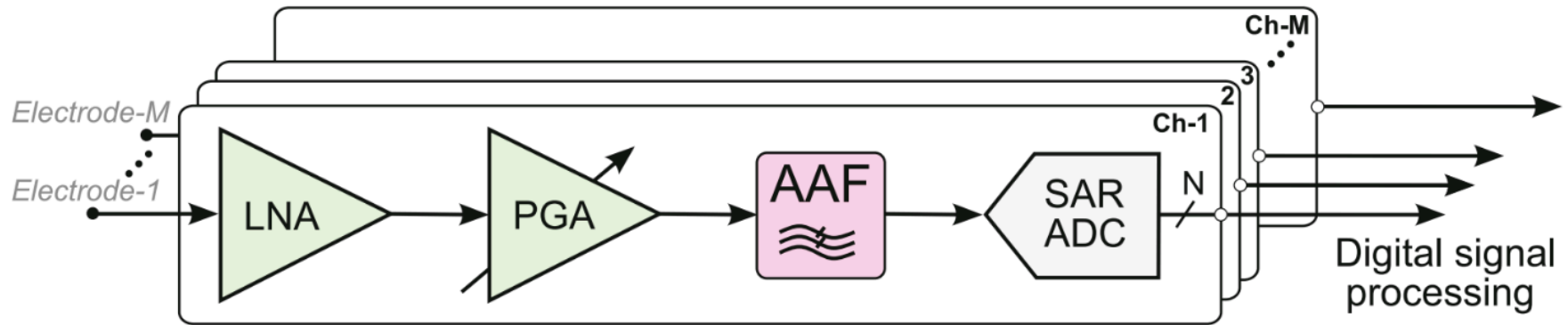



Big Ideas

- ❑ SQNR
 - SQNR determined by bit resolution, B
 - ENOB determined by SNR
- ❑ Oversampling
 - Enables reduction in quantization noise and reduces stress on AAF.
More next lecture...
- ❑ Nyquist ADCs
 - Speed vs. SNR tradeoff favors certain architectures for given application
 - Flash ADCs
 - Word-at-a-time for high speed, low resolution applications
 - SAR ADCs
 - Bit-at-a-time for low speed, low power applications
 - Highly suited for medical devices



Admin

- Lab tomorrow
 - More PCB population and testing