

ESE 3400: Medical Devices Lab

Lec 5: September 19, 2022

Signal Conditioning/Interface Circuits, Pt. 1




Lecture Outline

- Amplification
 - Opamp
 - Practical Opamp Circuits
- Biopotential Amplifier
- Lab 3 Setup
 - LT Spice
 - Amplification and filter schematic

Amplification

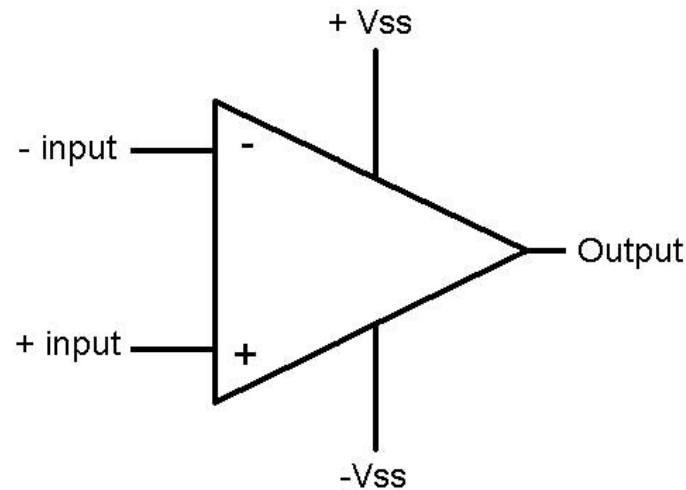
- ❑ Sensor outputs may (read: almost always) need amplification for any sort of acquisition and data analysis
- ❑ Use operational amplifier to do this
 - Amplifies differential input: $\text{Out} = A(V_{\text{in}+} - V_{\text{in}-})$, where A is large



Opamp

Ideal Opamp

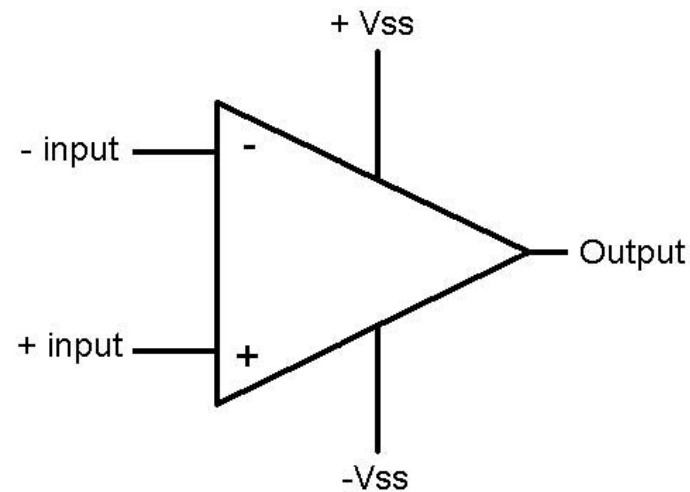- The ideal opamp characterized by seven properties
 - Knowledge of these properties is sufficient to design and analyze a large number of useful circuits






Basic Opamp Properties

- ❑ Property No.1: Infinite Open-Loop Gain
 - Open-Loop Gain A_{VOL} is the gain of the opamp without positive or negative feedback
 - In the ideal opamp A_{VOL} is infinite
 - Typical values range from 20,000 to 200,000 in real devices
- ❑ Property No.2: Infinite Input Impedance
 - Input impedance is the ratio of input voltage to input current, $Z_{in} = V_{in} / I_{in}$
 - When Z_{in} is infinite, the input current $I_{in} = 0$
 - High-grade opamps can have input impedance in the T Ω range
 - Some low-grade opamps, on the other hand, can have mA input currents

Basic Opamp Properties

□ Property No. 3: Zero Output Impedance

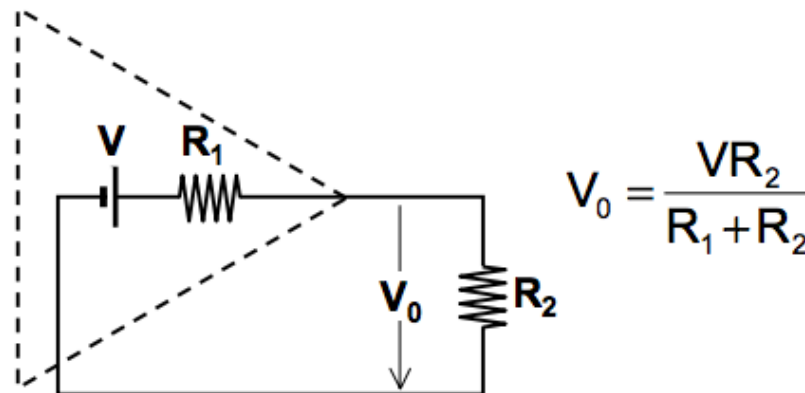- The ideal opamp acts as a perfect internal voltage source with no internal resistance
 - This internal resistance is in series with the load, reducing the output voltage available to the load
 - Real opamps have output-impedance in the 10-20 Ω range
- Example






Basic Opamp Properties

- ❑ Property No. 4: Zero Noise Contribution
 - In the ideal opamp, zero noise voltage is produced internally
 - That is, any noise at the output must have been at the input as well
 - Practical opamp are affected by several noise sources, such as resistive and semiconductor noise
 - These effects can have considerable effects in low signal-level applications

Basic Opamp Properties

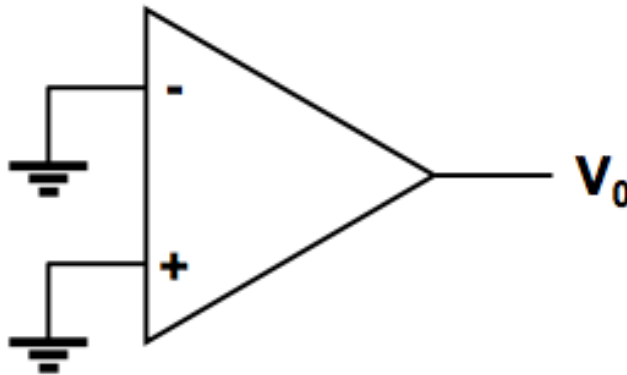- Property No. 5: Zero output Offset
 - The output offset is the output voltage of an amplifier when both inputs are grounded
 - The ideal opamp has zero output offset, but real opamps have some amount of output offset voltage






Basic Opamp Properties

- ❑ Property No. 6: Infinite Bandwidth
 - The ideal opamp will amplify all signals from DC to the highest AC frequencies
 - In real opamps, the bandwidth is rather limited
 - This limitation is specified by the Gain-Bandwidth product
 - $GBW = f_{3dB} * Gain_{3dB}$
 - Some opamps, such as the 741 family, have very limited bandwidth of up to a few KHz
- ❑ Property No. 7: Differential Inputs Stick Together*
 - In the ideal opamp, a voltage applied to one input also appears at the other input
 - *when connected in feedback

Ohm's Law and Kirchoff's Laws

□ Ohm's Law

- $V = IR$

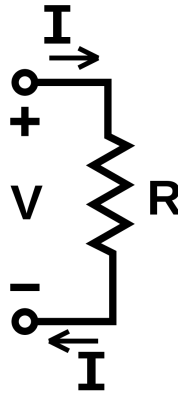

□ KCL – Kirchoff's Current Law


- The sum of the currents into a node = 0

□ KVL – Kirchoff's Voltage Law

- The sum of the voltage differences around any closed loop in a circuit must be zero


KCL

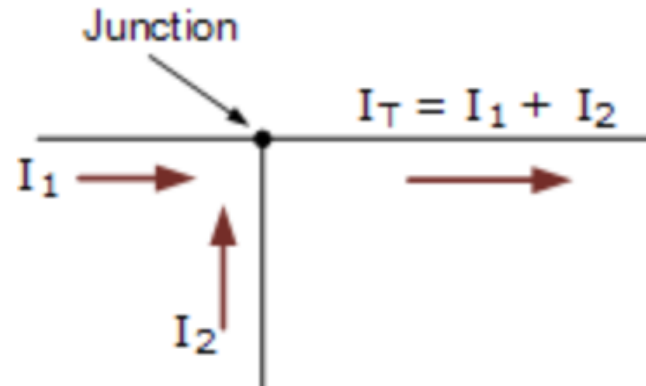- KCL – Kirchoff's Current Law
 - The sum of the currents into a node = 0



KVL

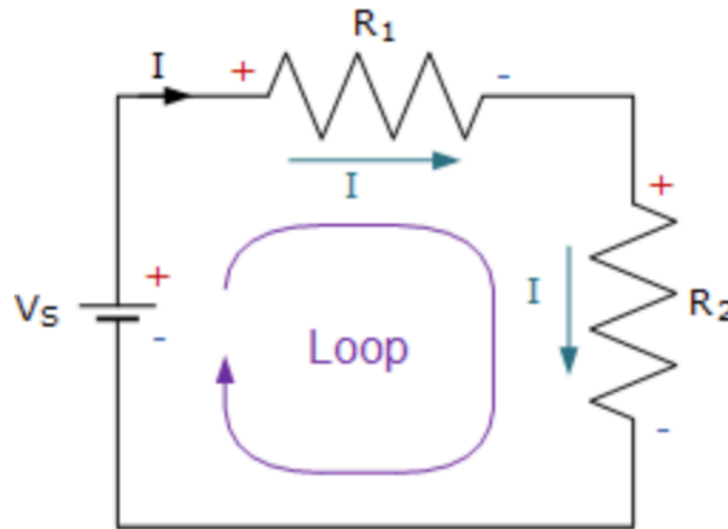
- KVL – Kirchoff's Voltage Law
 - The sum of the voltage differences around any closed loop in a circuit must be zero






Opamp Practical Circuits

□ A)


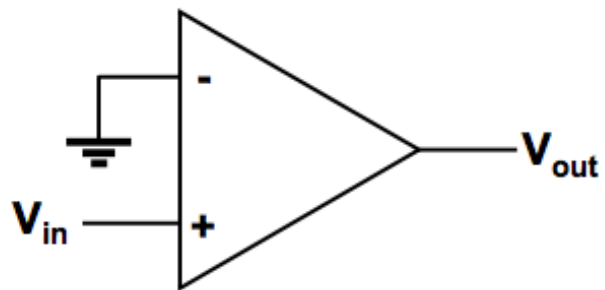


□ B)

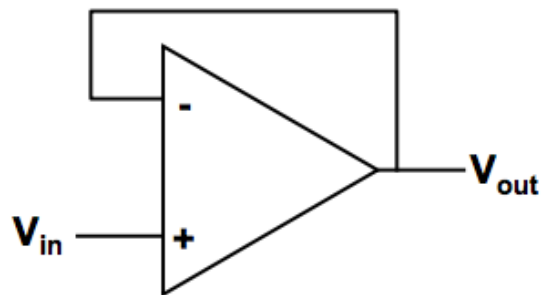


Opamp Practical Circuits

□ A) Voltage comparator

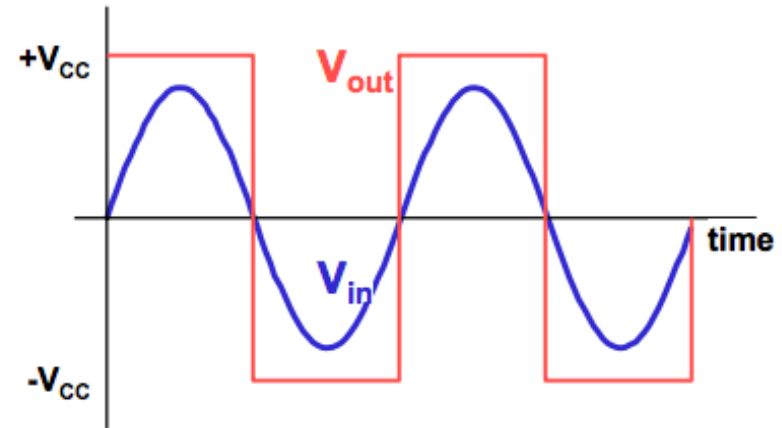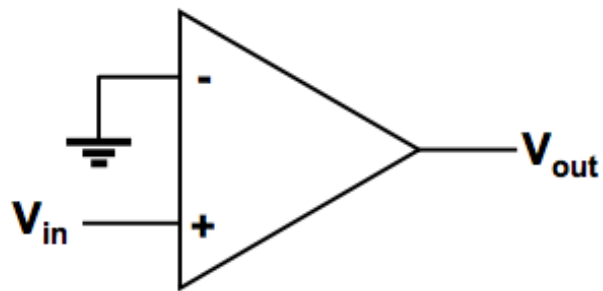


□ B) Voltage follower (Buffer)

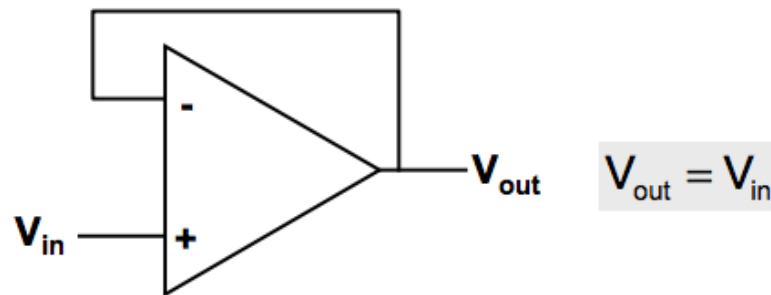


Opamp Practical Circuits

□ C)

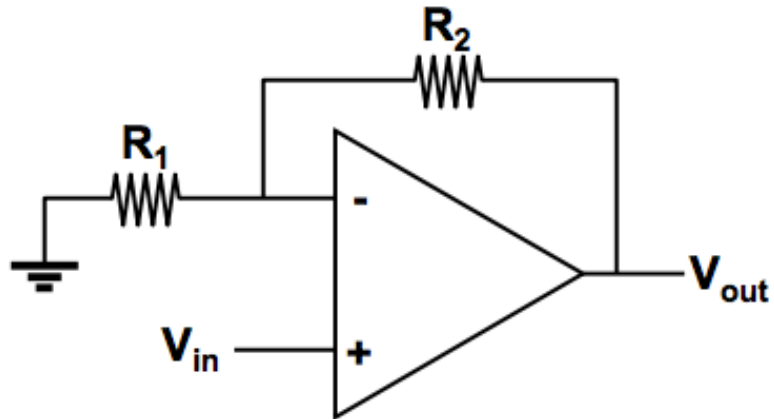


□ D)

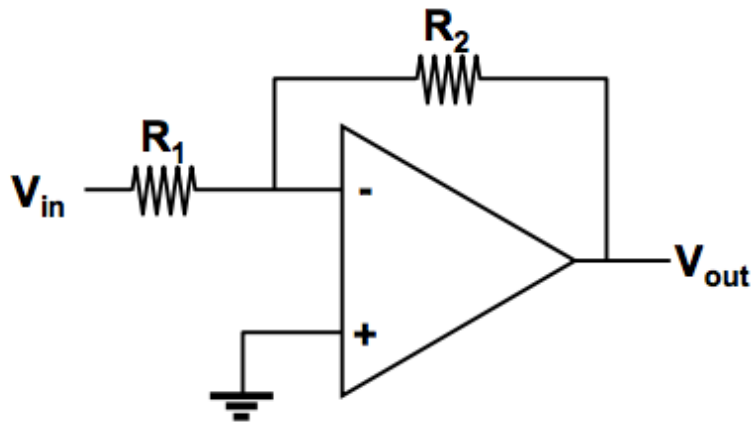


Opamp Practical Circuits

□ C) Non-inverting amplifier

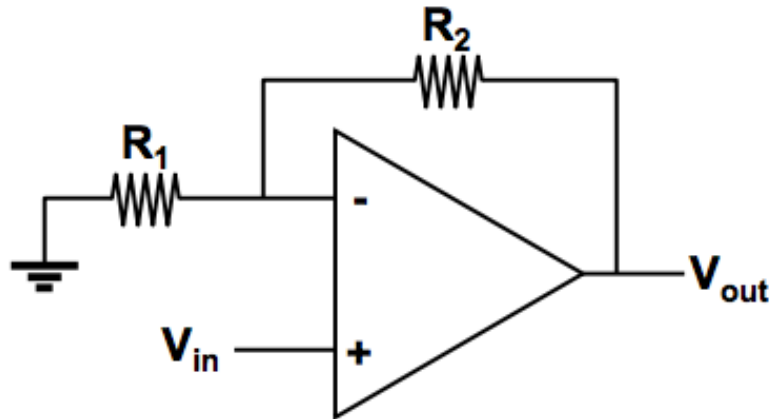

$$V_{\text{out}} = \left(1 + \frac{R_2}{R_1}\right) V_{\text{in}}$$


□ D) Inverting amplifier

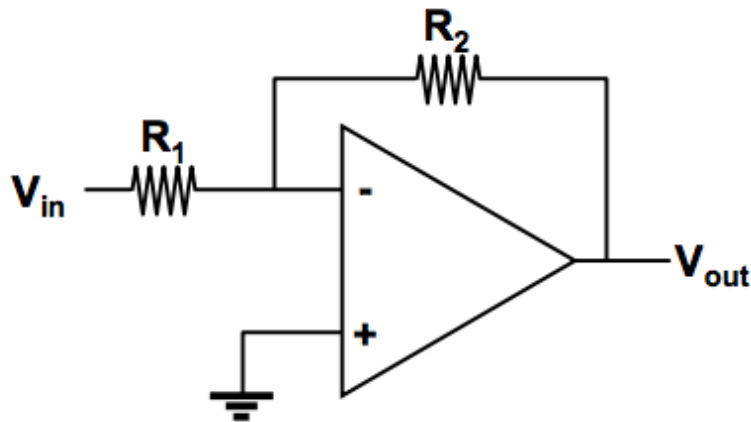

$$V_{\text{out}} = -\frac{R_2}{R_1} V_{\text{in}}$$

Biopotential Amplifier

- Differential amplifier

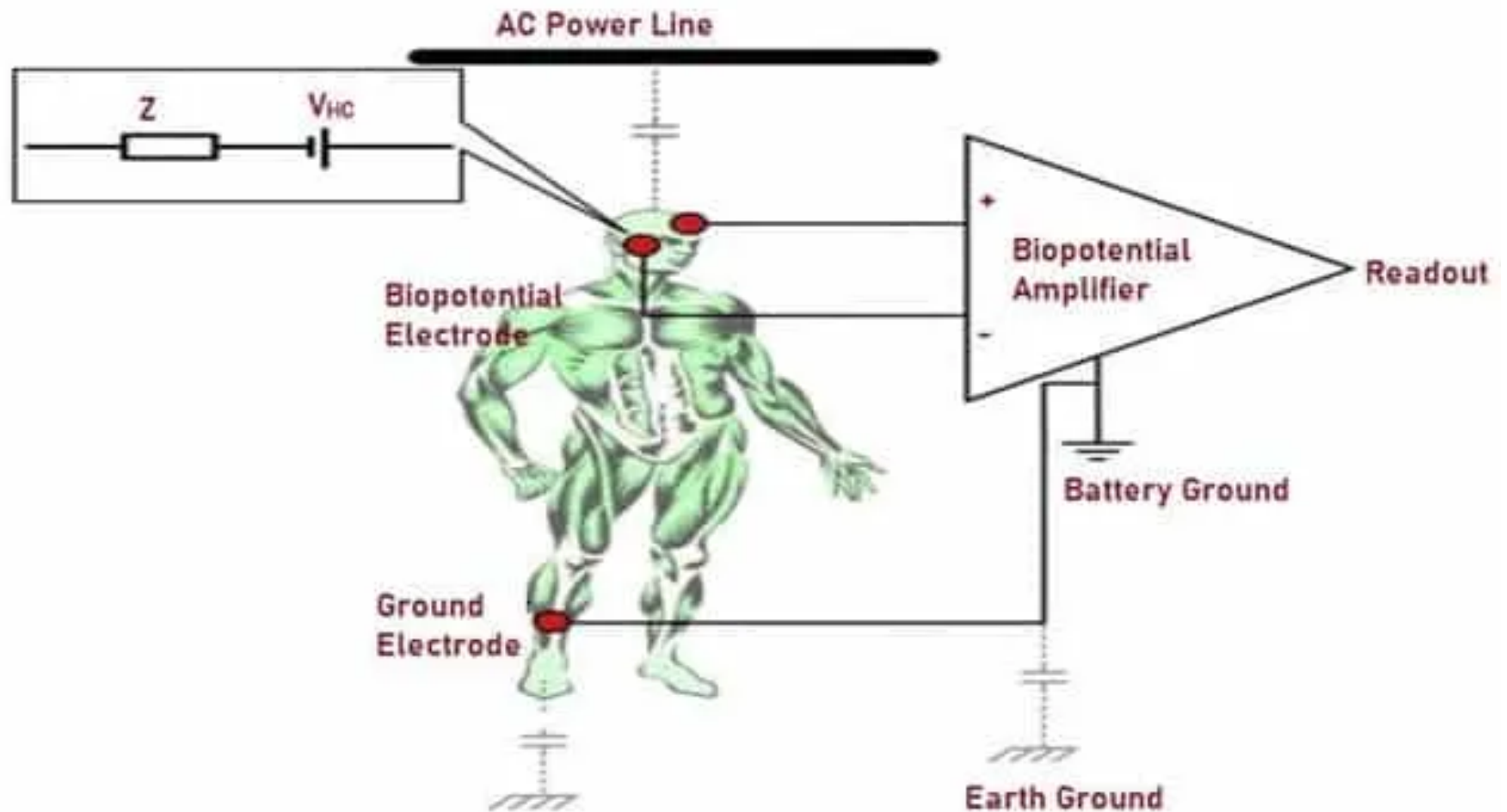

Biopotential Amplifier

□ Differential amplifier

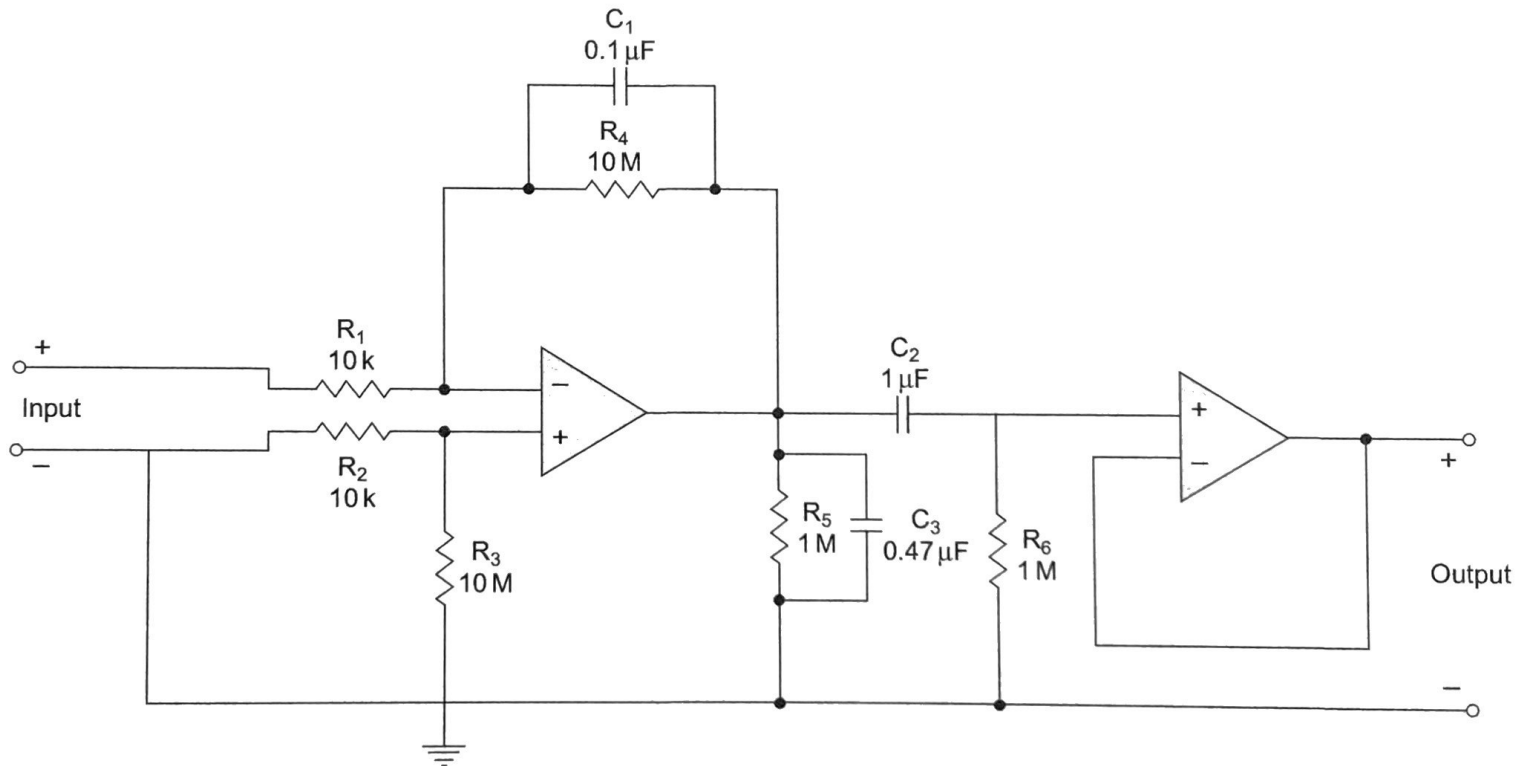


FIGURE 1.20

Differential biopotential amplifier.

Adapted from Prutchi and Norris (2005).

Biopotential Amplifier

□ Differential amplifier

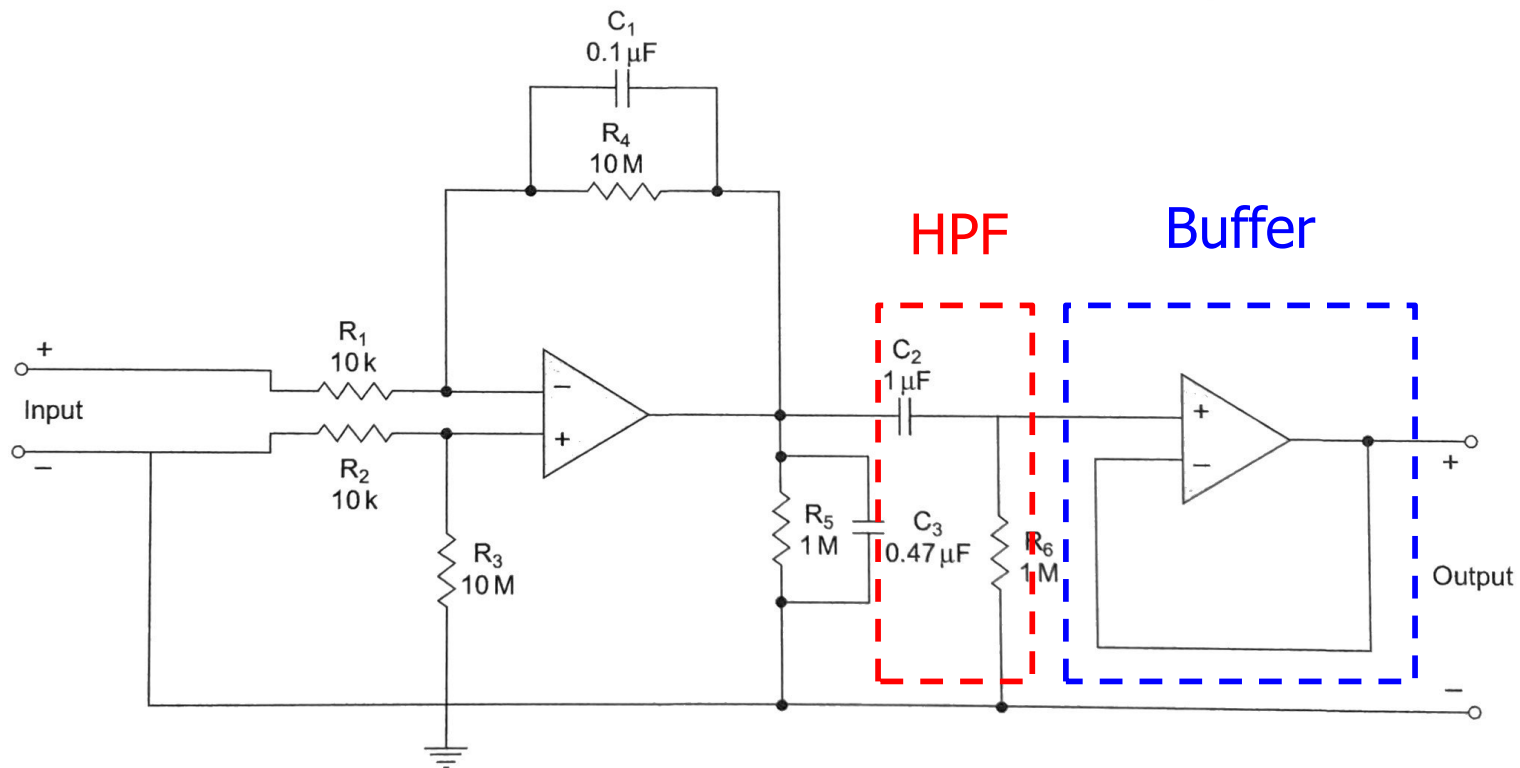


FIGURE 1.20

Differential biopotential amplifier.

Adapted from Prutchi and Norris (2005).

Biopotential Amplifier

□ Differential amplifier

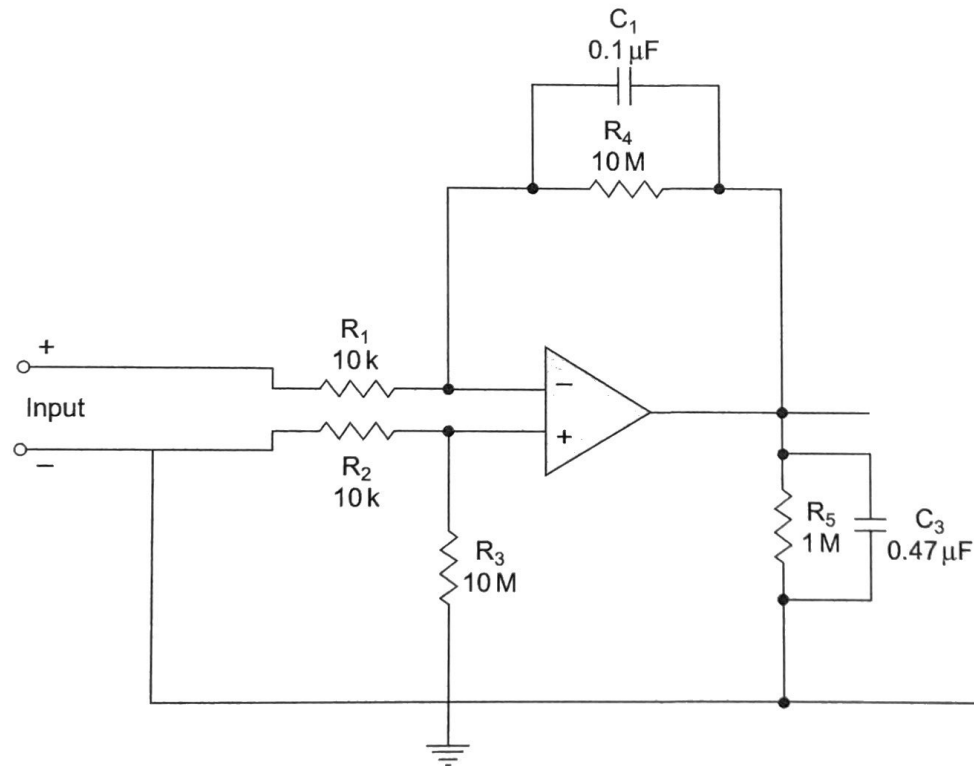


FIGURE 1.20

Differential biopotential amplifier.

At

Biopotential Amplifier

□ Differential amplifier

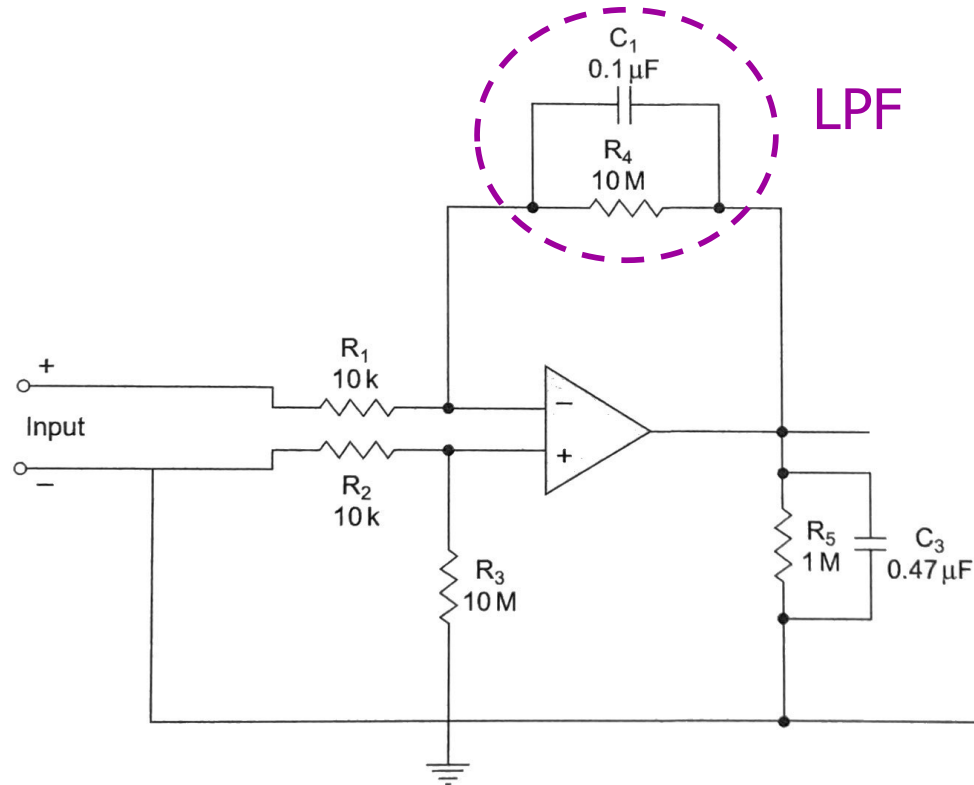


FIGURE 1.20

Differential biopotential amplifier.

At

Biopotential Amplifier

□ Differential amplifier

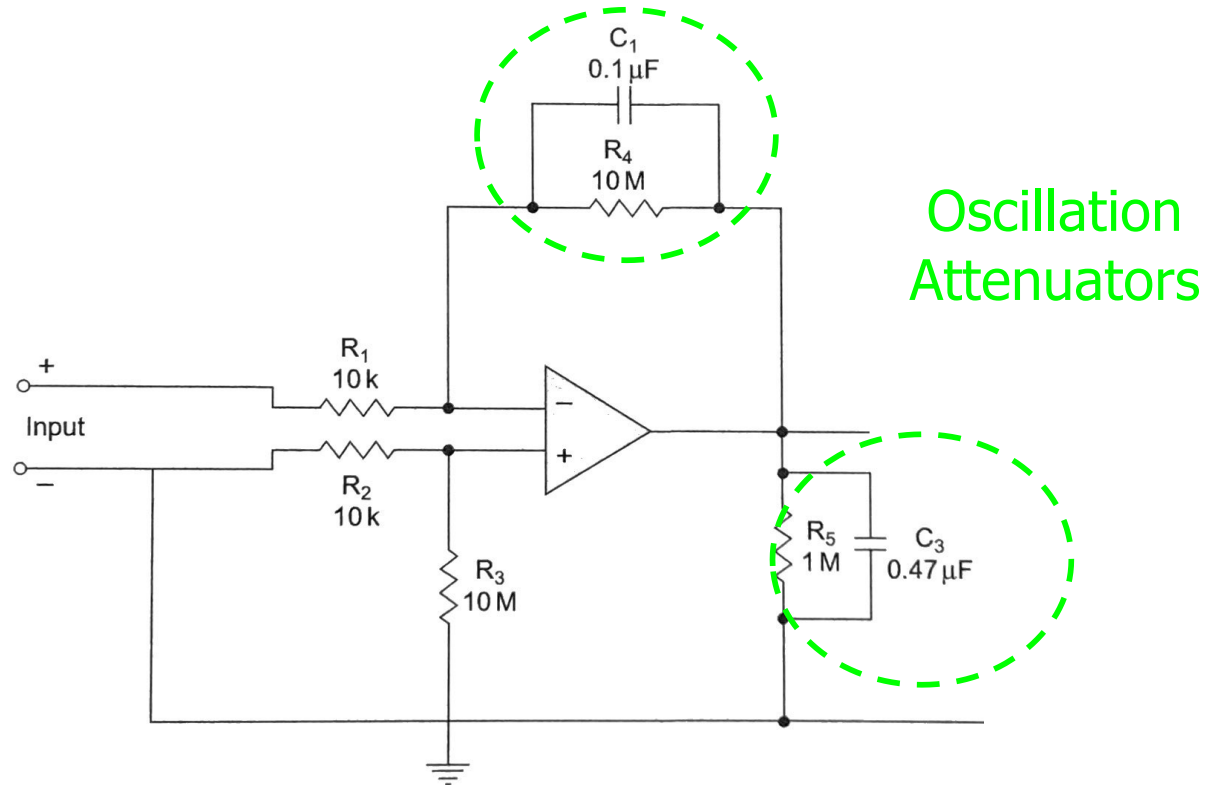


FIGURE 1.20

Differential biopotential amplifier.

A_c



Lab 3

- ❑ LT Spice
- ❑ Simulate the signal conditioning specific to our ECG design




LT Spice

□ Circuit Simulator

- LTspice is high performance SPICE simulator software, including a graphical schematic capture interface. Schematics can be probed to produce simulation results—easily explored through LTspice’s built-in waveform viewer.

LT Spice BP Filter Example

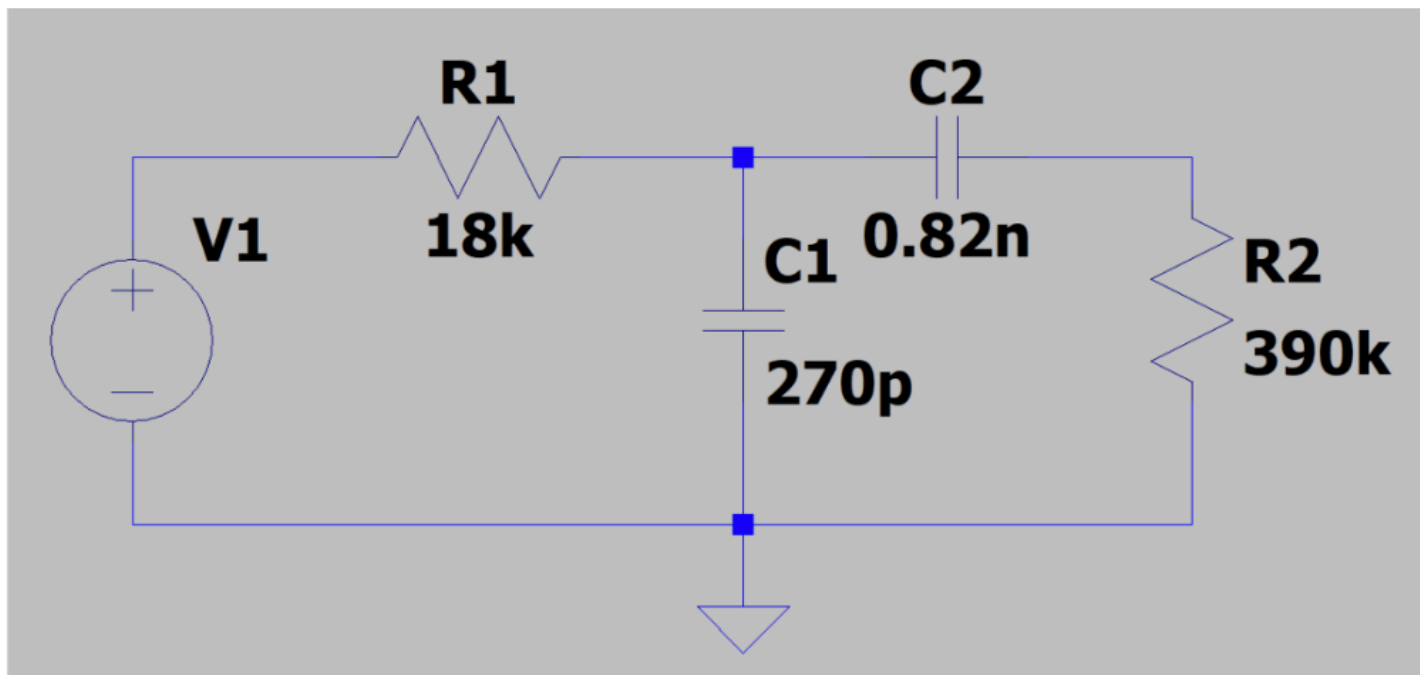

Lab 3


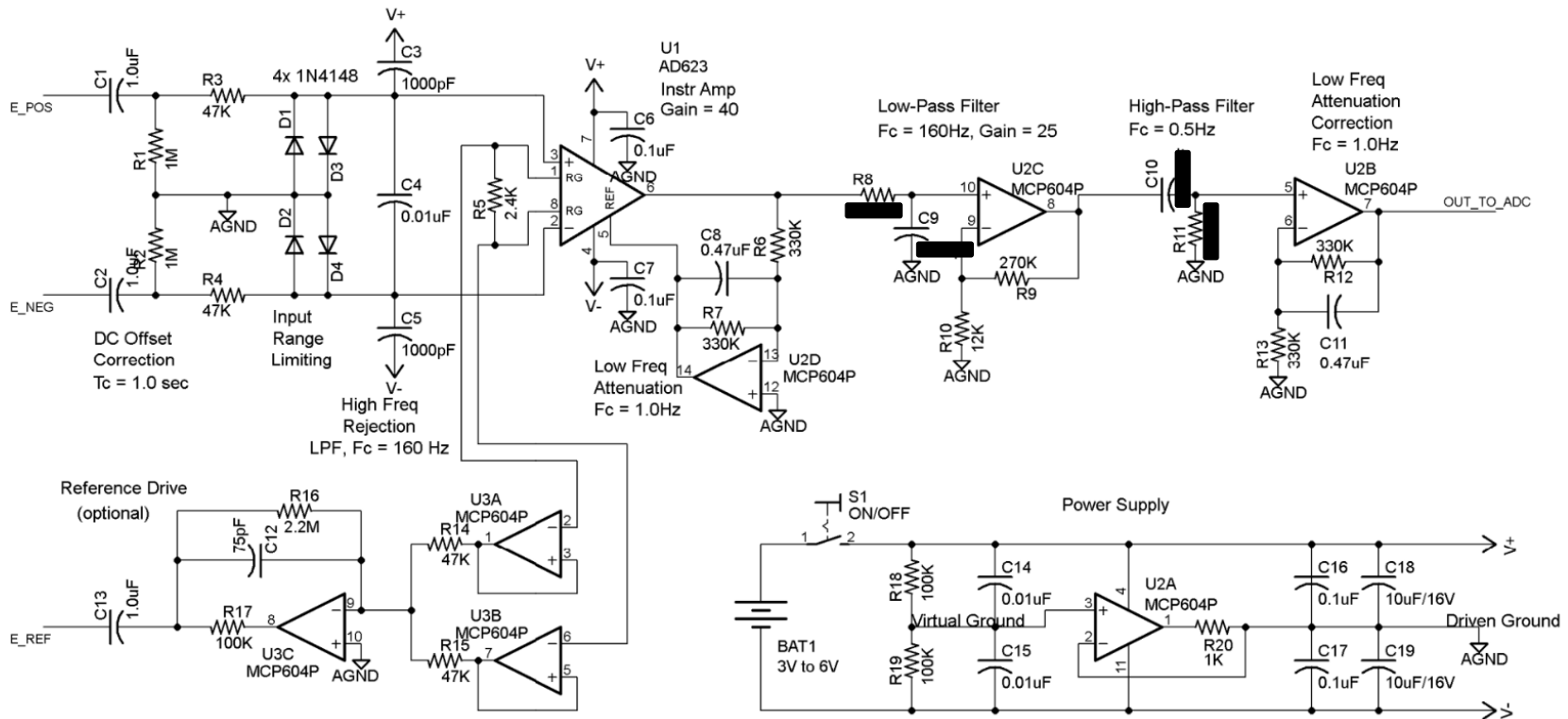



Figure 2: Schematic of 2-Electrode ECG Amplifier with Optional Driven Reference Electrode

Lab 3

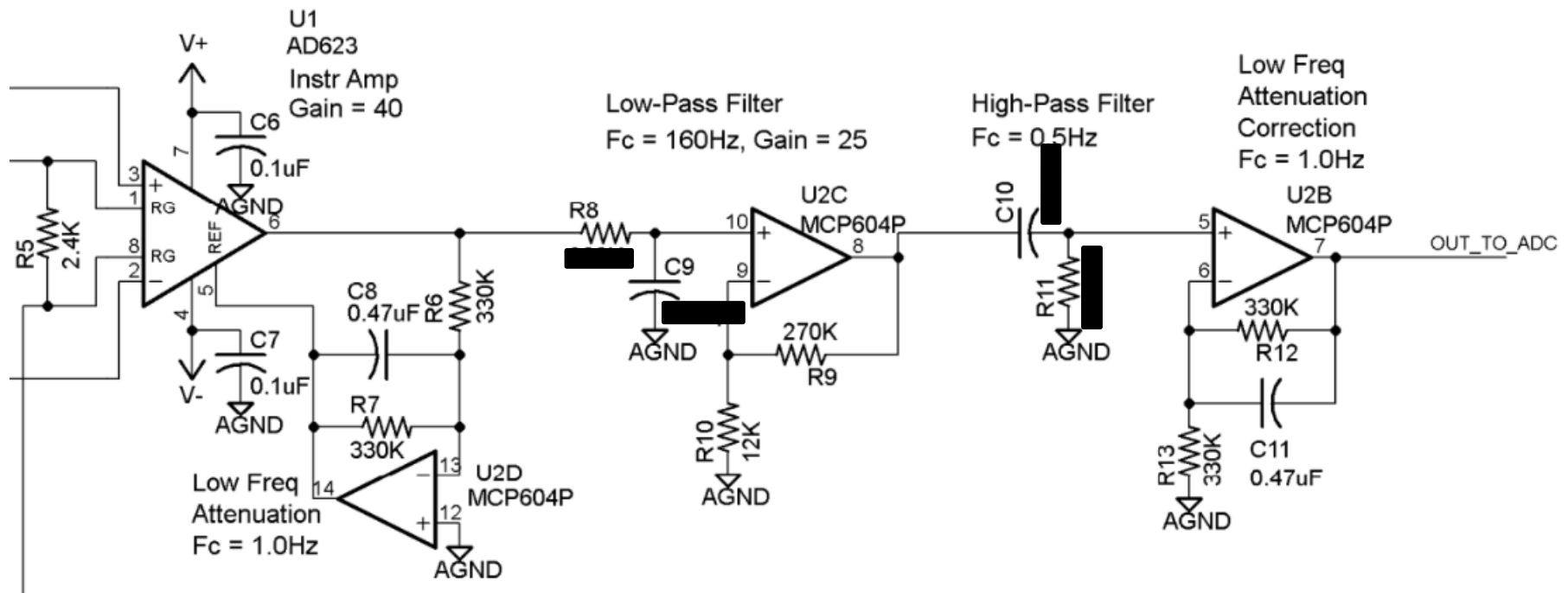



Lab 3

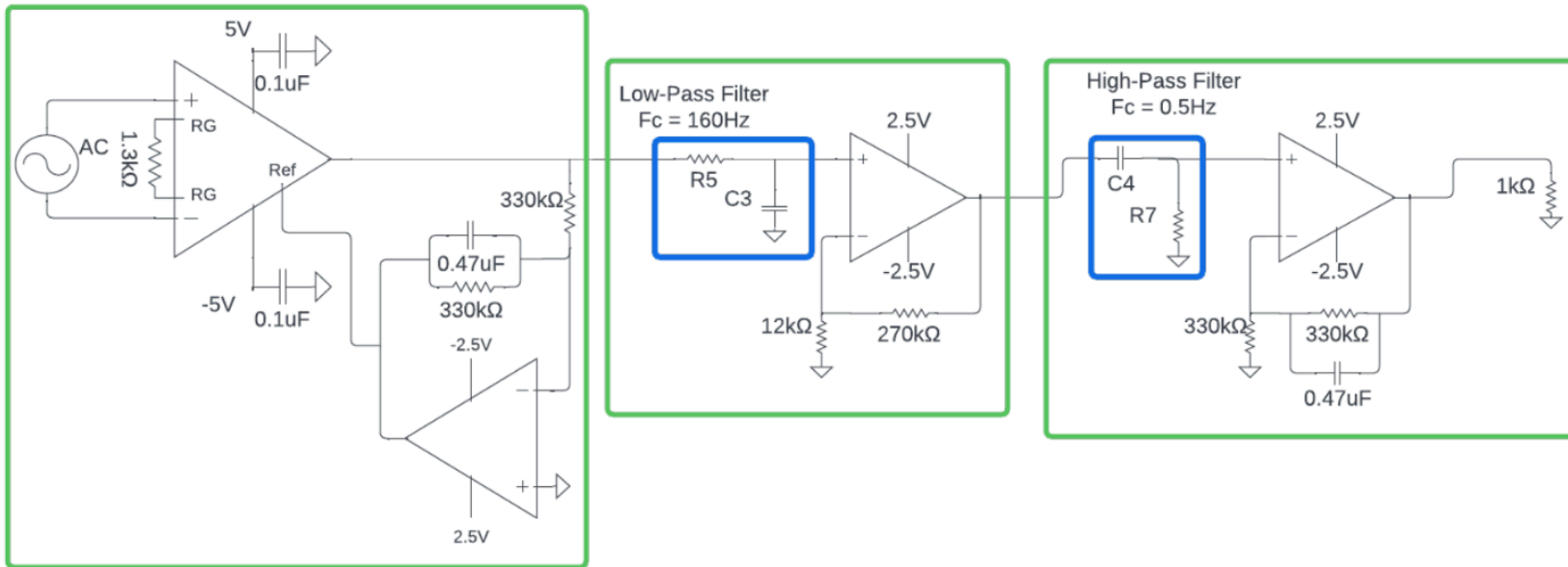



Big Ideas

- ❑ Amplification
 - Use operational amplifier with differential signaling
- ❑ Biopotential Amplifier
 - Designed to amplify and filter sensor outputs for data acquisition or driving



Admin

- ❑ Finish Lab 2 and submit deliverables in Canvas by next lab day at midnight