

# ESE 3400: Medical Devices Lab

---

Lec 6: September 21, 2022  
Interface Circuits, Pt. 2




# Lecture Outline

---

- ❑ Biopotential Amplifier
  - Non-idealities
- ❑ Instrumentation Amplifier
- ❑ Driven Right Leg System
- ❑ Lab 3 Circuit


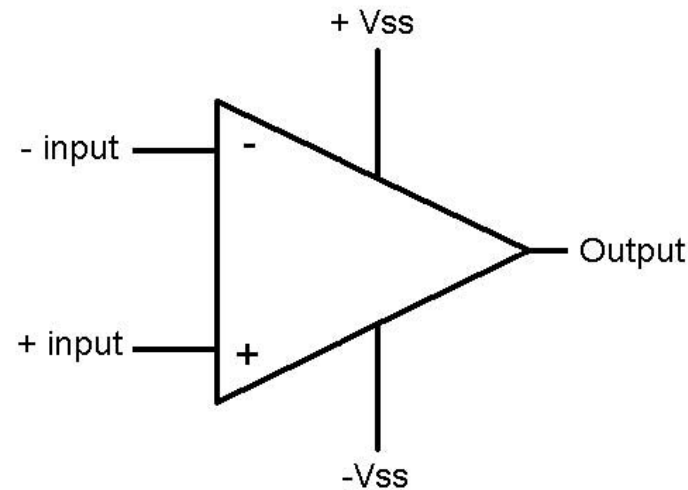
# Amplification

- ❑ Sensor outputs may (read: almost always) need amplification for any sort of acquisition and data analysis
- ❑ Use operational amplifier to do this
  - Amplifies differential input:  $\text{Out} = A(V_{\text{in}+} - V_{\text{in}-})$ , where  $A$  is large




# Opamp Practical Circuits

## □ A) Voltage comparator

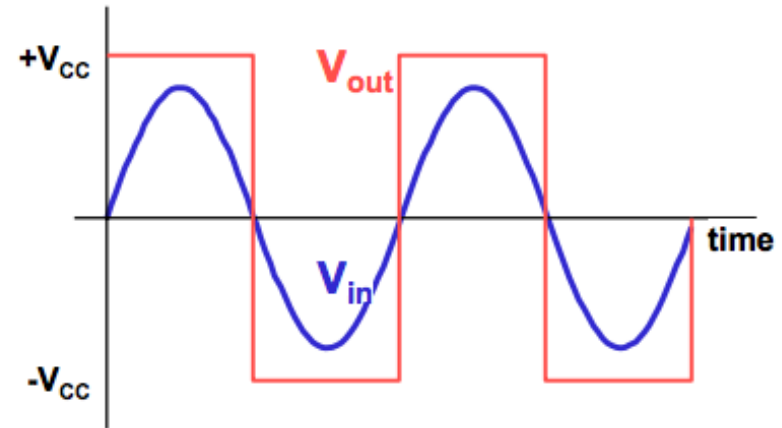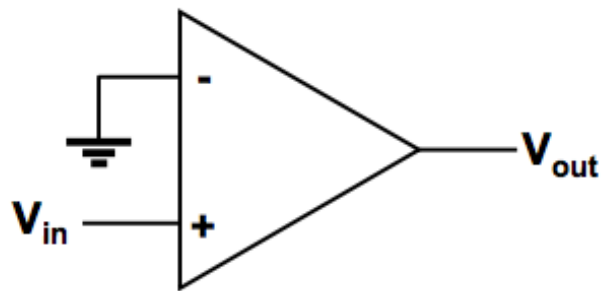


## □ B) Voltage follower (Buffer)

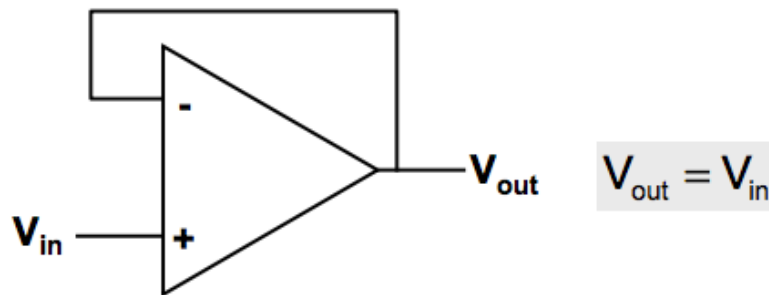


# Opamp Practical Circuits

## □ C) Non-inverting amplifier

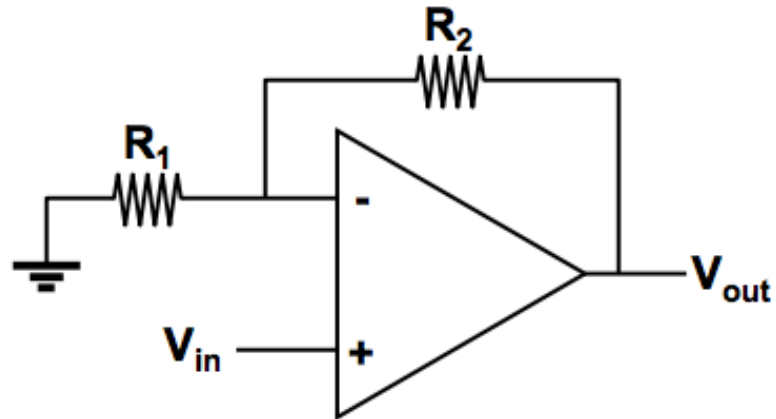

$$V_{out} = \left(1 + \frac{R_2}{R_1}\right) V_{in}$$


## □ D) Inverting amplifier

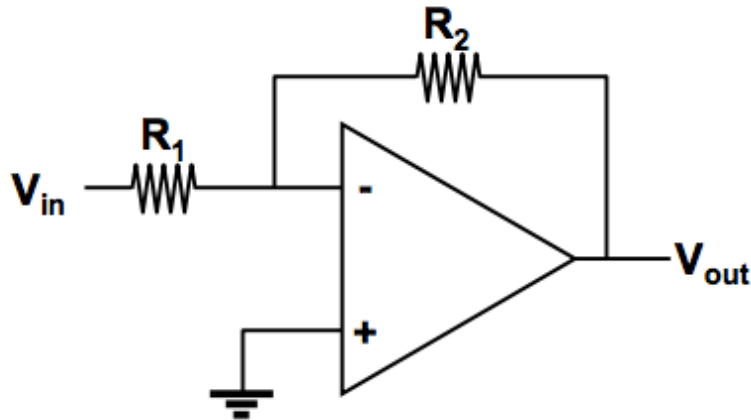

$$V_{out} = -\frac{R_2}{R_1} V_{in}$$


# Biopotential Amplifier

## □ Differential amplifier

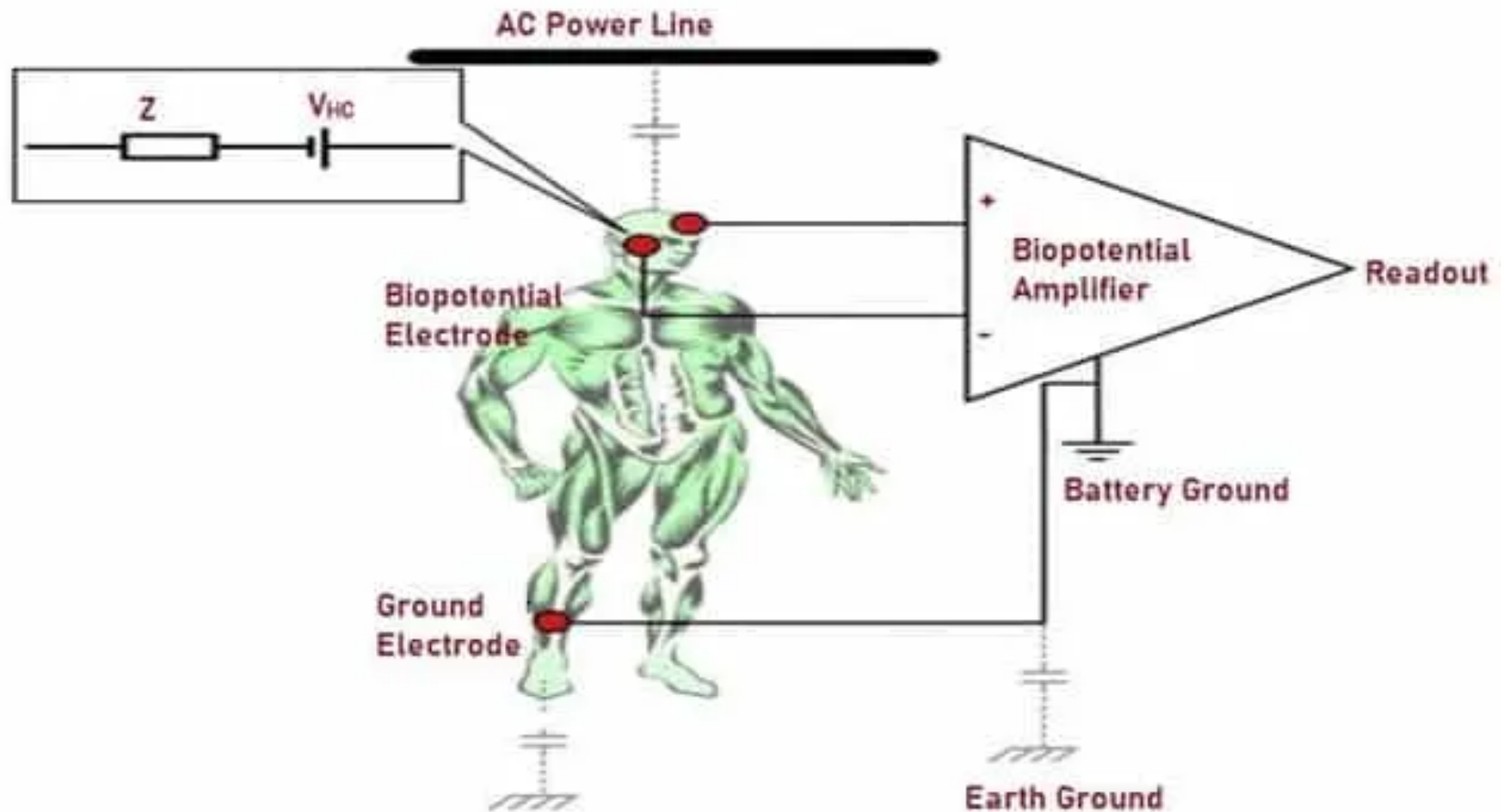

# Biopotential Amplifier

## □ Differential amplifier

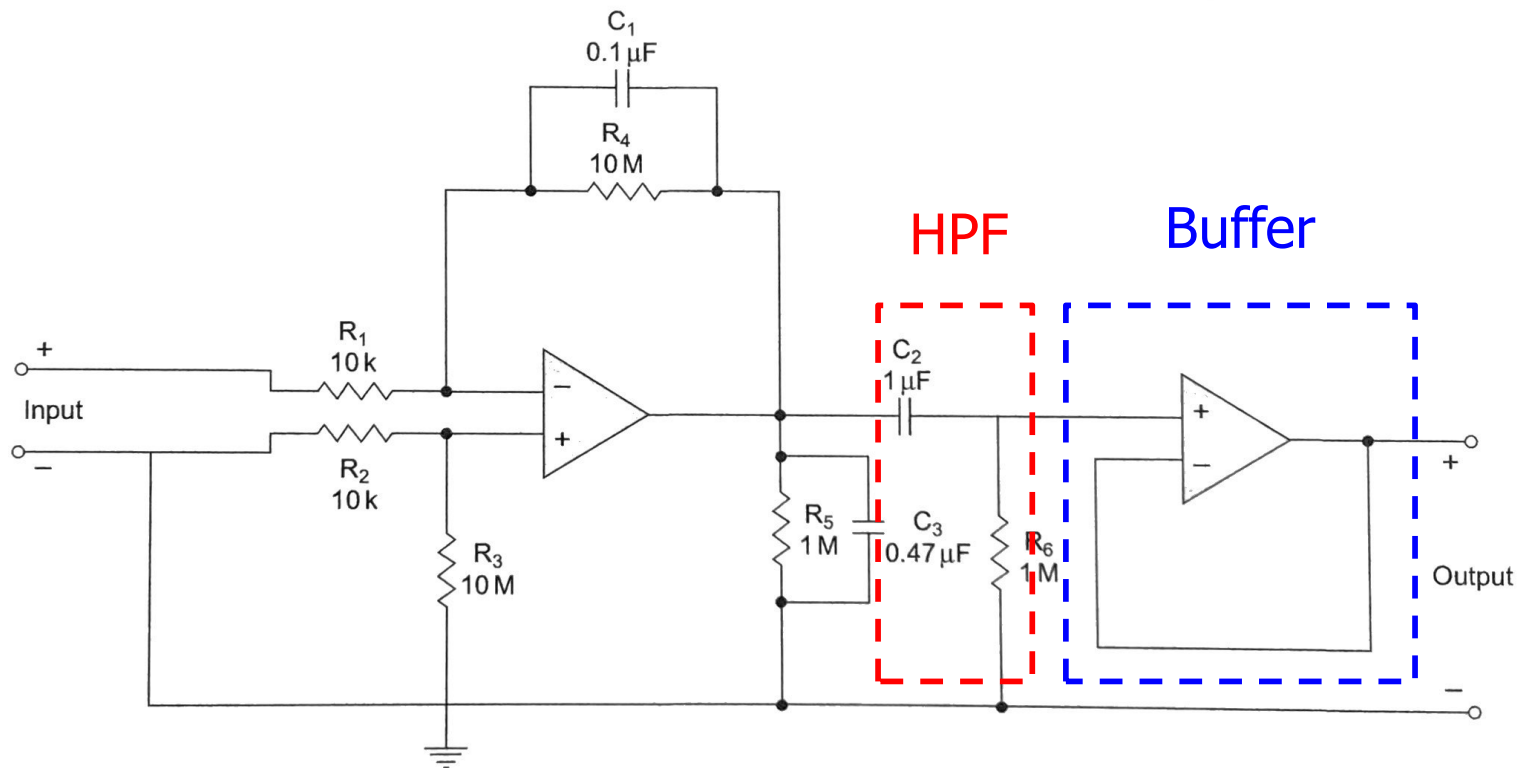


**FIGURE 1.20**

Differential biopotential amplifier.

*Adapted from Prutchi and Norris (2005).*

# Biopotential Amplifier

## □ Differential amplifier

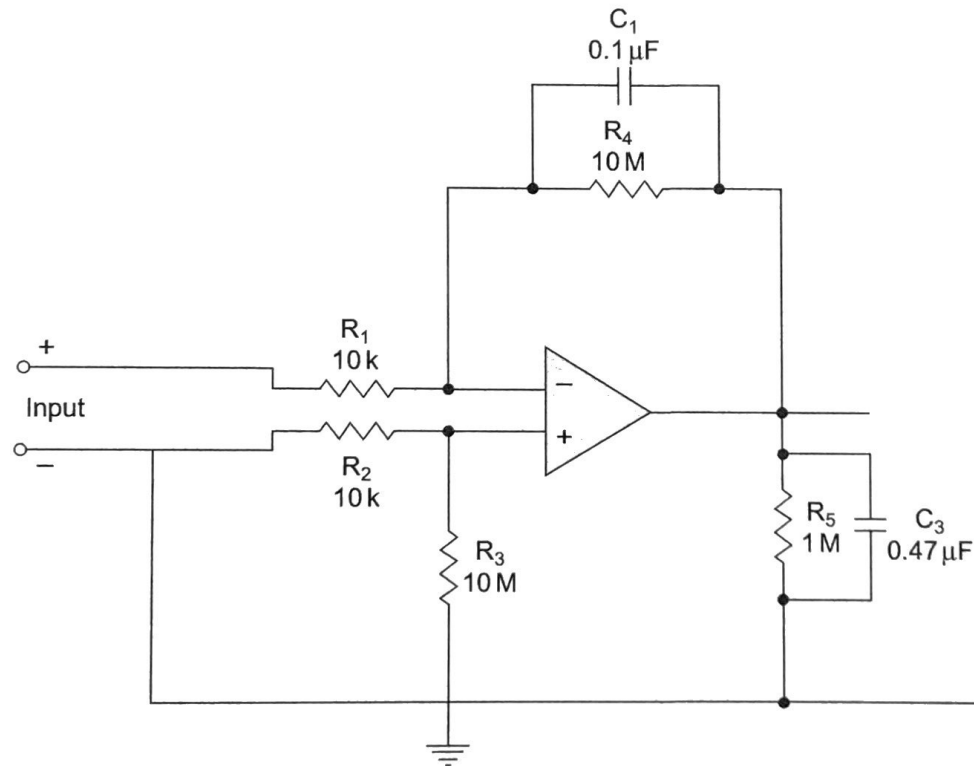

**FIGURE 1.20**


Differential biopotential amplifier.

*A<sub>c</sub>*



# Biopotential Amplifier

## □ Differential amplifier

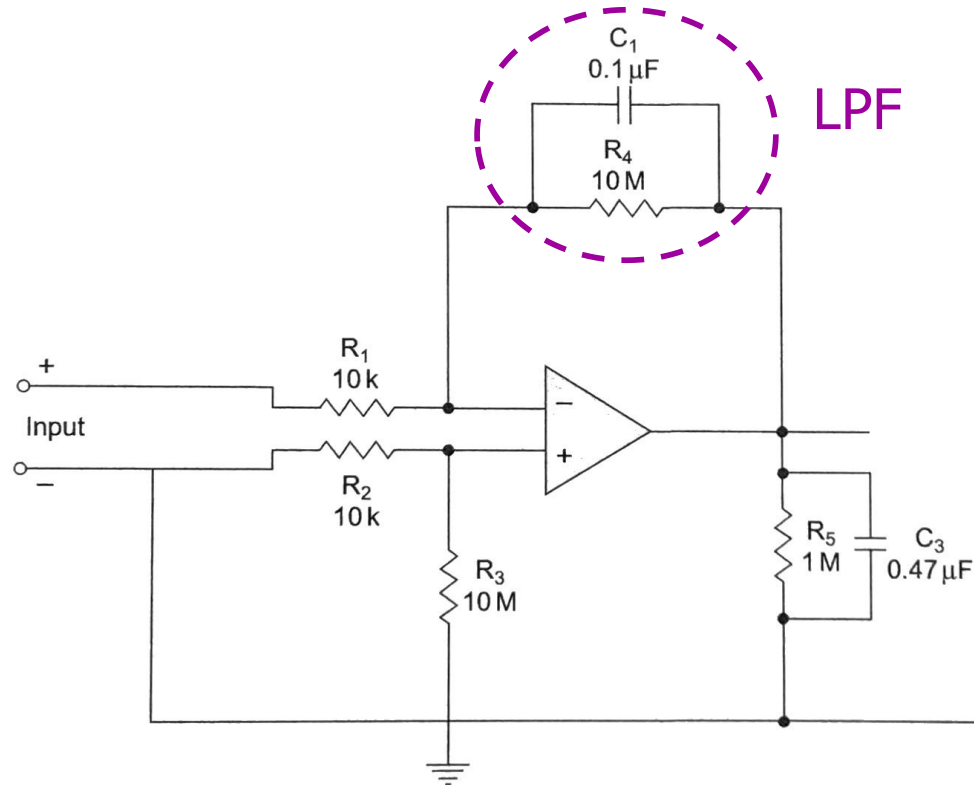


**FIGURE 1.20**

Differential biopotential amplifier.

$A_c$

# Biopotential Amplifier

## □ Differential amplifier

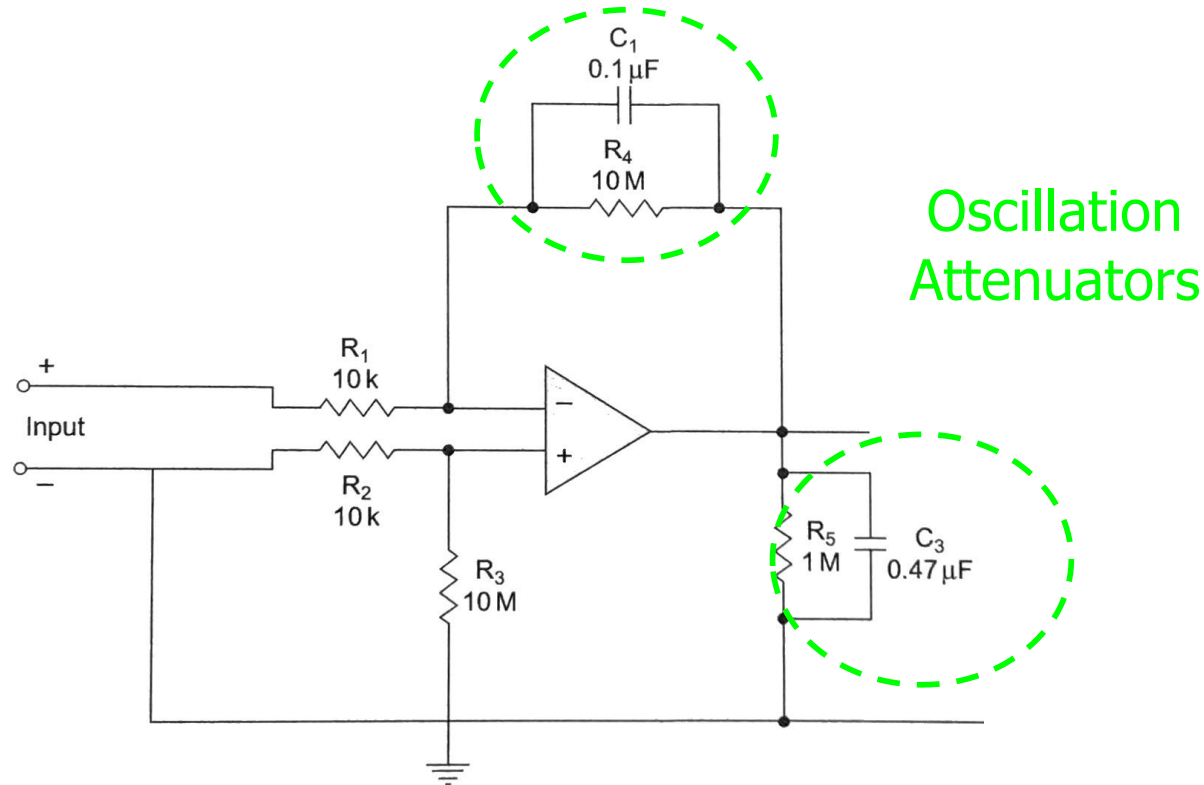

**FIGURE 1.20**

Differential biopotential amplifier.

$A_c$



# Biopotential Amplifier

---

- ❑ Basic function to increase the amplitude of a weak electric signal of biological origin typically process voltages
  
- ❑ Typical bio-amp requirements
  - High input impedance greater than  $10\text{ M}\Omega$
  - Safety: protect the organism being studied
    - Careful design to prevent macro and microshocks
    - Isolation and protection circuitry to limit the current through the electrode to safe level




# Biopotential Amplifier

---

- ❑ Typical bio-amp requirements (con't)
  - Output impedance of the amplifier
    - should be low to drive any external load with minimal distortion
  - Gain greater than 1000
    - Biopotentials are typically less than a millivolt
  - Most are differential
  - High common mode rejection ratio
    - Biopotentials ride on a large offset signal
  - Rapid calibration of the amplifier in laboratory conditions
  - Adjustable gains
    - Often the change in scale is automatic

# Voltage and Frequency Range

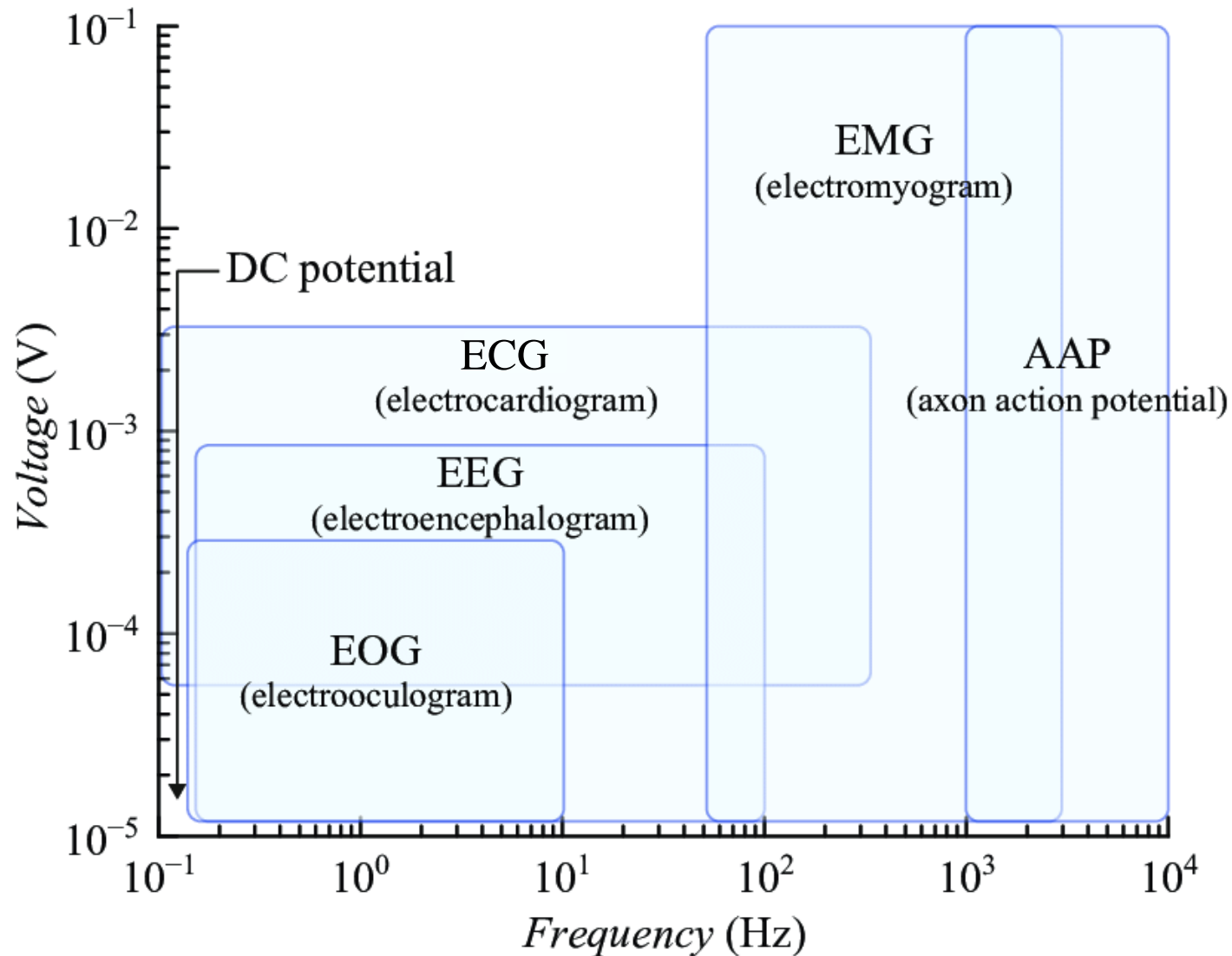


# ECG Amplifiers

- ❑ Beating heart generates electric signal
  - monitored to understand heart functions
- ❑ Measurements are functions of
  - location at which the signal is detected
  - time-dependence of the signal amplitude
- ❑ Different pairs of electrodes at different locations yield different measurements
  - hence placement is standardized


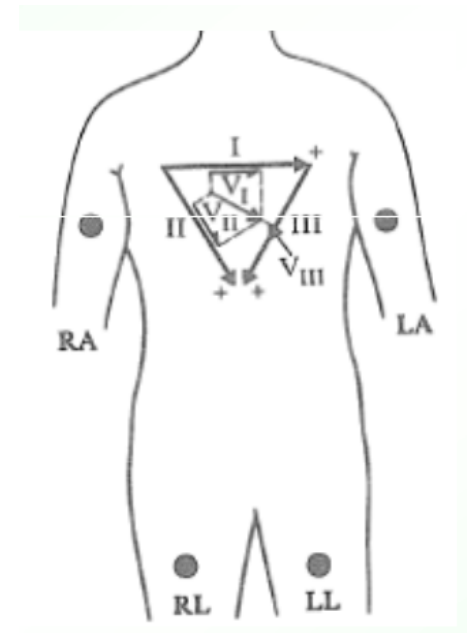
# ECG Leads

- ❑ In clinical electrocardiography
  - more than one lead must be recorded to describe the heart's electric activity fully
  - several leads are taken in the frontal plane and the transverse plane
    - frontal plane: parallel to the back when lying
    - transverse plane: parallel to the ground when standing
- ❑ Frontal plane lead placement called Eindhoven's triangle




# Problems in ECG Measurement

- ❑ Frequency distortion
  - If filter specification does not match the frequency content of biopotential then the results is high and low frequency distortion
- ❑ Saturation of cutoff distortion
  - High electrode offset voltage can drive the amplifier to saturation causing peaks of waveform (QRS) to be cut off
- ❑ Ground loops
  - Can cause small currents to flow through patient's body
- ❑ Electric/magnetic field coupling
  - Open lead wires and long loops pick up EMI
- ❑ Interference from power lines (60Hz noise)

60Hz supply noise

Coupled to ECG

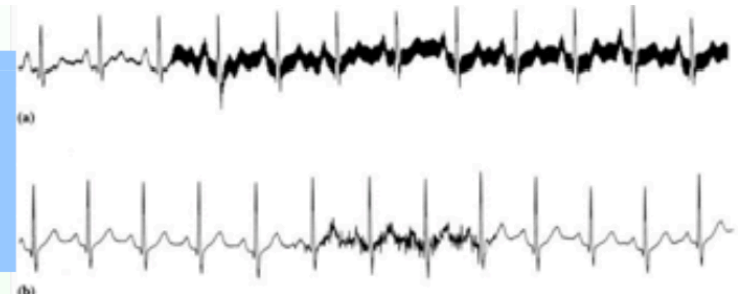






# Interference Reduction Techniques


---

- ❑ Common-mode voltages can be responsible for much of the interference in biopotential amplifiers.
  - Solution 1:
    - Amplifier with a very high common-mode rejection
  - Solution 2:
    - Eliminate the source of interference
- ❑ Ways to eliminate interference
  - Use shielding techniques
    - Electrostatic shielding: Place a grounded conducting plane between the source of the interference and measurement system
      - Very important for EEG measurement
    - Magnetic shield: Use high permeability materials (sheet steel)
    - Use twisted cables to reduce loops


# Illustration of Common Mode Influence

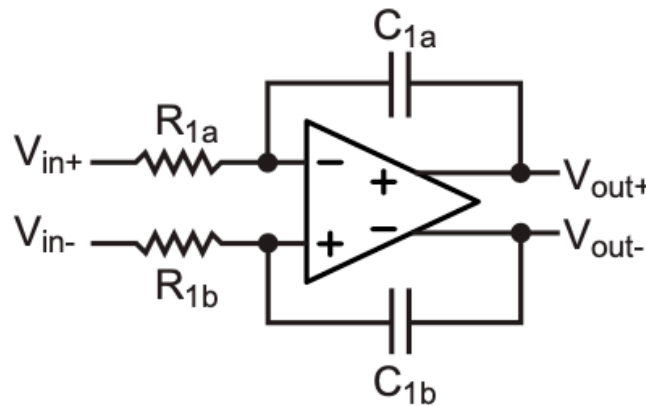


**Common-Mode Too High**

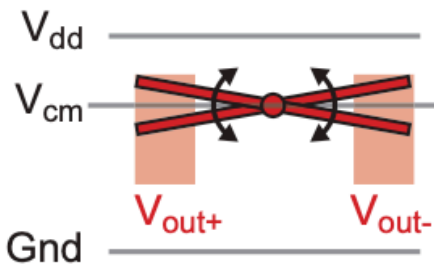

**Common-Mode Too Low**

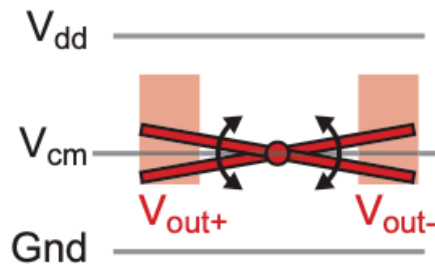


**Common-Mode Just Right**

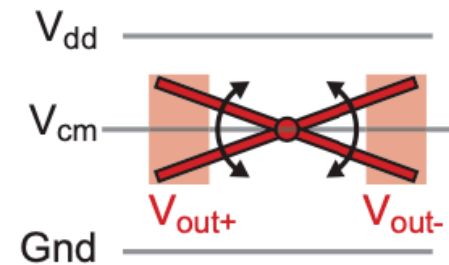

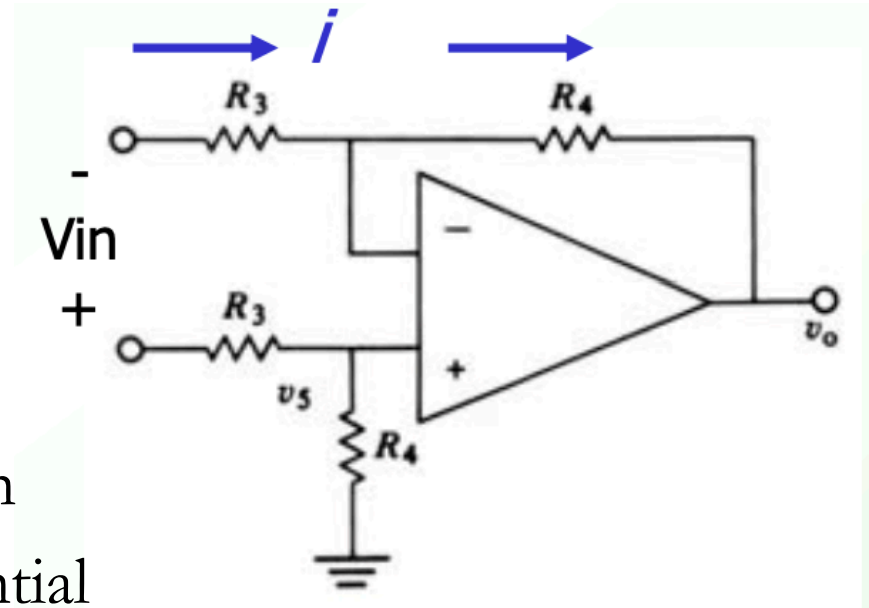
# Differential Amplifier

- ❑ One-amp differential amplifier
- ❑ Differential gain:
  - $\frac{v_o}{v_i} = \frac{R_4}{R_3}$ , where  $R_4 \gg R_3$
- ❑ Characteristics
  - Good common mode rejection
  - Input resistance of the differential amplifier is lower than ideal op-amp
    - Not good for many biomedical applications



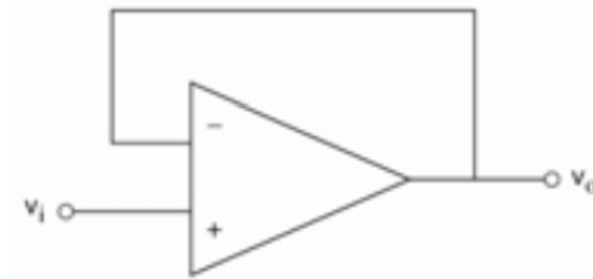
# Differential Amplifier

- ❑ How can we fix the low input impedance?
- ❑ Option 1: Add voltage follower at each input
  - Pros and cons?



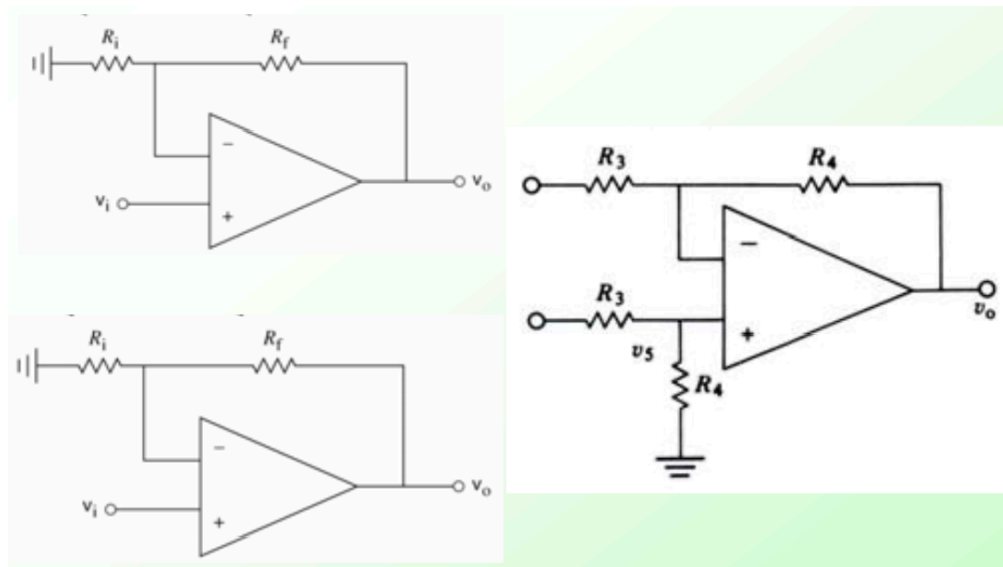
- ❑ Option 2: Add non-inverting amplifier at each input
  - Pros and cons?



# Instrumentation Amplifier

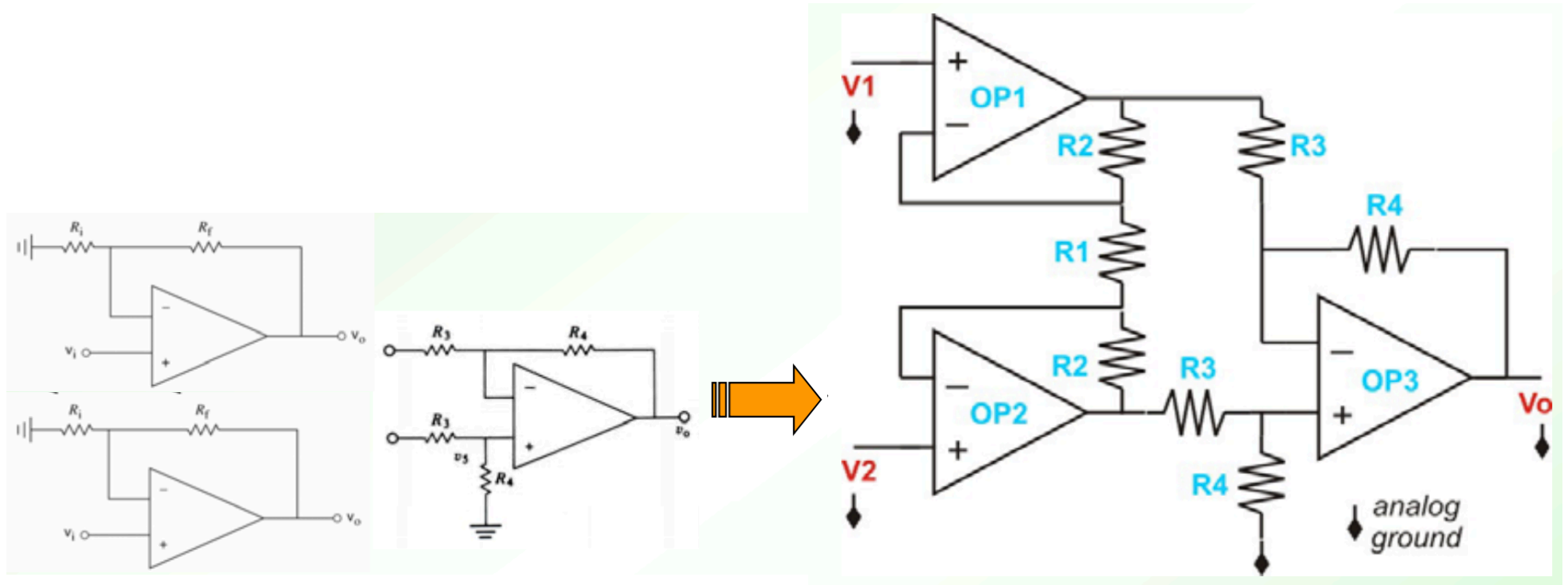
## □ Better option

- Share R in input amps and eliminate ground connection



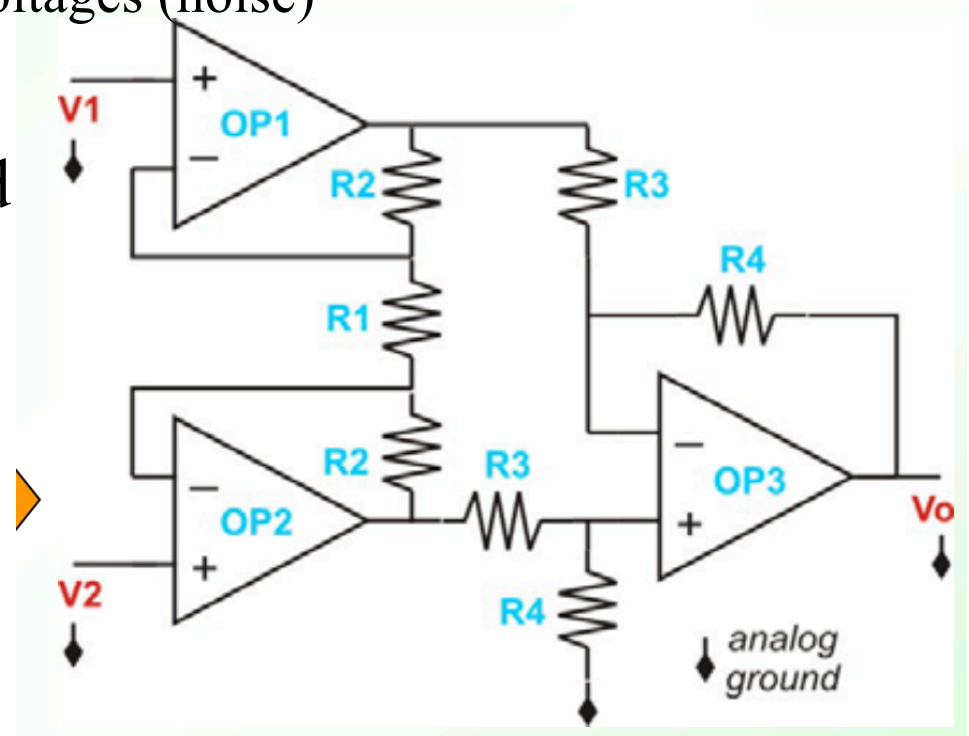
# Instrumentation Amplifier


- ❑ This 3-op-amp circuit is called an **instrumentation amplifier**
- ❑ Input stage characteristics
  - low common-mode gain
    - -rejects common mode voltages (noise)
  - high input impedance
  - Input stage gain adjusted



# Instrumentation Amplifier

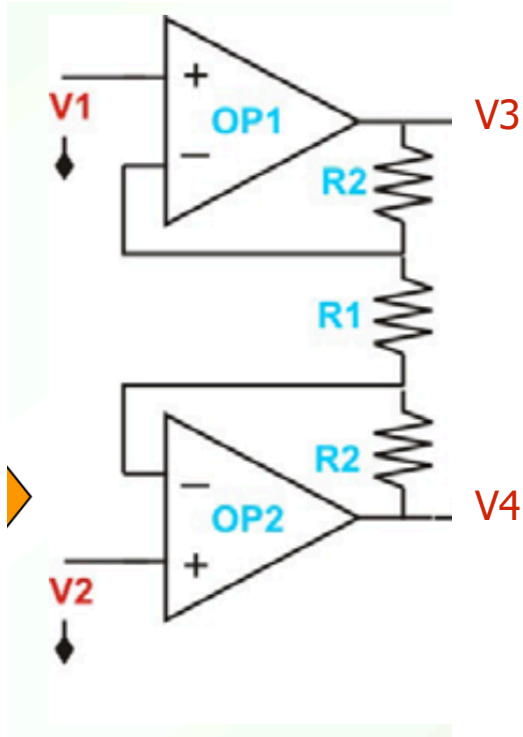

# Instrumentation Amplifier

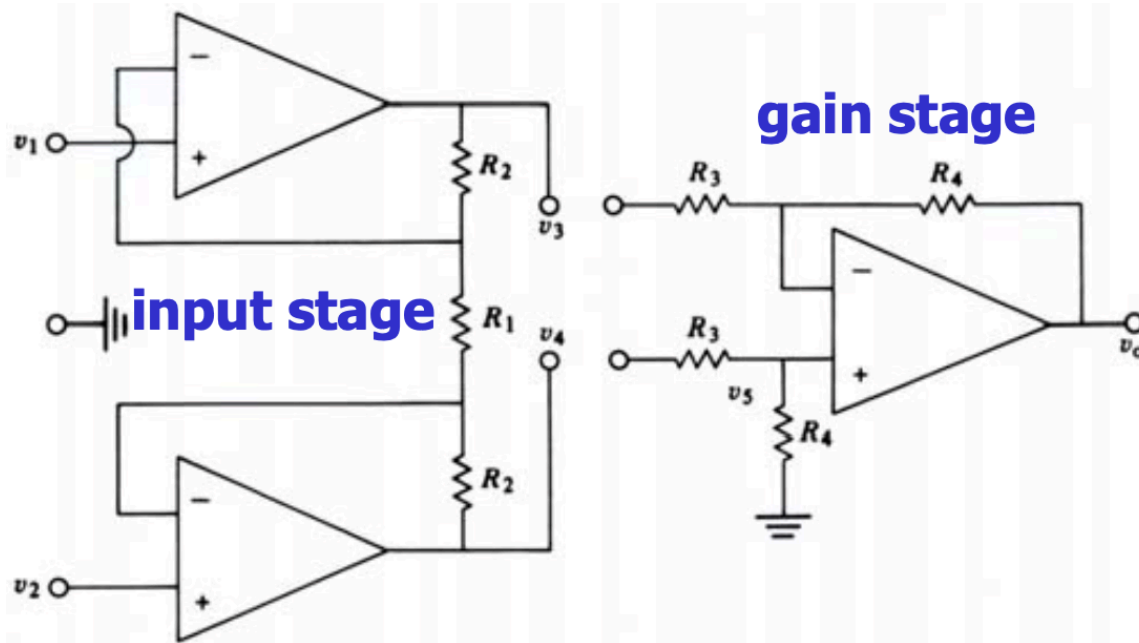

$$\frac{v_o}{v_i} = \left( \frac{2R_2 + R_1}{R_1} \right) \frac{R_4}{R_3}$$

## ❑ Overall amplifier

- Amplifies only the differential component
  - High common mode rejection ratio
- High input impedance suitable for biopotential electrodes




# Driven Right Leg System

## ❑ Motivation



- Reduce interference in amplifier
- Improve patient safety
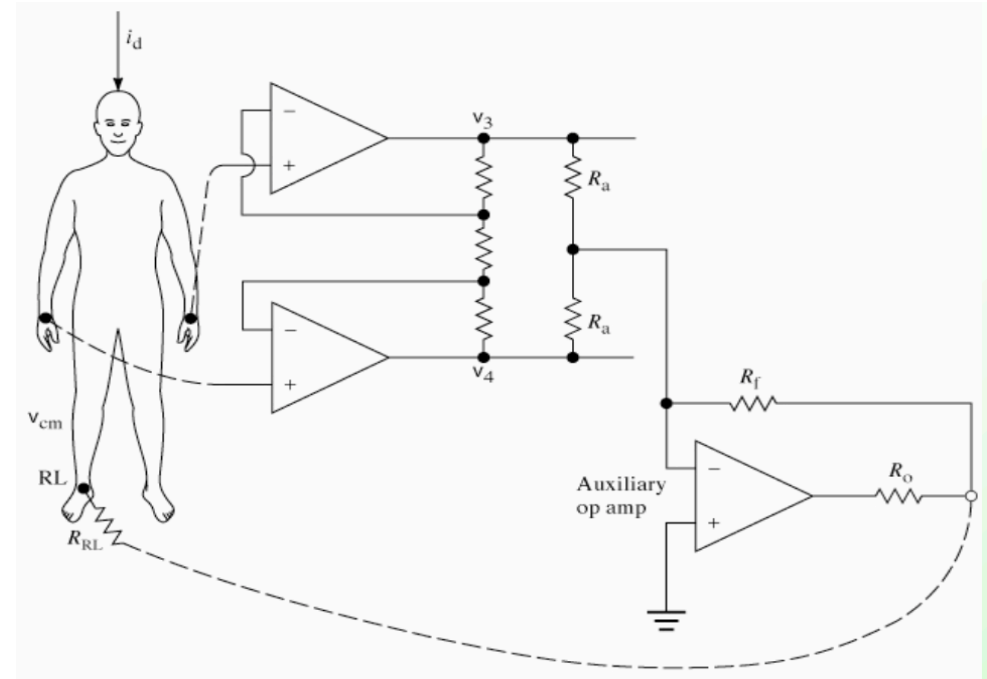
## ❑ Approach

- Patient right leg tied to output of an auxiliary amp rather than ground
- Common mode voltage on body sensed by averaging resistors,  $R_a$ 's & fed back to right leg
- Provides negative feedback to reduce common mode voltage
- If high voltage appears between patient and ground, auxiliary amp effectively un-grounds the patient to stop current flow




# Driven Right Leg System Example

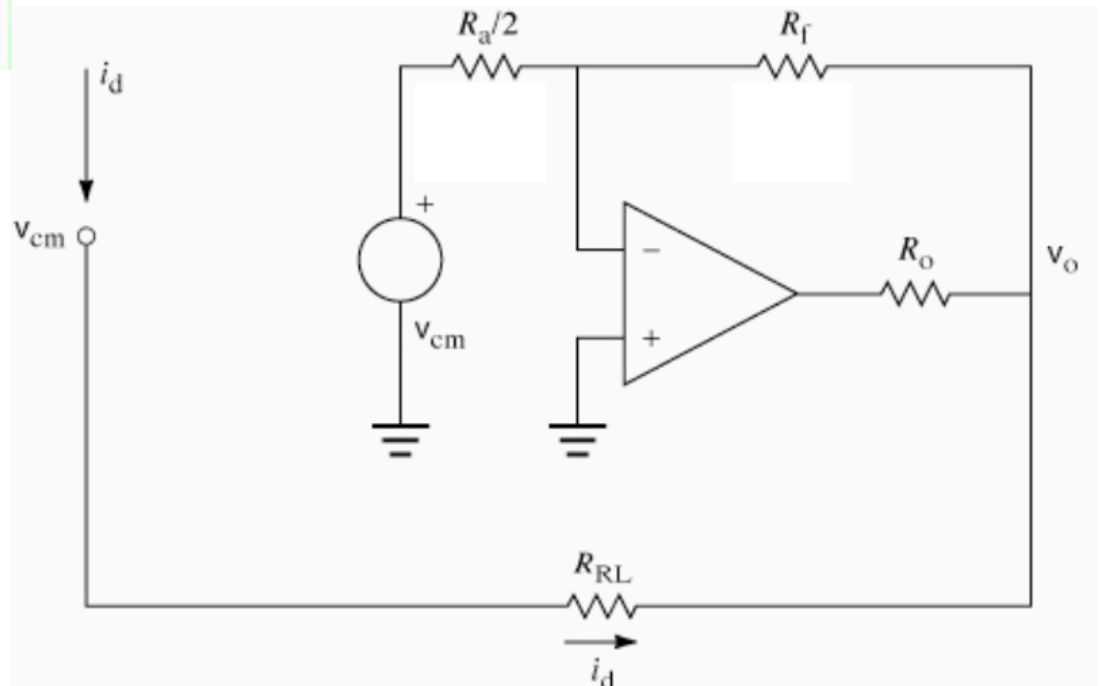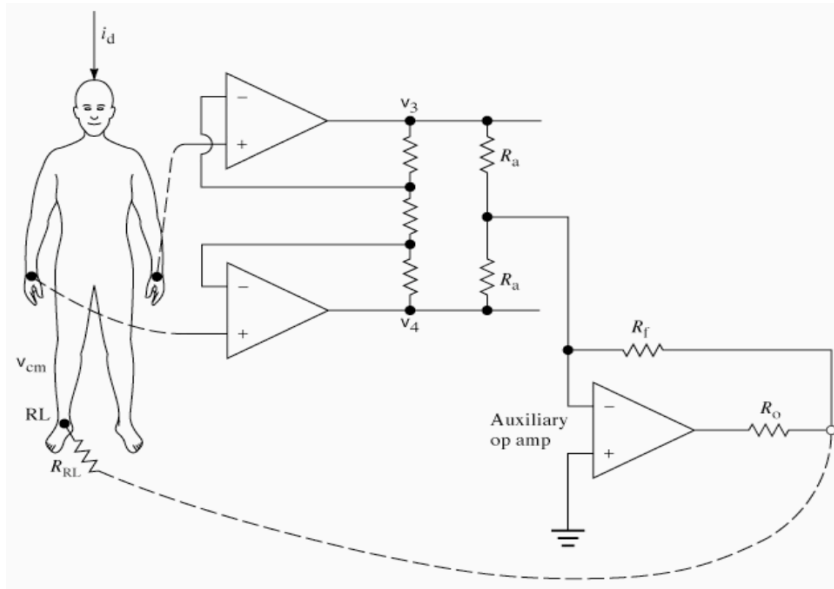

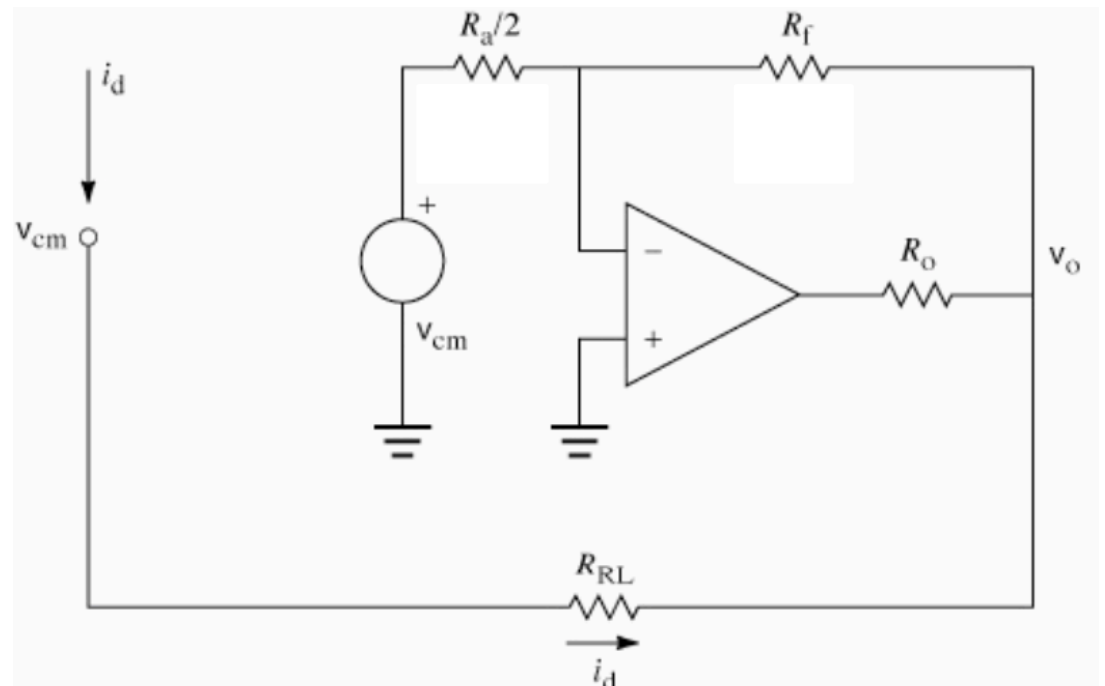
# Driven Right Leg System Example

- ❑ **Problem:** Determine the common-mode voltage  $v_{cm}$  on the patient in the driven-right-leg circuit when a displacement current  $i_d$  flows to the patient from the power lines. Choose appropriate values for the resistances in the circuit so that the common-mode voltage is minimal. With a worst-case electrode resistance of  $100k\Omega$ , what is the  $v_{cm}$  when  $i_d = 0.2\mu A$ ?





# Lab 3

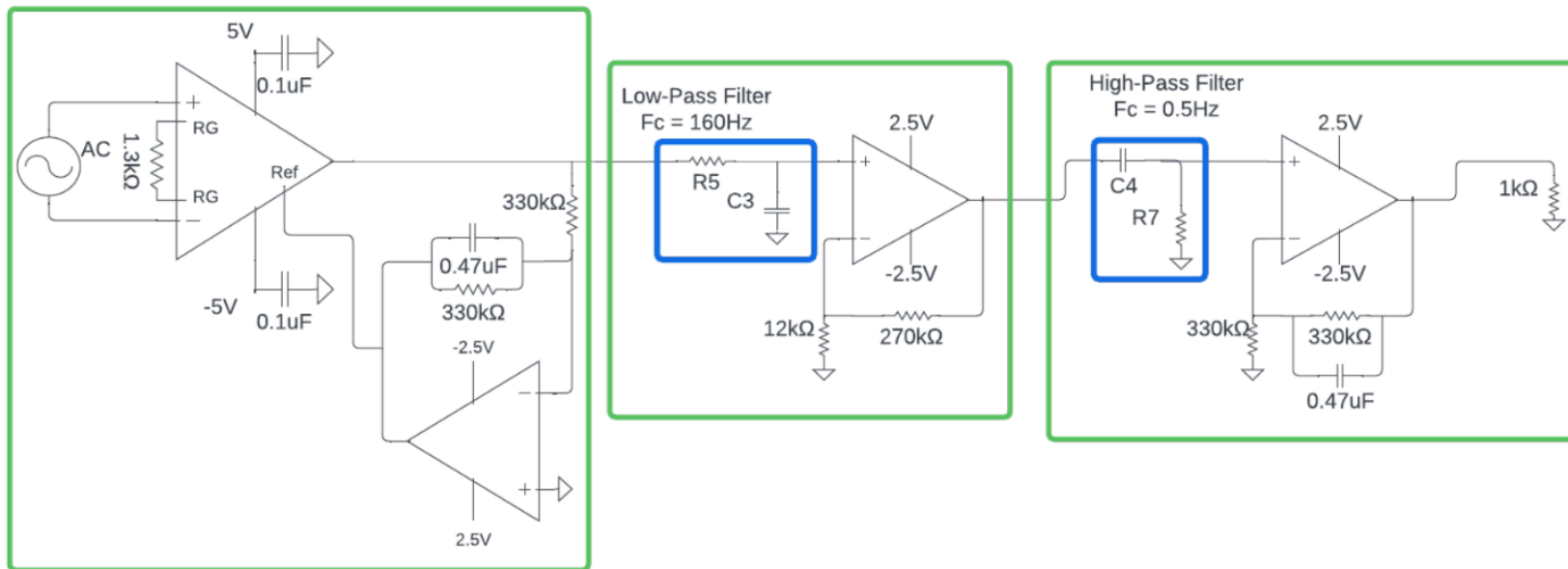



# Big Ideas

---

- ❑ Amplification
  - Use operational amplifier with differential signaling
- ❑ Instrumental Amplifier
  - Designed specifically for biopotential signals to compensate for non-idealities
  - Common-mode voltages responsible for much of the interference in biopotential amplifiers



# Admin

---

- ❑ Finish Lab 3 and submit deliverables in Canvas by next lab day at midnight
  - New handout with SPICE tips