

ESE 3400: Medical Devices Lab

Lec 5: September 20, 2023
Signal Conditioning/Interface Circuits




Lecture Outline

- ❑ Lab 2 Discussion
- ❑ Amplification
 - Opamp
 - Practical Opamp Circuits
- ❑ Biopotential Amplifier
- ❑ Instrumentation Amplifier
- ❑ Driven Right Leg System
- ❑ Lab 3 Setup
 - LT Spice
 - Amplification and filter schematic



Frequency response of a low pass filter

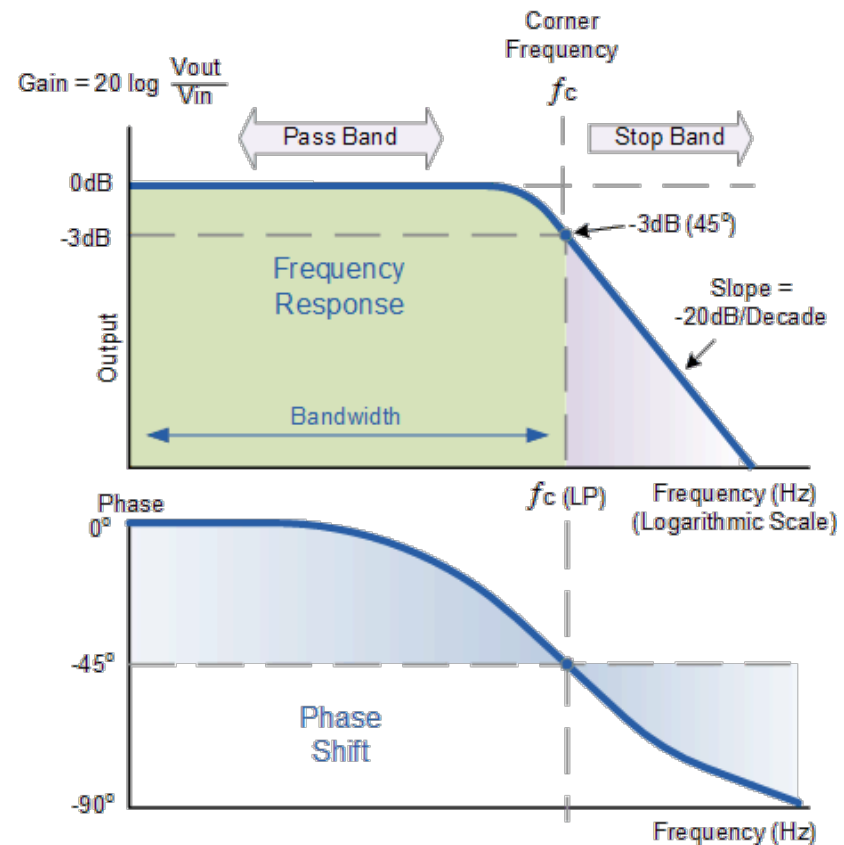- ❑ Gain
- ❑ Bandwidth
- ❑ Pass band vs stop band
- ❑ Corner frequency
- ❑ 3dB point
- ❑ Roll off




https://www.electronicstutorials.ws/filter/filter_2.html

Passive LPF vs. Active LPF w/ Gain

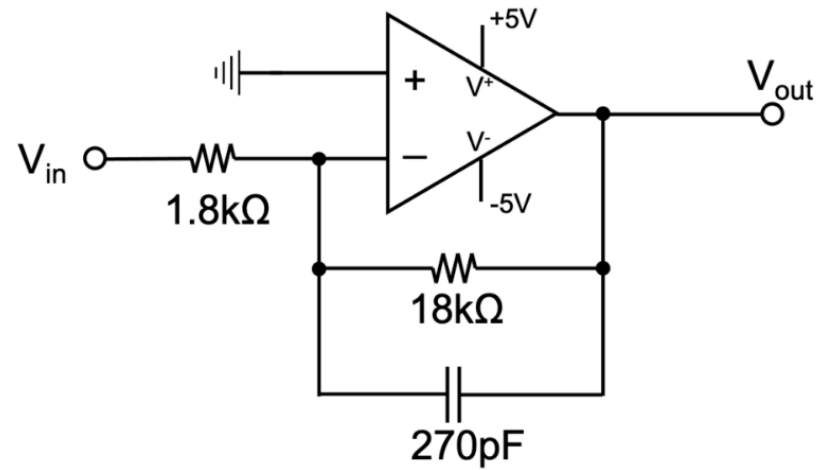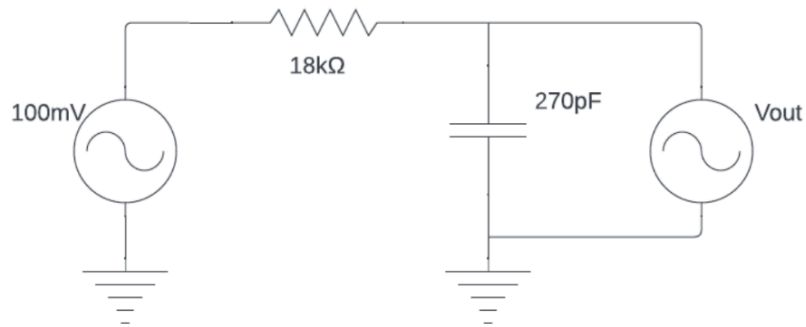


Notch Filter 3dB Cutoffs

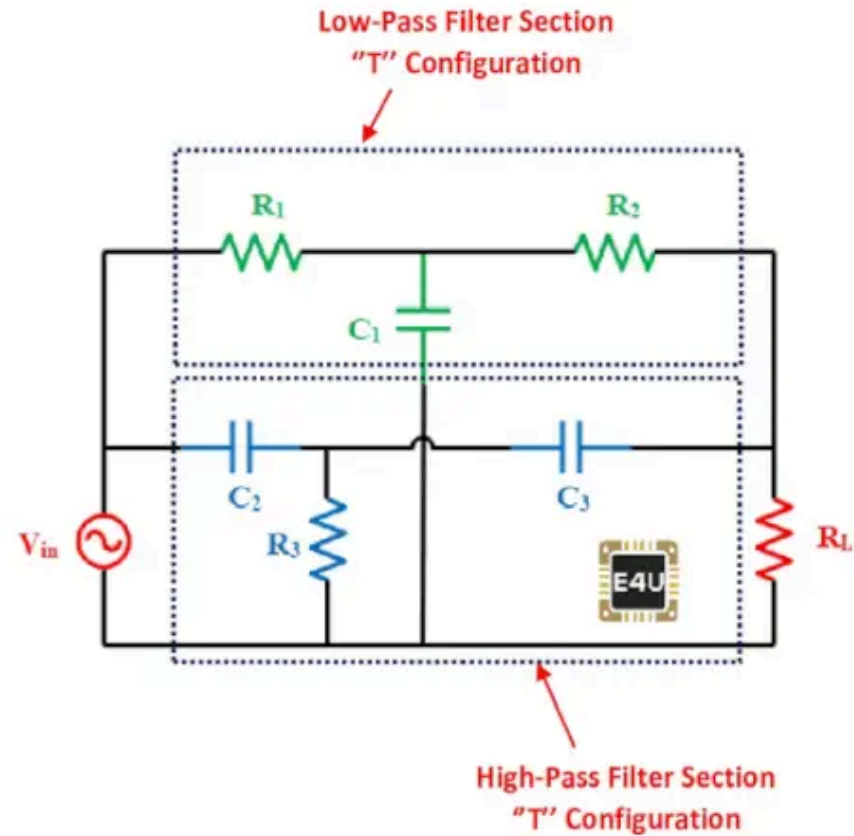

Amplification

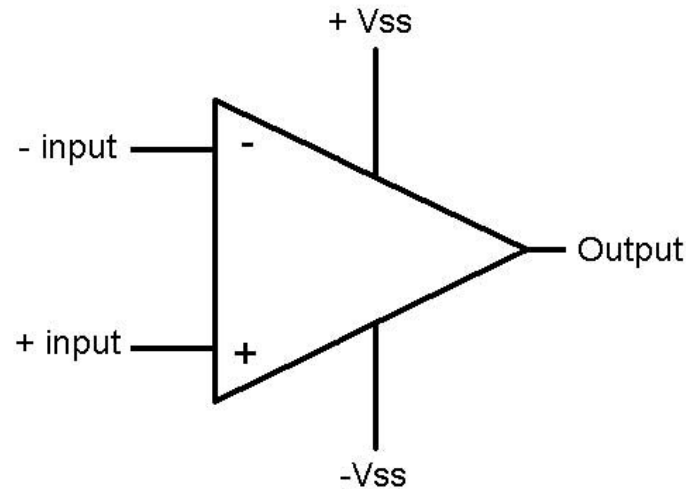
- ❑ Sensor outputs may (read: almost always) need amplification for any sort of acquisition and data analysis
- ❑ Use operational amplifier to do this
 - Amplifies differential input: $\text{Out} = A(V_{\text{in}+} - V_{\text{in}-})$, where A is large



Opamp

Ideal Opamp

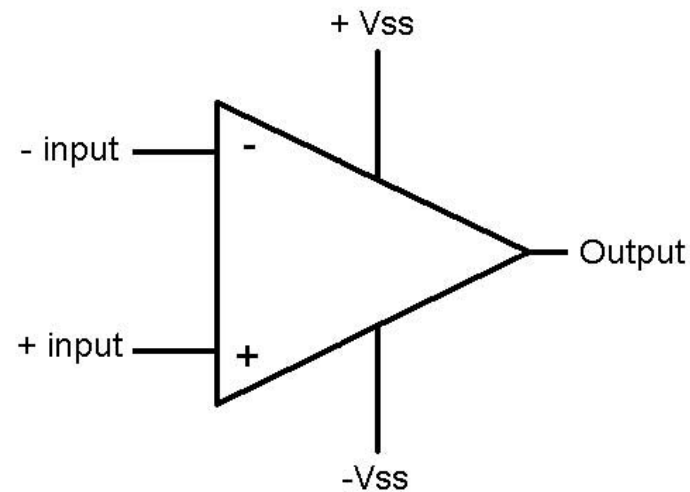- The ideal opamp characterized by seven properties
 - Knowledge of these properties is sufficient to design and analyze a large number of useful circuits






Basic Opamp Properties

- ❑ Property No.1: Infinite Open-Loop Gain
 - Open-Loop Gain A_{VOL} is the gain of the opamp without positive or negative feedback
 - In the ideal opamp A_{VOL} is infinite
 - Typical values range from 20,000 to 200,000 in real devices
- ❑ Property No.2: Infinite Input Impedance
 - Input impedance is the ratio of input voltage to input current, $Z_{in} = V_{in} / I_{in}$
 - When Z_{in} is infinite, the input current $I_{in} = 0$
 - High-grade opamps can have input impedance in the T Ω range
 - Some low-grade opamps, on the other hand, can have mA input currents

Basic Opamp Properties

□ Property No. 3: Zero Output Impedance

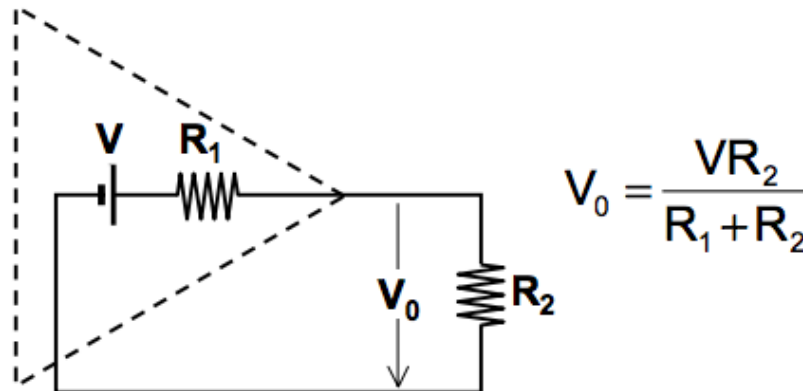- The ideal opamp acts as a perfect internal voltage source with no internal resistance
 - This internal resistance is in series with the load, reducing the output voltage available to the load
 - Real opamps have output-impedance in the 10-20 Ω range
- Example






Basic Opamp Properties

- Property No. 4: Zero Noise Contribution
 - In the ideal opamp, zero noise voltage is produced internally
 - That is, any noise at the output must have been at the input as well
 - Practical opamp are affected by several noise sources, such as resistive and semiconductor noise
 - These effects can have considerable effects in low signal-level applications

Basic Opamp Properties

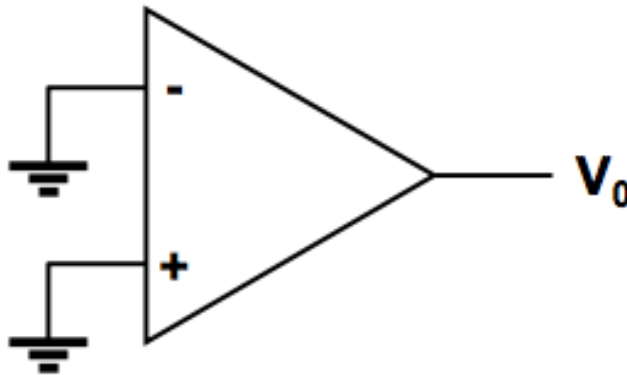- Property No. 5: Zero output Offset
 - The output offset is the output voltage of an amplifier when both inputs are grounded
 - The ideal opamp has zero output offset, but real opamps have some amount of output offset voltage






Basic Opamp Properties

- ❑ Property No. 6: Infinite Bandwidth
 - The ideal opamp will amplify all signals from DC to the highest AC frequencies
 - In real opamps, the bandwidth is rather limited
 - This limitation is specified by the Gain-Bandwidth product
 - $GBW = f_{3dB} * Gain_{3dB}$
 - Some opamps, such as the 741 family, have very limited bandwidth of up to a few KHz
- ❑ Property No. 7: Differential Inputs Stick Together*
 - In the ideal opamp, a voltage applied to one input also appears at the other input
 - *when connected in feedback

Ohm's Law and Kirchoff's Laws

□ Ohm's Law

- $V = IR$

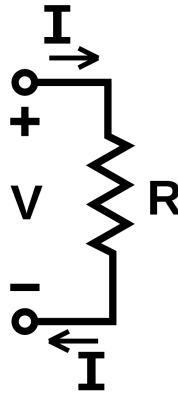

□ KCL – Kirchoff's Current Law


- The sum of the currents into a node = 0

□ KVL – Kirchoff's Voltage Law

- The sum of the voltage differences around any closed loop in a circuit must be zero


KCL

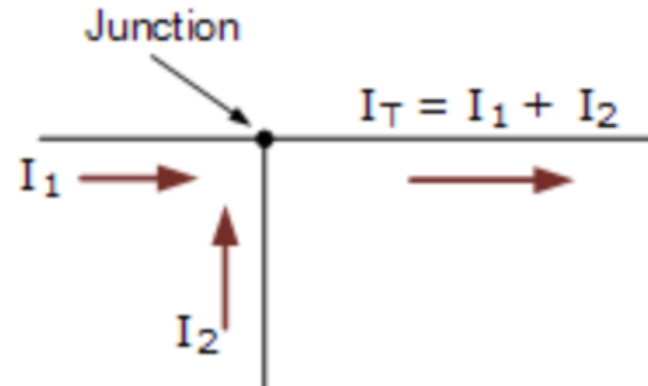- KCL – Kirchoff's Current Law
 - The sum of the currents into a node = 0




KVL

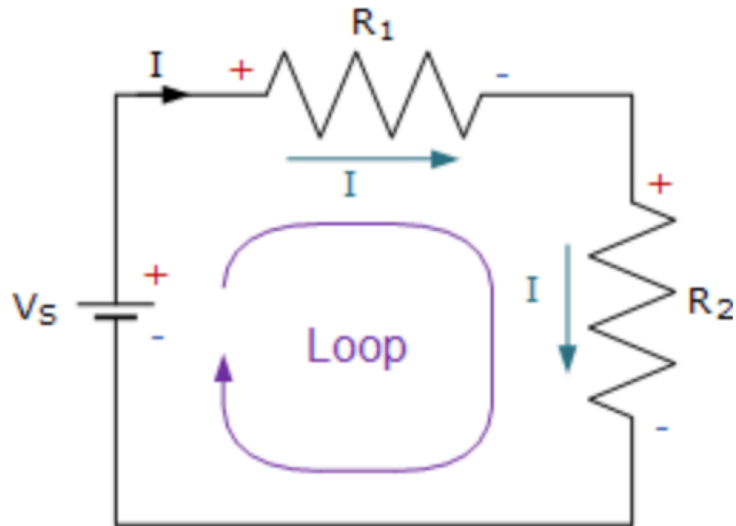- KVL – Kirchoff's Voltage Law
 - The sum of the voltage differences around any closed loop in a circuit must be zero




Opamp Practical Circuits

□ A)


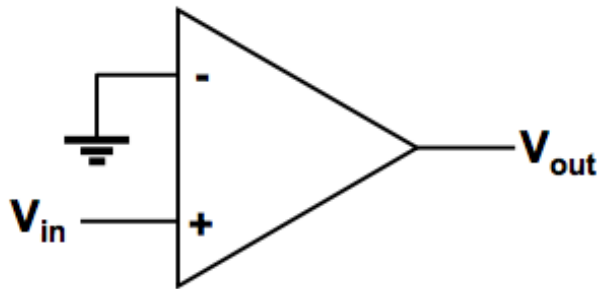


□ B)

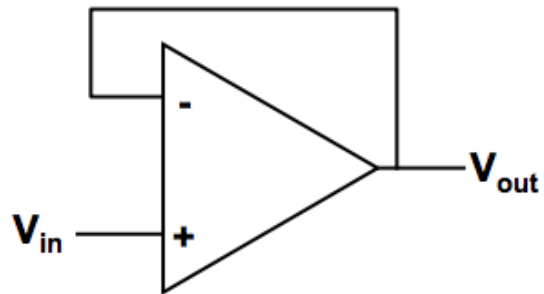


Opamp Practical Circuits

□ A) Voltage comparator

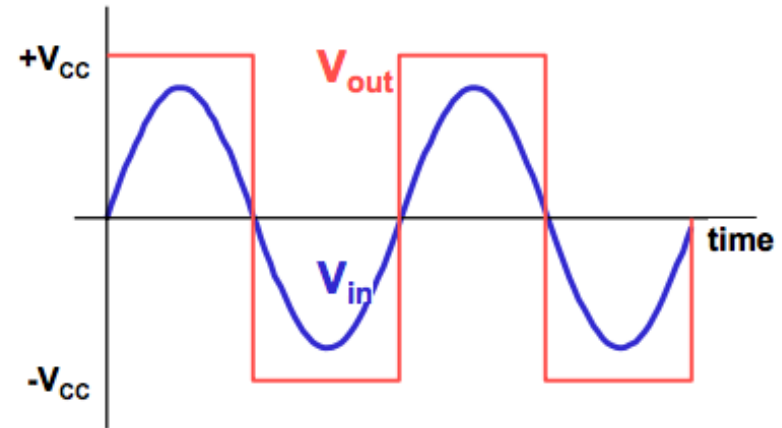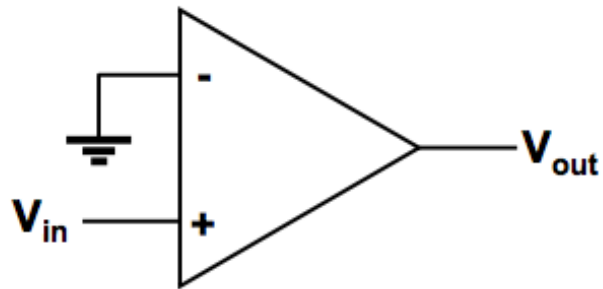


□ B) Voltage follower (Buffer)

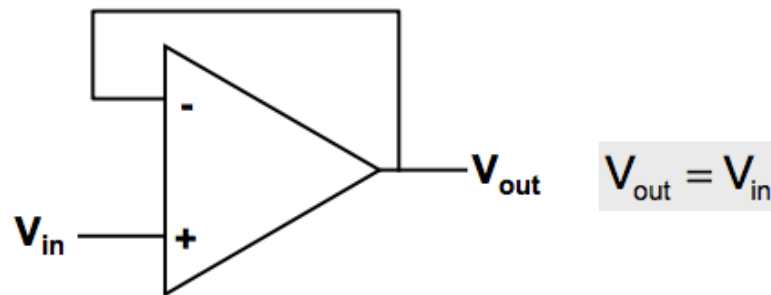


$$V_{out} = V_{in}$$

Opamp Practical Circuits

□ C)

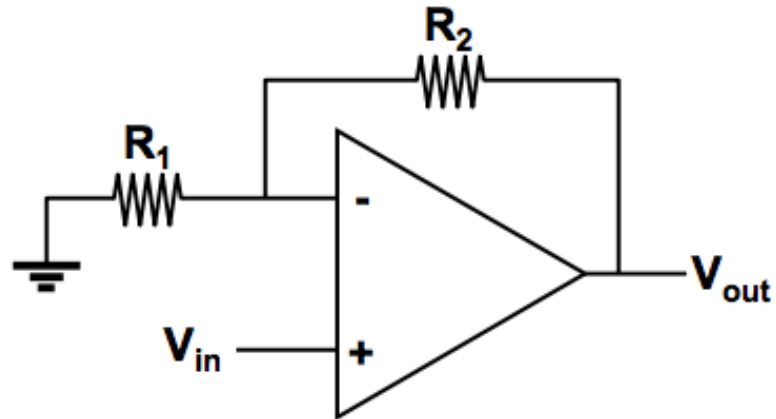


□ D)

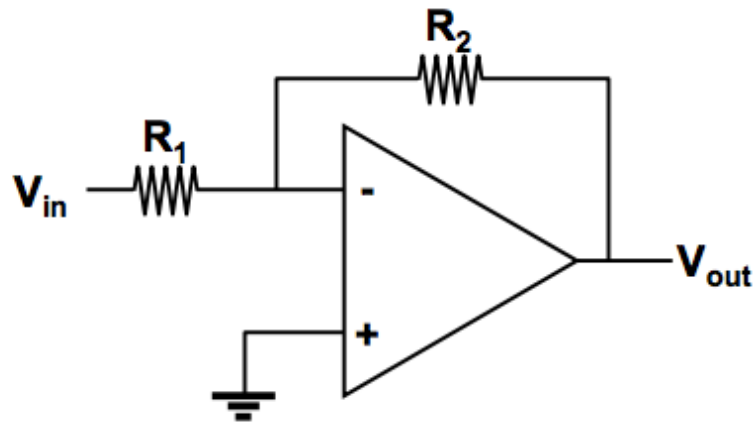


Opamp Practical Circuits

- C) Non-inverting amplifier

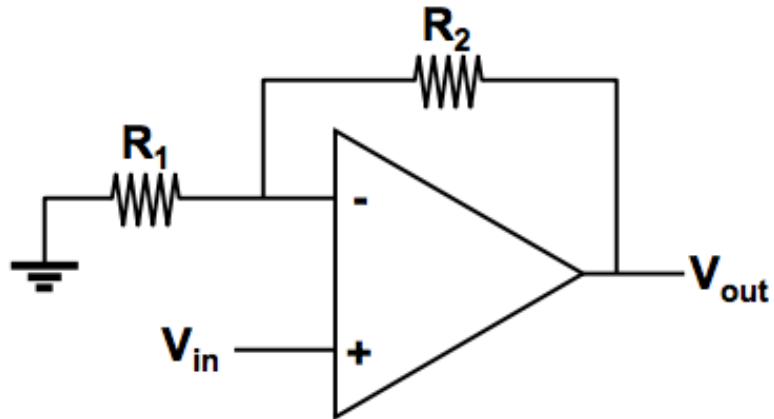

$$V_{\text{out}} = \left(1 + \frac{R_2}{R_1}\right) V_{\text{in}}$$


- D) Inverting amplifier

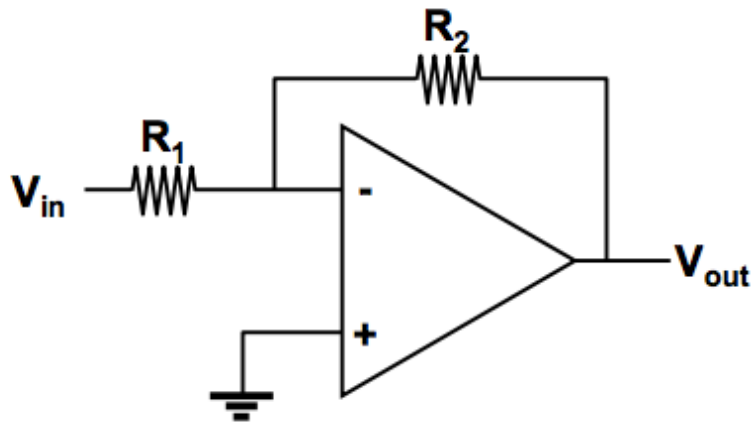


$$V_{\text{out}} = -\frac{R_2}{R_1} V_{\text{in}}$$

Common Mode and Differential Mode

SINGLE-ENDED

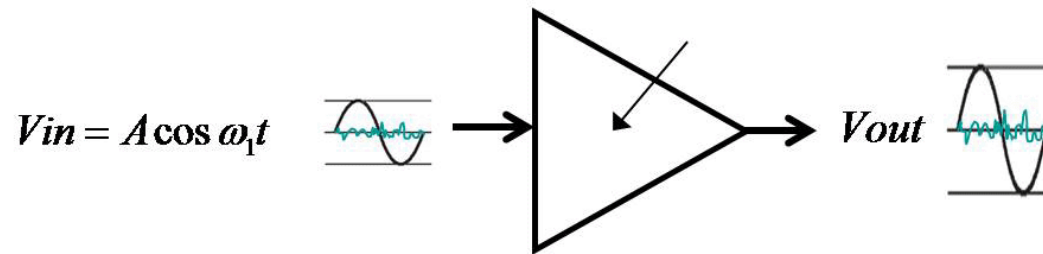


DIFFERENTIAL

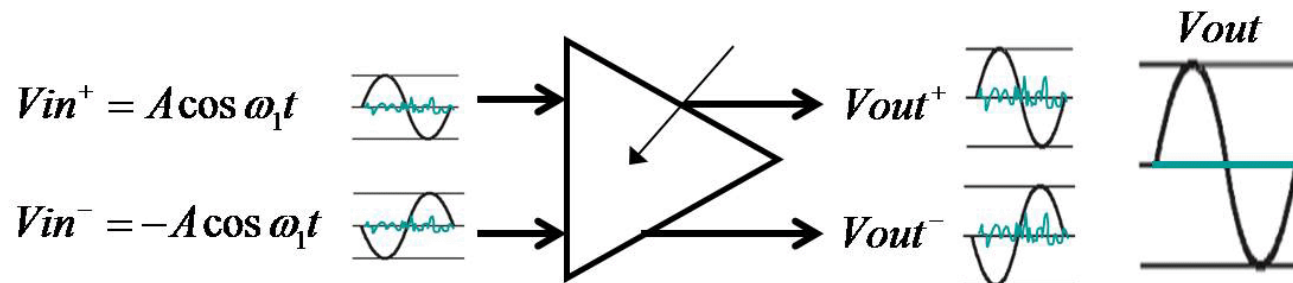

Biopotential Amplifier

- Differential amplifier

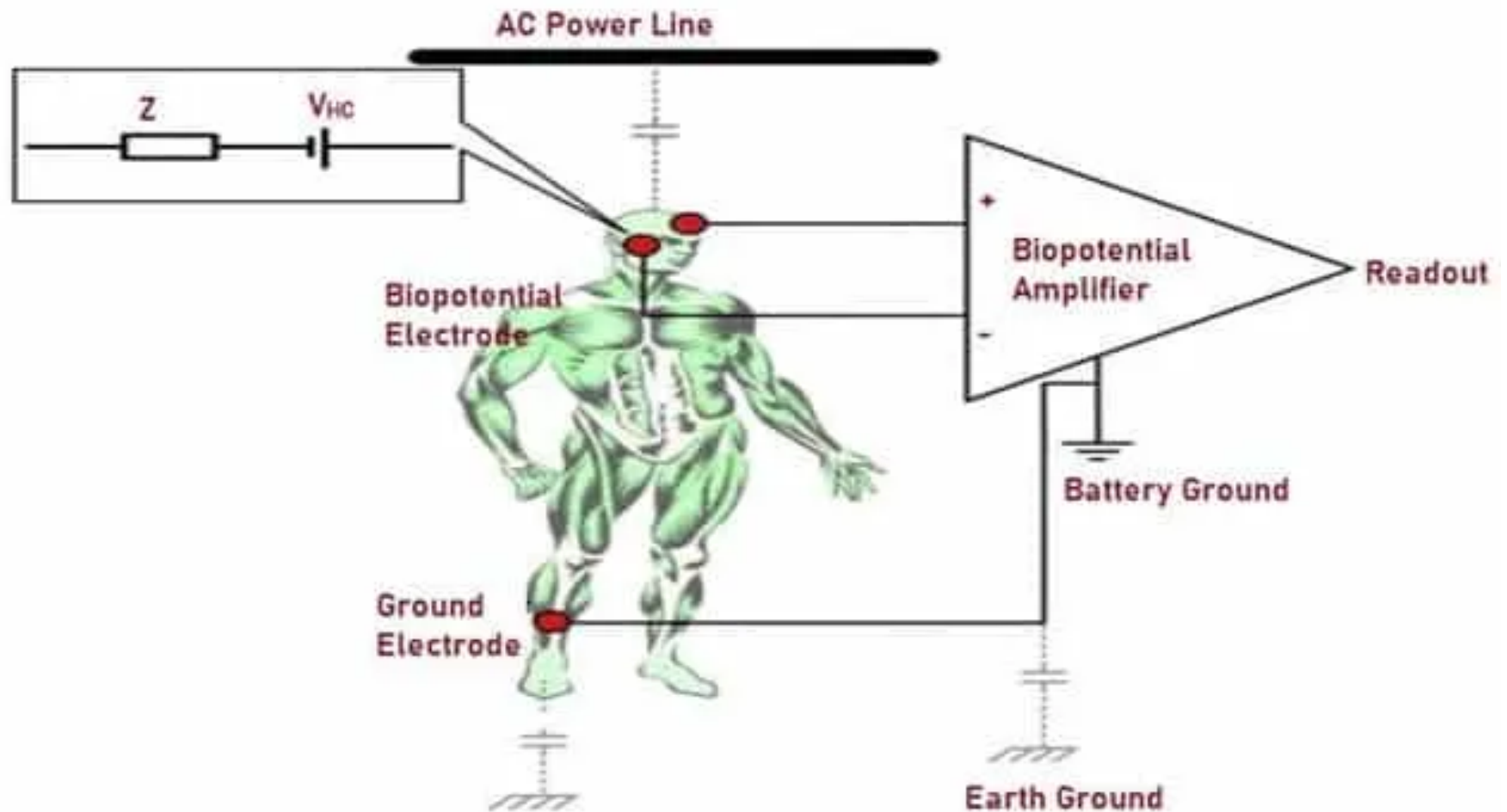

Biopotential Amplifier

□ Differential amplifier

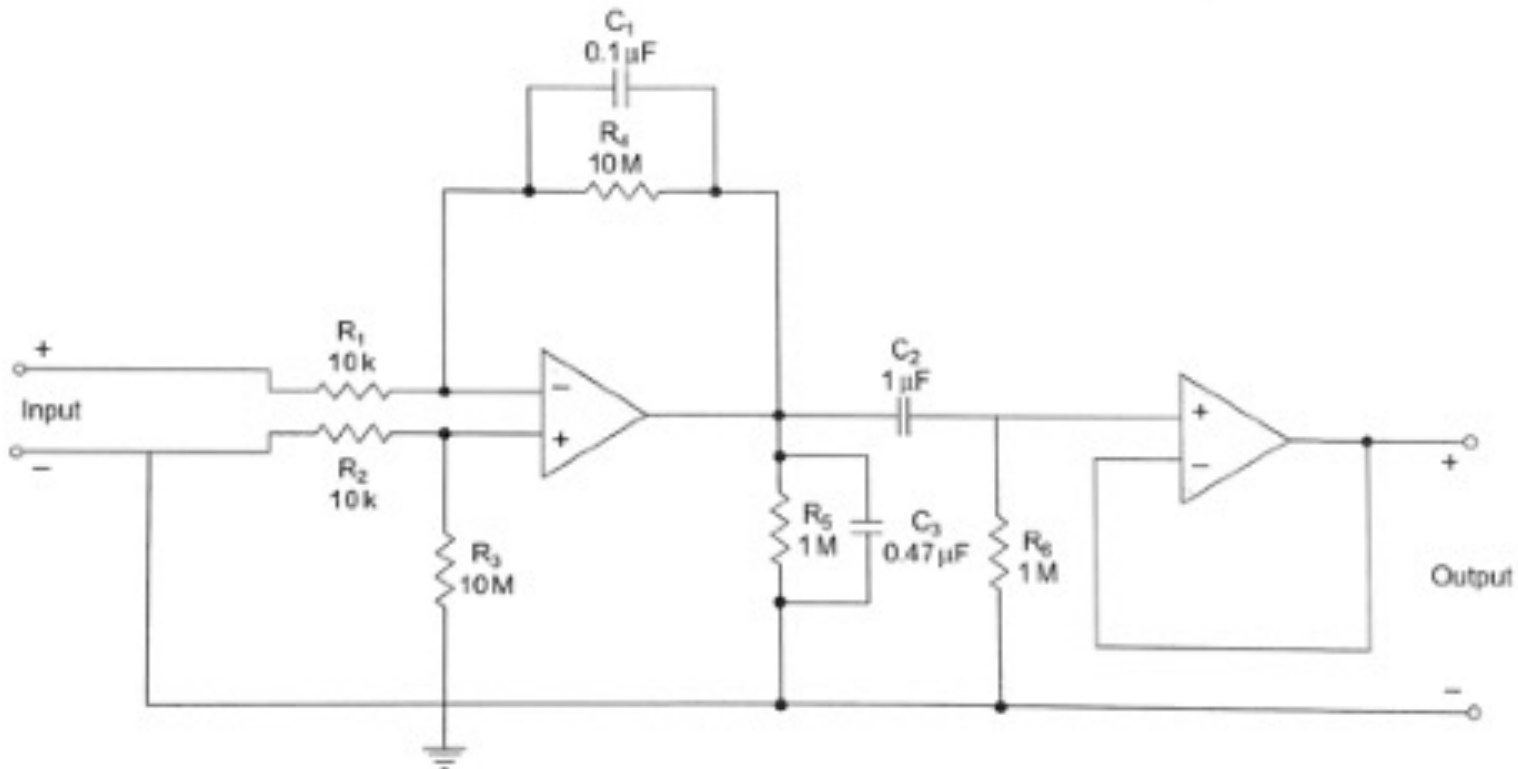


FIGURE 1.20

Differential biopotential amplifier.

Adapted from Prutchi and Norris (2005).

Biopotential Amplifier

□ Differential amplifier

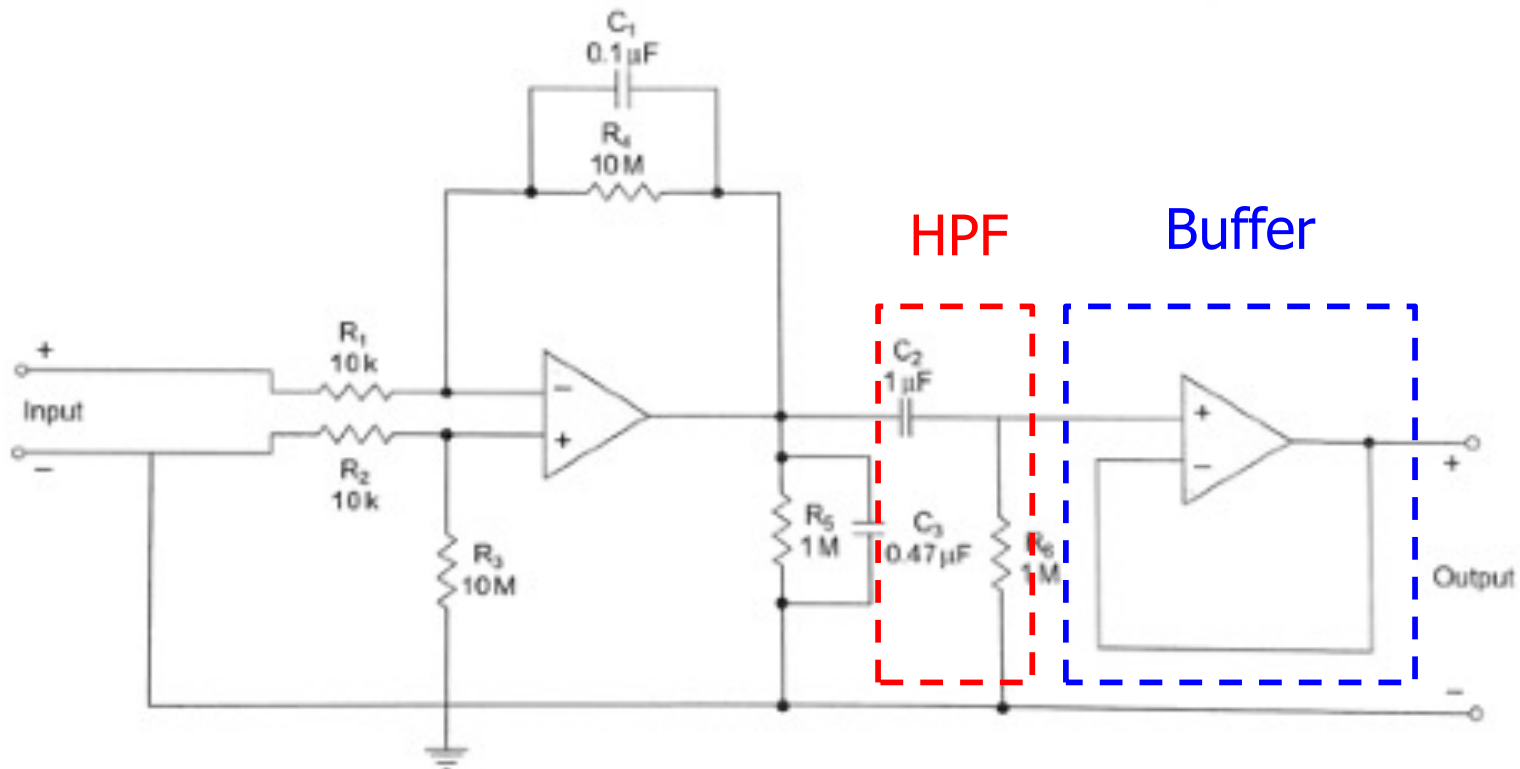


FIGURE 1.20

Differential biopotential amplifier.

Adapted from Prutchi and Norris (2005).

Biopotential Amplifier

□ Differential amplifier

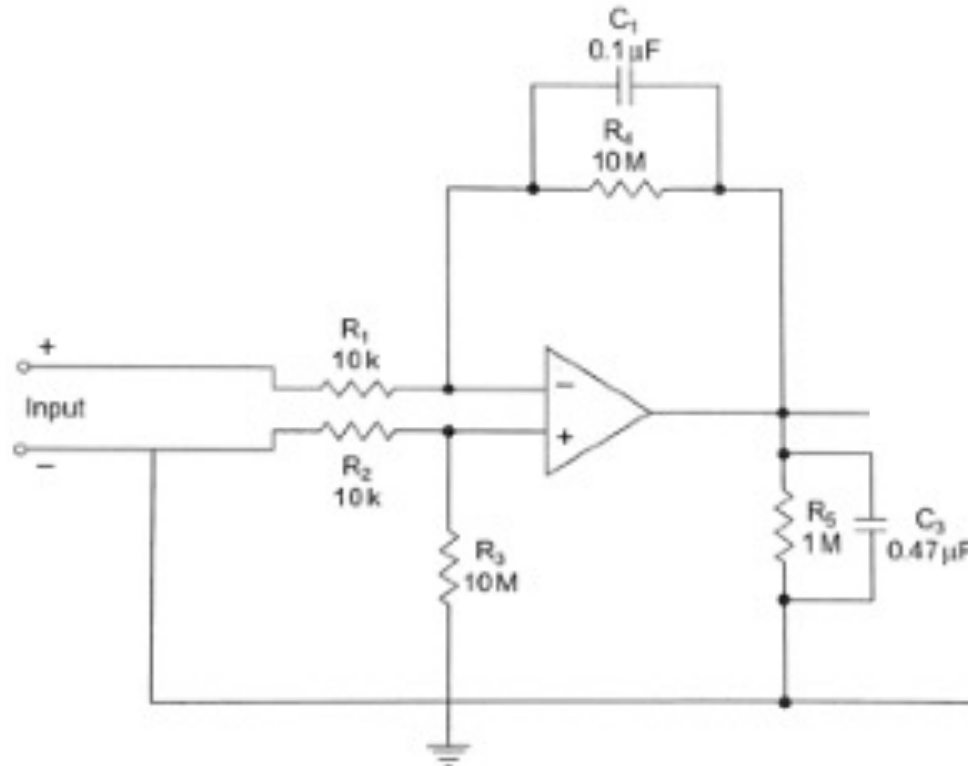


FIGURE 1.20

Differential biopotential amplifier.

At

Biopotential Amplifier

□ Differential amplifier

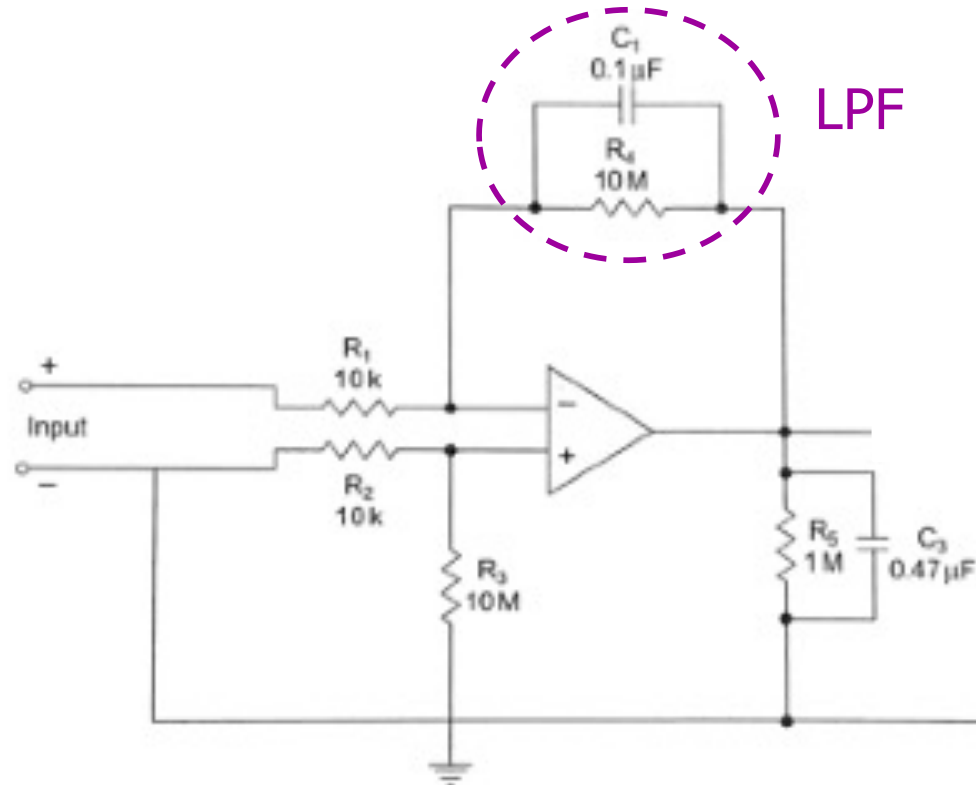


FIGURE 1.20

Differential biopotential amplifier.

At

Biopotential Amplifier

□ Differential amplifier

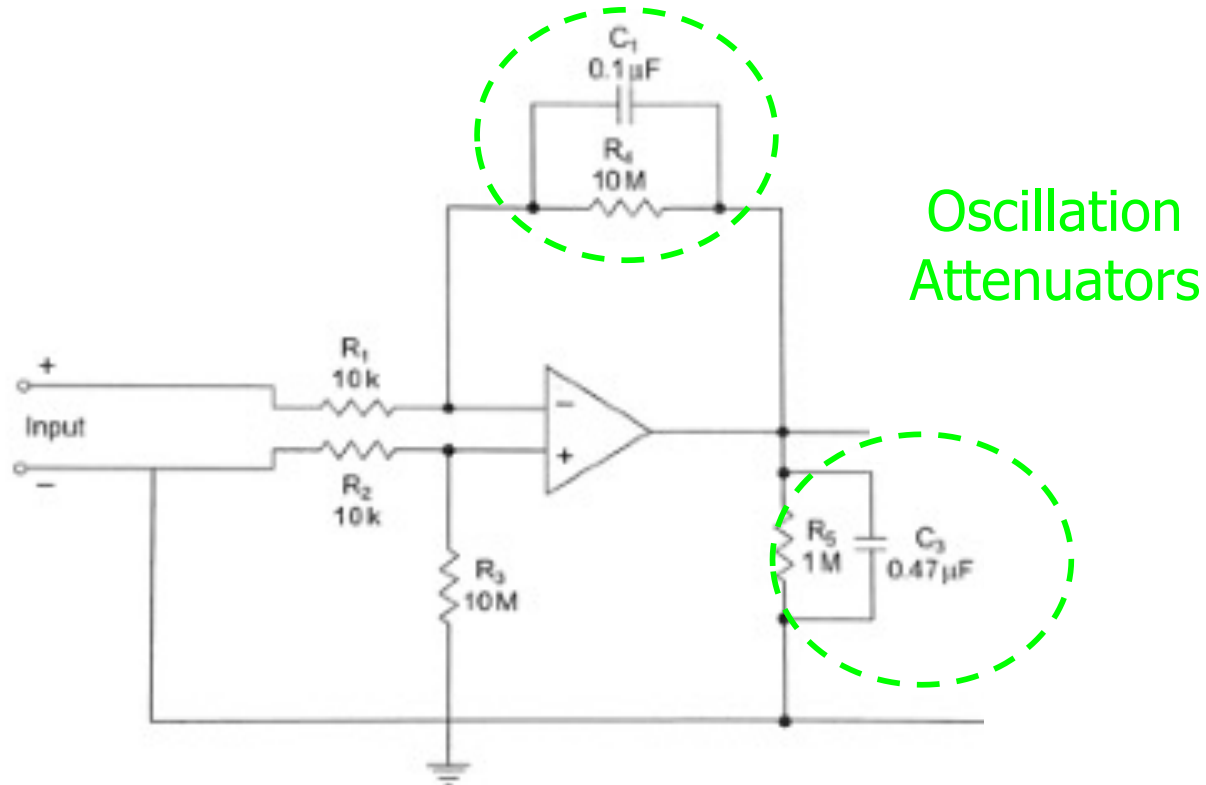


FIGURE 1.20

Differential biopotential amplifier.

At



Biopotential Amplifier

- ❑ Basic function to increase the amplitude of a weak electric signal of biological origin typically process voltages


- ❑ Typical bio-amp requirements
 - High input impedance greater than $10\text{ M}\Omega$
 - Safety: protect the organism being studied
 - Careful design to prevent macro and microshocks
 - Isolation and protection circuitry to limit the current through the electrode to safe level



Biopotential Amplifier


- Typical bio-amp requirements (con't)
 - Output impedance of the amplifier
 - should be low to drive any external load with minimal distortion
 - Gain greater than 1000
 - Biopotentials are typically less than a millivolt
 - Most are differential
 - High common mode rejection ratio
 - Biopotentials ride on a large offset signal
 - Rapid calibration of the amplifier in laboratory conditions
 - Adjustable gains
 - Often the change in scale is automatic

Voltage and Frequency Range

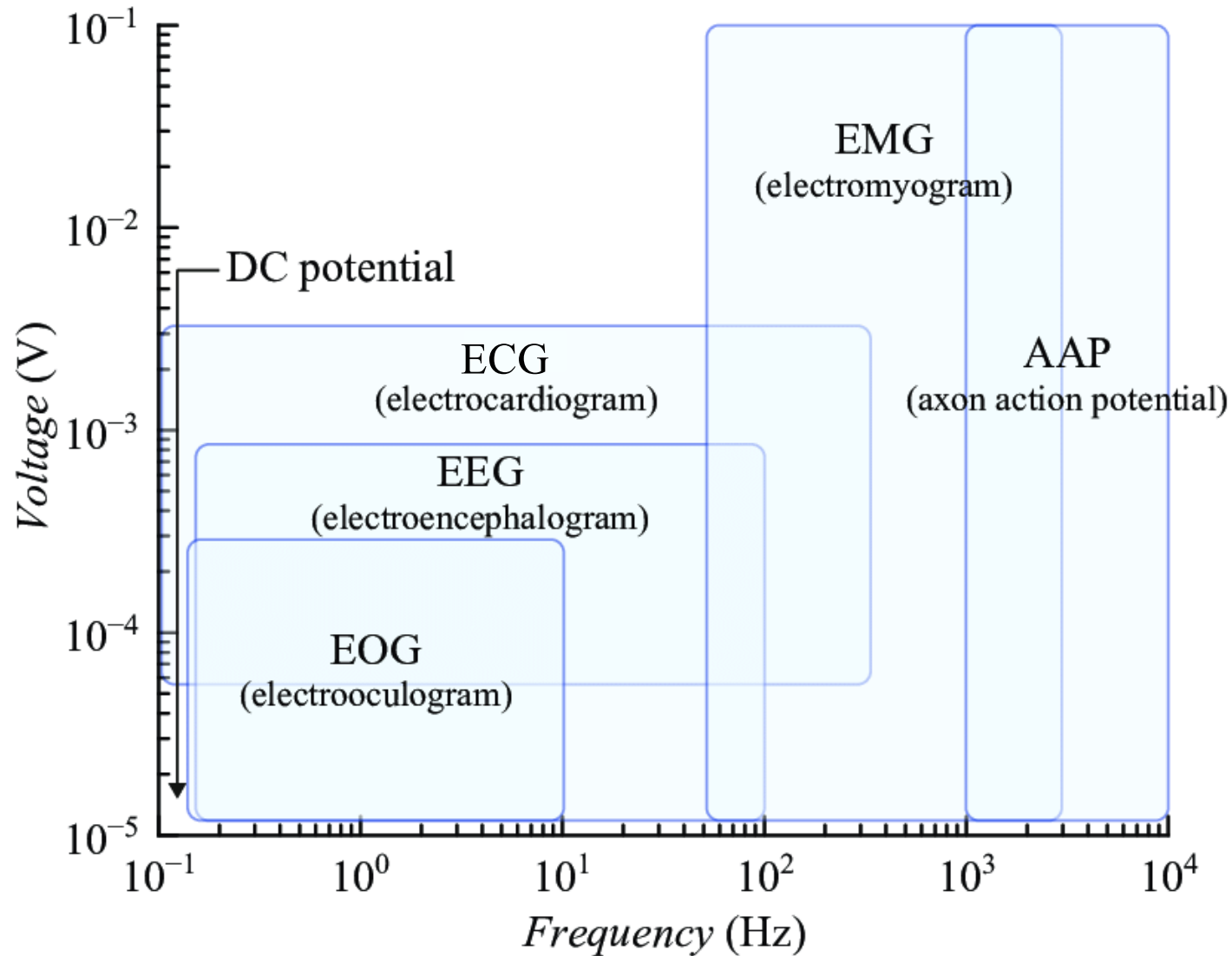


ECG Amplifiers

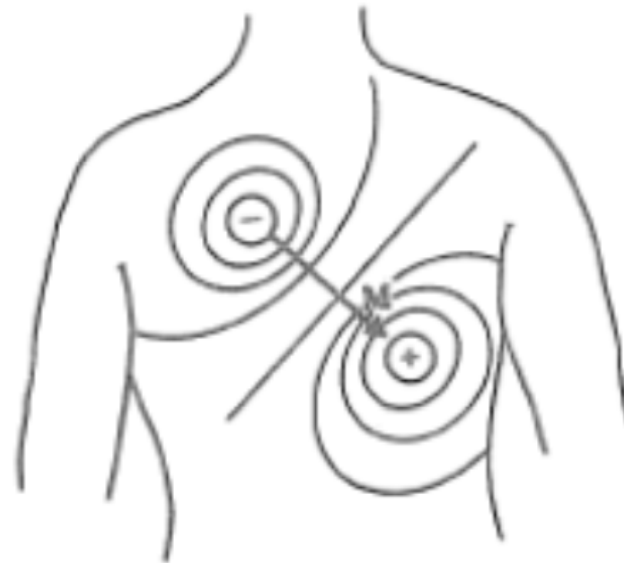- ❑ Beating heart generates electric signal
 - monitored to understand heart functions
- ❑ Measurements are functions of
 - location at which the signal is detected
 - time-dependence of the signal amplitude
- ❑ Different pairs of electrodes at different locations yield different measurements
 - hence placement is standardized




ECG Leads

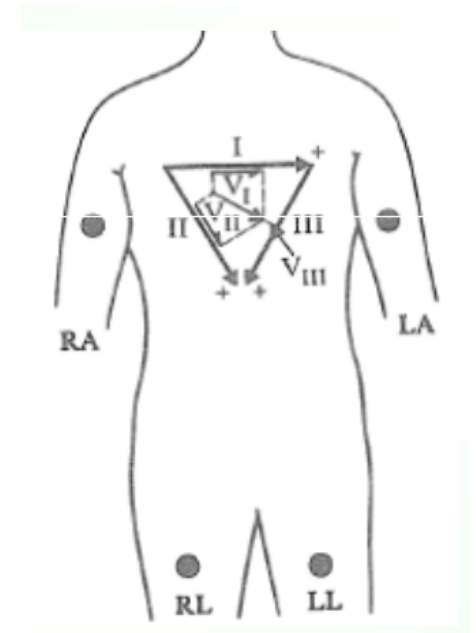- ❑ In clinical electrocardiography
 - more than one lead must be recorded to describe the heart's electric activity fully
 - several leads are taken in the frontal plane and the transverse plane
 - frontal plane: parallel to the back when lying
 - transverse plane: parallel to the ground when standing
- ❑ Frontal plane lead placement called Eindhoven's triangle



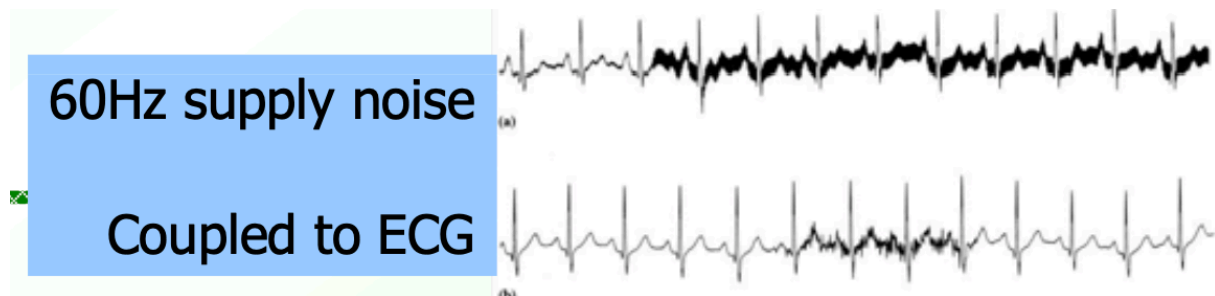Problems in ECG Measurement

- ❑ Frequency distortion
 - If filter specification does not match the frequency content of biopotential then the results is high and low frequency distortion
- ❑ Saturation of cutoff distortion
 - High electrode offset voltage can drive the amplifier to saturation causing peaks of waveform (QRS) to be cut off
- ❑ Ground loops
 - Can cause small currents to flow through patient's body
- ❑ Electric/magnetic field coupling
 - Open lead wires and long loops pick up EMI
- ❑ Interference from power lines (60Hz noise)







Interference Reduction Techniques

- ❑ Common-mode voltages can be responsible for much of the interference in biopotential amplifiers.
 - Solution 1:
 - Amplifier with a very high common-mode rejection
 - Solution 2:
 - Eliminate the source of interference
- ❑ Ways to eliminate interference
 - Use shielding techniques
 - Electrostatic shielding: Place a grounded conducting plane between the source of the interference and measurement system
 - Very important for EEG measurement
 - Magnetic shield: Use high permeability materials (sheet steel)
 - Use twisted cables to reduce loops


Illustration of Common Mode Influence

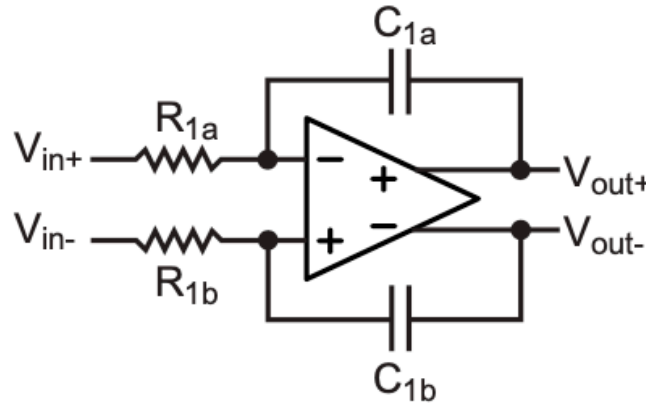


Common-Mode Too High

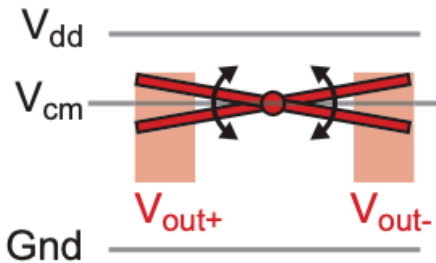

Common-Mode Too Low

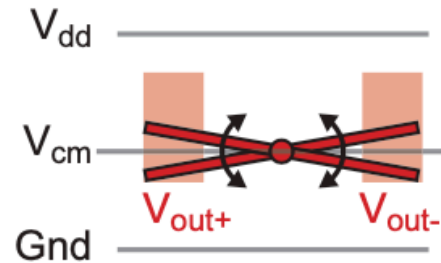

Common-Mode Just Right

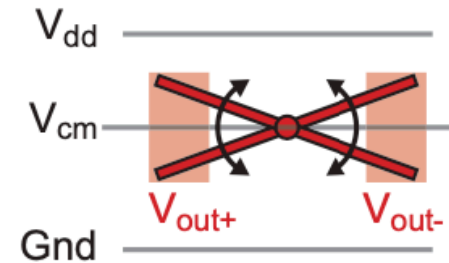

Biopotential Amplifier

- Differential amplifier

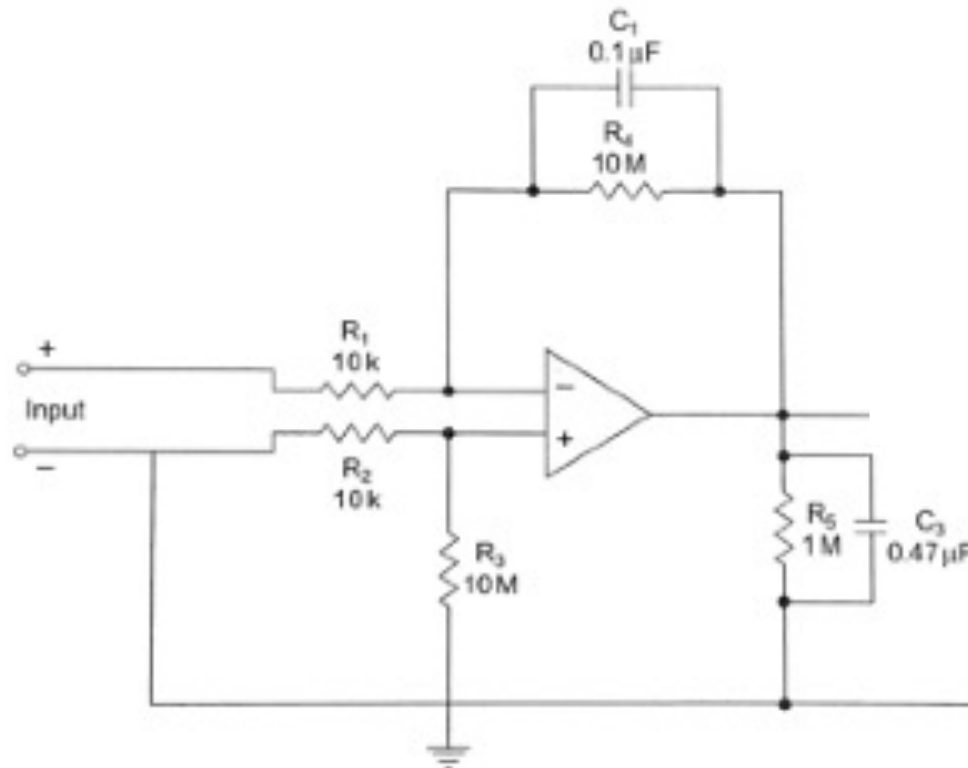



FIGURE 1.20

Differential biopotential amplifier.

At


Differential Amplifier

- One-amp differential amplifier

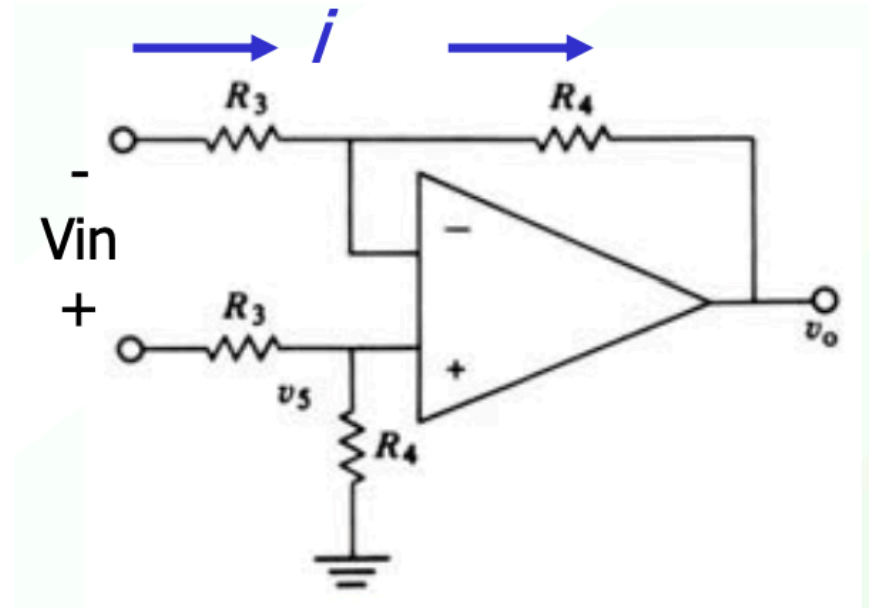


Differential Amplifier

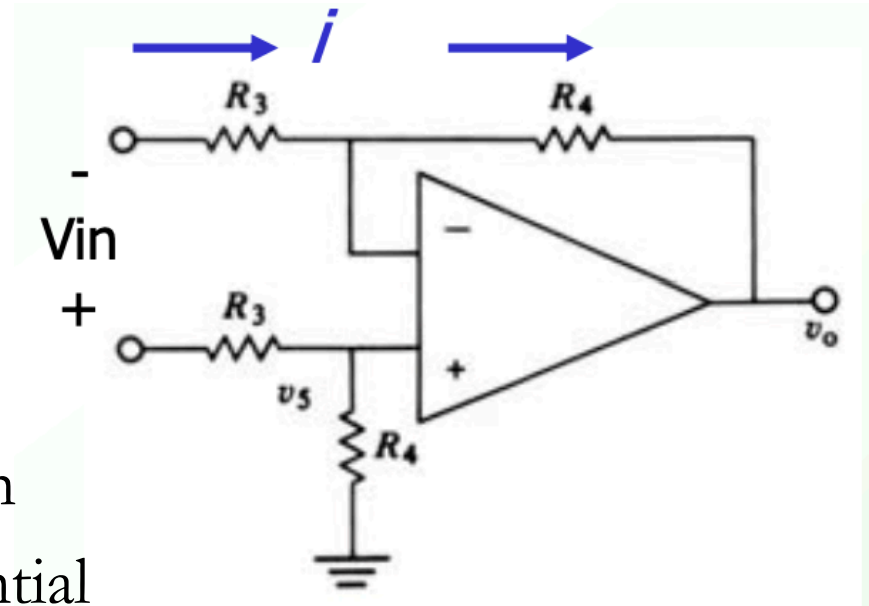- ❑ One-amp differential amplifier
- ❑ Differential gain:
 - $\frac{v_o}{v_i} = \frac{R_4}{R_3}$, where $R_4 \gg R_3$
- ❑ Characteristics
 - Good common mode rejection
 - Input resistance of the differential amplifier is lower than ideal op-amp
 - Not good for many biomedical applications




Differential Amplifier

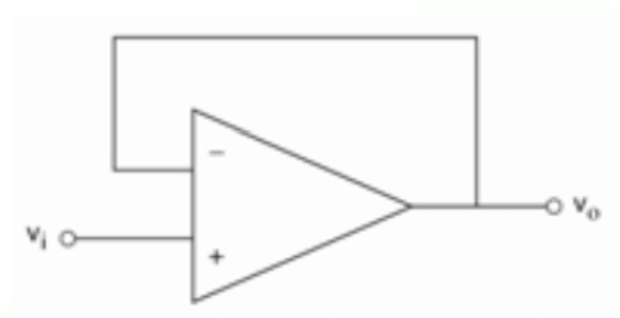- How can we fix the low input impedance?
- Option 1: Add voltage follower at each input
 - Pros and cons?




Differential Amplifier

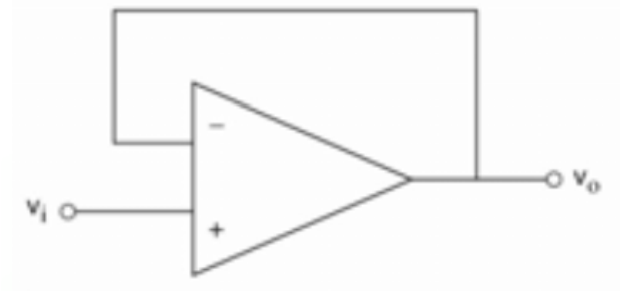- ❑ How can we fix the low input impedance?
- ❑ Option 1: Add voltage follower at each input
 - Pros and cons?




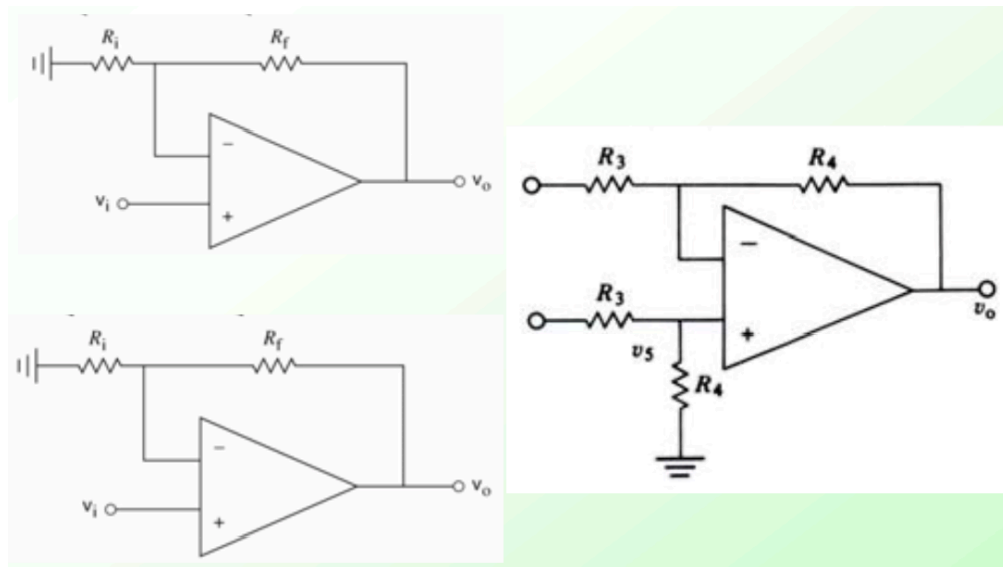- ❑ Option 2: Add non-inverting amplifier at each input
 - Pros and cons?




Instrumentation Amplifier

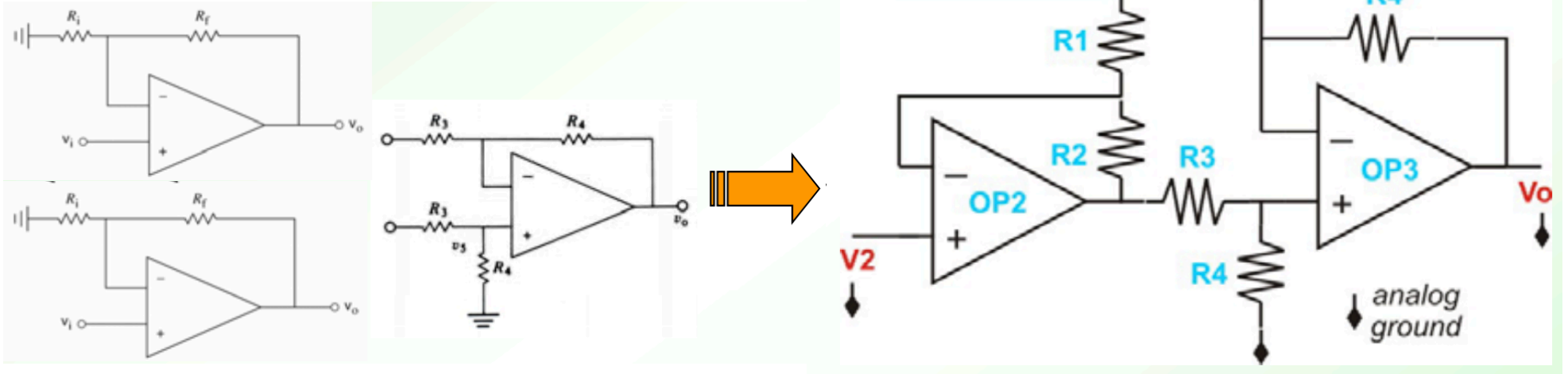- Better option
 - Share R in input amps and eliminate ground connection




Instrumentation Amplifier

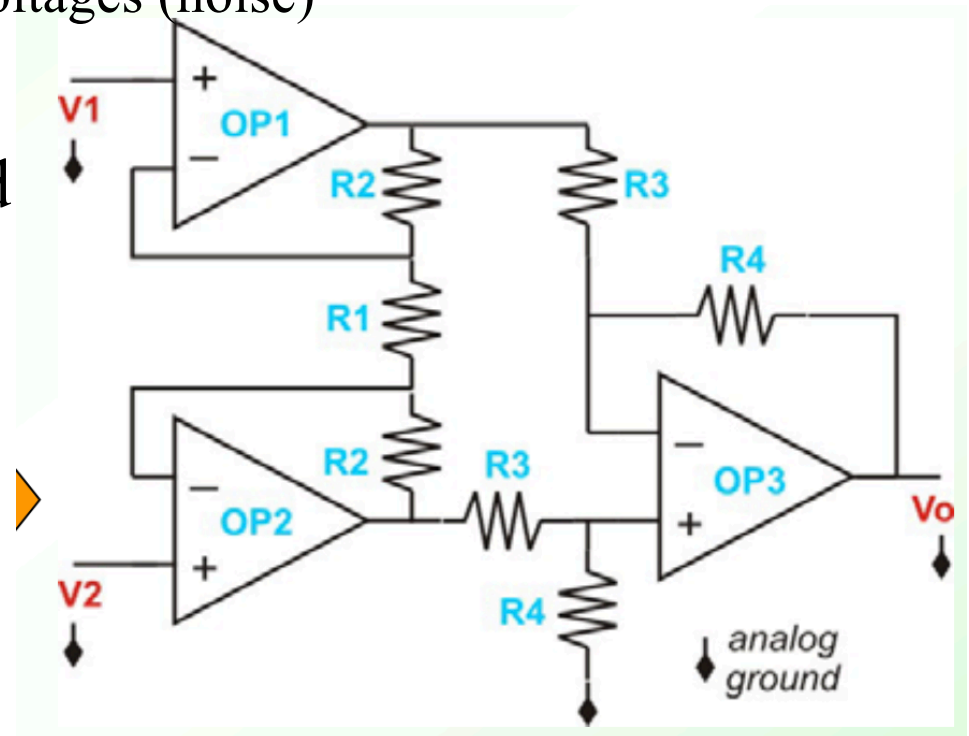
- ❑ This 3-op-amp circuit is called an **instrumentation amplifier**
- ❑ Input stage characteristics
 - low common-mode gain
 - -rejects common mode voltages (noise)
 - high input impedance
 - Input stage gain adjusted



Instrumentation Amplifier

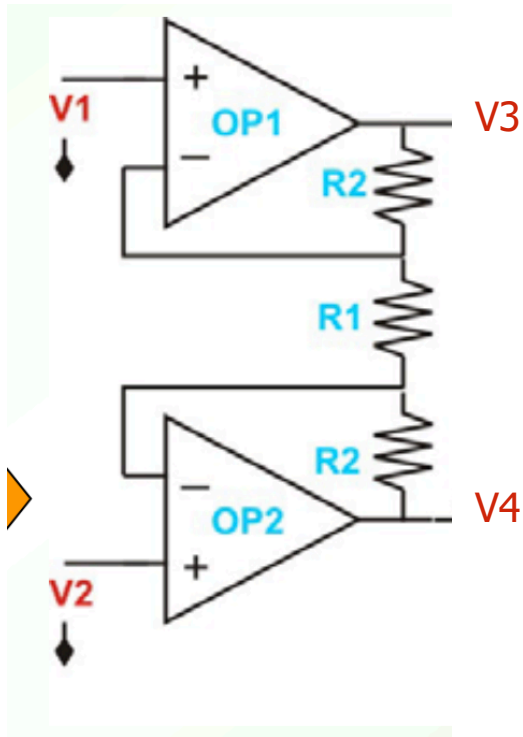

Instrumentation Amplifier

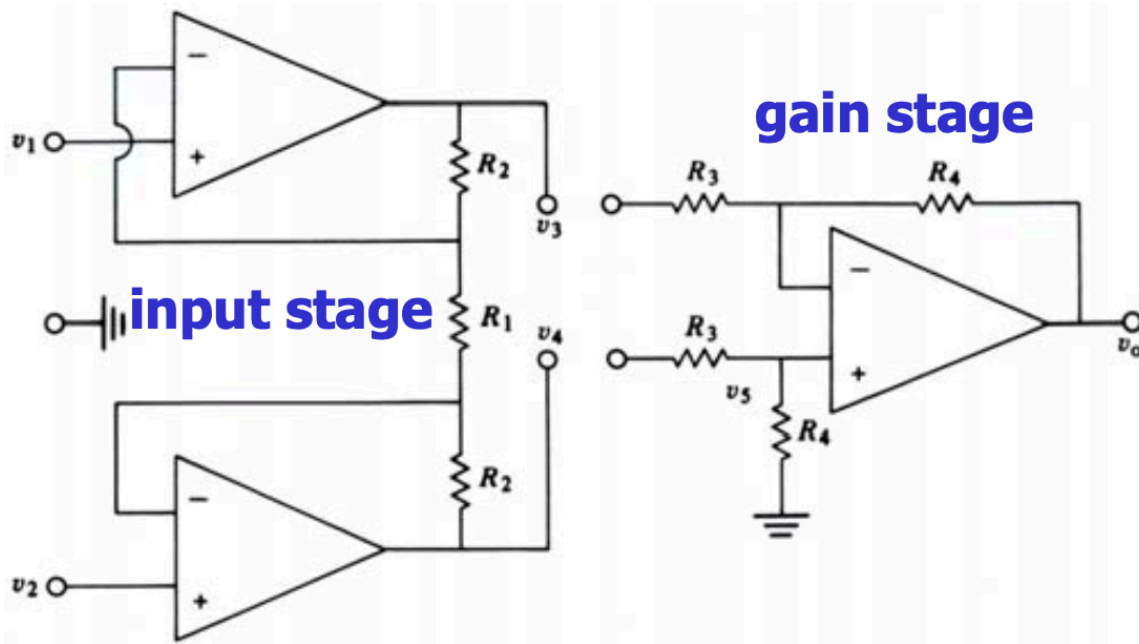

$$\frac{v_o}{v_i} = \left(\frac{2R_2 + R_1}{R_1} \right) \frac{R_4}{R_3}$$

❑ Overall amplifier

- Amplifies only the differential component
 - High common mode rejection ratio
- High input impedance suitable for biopotential electrodes


Driven Right Leg System

❑ Motivation



- Reduce interference in amplifier
- Improve patient safety

❑ Approach

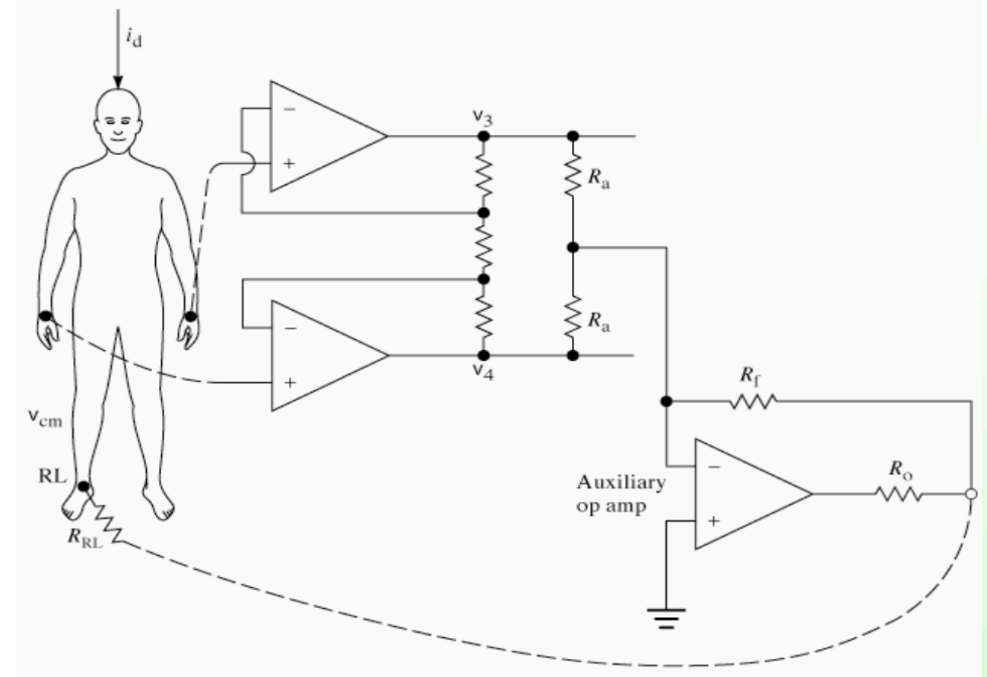- Patient right leg tied to output of an auxiliary amp rather than ground
- Common mode voltage on body sensed by averaging resistors, R_a 's & fed back to right leg
- Provides negative feedback to reduce common mode voltage
- If high voltage appears between patient and ground, auxiliary amp effectively un-grounds the patient to stop current flow




Driven Right Leg System Example

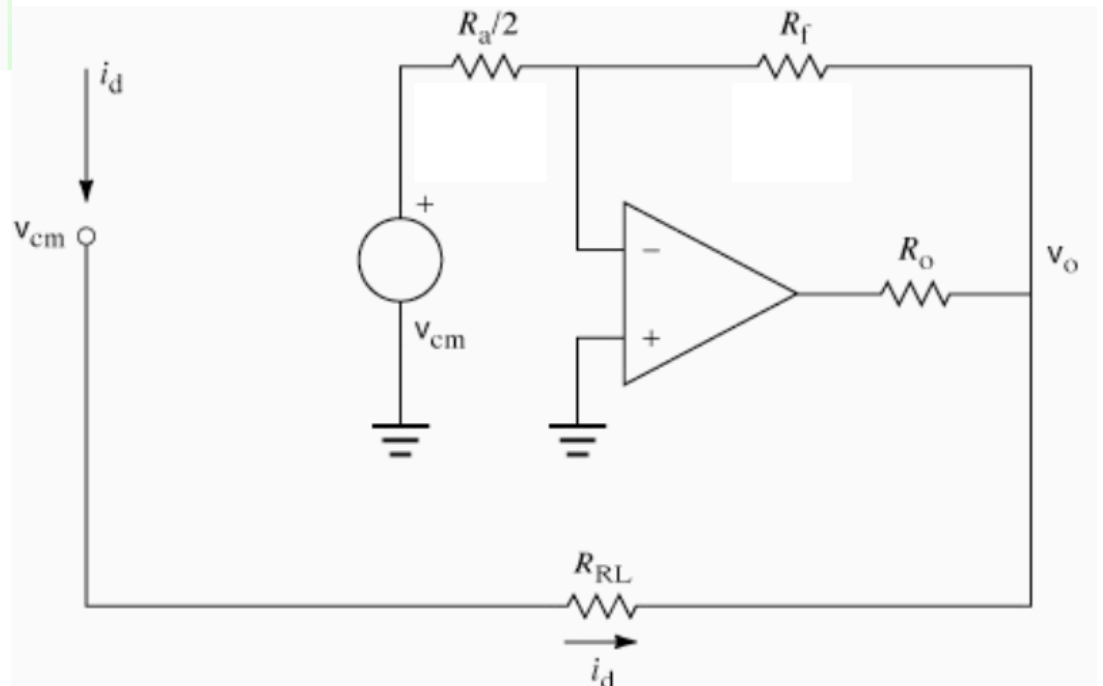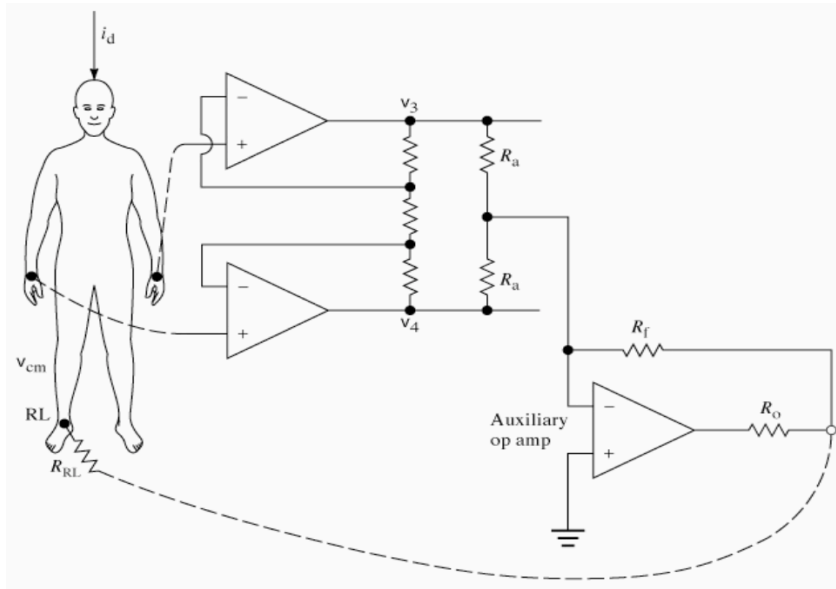

Driven Right Leg System Example

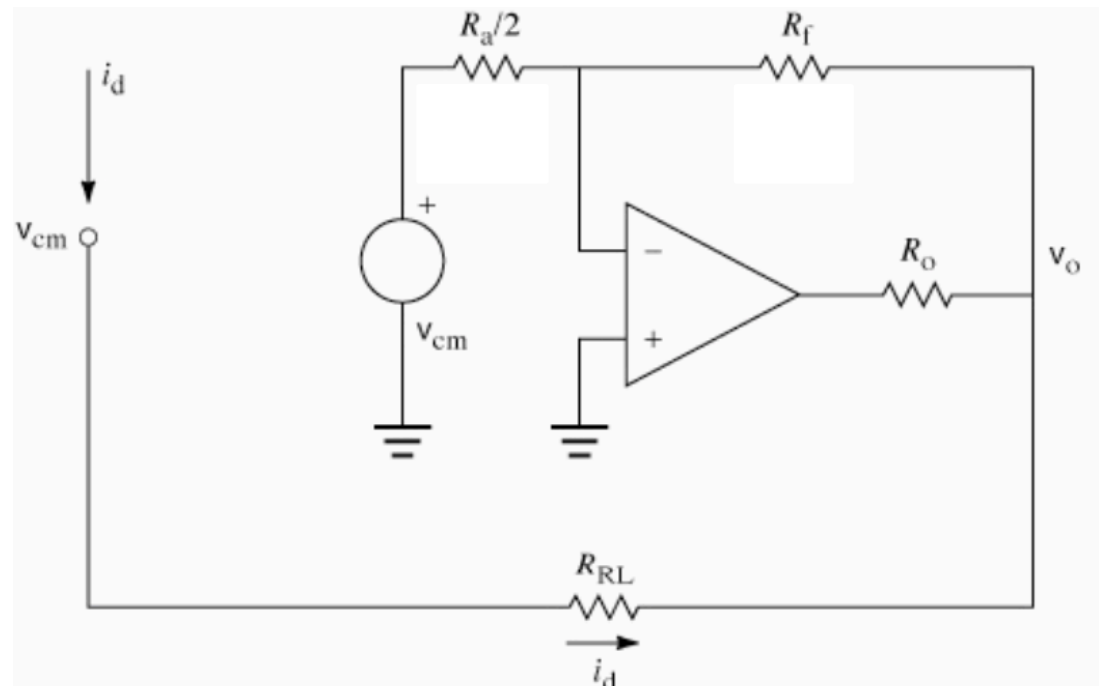- ❑ **Problem:** Determine the common-mode voltage v_{cm} on the patient in the driven-right-leg circuit when a displacement current i_d flows to the patient from the power lines. Choose appropriate values for the resistances in the circuit so that the common-mode voltage is minimal. With a worst-case electrode resistance of $100\text{k}\Omega$, what is the v_{cm} when $i_d = 0.2\mu\text{A}$?





Big Ideas

- ❑ Amplification
 - Use operational amplifier with differential signaling
- ❑ Biopotential Amplifier
 - Designed to amplify and filter sensor outputs for data acquisition or driving
- ❑ Instrumental Amplifier
 - Designed specifically for biopotential signals to compensate for non-idealities
 - Common-mode voltages responsible for much of the interference in biopotential amplifiers



Admin

- ❑ Finish Lab 2 and submit deliverables in Canvas by next lab day at midnight
- ❑ Lab 3 on Monday



Lab 3

- ❑ LT Spice
- ❑ Simulate the signal conditioning specific to our ECG design




LT Spice

□ Circuit Simulator

- LTspice is high performance SPICE simulator software, including a graphical schematic capture interface. Schematics can be probed to produce simulation results—easily explored through LTspice’s built-in waveform viewer.

LT Spice BP Filter Example

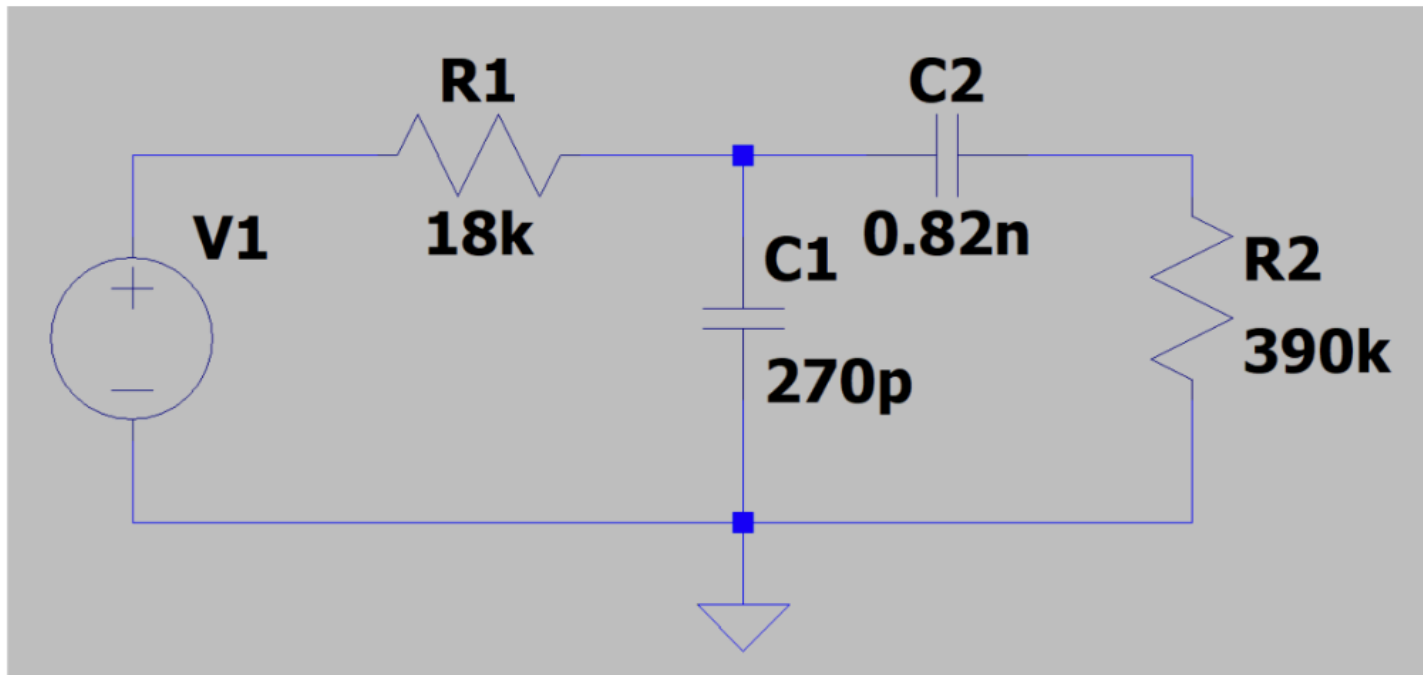

Lab 3


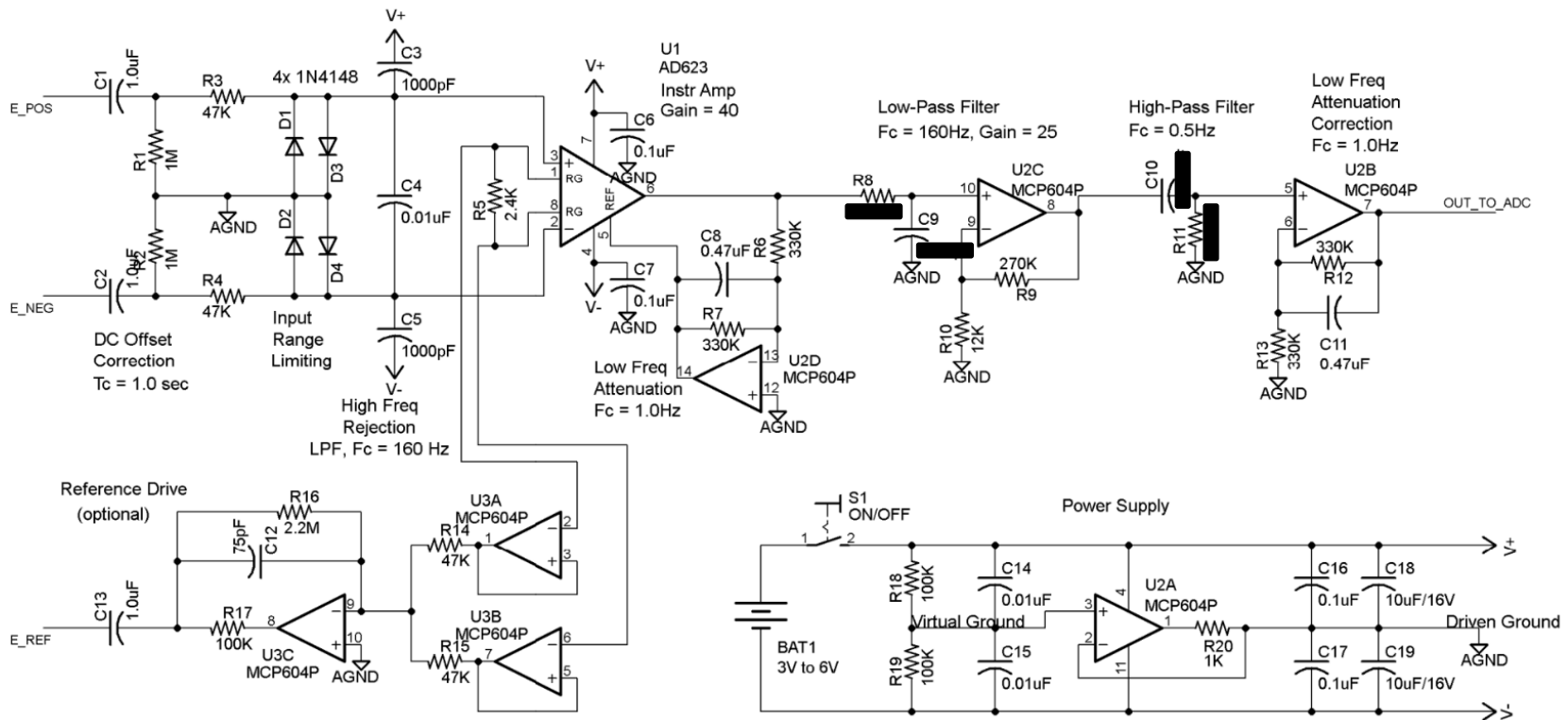


Figure 2: Schematic of 2-Electrode ECG Amplifier with Optional Driven Reference Electrode

Lab 3

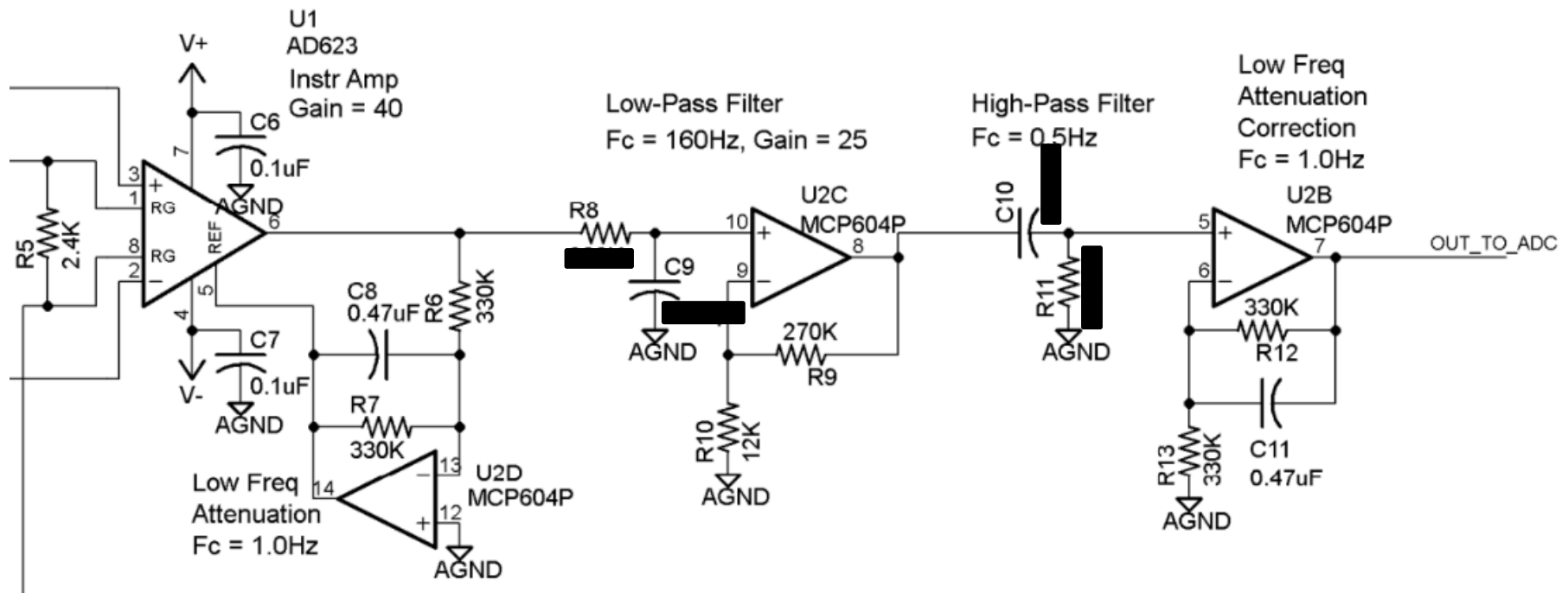



Lab 3

