

# ESE370: Circuit-Level Modeling, Design, and Optimization for Digital Systems

---

Lec 11: September 29, 2021  
Layout and Area



# Today

---

- Layout
  - Transistors
  - Gates
- Design rules
- Standard cells




# Transistor

---



Side view

 


Perspective view


 
# Layout

---


- ❑ Sizing & positioning of transistors
- ❑ Designer controls  $W$ ,  $L$
- ❑  $t_{\text{ox}}$  fixed for process
  - Sometimes thick/thin oxide “flavors”






# NMOS Geometry

---

 

Top view

 


Perspective view


 
# NMOS Geometry

---

- Color scheme
  - Red: gate (polysilicon material)
  - Green: source and drain areas (n type diffusion)




Top view


 
# PMOS Geometry




- Color scheme
  - Red: gate
  - Orange: source and drain areas (p type)
  - Green: n well
- NMOS built on p wafer
  - Must add n well material to build PMOS





 
 
 
# Body Contact

- ❑ “Fourth terminal”
- ❑ Needed to set voltage around device
  - PMOS:  $V_b = V_{dd}$
  - NMOS:  $V_b = GND$
- ❑ At right: PMOS (orange) with bulk contact (dark green)



 
 
 
# Body Contact

- ❑ Needed to set voltage around device
  - PMOS:  $V_b = V_{dd}$
  - NMOS:  $V_b = \text{GND}$
- ❑ What happens if NMOS body contact is  $V_{dd}$ ?



  
 
# Body Contact

- ❑ Needed to set voltage around device
  - PMOS:  $V_b = V_{dd}$
  - NMOS:  $V_b = GND$
- ❑ What happens if NMOS body contact is  $V_{dd}$ ?
  - Polarity of field wrong
  - Won't invert channel





# Transistor Geometry

  


NMOS

PMOS

B S G D


D G S B

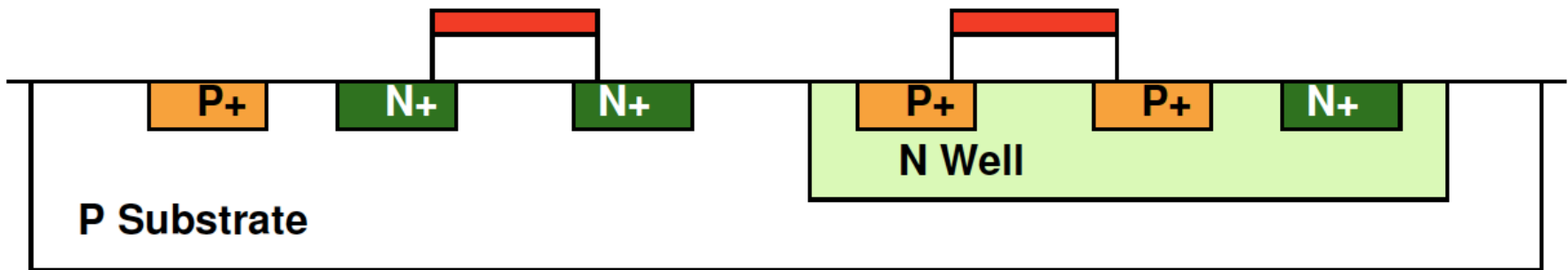


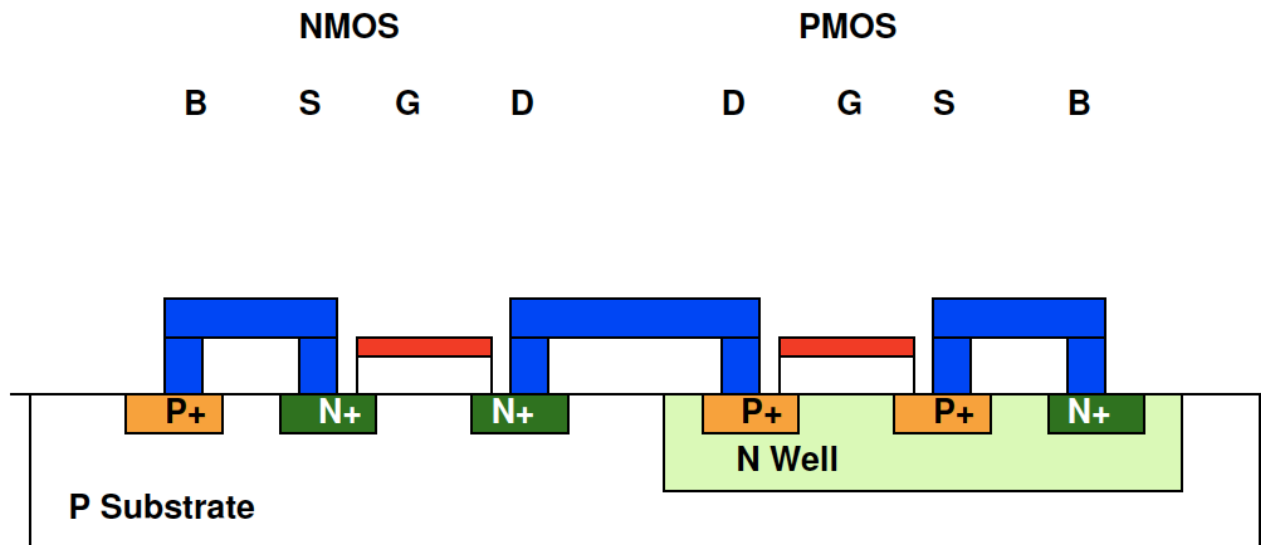
# Interconnect


- Connect transistors
  - Different layers of metal
    - “Contact” - metal to transistor
    - “Via” - metal to metal





 
# Interconnect

- Connect transistors
  - Different layers of metal
    - “Contact” - metal to transistor
    - “Via” - metal to metal




# Interconnect Cross Section

 

 
# Masks

- Define areas want to see in layer
  - Think of “stencil” for material deposition
- Use photoresist (PR) to form the “stencil”
  - Grow PR over entire wafer
  - Expose PR through mask
  - PR dissolves in exposed areas
  - Material is deposited/etched
    - Only “sticks” in area w/ dissolved PR










# Typical N-Well CMOS Process

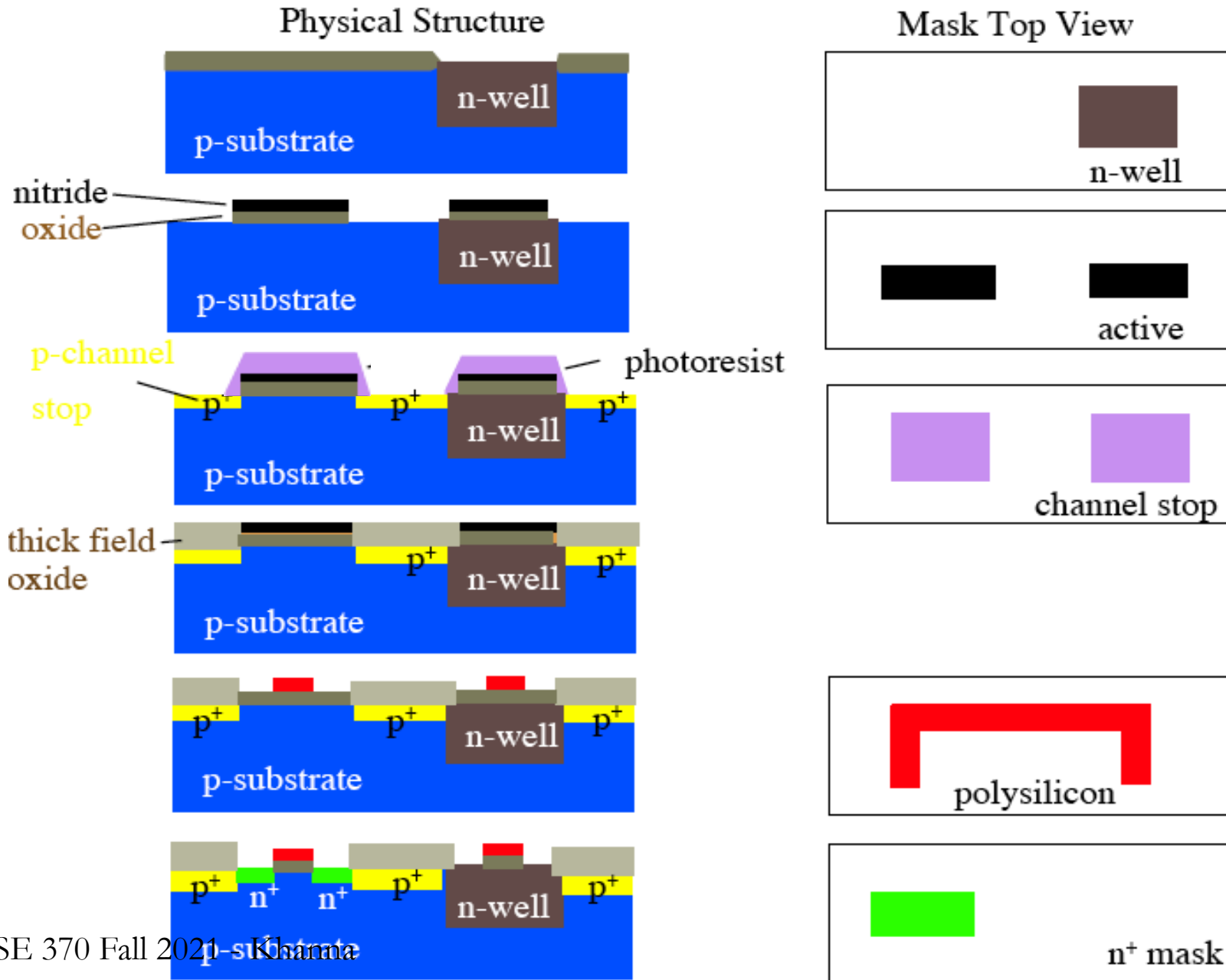

# Typical N-Well CMOS Process



Physical Structure

Mask Top View

     



  
# Reverse Engineer Inverter Layout (Preclass 1)






# Layout Revisited


- How to “decode” circuit from layout?

 

# Reverse Engineer Inverter Layout

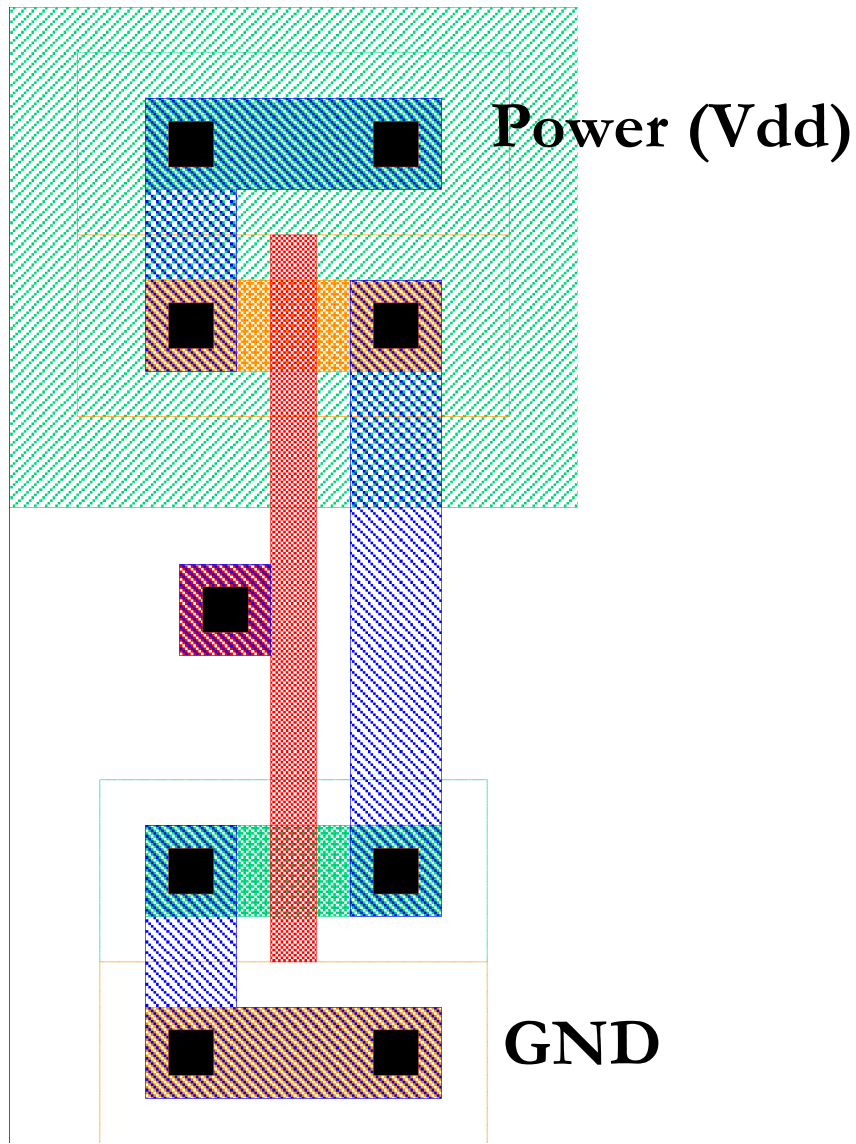

# Reverse Engineer Inverter Layout





 


- Where is PMOS transistor?
- NMOS?



# Layout to Circuit


- 1. Identify transistors

     



# Inverter Layout

□ Where is Input?

 






# Inverter Layout


□ Where is Input?

 



# Inverter Layout


□ Where is Output?

 




# Inverter Layout

□ Where is Output?

 




# Layout to Circuit

 


 - 2. Add connections
  - Drain connection







# Layout to Circuit

 


## 2. Add connections

### Gate connection

  




# Layout to Circuit

 


 - 2. Add connections
  - pMOS-source to VDD






# Layout to Circuit

 


 - 2. Add connections
  - nMOS source to GND





# Design Rules

 

## □ Why not adjacent transistors?

- Plenty of empty space
- If area is money, pack in as much as possible
  - Shortens connections
- Recall: processing is imprecise
  - Margin of error for process variation













# Design Rules

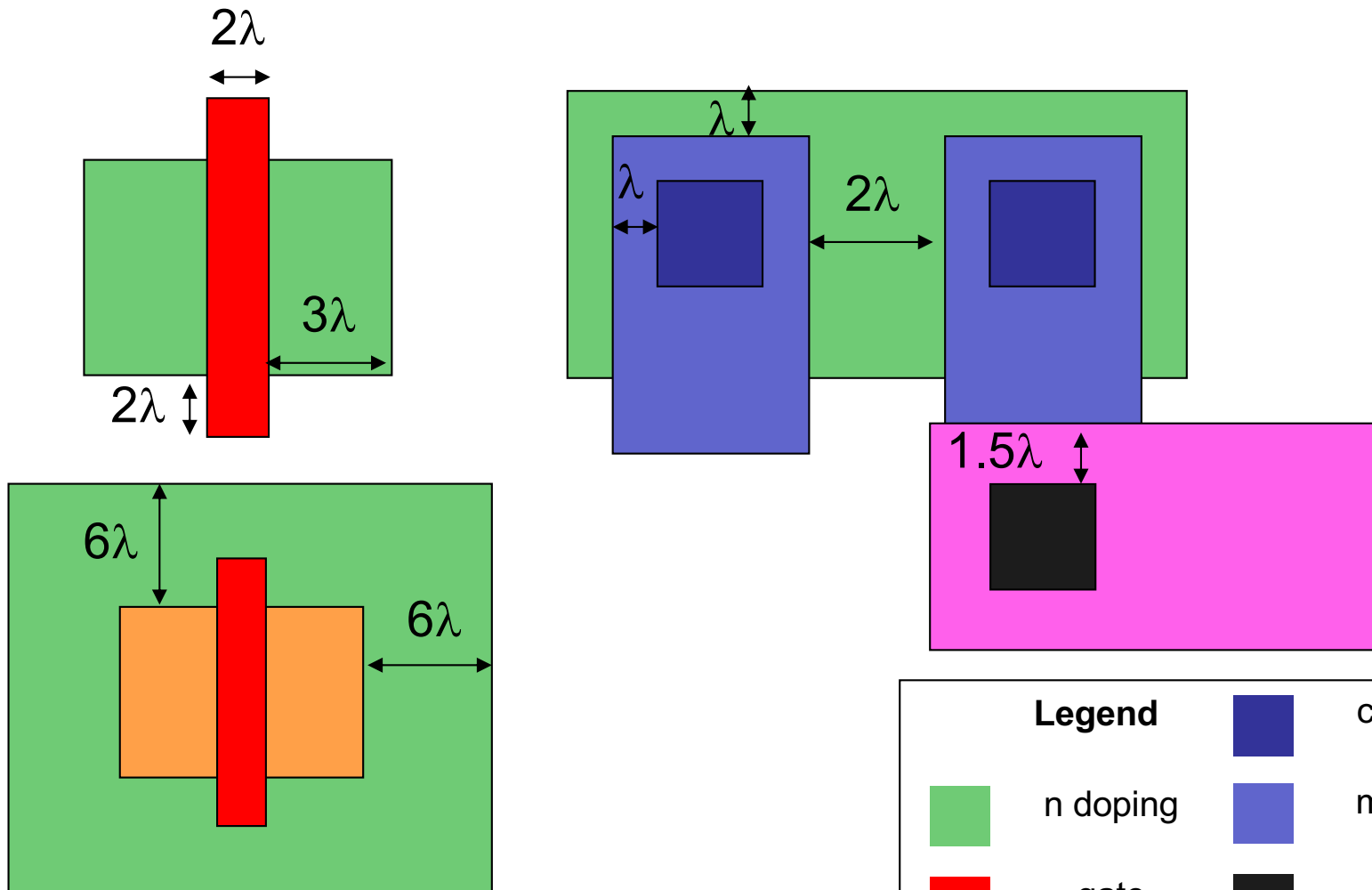---

- ❑ Contract between process engineer & designer
  - Minimum width/spacing
  - Can be (often are) process specific
  
- ❑ Lambda rules: scalable design rules
  - In terms of  $\lambda = 0.5 L_{\min}$  ( $L_{\text{drawn}}$ )
  - Can migrate designs from similar process with lambda factor

# Design Rules: Some Examples




Legend	
	n doping
	gate
	p doping
	contact
	metal 1
	via
	metal 2

# Potential Consequences of Design Rule Violations


## ❑ Inter-Layer Design Rule Origins

Intended Transistor

 

Catastrophic Error –  
Unintended  
misalignment cause  
Source-Drain short  
circuit

Intended  
Unrelated Poly &  
Diffusion

 


Catastrophic Error –  
Unintended overlap  
cause fabrication of a  
parasitic Transistor

# Potential Consequences of Design Rule Violations

## □ Inter-Layer Design Rule Origins


### Contact and Via Masks

M1 contact to n-diffusion	}	-> Contact Mask
M1 contact to p-diffusion		
M1 contact to poly		
Mn contact to Mn-1 for n = 2, 3,..		-> Via Mask

 




# Layout #2 (preclass 2)

 
 
# Layout #2 (preclass 2)


- How many transistors?
  - PMOS?
  - NMOS?
- How connected?
  - PMOS, NMOS?
- Inputs connected how?
- Outputs?
- What is it?




 
# Symbolic Layout


- ❑ Stick diagrams capture spatial relationships, but abstract away design rules



- ❑ What is the gate function?
  - How many NMOS? PMOS? D/S connections?
  - Draw schematic

 
# Standard Cells

- Lay out gates so that heights match
  - Rows of adjacent cells
  - Standardized sizing of gate heights
- Motivation: automated place and route
  - EDA tools convert HDL to layout






# Standard Cells

 

Fanout 4x	0.5 $\mu\text{m}$	1.0 $\mu\text{m}$	2.0 $\mu\text{m}$
<i>A1_tphl</i>	0.595	0.711	0.919
<i>A1_tplh</i>	0.692	0.933	1.360
<i>B1_tphl</i>	0.591	0.739	1.006
<i>B1_tplh</i>	0.620	0.825	1.1.81
<i>C1_tphl</i>	0.574	0.740	1.029
<i>C1_tplh</i>	0.554	0.728	1.026


**3-input NAND cell**  
 (from Mississippi State Library)  
 characterized for fanout of 4 and  
 for three different technologies

# Standard Cell Layout Example

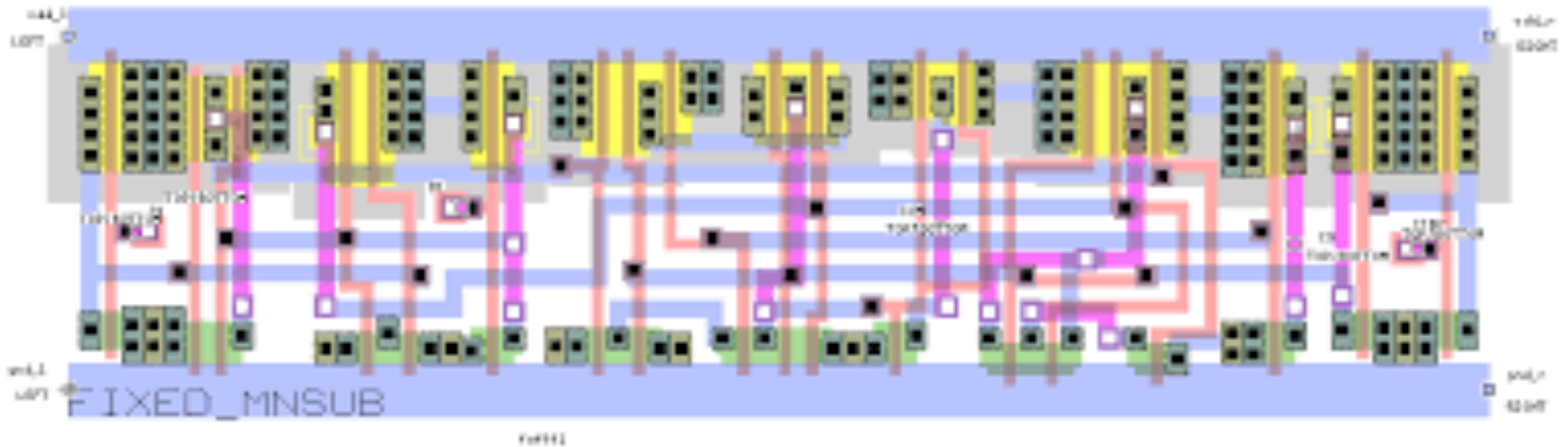




# Standard Cell Area

 


# Standard Cell Layout Example

 


<http://www.laytools.com/images/StandardCells.jpg>

# Standard Cell Layout Example

 


<http://www.laytools.com/images/StandardCells.jpg>

# 4x4 6T SRAM Memory

 

 
# Circuit Extraction

- ❑ Circuit extraction extracts a schematic representation of a layout, including transistors, wires, and possibly wire and device resistance and capacitance.




- ❑ Circuit extraction is used for LVS, and for spice simulation of layouts

# Circuit Extraction

 



# Circuit Extraction

 



 
# Big Idea

---

- ❑ Layouts are physical realization of circuit
  - Geometry tradeoff
    - Can decrease spacing at the cost of yield
    - Design rules
- ❑ Can go from circuit to stick diagram/layout or stick diagram/layout to circuit by inspection





# Admin

---

- ❑ Midterm 1 Friday 10/1
  - 7-9pm in Towne 309
  - No Lecture, virtual office hours
    - Use Tania OH link on Piazza
  - Virtual review session on Wednesday, will be recorded
    - See Piazza for updates
- ❑ HW 4 posted Friday 10/1 after midterm
  - Due following **Friday** 10/8 @midnight