

ESE370: Circuit-Level Modeling, Design, and Optimization for Digital Systems

Lec 13: October 6, 2021
Inverter Performance

Scale V separately with Factor U

Ideal scale factors:

$$S=100$$

$$U=100$$

$$\tau=1/100$$

$$f_{ideal}=100$$

$$\tau_{gd} = Q/I = (CV)/I$$

$$V' \rightarrow V/U$$

$$I'_d = (\mu C_{OX} S/2) ((W/S)/(L/S) (V_{gs}/U - V_{TH}/U)^2$$

$$I'_d \rightarrow S/U^2 \times I_d$$

$$C' \rightarrow C/S$$

$$\tau'_{gd} \rightarrow ((1/(SU)) / (S/U^2)) \times \tau_{gd}$$

$$\tau'_{gd} \rightarrow (U/S^2) \times \tau_{gd}$$

$$f' \rightarrow (S^2/U) \times f$$

$$f_{new}/f_{ideal} = 10$$

Cheating factors:

$$S=100$$

$$U=10$$

$$\tau=1/1000$$


$$f_{new}=1000$$



Power Density Impact

- ❑ $P = (1/2)CV^2 f$
- ❑ $P \rightarrow (1/S) (1/U^2) (S^2/U) = S/U^3$
- ❑ $P/A \rightarrow (S/U^3) / (1/S^2) = S^3/U^3$

- ❑ $U=10 \quad S=100$
- ❑ $P/A \rightarrow 1000 (P/A)$



Power Density Impact

- ❑ $P = (1/2)CV^2 f$
- ❑ $P \rightarrow (1/S) (1/U^2) (S^2/U) = S/U^3$
- ❑ $P/A \rightarrow (S/U^3) / (1/S^2) = S^3/U^3$

- ❑ $U=10 \quad S=100$
- ❑ $P/A \rightarrow 1000 (P/A)$

- ❑ **Compare with ideal scaling:**
- ❑ $P/A \rightarrow S^3 \times P$ (ideal scaling)
- ❑ $P/A \rightarrow 1,000,000 (P/A)$ (ideal scaling)


Scaling Methods

Table 3.8 Scaling scenarios for short-channel devices.

Parameter	Relation	Constant Field	General Scaling	Constant Voltage
W, L, t_{ox}		$1/S$	$1/S$	$1/S$
V_{DD}, V_T		$1/S$	$1/U$	1
N_{SUB}	V/W_{depl}^2	S	S^2/U	S^2
Area/Device	WL	$1/S^2$	$1/S^2$	$1/S^2$
C_{ox}	$1/t_{ox}$	S	S	S
C_{gate}	$C_{ox}WL$	$1/S$	$1/S$	$1/S$
k_n, k_p	$C_{ox}W/L$	S	S	S

$U < S$

42 Years of uP Trend Data

 




Conventional Scaling


- ❑ Ends in your lifetime
- ❑ Perhaps already:
 - "Basically, this is the end of scaling."
 - May 2005, Bernard Meyerson, V.P. and chief technologist for IBM's systems and technology group

ITRS 2.0 Report 2015

 - “After 2021, the report forecasts, it will no longer be economically desirable for companies to continue traditional transistor miniaturization in microprocessors.”




BUT...

 

Source: <https://newsroom.intel.com/newsroom/wp-content/uploads/sites/11/2017/09/mark-bohr-on-continuing-moores-law.pdf>

BUT...

 

Source: <https://newsroom.intel.com/newsroom/wp-content/uploads/sites/11/2017/09/mark-bohr-on-continuing-moores-law.pdf>



Previously

- Delay as RC-charging
- Transistor
 - Capacitance
 - Drive Current
 - Function of geometry (W/L)



Today

- τ -model
- Sizing
- Large Fanout
- Capacitance Revisited
 - Miller Effect

Transistor Sizing

- What happens to I_{ds} as a function of W ?

$$I_{DS} \approx v_{sat} C_{OX} W \left(V_{GS} - V_T - \frac{V_{DSAT}}{2} \right)$$

- What happens to C_g as a function of W ?

$$C_G \propto C_{ox} WL$$

Transistor Sizing

- What happens to I_{ds} as a function of W ?

$$I_{DS} \approx v_{sat} C_{OX} W \left(V_{GS} - V_T - \frac{V_{DSAT}}{2} \right)$$

- What happens to C_g as a function of W ?

$$C_G \propto C_{ox} WL$$

- **Conclude:** faster transistors present more load on their inputs



First Order Delay (preclass 1)

- ❑ $I_0 = I_{ds}$ of minimum size NMOS device
- ❑ $C_0 =$ gate capacitance of minimum size NMOS device

- ❑ $I_{drive} = WI_0$
- ❑ $C_g = WC_0$



First Order Delay (preclass 1)

- ❑ R_0 = Resistance of minimum size NMOS device
- ❑ C_0 = gate capacitance of minimum size NMOS device

- ❑ $R_{\text{drive}} = R_0/W$
- ❑ $C_g = WC_0$




τ model

- ❑ All delays are RC delays
- ❑ Always have an R_0C_0 term
- ❑ $\tau = R_0C_0$
- ❑ Express all delays in τ units
- ❑ Like λ units for measurement
 - Separate delay into
 - Technology dependent term $\tau = R_0C_0$
 - Technology independent coefficient

How to Size Transistors (preclass 2)

- How should we size to equalize Rise and Fall?
 - Given:
 - $\mu_n = 500 \text{cm}^2/\text{Vs}$, $\mu_p = 200 \text{cm}^2/\text{Vs}$
 - $R_{\text{drive}} = R_0/2$ ($I_{\text{drive}} = 2I_0$)
 
$$I_{DS} = \mu C_{OX} \frac{W}{L} (V_{GS} - V_T)^2$$




How to Size Transistors (preclass 2)

□ How should we size to equalize Rise and Fall?


- Given:
- $\mu_n = 500 \text{cm}^2/\text{Vs}$, $\mu_p = 200 \text{cm}^2/\text{Vs}$
- $R_{\text{drive}} = R_0/2$ ($I_{\text{drive}} = 2I_0$)
 
$$I_{DS} = \mu C_{OX} \frac{W}{L} (V_{GS} - V_T)^2$$




- What is input capacitance for sized devices?

Size Transistors – Minimum Avg Delay

 


- β of 2.4 (= 31 k Ω /13 k Ω) gives symmetrical response
- β of 1.6 to 1.9 gives optimal performance

SPICE Simulation 45nm

 

SPICE Simulation 22nm

 




Equalizing Delay

- For simplicity, for today
 - Assume $W_p = W_n$ equalizes I_{ds}
 - I.e $I_{0,n} = I_{0,p}$


Inverter Sizing

 - What is the impact of the delay if we double size of all the transistors?




Multistage Delay

 - Total delay = sum of stage delays
- What is delay here?
 - From (P1,N1) to final capacitive load




Large Fanout Delay (preclass 3)

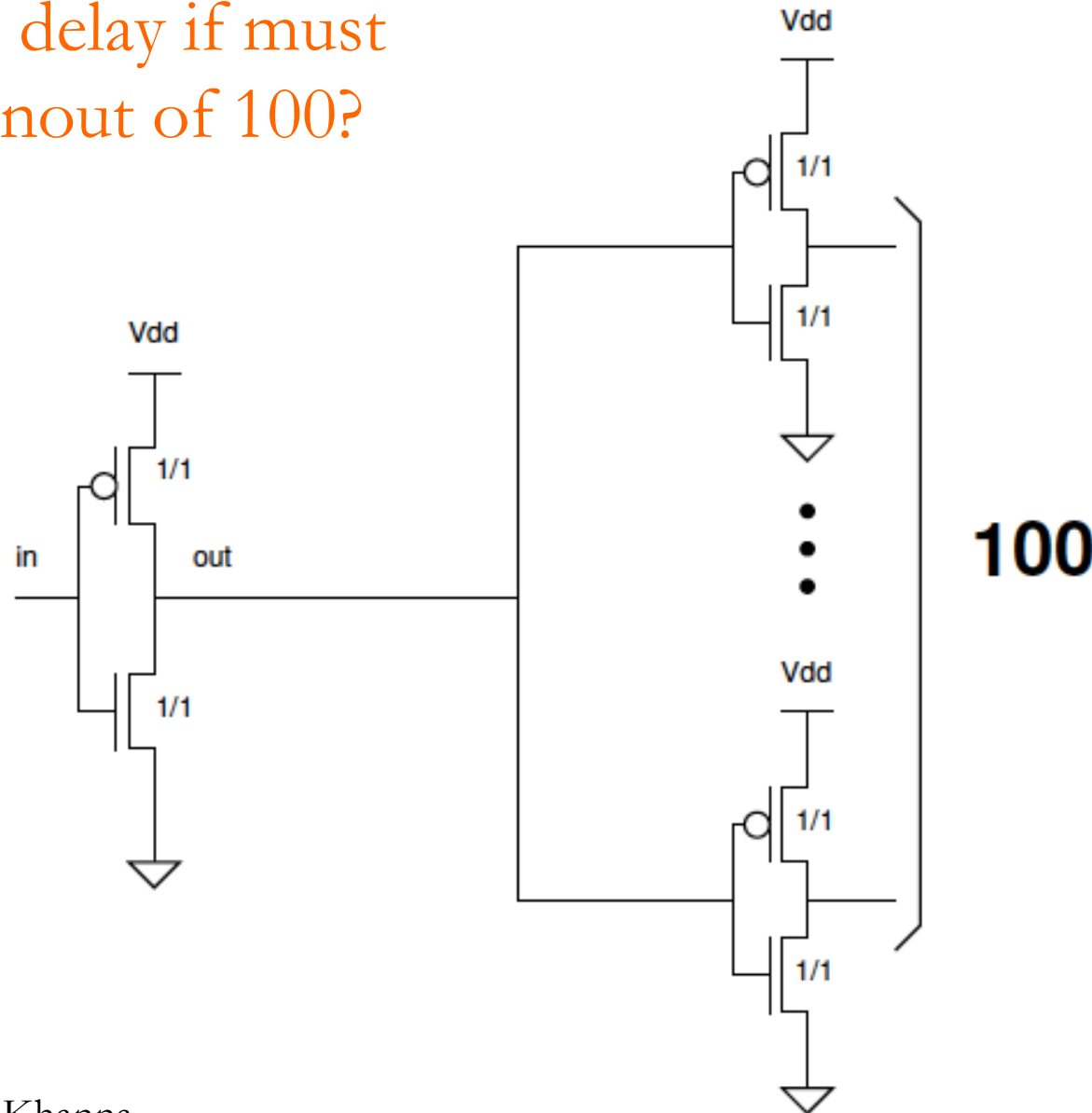- What is delay if must drive fanout of 100?




Graduated Fanout Delay (preclass 3)

□ What is delay here?

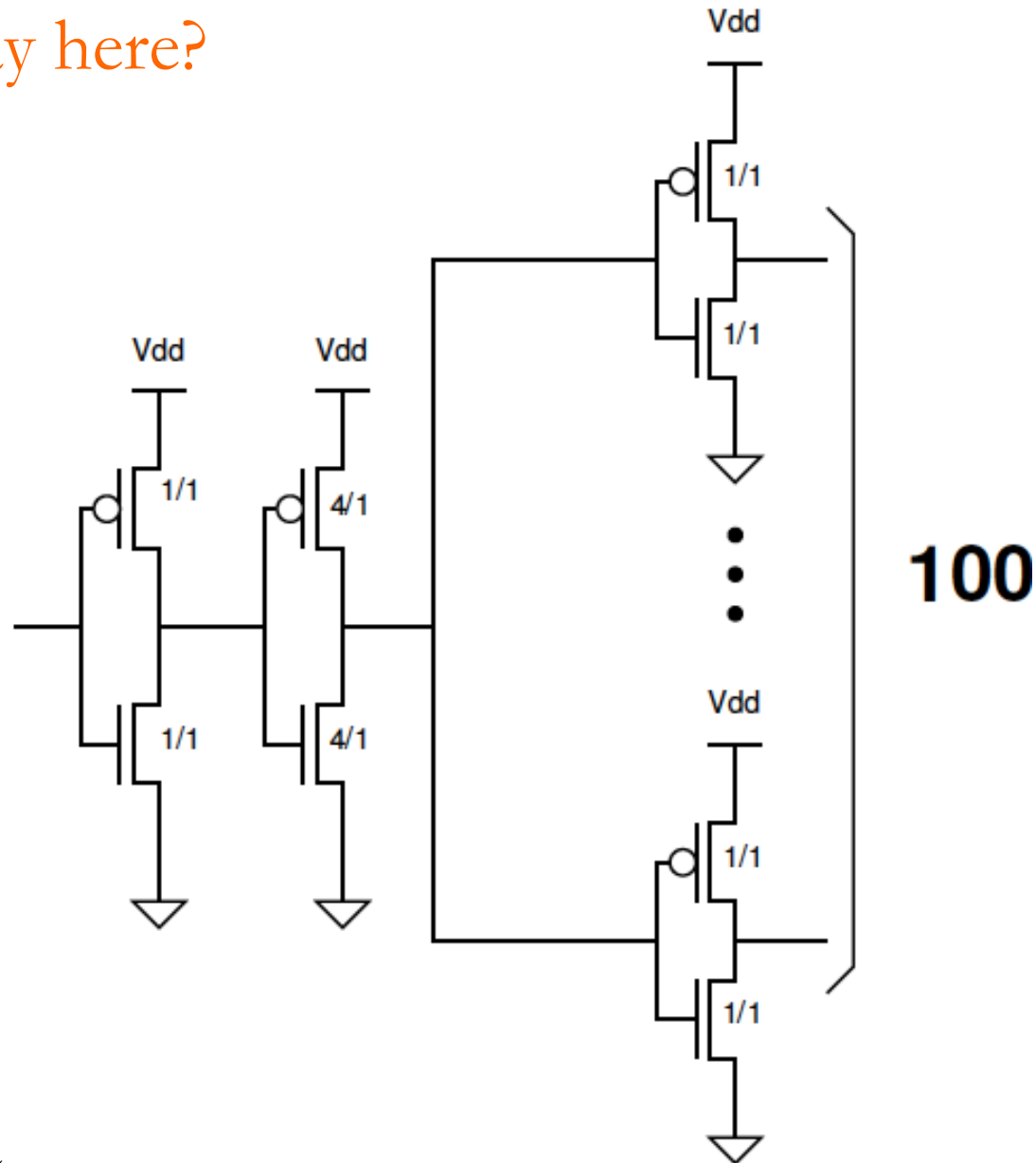

Optimize Fanout Delay (preclass 4)

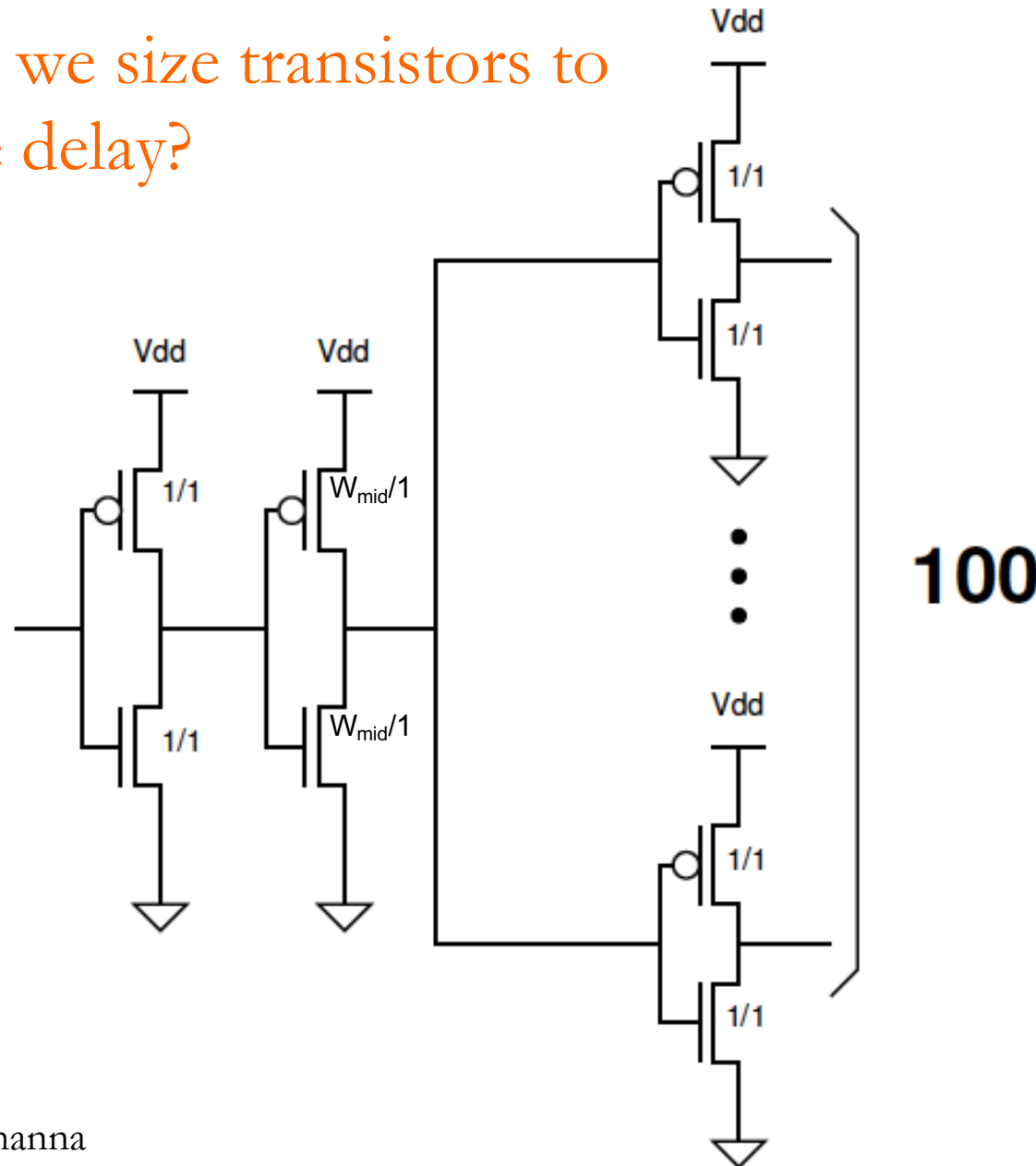- How can we size transistors to minimize delay?



Optimizing (preclass 4)

□ Derivate to minimize

$$\tau_{est} = R_0 \times 2W_{mid}C_0 + \frac{R_0}{W_{mid}} \times 200C_0$$

$$\frac{\partial \tau_{est}}{\partial W_{mid}} = 0$$


$$2R_0C_0 - \frac{200}{W_{mid}^2} R_0C_0 = 0$$

$$W_{mid} = \sqrt{100} = 10$$




Delay? (preclass 4)

- Delay at optimal W_{mid} ?

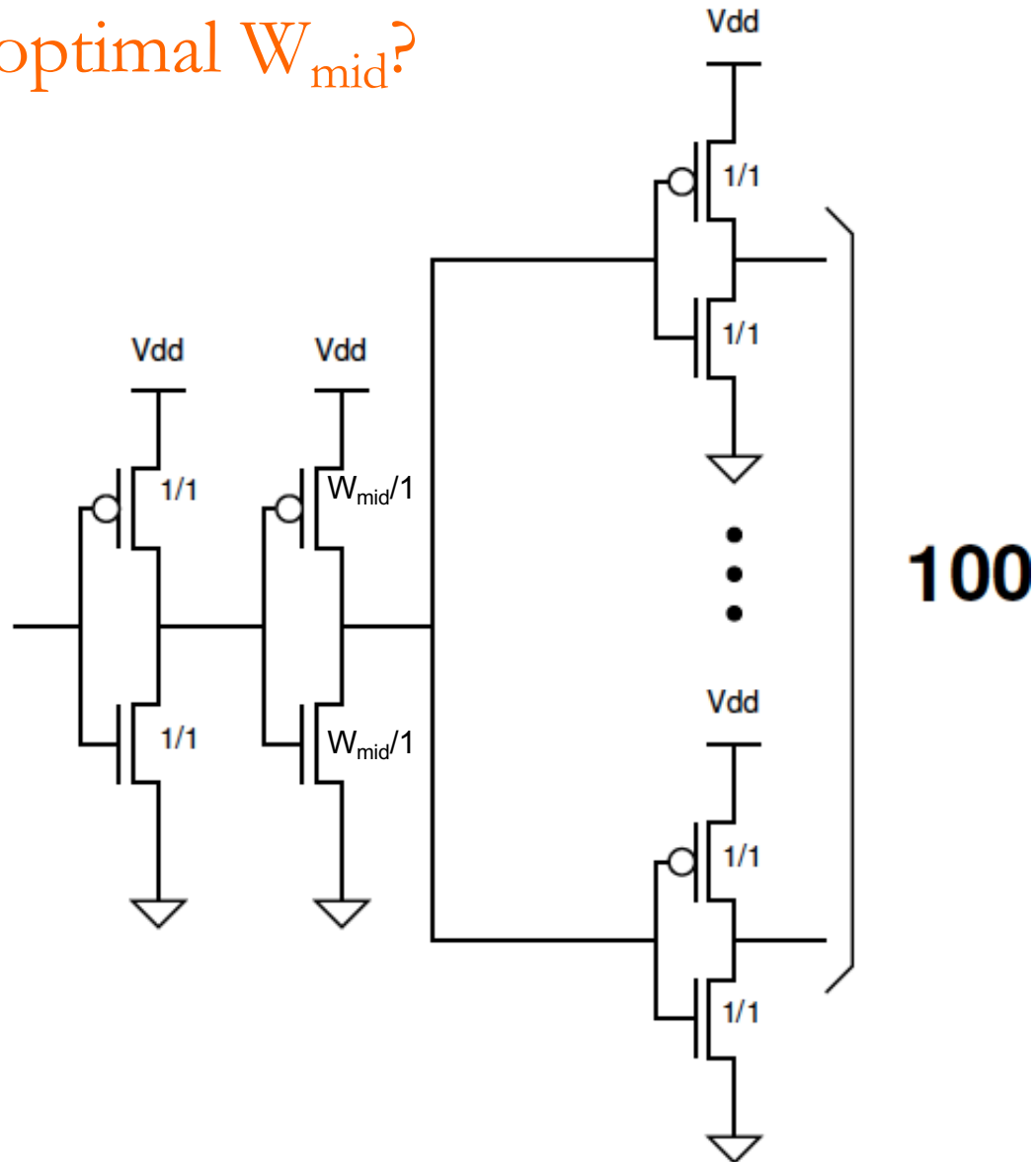


Try Again with More Stages (preclass 5)

□ What is the delay here?

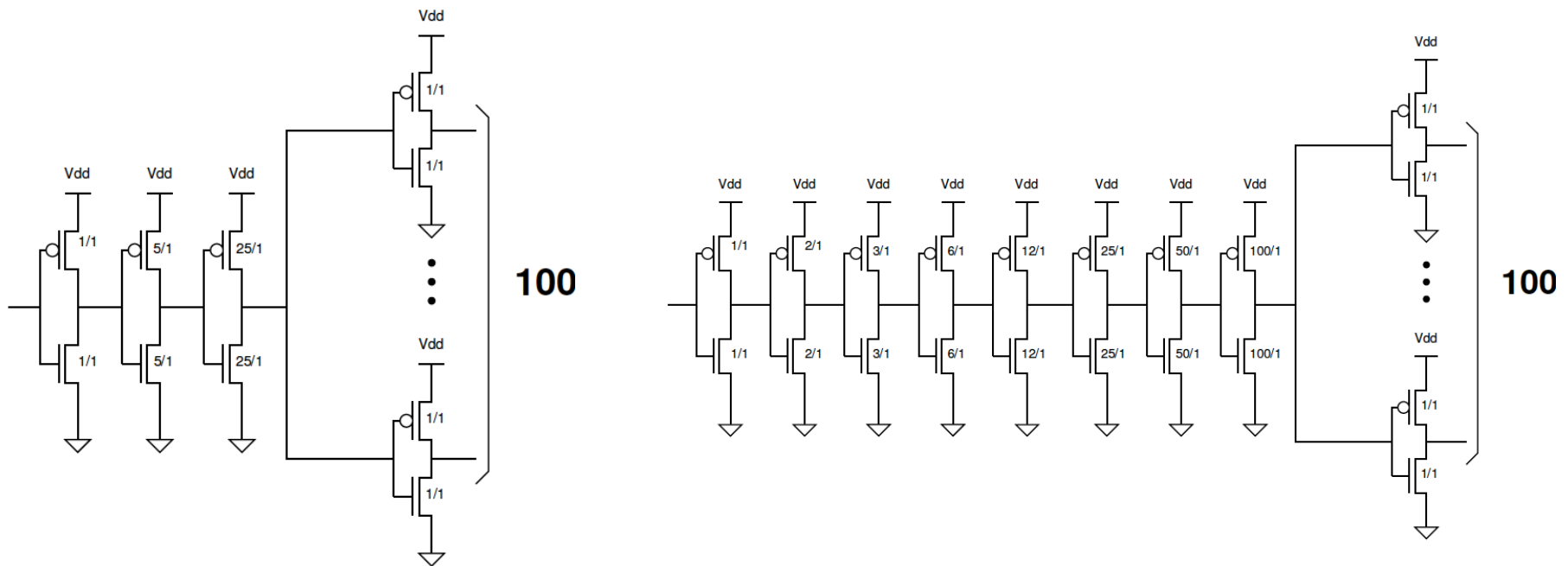


Try Again with More Stages (preclass 5)

- What is the delay here?

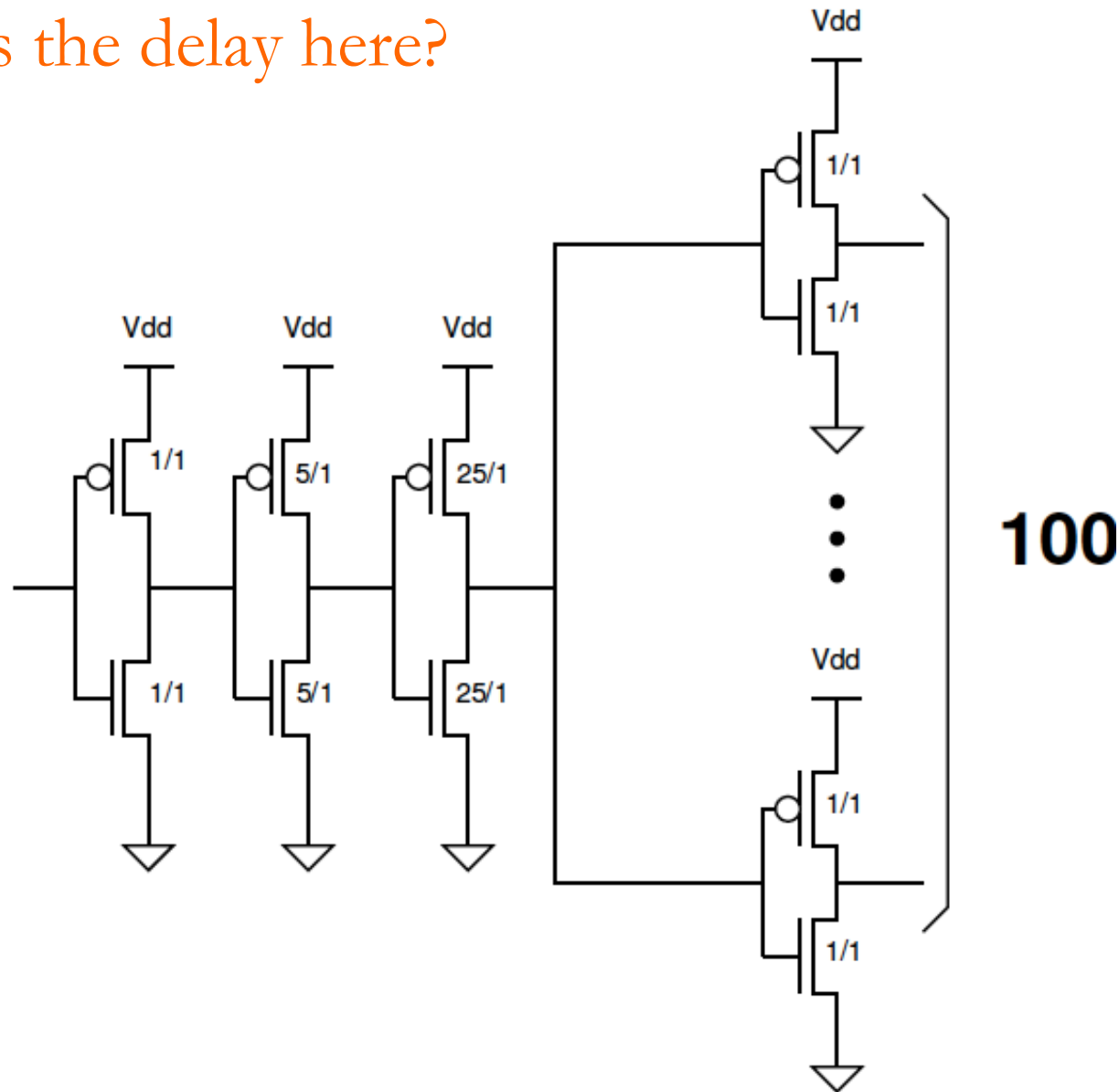





...and Again (preclass 5)

□ Delay here?

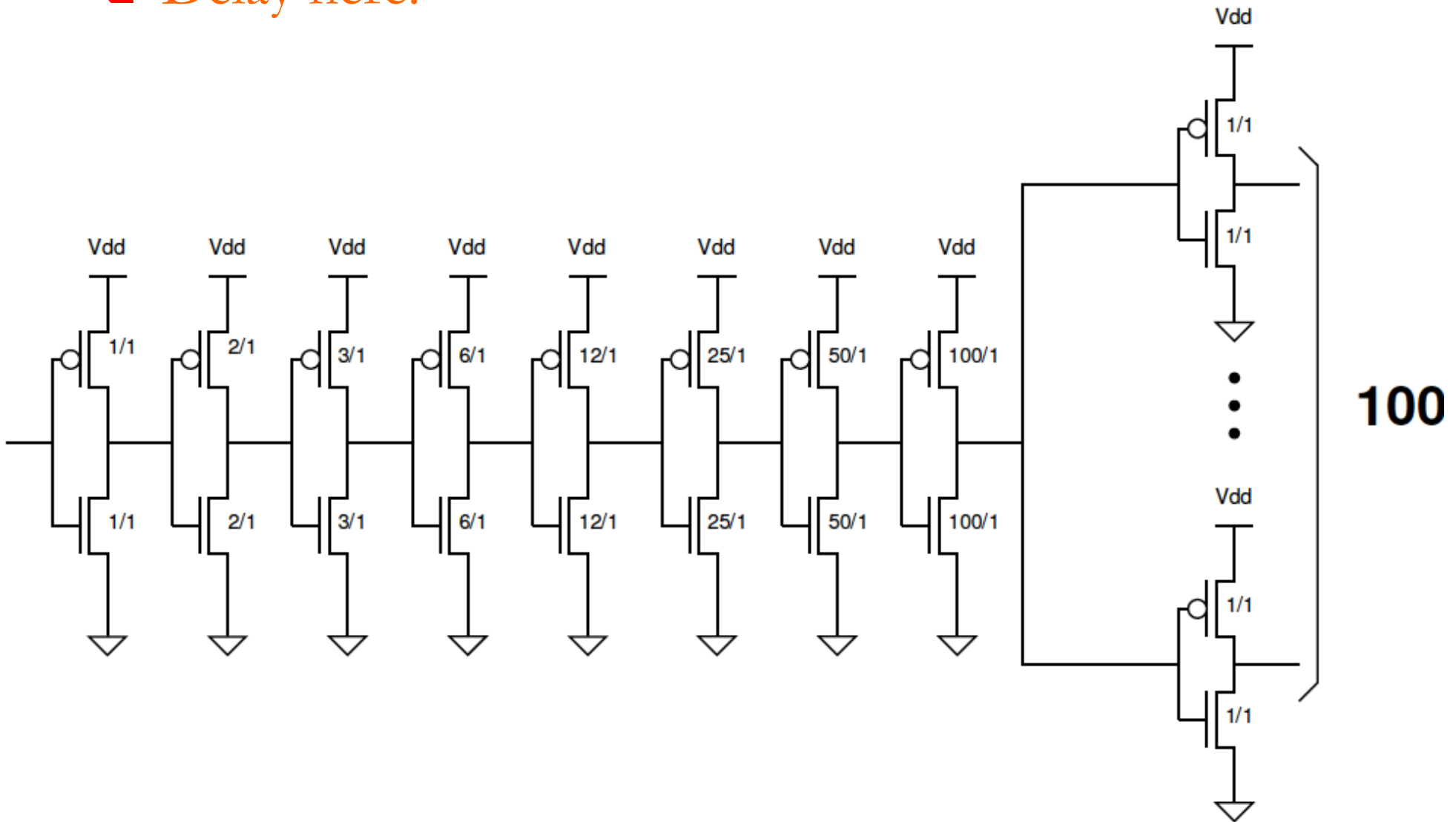



Delay Summary

    





Lesson

- ❑ Don't drive large fanout with a single stage
- ❑ Must scale up over a number of stages
- ❑ ...but not too many
- ❑ Exact number will be technology dependent


Capacitance Reminder

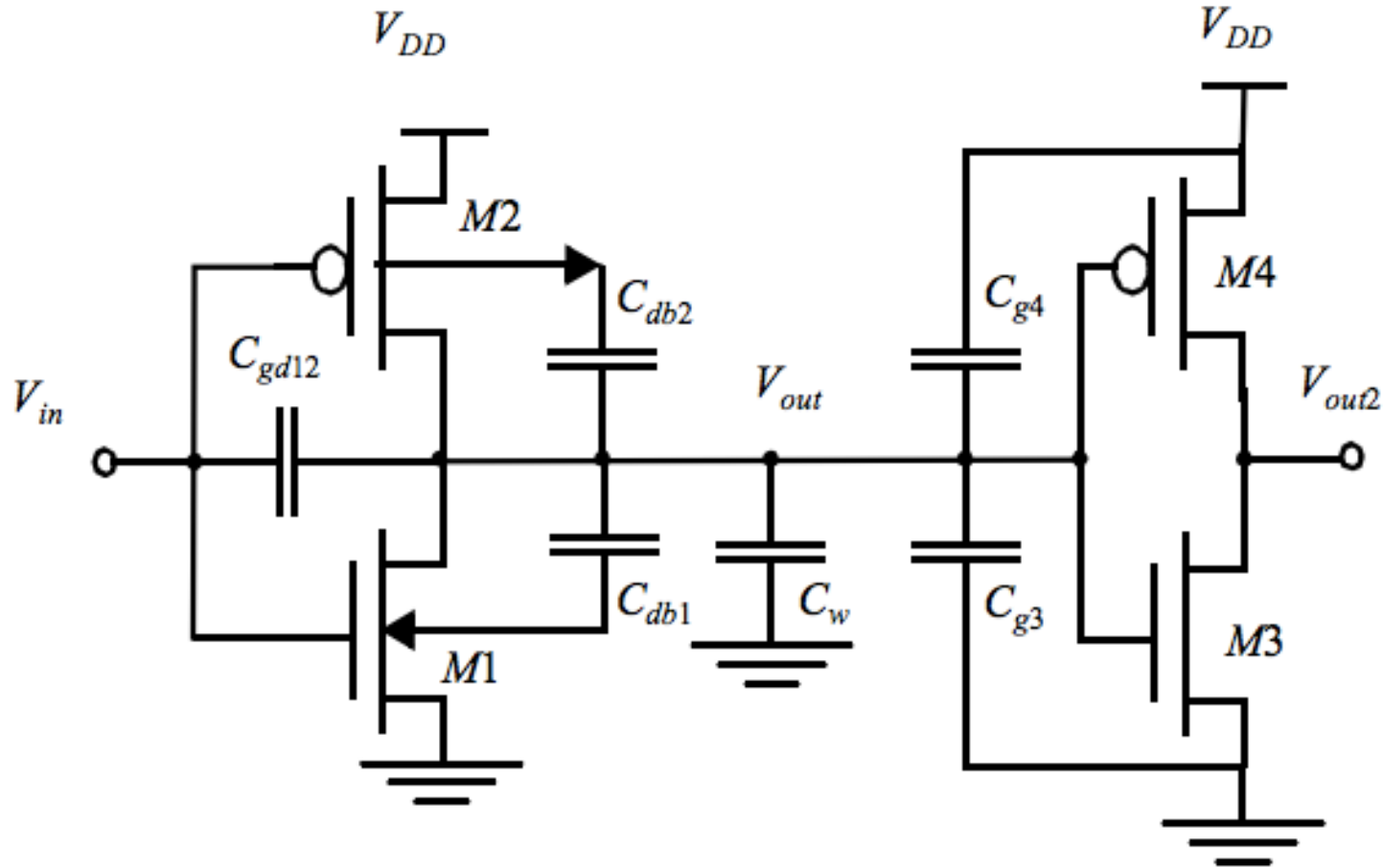

Charge on Capacitors (preclass 6)

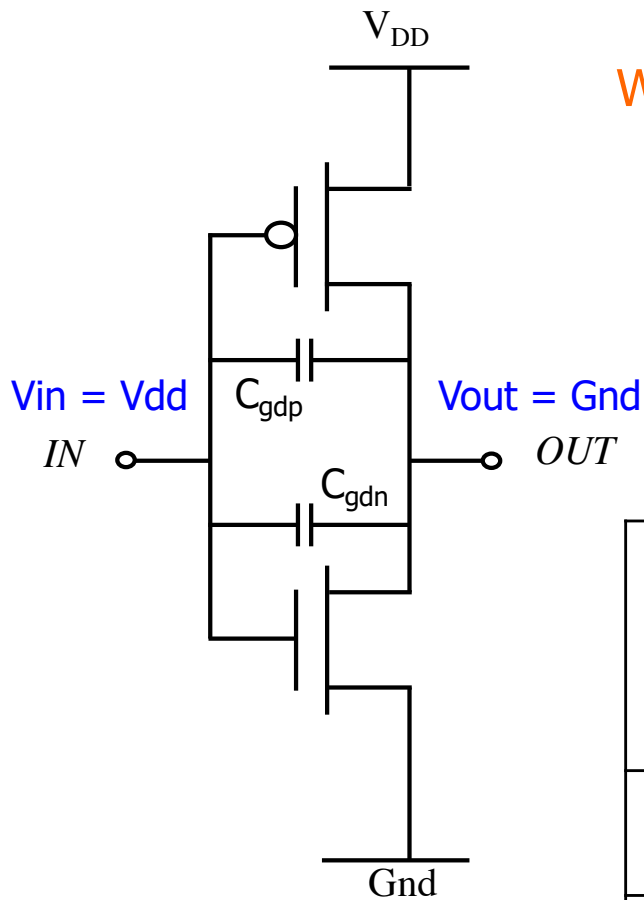

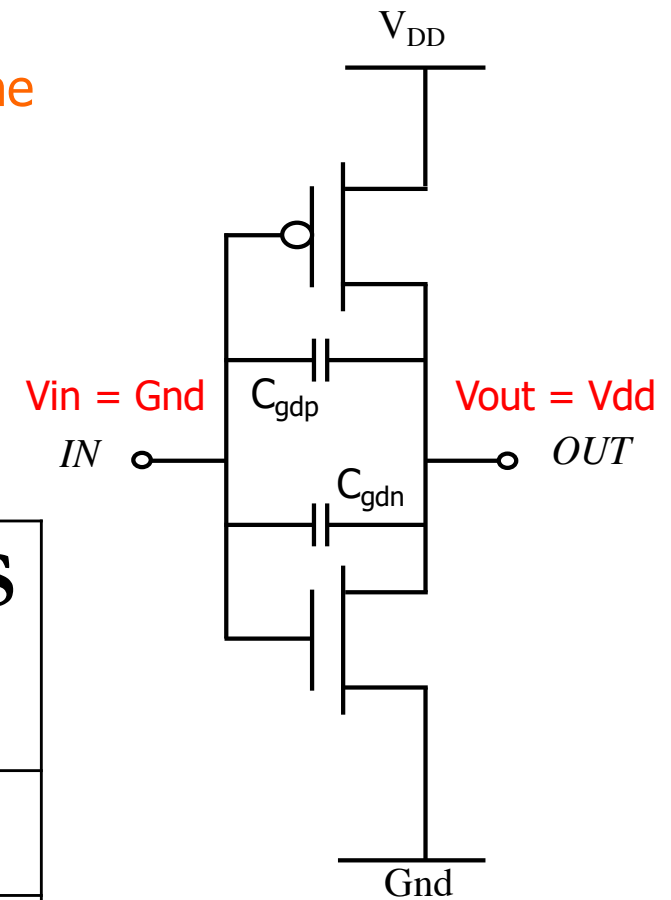What is charge, Q , on each of the capacitors when $V_{in} = V_{DD}$ and $V_{in} = Gnd$?



	PMOS	NMOS
V_{in}	C_{gdp}	C_{gdn}
V_{DD}		
Gnd		


Questions

- What is ΔQ on each C_{gd} when input switched?
- Assuming $\Delta V = V_{dd}$, what is equivalent capacitance?


	PMOS	NMOS
Vin	C_{gdp}	C_{gdn}
Vdd		
Gnd		

Miller Effect For an Inverter

 - ❑ Feedback capacitance (C_{gd}) between input and output must swing $2 V_{dd}$
- ❑ Or...behaves same as a double-sized capacitor on the output



Miller Effect For an Inverter

 

“A capacitor experiencing identical but opposite voltage swings at both its terminals can be replaced by a capacitor to ground, whose value is two times the original value.”



Ideas

- ❑ First order delay reason in $\tau = R_0 C_0$ units
- ❑ Scaling everything up doesn't help
- ❑ Drive large capacitive loads in stages
 - But not too many



Admin

- ❑ HW4 due Friday

- ❑ Drop date is on Monday
 - Email me if you want to talk about your standing in the class