


Let:

- R_0 – equivalent resistance of minimum size ($W = L = 1$) NMOS transistor
- I_0 – equivalent current of minimum size ($W = L = 1$) NMOS transistor
- C_0 – gate capacitance of minimum size transistor
- $\tau = R_0C_0$ – technology-specific delay unit (maybe more accurate today $\tau = C_0/I_0$)

1. What are I_{ds} , R , and C in terms of I_0 , R_0 , and C_0 for a transistor with width W :

R_{drive}	
I_{drive}	
C_{gate}	

2. How size for equal rise/fall times assuming $\mu_n=500 \text{ cm}^2/(V \cdot s)$ and $\mu_p=200 \text{ cm}^2/(V \cdot s)$, velocity saturated, and $|V_{Tp}| = |V_{Tn}|$ and targeting $R_{drive} = \frac{R_0}{2}$.

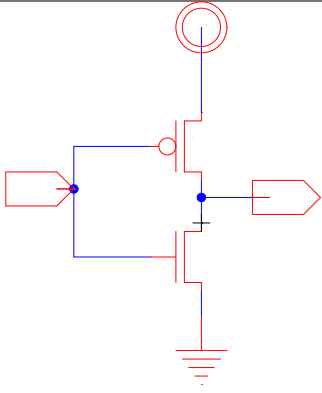	W_p	W_n	C_{in} in multiples of C_0
			



3. What is the delay in τ units?

	Delay


4. How should we size the transistors in middle stage?

	W_p	W_n	Delay in τ

5. What is the delay in τ units?

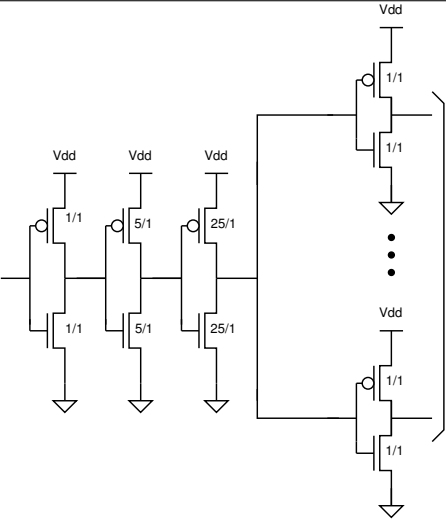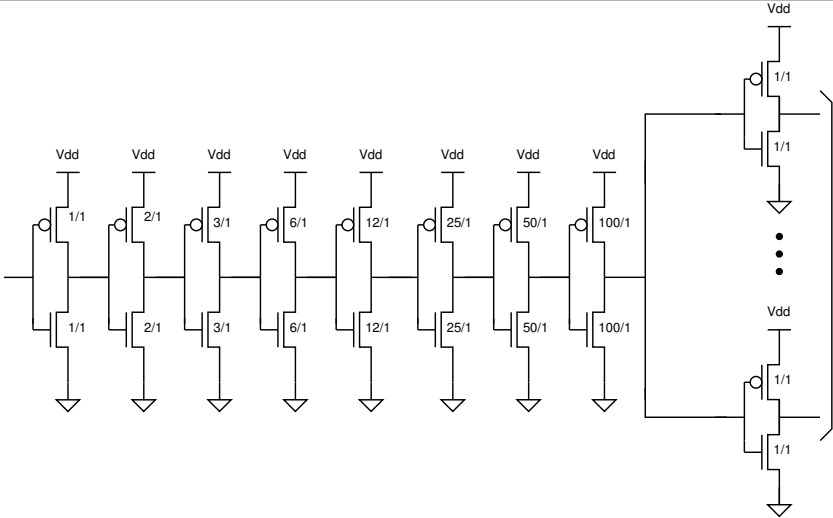	Delay
	
	

6. Identify charges and capacitances:

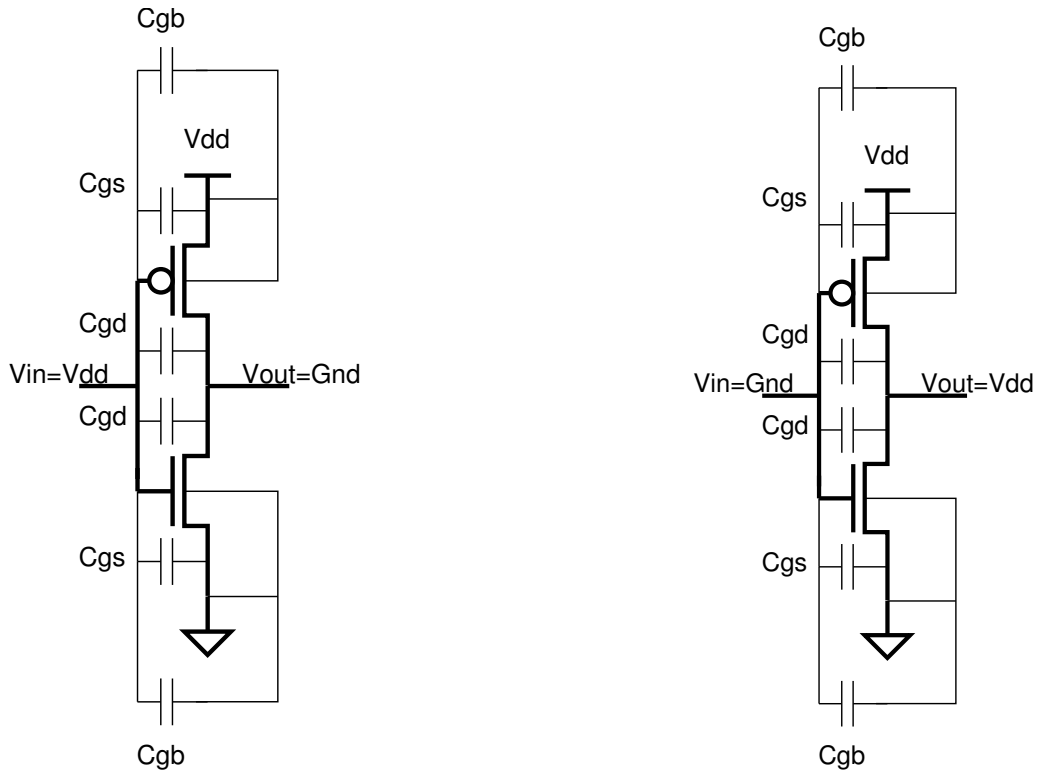

(a) What is charge, Q , on each of the capacitors when $V_{in} = V_{dd}$ and $V_{in} = Gnd$? Pay careful attention to polarities. ($Q_{ab} = -Q_{ba}$)

V_{in}	PMOS			NMOS		
	C_{gd}	C_{gb}	C_{gs}	C_{gd}	C_{gb}	C_{gs}
V_{dd}						
Gnd						

(b) What is the total ΔQ on each C_{gd} when V_{in} switches from V_{dd} to Gnd ? (and vice versa)

(c) Assuming $\Delta V = V_{dd}$, what is the equivalent capacitance switched?