
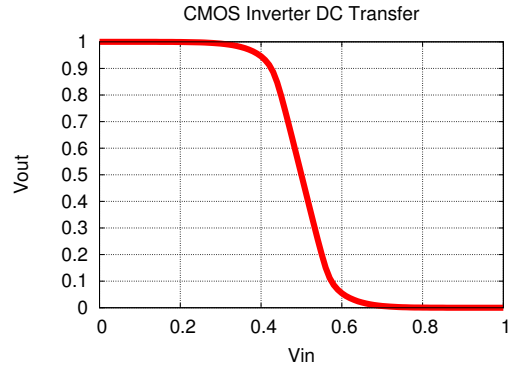


Device	$V_{gs}$	$I_d$
NMOS	$V_{gs} < V_{thn}$	$(3 \times 10^{-7}) e^{\frac{V_{gs} - V_{thn}}{40mV}}$
	$V_{gs} > V_{thn}$	$1.8 \times 10^{-4} (V_{gs} - V_{thn})$
PMOS	$V_{gs} > V_{thp}$	$(3 \times 10^{-7}) e^{-\left(\frac{V_{gs} - V_{thp}}{40mV}\right)}$
	$V_{gs} < V_{thp}$	$-1.8 \times 10^{-4} (V_{gs} - V_{thp})$

Consider an inverter:

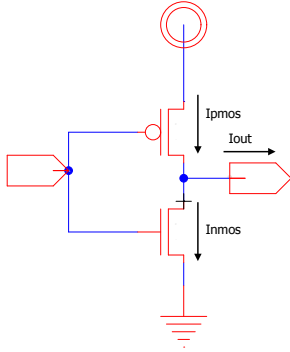

Useful:  $e^{-1} \approx 0.37$ ,  $e^{-4} \approx 0.02$ ,  $e^{-7.5} \approx 6 \times 10^{-4}$



- $V_{dd}=1V$ ,  $V_{thn}=300mV$ ,  $V_{thp}=-300mV$ .

$V_{in}$	$I_{pmos}$	$I_{nmos}$	$\approx I_{pwr,gnd}$	
0V				A
140mV				B
400mV				C
500mV				D
600mV				E
860mV				F
1V				G

Approximate  $I_{pwr,gnd} \approx \min(I_{nmos}, I_{pmos})$ .

Device	$V_{gs}$	$V_{ds}$	$I_d$
NMOS	$V_{gs} < V_{thn}$	any	$(3 \times 10^{-7}) e^{\frac{V_{gs}-V_{thn}}{40mV}}$
	$V_{gs} > V_{thn}$	$V_{ds} < V_{gs} - V_{thn}$	$3.6 \times 10^{-4} (V_{gs} - V_{thn}) \times V_{ds}$
		$V_{ds} > V_{gs} - V_{thn}$	$1.8 \times 10^{-4} (V_{gs} - V_{thn})$
PMOS	$V_{gs} > V_{thp}$	any	$(3 \times 10^{-7}) e^{-\left(\frac{V_{gs}-V_{thp}}{40mV}\right)}$
	$V_{gs} < V_{thp}$	$V_{ds} > V_{gs} - V_{thp}$	$-3.6 \times 10^{-4} (V_{gs} - V_{thp}) \times V_{ds}$
		$V_{ds} < V_{gs} - V_{thp}$	$-1.8 \times 10^{-4} (V_{gs} - V_{thp})$

Consider an inverter:

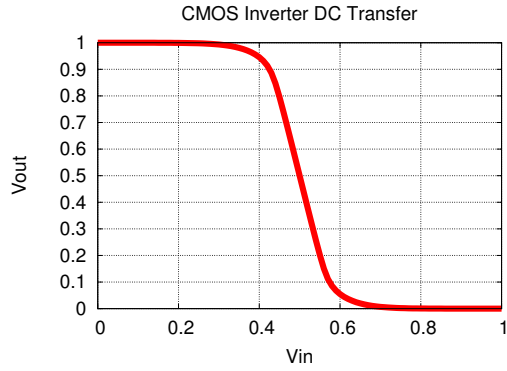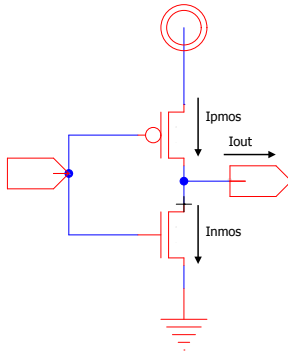

Useful:  $e^{-1} \approx 0.37$ ,  $e^{-4} \approx 0.02$ ,  $e^{-7.5} \approx 6 \times 10^{-4}$

2.  $V_{dd}=1V$ ,  $V_{thn}=300mV$ ,  $V_{thp}=-300mV$ , assume steady-state operation at  $V_{in}$  given.

$V_{in}$	$I_{pmos} = I_{nmos} = I_{pwr,gnd}$	Vout	
0V			A
140mV			B
400mV			C
500mV			D
600mV			E
860mV			F
1V			G

Approximate  $I_{pwr,gnd} \approx \min(I_{nmos}, I_{pmos})$ .