

# ESE370: Circuit-Level Modeling, Design, and Optimization for Digital Systems

---

Lec 17: October 18, 2021

Energy Optimization

Ratioed Logic



# Today

---

- Energy Tradeoffs
  - Reduce dynamic power
  
- Ratioed Logic
  - Break all the rules... (lose our nice properties)
    - Not rail-to-rail signals, steady-state-current...
  - Correctness



# Previously

---

- Three components of power

- $P_{tot} = P_{static} + P_{dyn} + P_{sc}$

- $P_{tot} \approx a(C_{load} + 2C_{sc})V^2f + VI'_s(W/L)e^{-V_t/(nkT/q)}$

# Reminder:

- $V_{dd}=1V$ ,  $V_{thn}=|V_{thp}|=300mV$

$V_{in}$	$I_{static}$	$I_{dynamic}$	$I_{sc}$
0V	180pA	126uA	
140mV	6nA	100uA	
400mV		36uA	18uA
500mV			36uA
600mV		36uA	18uA
860mV	6nA	100uA	
1V	180pA	126uA	



# Reduce $V_{dd}$

---

- What happens as reduce  $V$ ?
  - Energy?
    - Static
    - Switching
  - Delay?

# Reduce $V_{dd}$ (Preclass 2)

□  $V_{dd}=520\text{mV}$ ,  $V_{thn} = |V_{thp}| = 300\text{mV}$

$V_{in}$	$I_{static}$	$I_{dynamic}$	$I_{sc}$
0V			
140mV			
260mV			
380mV			
520mV			


# Reduce $V_{dd}$ (Preclass 2)

□  $V_{dd}=520\text{mV}$ ,  $V_{thn} = |V_{thp}| = 300\text{mV}$

$V_{in}$	$I_{static}$	$I_{dynamic}$	$I_{sc}$
0V	180pA	39.6uA	
140mV	6nA	14.4uA	
260mV	111nA		
380mV	6nA	14.4uA	
520mV	180pA	39.6uA	
 
# Reduce $V$ (no velocity saturation)

- ❑  $\tau_{gd} = Q/I = (CV)/I$
- ❑  $I_d = (\mu C_{OX}/2)(W/L)(V_{gs} - V_{TH})^2$
- ❑  $\tau_{gd}$  impact?
- ❑  $\tau_{gd} \propto \frac{1}{V}$





# Reduce $V$ (no velocity saturation)


- ❑  $\tau_{gd} = Q/I = (CV)/I$
- ❑  $I_d = (\mu C_{OX}/2)(W/L)(V_{gs} - V_{TH})^2$
- ❑  $\tau_{gd}$  impact?

- ❑  $\tau_{gd} \propto \frac{1}{V}$

- ❑ Ignoring leakage:



$$E \propto V^2$$

$$E\tau^2 \approx Const$$

 
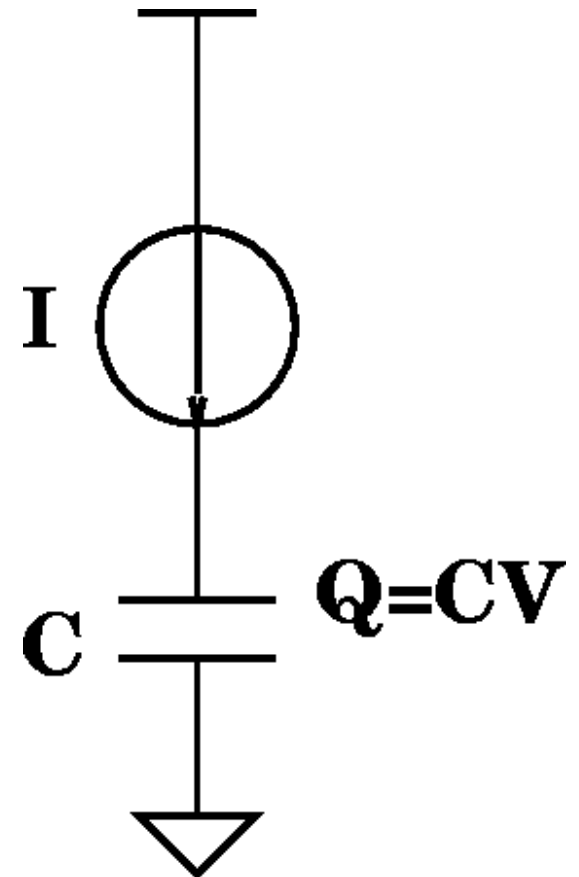 
# Reduce $V$ (velocity saturation)

- ❑  $\tau_{gd} = Q/I = (CV)/I$
- ❑  $I_d = (v_{sat} C_{OX})(W)(V_{gs} - V_{TH} - V_{DSAT}/2)$



# Reduce $V_{dd}$ (Preclass 3)

- $V_{thn} = |V_{thp}| = 300\text{mV}$ ,  $V_{in} = V_{dd}$ , estimate  $E\tau$

$V_{dd}$	$I_{dyn}$	$\tau / (\tau @ V_{dd}=1)$	$E_{switch} / (E_{switch} @ V_{d}=1)$	$E\tau$
1V		1	1	1
700mV				
500mV				
350mV				
260mV				




# Increase $V_{th}$ ?

---

- What is impact of increasing threshold on
  - Delay?
  - Leakage?
 
# Increase $V_{th}$

- $\tau_{gd} = Q/I = (CV)/I$
- $I_{ds} = (v_{sat} C_{OX})(W)(V_{gs} - V_{TH} - V_{DSAT}/2)$



# Increase $V_{th}$ (Preclass 4)

- What is impact of increasing threshold on
  - Delay?
  - Leakage?
- $V_{dd}=1V, V_{in}=V_{dd}$

$V_{thn} = -V_{thp}$	$I_{dyn}$	$\tau / (\tau @ V_{th} = 300mV)$	$I_{static}$	$I_{stat} / (I_{stat} @ V_{th} = 300mV)$
300mV		1		1
460mV				
600mV				



# Idea

---

- Tradeoff (knobs:  $V_{dd}$ ,  $V_{th}$ ,  $a$ , etc.)
  - Speed
  - Switching energy
  - Leakage energy
- Energy-Delay tradeoff:  $E\tau^2$ ,  $E\tau$

# Ratioed Logic

---





# Previously

---

- ❑ Restoration and Noise Margins
  - Allows for gate abstraction
- ❑ CMOS Gates
  - Drive outputs rail-to-rail
  - Only one PDN/PUN turned on in steady state
    - Only subthreshold leakage current in steady state



# Today


---

## □ Ratioed Gates

- Break all the rules... (nice properties)
  - No rail-to-rail outputs, steady-state-current is not subthreshold...
- Logic correctness
- Performance
- Power implications

 
# Idea

- ❑ Building both pull-up and pull-down can be expensive – many gates
- ❑ Seems wasteful to build logic function twice
  - Once in pullup, once in pulldown
  - Large gate capacitance



 
# Idea

- ❑ Maybe only need to build one
- ❑ Build NFET pulldown
  - Exploit high N mobility
    - traditional



 
# Ratioed Inverter

- Does this work?
  - What is  $V_{out}$  for  $V_{in} = Gnd$  ?
  - What is  $V_{out}$  for  $V_{in} = V_{dd}$  ?




# Ratioed Inverter in 22nm

 

 
# Ratioed Inverter (Preclass 5)

- How do we need to size N to make it “work”?
  - $V_{DD}=0.8$




# Ratioed Inverter in 22nm

 






# DC Transfer Function

 




# DC Transfer Function

 

 
# Ratioed Inverter (Preclass 5)


- How do we need to size P to make it work?
  - $V_{DD}=0.8$



# Ratioed Inverter in 22nm

 



# Ratioed Inverter in 22nm

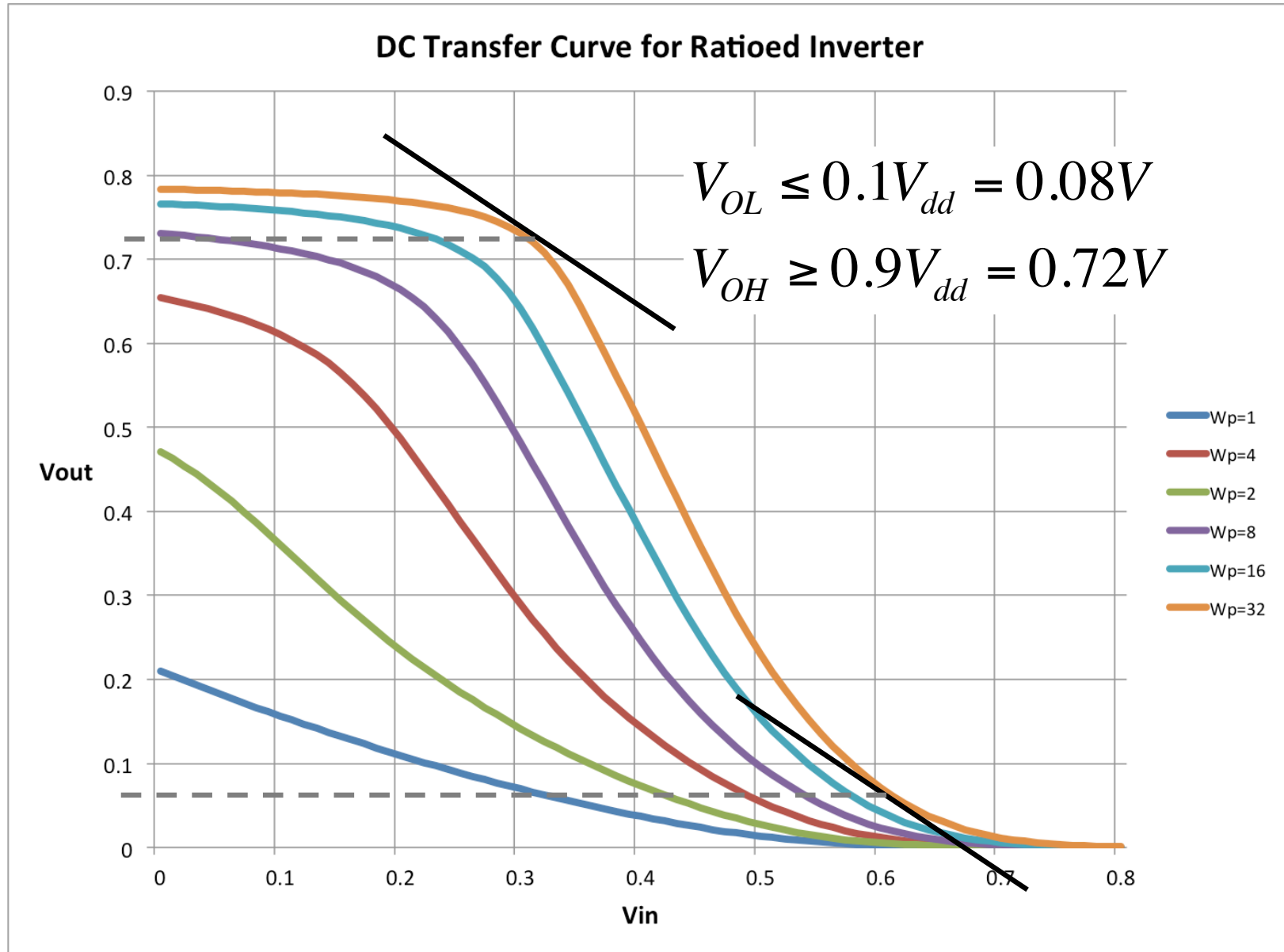


  
# P vs. N



❑ **Conclude:** still prefer N to P for ratioed logic



# Noise Margin Tradeoff


□ What is impact of increasing noise margin?

- On size
- On input capacitance

  
 
# Size for $R_0/2$ drive?


- How do we size for  $R_0/2$  drive?
  - (assume  $R_{0p} = R_{0n}$  for CMOS)




 
# Static Power

- $I_{\text{static}}$  ?
- Input low-Output high?
  - $I_{\text{leak}}$
- Input high-Output low?
  - $I_{\text{pmos\_on}}$
  - $\sim V_{\text{dd}} / (R_0 / 2)$  -- for our sample case





# Total Power

---

□  $P_{\text{tot}} \approx a(C_{\text{load}} + 2C_{\text{sc}})V^2f$



# Total Power

---

$$\begin{aligned} \square P_{\text{tot}} &\approx a(C_{\text{load}} + 2C_{\text{sc}})V^2f \\ &\quad + p(V_{\text{out}}=\text{low})V^2/R_{\text{pon}} \\ &\quad + p(V_{\text{out}}=\text{high})VI'_s(W/L)e^{-V_t/(nkT/q)} \end{aligned}$$

$p(V_{\text{out}}=\text{low})$  – probability the output is low

$p(V_{\text{out}}=\text{high})$  – probability the output is high

$$p(V_{\text{out}}=\text{high}) = 1 - p(V_{\text{out}}=\text{low})$$



# Compare Static CMOS


---

For  $R_{\text{drive}} = R_0/2$  inverter (assume  $R_{0p} = R_{0n}$  for CMOS)

- ❑ Total Transistor Width?
- ❑ Input capacitance load?


# How do we size for $R_0/2$ drive?

- 2-input nand?

 


# How do we size for $R_0/2$ drive?

- 2-input nor?


 

 
# How do we size for $R_0/2$ drive?

- ❑ k-input nor?
- ❑ What is the input capacitance for k-input nor?


  
# Which Implementation is faster in ratioed logic?







# Ideas

---

- ❑ There are other logic disciplines
- ❑ You have the tools to analyze
- ❑ Ratioed Logic
  - Tradeoff noise margin for
    - Reduced area? Capacitive load?
  - Dissipates non-leakage static power in one input case



# Admin

---

- ❑ Project 1 out now
  - Milestone due Friday (10/22)
    - Baseline is bare minimum, but can start thinking/working on optimizations before
    - Will give you feedback by Sunday morning
  - Design 8-bit ripple-carry adder
    - You already know how to do this
    - Refresh yourself on binary addition of 2 bits
  - Work **individually**
  - Full Report in two weeks (F 10/29)