
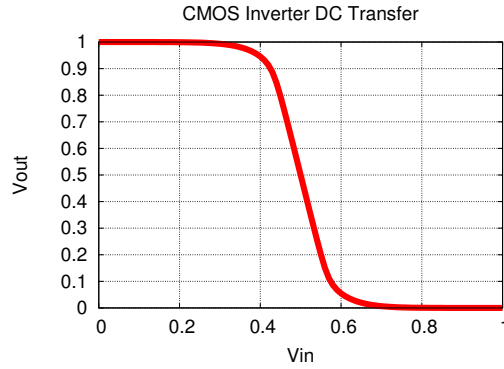


Device	$V_{gs}$	$I_d$
NMOS	$V_{gs} < V_{thn}$	$(3 \times 10^{-7}) e^{\frac{V_{gs} - V_{thn}}{40mV}}$
	$V_{gs} > V_{thn}$	$1.8 \times 10^{-4} (V_{gs} - V_{thn})$
PMOS	$V_{gs} > V_{thp}$	$(3 \times 10^{-7}) e^{-\left(\frac{V_{gs} - V_{thp}}{40mV}\right)}$
	$V_{gs} < V_{thp}$	$-1.8 \times 10^{-4} (V_{gs} - V_{thp})$

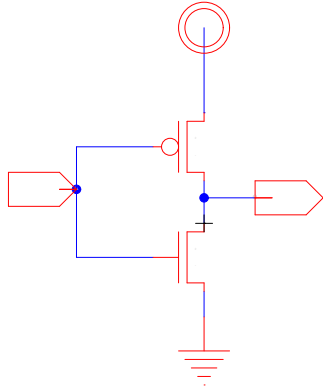Consider an inverter using the pmos and nmos devices described above:



Useful:  $e^{-1} \approx 0.37$ ,  $e^{-4} \approx 0.02$ ,  $e^{-7.5} \approx 6 \times 10^{-4}$ ,

- $V_{dd}=1V$ ,  $V_{thn}=300mV$ ,  $V_{thp}=-300mV$ , assume the static current is in steady-state operation and dynamic/short circuit current are the peak currents at  $V_{in}$  given.

$V_{in}$	$I_{static}$	$I_{dynamic}$	$I_{sc}$	
0V	180pA	126μA	0	A
140mV	6nA	100μA	0	B
400mV	0	36μA	18μA	C
500mV	0	0	36μA	D
600mV	0	36μA	18μA	E
860mV	6nA	100μA	0	F
1V	180pA	126μA	0	G

- $V_{dd}=520mV$ ,  $V_{thn}=300mV$ ,  $V_{thp}=-300mV$ , assume gate is unloaded (no output capacitance to charge).

$V_{in}$	$I_{static}$	$I_{dynamic}$	$I_{sc}$	
0V				A, F
140mV				B, G
260mV				C
380mV				D
520mV				E

Device	$V_{gs}$	$I_d$
NMOS	$V_{gs} < V_{thn}$	$(3 \times 10^{-7}) e^{\frac{V_{gs}-V_{thn}}{40mV}}$
	$V_{gs} > V_{thn}$	$1.8 \times 10^{-4} (V_{gs} - V_{thn})$
PMOS	$V_{gs} > V_{thp}$	$(3 \times 10^{-7}) e^{-\left(\frac{V_{gs}-V_{thp}}{40mV}\right)}$
	$V_{gs} < V_{thp}$	$-1.8 \times 10^{-4} (V_{gs} - V_{thp})$

Useful:  $e^{-1} \approx 0.37$ ,  $e^{-4} \approx 0.02$ ,  $e^{-7.5} \approx 6 \times 10^{-4}$ ,

3.  $V_{thn}=300mV$ ,  $V_{thp}=-300mV$ ,  $V_{in}=V_{dd}$ ; estimate  $\tau = CV/I$


$V_{dd}$	$I_{dyn}$	$\frac{\tau}{\tau(V_{dd}=1V)}$	$\frac{E_{switch}}{E_{switch}(V_{dd}=1V)}$	$E\tau$
1V		1	1	1
700mV				
500mV				
350mV				
260mV				

all  
A, E  
B, F  
C, G  
D



4.  $V_{dd}=1V$ ,  $V_{in}=V_{dd}$

$V_{thn} = -V_{thp}$	$I_{dyn}$	$\frac{\tau}{\tau( V_{th} =300mV)}$	$I_{static}$	$\frac{I_{static}}{I_{static}( V_{th} =300mV)}$
300mV		1		1
460mV				
600mV				


all  
A, B, C  
D, E, F, G

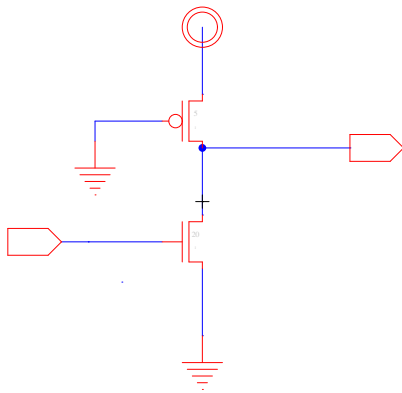

$W_p = 1$

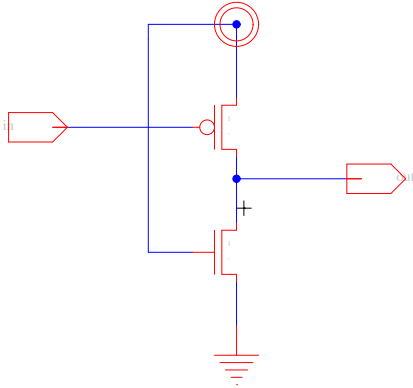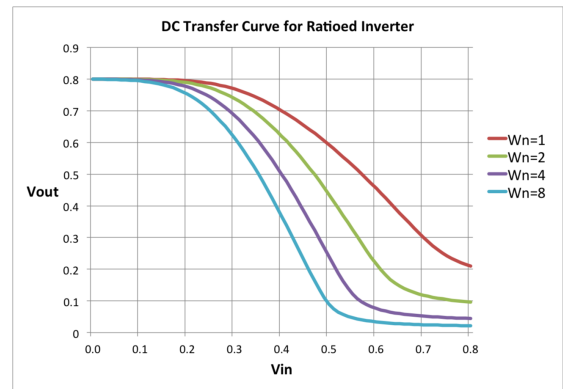

$W_n = 1$

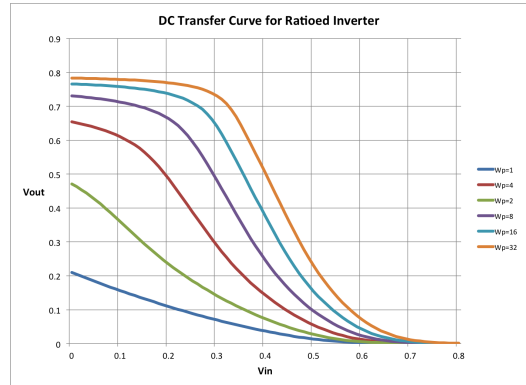

5. Size  $W_n$  or  $W_p$  for correct operation with  $V_{ol} \leq 0.1V_{dd}$  and  $V_{oh} \geq 0.9V_{dd}$ , where  $V_{dd} = 0.8$ . Assume extreme velocity saturation,  $R_{0p} = R_{0n}$ .

	$W_p$	$W_n$	$C_{in}$ in multiples of $C_0$
	1		
		1	