

ESE370: Circuit-Level Modeling, Design, and Optimization for Digital Systems

Lec 19: October 22, 2021
Design Space Exploration (con't)
Pass Transistor Logic

Design Space Exploration



Design Problem

- ❑ Function: Identify equivalence of two 32bit inputs
- ❑ Optimize: Minimize total energy
- ❑ Assumptions: Match case uncommon
 - Ie. Most of the time, the inputs won't be matched

- ❑ Deliberately focus on Energy to complement project
 - ...but will still talk about delay




Design Space Dimensions

- Topology
 - (A) Gate choice, logical optimization
 - (B) Fanin, fanout,
 - (C) Serial vs. parallel
 - Chain vs. tree
- Gate style / logic family
 - (D) CMOS, Ratioed (N load, P load), Pass (coming soon)
- (E) Transistor Sizing
- (F) V_{dd}
- (G) V_{th}


Gate Choice

- (A) What gates might we build?

 


Gate Choice

- (A) What gates might we build?

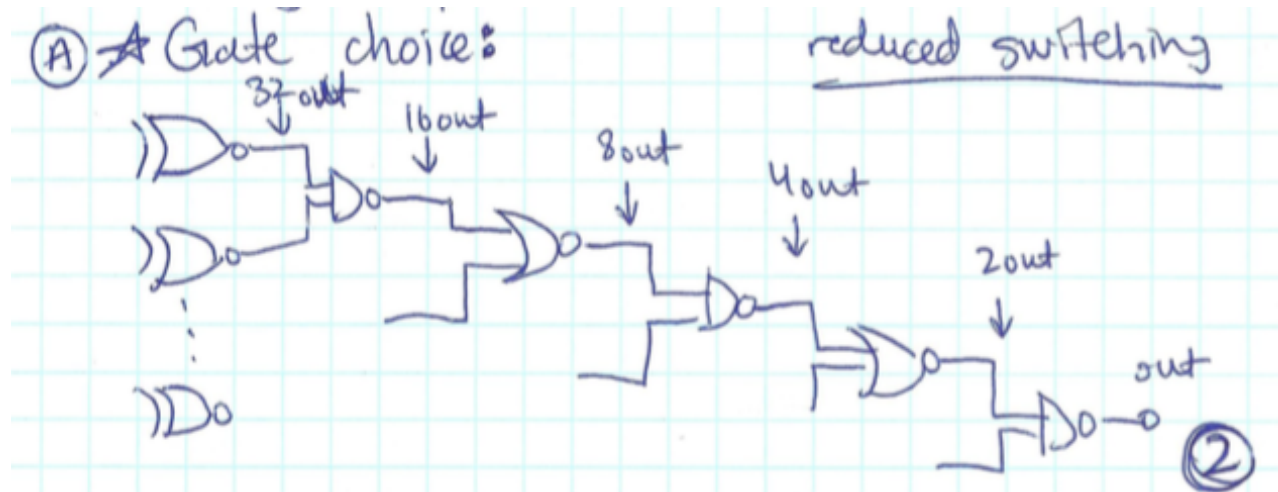


Gate Fan-in

□ (B) High fan-in?

 

Gate Topology

□ (C) Serial-Parallel?

 

(D) Logic Family

- ❑ Considerations for each logic family?
 - CMOS
 - Ratioed with PMOS load
 - Ratioed with NMOS load

- ❑ Ratioed Logic
 - Reduced C_{loads} result in lower switching power (P_{dyn} ↓)
 - Increased static power



(E) Sizing

- How do we want to size gates?
 - Sizing transistors up will reduce delay →
 - Reduces short circuit power

$$E = V_{dd} \times \left(I_{peak} \times t_{sc} \times \left(\frac{1}{2} \right) \right)$$

- Increases dynamic power

(F) Reduce Vdd

□ What happens as reduce V?

■ Energy?

■ Dynamic ↓

■ Static ↓

■ Switching Delay? ↑


▪ $\tau_{gd} = Q/I = (CV)/I$

▪ $I_d = (\mu C_{OX}/2)(W/L)(V_{gs} - V_{TH})^2$

▪ τ_{gd} impact?

▪ $\tau_{gd} \propto 1/V$

▪ Limit on Vdd?

 


(G) Increase V_{th} ?

□ What is impact of increasing threshold on

- Dynamic Energy? ↓
- Leakage Energy? ↓
- Delay? ↑

 - $\tau_{gd} = Q/I = (CV)/I$
- $I_{ds} = (v_{sat} C_{OX})(W)(V_{gs} - V_{TH} - V_{DSAT}/2)$






Ideas

- ❑ We know many things we can do to our circuits
- ❑ Design space is large
- ❑ Systematically identify dimensions
- ❑ Identify continuum (trends) tuning when possible
- ❑ Watch tradeoffs
 - ...don't over-tune

Pass Transistor Logic


Pass Transistor Logic (Preclass 1)

□ What does this do?

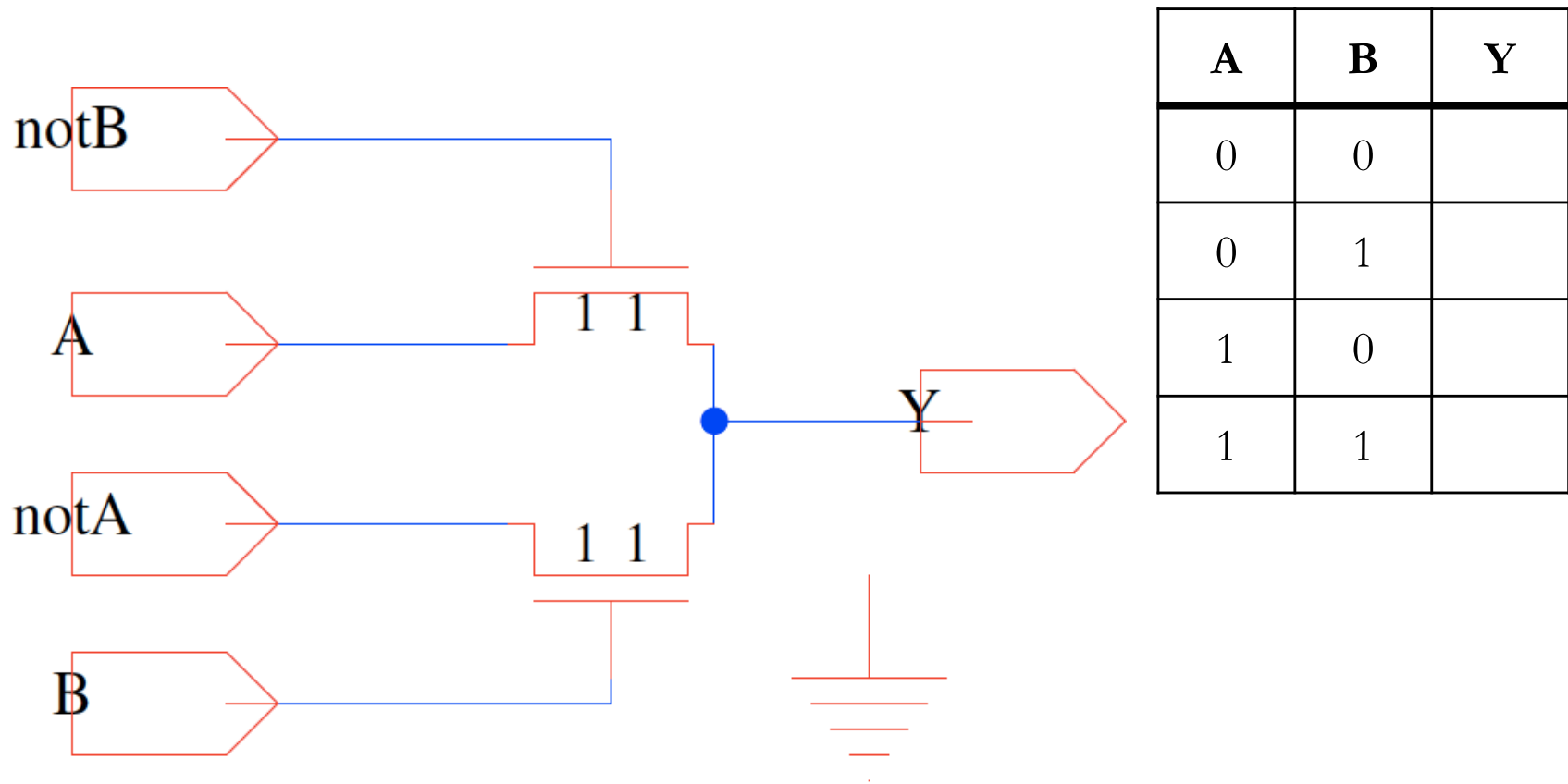


Identify Function (Preclass 2)

□ What function is this?

 


Area

□ Compare PT with CMOS circuit?

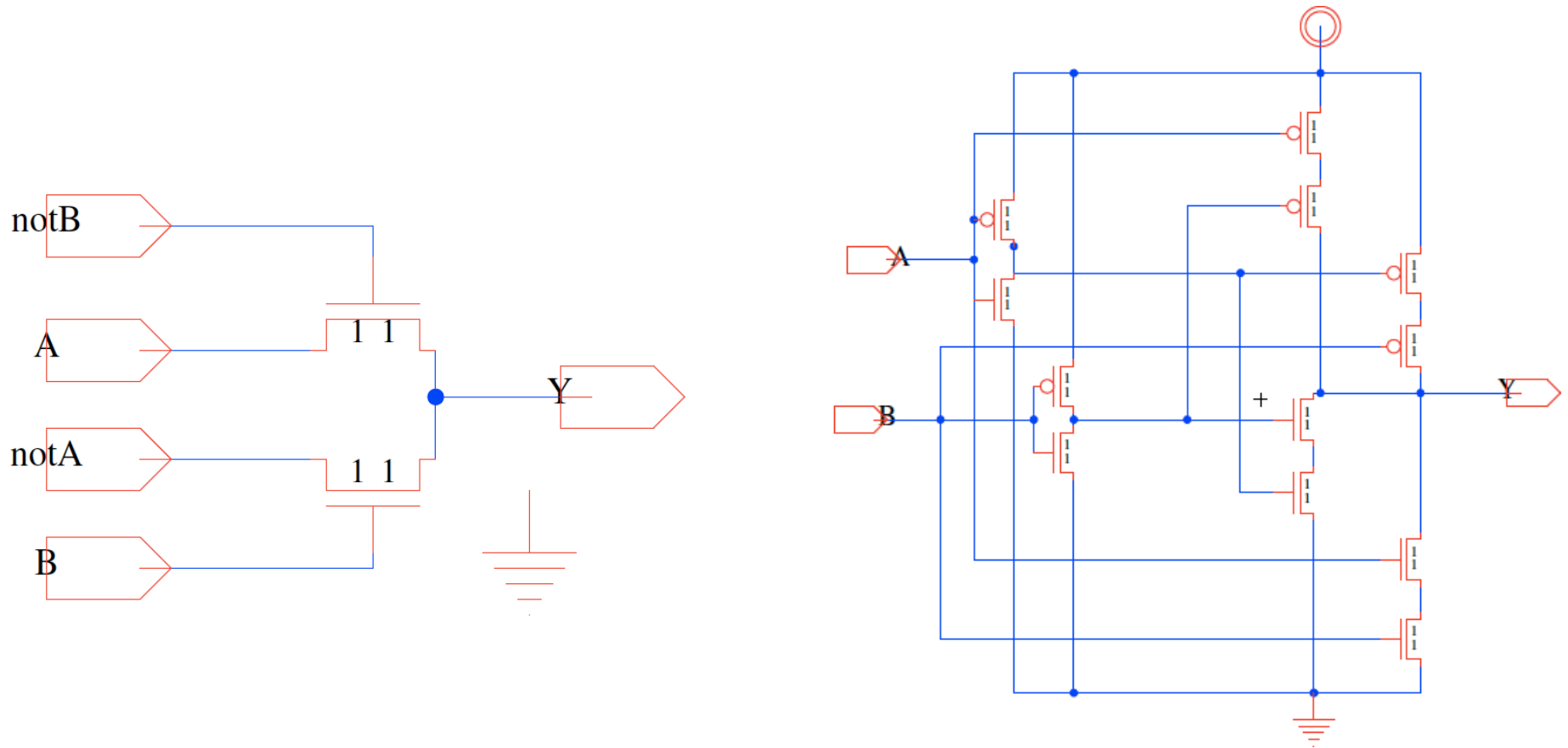


Output

□ Is this a regenerating/restoring gate?

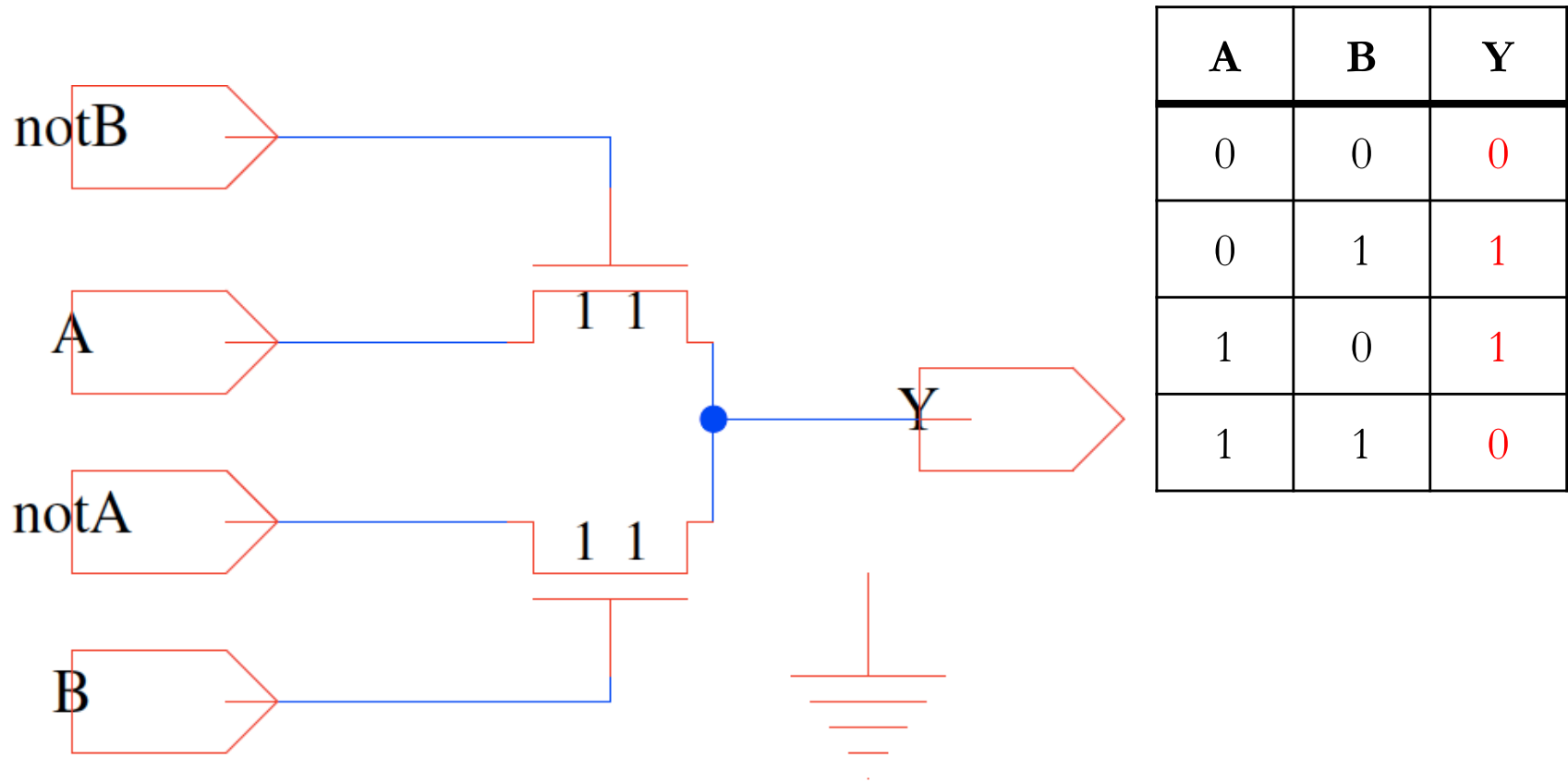


Output

 
- What does output look like (DC transfer)?
 - (B=1, notB=0, sweep A, notA=CMOS inv(A))



Pass TR transfer (B=1)

 


 
*** spice deck for cell test_passtr_xor2{sch} from library test






XOR Output

Reasonable Input to CMOS Inverter?

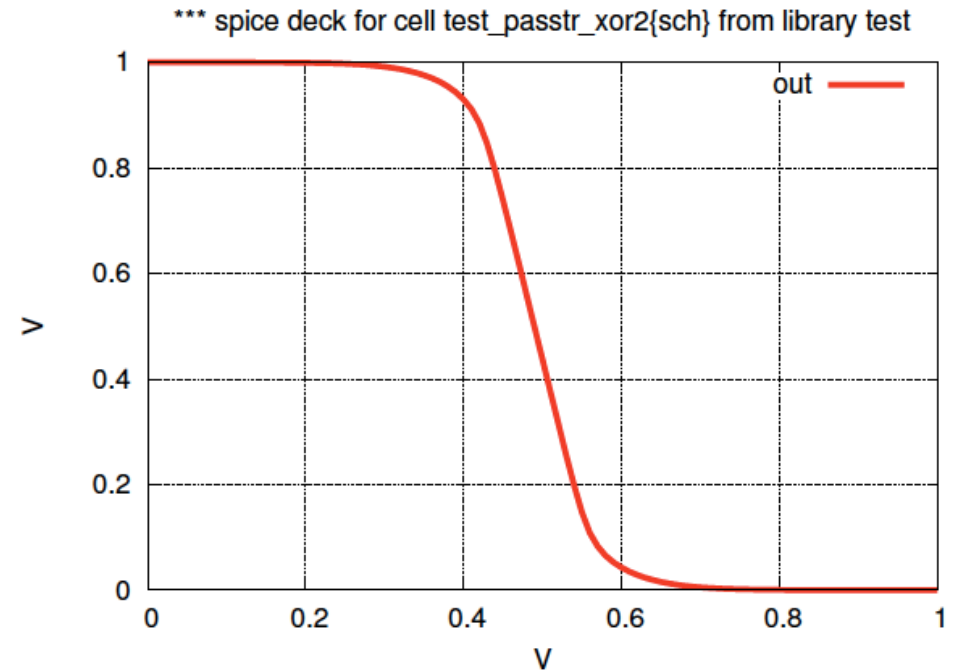 

Pass Transistor xor2 with inv restore

 




Required to use?

- ❑ What should we add to make suitable comparison with CMOS?



Restore Output

 - What should we add to make suitable comparison with CMOS?




Restore Output

- Area? (compare to CMOS)

  




Chain Together

 


Analyze Stage

 

Impact of Capacitance

 - ❑ $C_{GS} = C_{GCS} + C_{GSO}$
- ❑ $C_{GD} = C_{GCD} + C_{GDO}$
- ❑ $C_{GB} = C_{GCB}$
- ❑ $C_{SB} = C_{diff}$
- ❑ $C_{DB} = C_{diff}$




Contact/Diffusion Capacitance

- C_j – diffusion depletion
- C_{jsw} – sidewall capacitance
- L_S – length of diffusion


$$C_{diff} = C_j L_S W + C_{jsw} (2L_S + W)$$

Define: $C_{diff0} \approx \gamma C_0$
 
$$C_{diff} \approx WC_{diff0} = W \cdot \gamma C_0$$



First Order Model

 

□ Switch


- Loads **all terminals** capacitively
 - Draw no steady-state current for a CMOS gate
 - Does not impact steady-state output voltage
 - Impacts Settling time/Delay
- Has finite drive strength
 - Could form voltage divider with resistive load
 - Impacts Settling time/Delay

First Order Delay



- R_0 = Resistance of minimum size NMOS device
- C_0 = gate capacitance of minimum size NMOS device
- C_{diff0} = diffusion capacitance on minimum size NMOS
 - $C_{diff0} = \gamma C_0$
- $R_{drive} = R_0/W$
- $C_g = WC_0$
- $C_{diff} = WC_{diff0} = \gamma WC_0$

Inverter Delay

 - Delay driving another (min size) inverter?
 - Include $C_{\text{diff}} = \gamma C_g = \gamma W C_0$




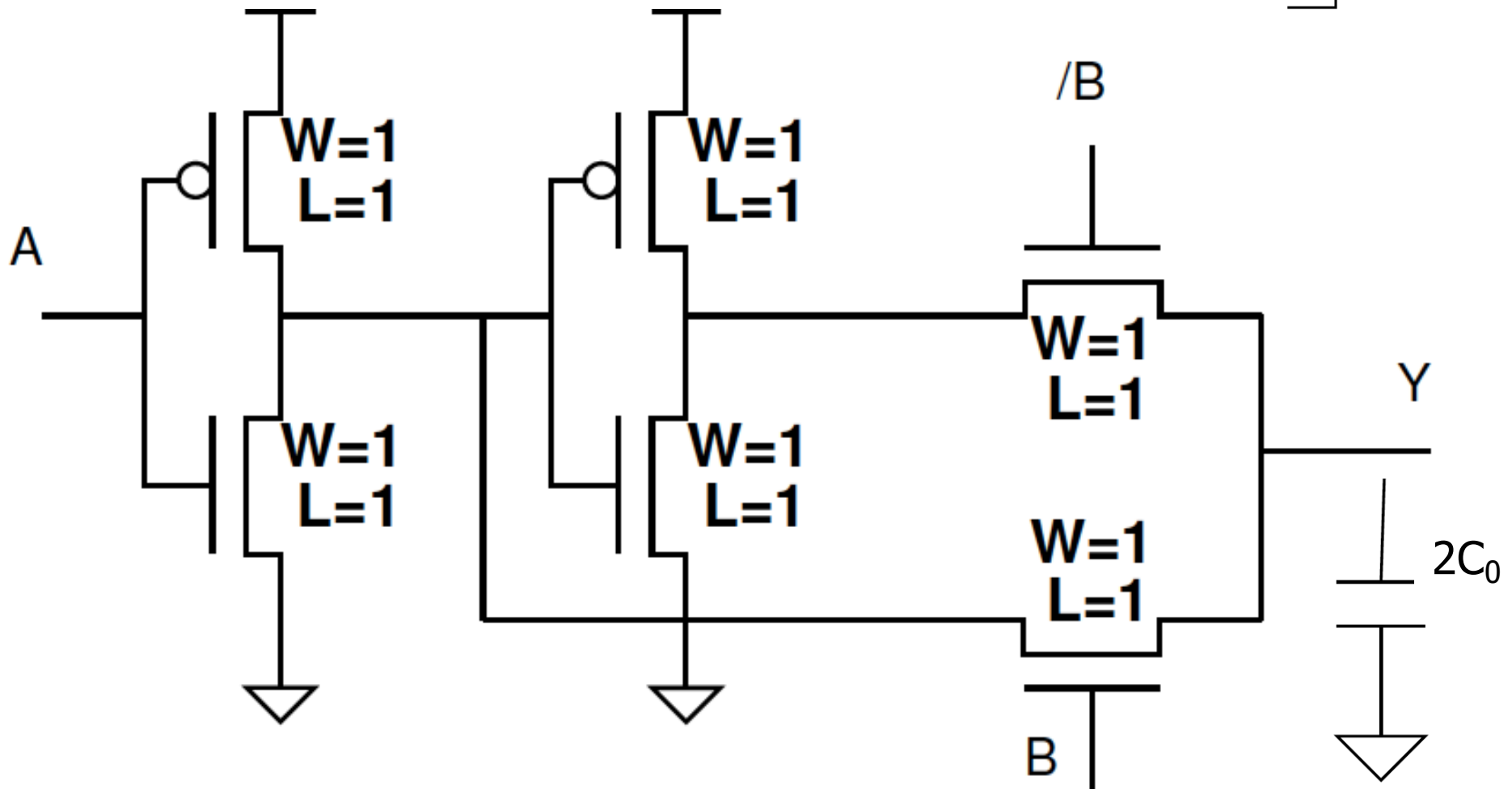 Delay $A=1, B=0, C_{diff0}=\gamma C_0?$ (Preclass 3)




Delay $A=1$, $B=0$, $C_{diff0}=\gamma C_0$? (Preclass 3)

- What's the equivalent RC circuit?

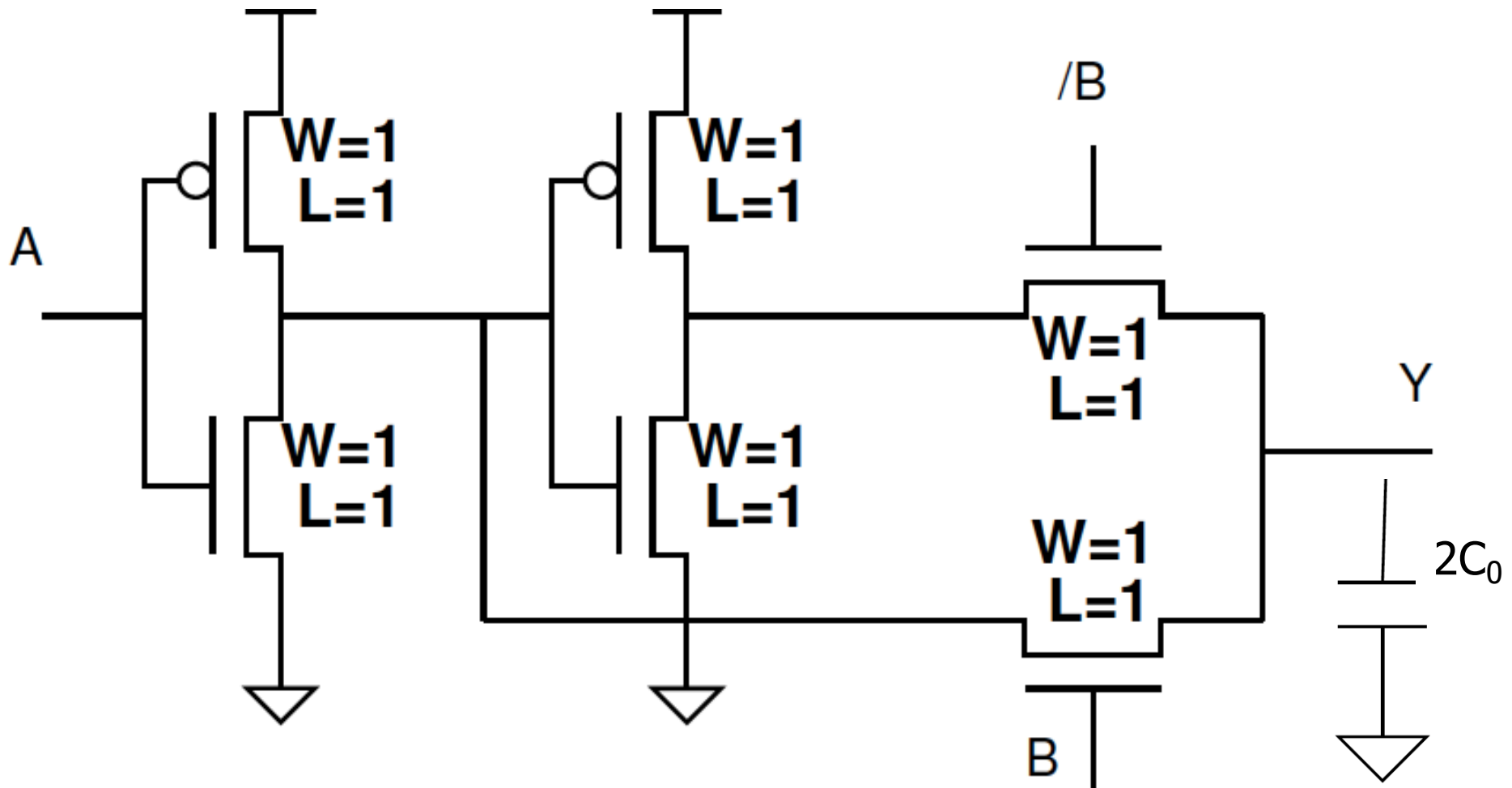


Delay $A=1$, $B=0$, $C_{diff0}=\gamma C_0$? (Preclass 3)

- What's the equivalent RC circuit?

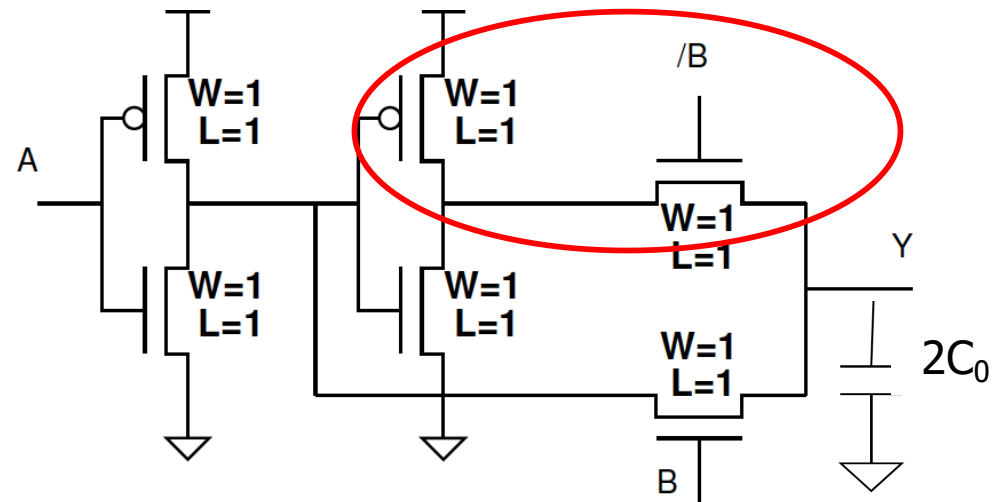


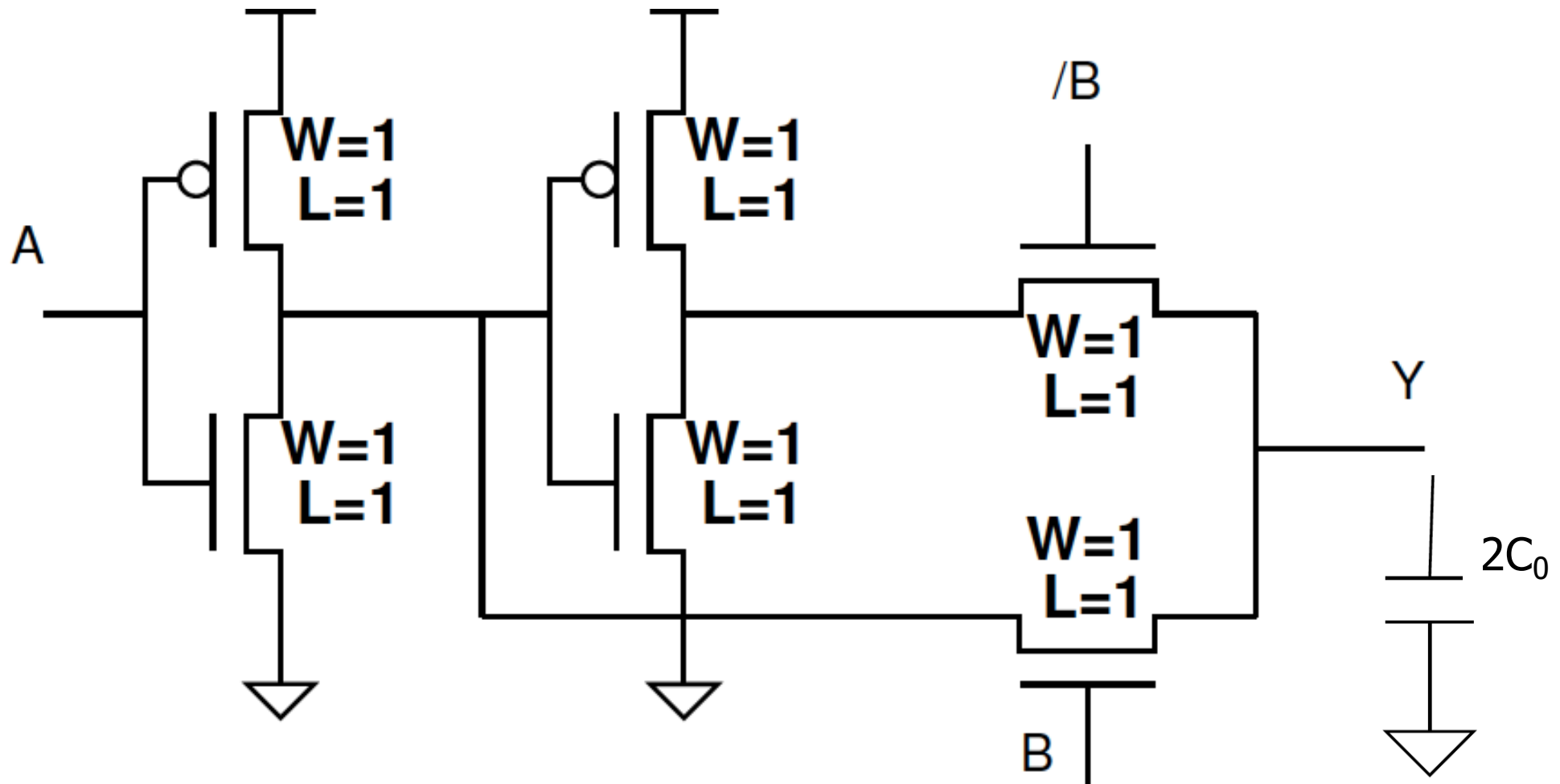Delay $A=1, B=1, C_{diff0}=\gamma C_0?$ (Preclass 3)



Delay $A=1, B=1, C_{diff0}=\gamma C_0$? (Preclass 3)


- What's the equivalent RC circuit?

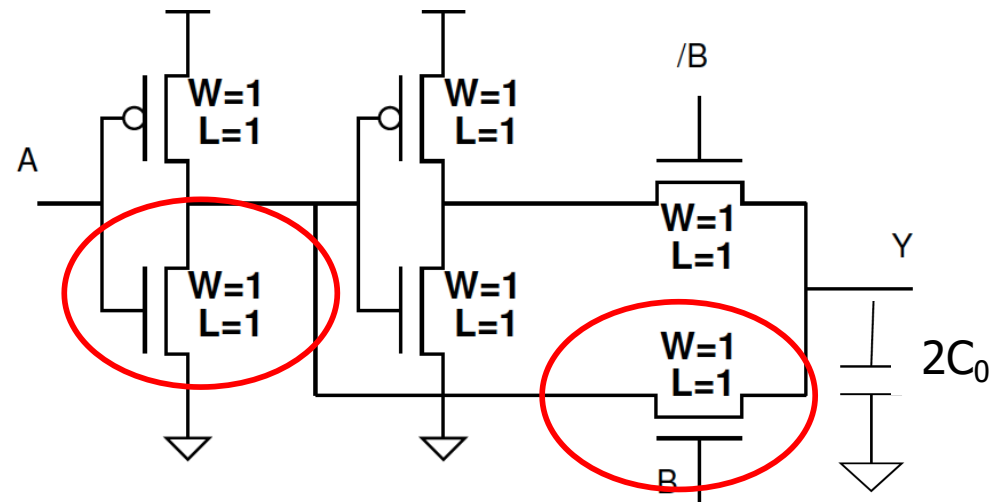



Bonus

□ What does this do?

 

A	B	Y
0	0	
0	1	
1	0	
1	1	



Idea

- ❑ There are other circuit disciplines
- ❑ Can use pass transistors for logic
 - Sometimes gives area or delay win



Admin

- Project 1
 - Milestone due tonight @midnight
 - Will get feedback by Sunday morning
 - Can't pass the class if you don't turn in projects
 - Can't do project last minute
 - Really should be into exploring optimizations for baseline