

ESE370: Circuit-Level Modeling, Design, and Optimization for Digital Systems

Lec 2: September 3, 2021
Transistor Introduction and
Gates from Transistors




Today


- Transistors – MOSFET
 - Model
- Zero-th order transistor model
 - Good enough for [what?]
- How to construct static CMOS gates
 - Gate function identification (preclass)
 - CMOS gate structure
 - Pullup/pulldown networks

Transistor

 - Electrical switch to conduct electricity
 - Instead of physically connecting conducting materials to conduct electricity, apply a voltage to conduct



MOSFET

 


$$V_{GS} = V_G - V_S$$

$$V_{DS} = V_D - V_S$$

$$I_D = f(V_{DS}, V_{GS})$$


- Metal Oxide Semiconductor Field Effect Transistor
 - Primary **active** component for the term
 - Three terminal device
 - Voltage at gate controls conduction between two other terminals (source, drain)

MOSFET – IV Characteristics

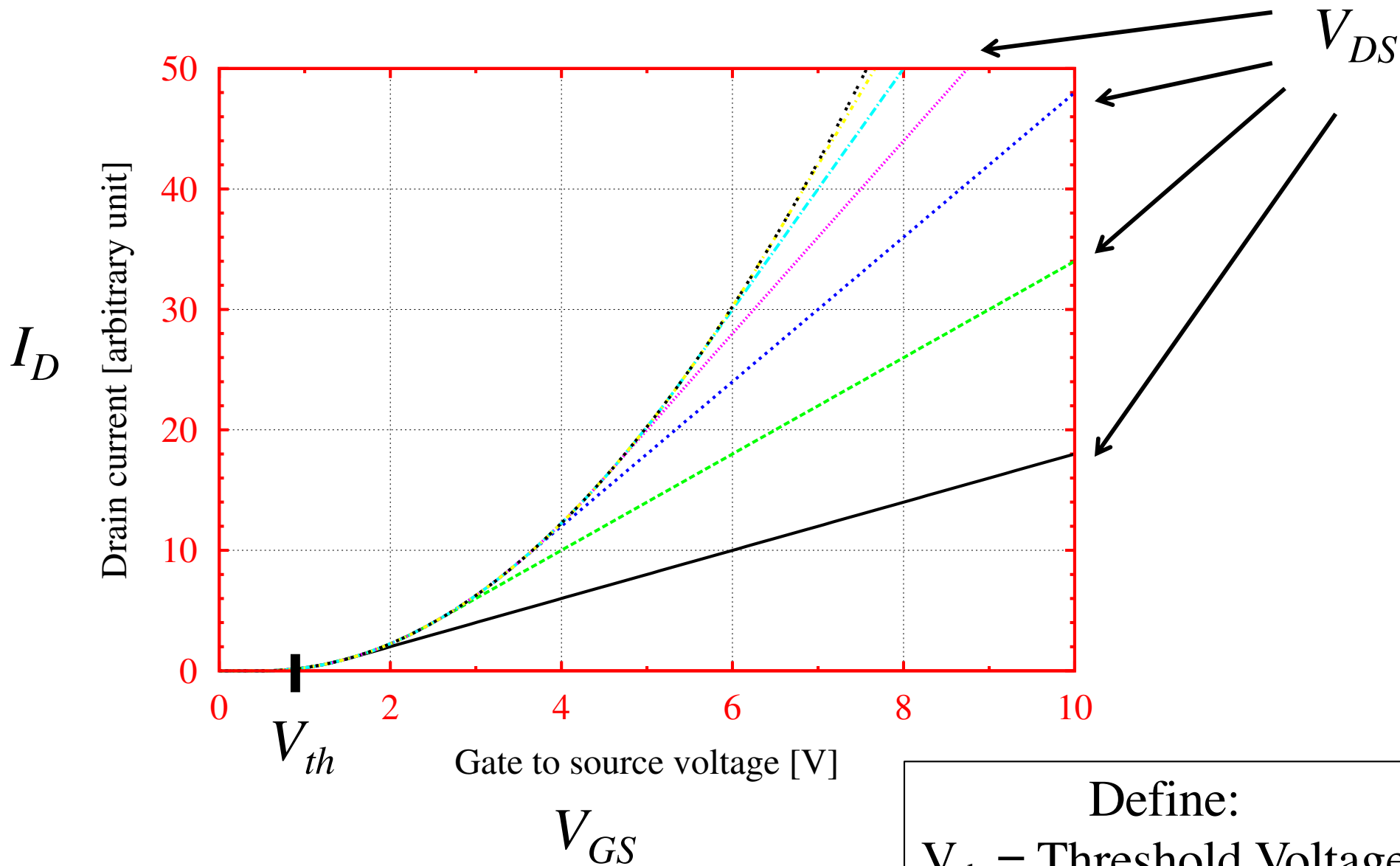


Define:
 $V_{th} = \text{Threshold Voltage}$


MOSFET – IV Characteristics

 

MOSFET – IV Characteristics

 

MOSFET – Zeroeth Order Model

 

□ Ideal Switch



$V_{GS} > V_{th} \rightarrow$ switch is closed, conducts

$V_{GS} < V_{th} \rightarrow$ switch is open, does not conduct

□ Gate draws no current from input

- Loads input capacitively (gate capacitance)


MOSFET – Zeroeth Order Model

 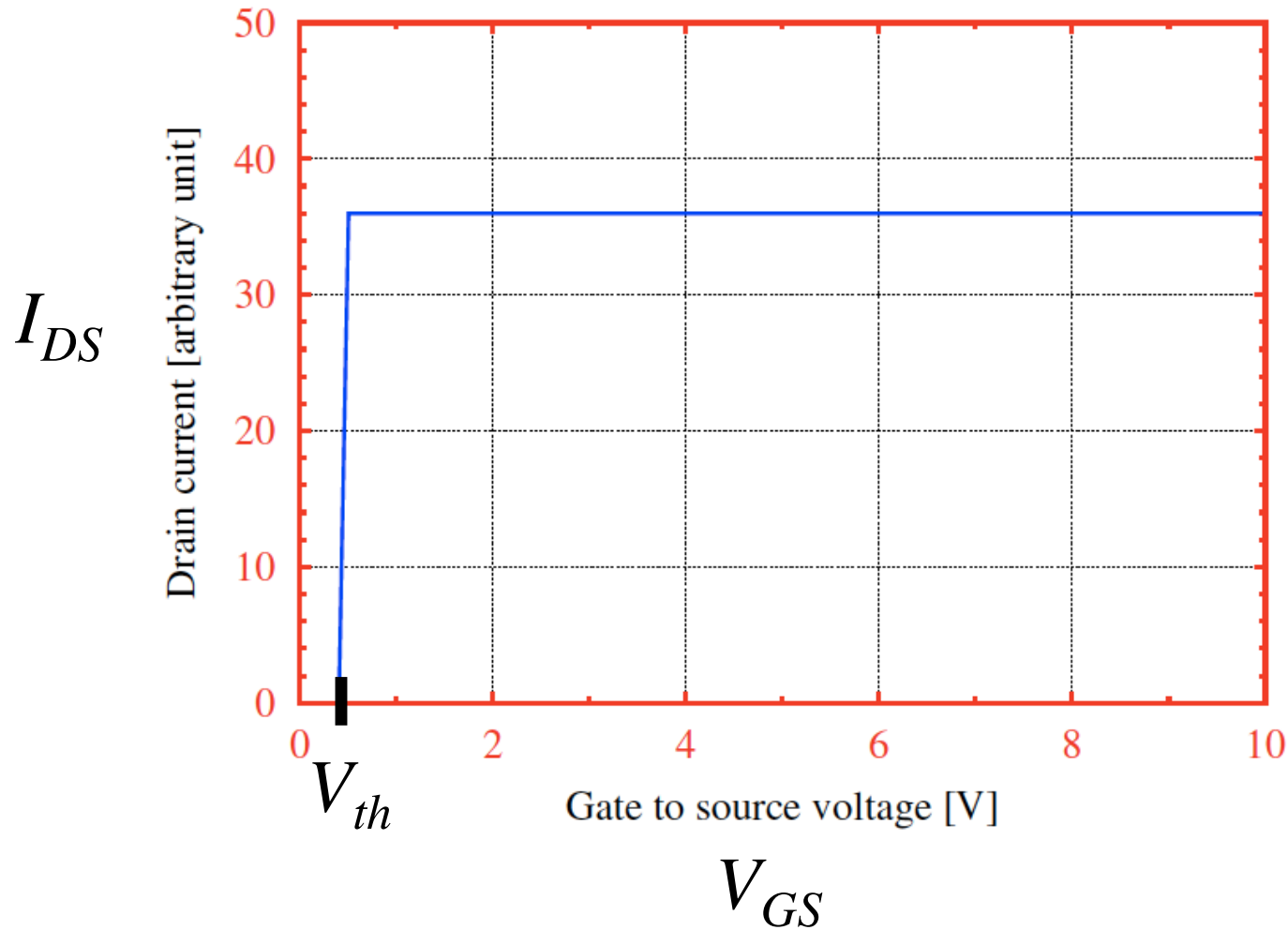



MOSFET - Symmetric

 
- Switch turned on for positive V_{GS}
 - Which side is drain or source?



MOSFET – N-Type

- Switch turned on for positive V_{GS}


$$V_D > V_S$$

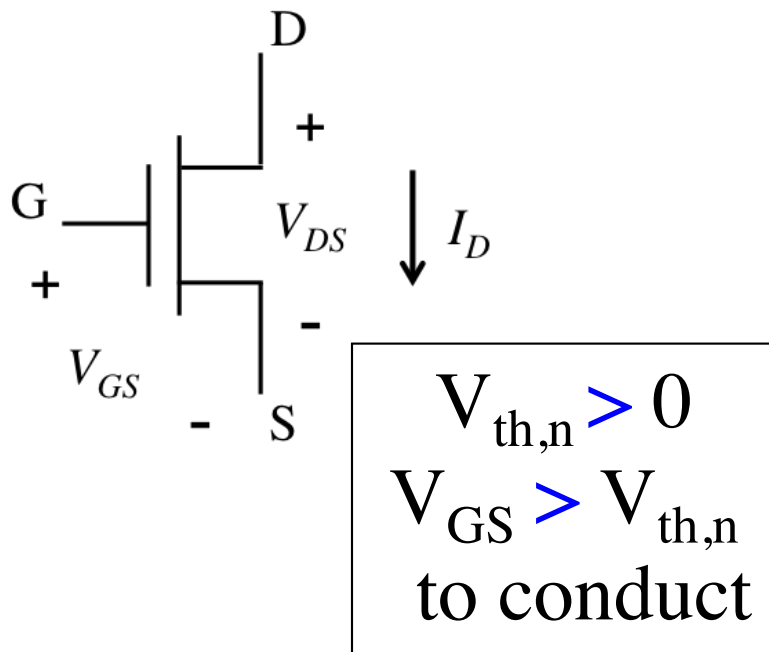

MOSFET – N-Type, P-Type

□ Switch turned on for
positive V_{GS}


$$V_D > V_S$$

 

$V_{th,n} > 0$
 $V_{GS} > V_{th,n}$
to conduct

□ Switch turned on for
negative V_{GS}


$$V_S > V_D$$

 

MOSFET – N-Type, P-Type

□ Switch turned on for
positive V_{GS}


$$V_D > V_S$$

 

$$\begin{aligned} V_{th,n} &> 0 \\ V_{GS} &> V_{th,n} \\ \text{to conduct} \end{aligned}$$

□ Switch turned on for
negative V_{GS}

$$V_S > V_D$$

 


$$\begin{aligned} V_{th,p} &< 0 \\ V_{GS} &< V_{th,p} \\ \text{to conduct} \end{aligned}$$

MOSFET – N-Type, P-Type

□ Switch turned on for
positive V_{GS}


$$V_D > V_S$$

 

$$\begin{aligned} V_{th,n} &> 0 \\ V_{GS} &> V_{th,n} \\ \text{to conduct} \end{aligned}$$

□ Switch turned on for
negative V_{GS}

$$V_S > V_D$$


 


$$\begin{aligned} |V_{th,p}| &> 0 \\ |V_{GS}| &> |V_{th,p}| \\ \text{to conduct} \end{aligned}$$

Apply zero-order model

Note S, D annotation on this slide (won't be labeled in future)




Why is it this way?

 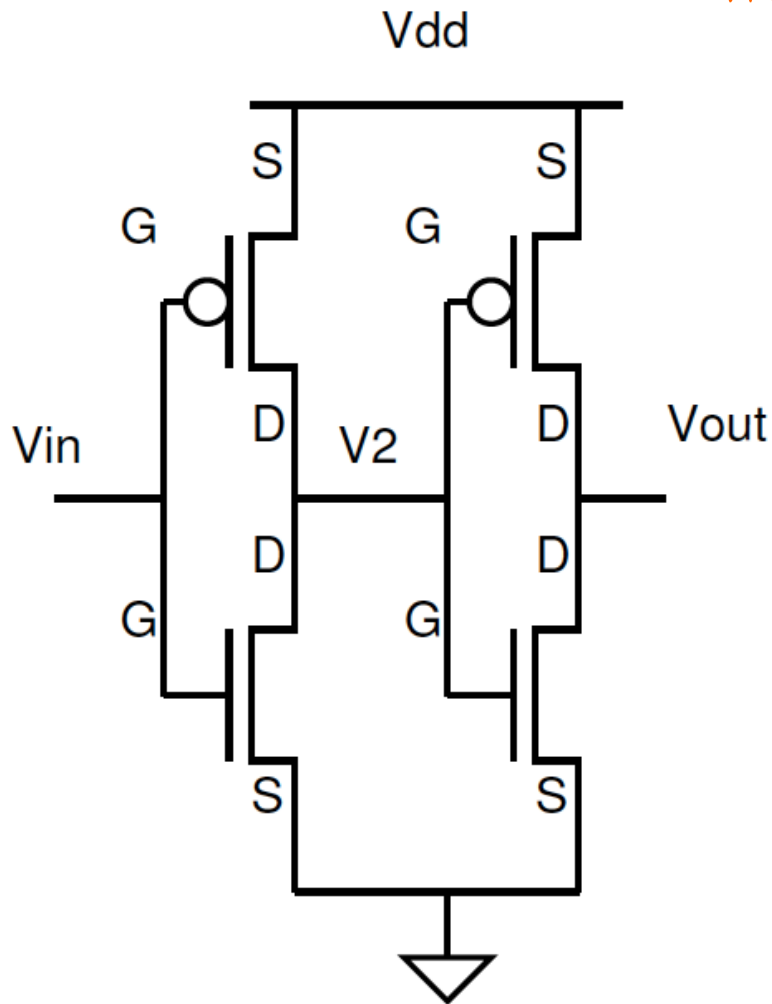

Apply zero-order model?

What happens when $V_{in} = V_{dd} > V_{thn}$?

  
 
$$V_{th,p} = -V_{th,n}$$
$$V_{GS} = V_G - V_S$$



Apply zero-order model?

What happens when $V_{in} = 0$?
  
$$V_{th,p} = -V_{th,n}$$
$$V_{GS} = V_G - V_S$$





Convince yourself that $V_{out} = 0$.



Zeroeth Order Model


- Allows us to reason (mostly) at logic level about steady-state functionality of typical gate circuits before worrying about performance (speed, power, etc.) details

What is missing in Zeroeth Order Model?

  


- ❑ Delay
 - Parasitic capacitances and resistances
- ❑ Dynamics
- ❑ Zeroeth Order captures behaviour if our circuit is **not**:
 - Capacitively loaded, acyclic (if there are Loops), rail-to-rail drive

How to construct static CMOS gates

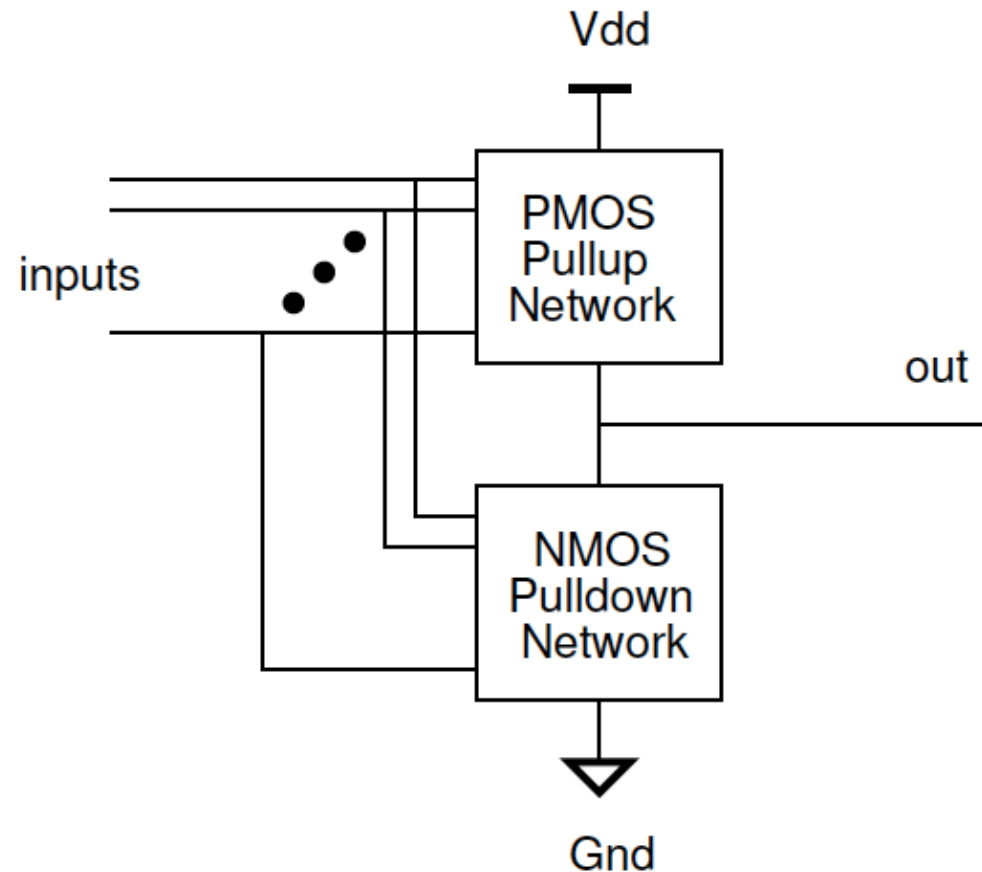


- Complementary Metal Oxide Semiconductor

What gate is this? Preclass 1

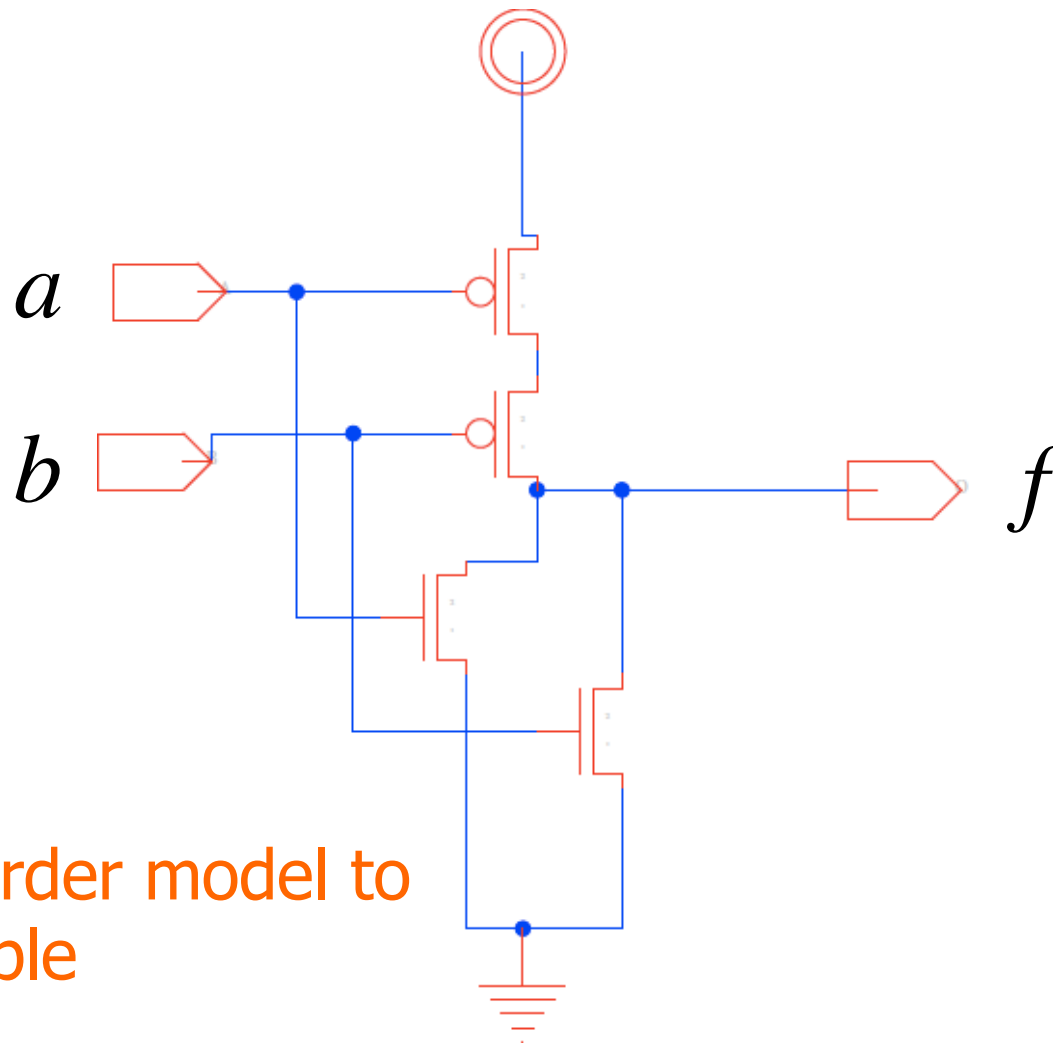


Hint: use zero order model to make a truth table

What gate is this?

 


What gate is this? Preclass 2

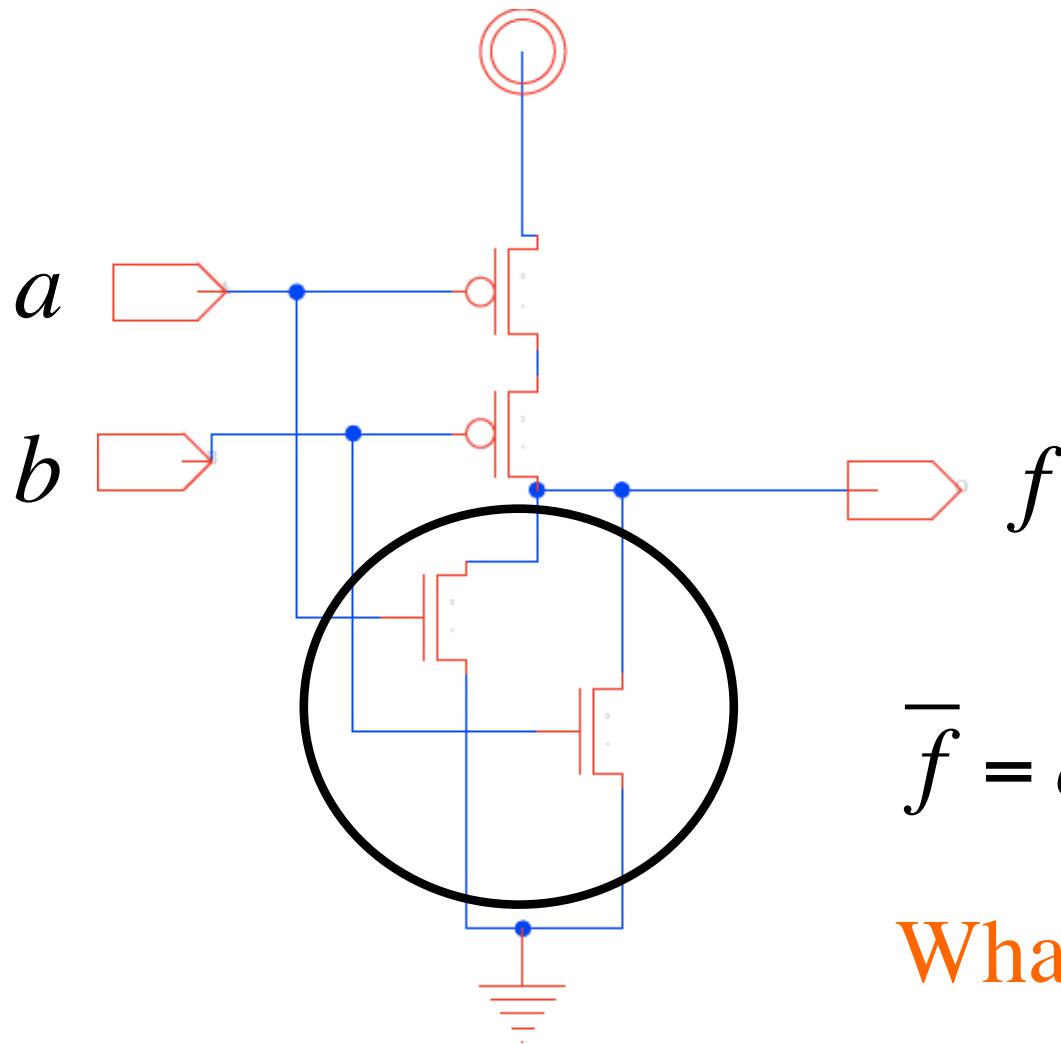


$$\overline{f} = a + b$$

What is f ?


What gate is this?

 



What gate is this?

 

Static CMOS Gate Structure

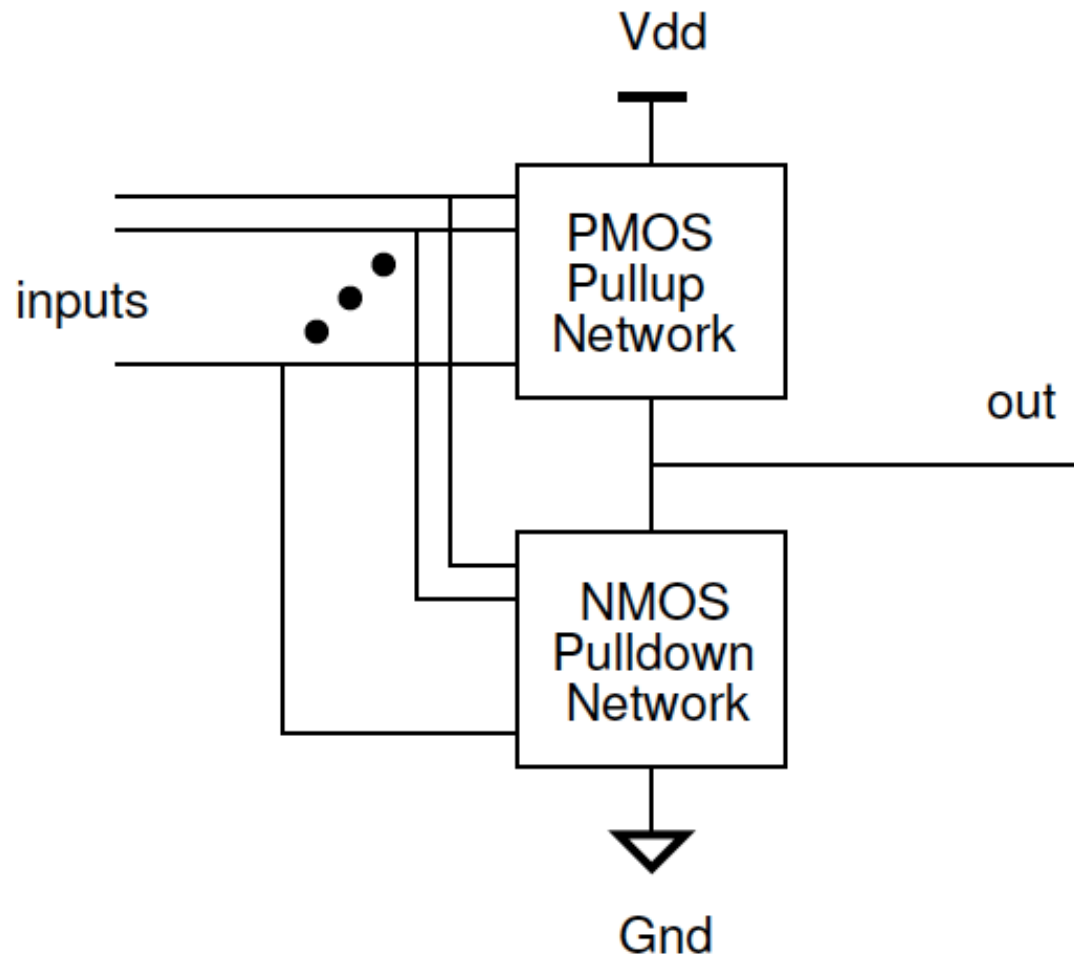

Static CMOS Gate Structure

 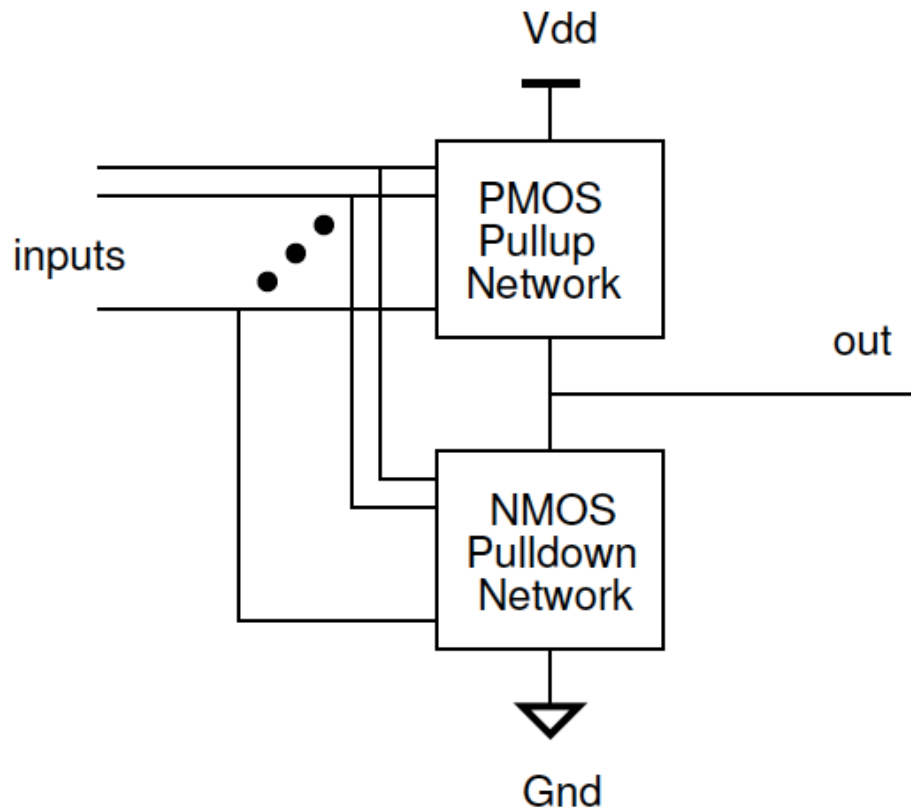




CMOS

- ❑ Complementary Metal Oxide Semiconductor
- ❑ Uses *complementary* transistors
 - NMOS, PMOS
- ❑ Pull-down and pull-up networks are *complements* of each other
 - Only one network active (on) at a time to charge or discharge output to V_{dd} or Gnd respectively

Static CMOS Gate Structure

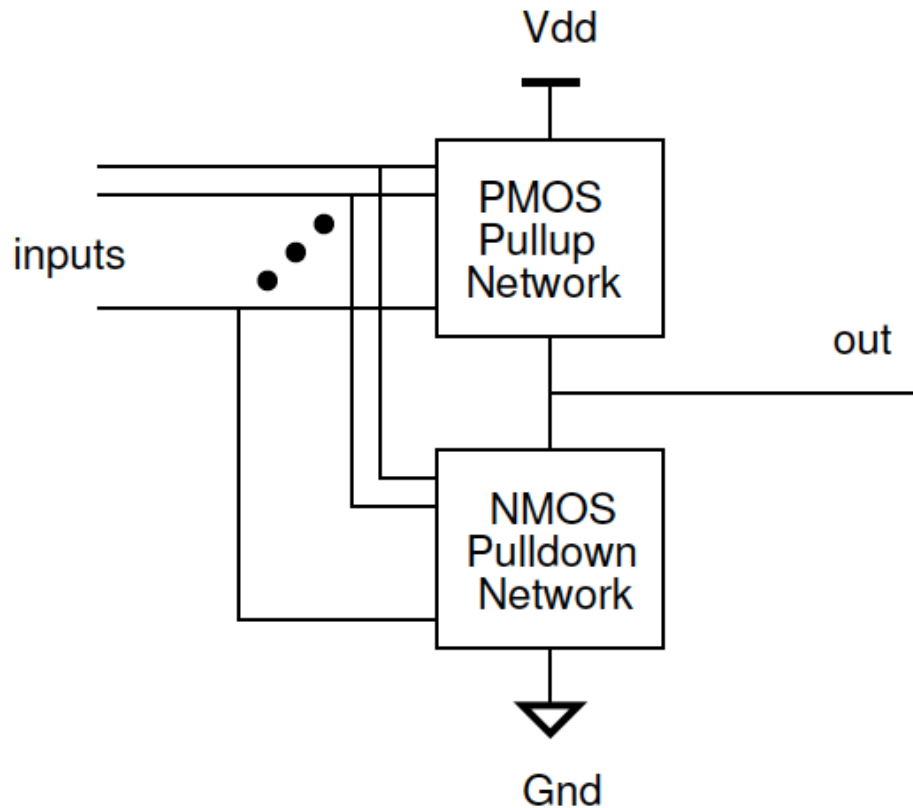


- Drives rail-to-rail
 - Power rails are V_{dd} and Gnd
 - output is V_{dd} or Gnd
- Input connects to gates
 - load is capacitive
- Once output node is charged doesn't use energy (no static current)
- Output actively driven

Gate Design Example Preclass 3

□ Design gate to perform: $f = (\bar{a} + \bar{b}) \cdot \bar{c}$

□ Strategy:

 
1. Use static CMOS structure
2. Design PMOS pullup for f
3. Use DeMorgan's Law to determine f'
4. Design NMOS pulldown for f'



Gate Design Example

□ Design gate to perform: $f = (\bar{a} + \bar{b}) \cdot \bar{c}$

□ PMOS Pullup for f ?

 


Gate Design Example

□ Design gate to perform: $f = (\bar{a} + \bar{b}) \cdot \bar{c}$


□ What is f' ?

■ DeMorgan's Law

 



Gate Design Example

 - Design gate to perform: $f = (\bar{a} + \bar{b}) \cdot \bar{c}$
- Design NMOS pulldown for f'



Gate Design Example

 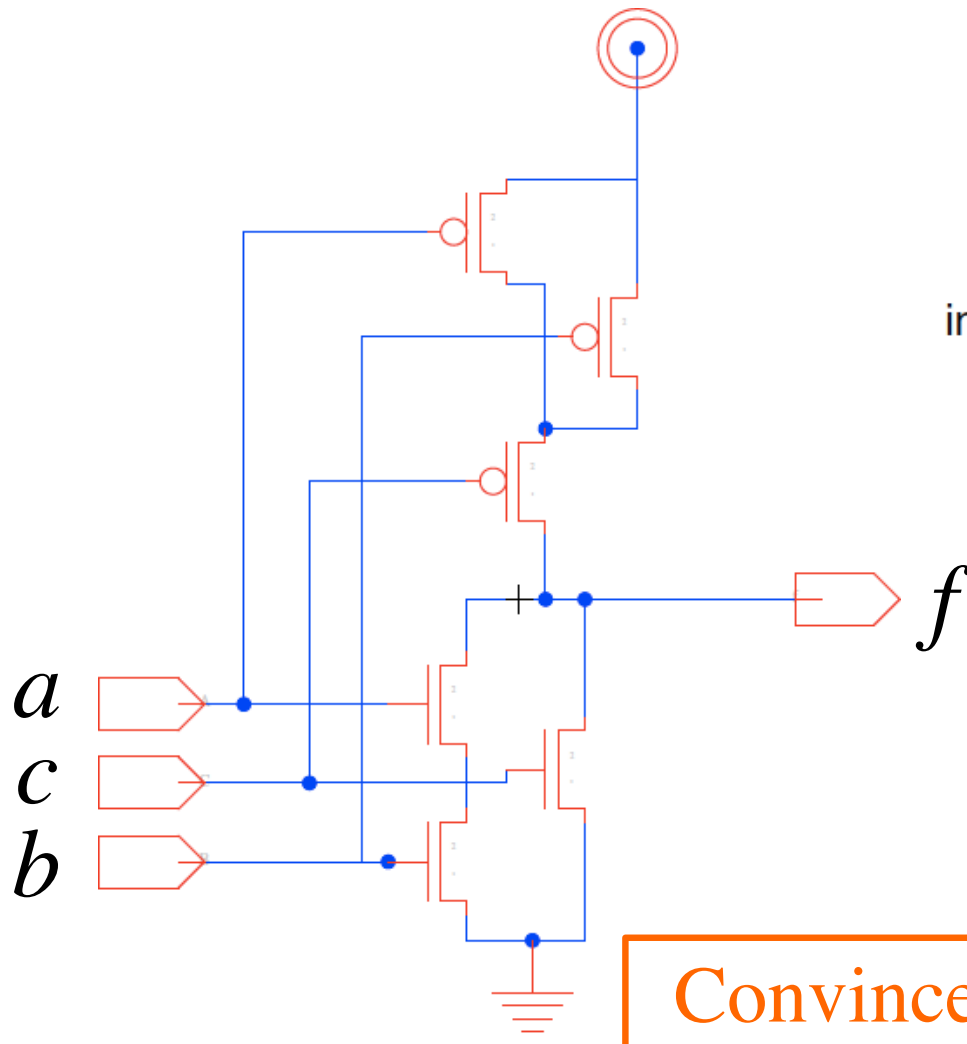- Design gate to perform: $f = (\bar{a} + \bar{b}) \cdot \bar{c}$



Convince yourself with a truth table.




Big Idea

- ❑ MOSFET Transistor as switch
- ❑ Functionality-driven simplified modeling (Zero order)
 - Aid reasoning
 - Sanity check
 - Simplify design

Big Idea

□ Systematic construction of any gate from transistors

 1. Use static CMOS structure
2. Design PMOS pullup for f
3. Use DeMorgan's Law to determine f'
4. Design NMOS pulldown for f'





Admin

- ❑ Access Survey – due tomorrow night for credit
- ❑ Diagnostic – due Tuesday
- ❑ HW 1 out – due 9/14
 - Will take time to learn Electric CAD tool, start early
- ❑ No class on Monday
- ❑ Wednesday – no lecture, Lab in Ketterer
- ❑ Friday regular lecture in Towne 307