

ESE370: Circuit-Level Modeling, Design, and Optimization for Digital Systems

Lec 20: October 25, 2021



Pass Transistor Logic, Pt2




Today

- Pass Transistor Circuit
 - $C_{\text{diff}} > 0$
 - Output levels
 - Cascading
 - Series pass transistors?
 - Delay
- Start on Distributed RC
 - Analyzing delay for pass-tr designs

Previously: Two XOR Gates

  


Cascaded Pass Gates

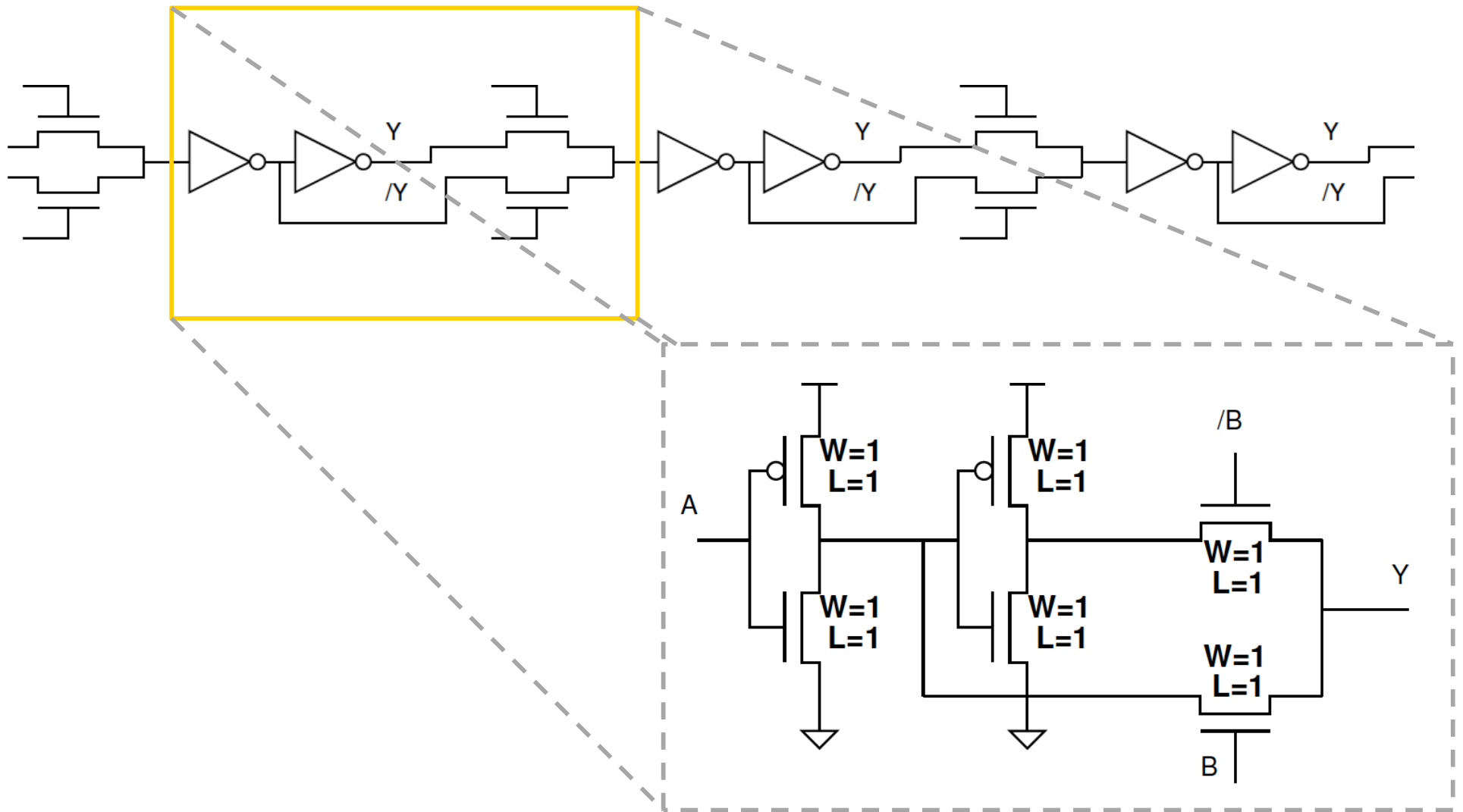


First Order Delay

 - R_0 = Resistance of minimum size NMOS device
- C_0 = gate capacitance of minimum size NMOS device
- C_{diff0} = diffusion capacitance on minimum size NMOS
 - $C_{diff0} = \gamma C_0$
- $R_{drive} = R_0/W$
- $C_g = WC_0$
- $C_{diff} = WC_{diff0}$





Delay $A=1, B=0, C_{diff0}=\gamma C_0?$ (Preclass 1)

- What's the equivalent RC circuit?

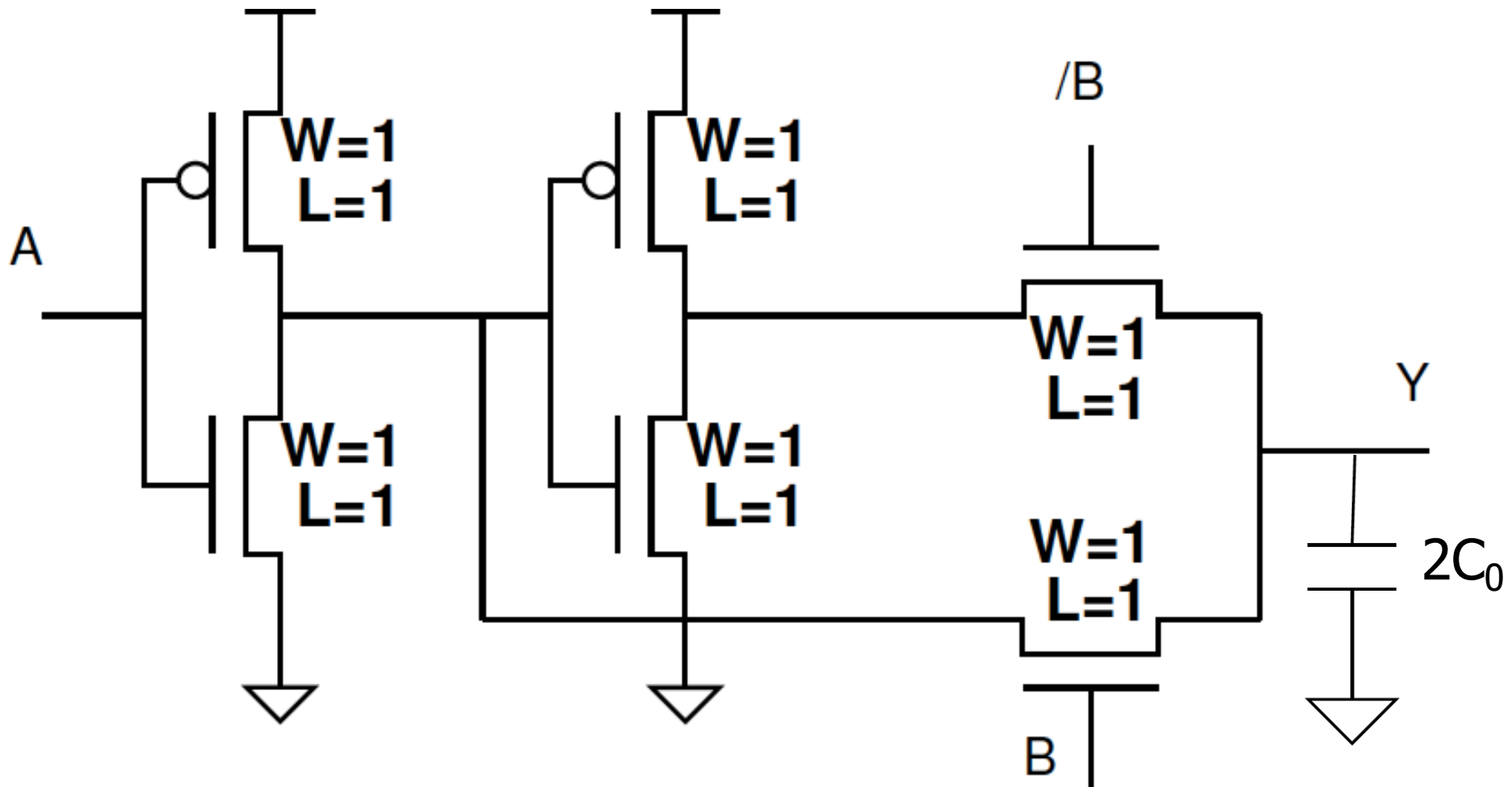


Delay $A=1, B=0, C_{diff0}=\gamma C_0$? (Preclass 1)

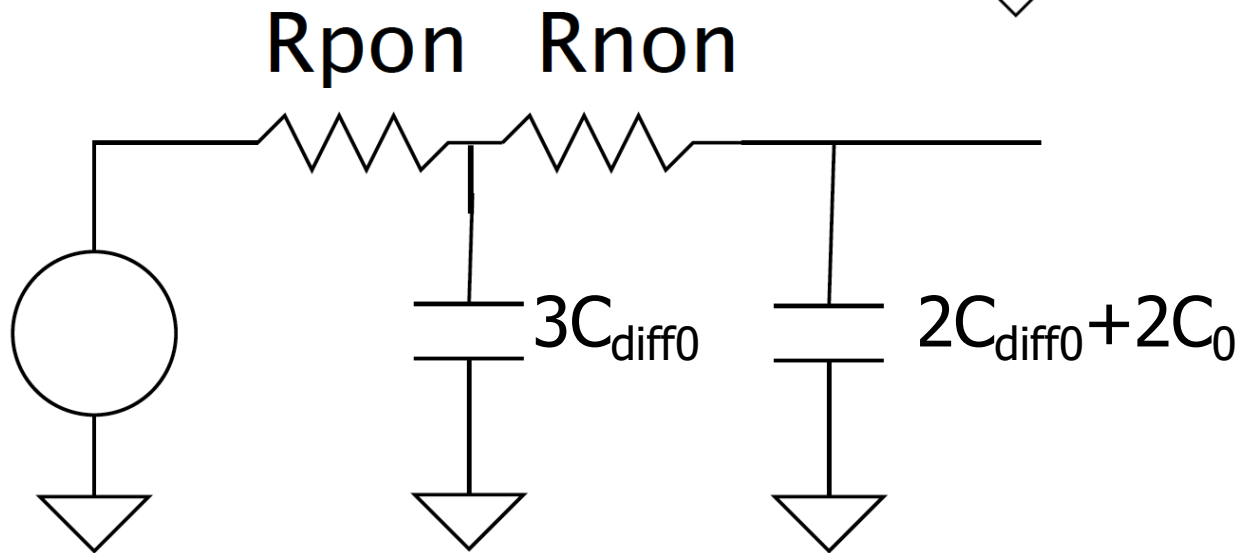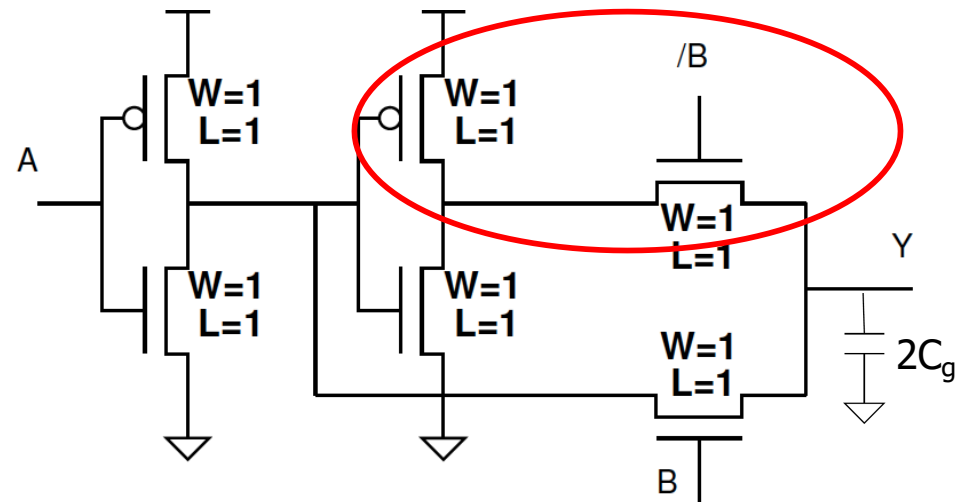- What's the equivalent RC circuit?
 - What is the total delay?
 - From A to Y





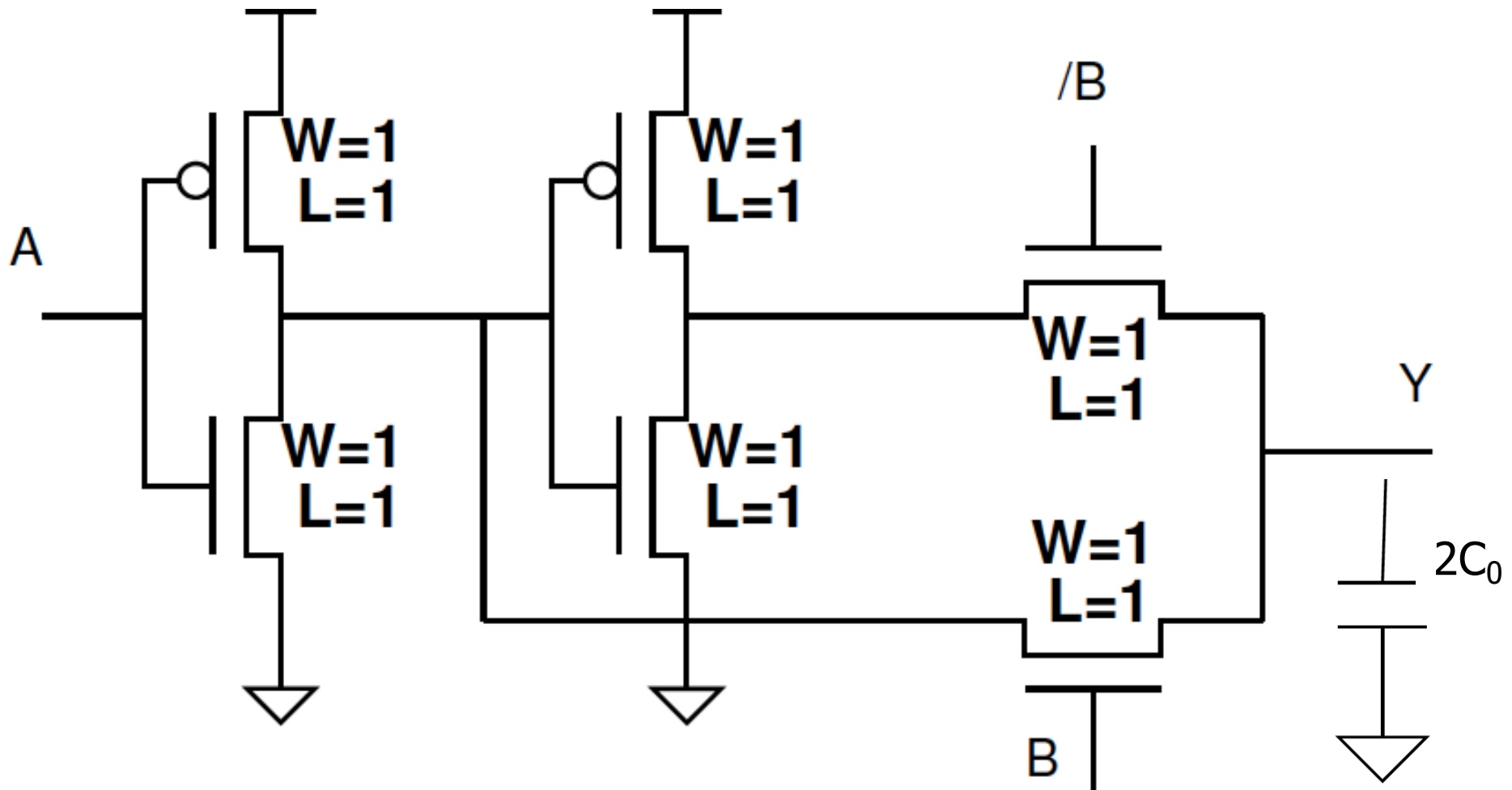Delay $A=1, B=1, C_{diff0}=\gamma C_0?$ (Preclass 1)



Delay $A=1, B=1, C_{diff0}=\gamma C_0$? (Preclass 1)


- What's the equivalent RC circuit?

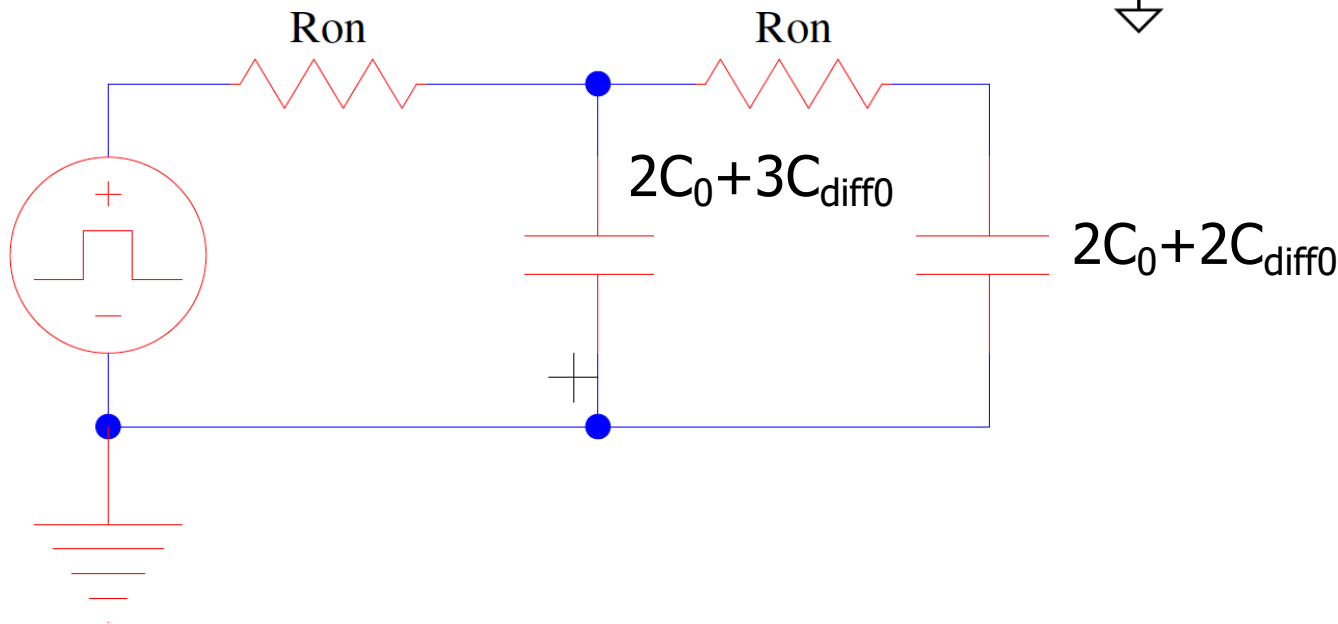 



Bonus

□ What does this do?

 


A	B	Y
0	0	
0	1	
1	0	
1	1	



Bonus

□ What does this do?

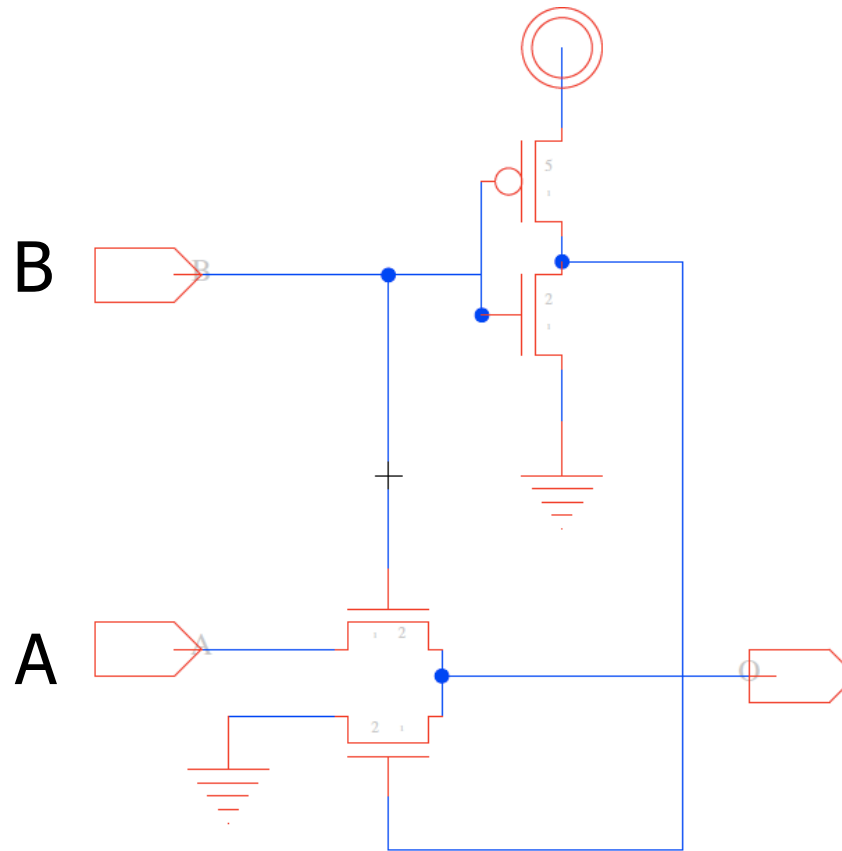

A	B	Y
0	0	0
0	1	0
1	0	0
1	1	1


More examples in the text

Cascading Pass Transistors




Chain without Inverters

□ What if we did this?

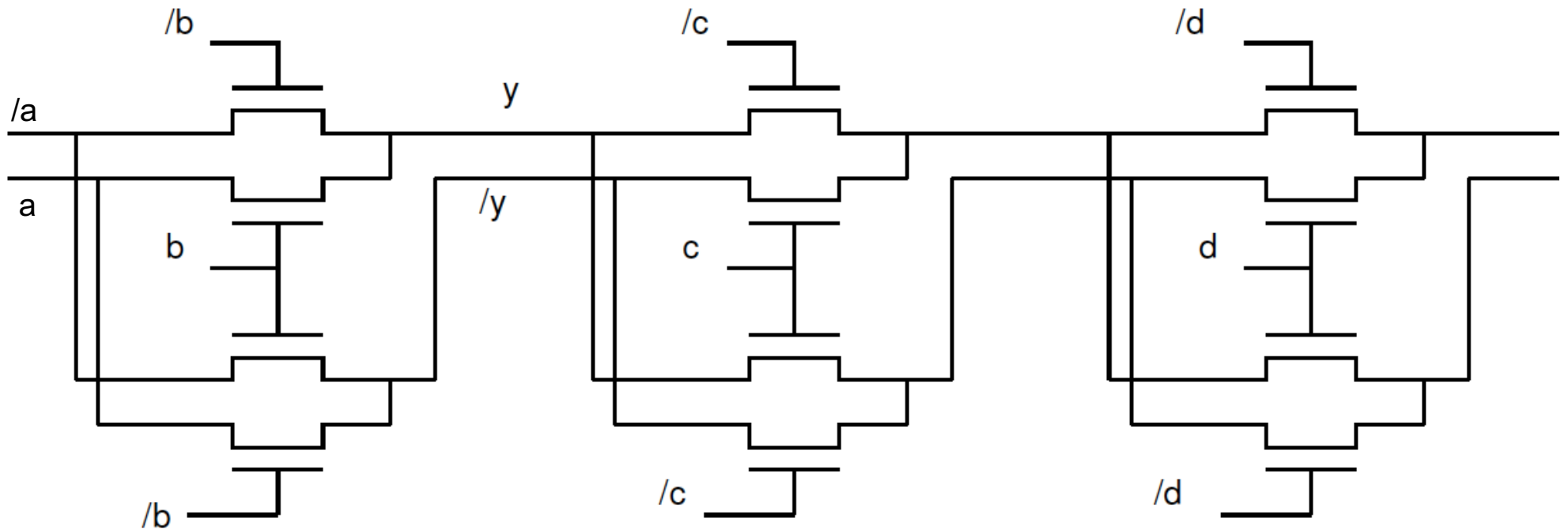

Chain without Inverters

- Extract key path

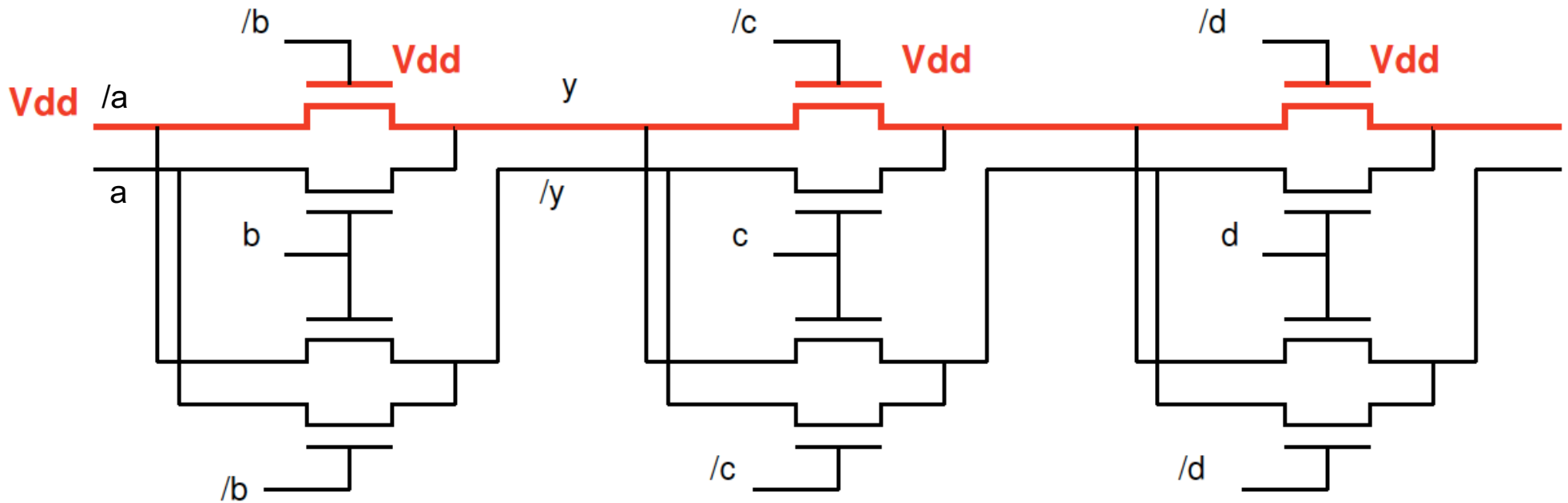


Voltage of Chain (Preclass 2)

□ What is voltage at output?

$$V_{dd} = 1V$$

$$V_{thn} = -V_{thp} = 0.3V$$

 


Voltage of Chain (Preclass 2)

□ What is voltage at output?

$$V_{dd} = 1V$$



$$V_{thn} = -V_{thp} = 0.3V$$

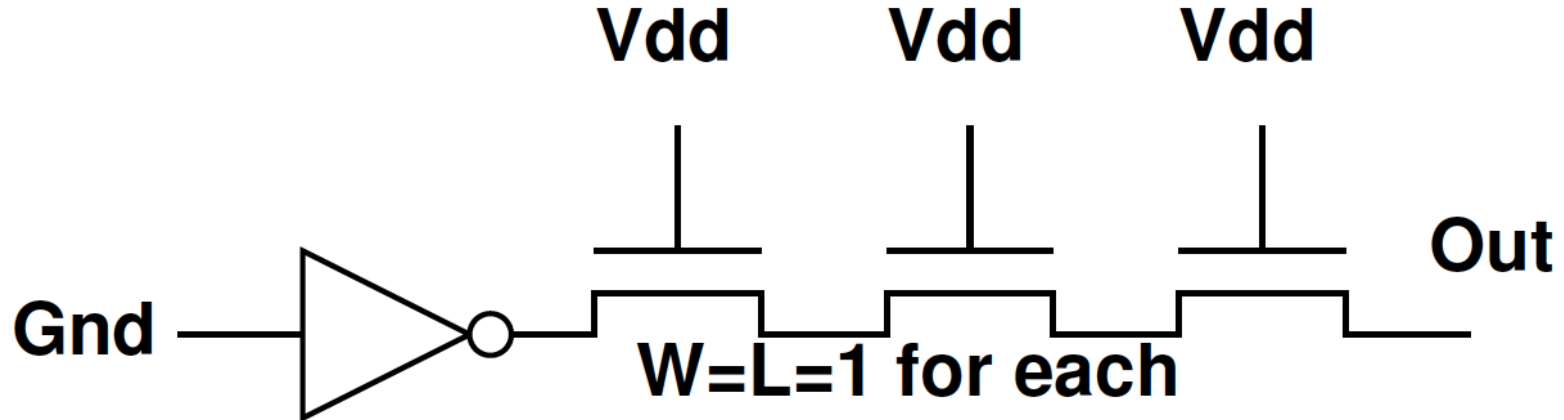


How compare (Preclass 2)

□ Compare
  
$$V_{dd} = 1V$$
$$V_{thn} = -V_{thp} = 0.3V$$





DC Analysis – chain of 3 vs length of 3

 

Conclude

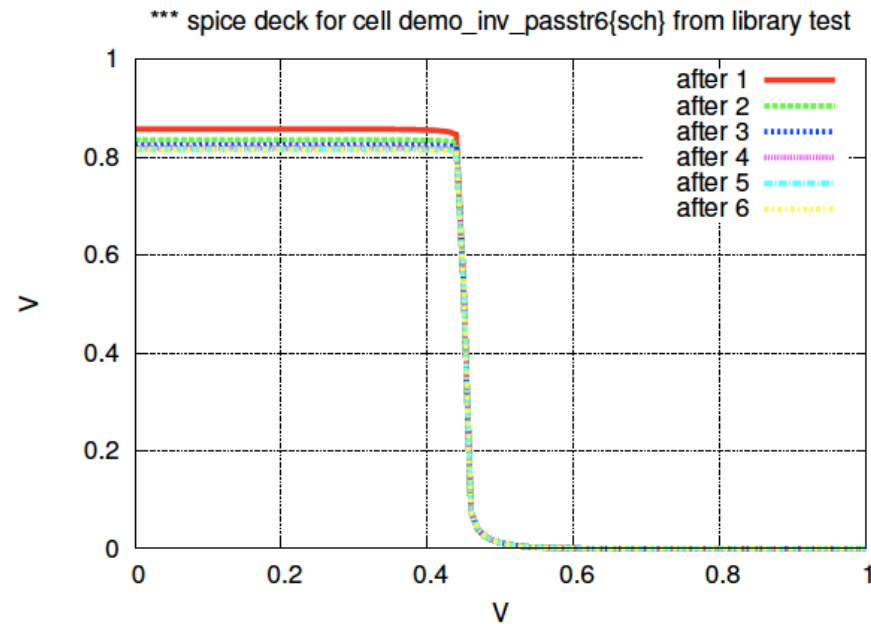 
- Can chain any number of pass transistors and only drop a single V_{th}





Transient


Transient Response for pass tr cascade

 



Transient: Zoomed Closeup


Transient Response for pass tr cascade

 



Capacitance

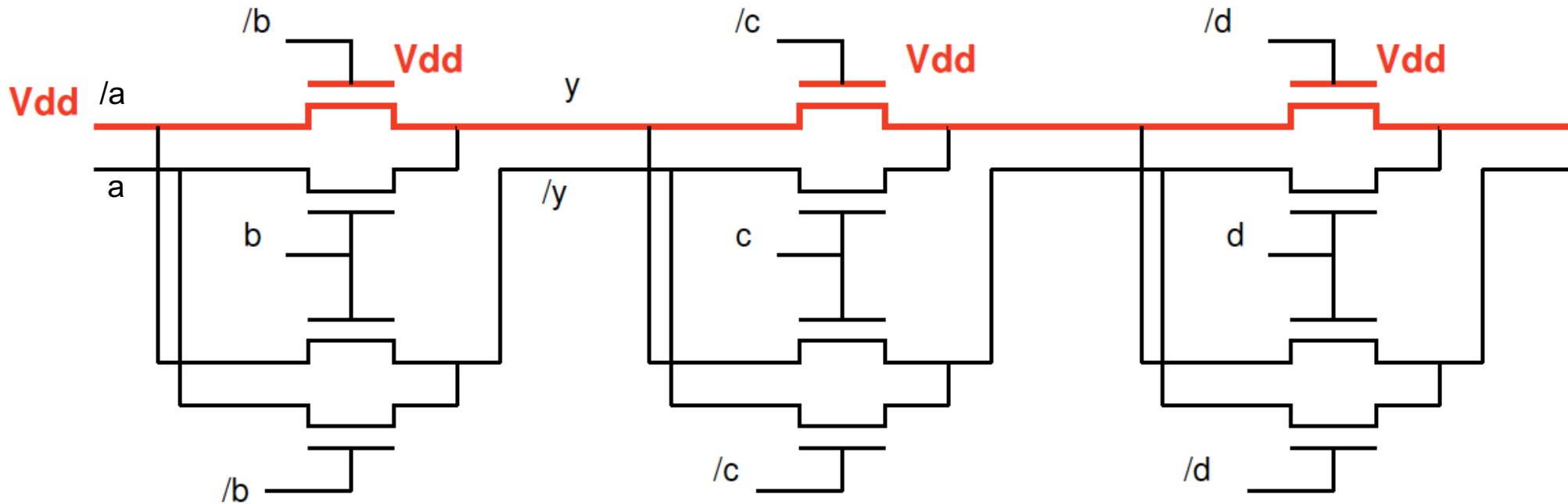
- What is output capacitance per stage?
 - I.e. What is the capacitance at output y ?





Delay Setup

- What does RC circuit look like?

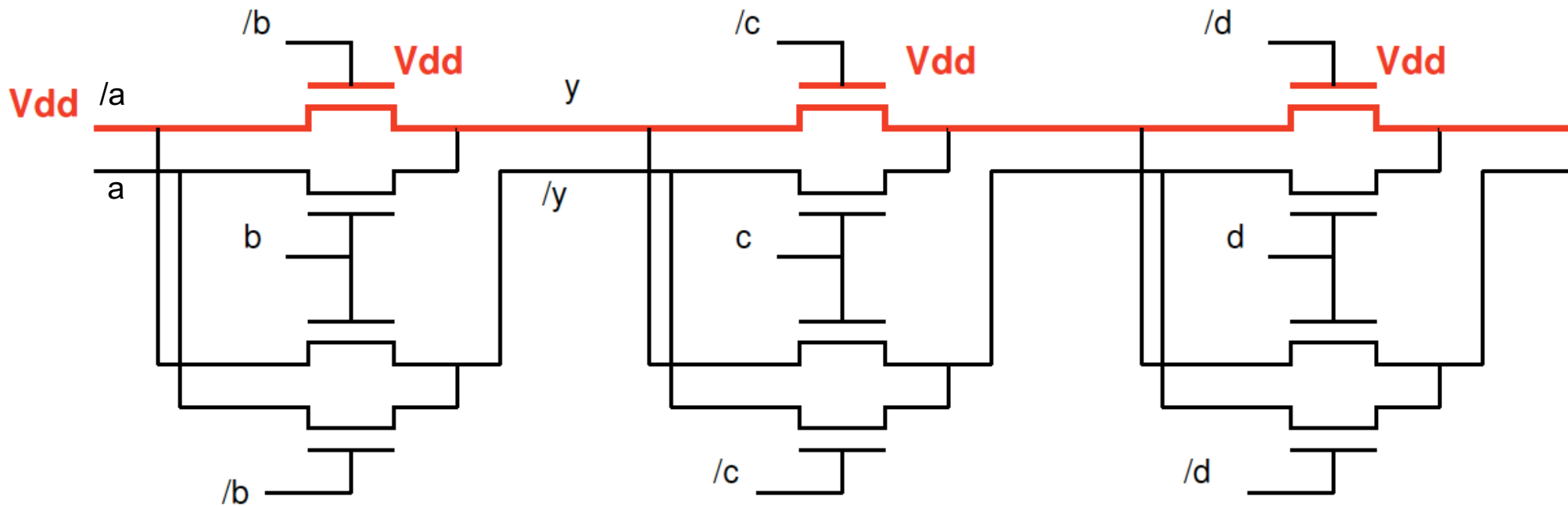


Gate Cascade? (Preclass 3)

□ What are the voltages?

$$V_{dd} = 1V$$


$$V_{thn} = -V_{thp} = 0.3V$$

 




Conclude

 - ❑ Cannot cascade degraded inputs into **gates**.




Distributed RC (setup)


What is response? (Preclass 4)

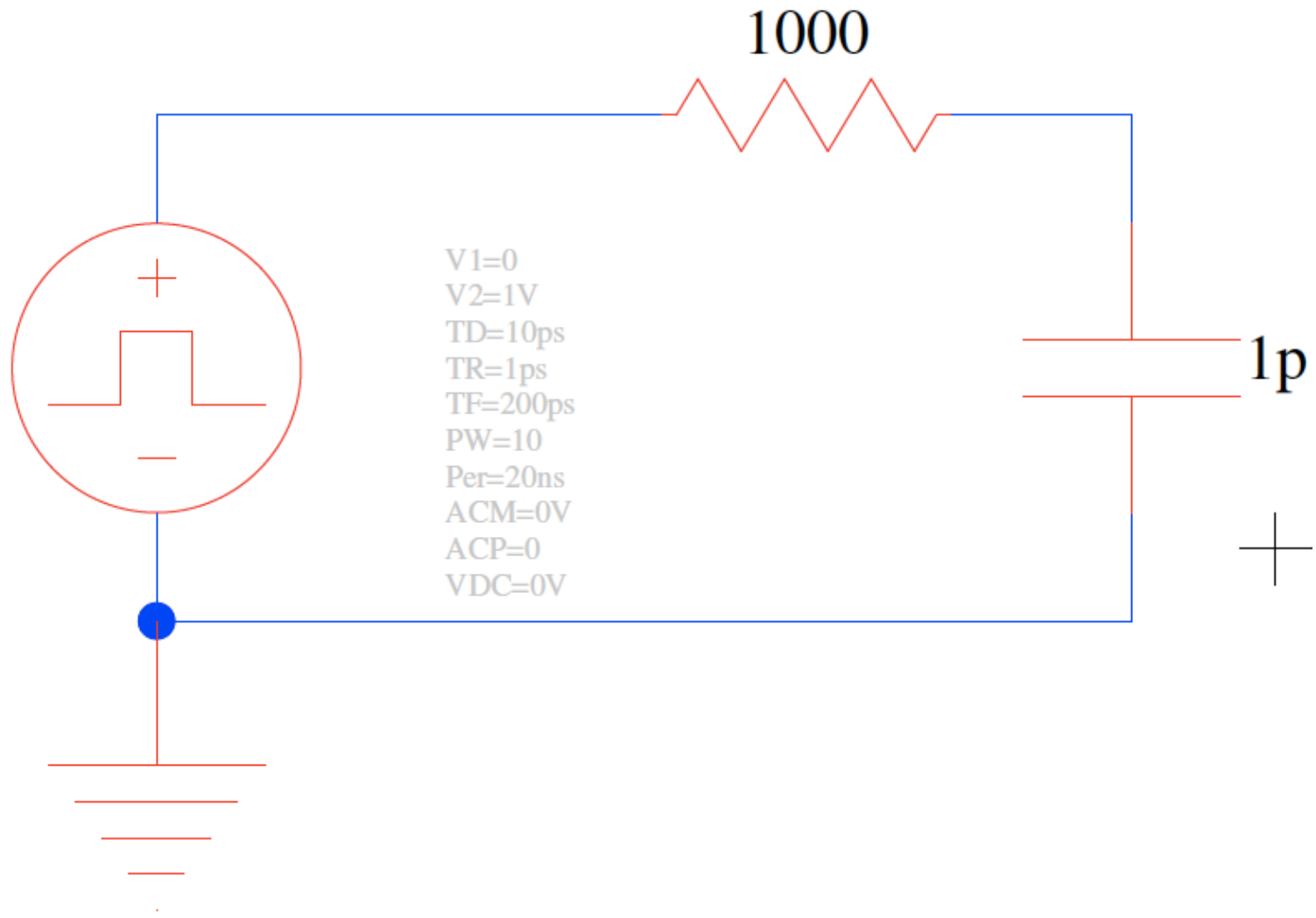

What is response? (Preclass 4)

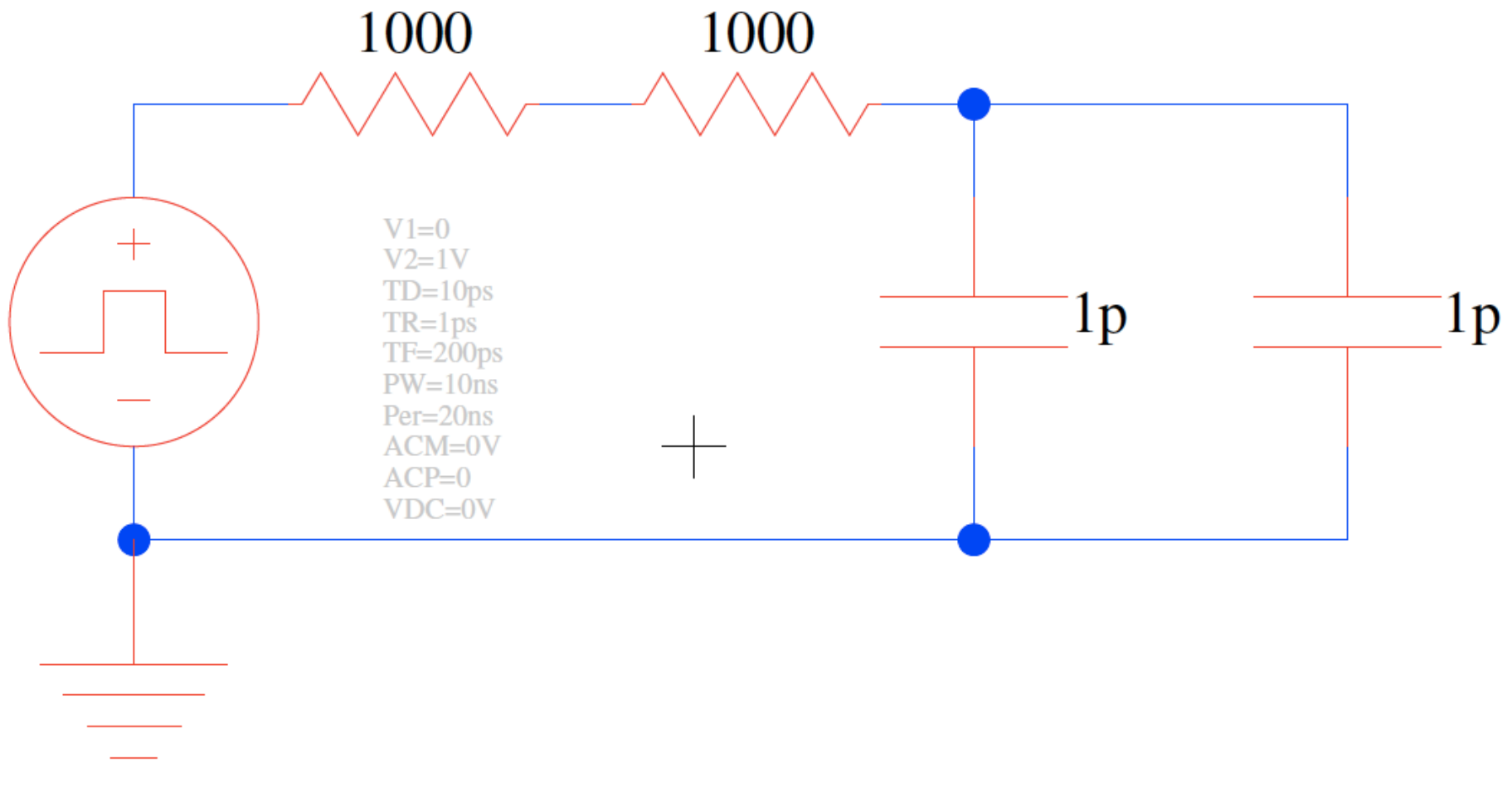


What is response? (Preclass 4)

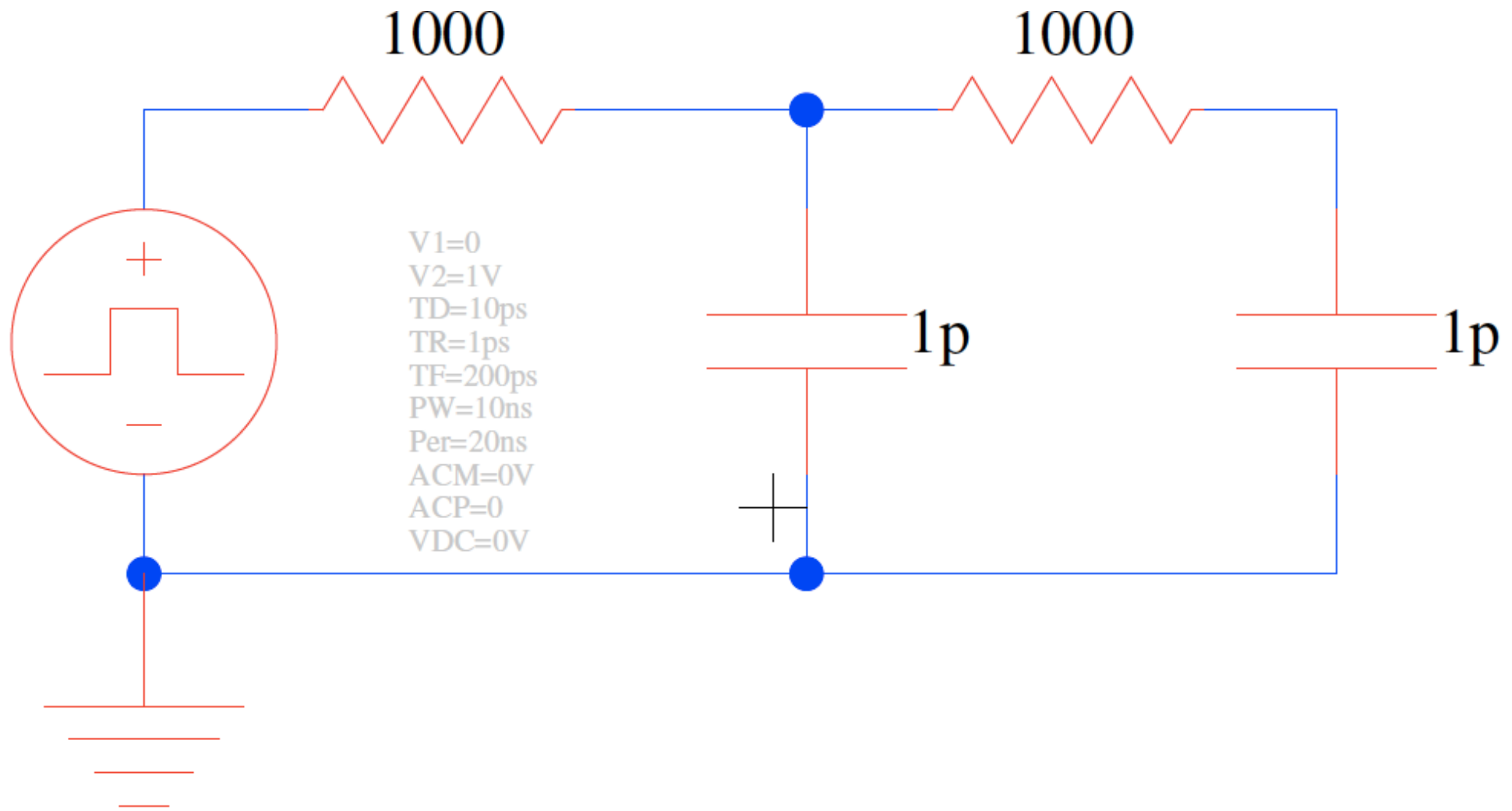




SPICE Response

 





SPICE Response

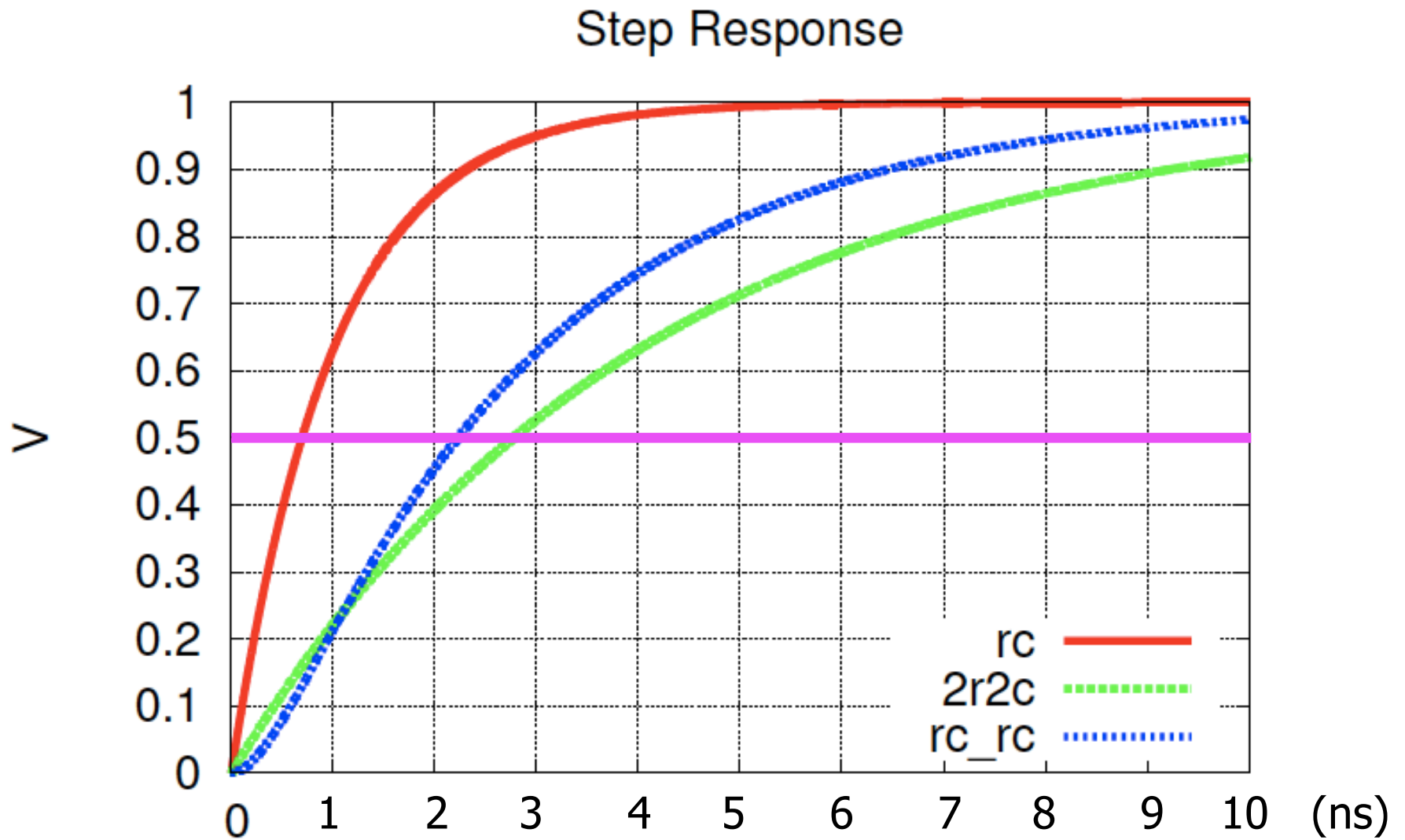


Intuition

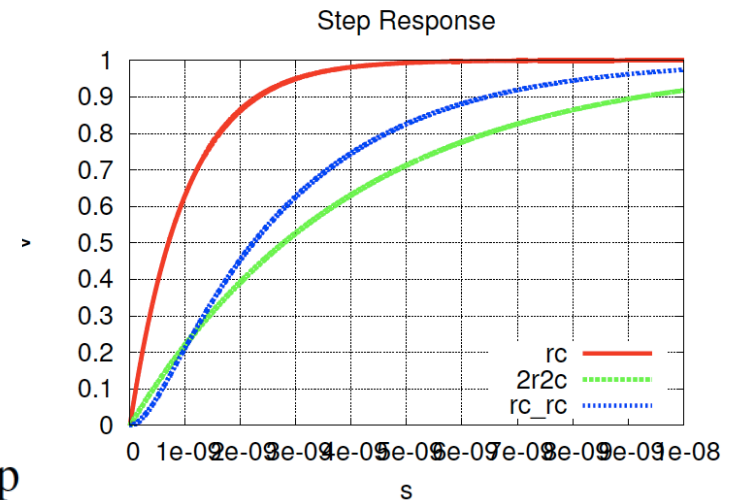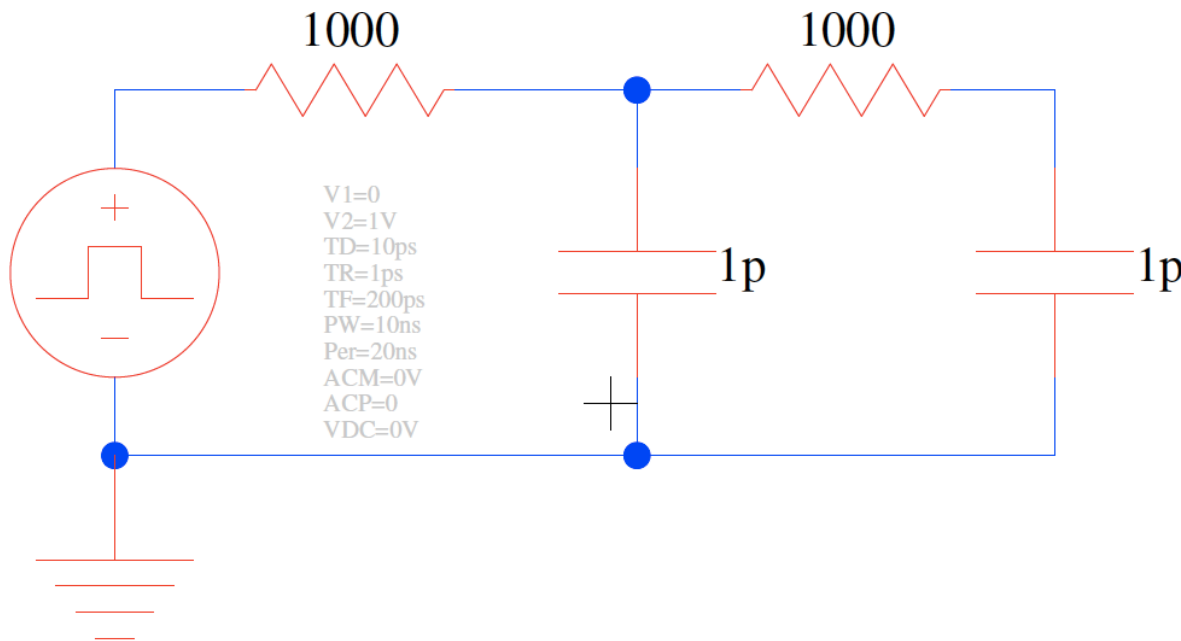- Look at series of R's on path
 - Must move $Q=V(\Sigma C)$ across each R



Elmore Delay: Distributed RC network

 - The delay from source s to node 5
 - $N =$ number of nodes in circuit




Elmore Delay: Distributed RC network

- The delay from source s to node 5
 - N = number of nodes in circuit

$$R_{5k} = \sum R_j \Rightarrow (R_j \in [\text{path}(s \rightarrow 5) \cap \text{path}(s \rightarrow k)])$$

$$\tau_{D5} = \sum_{k=1}^N C_k R_{5k}$$

 


Elmore Delay: Distributed RC network

- The delay from source s to node 5
 - N = number of nodes in circuit

$$R_{5k} = \sum R_j \Rightarrow (R_j \in [path(s \rightarrow 5) \cap path(s \rightarrow k)])$$

$$\tau_{D5} = \sum_{k=1}^N C_k R_{5k}$$

 


Elmore Delay: Distributed RC network

- The delay from source s to node 5
 - N = number of nodes in circuit

$$R_{5k} = \sum R_j \Rightarrow (R_j \in [\text{path}(s \rightarrow 5) \cap \text{path}(s \rightarrow k)])$$

$$\tau_{D5} = \sum_{k=1}^N C_k R_{5k}$$

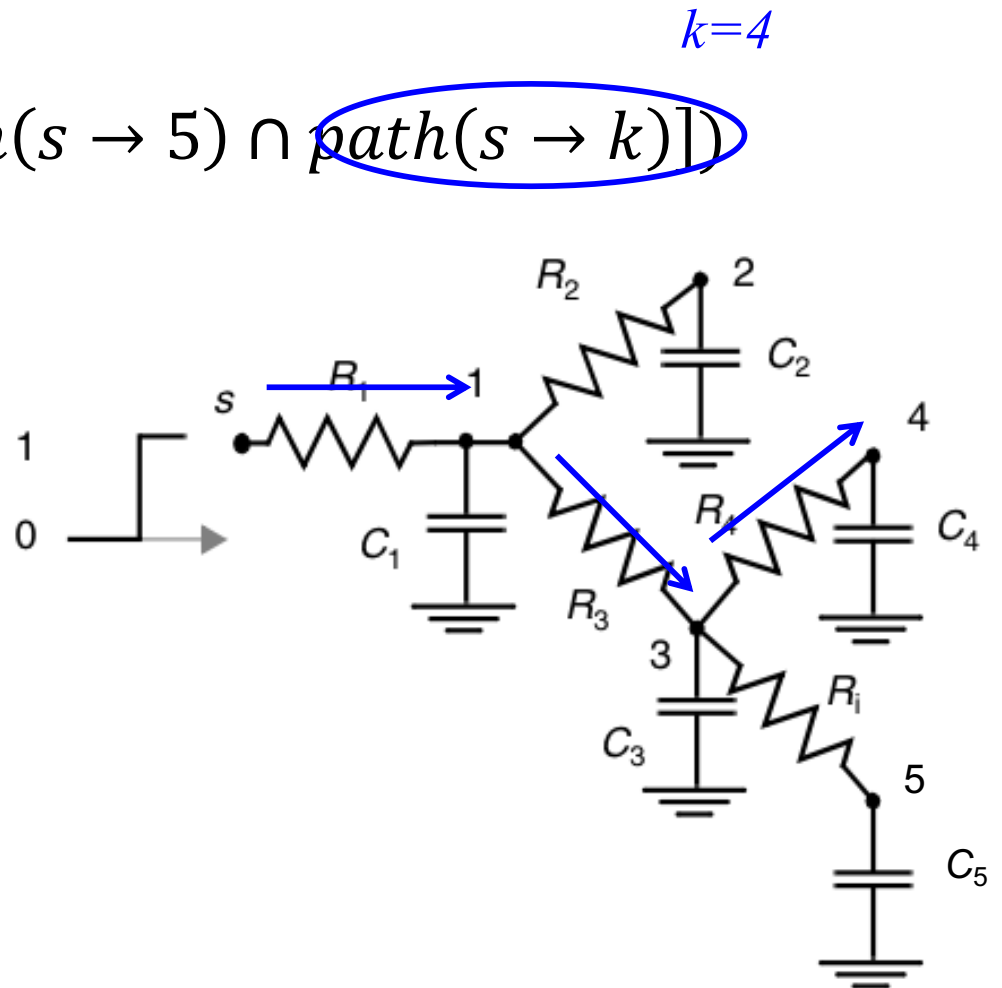


Elmore Delay: Distributed RC network

- The delay from source s to node 5
 - N = number of nodes in circuit

$$R_{5k} = \sum R_j \Rightarrow (R_j \in [\text{path}(s \rightarrow 5) \cap \text{path}(s \rightarrow k)])$$

$$\tau_{D5} = \sum_{k=1}^N C_k R_{5k}$$

 


Elmore Delay: Distributed RC network

- The delay from source s to node 5
 - N = number of nodes in circuit

$$R_{5k} = \sum R_j \Rightarrow (R_j \in [\text{path}(s \rightarrow 5) \cap \text{path}(s \rightarrow k)])$$

$$\tau_{D5} = \sum_{k=1}^N C_k R_{5k}$$

 


Elmore Delay: Distributed RC network

- The delay from source s to node 5
 - N = number of nodes in circuit

$$R_{5k} = \sum R_j \Rightarrow (R_j \in [\text{path}(s \rightarrow 5) \cap \text{path}(s \rightarrow k)])$$
 
$$\tau_{D5} = \sum_{k=1}^N C_k R_{5k} = ?$$




Elmore Delay: Distributed RC network

- The delay from source s to node 5
 - N = number of nodes in circuit

$$R_{5k} = \sum R_j \Rightarrow (R_j \in [path(s \rightarrow 5) \cap path(s \rightarrow k)])$$
 
$$\tau_{D5} = \sum_{k=1}^N C_k R_{5k} = ?$$




Elmore Delay: Practice

- The delay from source s to node O
 - N = number of nodes in circuit

$$R_{Ok} = \sum R_j \Rightarrow (R_j \in [\text{path}(s \rightarrow O) \cap \text{path}(s \rightarrow k)])$$
 
$$\tau_{DO} = \sum_{k=1}^N C_k R_{Ok} = ?$$





Idea

- ❑ There are other circuit disciplines
- ❑ Can use pass transistors for logic
 - Even chains of pass transistors
 - Mostly gives area win, sometimes gives delay win
 - Will talk more about delay on Monday
- ❑ Do not cascade as easily as CMOS
- ❑ Additional diffusion capacitance leads to distributed RC networks
 - More next lecture



Logic Types

- ❑ CMOS Gates
 - Dual pull-down and pull-up networks, only one enabled at a time
 - Performance of gate is strong function of the fanin of gate
 - Techniques to improve performance include sizing, input reordering, and buffering (staging)
- ❑ Ratioed Gates
 - Have active pull-down (-up) network connected to load device
 - Reduced gate complexity at expense of static power asymmetric transfer function
 - Techniques to improve performance include sizing to improve noise margins and reduce static power
- ❑ Pass Gates
 - Implement logic gate as switch network for reduced area and load capacitance
 - Long cascades of switches result in quadratic increase in delay
 - Also suffer from reduced noise margins (V_T drop)
 - Use level-restoring buffers to improve noise margins



Admin

□ Project 1

- Milestones were mostly all good
 - Show me the results! Justify all metrics
- Use Piazza and office hours
- Should be working hard on project
 - Not enough to know what to do. You have to actually do it.
- Rewarding experience and worth the time once you get it
 - Design and test takes time