

# ESE370: Circuit-Level Modeling, Design, and Optimization for Digital Systems

---

Lec 21: October 27, 2021

Distributed RC Wire and Elmore Delay





# Today

---


- Estimate delay in RC Network
  - Elmore delay calculation
- Apply to wire delay
- Apply to pass transistor circuits




# Previously: Equivalent RC

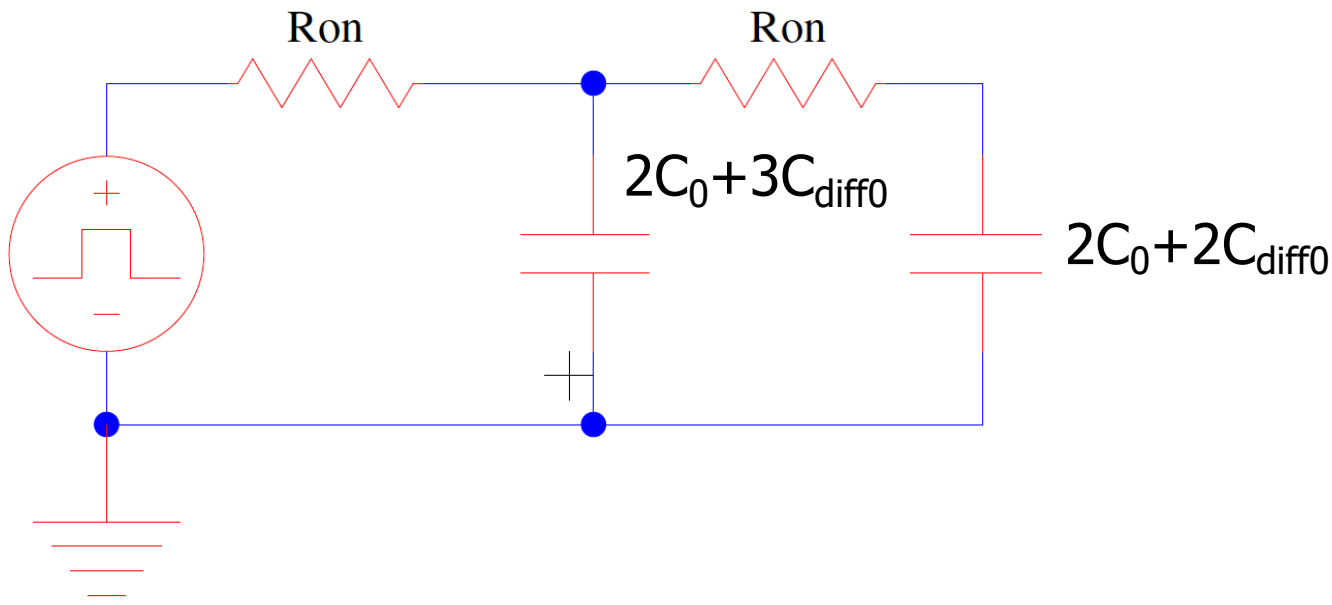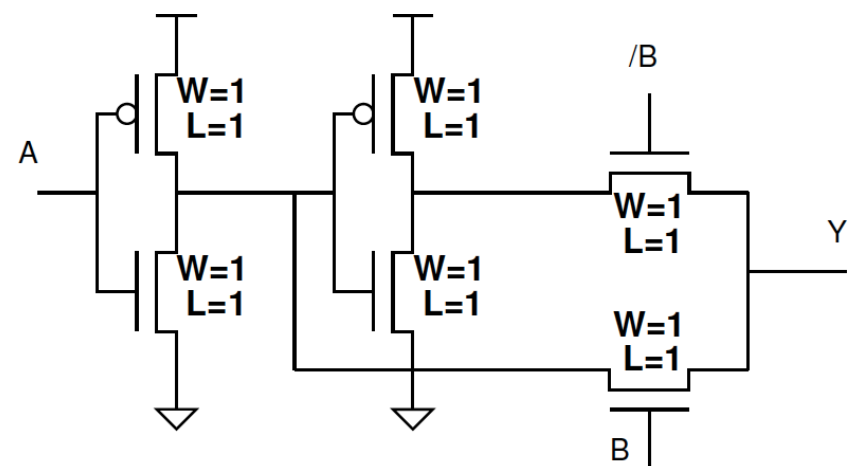
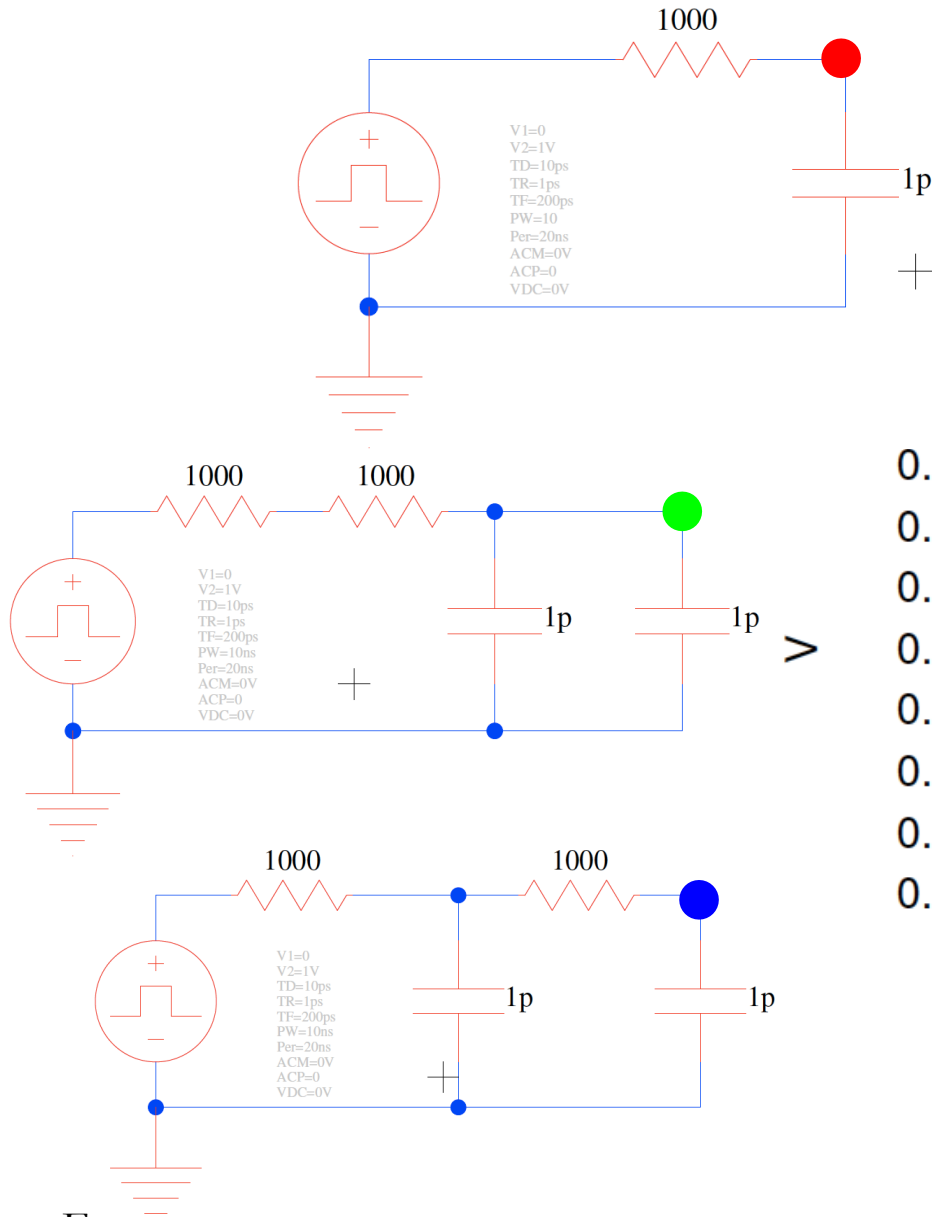
# Previously: Distributed RC (preclass 1)



□ What are the time constants?

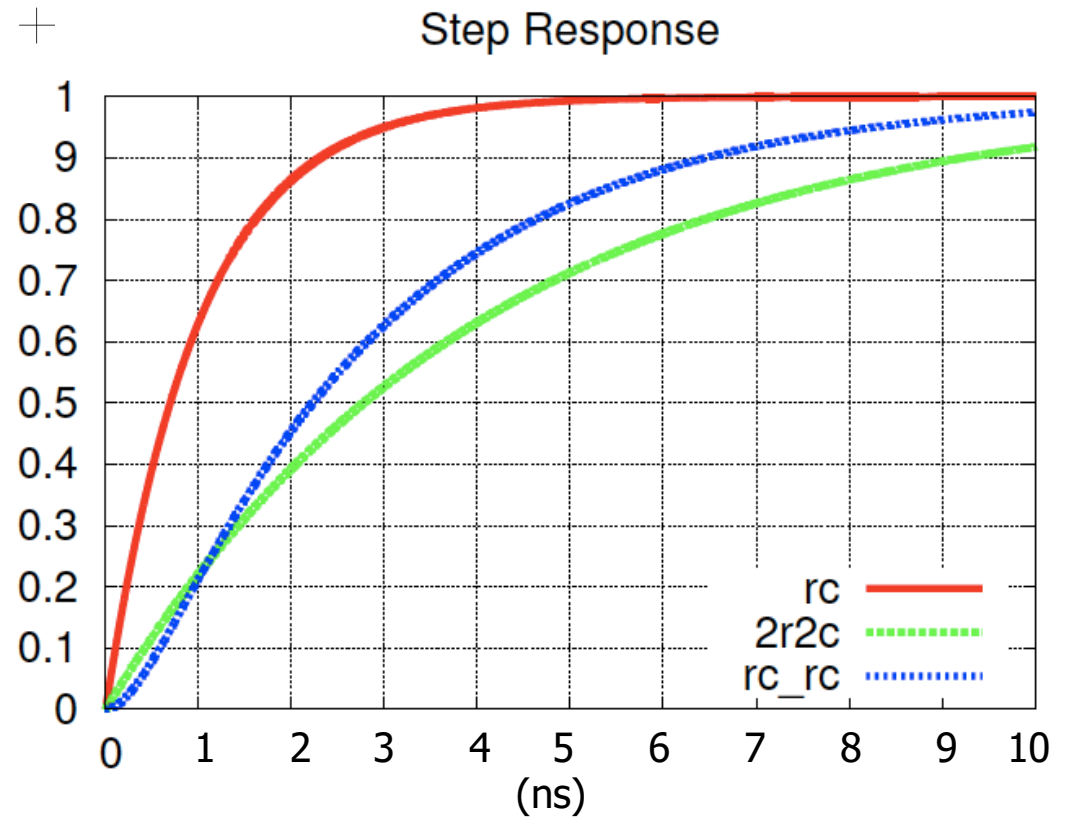


# Elmore Delay: Distributed RC network

- The delay from source  $s$  to node 5
  - $N$  = number of nodes in circuit



$$R_{5k} = \sum R_j \Rightarrow (R_j \in [\text{path}(s \rightarrow 5) \cap \text{path}(s \rightarrow k)])$$

$$\tau_{D5} = \sum_{k=1}^N C_k R_{5k}$$

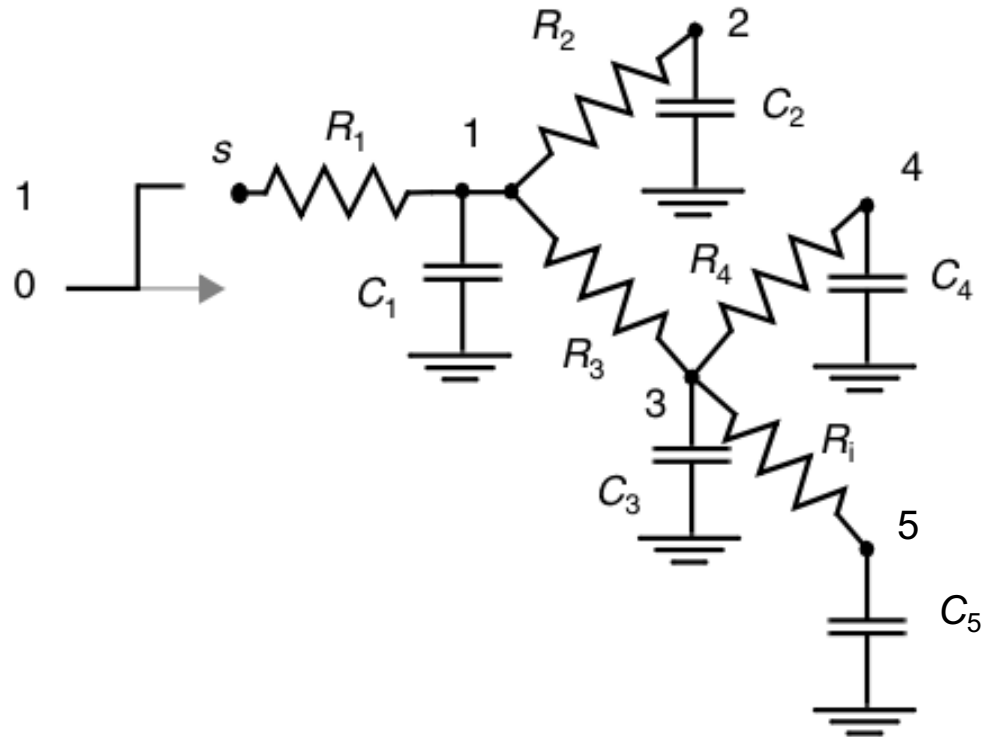



# What is response?

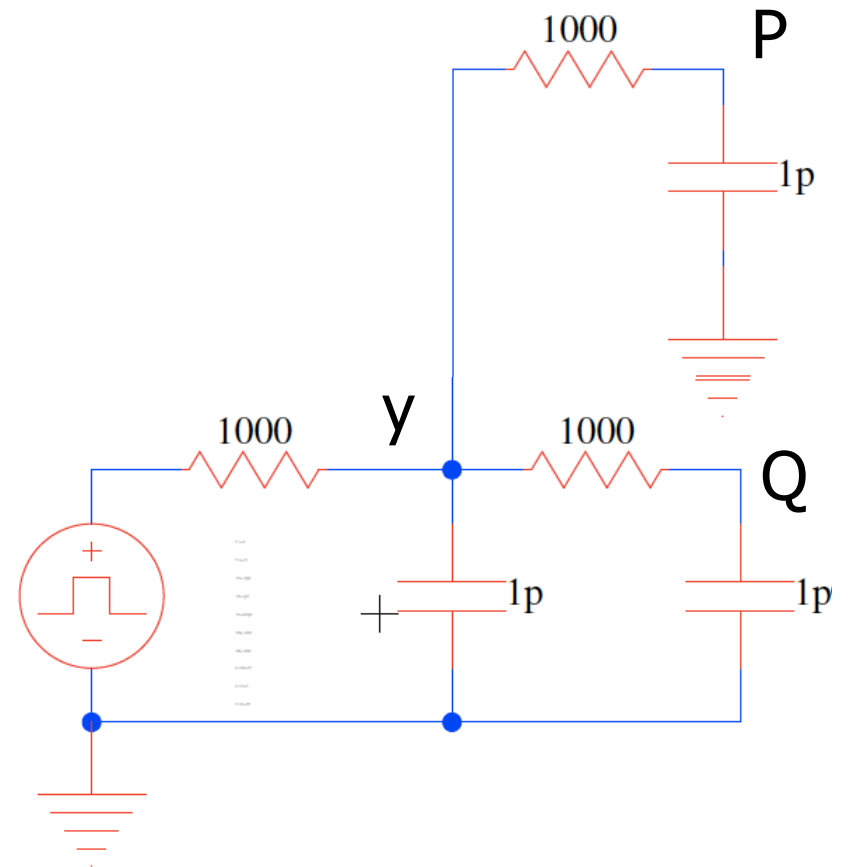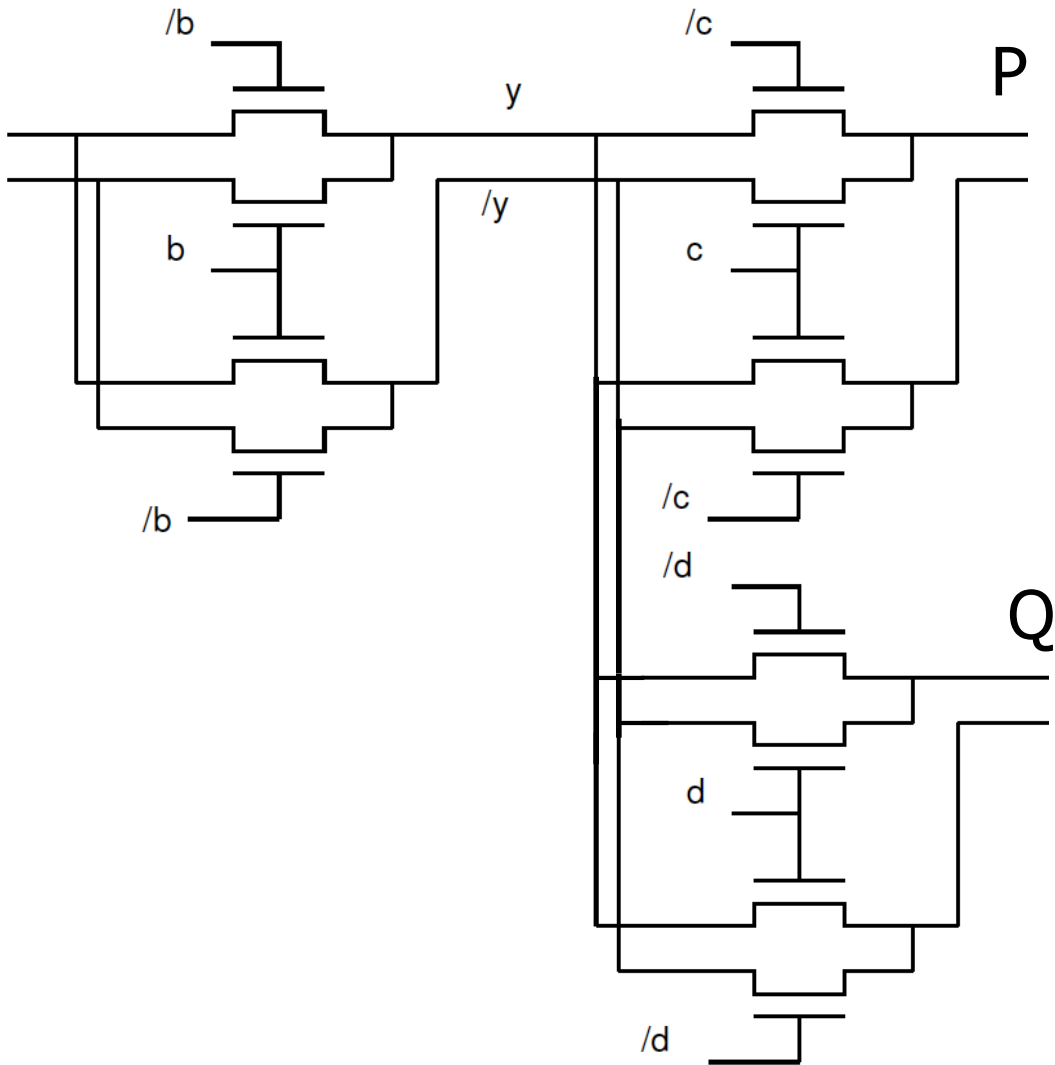


# Elmore Delay: Practice (preclass 1)

- The delay from source  $s$  to node  $i$ 
  - $N$  = number of nodes in circuit

$$R_{ik} = \sum R_j \Rightarrow (R_j \in [path(s \rightarrow i) \cap path(s \rightarrow k)])$$


$$\tau_{Di} = \sum_{k=1}^N C_k R_{ik}$$

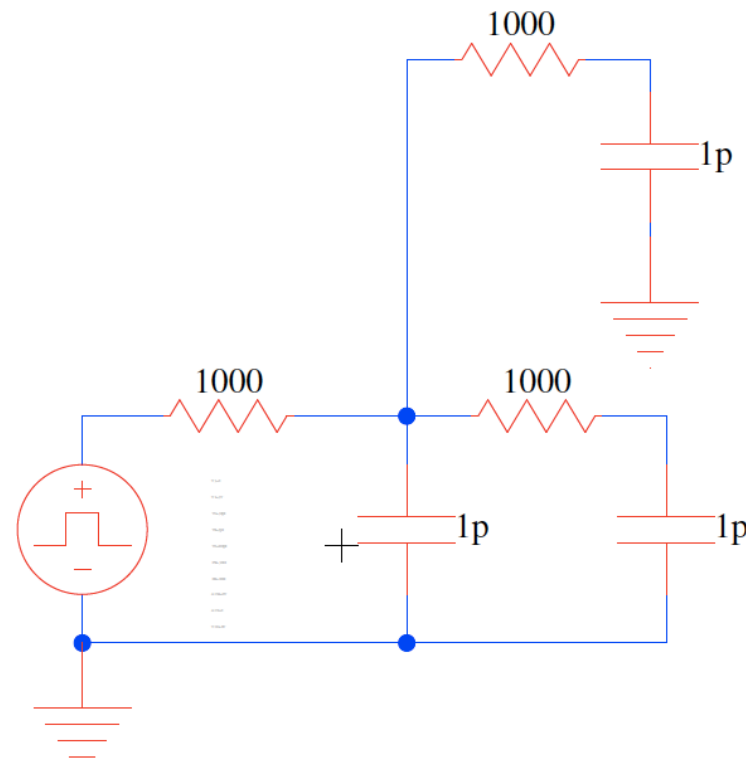


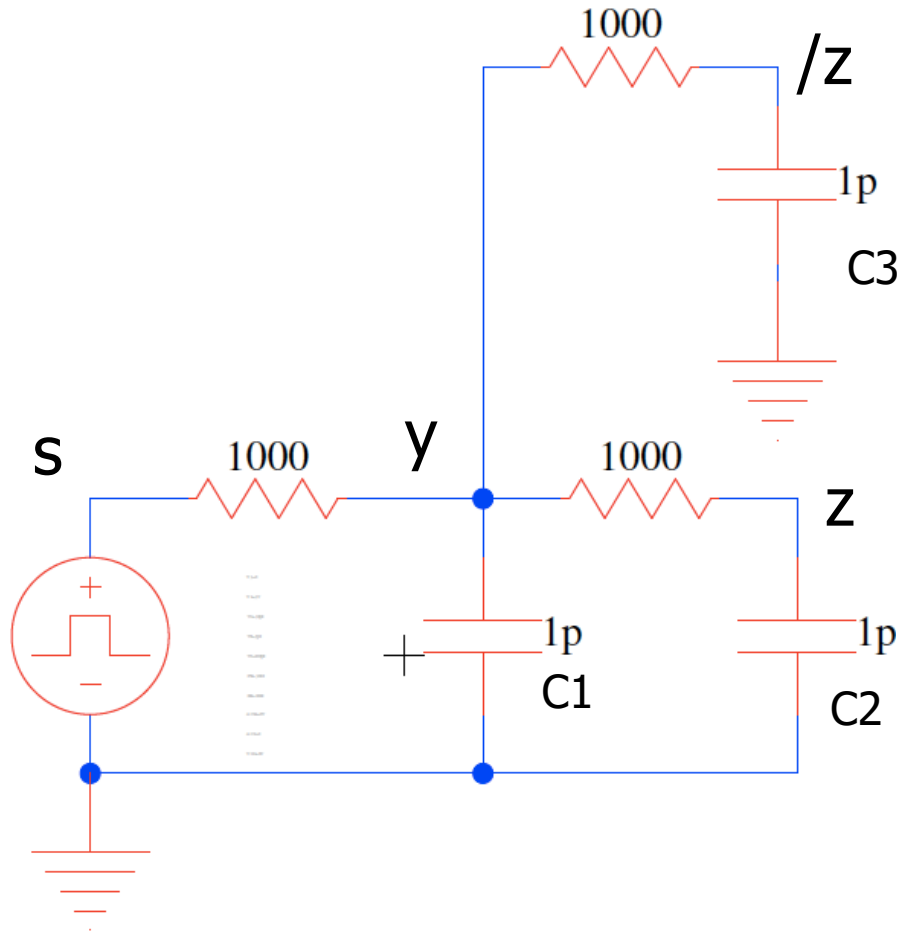
# Apply (preclass 1)



- What is Elmore delay?
  - $S \rightarrow Z$








# SPICE Response

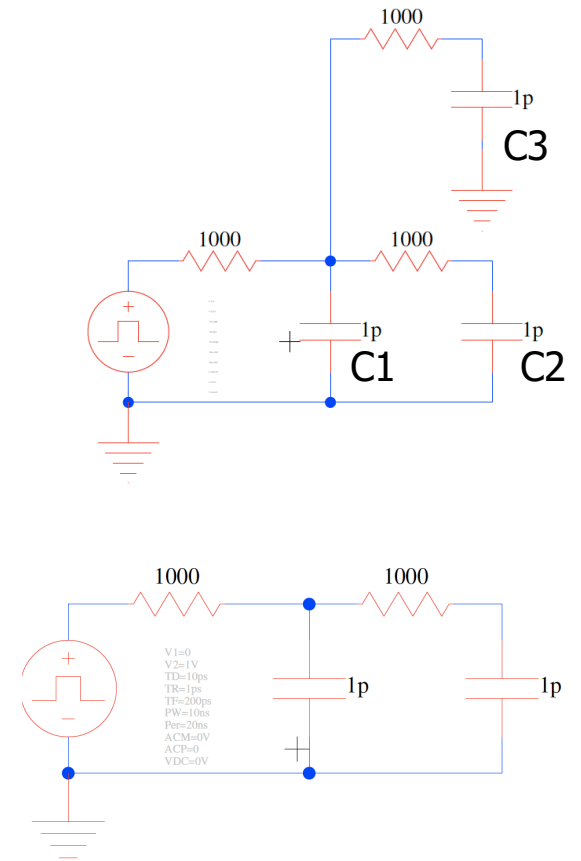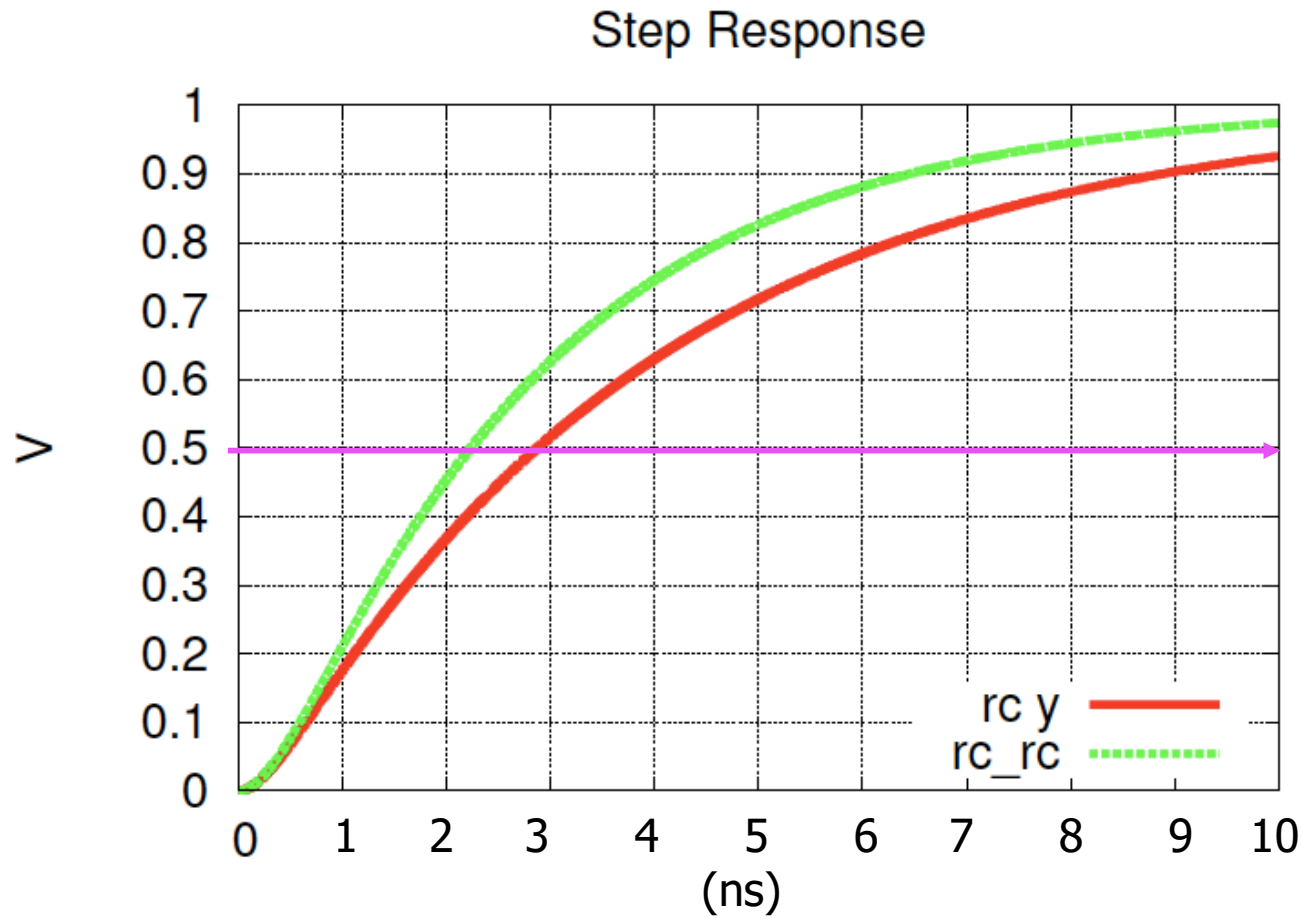
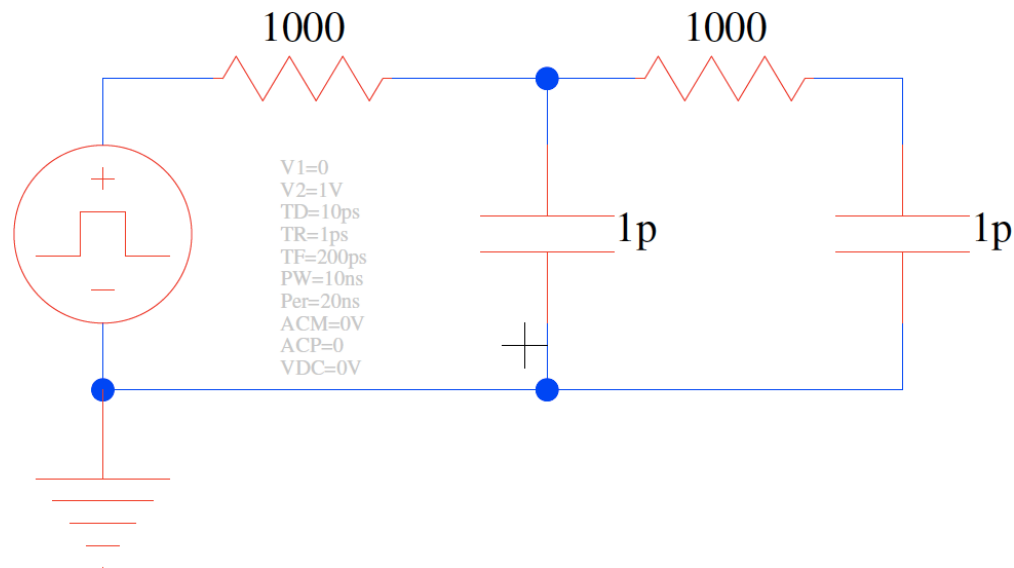
# Elmore Delay: Special Ladder Case

- For each resistor  $C_k$  in path
  - Compute  $R_{kk} =$  sum of all Rs upstream of  $C_k$

$$\tau_{DN} = \sum_{k=1}^N C_k \sum_{j=1}^k R_j = \sum_{k=1}^N C_k R_{kk}$$




# Elmore Delay: Special Ladder Case

- For each resistor  $C_k$  in path
  - Compute  $R_{kk} =$  sum of all Rs upstream of  $C_k$

$$\tau_{DN} = \sum_{k=1}^N C_k \sum_{j=1}^k R_j = \sum_{k=1}^N C_k R_{kk}$$

$$C_1 * (R_1) + C_2 * (R_1 + R_2)$$

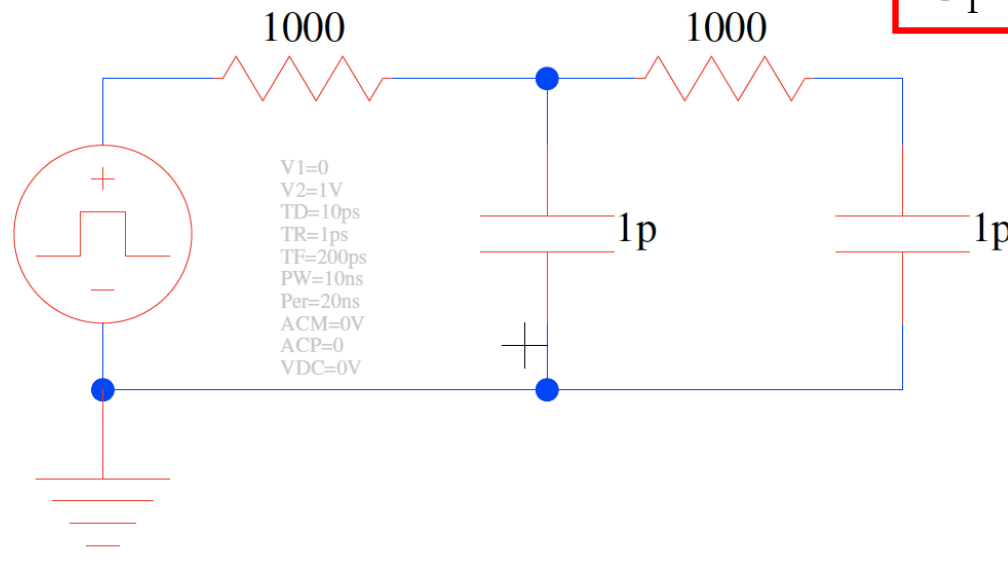


# Elmore Delay: Special Ladder Case

- For each resistor  $C_k$  in path
  - Compute  $R_{kk} =$  sum of all Rs upstream of  $C_k$

$$\tau_{DN} = \sum_{k=1}^N C_k \sum_{j=1}^k R_j = \sum_{k=1}^N C_k R_{kk}$$

$$C_1 * (R_1) + C_2 * (R_1 + R_2)$$

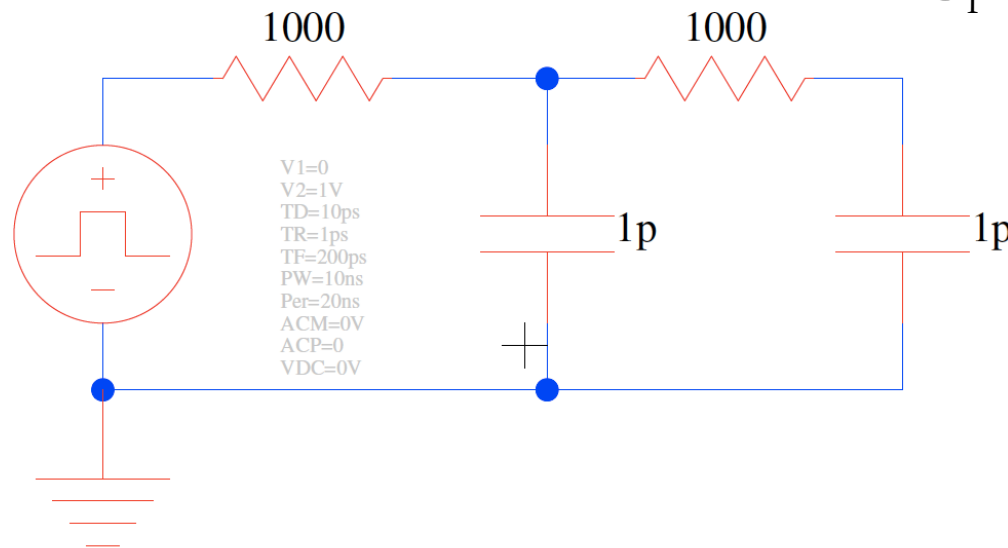

$$= 3RC$$


$$= 3ns$$

# Compare KCL: Setup
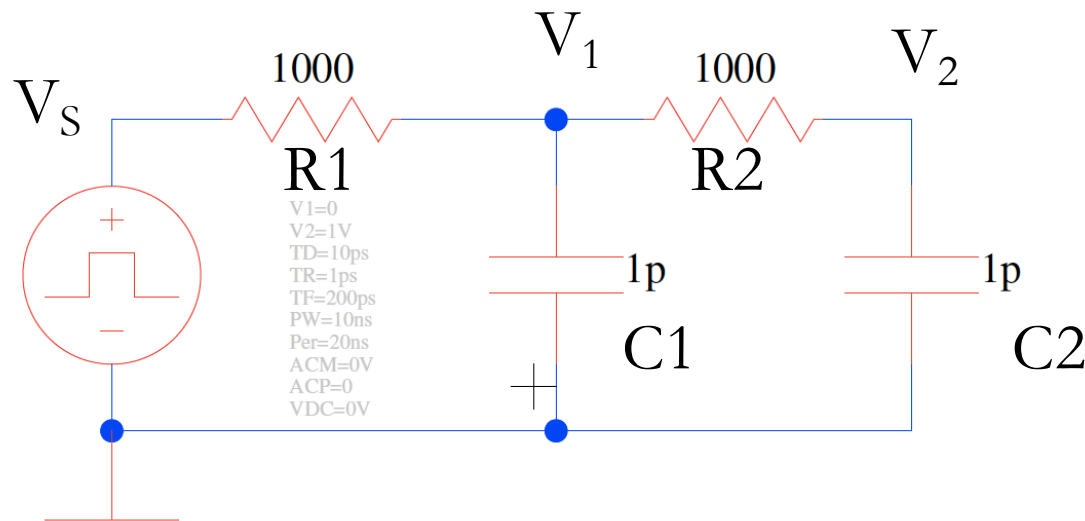
## □ Equations from KCL?

$$\text{@}V_1: \frac{V_S - V_1}{R_1} = \frac{V_1 - V_2}{R_2} + C_1 \frac{dV_1}{dt}$$

$$\text{@}V_2: \frac{V_1 - V_2}{R_2} = C_2 \frac{dV_2}{dt}$$



# Compare KCL: Math

@ $V_1$ :

$$\frac{V_S - V_1}{R_1} = \frac{V_1 - V_2}{R_2} + C_1 \frac{dV_1}{dt}$$

$$\frac{V_S}{R_1} = \frac{V_1}{R_1} + \frac{V_1}{R_2} - \frac{V_2}{R_2} + C_1 \frac{dV_1}{dt}$$

$$V_S = V_1 \left( 1 + \frac{R_1}{R_2} \right) - \frac{R_1 V_2}{R_2} + R_1 C_1 \frac{dV_1}{dt}$$

@ $V_2$ :

$$\frac{V_1 - V_2}{R_2} = C_2 \frac{dV_2}{dt}$$

$$\frac{V_1}{R_2} = \frac{V_2}{R_2} + C_2 \frac{dV_2}{dt}$$

$$V_1 = V_2 + R_2 C_2 \frac{dV_2}{dt}$$

$$\frac{dV_1}{dt} = \frac{dV_2}{dt} + R_2 C_2 \frac{d^2 V_2}{dt^2}$$



# Compare KCL: Math

---

$$V_S = V_1 \left( 1 + \frac{R_1}{R_2} \right) - \frac{R_1}{R_2} V_2 + R_1 C_1 \frac{dV_1}{dt}$$

$$V_S = \left( V_2 + R_2 C_2 \frac{dV_2}{dt} \right) \left( 1 + \frac{R_1}{R_2} \right) - \frac{R_1}{R_2} V_2 + R_1 C_1 \left( \frac{dV_2}{dt} + R_2 C_2 \frac{d^2 V_2}{dt^2} \right)$$

$$V_S = V_2 + \left( R_2 C_2 \left( 1 + \frac{R_1}{R_2} \right) + R_1 C_1 \right) \frac{dV_2}{dt} + R_1 C_1 R_2 C_2 \frac{d^2 V_2}{dt^2}$$

$$V_S = V_2 + (R_2 C_2 + R_1 C_2 + R_1 C_1) \frac{dV_2}{dt} + R_1 C_1 R_2 C_2 \frac{d^2 V_2}{dt^2}$$



# Compare KCL: Math

---

$$R_1 = R_2 = R$$

$$C_1 = C_2 = C$$

$$V_S = V_2 + (R_2 C_2 + R_1 C_2 + R_1 C_1) \frac{dV_2}{dt} + R_1 C_1 R_2 C_2 \frac{d^2 V_2}{dt^2}$$

$$V_S = V_2 + 3RC \frac{dV_2}{dt} + R^2 C^2 \frac{d^2 V_2}{dt^2}$$





# Compare KCL: Math

---

$$R_1 = R_2 = R$$

$$C_1 = C_2 = C$$

$$V_S = V_2 + (R_2 C_2 + R_1 C_2 + R_1 C_1) \frac{dV_2}{dt} + R_1 C_1 R_2 C_2 \frac{d^2 V_2}{dt^2}$$

$$V_S = V_2 + 3RC \frac{dV_2}{dt} + R^2 C^2 \frac{d^2 V_2}{dt^2}$$

$$V_2 = A(1 + e^{-\alpha t}) \rightarrow$$

$$V_S = A(1 + e^{-\alpha t}) - 3RC \cdot \alpha A e^{-\alpha t} + R^2 C^2 \cdot \alpha^2 A e^{-\alpha t}$$



# Compare KCL: Math

---

$$V_2 = A(1 + e^{-\alpha t}) \rightarrow$$

$$V_S = A(1 + e^{-\alpha t}) - 3RC \cdot \alpha A e^{-\alpha t} + R^2 C^2 \cdot \alpha^2 A e^{-\alpha t}$$

$$t = \infty \rightarrow V_2 = V_S = A$$



# Compare KCL: Math

---

$$V_2 = A(1 + e^{-\alpha t}) \rightarrow$$

$$V_S = A(1 + e^{-\alpha t}) - 3RC \cdot \alpha A e^{-\alpha t} + R^2 C^2 \cdot \alpha^2 A e^{-\alpha t}$$

$$t = \infty \rightarrow V_2 = V_S = A$$

$$V_S = V_S(1 + e^{-\alpha t}) - 3RC \cdot \alpha V_S e^{-\alpha t} + R^2 C^2 \cdot \alpha^2 V_S e^{-\alpha t}$$

$$0 = e^{-\alpha t} - 3RC \cdot \alpha e^{-\alpha t} + R^2 C^2 \cdot \alpha^2 e^{-\alpha t}$$

$$0 = e^{-\alpha t} (1 - 3RC\alpha + R^2 C^2 \cdot \alpha^2)$$

$$0 = 1 - 3RC\alpha + R^2 C^2 \cdot \alpha^2$$


# Compare KCL: Math

$$V_2 = V_S(1 + e^{-\alpha t})$$

$$0 = 1 - 3RC\alpha + R^2C^2 \cdot \alpha^2$$

$$\alpha = \frac{3RC \pm \sqrt{9(RC)^2 - 4(RC)^2}}{2(RC)^2} = \frac{3RC \pm \sqrt{5}RC}{2(RC)^2} = \frac{3 \pm \sqrt{5}}{2RC}$$
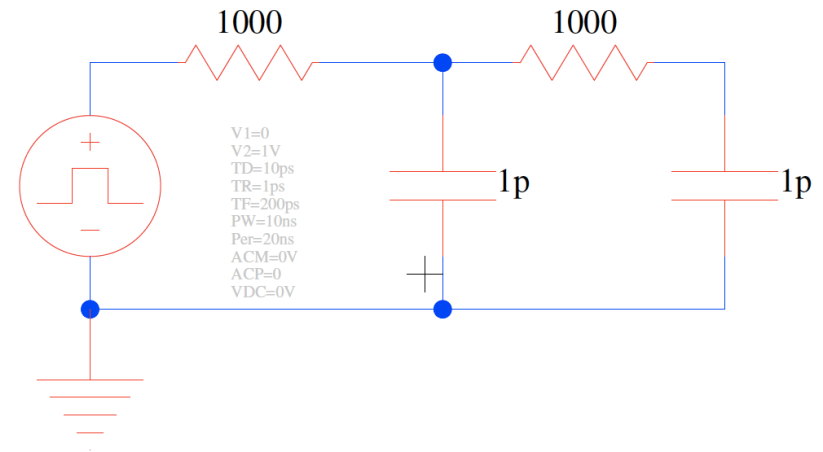
$$\rightarrow \tau = \frac{2}{3 \pm \sqrt{5}} RC \approx 2.6RC$$




# Compare KCL: Math

$$V_2 = V_S(1 + e^{-\alpha t})$$

$$0 = 1 - 3RC\alpha + R^2C^2 \cdot \alpha^2$$

$$\alpha = \frac{3RC \pm \sqrt{9(RC)^2 - 4(RC)^2}}{2(RC)^2} = \frac{3RC \pm \sqrt{5}RC}{2(RC)^2} = \frac{3 \pm \sqrt{5}}{2RC}$$
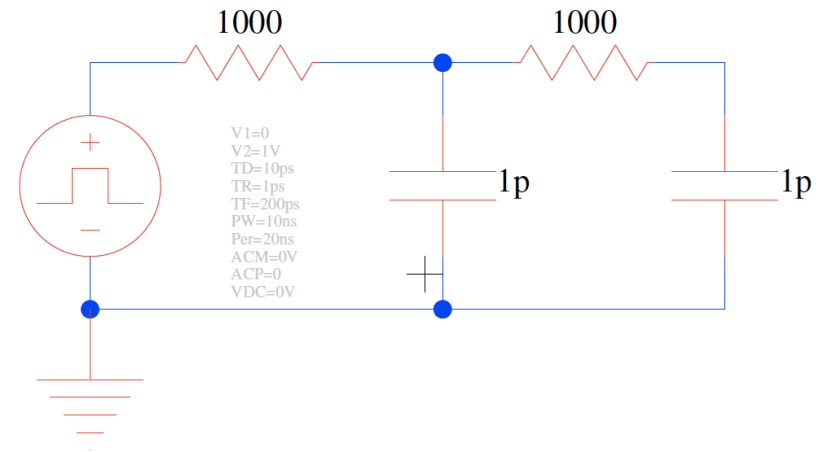
$$\rightarrow \tau = \frac{2}{3 \pm \sqrt{5}} RC \approx 2.6RC$$



$$= 3RC$$
$$= 3\text{ns}$$

# Elmore Delay: Distributed RC network

- The delay from source to node  $i$ 
  - $N$  = number of nodes in circuit

$$R_{ik} = \sum R_j \Rightarrow (R_j \in [\text{path}(s \rightarrow i) \cap \text{path}(s \rightarrow k)])$$

$$\tau_{Di} = \sum_{k=1}^N C_k R_{ik}$$


- Special ladder case

$$\tau_{DN} = \sum_{k=1}^N C_k \sum_{j=1}^k R_j = \sum_{k=1}^N C_k R_{kk}$$

# Wire Delay

---

# Wire Resistance

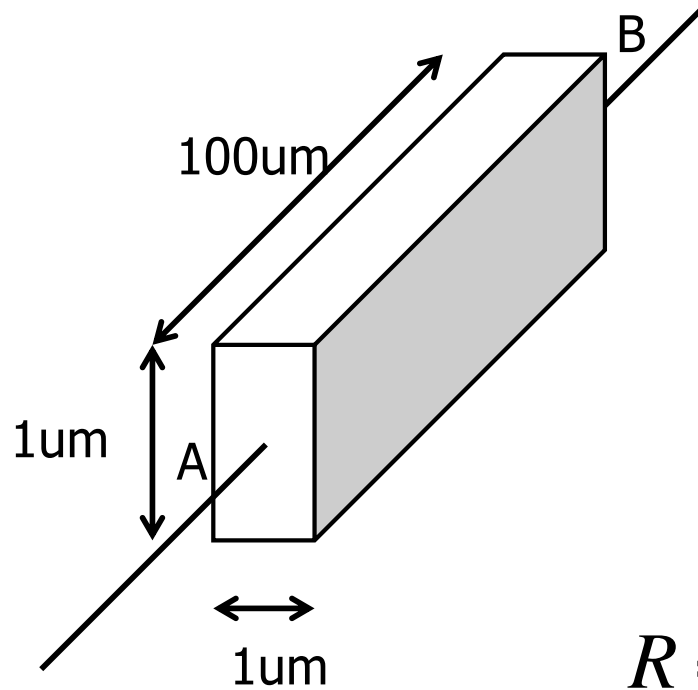

$$R = \frac{\rho L}{A}$$


$$R = \frac{10^{-7} \Omega \cdot m \cdot 100 \mu m}{1 \mu m \cdot 1 \mu m} = 10 \Omega$$






# Wire Capacitance

$$C = \epsilon_d \frac{A}{d}$$

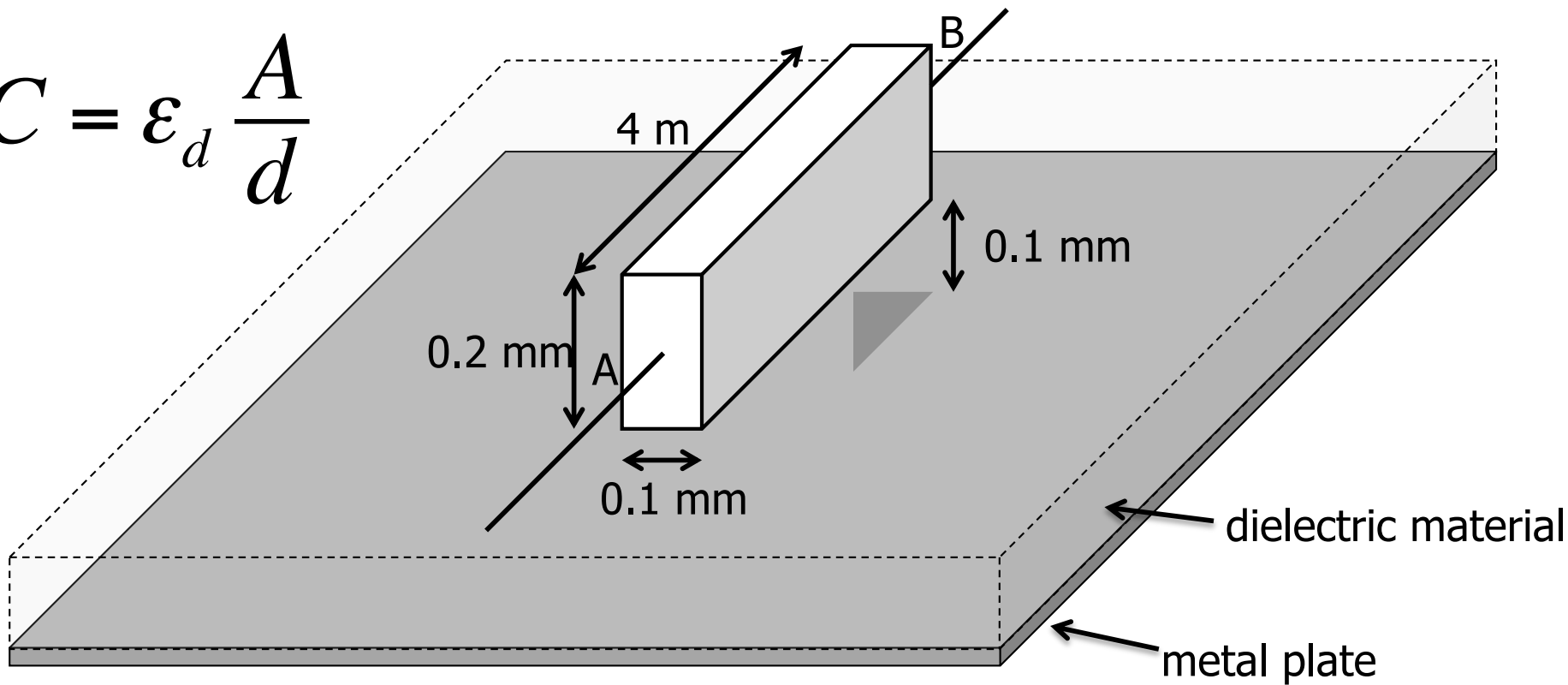
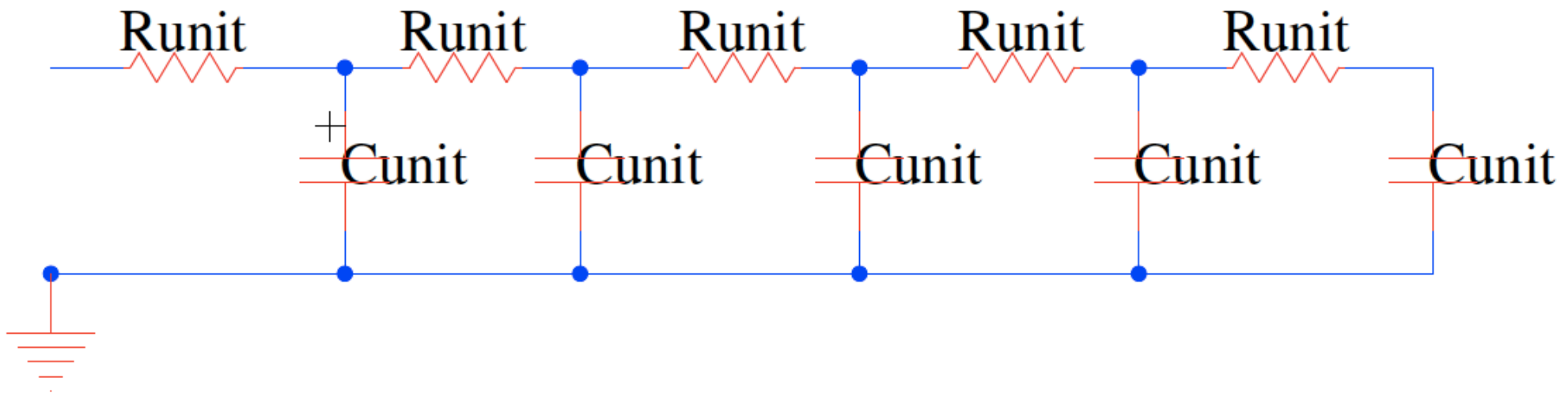
# Wire as Distributed RC Ladder


- Measure wire length in units
  - Say  $\lambda$
  - Each  $\lambda$  unit has  $C_{\text{unit}}, R_{\text{unit}}$ 
    - Unit capacitance and resistance of wire of length  $\lambda$





# Wire Delay

- Delay of Wire  $N$  units long:

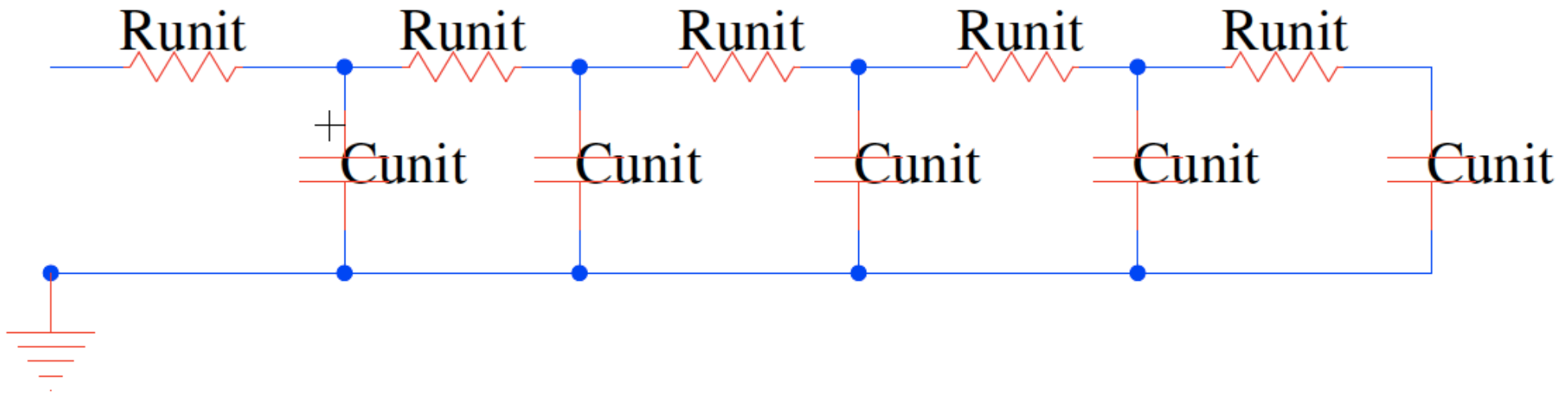




# Wire Delay

□ Delay of Wire N units long:

$$R_{\text{unit}} C_{\text{unit}}$$

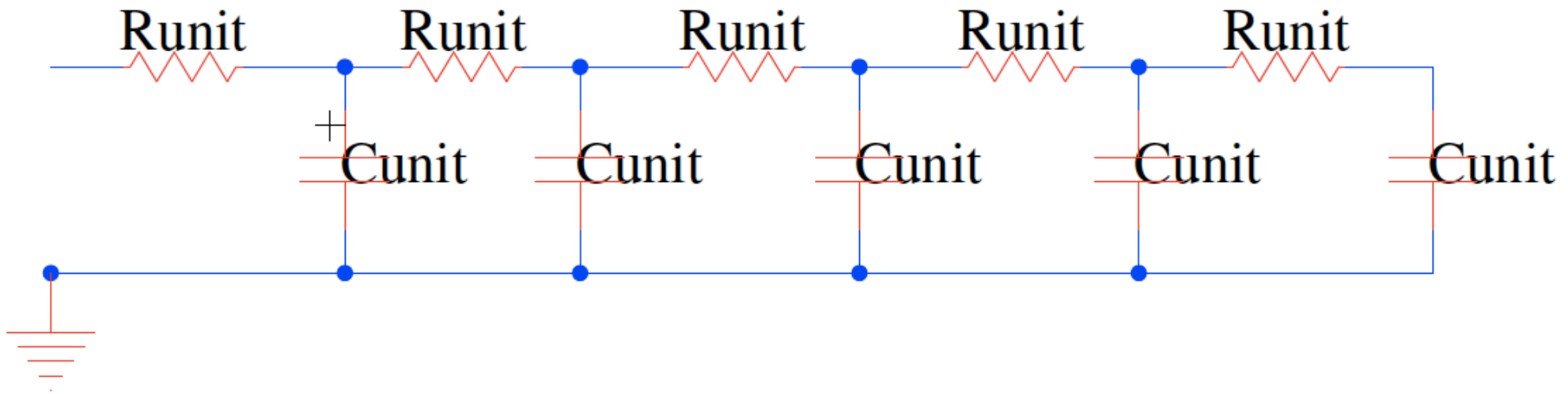



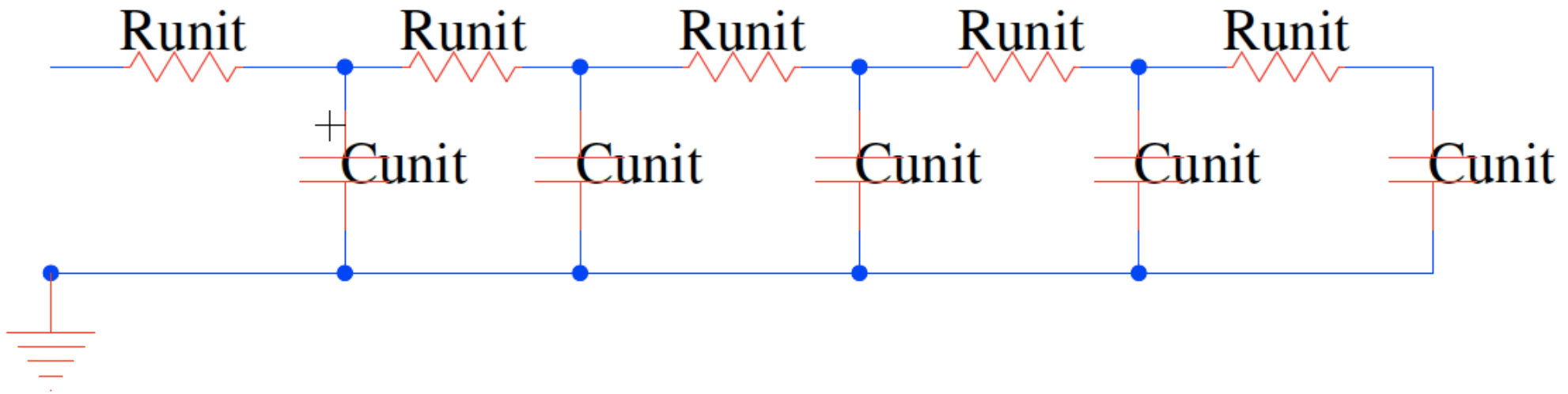
# Wire Delay

□ Delay of Wire N units long:

$$R_{\text{unit}}C_{\text{unit}} + 2R_{\text{unit}}C_{\text{unit}}$$





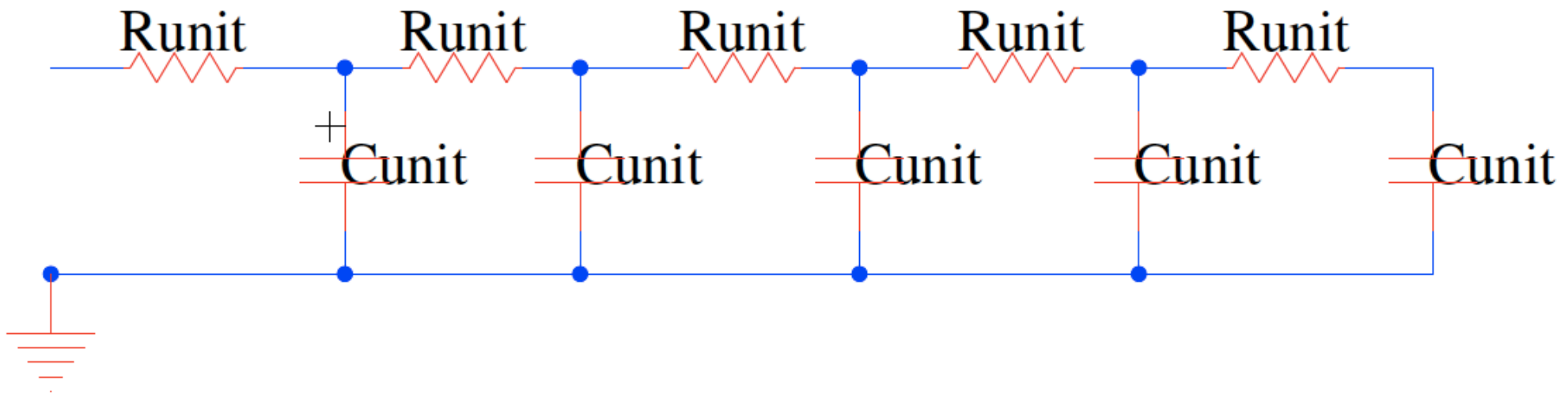
# Wire Delay

□ Delay of Wire N units long:

$$\begin{aligned} & R_{\text{unit}} C_{\text{unit}} \\ & + 2R_{\text{unit}} C_{\text{unit}} \\ & + 3R_{\text{unit}} * C_{\text{unit}} + \dots + NR_{\text{unit}} * C_{\text{unit}} \\ & = (R_{\text{unit}} * C_{\text{unit}}) * (N + (N-1) + (N-2) + \dots + 1) \end{aligned}$$





# Sum of integers (preclass 2)

---

- What's the sum of the integer 1 to N?

$$\sum_{k=0}^N k =$$



# Sum of integers

---

- What's the sum of the integer 1 to N?


$$\sum_{k=0}^N k = \frac{N(N+1)}{2} \approx \frac{N^2}{2}$$


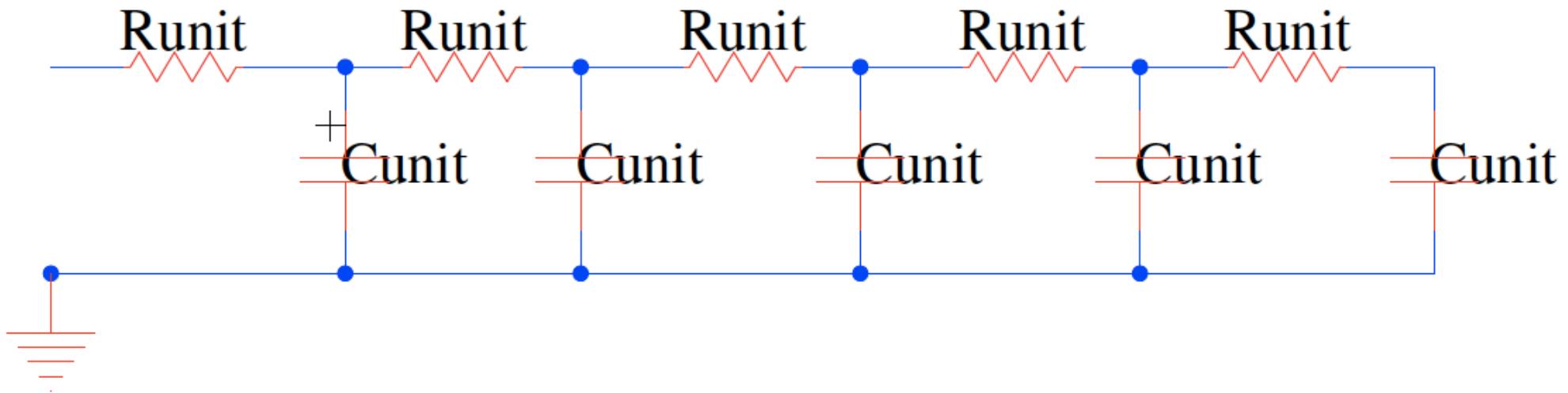
# Wire Delay (preclass 3)

□ Delay of Wire N units long:

$$\begin{aligned} & R_{\text{unit}} * (N * C_{\text{unit}}) \\ & + R_{\text{unit}} * ((N-1) * C_{\text{unit}}) \\ & + R_{\text{unit}} * (N-2) * C_{\text{unit}} + \dots + R_{\text{unit}} * C_{\text{unit}} \\ & = (R_{\text{unit}} * C_{\text{unit}}) * (N + N-1 + N-2 + \dots + 1) \\ & \sim R_{\text{unit}} C_{\text{unit}} * N^2 / 2 \end{aligned}$$




# Lumped RC Wire? (preclass 4)

- What would the delay be if we treated the wire as lumped R and C?

$$R_{\text{wire}} = N \times R_{\text{unit}}$$
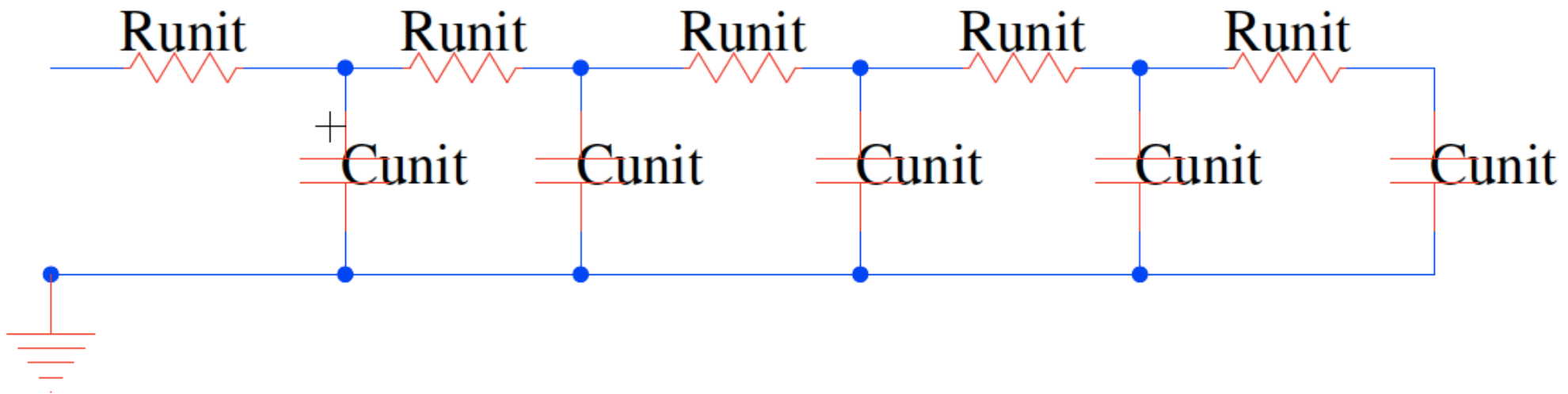
$$C_{\text{wire}} = N \times C_{\text{unit}}$$





# Wire Delay

---

- ❑  $R_{\text{wire}} = N * R_{\text{unit}}$
- ❑  $C_{\text{wire}} = N * C_{\text{unit}}$
- ❑ Lumped RC wire delay =  $R_{\text{unit}} * C_{\text{unit}} * N^2$
- ❑ Distributed RC Wire delay =  $R_{\text{unit}} * C_{\text{unit}} * N^2 / 2$
  
- ❑ Distributed has half the delay of lumped RC product
- ❑ Delay is quadratic in length of wire in both cases

# Apply to Gates



---

## Pass Transistor and CMOS




# Pass Transistor XOR

□ Delay when  $A=B=1$ ?

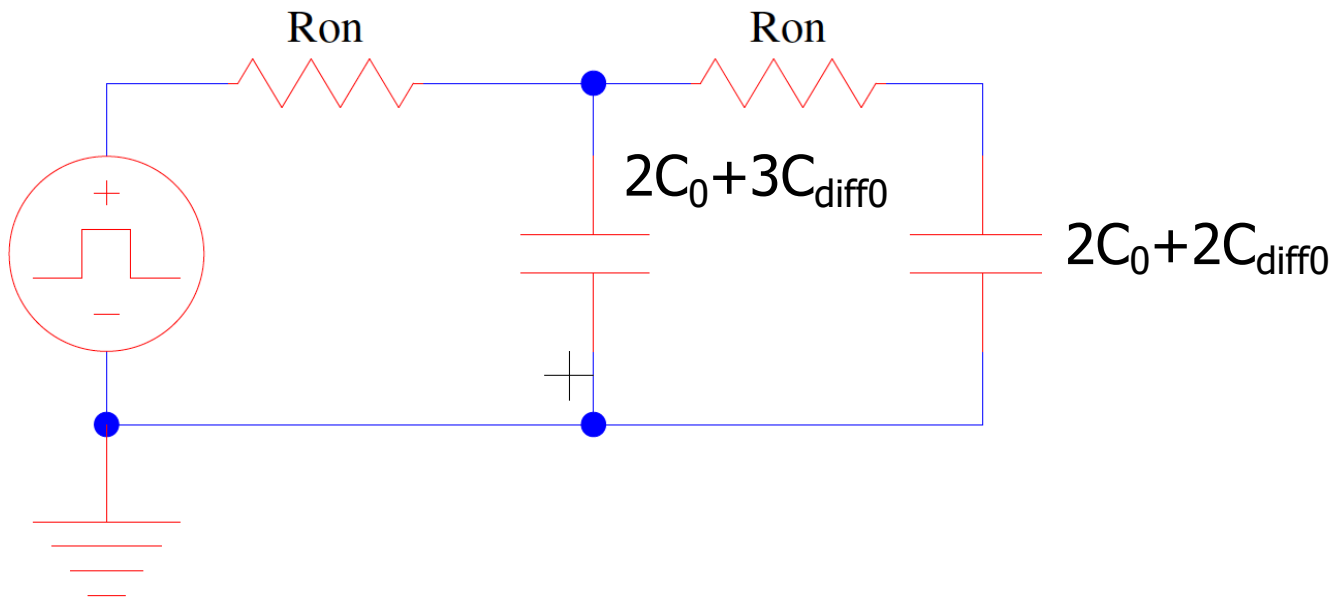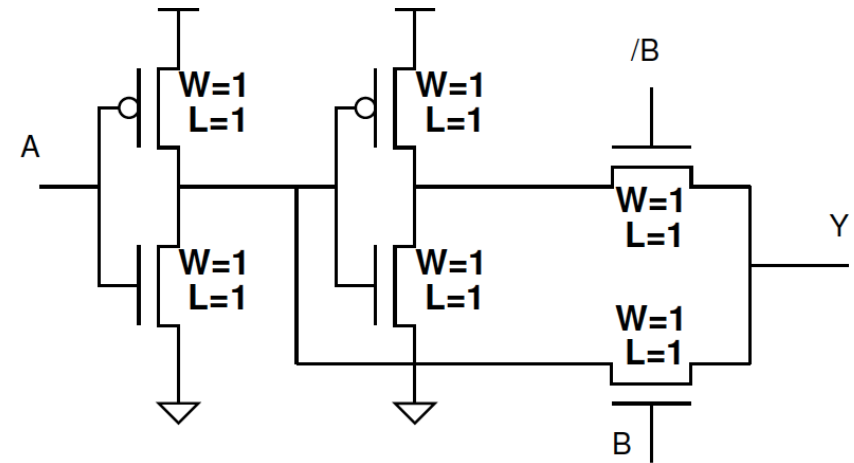
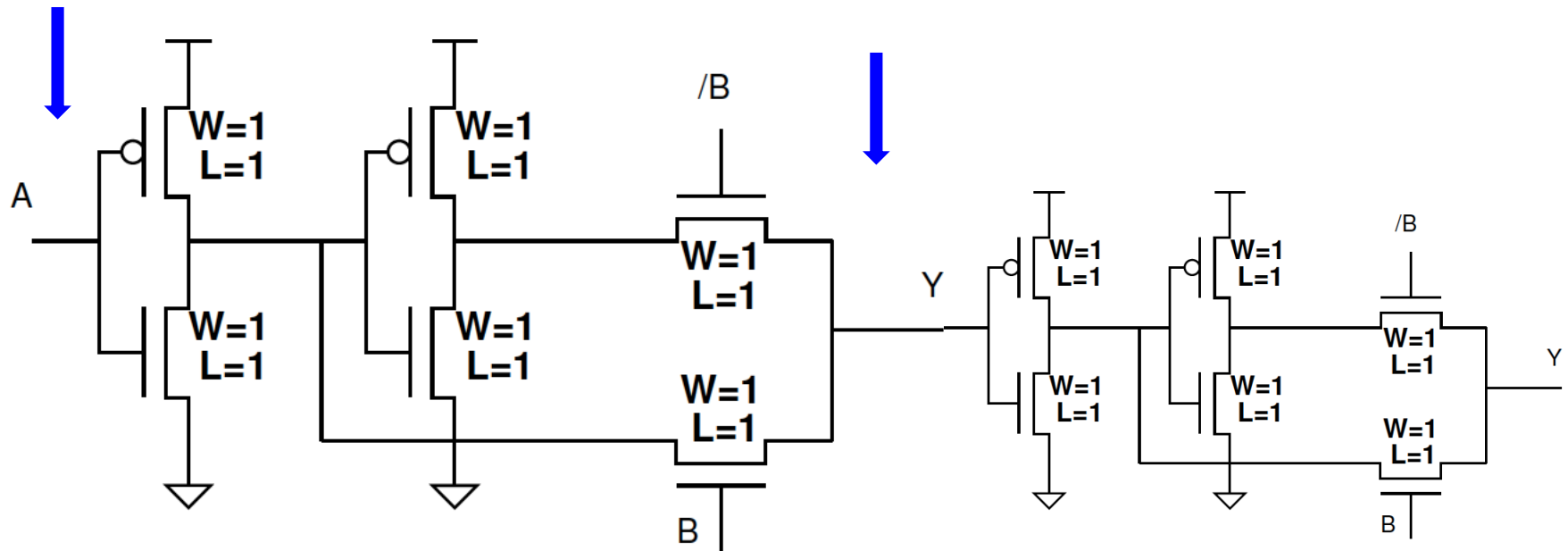
# Pass Transistor XOR (preclass 5)

- Delay when  $A=1, B=0$ ?
  - Start with equivalent RC circuit






# Unbuffered (preclass 6)

□ Circuit → Delay?

■ 2 stages

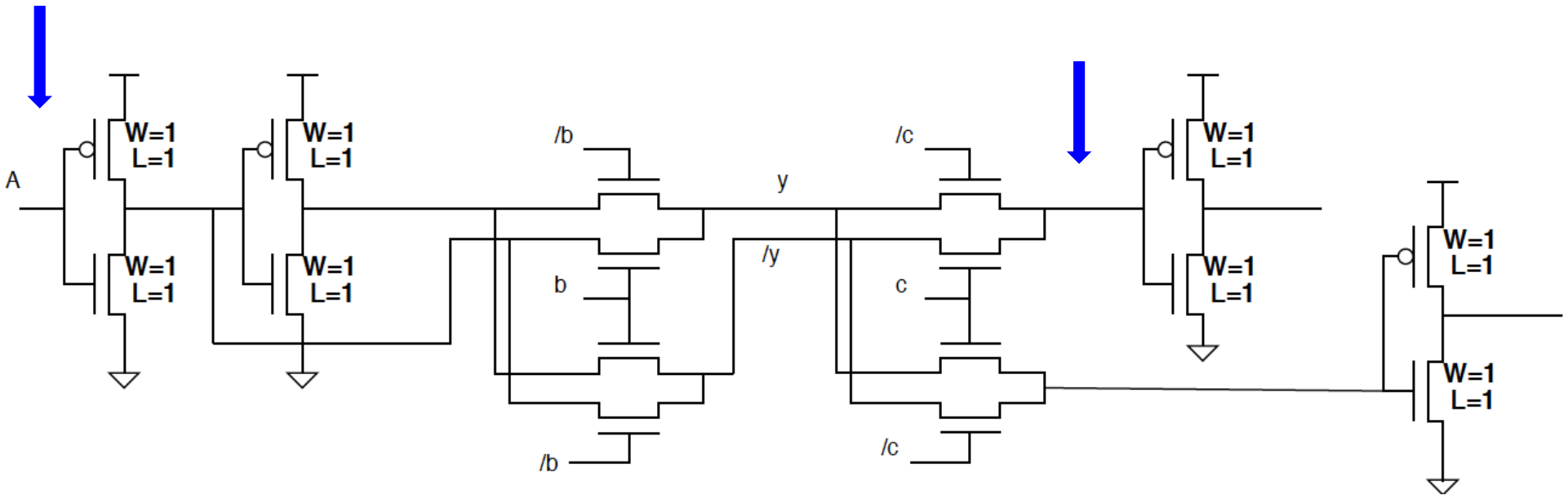




# Unbuffered (preclass 7)

□ Circuit → Delay?

■ 3 stages

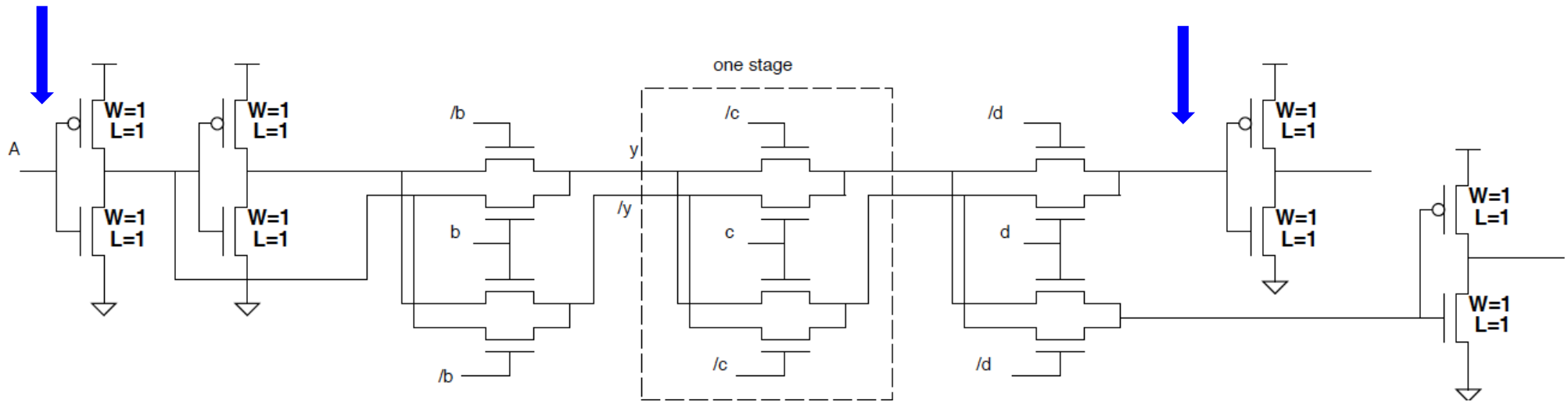






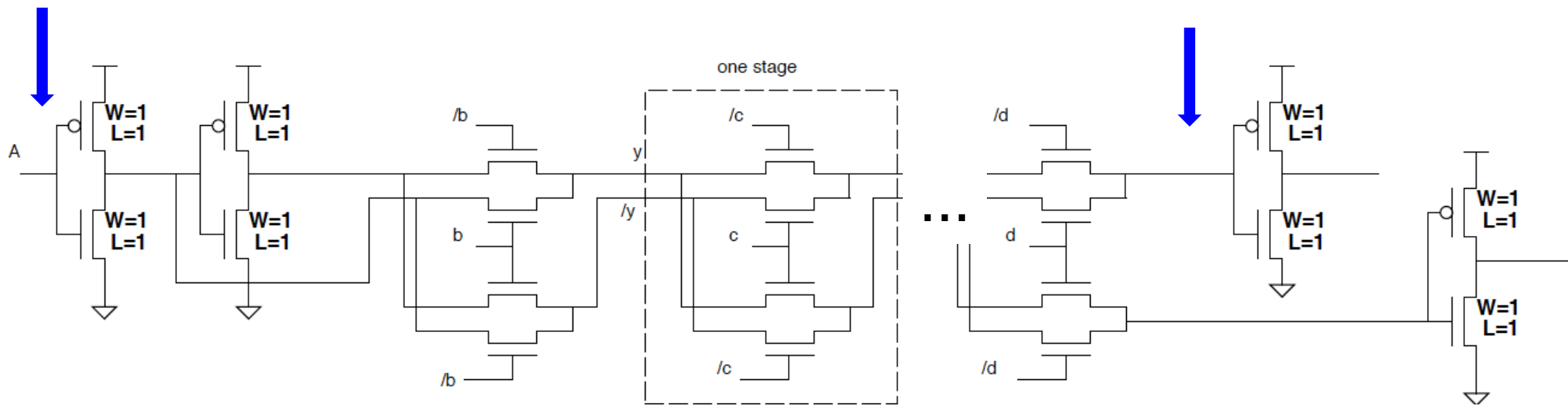
# Unbuffered (preclass 8)

□ Delay as a function of number of stages,  $k$ ?



# CMOS XOR (preclass 9)

- Delay with  $C_{diff} > 0$ ?

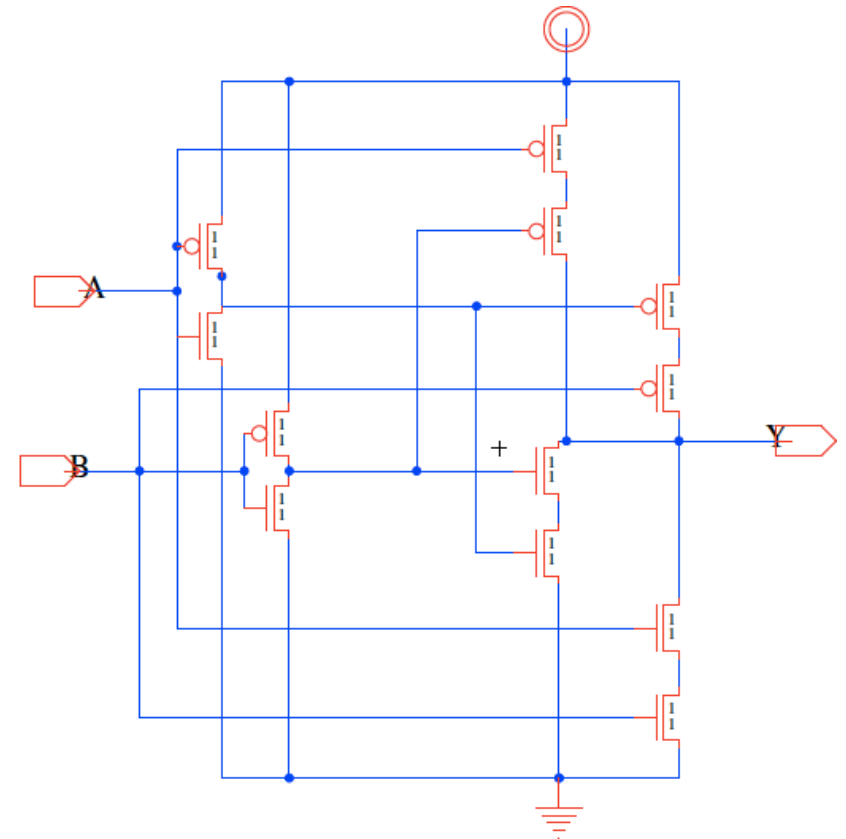



# Idea

---

- ❑ Elmore delay calculation allows us to estimate delay for distributed RC network
  - Necessary for pass transistors
- ❑ Wires are distributed RC
  - Half delay lumped calculation
  - Still quadratic in length



# Admin

---

- Project 1
  - Final report due **Friday 10/29** midnight