

ESE370: Circuit-Level Modeling, Design, and Optimization for Digital Systems

Lec 22: October 29, 2021

CMOS Worst Case Analysis and Logic Type
Comparisons




Lecture Outline

- ❑ Pass transistor Round-up
- ❑ CMOS Gates Review
 - CMOS Worst Case Analysis
- ❑ Logic Type Comparisons


Previously: First Order Delay

 - R_0 = Resistance of minimum size NMOS device
- $I_0 = I_{ds}$ of minimum size NMOS device
- C_0 = gate capacitance of minimum size NMOS device
- C_{diff0} = diffusion capacitance of minimum size NMOS device
 - $C_{diff0} = \gamma C_0$



Previously: First Order Delay

 - ❑ For device of width W (multiple of minimum size)
- ❑ $R_{ON} = R_0/W$
- ❑ $I_D = W * I_0$
- ❑ $C_G = W * C_0$
- ❑ $C_{diff} = W * C_{diff0}$
 - $C_{diff} = W * \gamma C_0$






Unbuffered

□ Circuit → Delay?


■ 3 stages

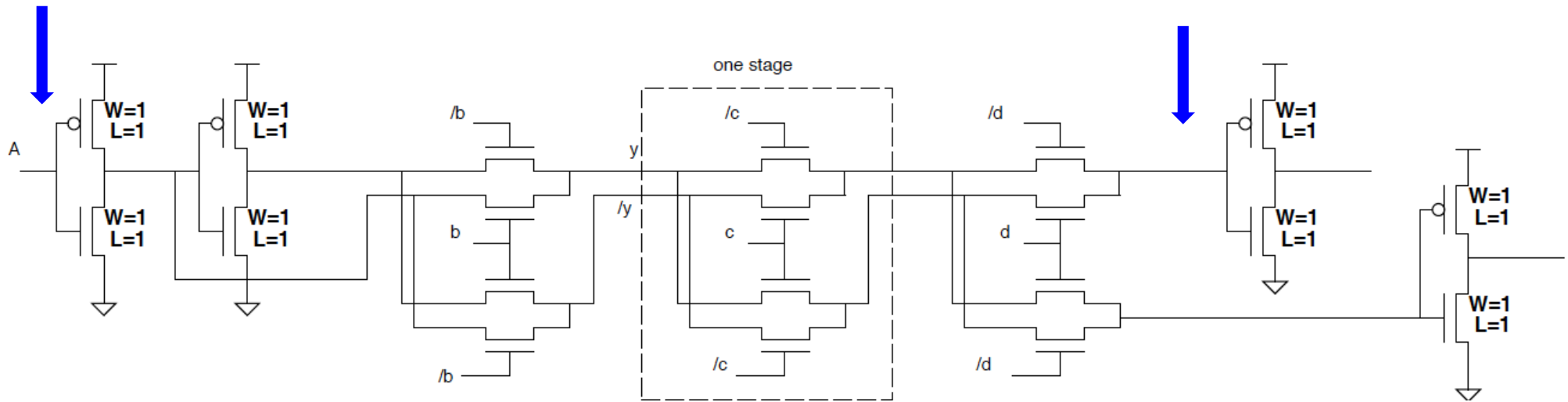



Unbuffered

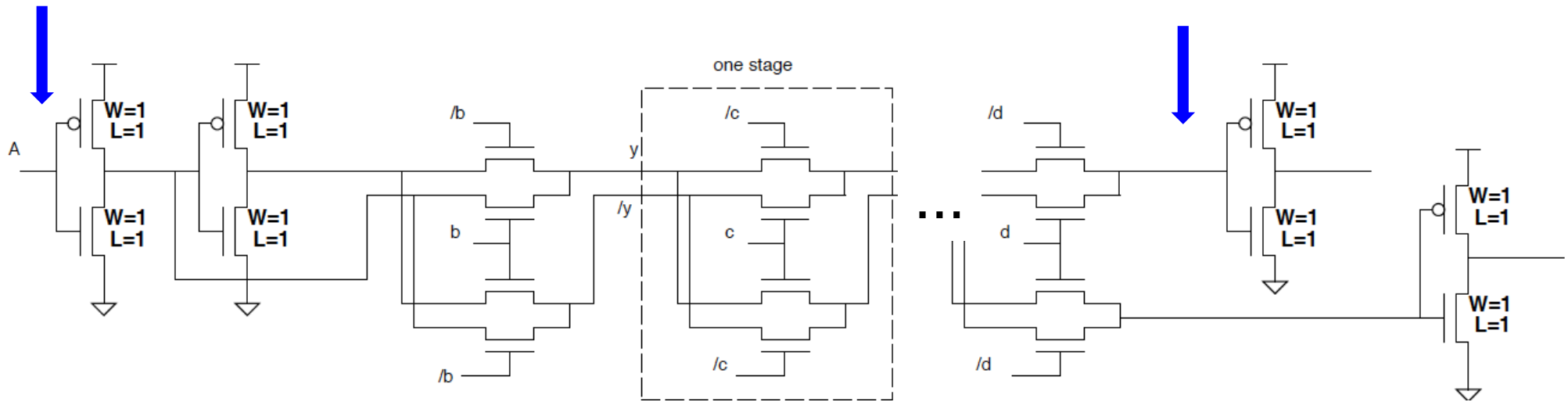
□ Delay as a function of number of stages, k ?







CMOS XOR

□ Delay with $C_{diff} > 0$?


 


Review: Two-Input NOR Gate (NOR2)

 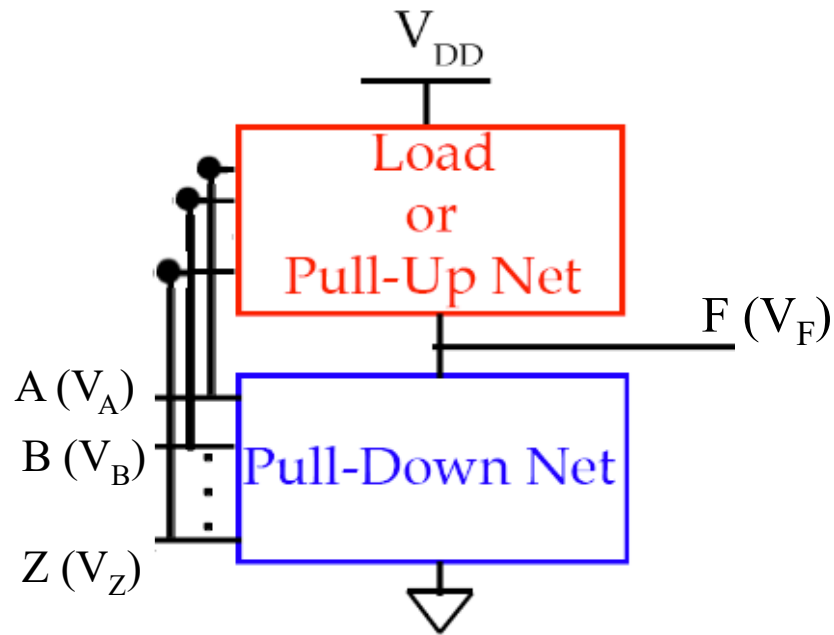

- ❑ Worst case delay of NOR2?
 - Minimum size, Loaded with itself

NOR2 Transfer Curve

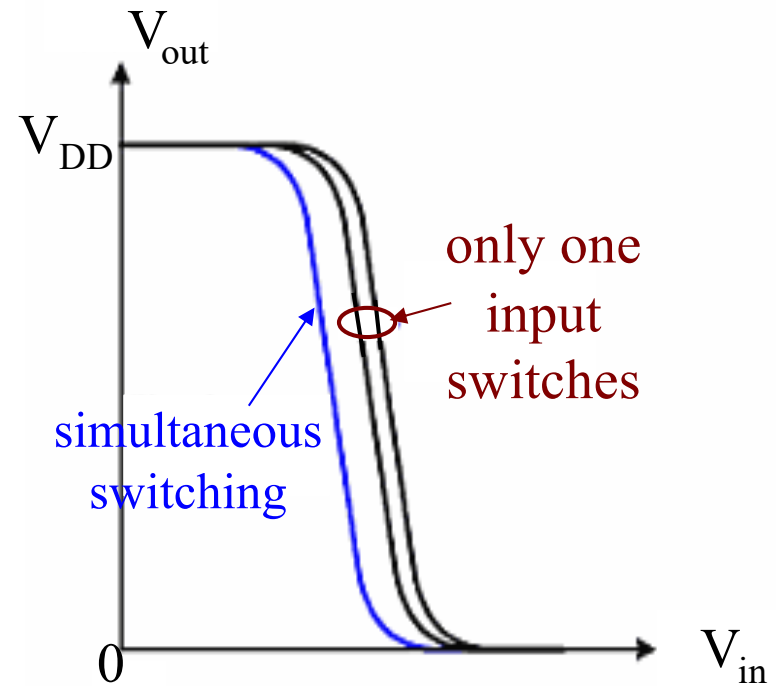 

3 VTC Cases

$$V_1 = 0 \text{ V}; V_2 = 0 \rightarrow V_{DD}$$

$$V_1 = 0 \rightarrow V_{DD}; V_2 = 0$$


$$V_1 \text{ and } V_2 = 0 \rightarrow V_{DD} \text{ simultaneously}$$

Switching Threshold Voltage:

$$V_1 = V_2 = V_{out} = V_t$$

NOR2 Delay (preclass 1)


- Worst case delay for Pull-up?

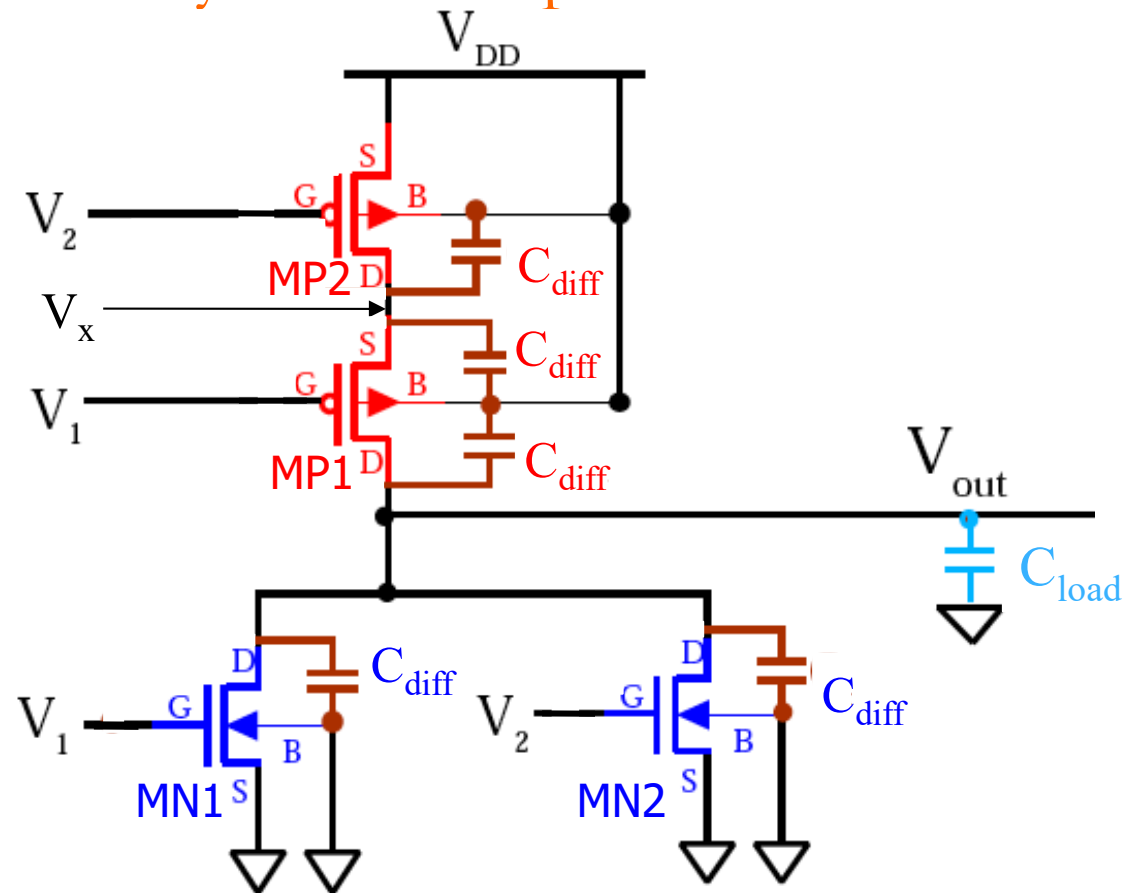



NOR2 Delay

- Worst case delay for Pull-up?

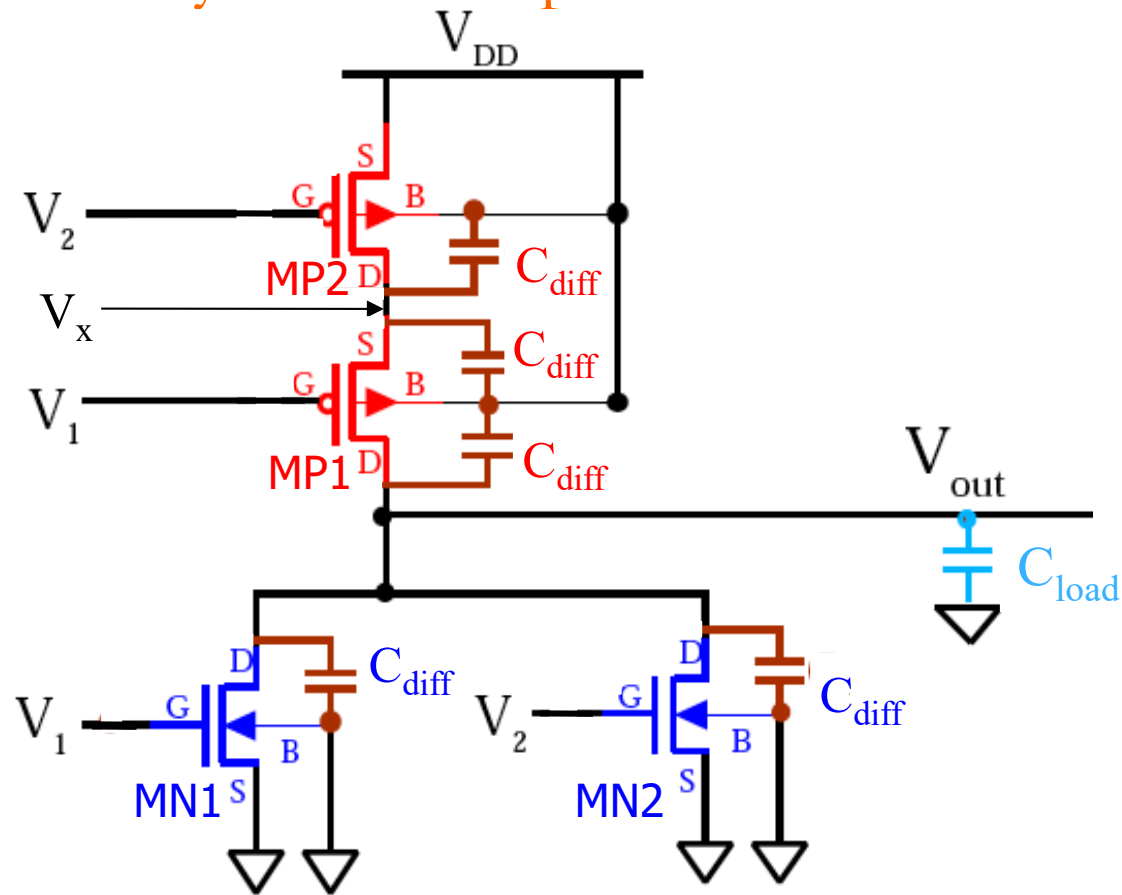

Worst Case for Pull-up $\rightarrow V_1 = 0, V_2 = V_{DD} \rightarrow 0$ @ $t=0$ & $V_x \approx V_{out} = 0 \rightarrow V_{DD}$


NOR2 Delay

□ Worst case delay for Pull-up?

$$C_{\text{load-NR2}} \approx 2C_{\text{diff}} + 3C_{\text{diff}} + C_{\text{load}}$$

$$R_{\text{EQV}} = R_{p2} + R_{p1}$$


Lumped Model

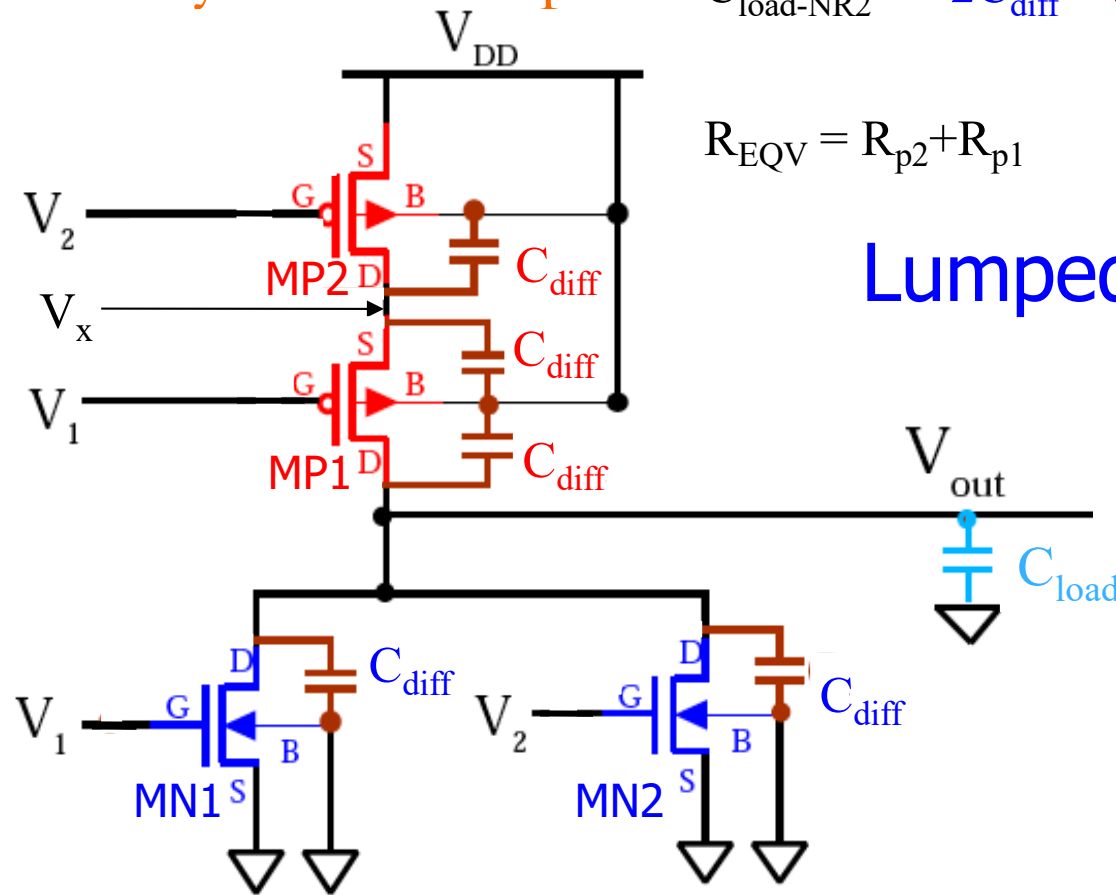

Worst Case for Pull-up $\rightarrow V_1 = 0, V_2 = V_{DD} \rightarrow 0$ @ $t=0$ & $V_x \approx V_{\text{out}} = 0 \rightarrow V_{DD}$

NOR2 Delay

□ Worst case delay for Pull-up?

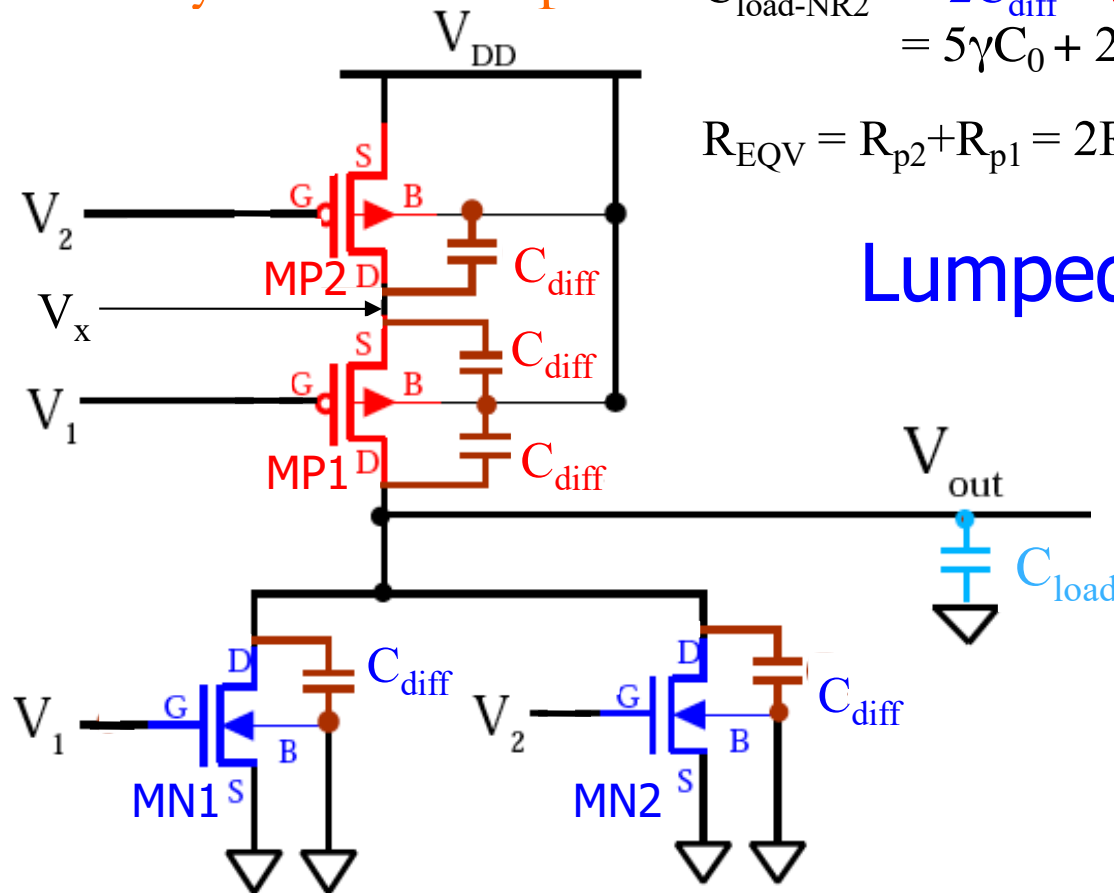

$$C_{\text{load-NR2}} \approx 2C_{\text{diff}} + 3C_{\text{diff}} + C_{\text{load}} = 5\gamma C_0 + 2C_0$$

$$R_{\text{EQV}} = R_{p2} + R_{p1} = 2R_0$$


Lumped Model

Worst Case for Pull-up $\rightarrow V_1 = 0, V_2 = V_{DD} \rightarrow 0$ @ $t=0$ & $V_x \approx V_{\text{out}} = 0 \rightarrow V_{DD}$

$$\text{delay} = (5\gamma C_0 + 2C_0)(2R_0) = (10\gamma + 4)\tau$$

NOR2 Delay

□ Worst case delay?

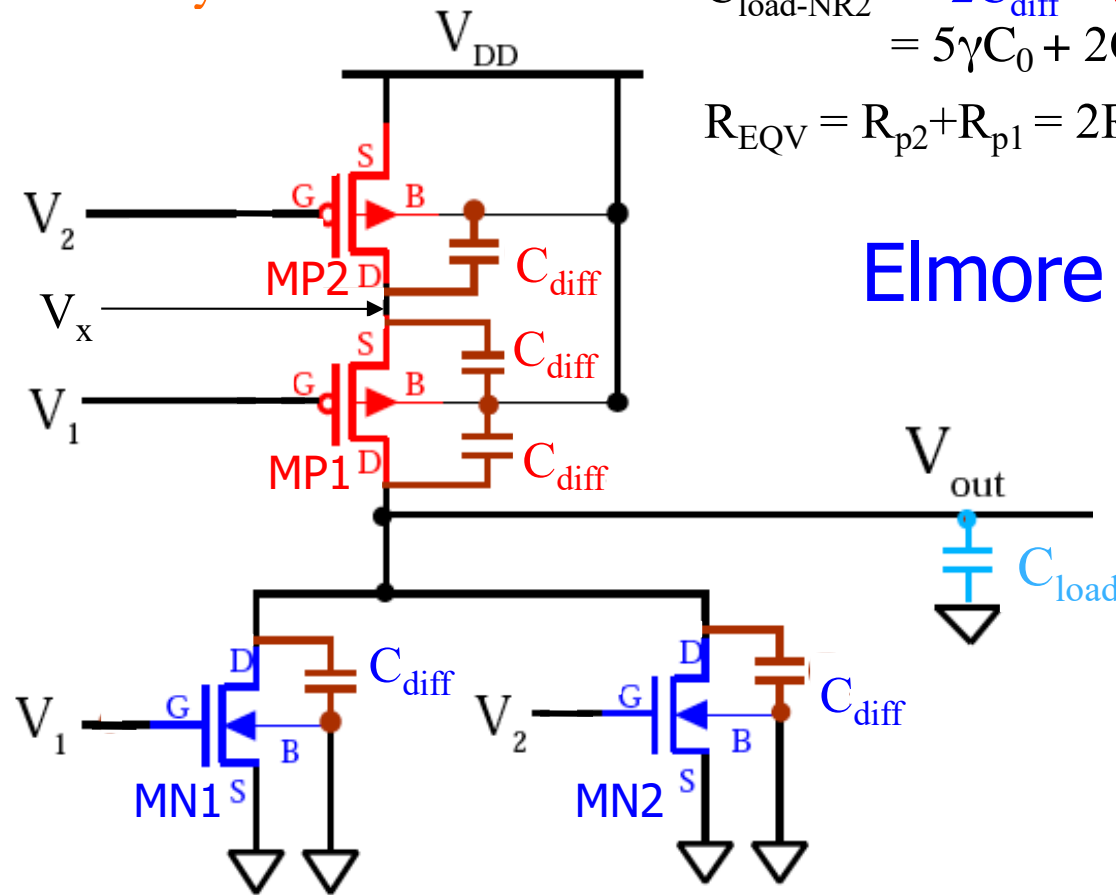

$$C_{\text{load-NR2}} \approx 2C_{\text{diff}} + 3C_{\text{diff}} + C_{\text{load}} = 5\gamma C_0 + 2C_0$$

$$R_{\text{EQV}} = R_{p2} + R_{p1} = 2R_0$$


Elmore Model?

Worst Case for Pull-up $\rightarrow V_1 = 0, V_2 = V_{DD} \rightarrow 0 @t=0$ & $V_x \approx V_{\text{out}} = 0 \rightarrow V_{DD}$



NOR2 Delay

❑ Worst case delay?

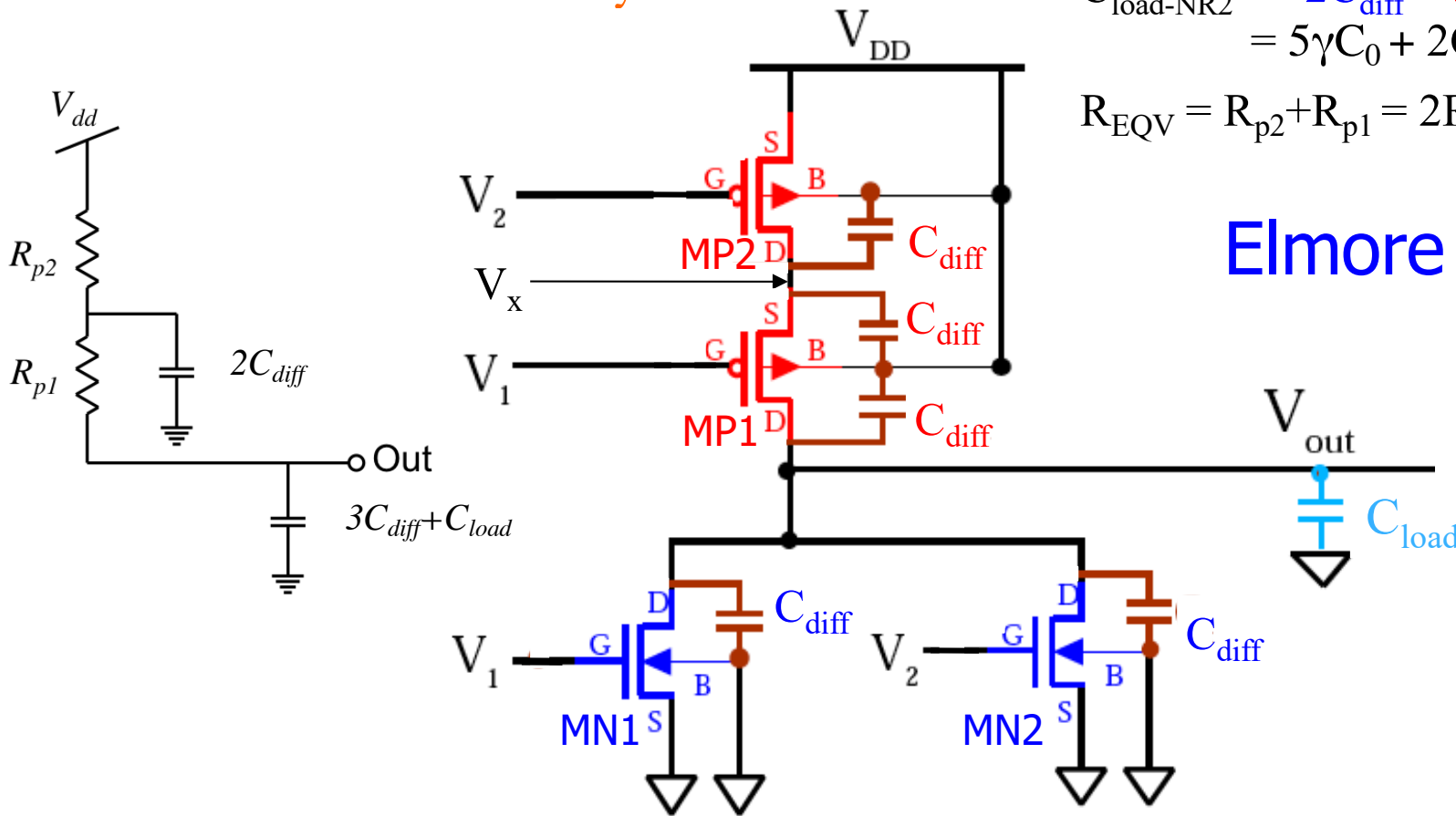

$$C_{\text{load-NR2}} \approx 2C_{\text{diff}} + 3C_{\text{diff}} + C_{\text{load}} = 5\gamma C_0 + 2C_0$$

$$R_{\text{EQV}} = R_{p2} + R_{p1} = 2R_0$$


Elmore Model?

Worst Case for Pull-up $\rightarrow V_1 = 0, V_2 = V_{DD} \rightarrow 0 @t=0$ & $V_x \approx V_{\text{out}} = 0 \rightarrow V_{DD}$



NOR2 Delay

Worst case delay?

 

$$C_{\text{load-NR2}} \approx 2C_{\text{diff}} + 3C_{\text{diff}} + C_{\text{load}} = 5\gamma C_0 + 2C_0$$

$$R_{\text{EQV}} = R_{p2} + R_{p1} = 2R_0$$

Elmore Model?


Worst Case for Pull-up $\rightarrow V_1 = 0, V_2 = V_{DD} \rightarrow 0 @t=0$ & $V_x \approx V_{\text{out}} = 0 \rightarrow V_{DD}$

$$\text{delay} = (2C_{\text{diff}})(R_{p2}) + (3C_{\text{diff}} + C_{\text{load}})(R_{p1} + R_{p2}) = (8\gamma + 4)\tau$$




NOR2 Delay

- Worst case delay Pull-down?

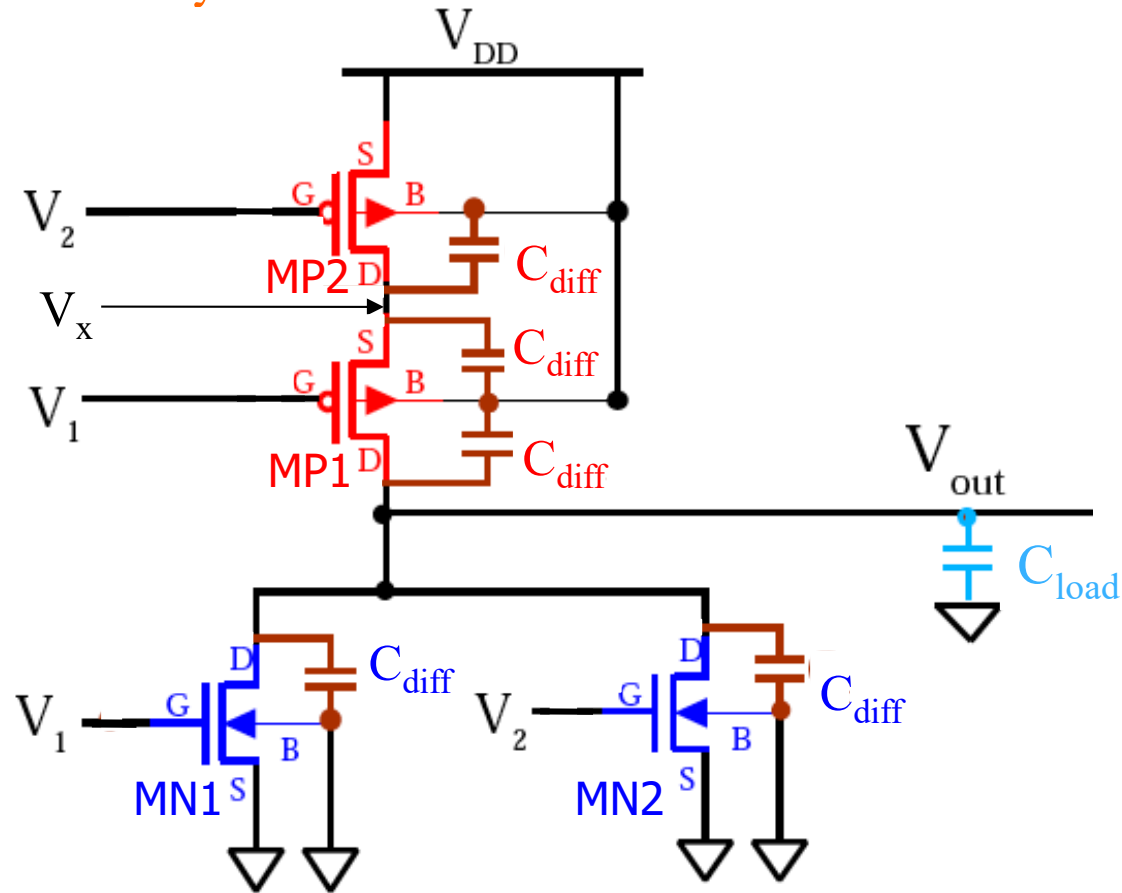

NOR2 Delay

- Worst case delay Pull-down?

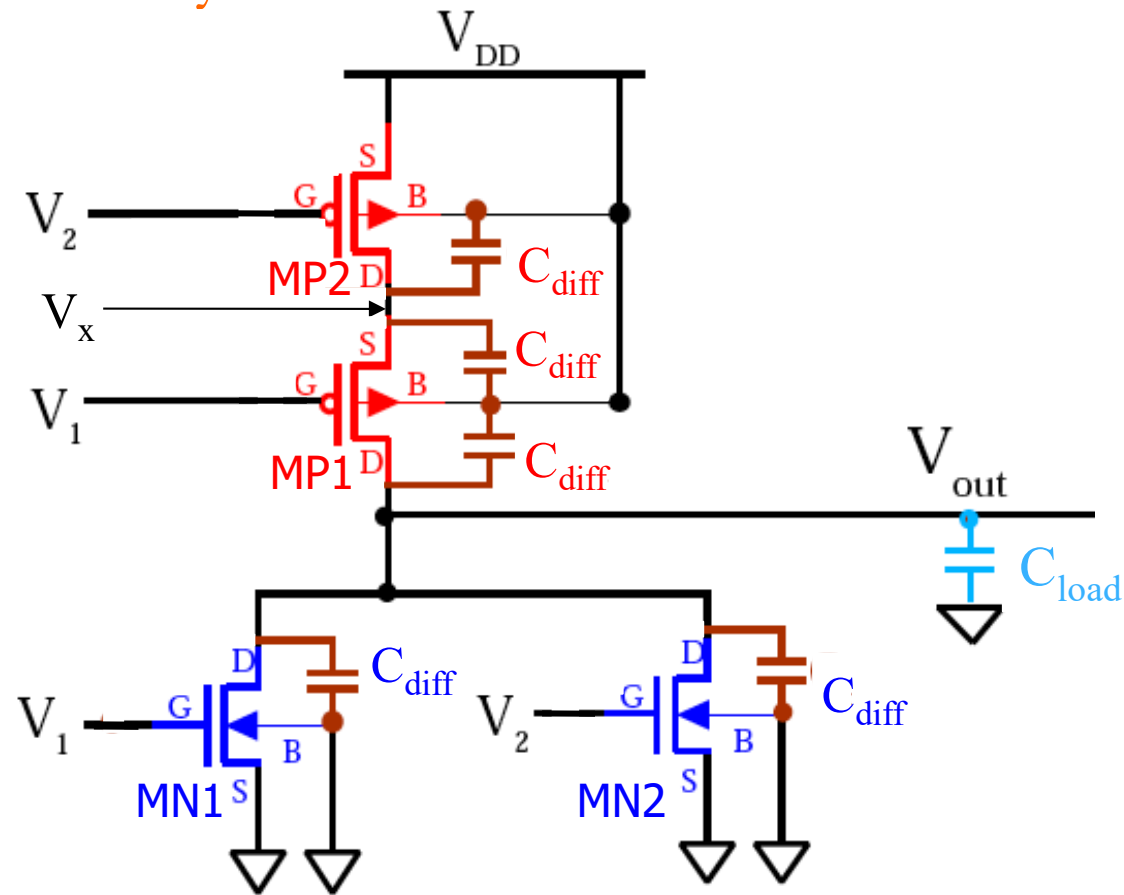


Worst case for Pull-down $\rightarrow V_1 = 0, V_2 = 0 \rightarrow V_{DD} @ t=0$ & $V_x \approx V_{out} = V_{DD} \rightarrow 0$



NOR2 Delay

- Worst case delay Pull-down?

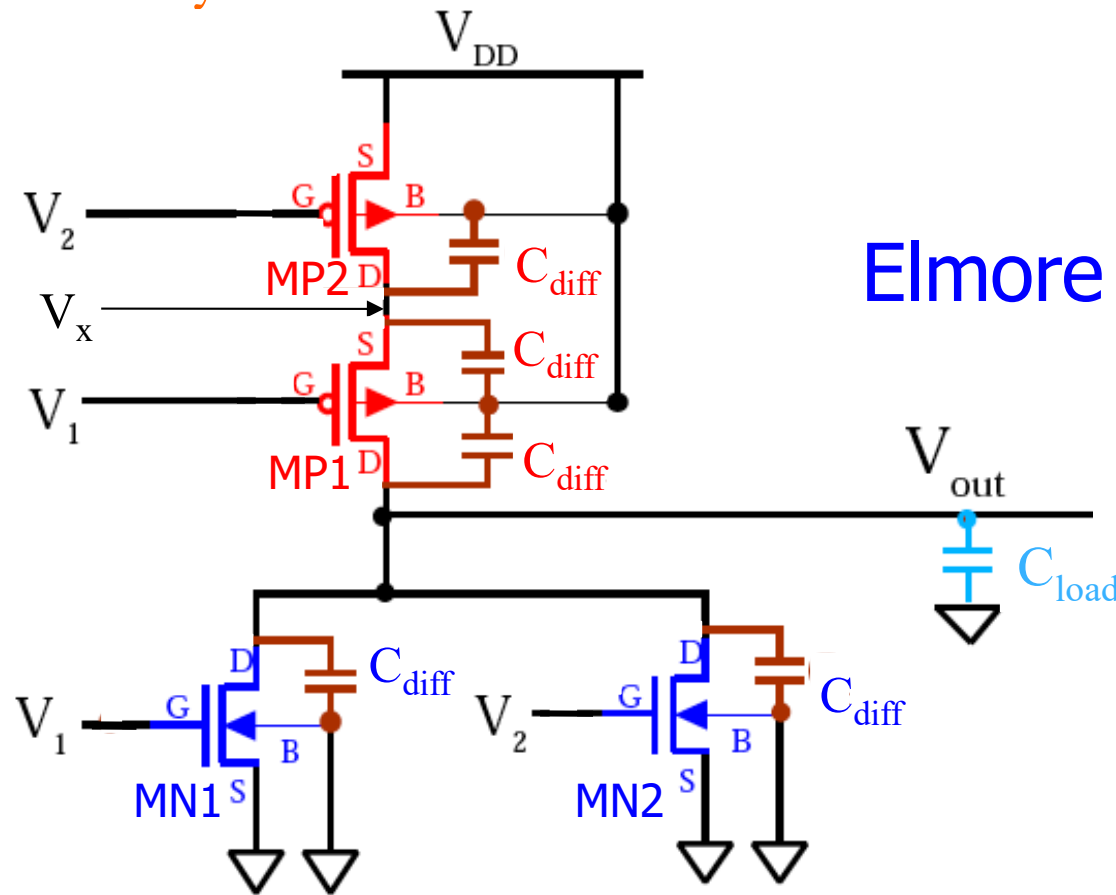


Worst case for Pull-down $\rightarrow V_1 = 0, V_2 = 0 \rightarrow V_{DD} @ t=0$ & $V_x \approx V_{out} = V_{DD} \rightarrow 0$



NOR2 Delay

❑ Worst case delay Pull-down?

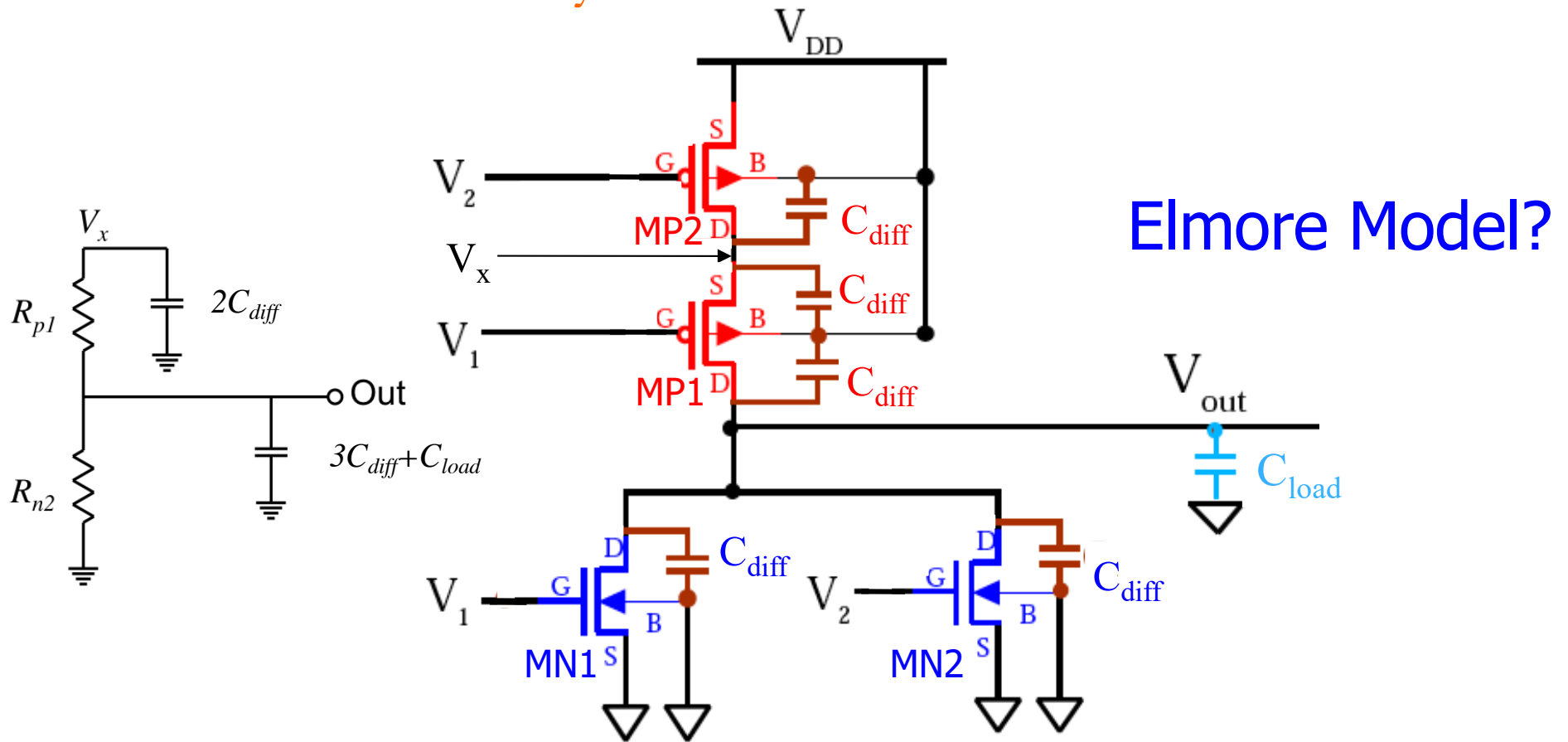


Worst case for Pull-down $\rightarrow V_1 = 0, V_2 = 0 \rightarrow V_{DD} @ t=0$ & $V_x \approx V_{out} = V_{DD} \rightarrow 0$


$$\text{delay} = (2C_{diff})(R_{p1} + R_{n2}) + (3C_{diff} + C_{load})(R_{n2}) = (7\gamma + 2)\tau$$




NAND2 Delay (preclass 2)

 

Parasitic Caps for NAND2 (worst case)

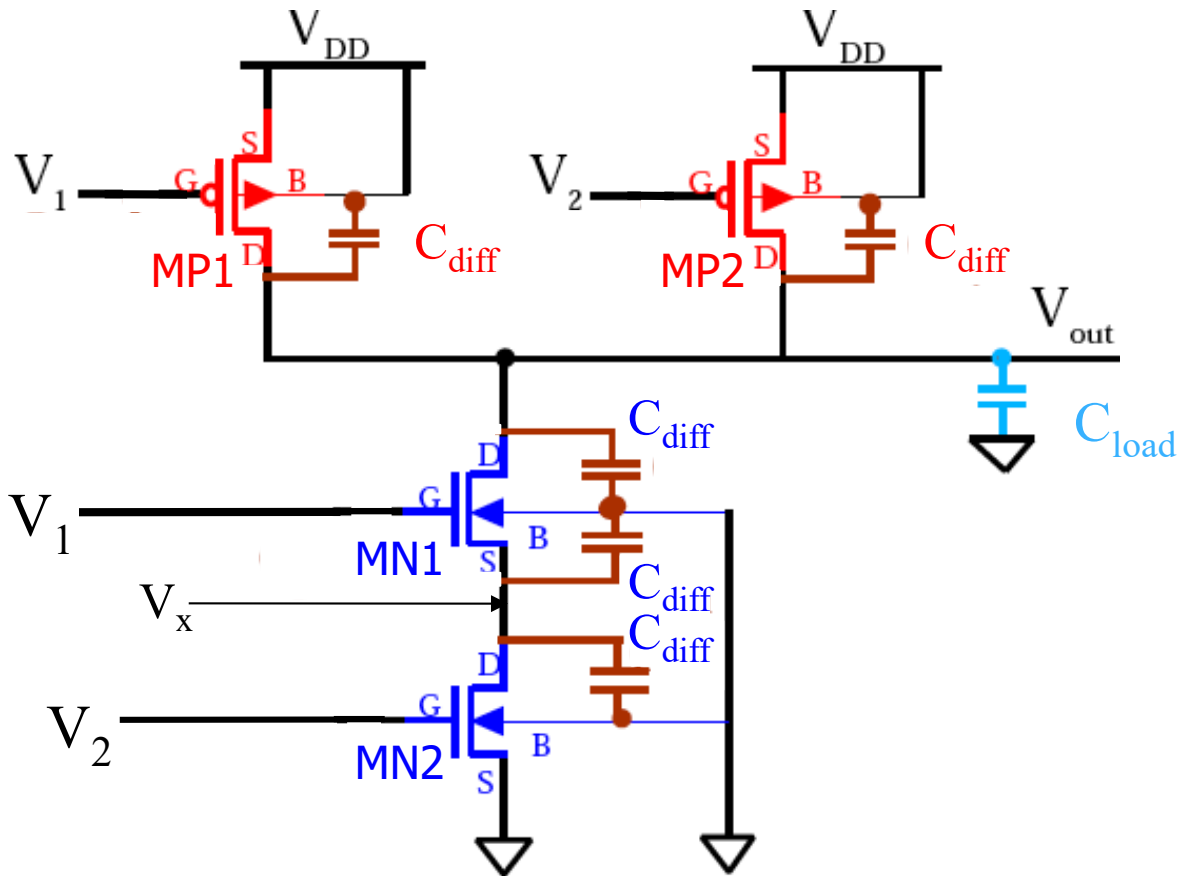


Parasitic Caps for NAND2 (worst case)

 


Worst case for Pull-up →

Parasitic Caps for NAND2 (worst case)

 


Worst case for Pull-up $\rightarrow V_1 = V_{DD}, V_2 = V_{DD} \rightarrow 0 @t=0$ & $V_x \approx V_{out} = 0 \rightarrow V_{DD}$

Parasitic Caps for NAND2 (worst case)

 

Worst case for pull down →

Parasitic Caps for NAND2 (worst case)


 


Worst case for pull down $\rightarrow V_1 = V_{DD}, V_2 = 0 \rightarrow V_{DD} @ t=0$ & $V_x \approx V_{out} = V_{DD} \rightarrow 0$



CMOS XOR

□ Delay with $C_{diff} > 0$?

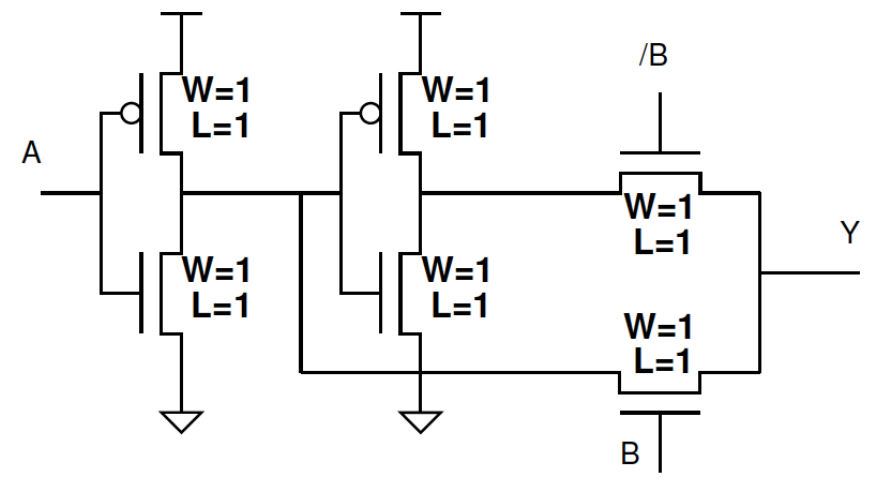 



Logic Types

- ❑ CMOS Gates
 - Dual pull-down and pull-up networks, only one enabled at a time
 - Performance of gate is strong function of the fanin of gate
 - Techniques to improve performance include sizing, input reordering, and buffering (staging)
- ❑ Ratioed Gates
 - Have active pull-down (-up) network connected to load device
 - Reduced gate complexity at expense of static power asymmetric transfer function
 - Techniques to improve performance include sizing to improve noise margins and reduce static power
- ❑ Pass Gates
 - Implement logic gate as switch network for area and often delay win
 - Long cascades of switches result in quadratic increase in delay
 - Also suffer from reduced noise margins (V_T drop)
 - Use level-restoring buffers to improve noise margins
- ❑ Dynamic logic ... next time



Idea

- ❑ CMOS Logic
 - Complimentary dual pull-up/down networks
- ❑ There are other logic disciplines
 - We have the tools to analyze
- ❑ Ratioed Logic
 - Tradeoff noise margin for
 - Reduced area? Capacitive load?
 - Dissipates static power in one mode
- ❑ Can use pass transistors for logic
 - Sometimes gives area or delay win



Admin

- ❑ Project 2 due **tonight @ midnight**
 - Leave time to write the report!
- ❑ Wednesday 11/3 Midterm 2 (next week)
 - 7-9pm DRLB 3C2
 - Lectures 1-22
 - Closed note, calculator allowed
 - All old exams online
 - focus on 2015-2019 ← taught in person by me
 - Study them!
 - Felicity review session
 - Monday 11/1, keep eye on Piazza



Admin: Midterm 2 Topics (up to Lec 22)

- Sizing
- Tau-model
 - Estimation and optimization
- Elmore-delay
 - Estimation and optimization
- Energy and power
 - Estimation and optimization
 - Dynamic and static
- Logic
 - CMOS
 - Ratioed
 - Pass transistor
- Transistor
 - Regions of operation
 - Parasitic Capacitance Model

“idea” slides