

ESE370: Circuit-Level Modeling, Design, and Optimization for Digital Systems

Lec 25: November 8, 2021
Dynamic Logic Pt. 1




Today

- Dynamic (Clocked) Logic
 - Strategy
 - Form
 - Compare CMOS


Clocking

Latch Timing Issues

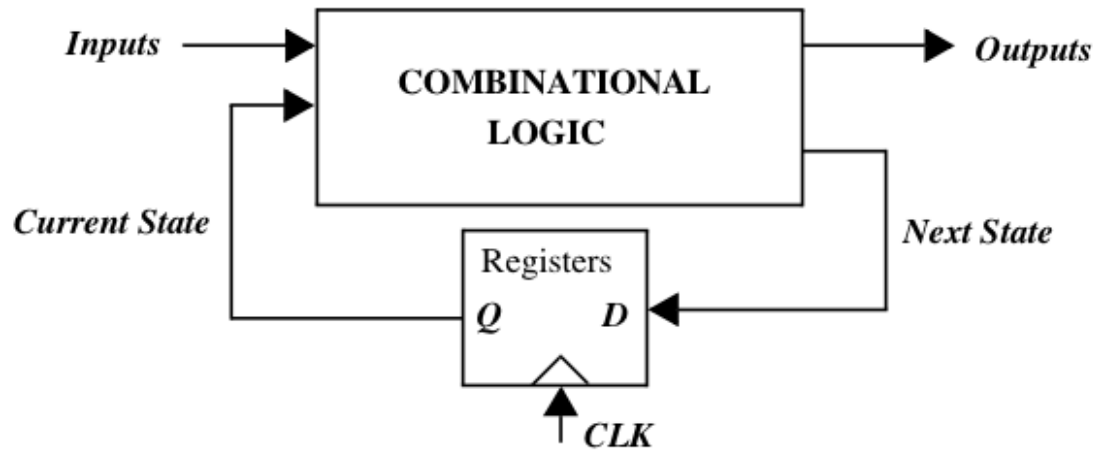


$$T \geq t_{c-q} + t_{plogic} + t_{su}$$
 
$$t_{cdregister} + t_{cdlogic} \geq t_{hold}$$





Setup Time Simulation

 


$t_{\text{su}} = 0.21 \text{ ns}$

works correctly



Setup Time Simulation

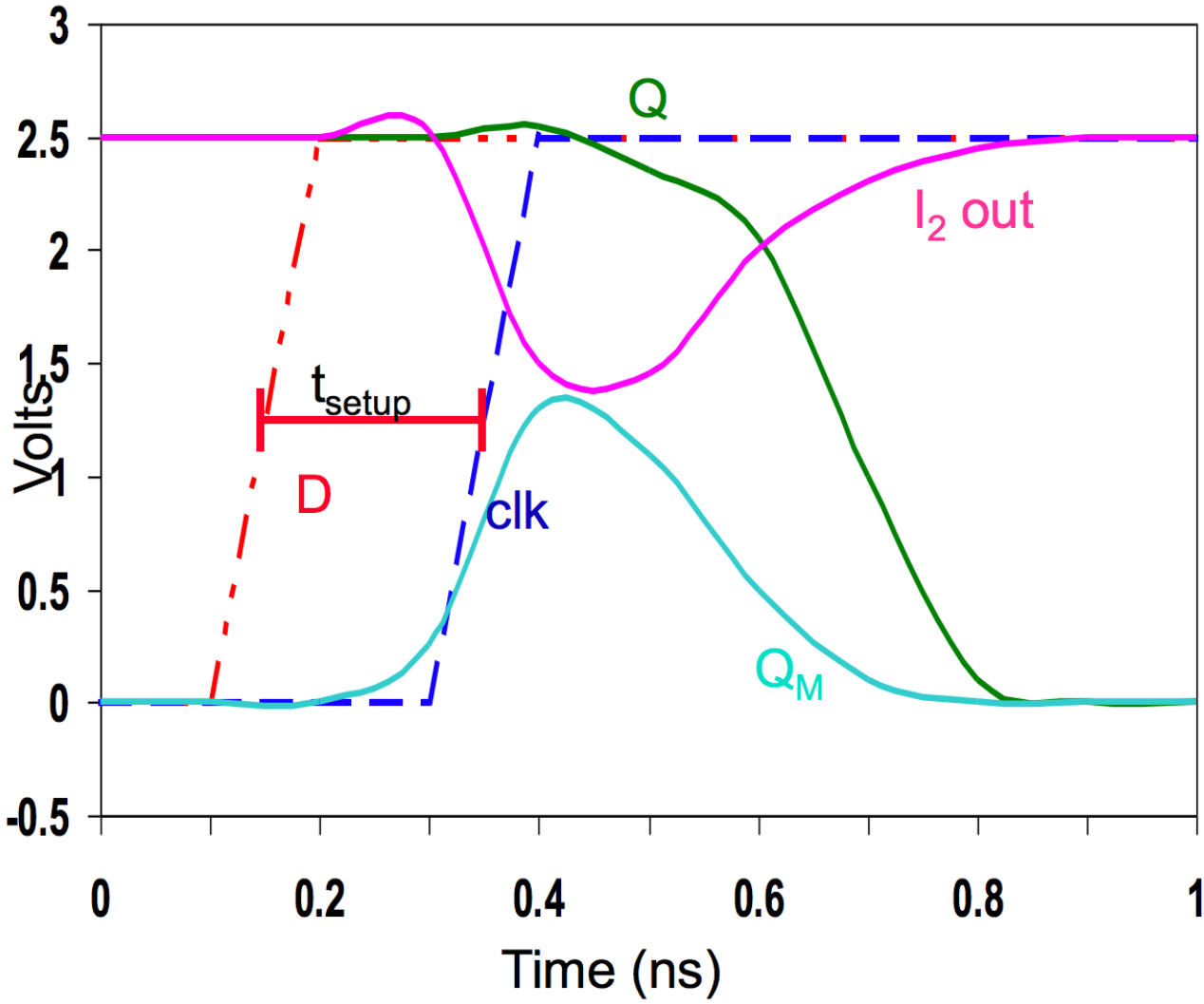


$t_{\text{su}} = 0.20 \text{ ns}$

fails

Timing Example (Preclass1)

	Min	Max
OR/AND	3ns	5ns
NOR/NAND	2ns	4ns
NOT	1ns	2ns
XOR	3ns	9ns

Latch:		Min	Max
	<i>Clock to Q</i>	2ns	3ns
	<i>Setup time</i>	7ns	
	<i>Hold time</i>	6ns	

 


$$T \geq t_{c-q} + t_{plogic} + t_{su}$$

Timing Example (Preclass1)

	Min	Max
OR/AND	3ns	5ns
NOR/NAND	2ns	4ns
NOT	1ns	2ns
XOR	3ns	9ns

Latch:		Min	Max
	<i>Clock to Q</i>	2ns	3ns
	<i>Setup time</i>	7ns	
	<i>Hold time</i>	6ns	

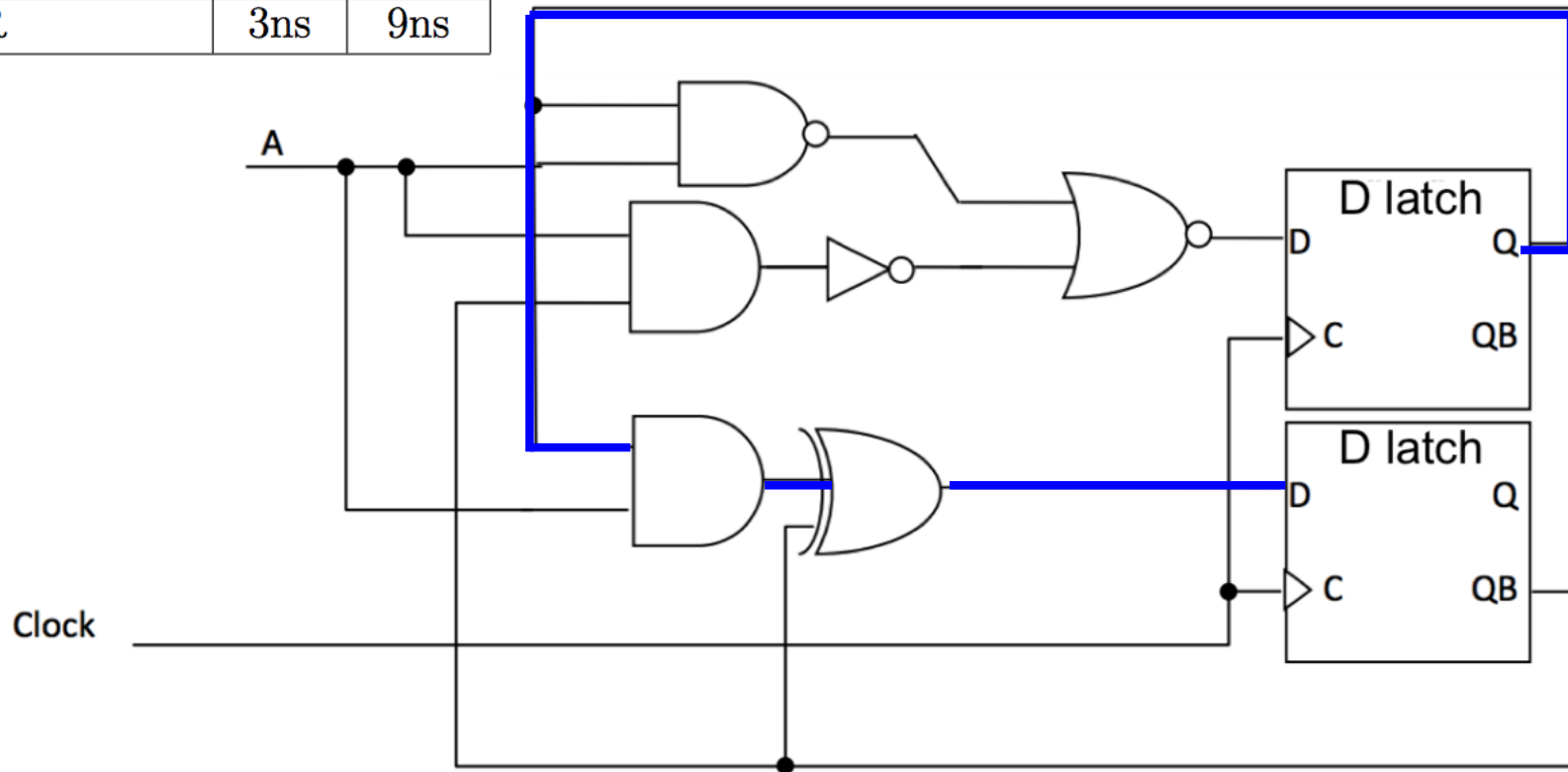


$$T \geq t_{c-q} + t_{plogic} + t_{su}$$

Timing Example (Preclass1)

	Min	Max
OR/AND	3ns	5ns
NOR/NAND	2ns	4ns
NOT	1ns	2ns
XOR	3ns	9ns

Latch:		Min	Max
	<i>Clock to Q</i>	2ns	3ns
	<i>Setup time</i>	7ns	
	<i>Hold time</i>	6ns	

 


$$t_{cdregister} + t_{cdlogic} \geq t_{hold}$$

Timing Example (Preclass1)

	Min	Max
OR/AND	3ns	5ns
NOR/NAND	2ns	4ns
NOT	1ns	2ns
XOR	3ns	9ns

Latch:		Min	Max
	<i>Clock to Q</i>	2ns	3ns
	<i>Setup time</i>	7ns	
	<i>Hold time</i>	6ns	

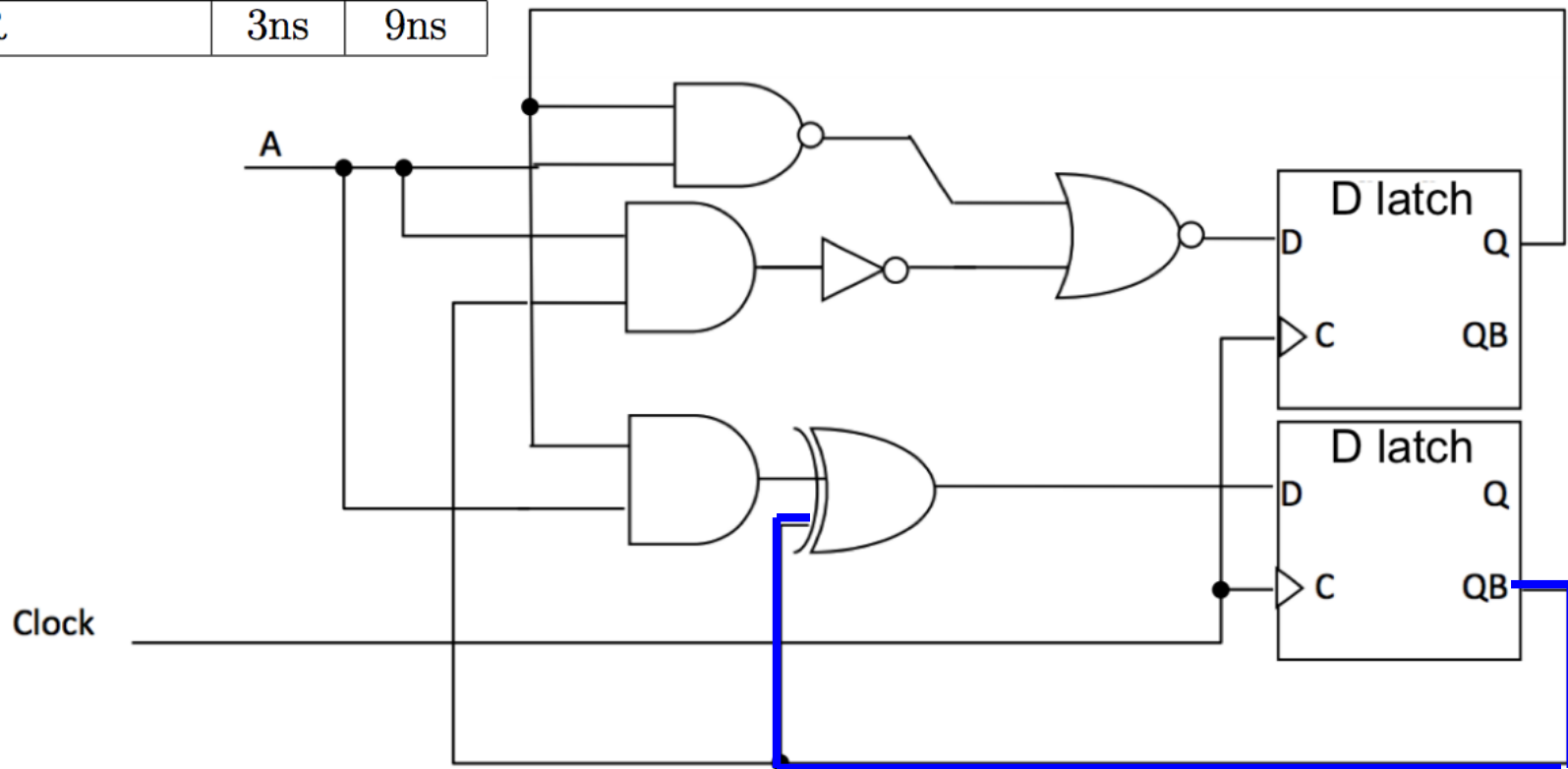


$$t_{cdregister} + t_{cdlogic} \geq t_{hold}$$

Timing Example (Preclass1)



	Min	Max
OR/AND	3ns	5ns
NOR/NAND	2ns	4ns
NOT	1ns	2ns
XOR	3ns	9ns

Latch:		Min	Max
	<i>Clock to Q</i>	2ns	3ns
	<i>Setup time</i>	7ns	
	<i>Hold time</i>	6ns	

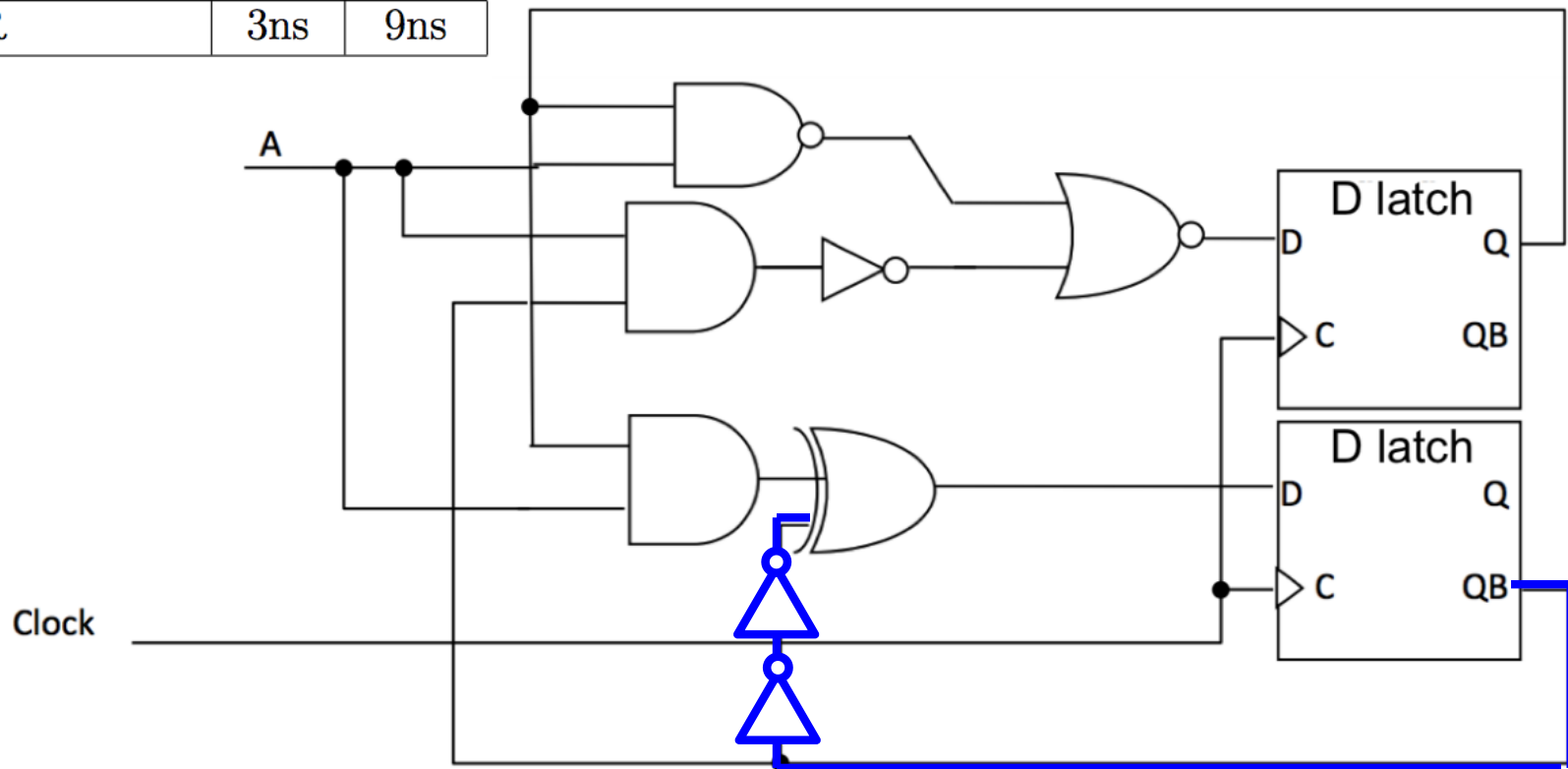

$$t_{cdregister} + t_{cdlogic} \geq t_{hold}$$

Register Implementation (Preclass 2)

 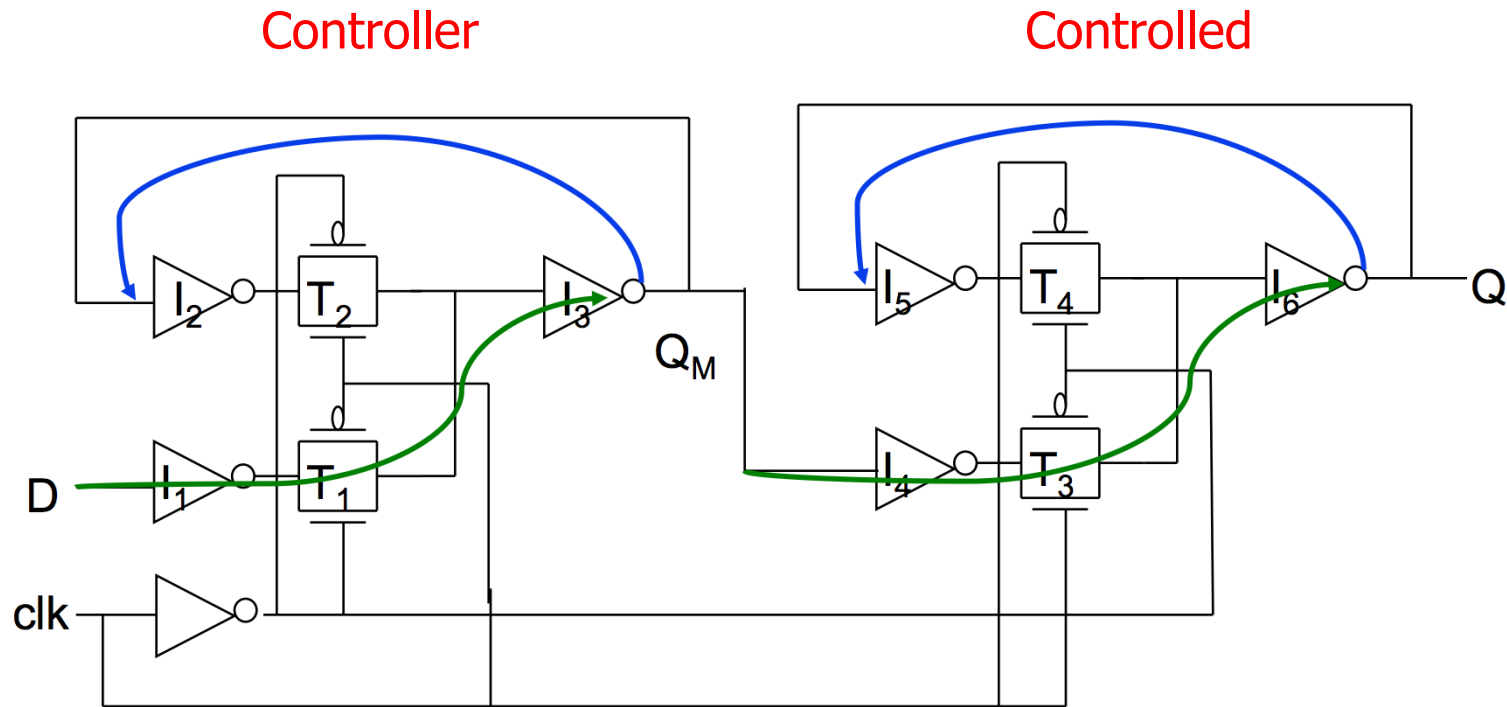



Timing Properties (Preclass 2)

- ❑ Assume propagation delays are t_{pd_inv} and t_{pd_tx} , and that the inverter delay to drive !clk is 0
- ❑ **Set-up time?** - time before rising edge of clk that D must be valid
- ❑ **Propagation delay?** - time from clk \rightarrow Q
- ❑ **Hold time?** - time D must be stable after rising edge of clk

- ❑ Come to office hours or post on Piazza for discussions/solutions



Clocking Highlights

- ❑ Breaking logic up with registers allows circuit to run at high frequency
 - Inputs decoupled from outputs
- ❑ Clock discipline simplifies logic composition
 - Abstracts many internal timing details
 - Just concerned with making clock period long enough
- ❑ Design Discipline – keeping data stable around clock edge
 - Setup, hold time – determined by latch circuit
 - Worst case and minimum $\text{Clk} \rightarrow \text{Q}$ delay for latch



Clocking


- ❑ Circuits typically operate in a clocked environment
 - Synchronous circuits
- ❑ Gives some additional structure we can exploit →
dynamic logic

Dynamic Logic



Motivation

 
- ❑ We would like to avoid driving both pullup/pulldown networks
 - reduce capacitive load
 - Power, delay







Motivation

 - ❑ We would like to avoid driving both pullup/pulldown networks
 - reduce capacitive load
 - Power, delay
- ❑ Ratioed Logic



Motivation

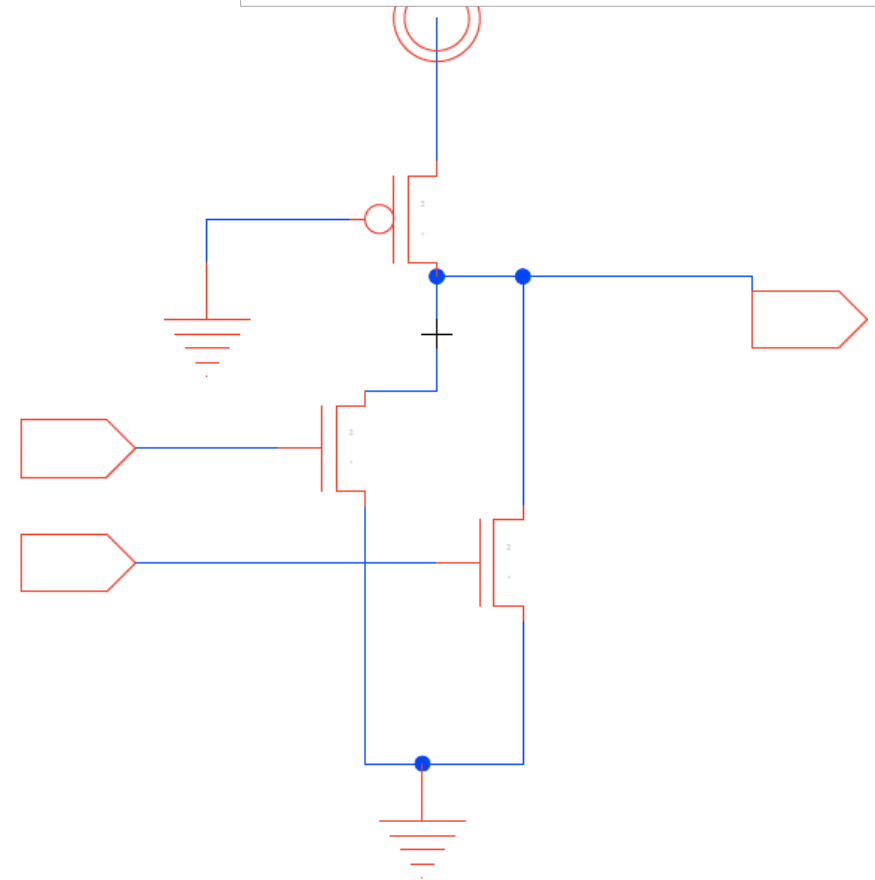
 
- ❑ We would like to avoid driving both pullup/pulldown networks
 - reduce capacitive load
 - Power, delay
- ❑ Ratioed Logic cons:
 - Large devices for ratioing
 - Meeting noise margins
 - Slow pullup
 - Static power





Idea

  
- ❑ Use clock to disable pullup network during logic evaluation






Idea

 - ❑ Use clock to disable pullup network during logic evaluation
- ❑ Define two phases
 - Pre-charge
 - Output pre-charged
 - Evaluation
 - Pulldown network evaluates gate logic




Discuss (Preclass 3)

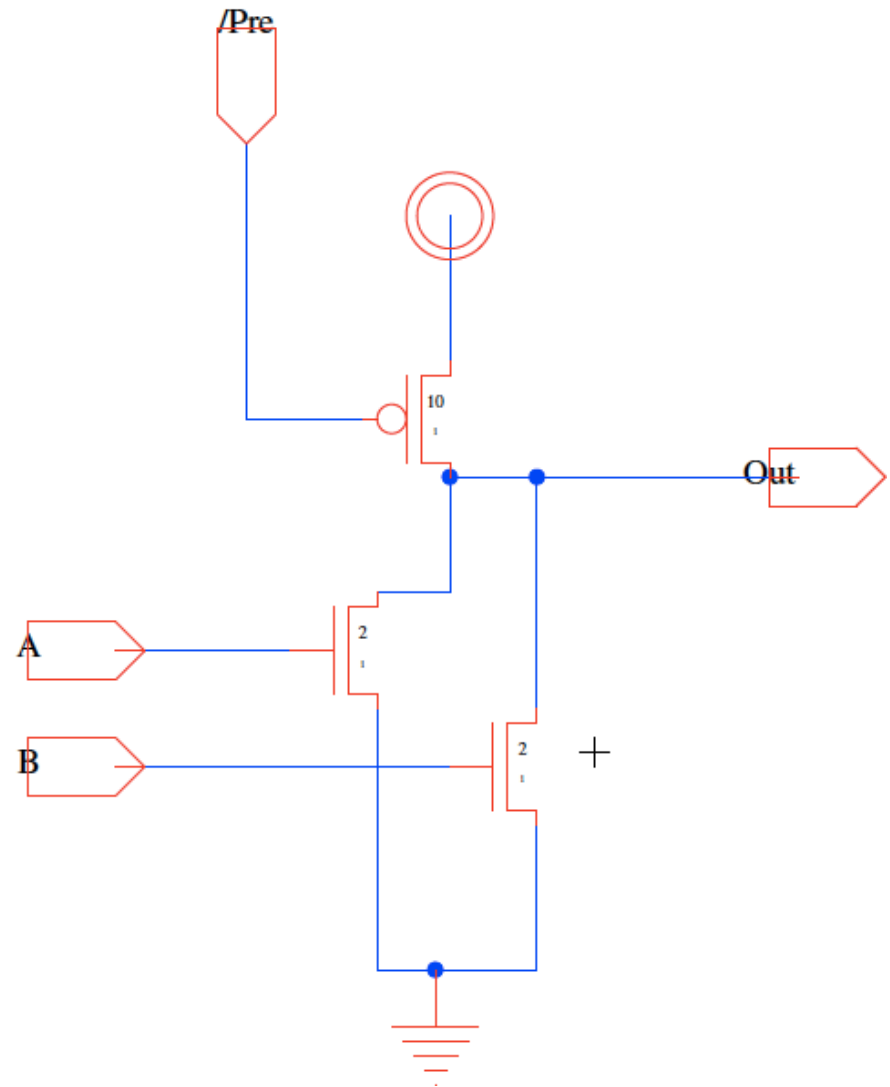- ❑ Use CLK to disable pullup during evaluation
- ❑ What is V_{out} when:
 - $/Pre=0, A=B=0$?
 - $/Pre=0 \rightarrow 1, A=B=0$?
 - $/Pre=1, A=0, B=0 \rightarrow 1$?




Discuss (Preclass 3)

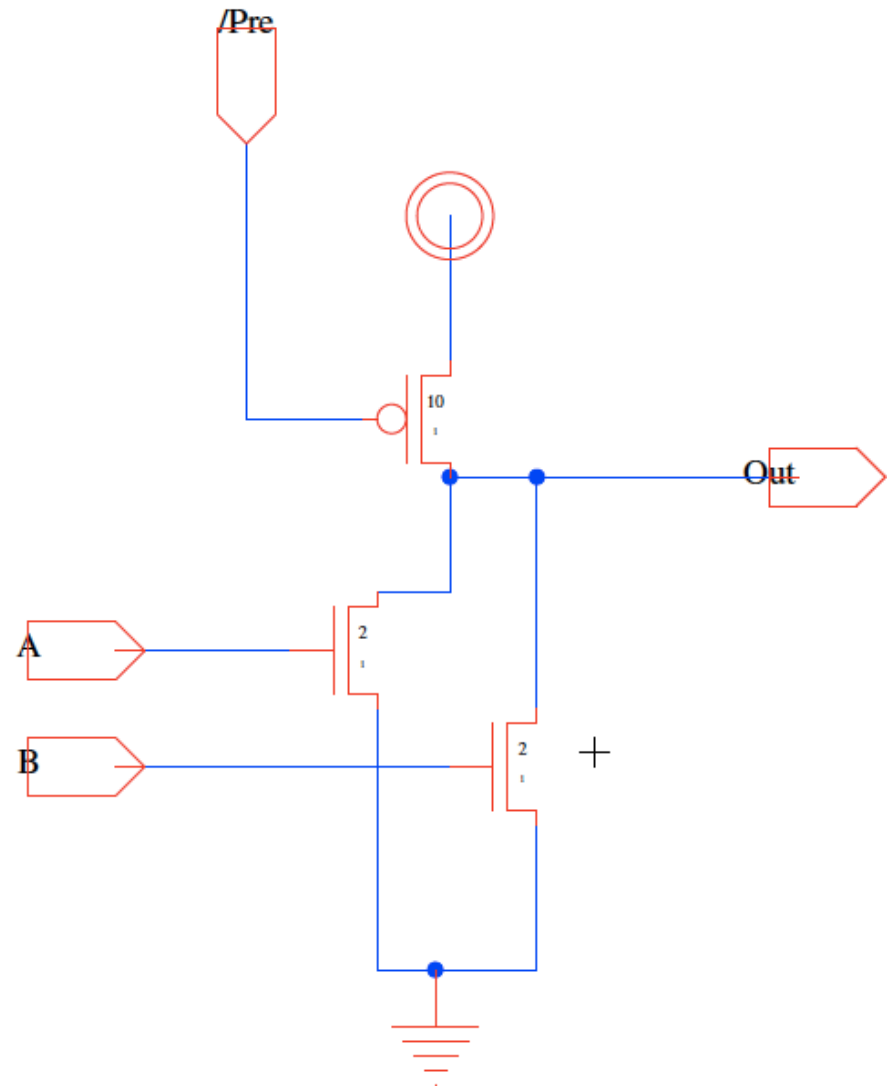- ❑ Use CLK to disable pullup during evaluation
- ❑ What is V_{out} when:
 - $/Pre=0, A=B=0$?
 - $/Pre=0 \rightarrow 1, A=B=0$?
 - $/Pre=1, A=0, B=0 \rightarrow 1$?
- ❑ Sizing implication?
- ❑ Concerns?
- ❑ Requirements?




Advantages


 
- ❑ Large load device
 - Driven by CLK—not data
 - Can pullup quickly without putting load on logic
- ❑ Single pulldown network
 - Don't have to size for ratio with pullup
 - Swings rail-to-rail





Cascaded Dynamic Logic

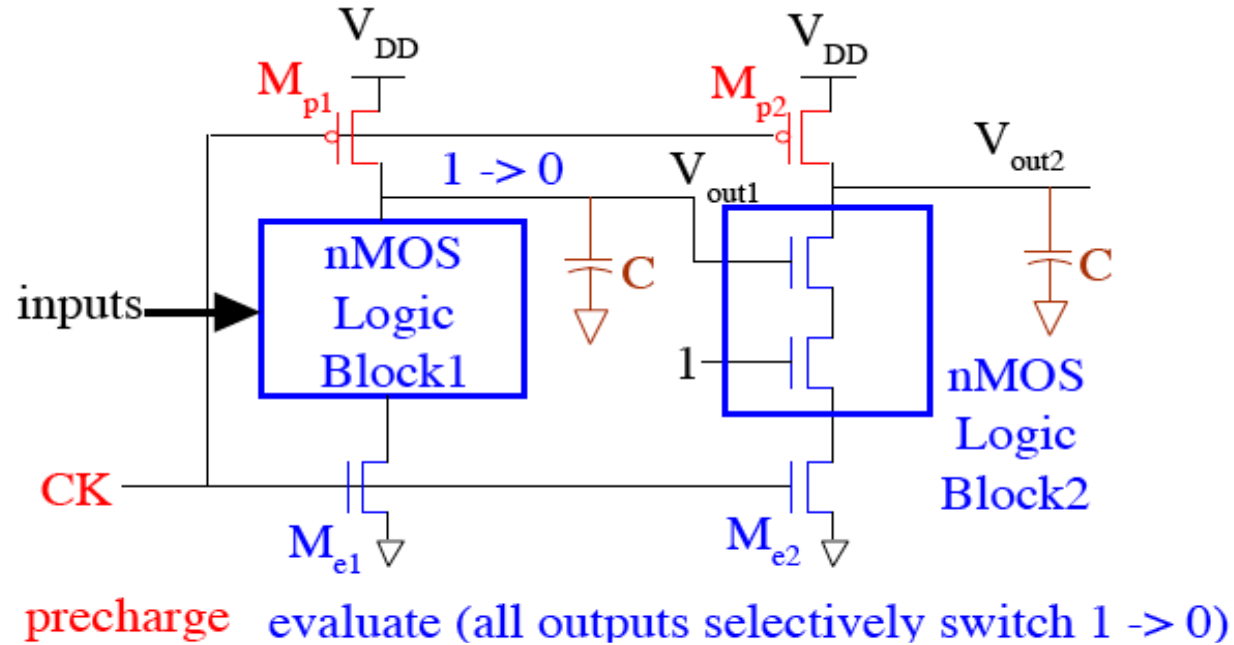


Cascaded Dynamic Logic

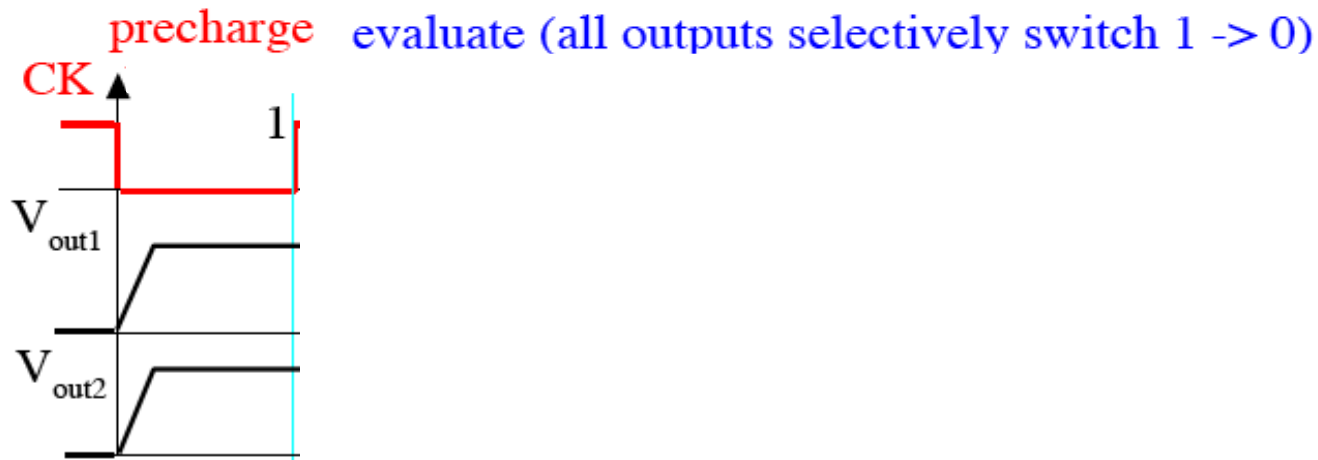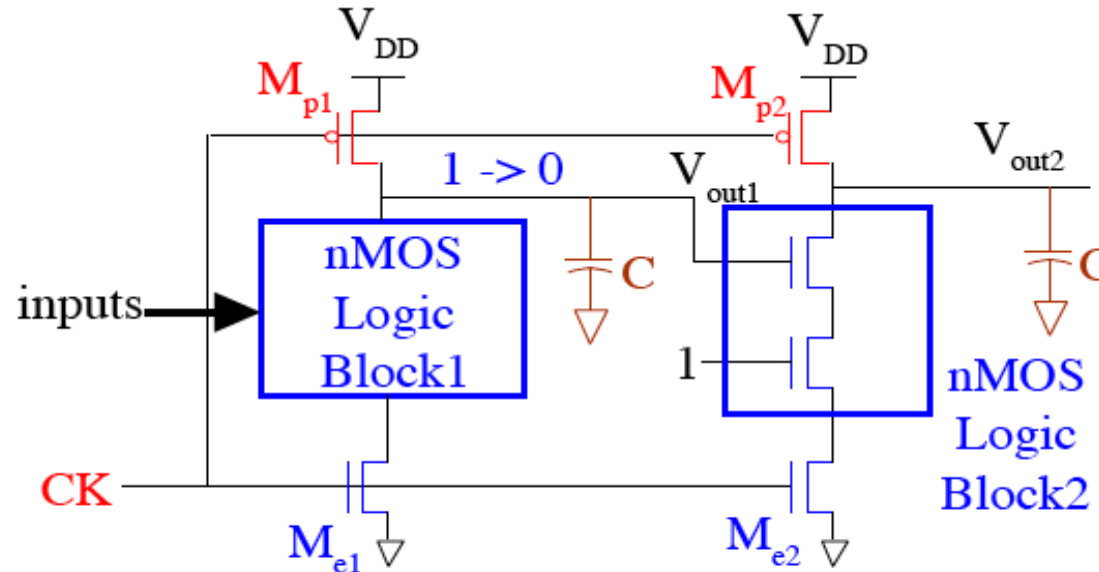


Cascaded Dynamic Logic

  

Cascaded Dynamic Logic

 


 
precharge evaluate (all outputs selectively switch 1 -> 0)



Precharged V_{out1} does not switch from "1" to "0" fast enough

evaluate:
 $M_{e1}, M_{e2} \rightarrow$ ON
 $M_{p1}, M_{p2} \rightarrow$ OFF


Cascaded Dynamic Logic

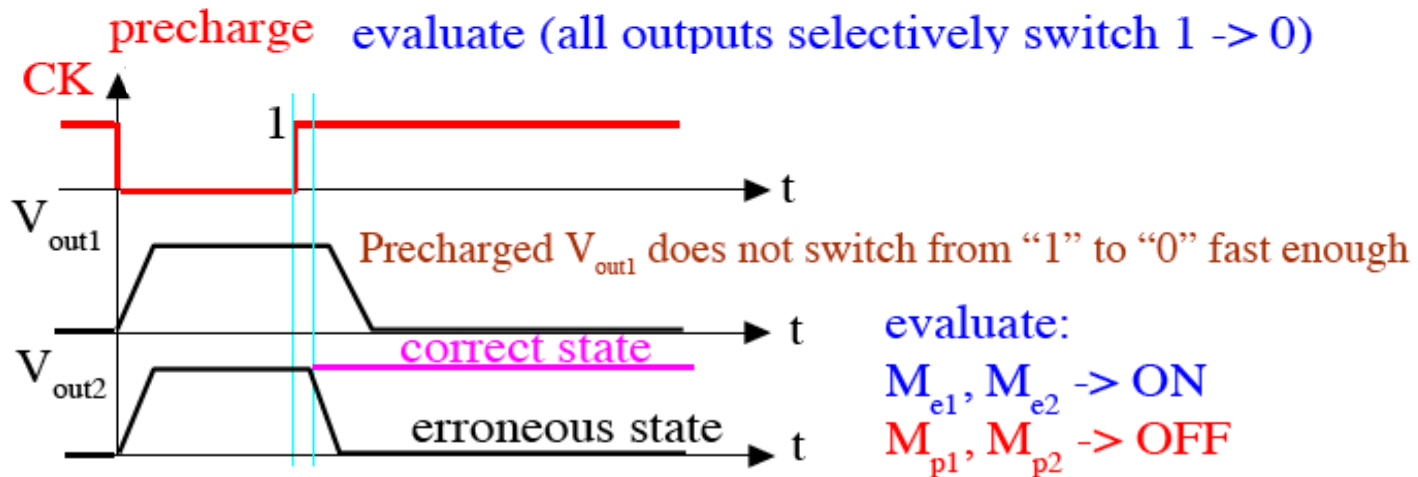 

**PROBLEM: ALL STAGES MUST EVALUATE SIMULTANEOUSLY
 SINGLE CLOCK DOES NOT PERMIT PIPELINING OF STAGES**




Domino Logic

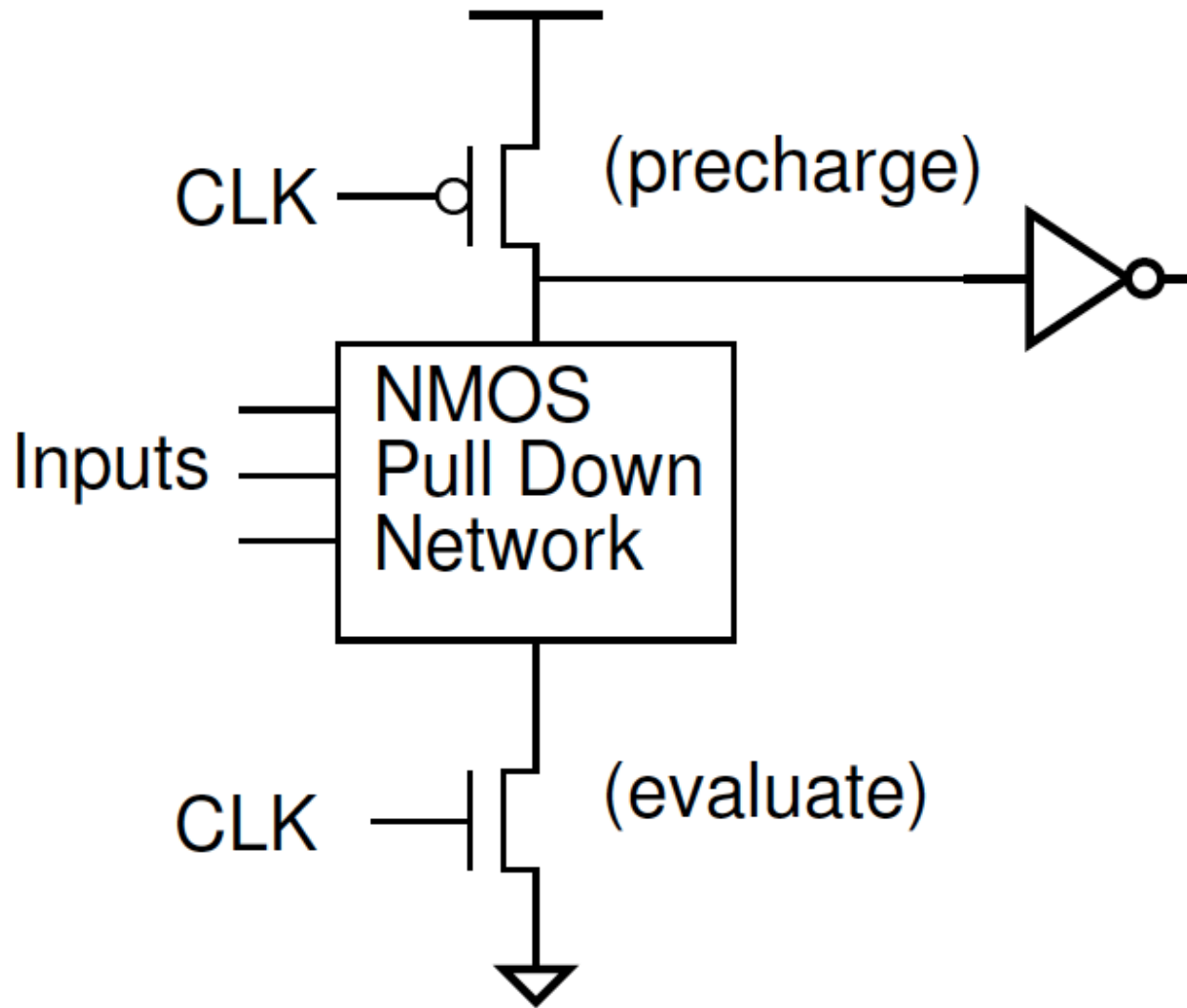




Requirements

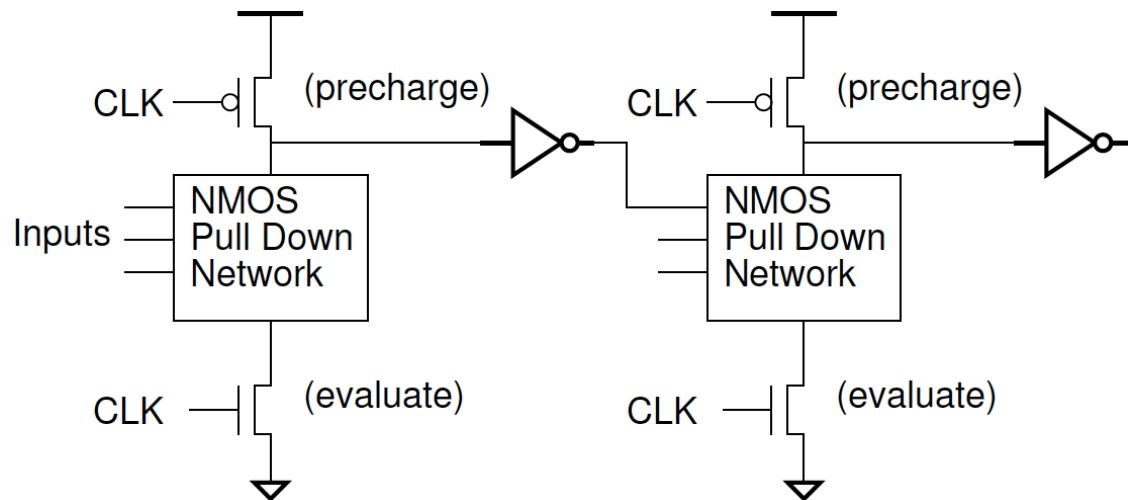
- ❑ Single transition
 - Once transitioned, it is done → like domino falling
- ❑ All inputs at 0 during precharge
 - “Outputs” pre-charged to 1 then inverted to 0
- ❑ Non-inverting gates fundamental gate





Cascaded Domino CMOS Logic Gates

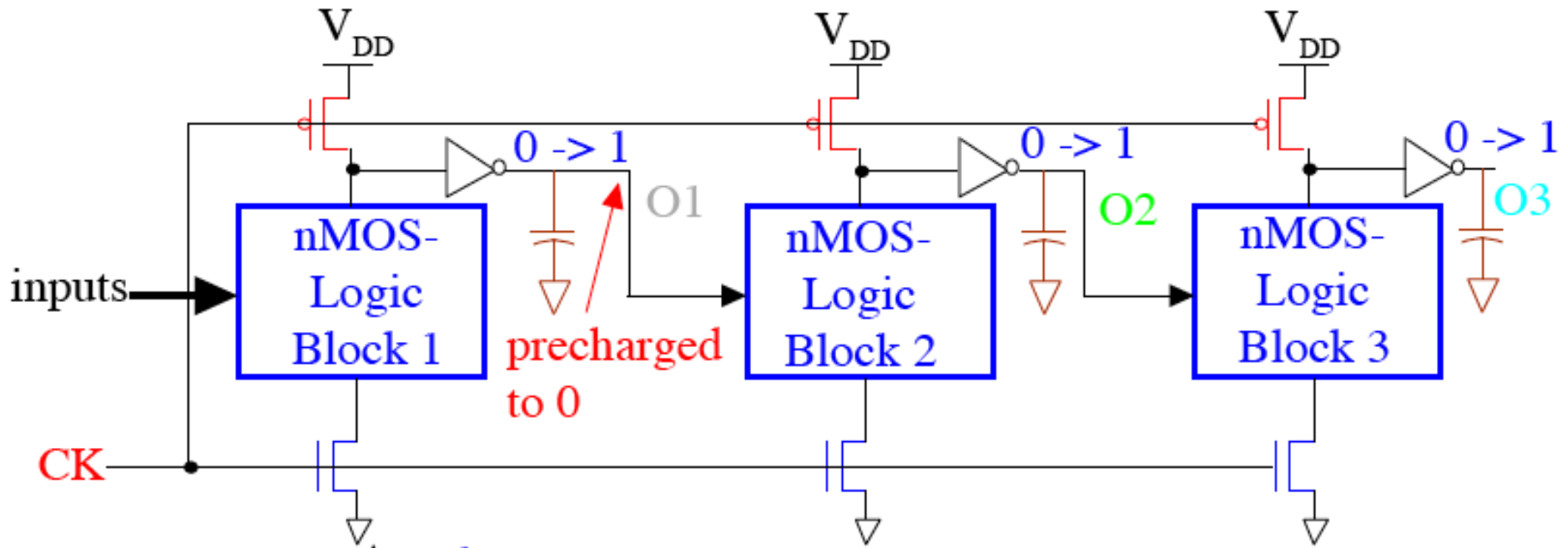

Cascaded Domino CMOS Logic Gates

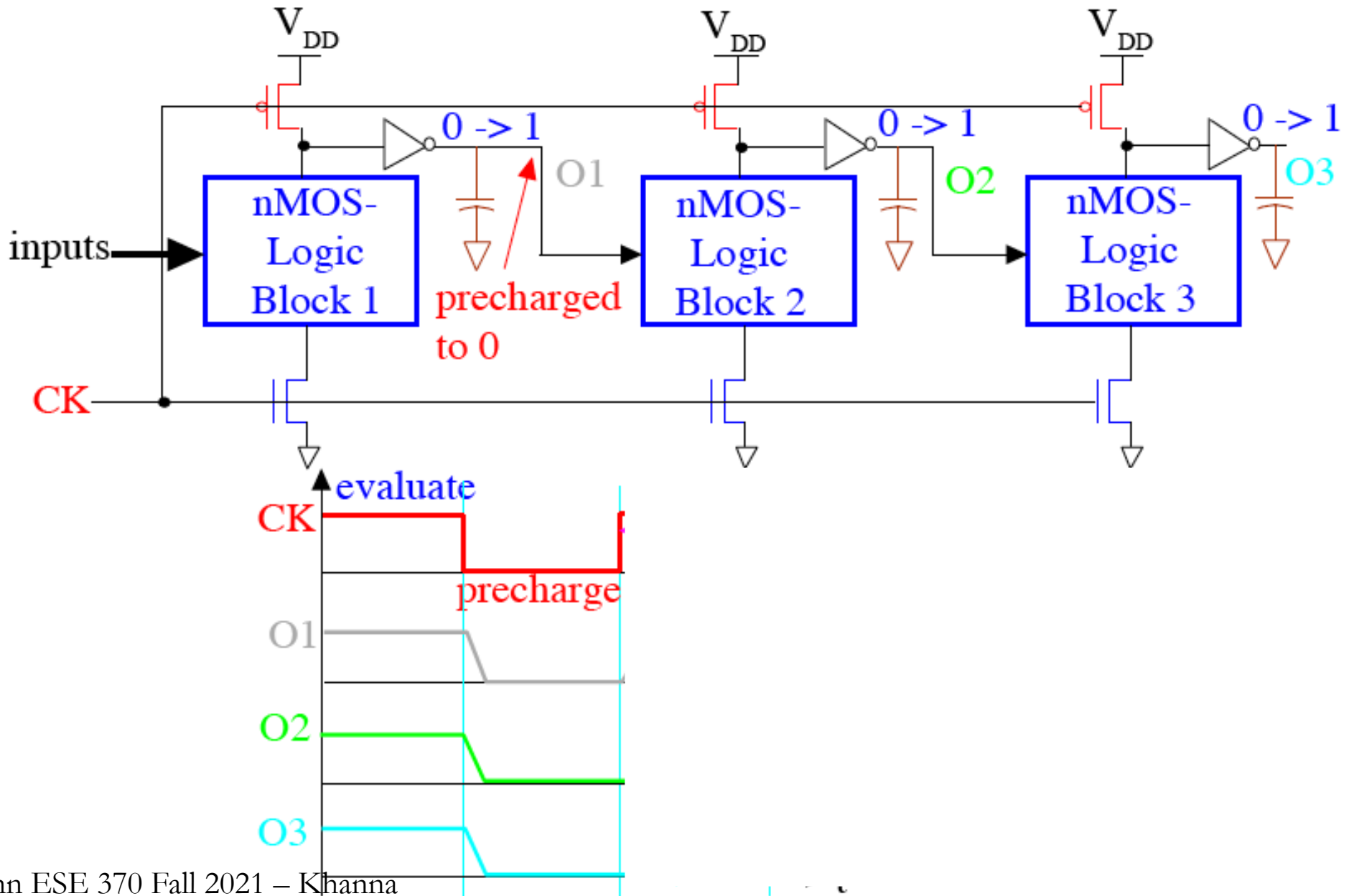

Cascaded Domino CMOS Logic Gates

 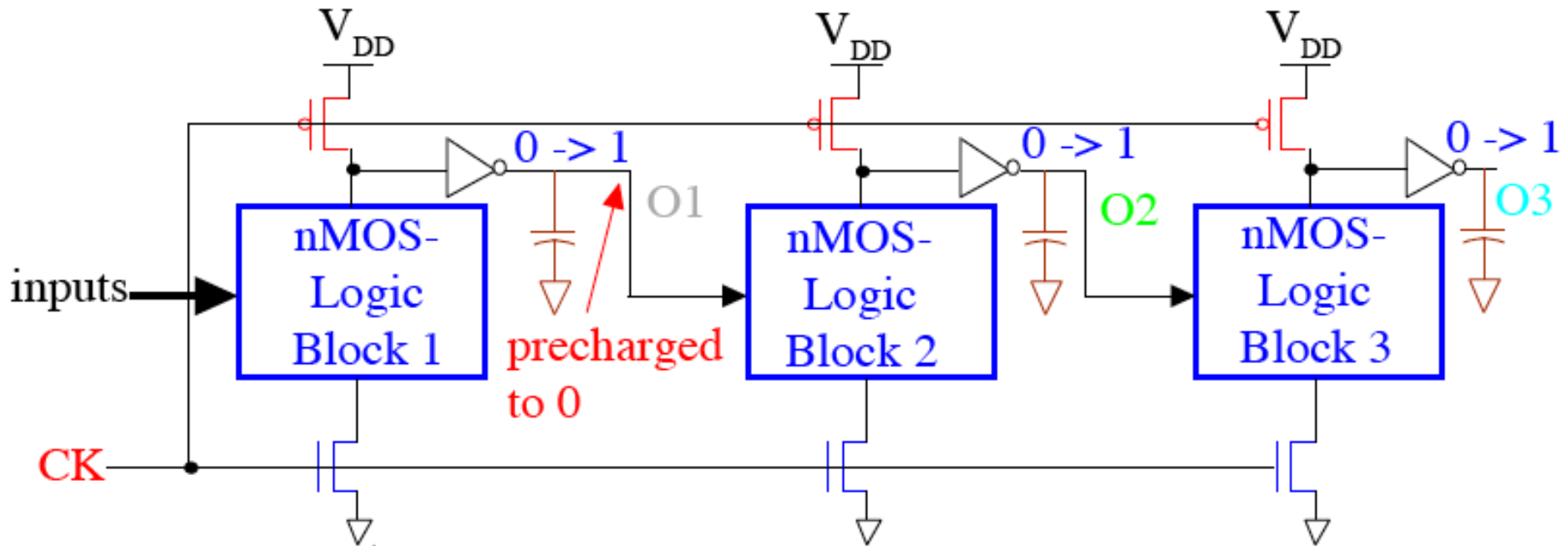


propagating gate decisions

Max # stages limited:
total prop delay $< t_{eval}$.



Domino or4 (Preclass 4)

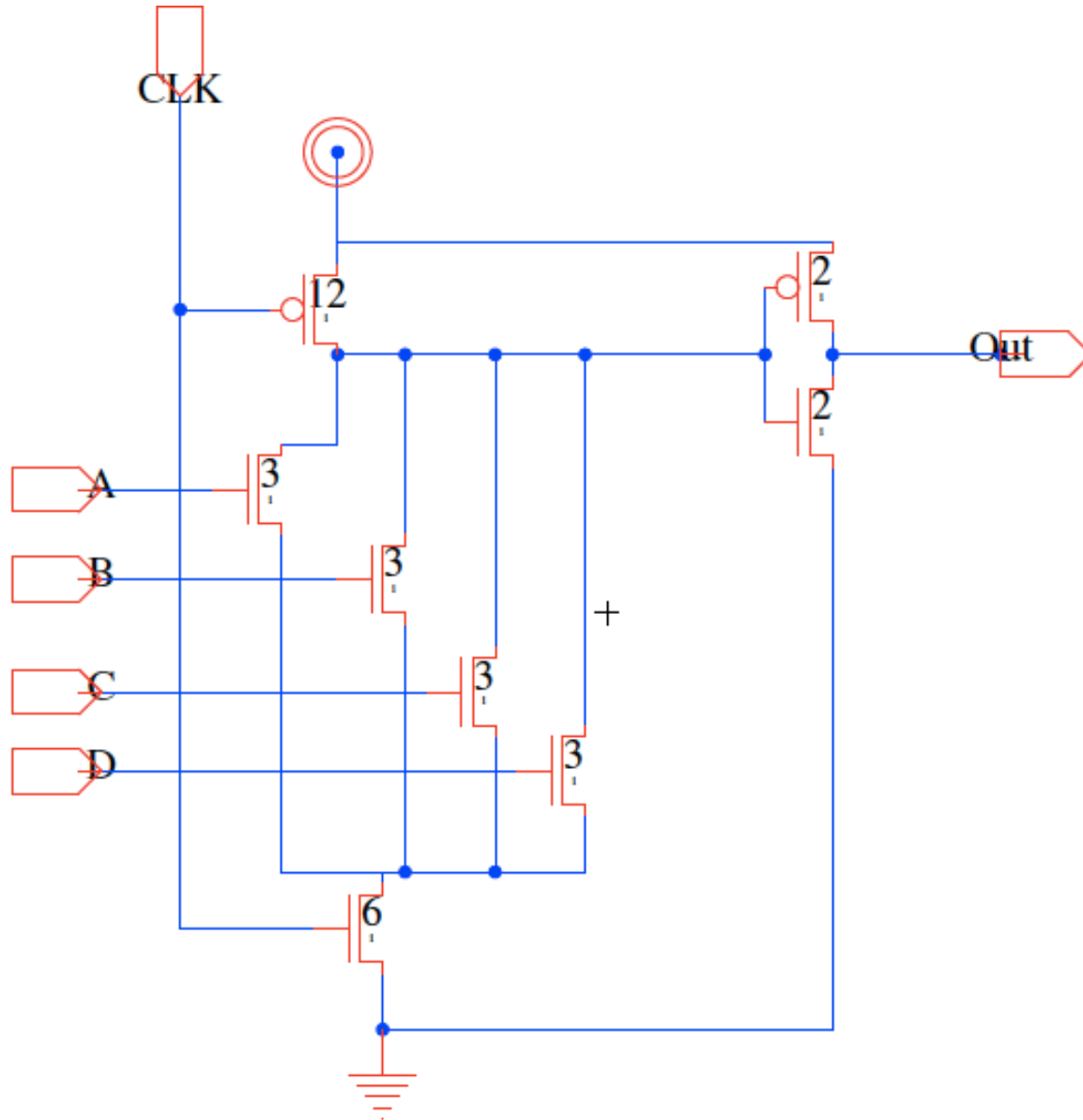


Domino Logic (Preclass 4)

□ Performance

- $R_0/2$ input


□ Compare to CMOS cases?

- nor4
- or4
- nand4

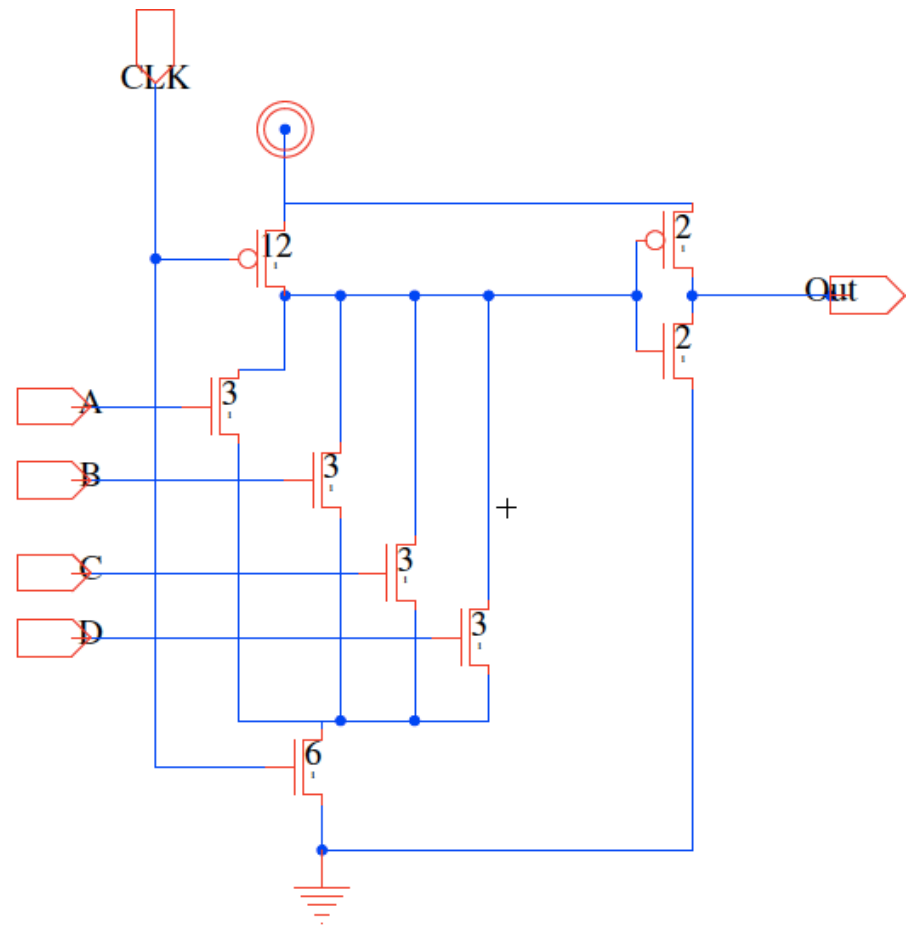


Dynamic OR4 (Preclass 4)

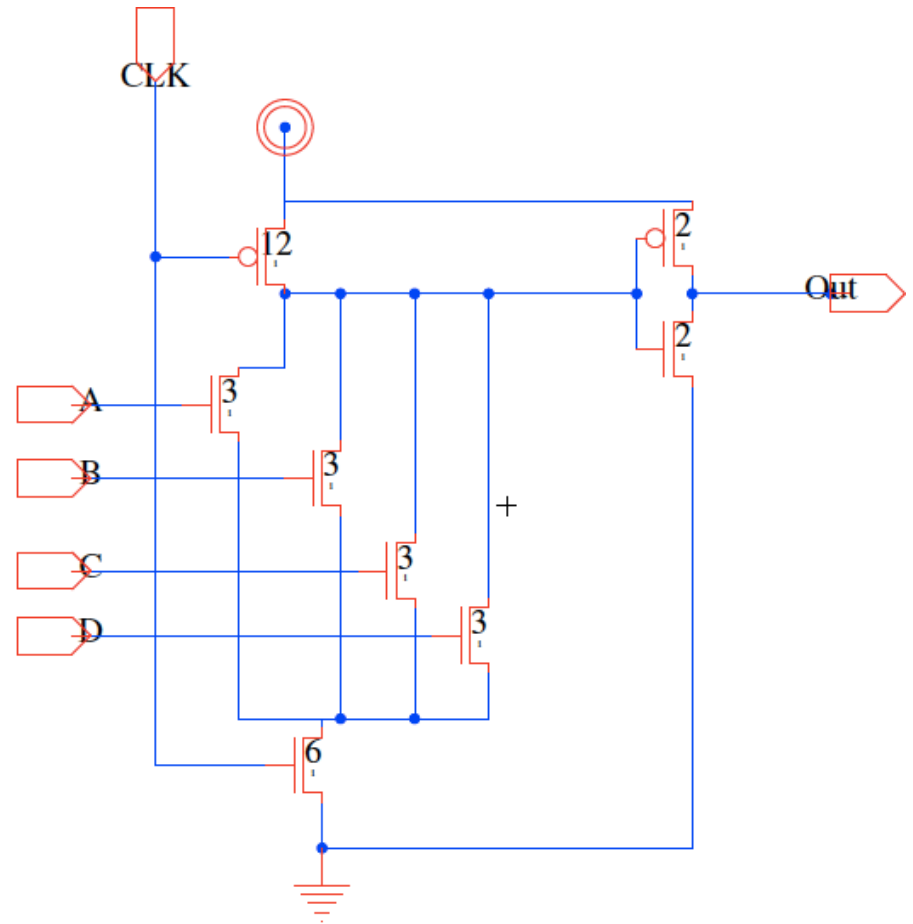- Precharge time?
- Driving input
 - With $R_0/2$ inverter
- Driving inverter?
- Self output Delay?




CMOS NOR4 (Preclass 4)

 - Driving input
 - With $R_0/2$ inverter
- Self output Delay?



CMOS NAND4 (Preclass 4)

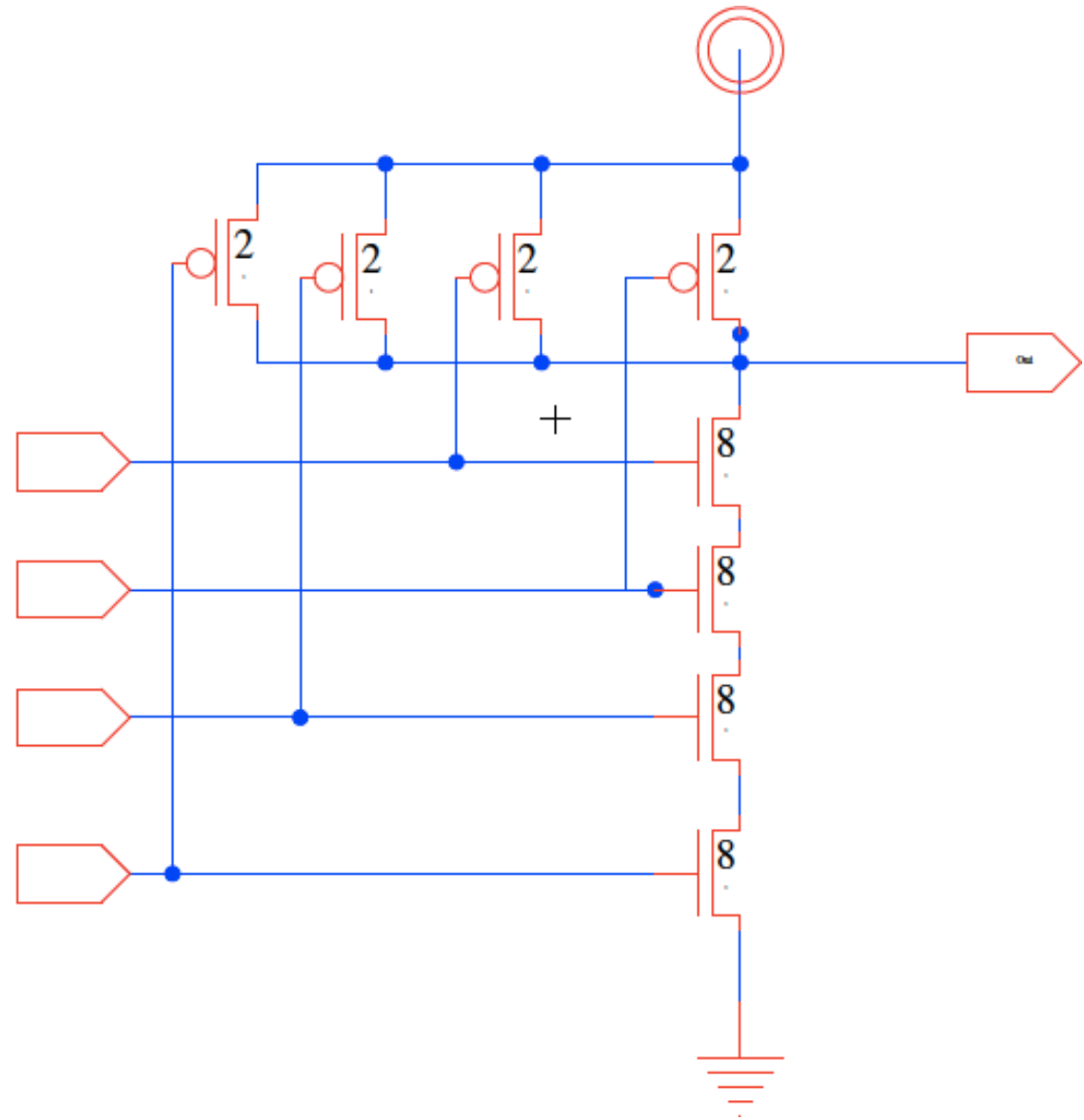- Driving input
 - With $R_0/2$
- Driving self cap?





Dynamic Logic Issues

- ❑ Noise sensitive

- During evaluation phase, when output is high it's floating and therefore more susceptible to noise

- ❑ Power

- Eliminates static current
- Higher activity factor—always a $0 \rightarrow 1$ transition, large pre-charge device dissipates extra switching power



Observe

- ❑ Better (lower) ratio of input capacitance to drive strength
- ❑ Particularly good for
 - Driving large loads
 - Large fanin gates
- ❑ Harder to design with
 - Timing and polarity restrictions
 - Avoiding noise
 - Especially with today's high variation tech
- ❑ Can consume more energy



Idea

- ❑ Clock discipline simplifies logic composition
 - Breaking logic up with registers allows circuit to run at high frequency
 - Abstracts many internal timing details
 - Setup/Hold time, $\text{clk} \rightarrow \text{q}$ delay
 - Just concerned with making clock period long enough
- ❑ Dynamic/clocked logic
 - Only build/drive one pulldown network
 - Domino Logic
 - Fast transition propagation
 - Spend delay (capacitance) on pullup of critical path of logic
 - More complicated design, power dissipation
 - Reserve for when most needed



Admin

- Homework 6
 - Due **Friday 11/12**