

ESE370: Circuit-Level Modeling, Design, and Optimization for Digital Systems

Lec 26: November 10, 2021

Dynamic Logic Pt 2, Memory Overview




Today

- Dynamic (Clocked) Logic
 - Domino Logic
 - Compare CMOS
- Memory Overview



Dynamic Logic

Idea

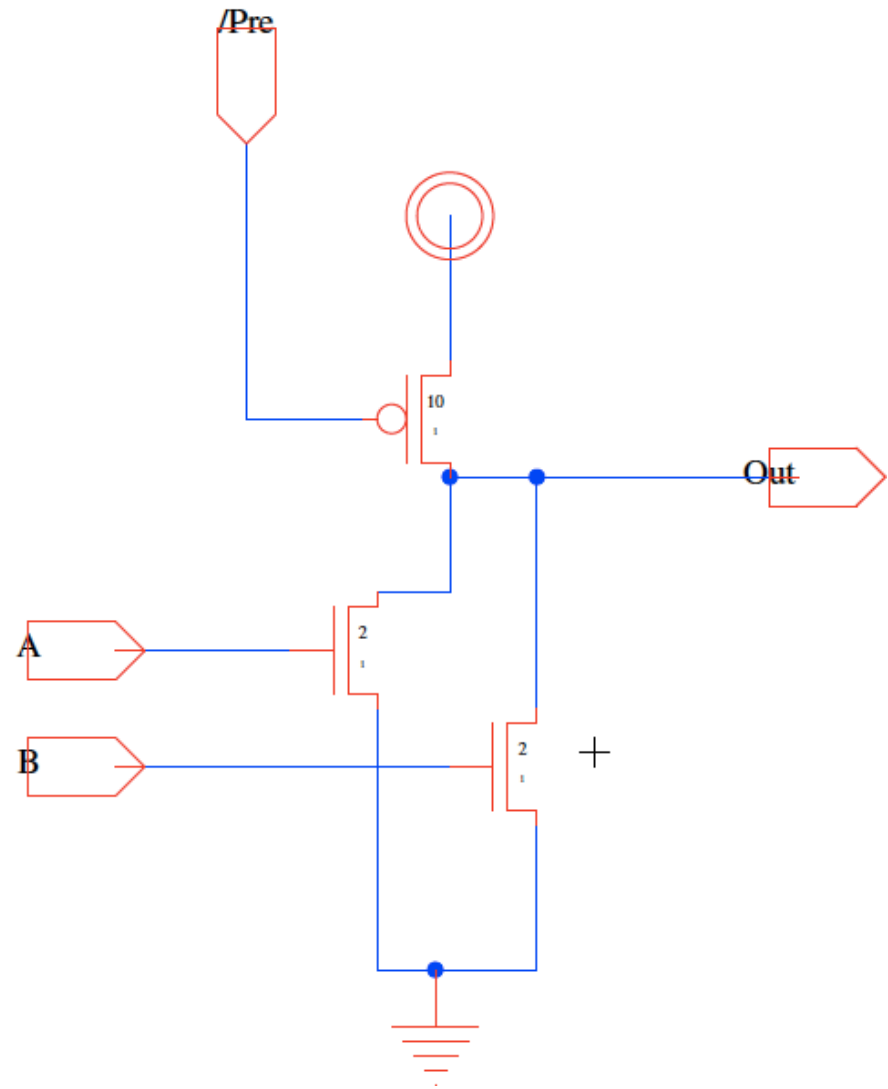- ❑ Use clock to disable pullup network during logic evaluation
- ❑ Define two phases
 - Pre-charge
 - Output pre-charged
 - Evaluation
 - Pulldown network evaluates gate logic




Cascaded Dynamic Logic

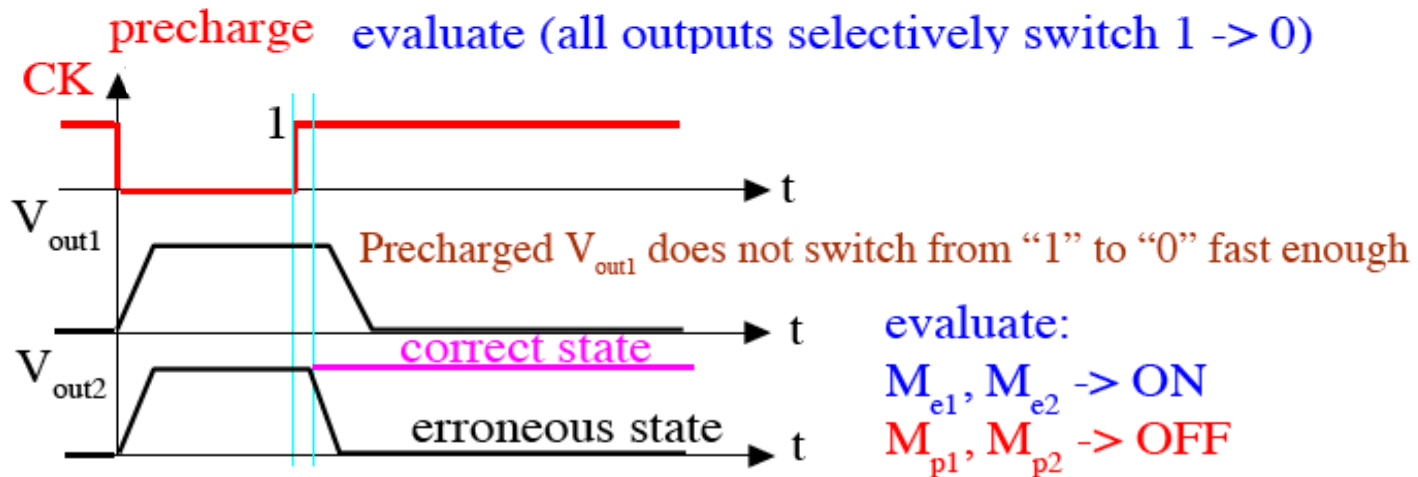 

**PROBLEM: ALL STAGES MUST EVALUATE SIMULTANEOUSLY
 SINGLE CLOCK DOES NOT PERMIT PIPELINING OF STAGES**




Domino Logic

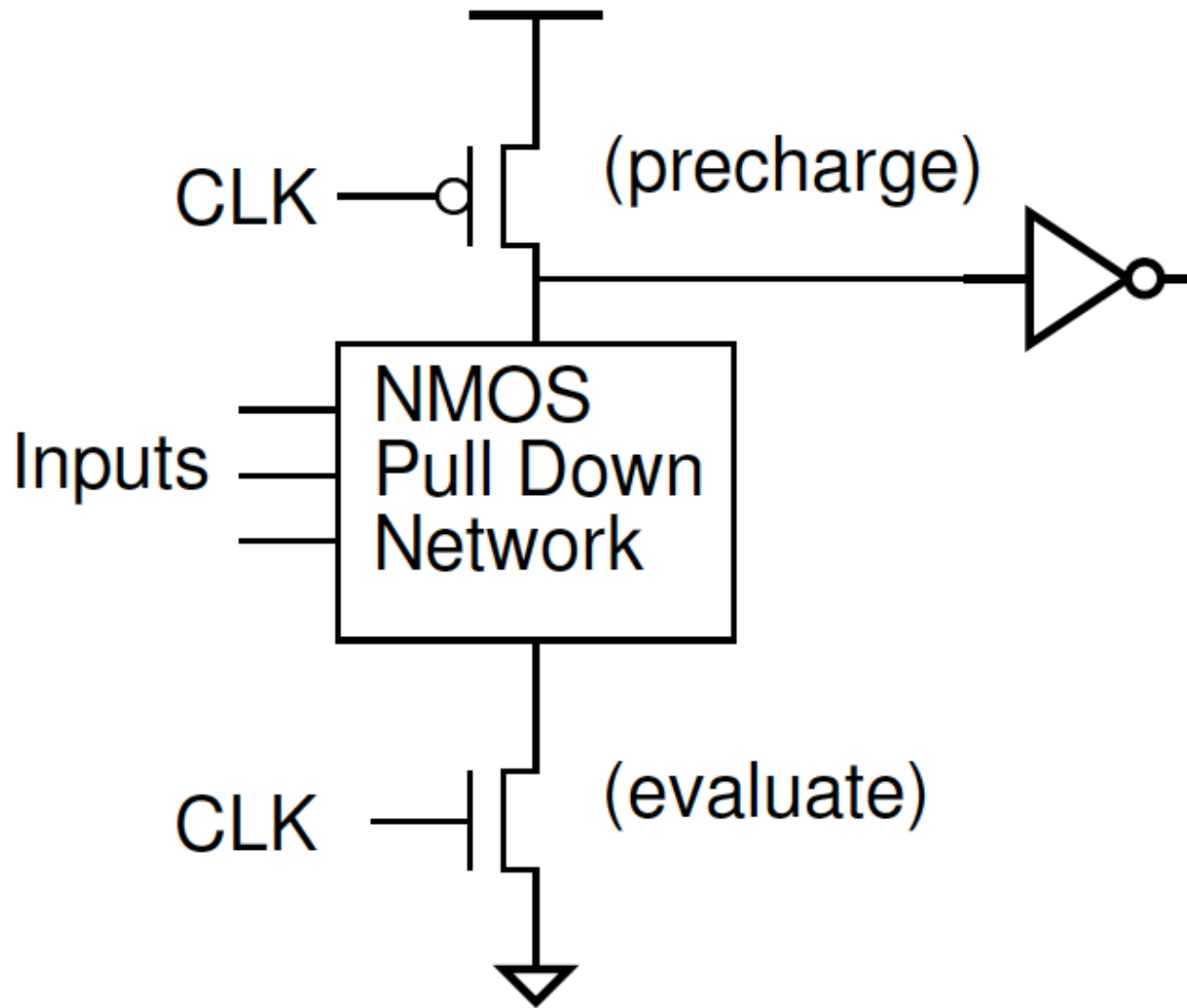




Requirements


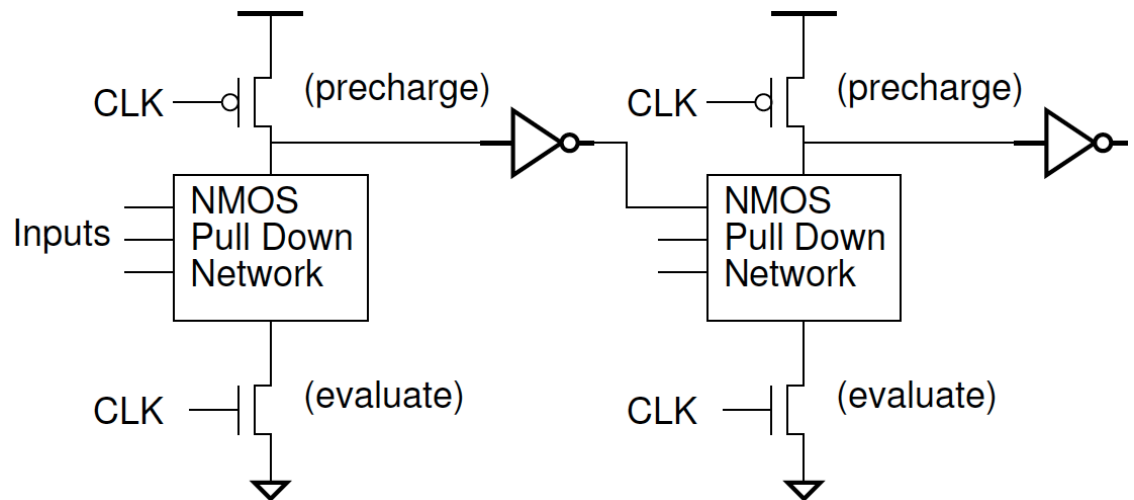
- ❑ Single transition
 - Once transitioned, it is done → like domino falling
- ❑ All inputs at 0 during precharge
 - “Outputs” pre-charged to 1 then inverted to 0
- ❑ Non-inverting gates fundamental gate





Cascaded Domino CMOS Logic Gates

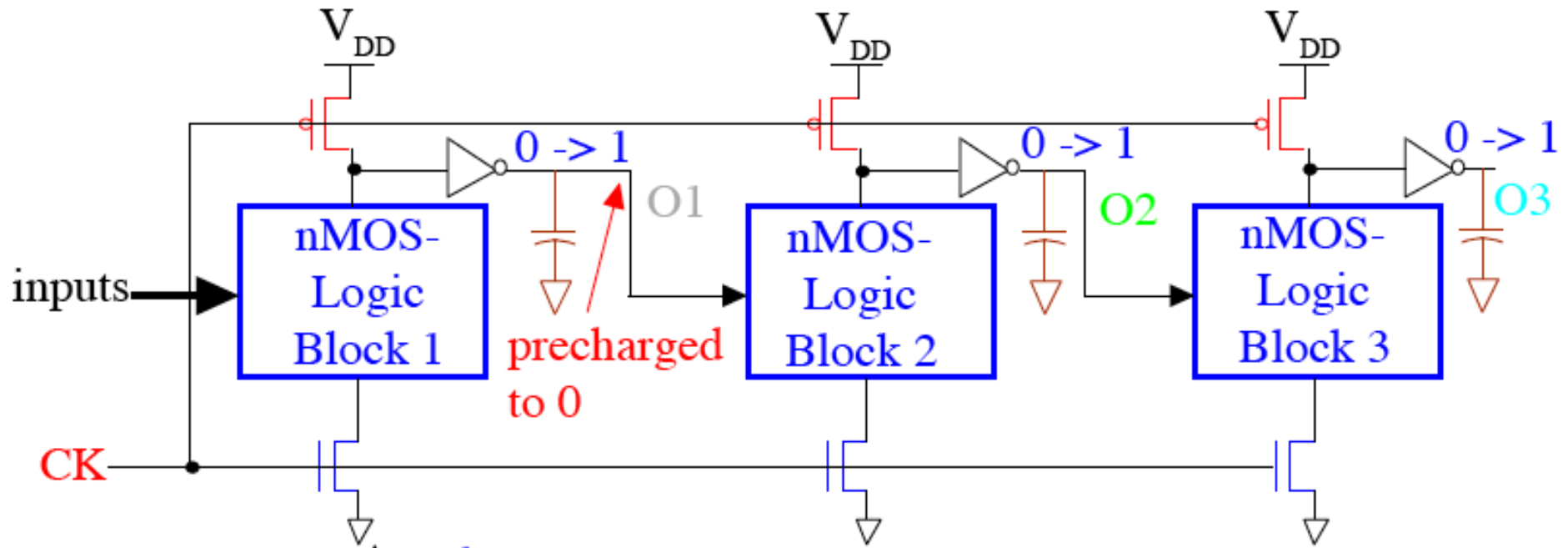

Cascaded Domino CMOS Logic Gates

 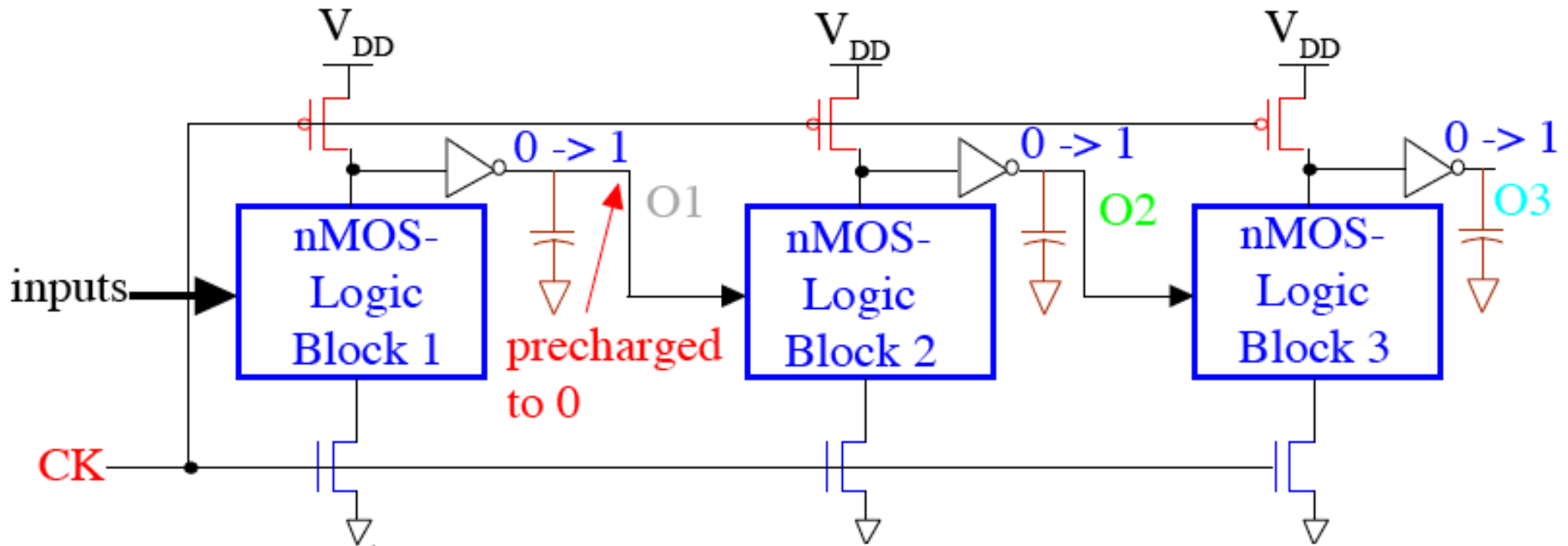

Cascaded Domino CMOS Logic Gates

 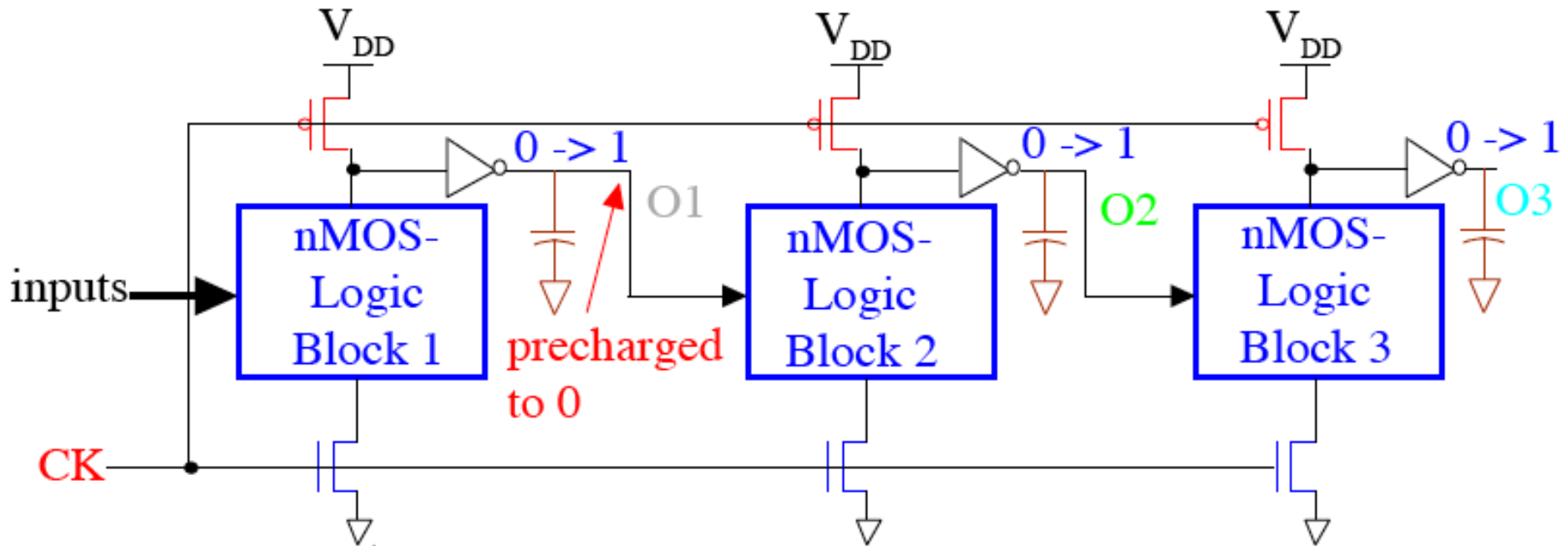


propagating gate decisions

Max # stages limited:
total prop delay $< t_{eval}$.



Domino or4 (Preclass 3)

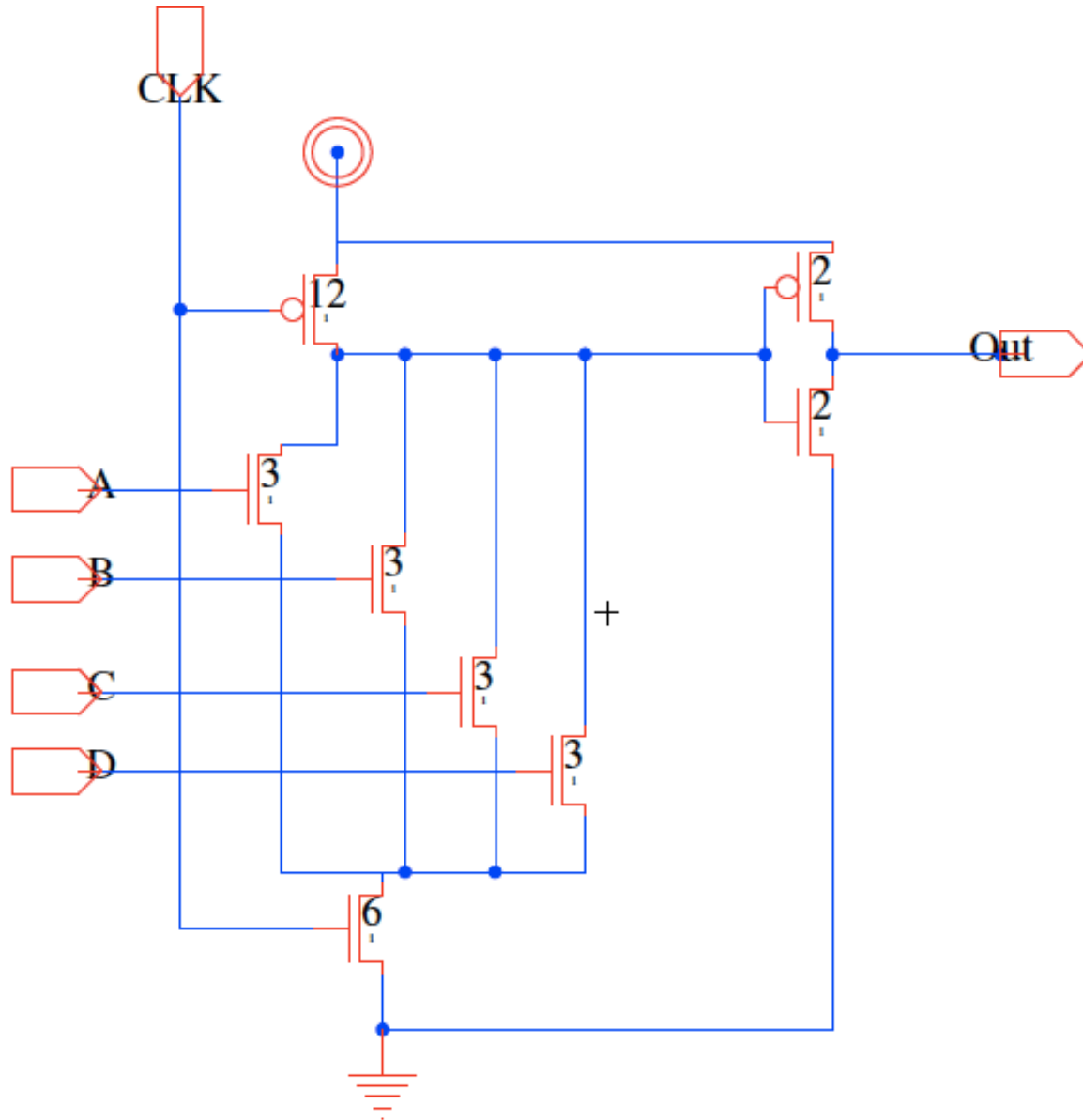


Domino Logic (Preclass 3)

□ Performance

- $R_0/2$ input


□ Compare to CMOS cases?

- nor4
- or4
- nand4

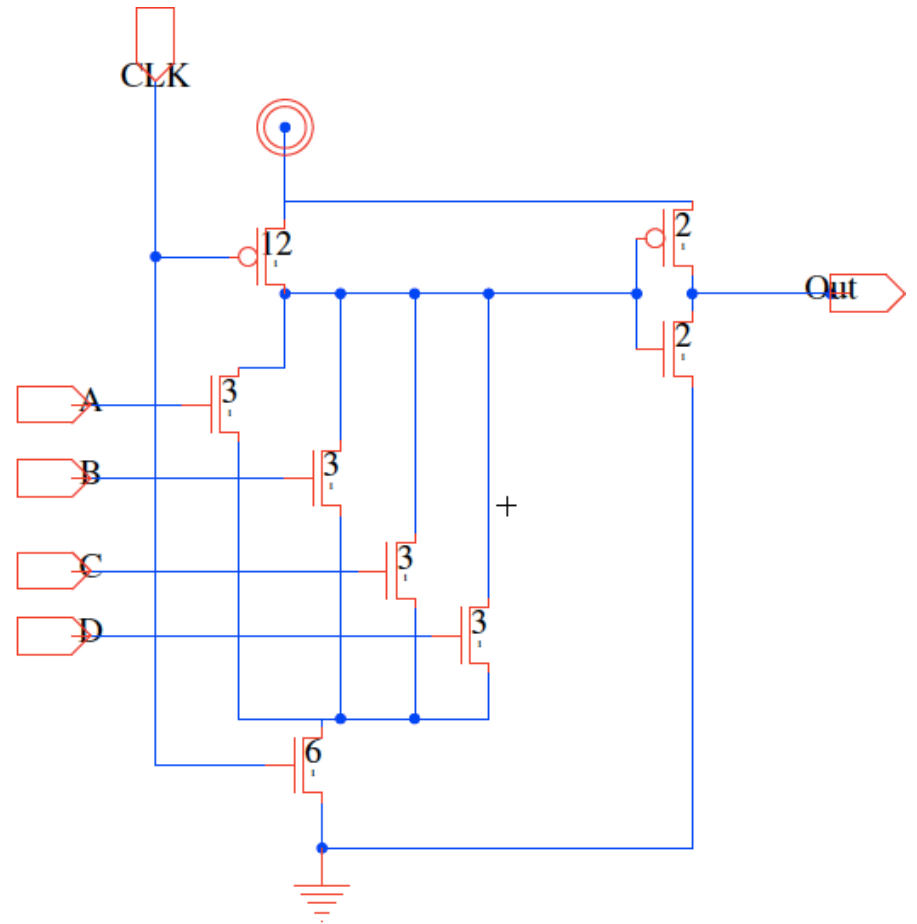


Dynamic OR4 (Preclass 3)

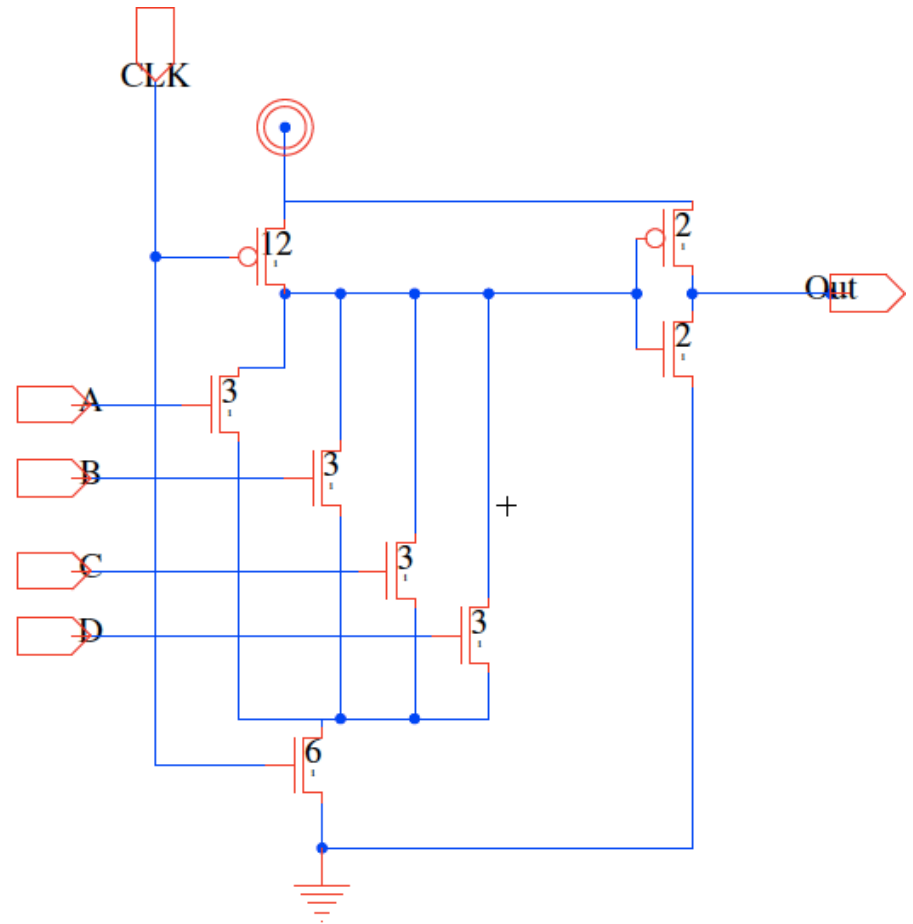- ❑ Precharge time?
- ❑ Driving input
 - With $R_0/2$ inverter
- ❑ Driving inverter?
- ❑ Self output Delay?



CMOS NOR4 (Preclass 3)

 - Driving input
 - With $R_0/2$ inverter
- Self output Delay?





Dynamic Logic Issues

- ❑ Noise sensitive

- During evaluation phase, when output is high it's floating and therefore more susceptible to noise

- ❑ Power

- Eliminates static current
- Higher activity factor—always a $0 \rightarrow 1$ transition, large pre-charge device dissipates extra switching power



Observe

- ❑ Better (lower) ratio of input capacitance to drive strength
- ❑ Particularly good for
 - Driving large loads
 - Large fanin gates
- ❑ Harder to design with
 - Timing and polarity restrictions
 - Avoiding noise
 - Especially with today's high variation tech
- ❑ Can consume more energy


Memory Overview



Semiconductor Memory Classification


RWM		NVRWM	ROM
Random Access	Non-Random Access	EPROM E ² PROM FLASH	Mask-Programmed Programmable (PROM)
SRAM DRAM	FIFO LIFO Shift Register CAM		

Memory Architecture: Core

 

N words \Rightarrow N select signals
Too many select signals

Memory Architecture: Decoders

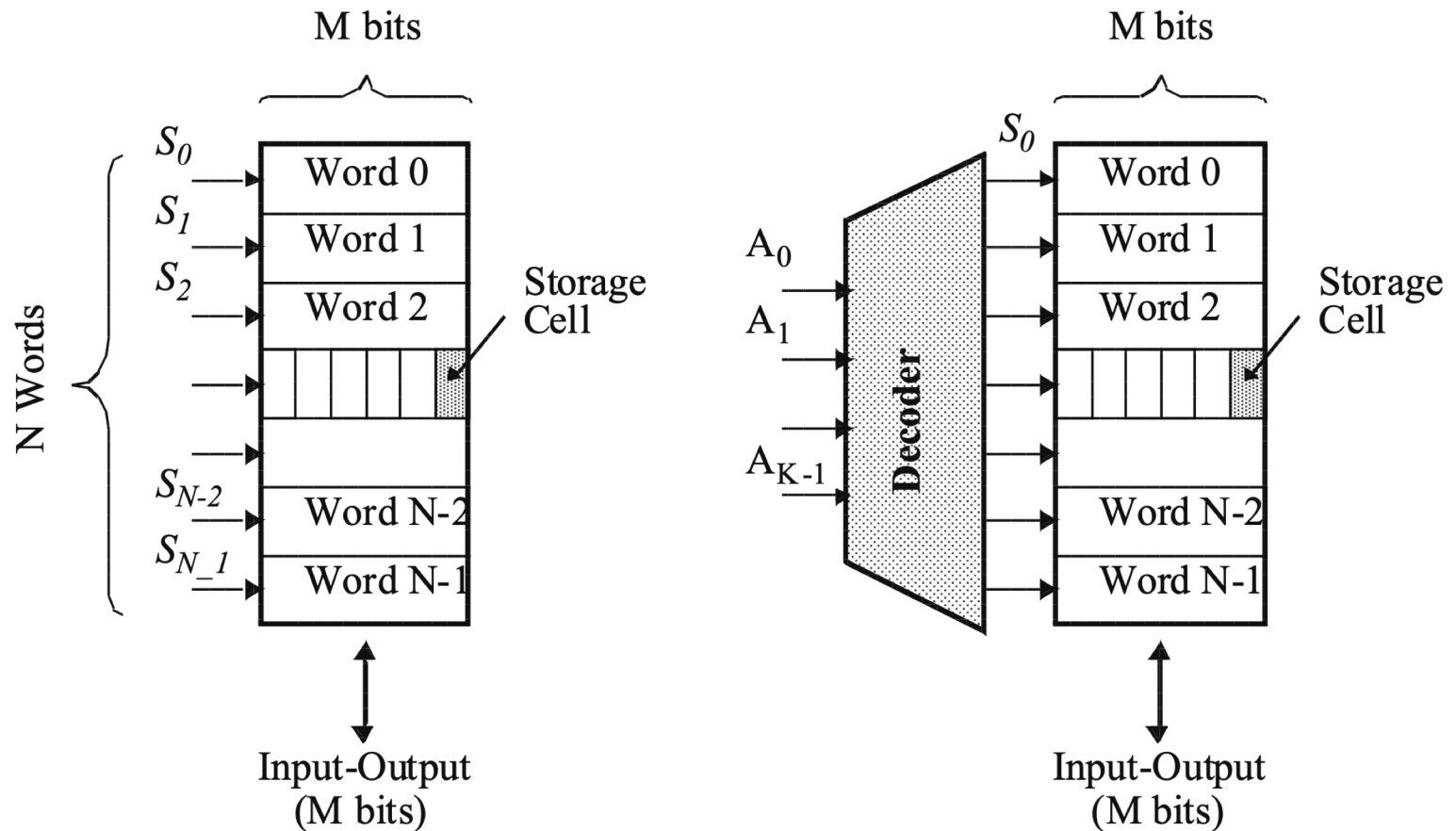


N words $\Rightarrow N$ select signals
Too many select signals

Decoder reduces # of select signals
 $K = \log_2 N$



Array-Structured Memory Architecture

Problem: ASPECT RATIO or HEIGHT >> WIDTH

 


Latches/Register – Can Store a State

  - ❑ Build register from pair of latches
- ❑ Control with non-overlapping clocks




ROM Memories

MOS NOR ROM

 




MOS NOR ROM

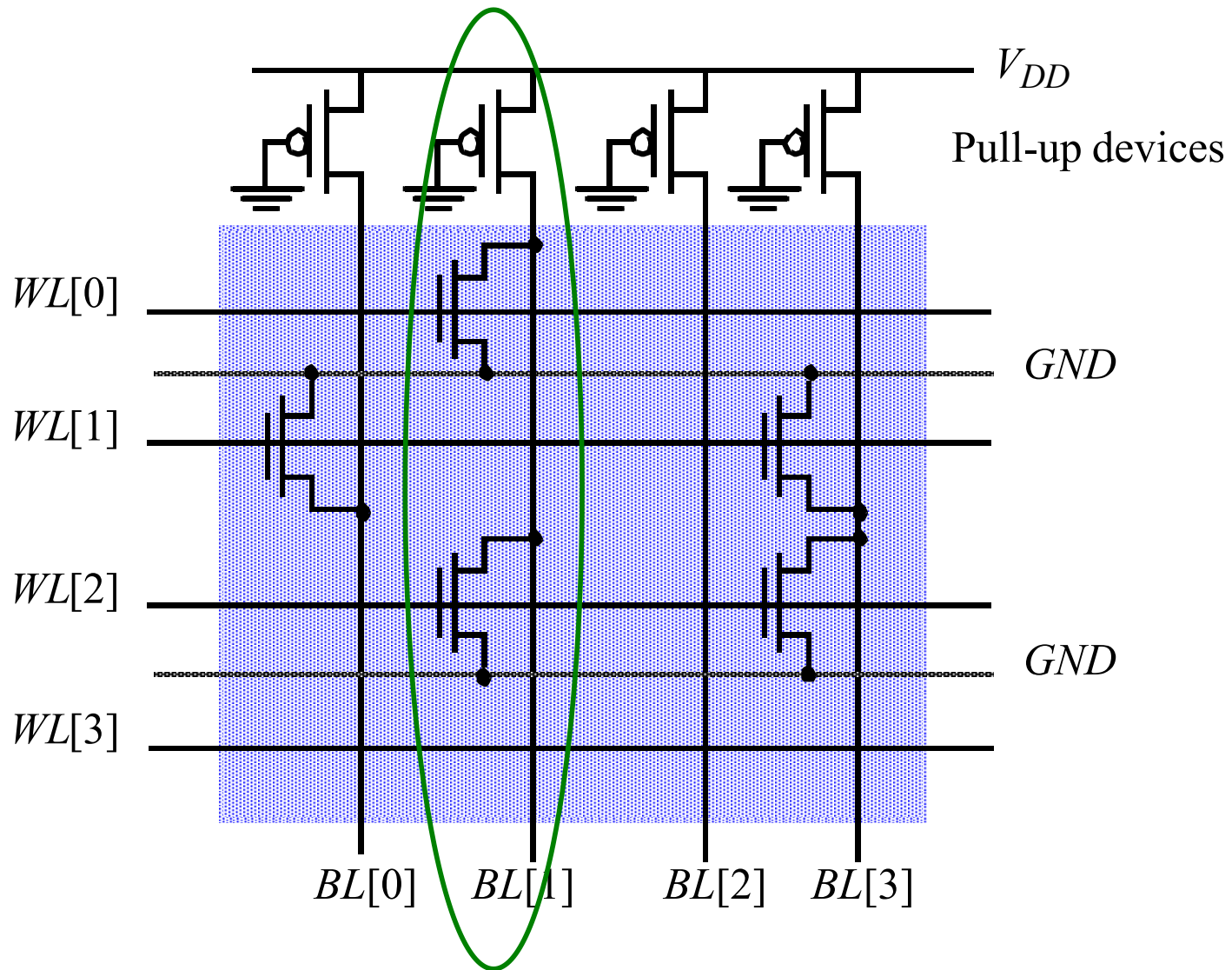




MOS NOR ROM

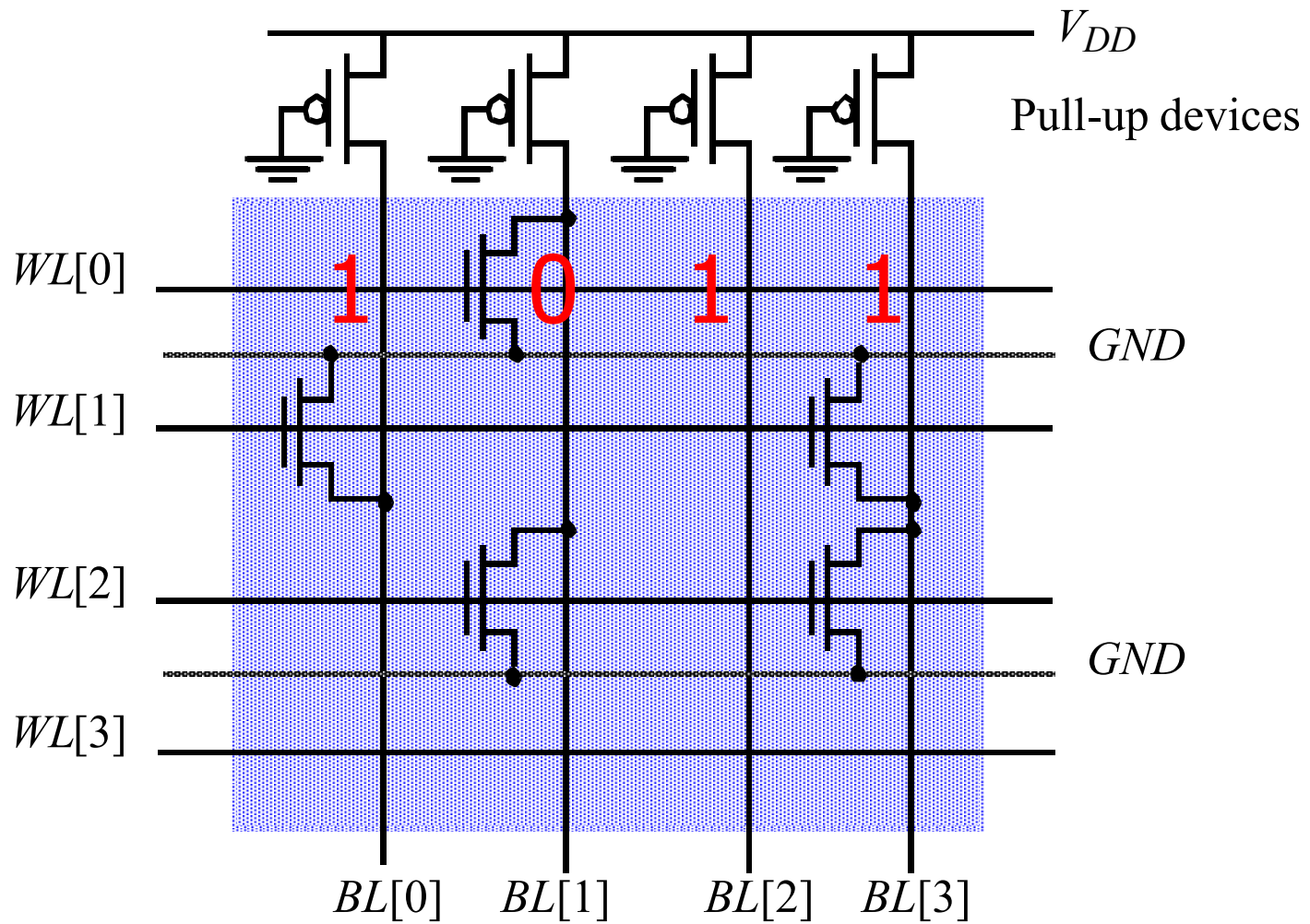




MOS NOR ROM

 




MOS NAND ROM

 

All word lines high by default with exception of selected row




MOS NAND ROM

 

All word lines high by default with exception of selected row




MOS NAND ROM

 

All word lines high by default with exception of selected row

Array-Structured Memory Architecture

Problem: ASPECT RATIO or HEIGHT >> WIDTH

 



Idea

- ❑ Dynamic/clocked logic
 - Only build/drive one pulldown network
 - Domino Logic
 - Fast transition propagation
 - Spend delay (capacitance) on pullup of critical path of logic
 - More complicated design, power dissipation
 - Reserve for when most needed
- ❑ Memory for compact state storage
 - Minimize area per bit → maximize density



Admin

- Homework 6
 - Due **Friday 11/12**