

Assume: velocity saturated, $R_0/2$ sizing for gate drive; inverter sizing is: $W_n=W_p=2$

1. Determine delays (express in τ units in terms of γ):

	Precharge	Drive Input	Drive Inv. and Self Output
	(pullup transistor charging inverter)		
	—	Input	Self Output Delay