

ESE370: Circuit-Level Modeling, Design, and Optimization for Digital Systems

Lec 27: November 12, 2021

Memory Periphery, Serial Access Memories




Today

- Memory
 - Classification
 - Architecture
 - Periphery
 - Serial Access Memories

- Project 2 is on this

Array-Structured Memory Architecture

 
Problem: ASPECT RATIO or HEIGHT \gg WIDTH



ROM Memories




MOS NOR ROM

 




MOS NOR ROM

 




MOS NAND ROM

 

All word lines high by default with exception of selected row




MOS NAND ROM

 

All word lines high by default with exception of selected row



MOS NAND ROM

 

All word lines high by default with exception of selected row

Memory Periphery




Periphery

- ❑ Decoders
- ❑ Column Circuitry
 - Bit-line Conditioning
 - Sense Amplifiers
 - Input/Output Buffers
- ❑ Control/Timing Circuitry


Array Architecture

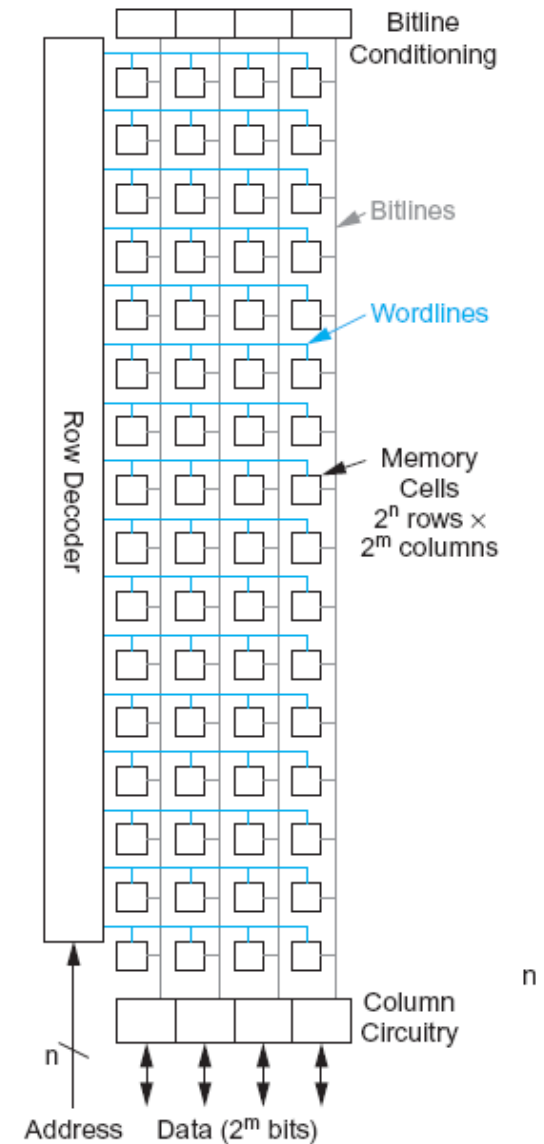- ❑ 2^n words of 2^m bits each
- ❑ Good regularity – easy to design
- ❑ Very high density if good cells are used



Array Architecture

 
- ❑ 2^n words of 2^m bits each
- ❑ Good regularity – easy to design
- ❑ Very high density if good cells are used



Decoders

Array Architecture

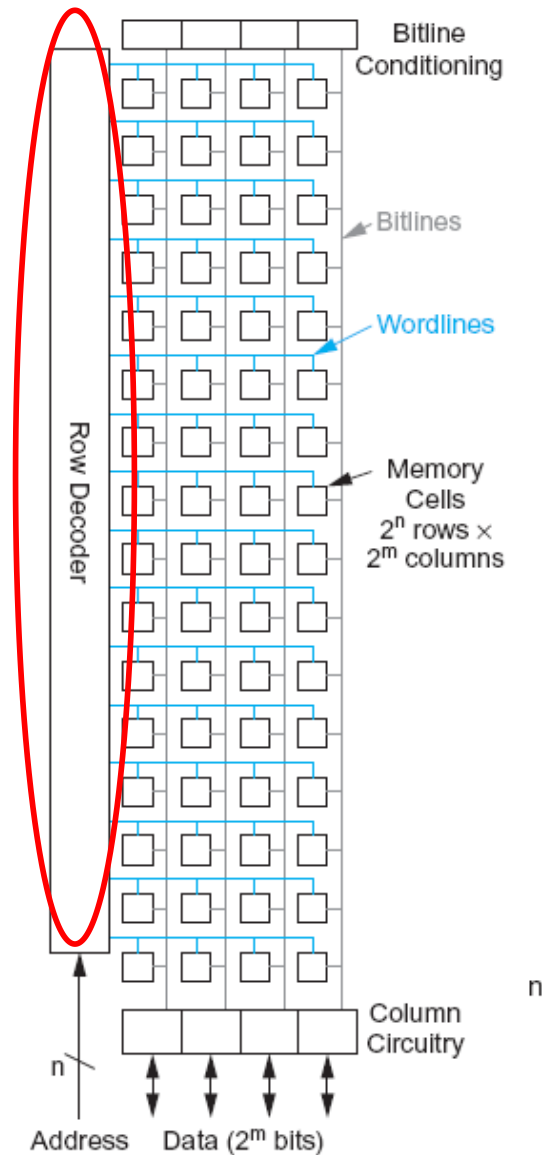- ❑ 2^n words of 2^m bits each
- ❑ Good regularity – easy to design
- ❑ Very high density if good cells are used






Decoders

- $n:2^n$ decoder consists of 2^n n -input AND gates
 - One needed for each row of memory
 - Build AND from NAND or NOR gates


Static CMOS

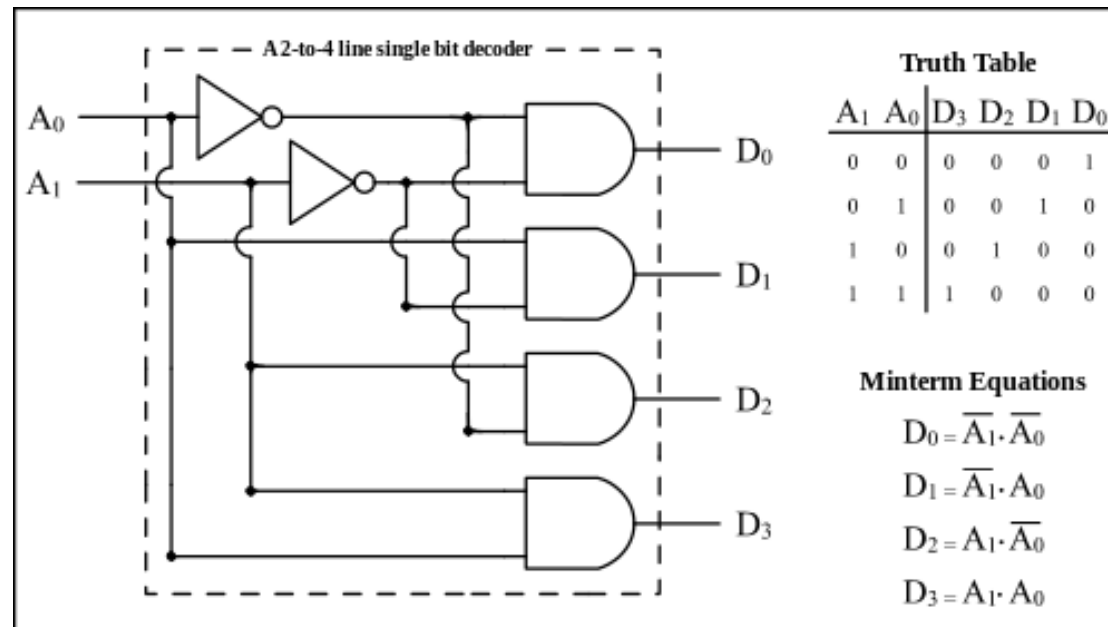



Large Decoders

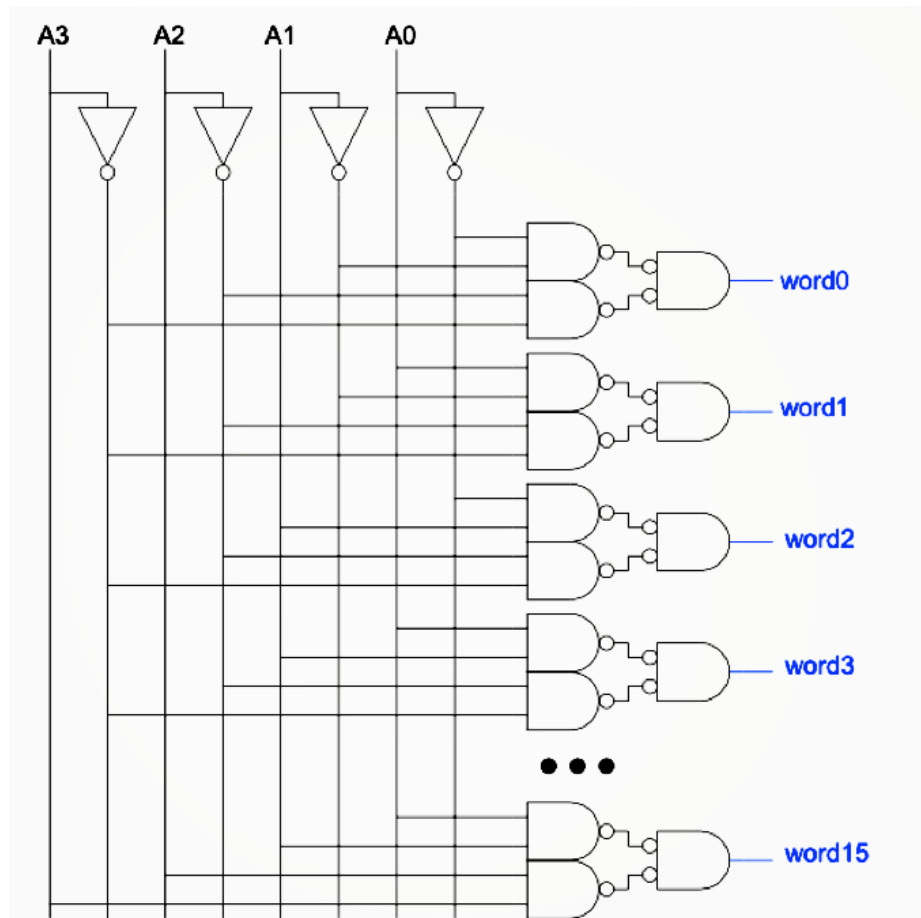
- ❑ For $n > 4$, NAND gates become slow
 - Break large gates into multiple smaller gates





Large Decoders

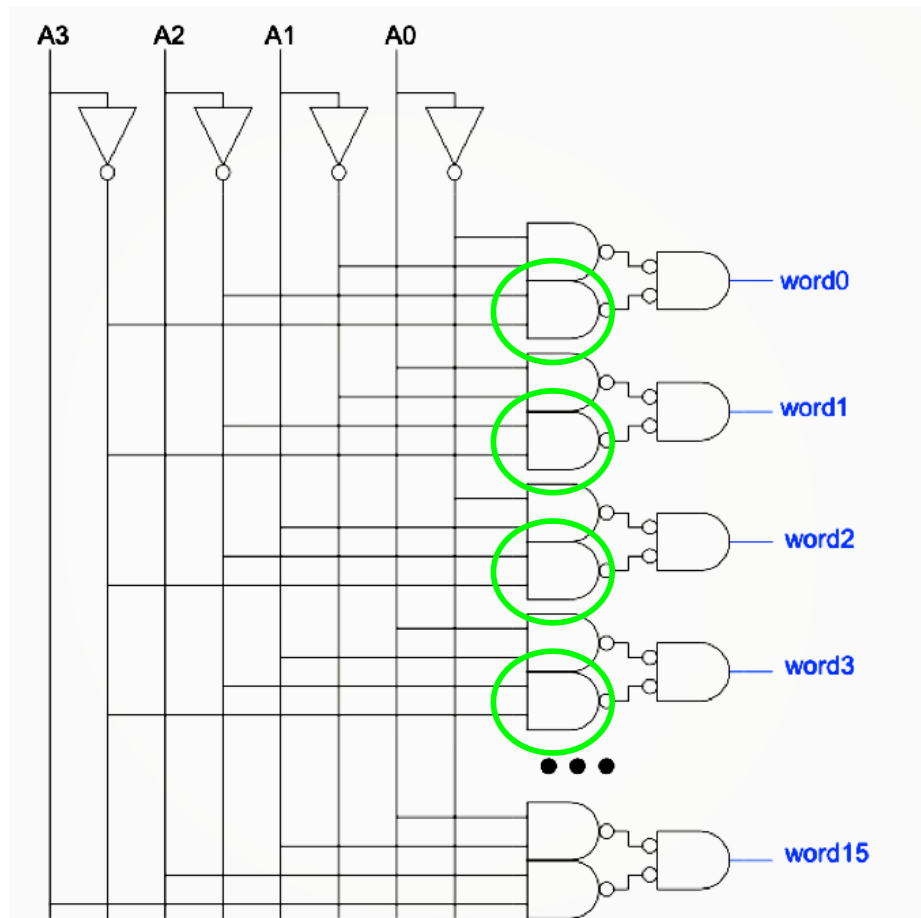
- ❑ For $n > 4$, NAND gates become slow
 - Break large gates into multiple smaller gates






Predecoding

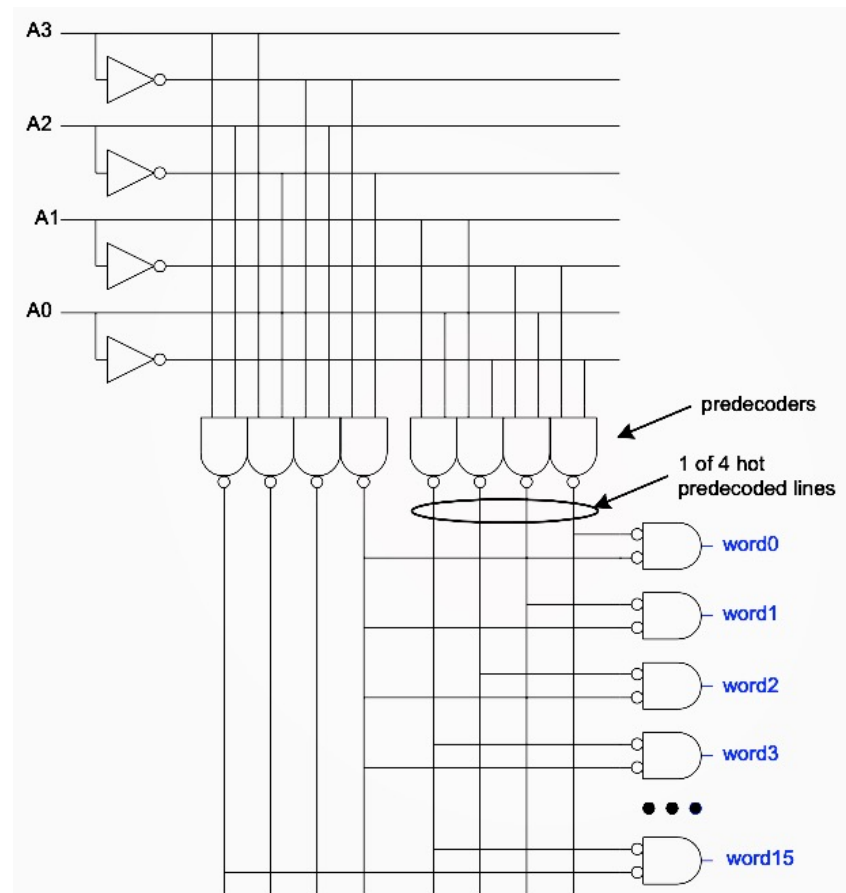- ❑ Many of these gates are redundant
 - Factor out common gates into predecoder
 - Saves area
 - Same path effort




Row Select: Precharge NAND

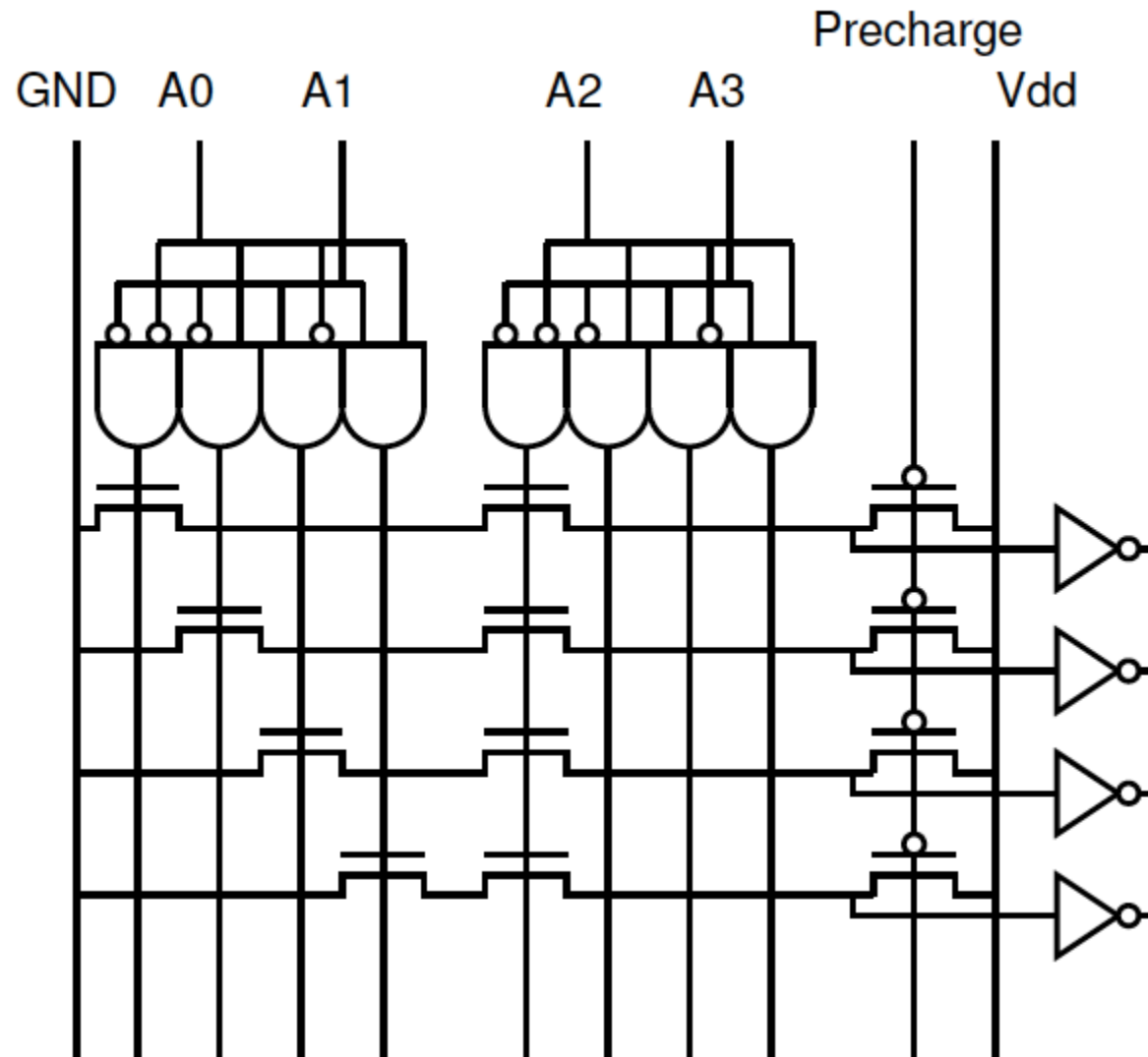




Row Select: Precharge NAND

 

Row Select: Precharge NOR

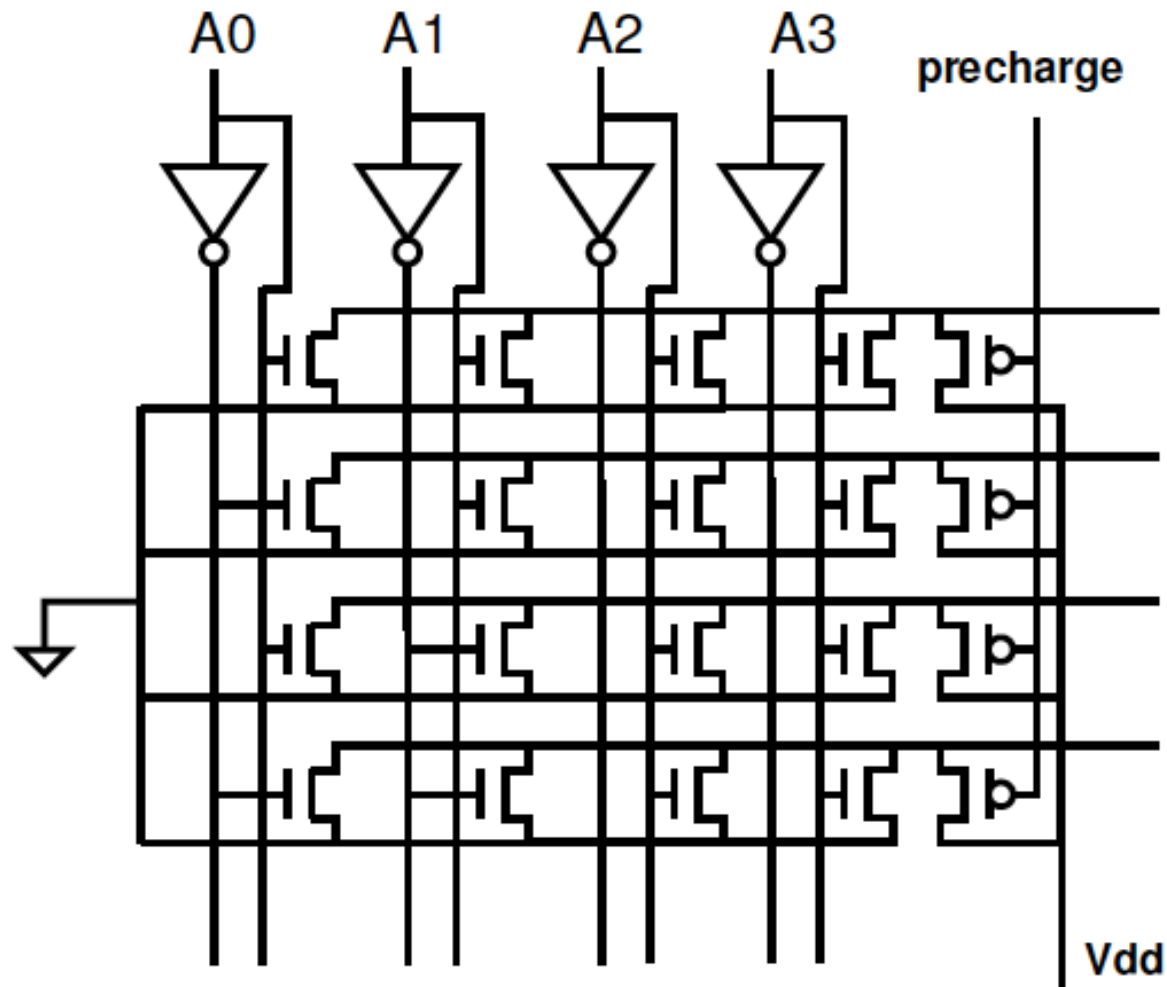


Column Circuitry

& Bit-line Conditioning


Array Architecture

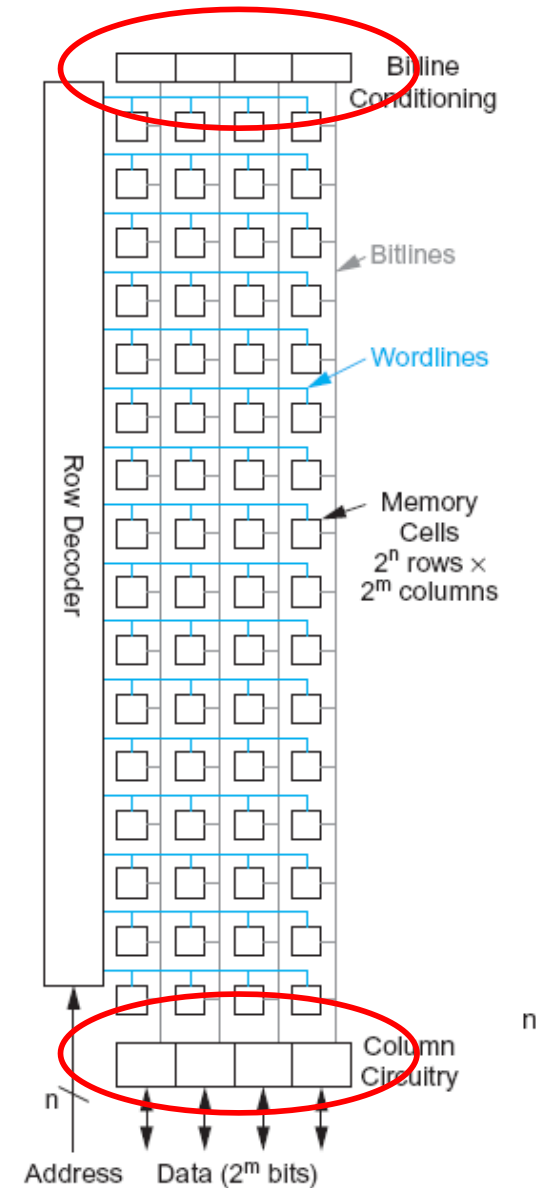- ❑ 2^n words of 2^m bits each
- ❑ Good regularity – easy to design
- ❑ Very high density if good cells are used




Array Architecture

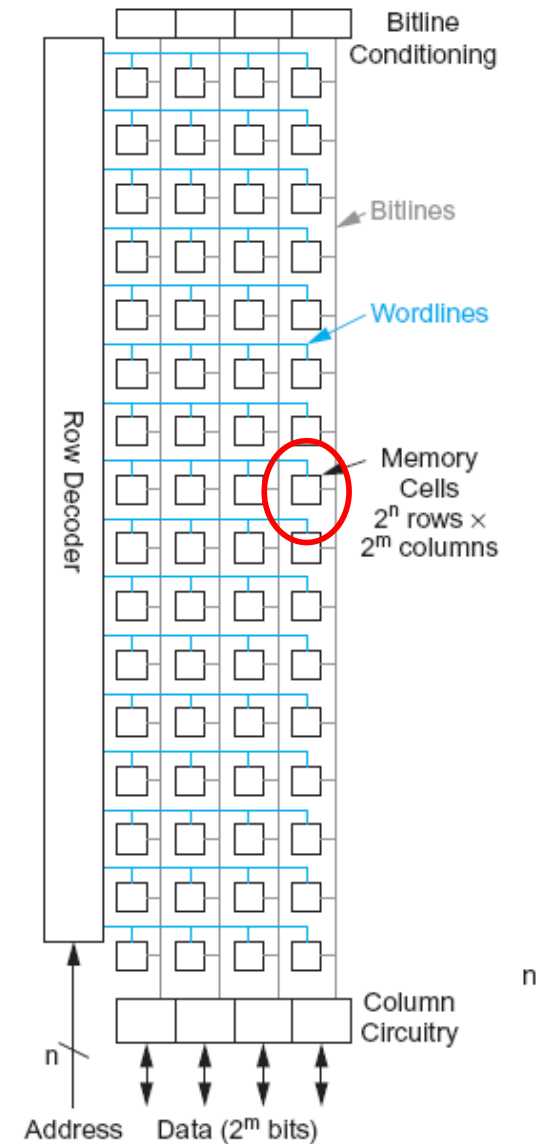- ❑ 2^n words of 2^m bits each
- ❑ Good regularity – easy to design
- ❑ Very high density if good cells are used



6T SRAM Cell

 - ❑ Cell size accounts for most of array size
 - Reduce cell size at expense of complexity
- ❑ 6T SRAM Cell
 - Used in most commercial chips
 - Data stored in cross-coupled inverters
- ❑ Read:
 - Precharge BL, BL'
 - Raise WL
- ❑ Write:
 - Drive data onto BL, BL'
 - Raise WL






Column Circuitry

- Some circuitry is required for each column
 - **Required:** Bitline conditioning
 - Precharging
 - Driving input data to bitline
 - **Increased speed:** Sense amplifiers
 - **Aspect ratio (square memory):** Column multiplexing (AKA Column Decoders)



Bitline Conditioning


 
- ❑ Precharge bitlines high before read operations







Bitline Conditioning

- ❑ Precharge bitlines high before reads

  

Bitline Conditioning



- Precharge bitlines high before reads

  

- What if pre-charged to $V_{DD}/2$?
 - Pros: reduces read-upset
 - Challenge: generate $V_{DD}/2$ voltage on chip



Column Capacitance Consequence

  - ❑ Preclass1: What is capacitance of a bitline?
 - ❑ W_{access} (pass transistor size), d rows, $\gamma = C_{\text{diff0}}/C_0$
- ❑ Preclass2: What is the delay for the cell to drive the bitline during a read?
 - ❑ W_{buf} (inverter size in cell), R_0





Column Capacitance Consequence

  - ❑ Preclass1: What is capacitance of a bitline?
 - ❑ W_{access} (pass transistor size), d rows, $\gamma = C_{\text{diff0}}/C_0$
- ❑ Preclass2: What is the delay for the cell to drive the bitline during a read?
 - ❑ W_{buf} (inverter size in cell), R_0
- ❑ Preclass3: $W_{\text{access}} = W_{\text{buf}} = 1$, $\gamma = 1/2$
 - ❑ Delay for $d = 32, 512$?




Column Capacitance Consequence

 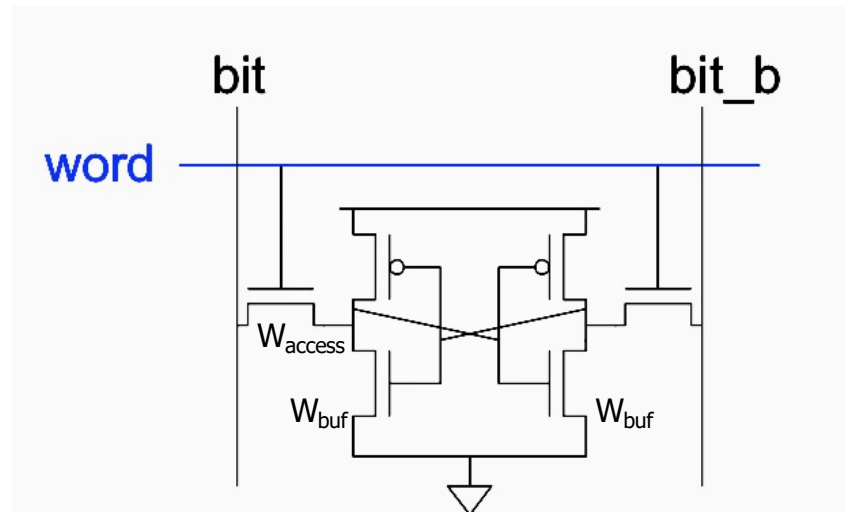- ❑ Preclass1: What is capacitance of a bitline?
 - ❑ W_{access} (pass transistor size), d rows, $\gamma = C_{\text{diff0}}/C_0$
- ❑ Preclass2: What is the delay for the cell to drive the bitline during a read?
 - ❑ W_{buf} (inverter size in cell), R_0
- ❑ **Conclude:** Can't size up cell \rightarrow driving bitline will be slow




Sense Amplifiers

 - Bitlines have many cells attached
 - Ex: 32-kbit SRAM has 128 rows x 256 cols
 - 128 cells on each bitline
- $t_{pd} \propto (C/I) \Delta V$
 - Even with shared diffusion contacts, 64C of diffusion capacitance (big C)
 - Discharged slowly through small transistors in each memory cell (small I)
- *Sense amplifiers* are triggered on small voltage swing (ΔV)



Clocked Sense Amp

 - ❑ Clocked sense amp saves power
- ❑ Requires sense_clk after enough bitline swing
- ❑ Isolation transistors cut off large bitline capacitance





Word Line Capacitance

□ Preclass4: What is capacitance of word line (row)?

- W_{access} – transistor width of column device
- w columns
- $\gamma = C_{\text{diff0}} / C_0$


□ Preclass5: Delay driving word line?

- W_{wldrive} Drive inverter

 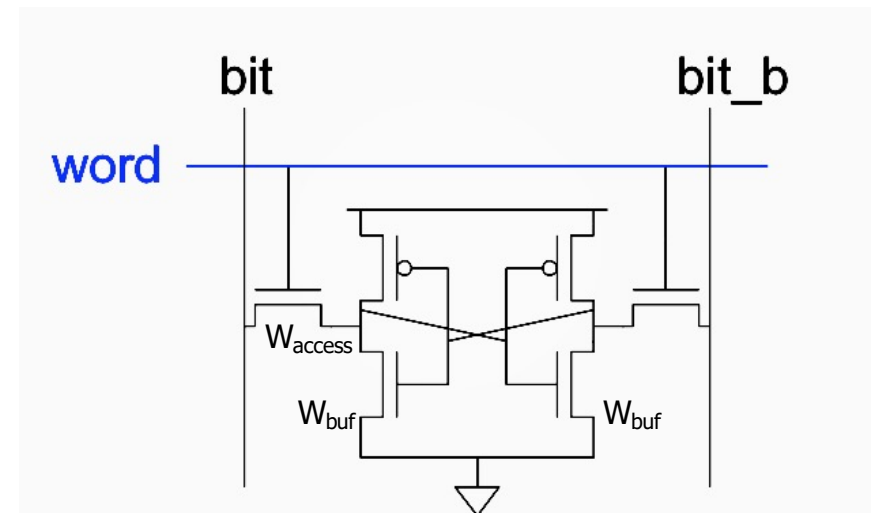




Column Drivers: Memory Bank

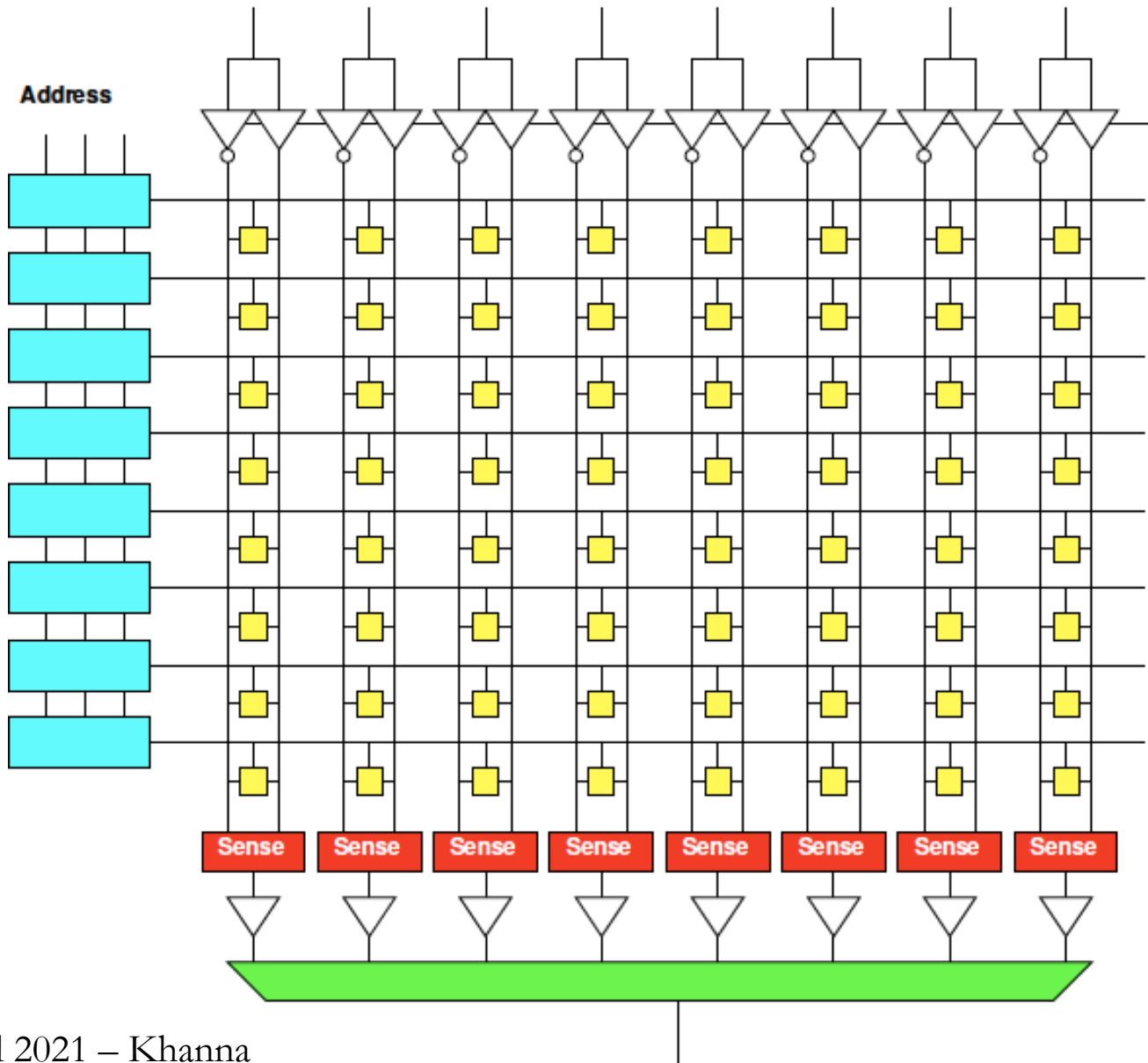


Column Drivers: Memory Bank

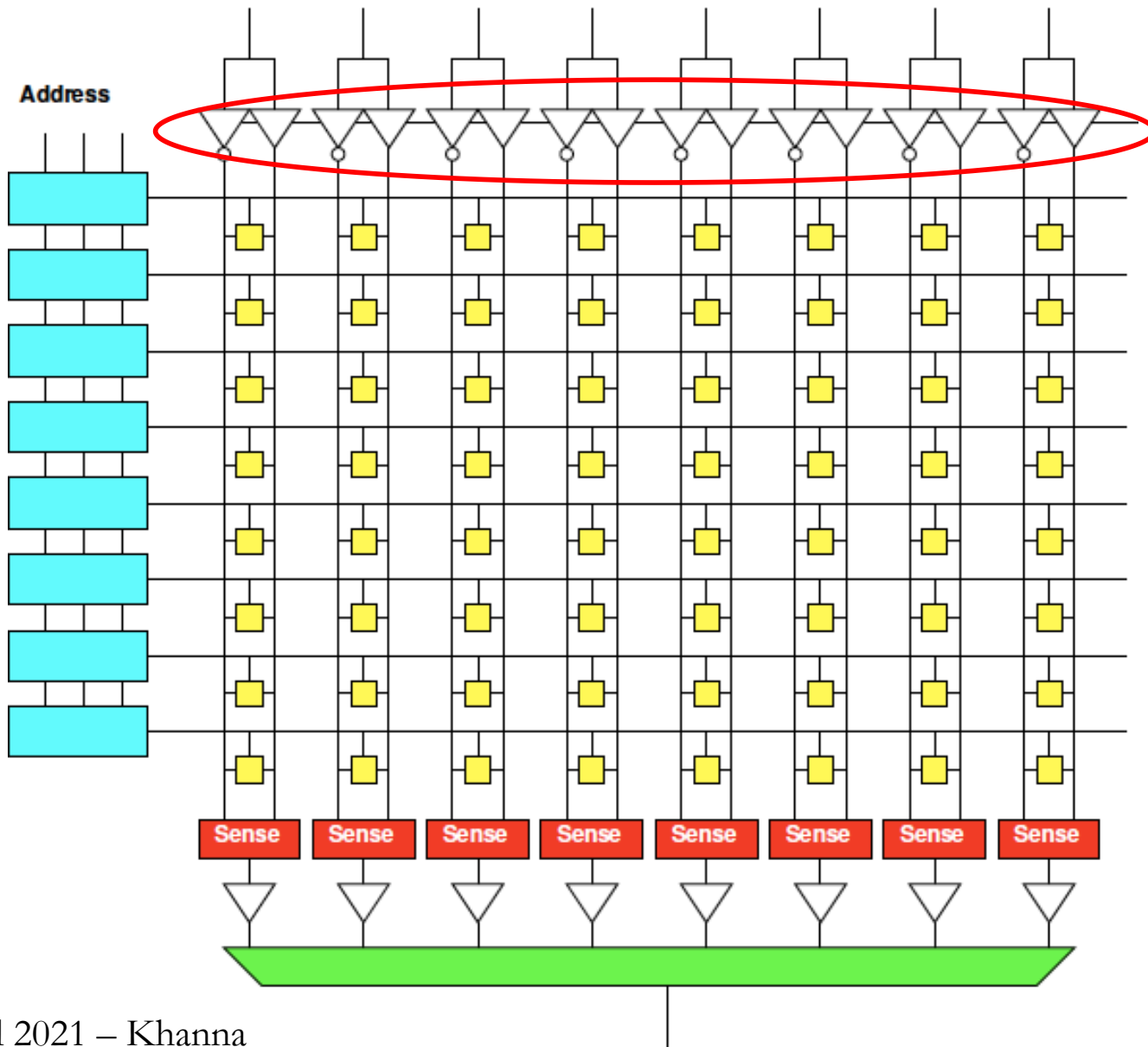

Tristate Buffer

 - ❑ Typically used for signal traveling, e.g. bus
- ❑ Ideally all devices connected to a bus should be disconnected except for active device reading or writing to bus
- ❑ Use high-impedance state to simulate disconnecting






Active-high buffer

Input	En	Ouput
0	0	Z
1	0	Z
0	1	0
1	1	1






Tristate Buffer

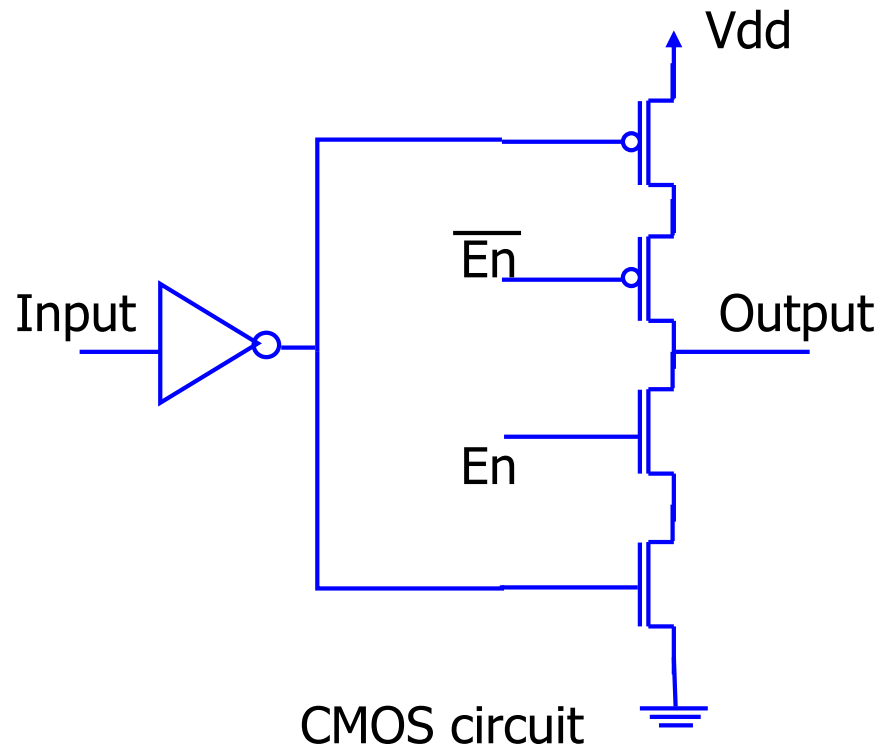  



Tristate Inverters

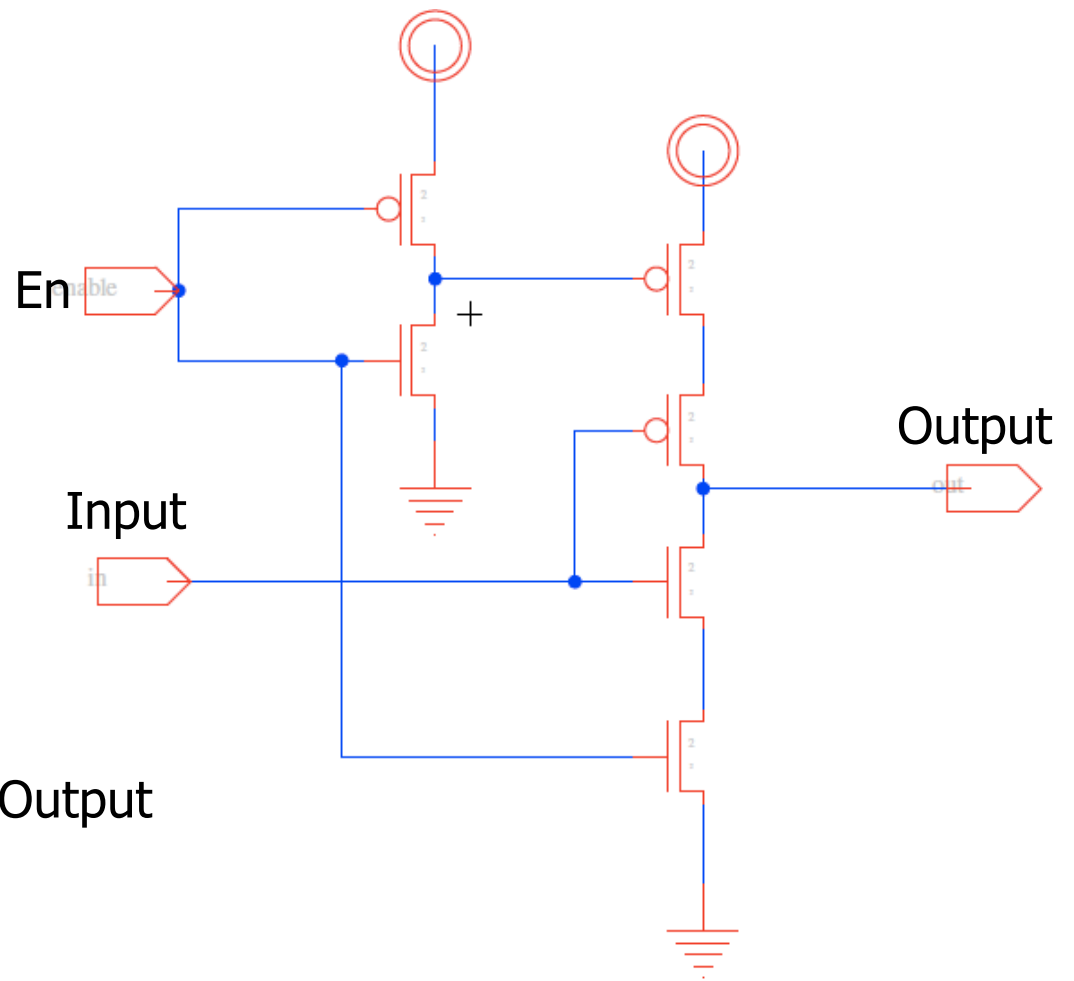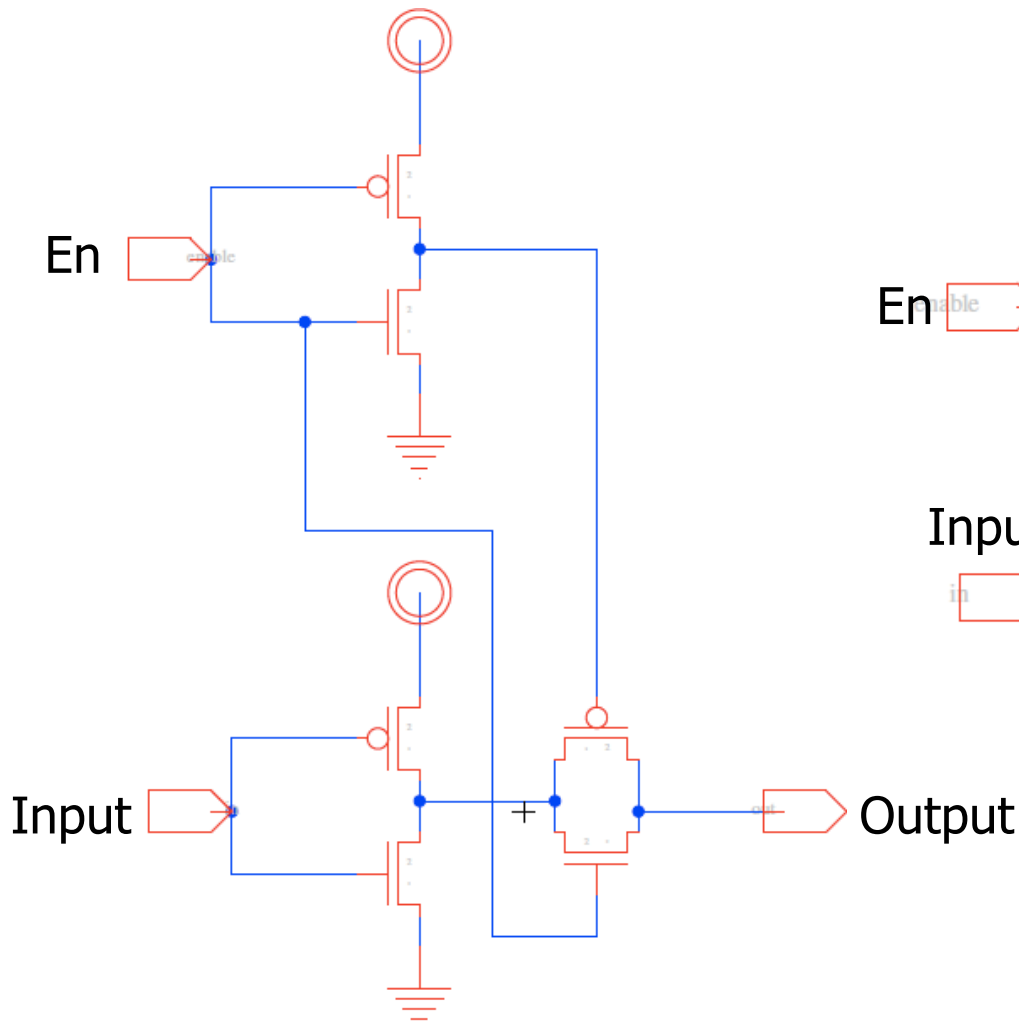 




Serial Access Memories

- ❑ Serial access memories do not use an address
 - Serial In Parallel Out (SIPO)
 - Parallel In Serial Out (PISO)
 - Shift Registers
 - Queues (FIFO, LIFO)



Serial In Parallel Out

 
- 1-bit shift register reads in serial data
 - After N steps, presents N-bit parallel output





Parallel In Serial Out

 
- ❑ Load all N bits in parallel when $\text{shift} = 0$
 - Then shift one bit out per cycle






Shift Register

 - ❑ *Shift registers* store and delay data
- ❑ Simple design: cascade of registers



Denser Shift Registers

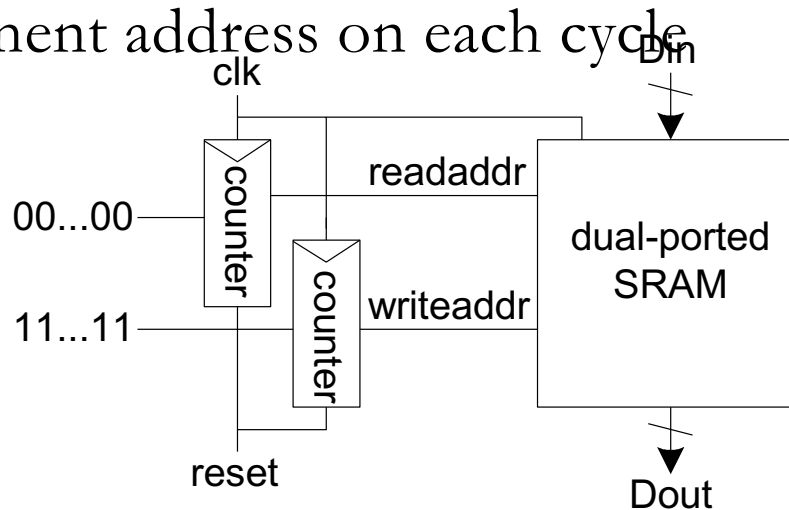
- ❑ Flip-flops aren't very area-efficient
- ❑ For large shift registers, keep data in SRAM instead
- ❑ Move read/write pointers to RAM rather than move data
 - Initialize read address to first entry, write to last
 - Increment address on each cycle





Queues

 - ❑ *Queues* allow data to be read and written at different rates.
- ❑ Read and write each use their own clock, data
- ❑ Queue indicates whether it is full or empty
- ❑ Build with SRAM and read/write counters (pointers) storing read/write address





FIFO, LIFO Queues

- *First In First Out* (FIFO)
 - Initialize read and write pointers to first element
 - Queue is EMPTY
 - On write, increment write pointer
 - If write almost catches read, Queue is FULL
 - On read, increment read pointer
 - If read catches write, Queue is EMPTY
- *Last In First Out* (LIFO)
 - Also called a *stack*
 - Use a single *stack pointer* for read and write



Idea

- ❑ Memory for compact state storage
- ❑ Share circuitry across many bits
 - Minimize area per bit → maximize density
- ❑ Aggressively use:
 - Pass transistors, Ratioing
 - Precharge, Amplifiers to keep area down



Admin

- ❑ Homework 6 due **tonight**
- ❑ Project 2 out Monday 11/15
 - Work in teams of up to two
 - Milestone due Monday 11/22
 - I will give feedback by Wednesday (night) 11/24
 - Final report due 12/3