

ESE370: Circuit-Level Modeling, Design, and Optimization for Digital Systems

Lec 28: November 15, 2021

Memory Core Part 1





Today

- Memory Array examples
- Serial Access Memories
- Memory
 - Memory core
 - 6T SRAM
- Project 2 is on this


Column Capacitance Consequence

 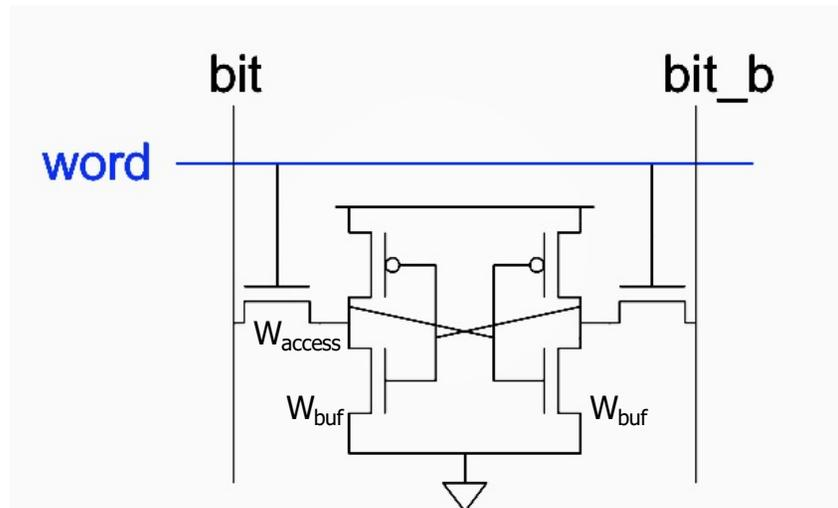- ❑ Preclass1: What is capacitance of a bitline?
 - ❑ W_{access} (pass transistor size), d rows, $\gamma = C_{\text{diff0}}/C_0$
- ❑ Preclass2: What is the delay for the cell to drive the bitline during a read?
 - ❑ W_{buf} (inverter size in cell), R_0
- ❑ **Conclude:** Can't size up cell \rightarrow driving bitline will be slow




Sense Amplifiers

 - Bitlines have many cells attached
 - Ex: 32-kbit SRAM has 128 rows x 256 cols
 - 128 cells on each bitline
- $t_{pd} \propto (C/I) \Delta V$
 - Even with shared diffusion contacts, $64C$ of diffusion capacitance (big C)
 - Discharged slowly through small transistors in each memory cell (small I)
- *Sense amplifiers* are triggered on small voltage swing (ΔV)



Clocked Sense Amp

 - ❑ Clocked sense amp saves power
- ❑ Requires sense_clk after enough bitline swing
- ❑ Isolation transistors cut off large bitline capacitance





Word Line Capacitance

□ Preclass4: What is capacitance of word line (row)?

- W_{access} – transistor width of column device
- w columns
- $\gamma = C_{\text{diff0}} / C_0$


□ Preclass5: Delay driving word line?

- W_{wldrive} Drive inverter

 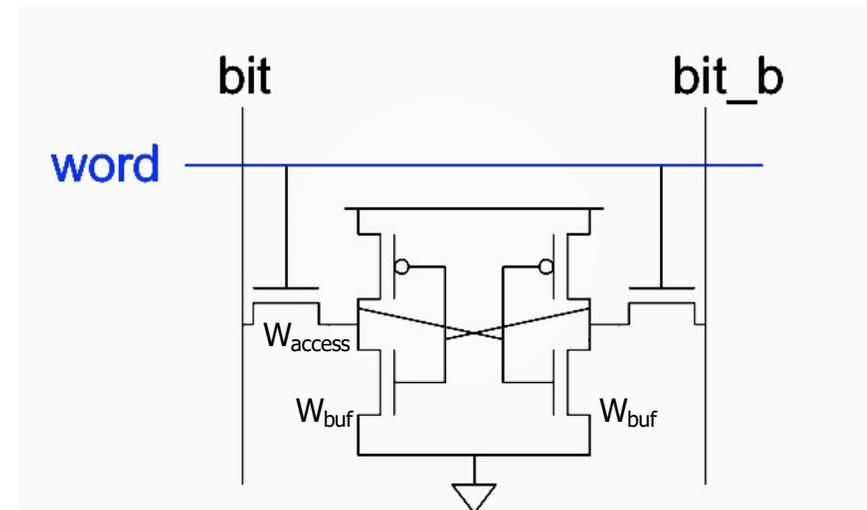




Column Drivers: Memory Bank

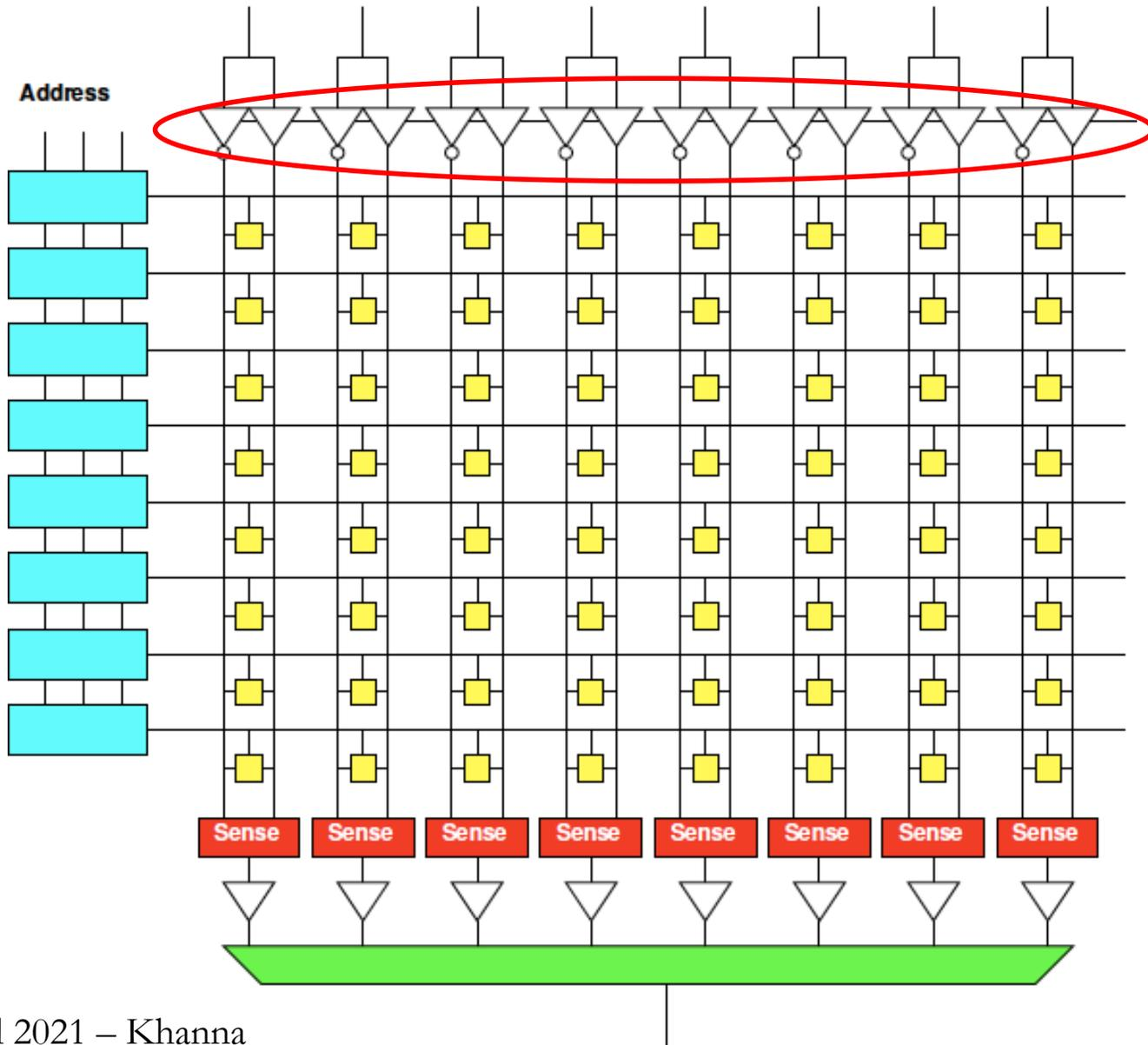

Tristate Buffer

 - ❑ Typically used for signal traveling, e.g. bus
- ❑ Ideally all devices connected to a bus should be disconnected except for active device reading or writing to bus
- ❑ Use high-impedance state to simulate disconnecting






Active-high buffer

Input	En	Ouput
0	0	Z
1	0	Z
0	1	0
1	1	1





Tristate Buffer

   




Tristate Inverters

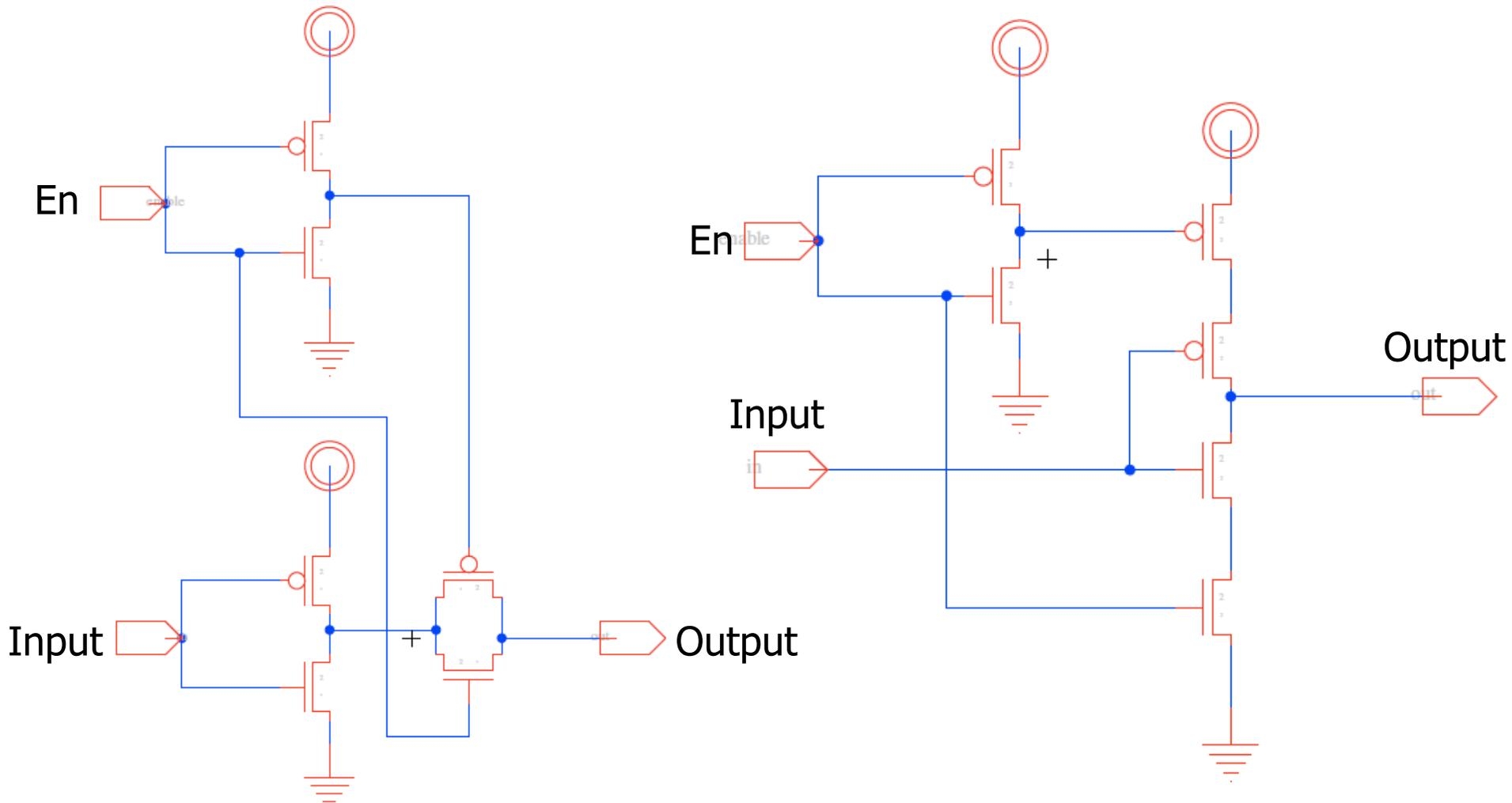 


8x4 Memory with column decoder

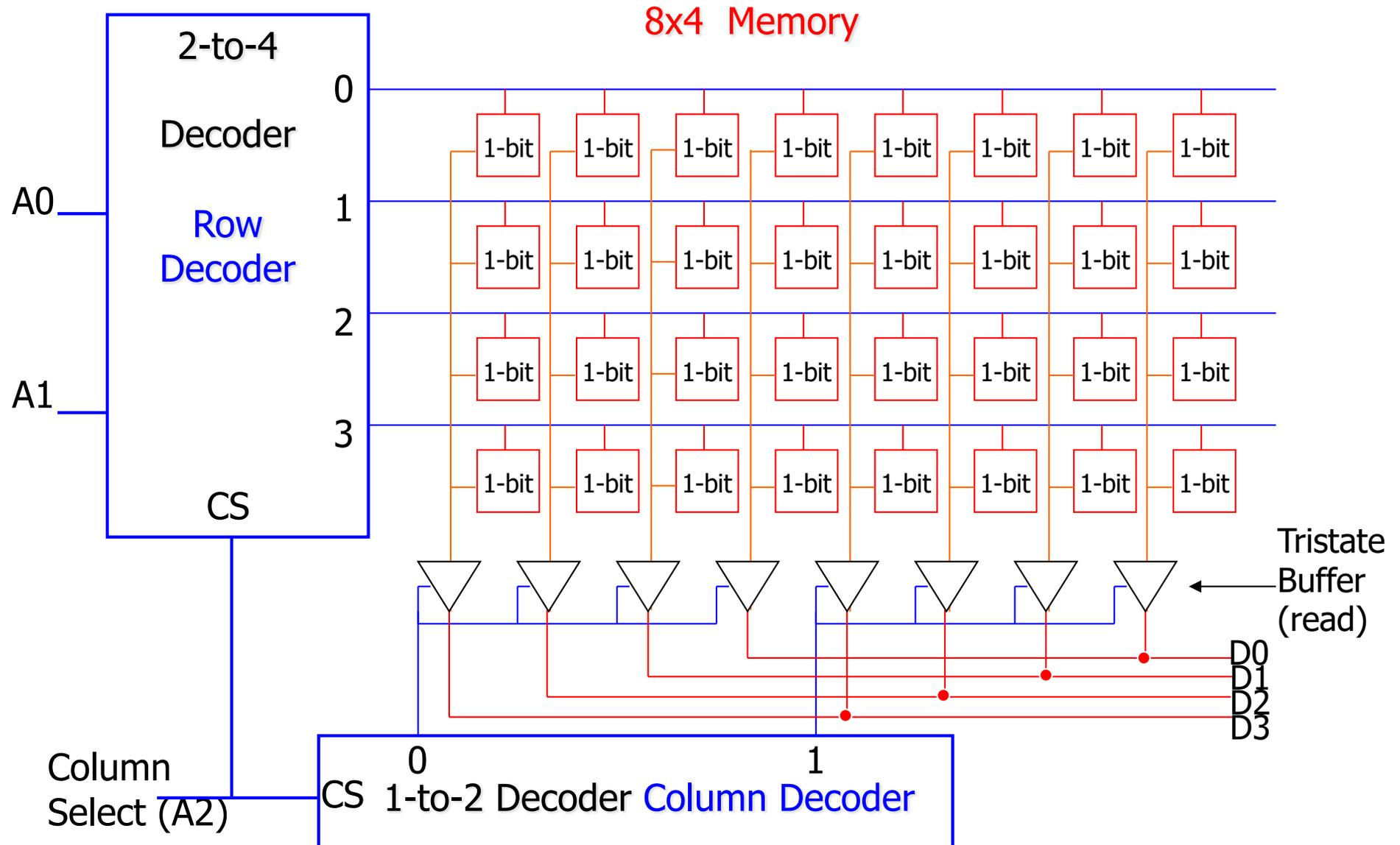





Read/Write Memory

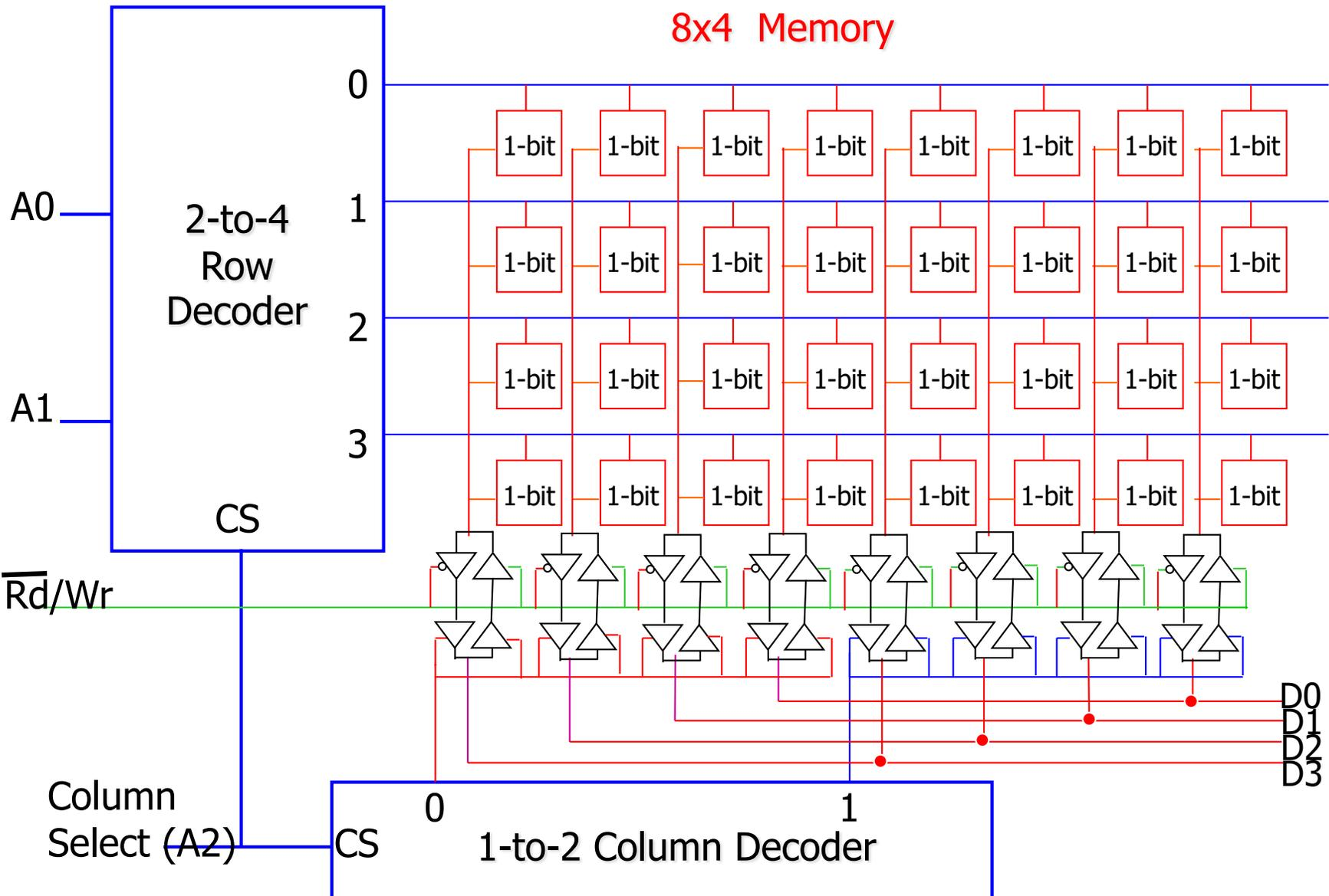

Read/Write Memory

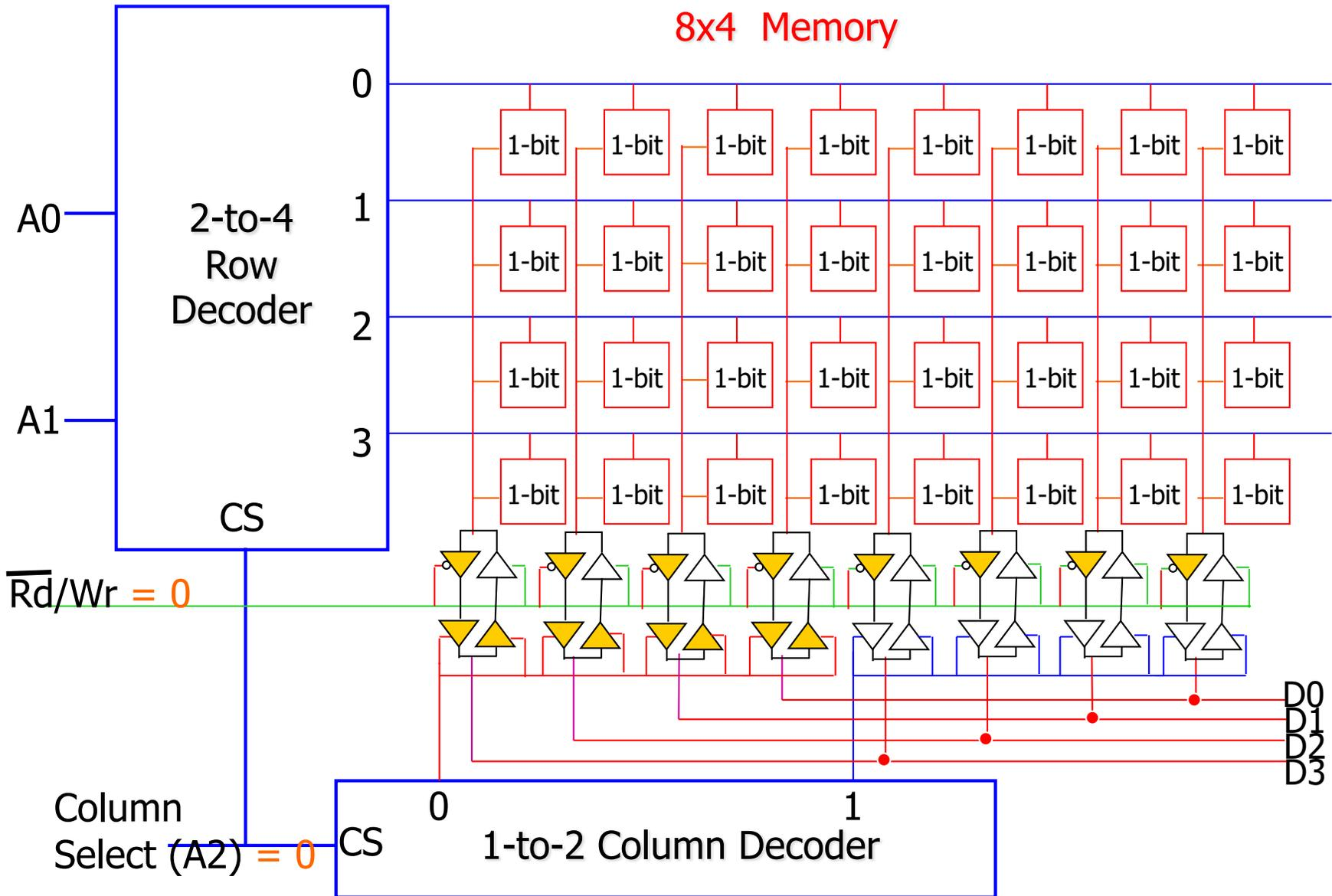

Read/Write Memory

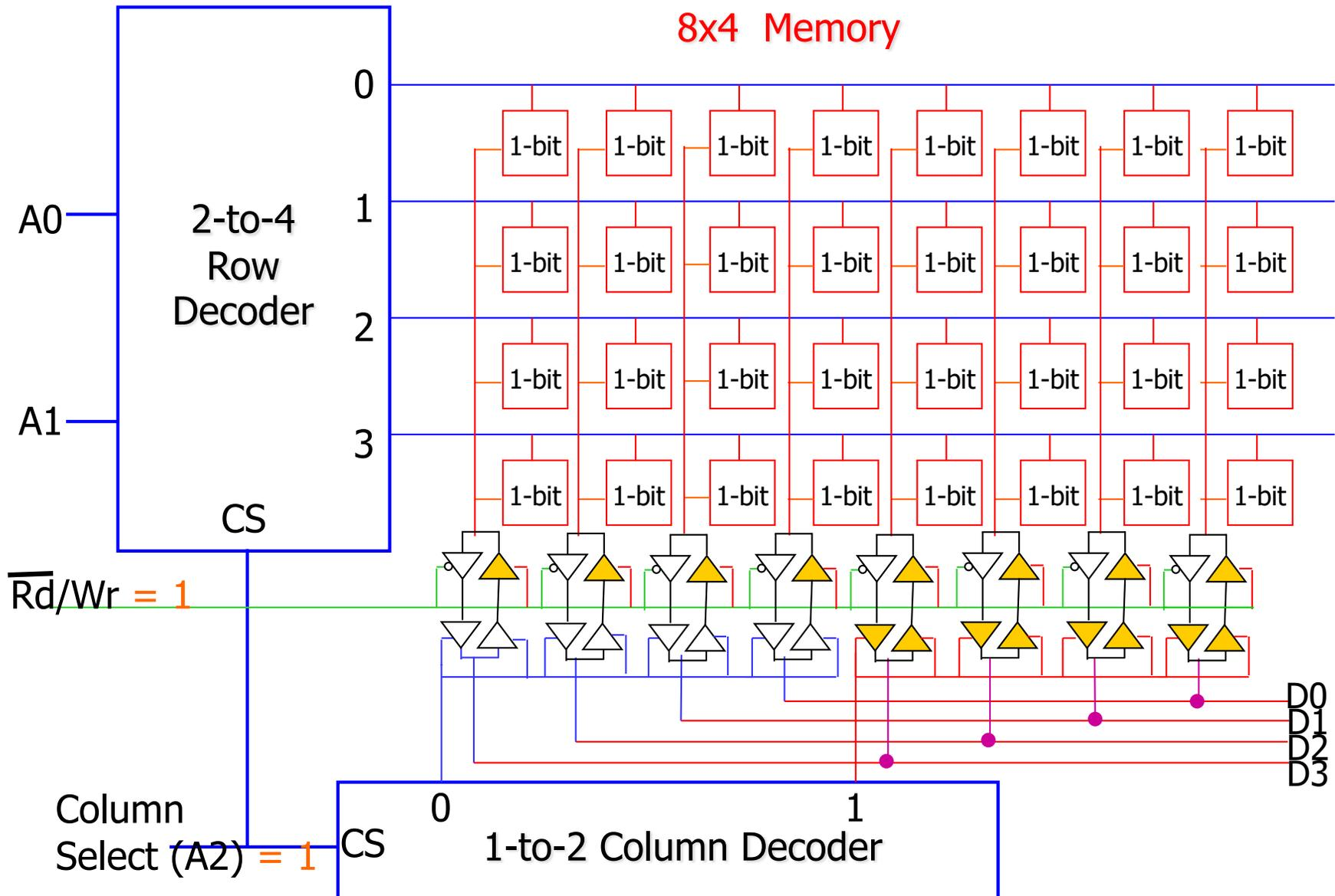




Serial Access Memories

- ❑ Serial access memories do not use an address
 - Serial In Parallel Out (SIPO)
 - Parallel In Serial Out (PISO)
 - Shift Registers
 - Queues (FIFO, LIFO)

Serial In Parallel Out

 
- 1-bit shift register reads in serial data
 - After N steps, presents N -bit parallel output





Parallel In Serial Out

 
- Load all N bits in parallel when $\text{shift} = 0$
 - Then shift one bit out per cycle






Shift Register

 - ❑ *Shift registers* store and delay data
- ❑ Simple design: cascade of registers



Denser Shift Registers

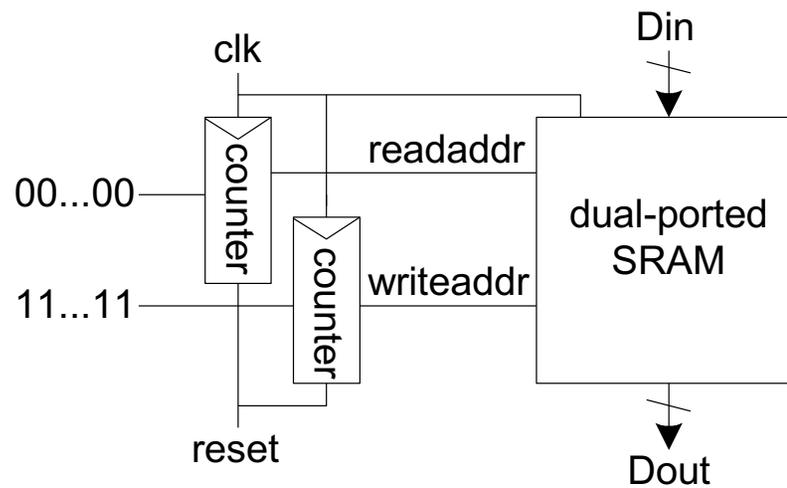
- ❑ Flip-flops aren't very area-efficient
- ❑ For large shift registers, keep data in SRAM instead
- ❑ Move read/write pointers to RAM rather than move data
 - Initialize read address to first entry, write to last
 - Increment address on each cycle





Queues

 - ❑ *Queues* allow data to be read and written at different rates.
- ❑ Read and write each use their own clock, data
- ❑ Queue indicates whether it is full or empty
- ❑ Build with SRAM and read/write counters (pointers) storing read/write address





FIFO, LIFO Queues

□ *First In First Out* (FIFO)


- Initialize read and write pointers to first element
- Queue is EMPTY
- On write, increment write pointer
- If write catches read, Queue is FULL
- On read, increment read pointer
- If read catches write, Queue is EMPTY

□ *Last In First Out* (LIFO)

- Also called a *stack*
- Use a single *stack pointer* for read and write


Array-Structured Memory Architecture

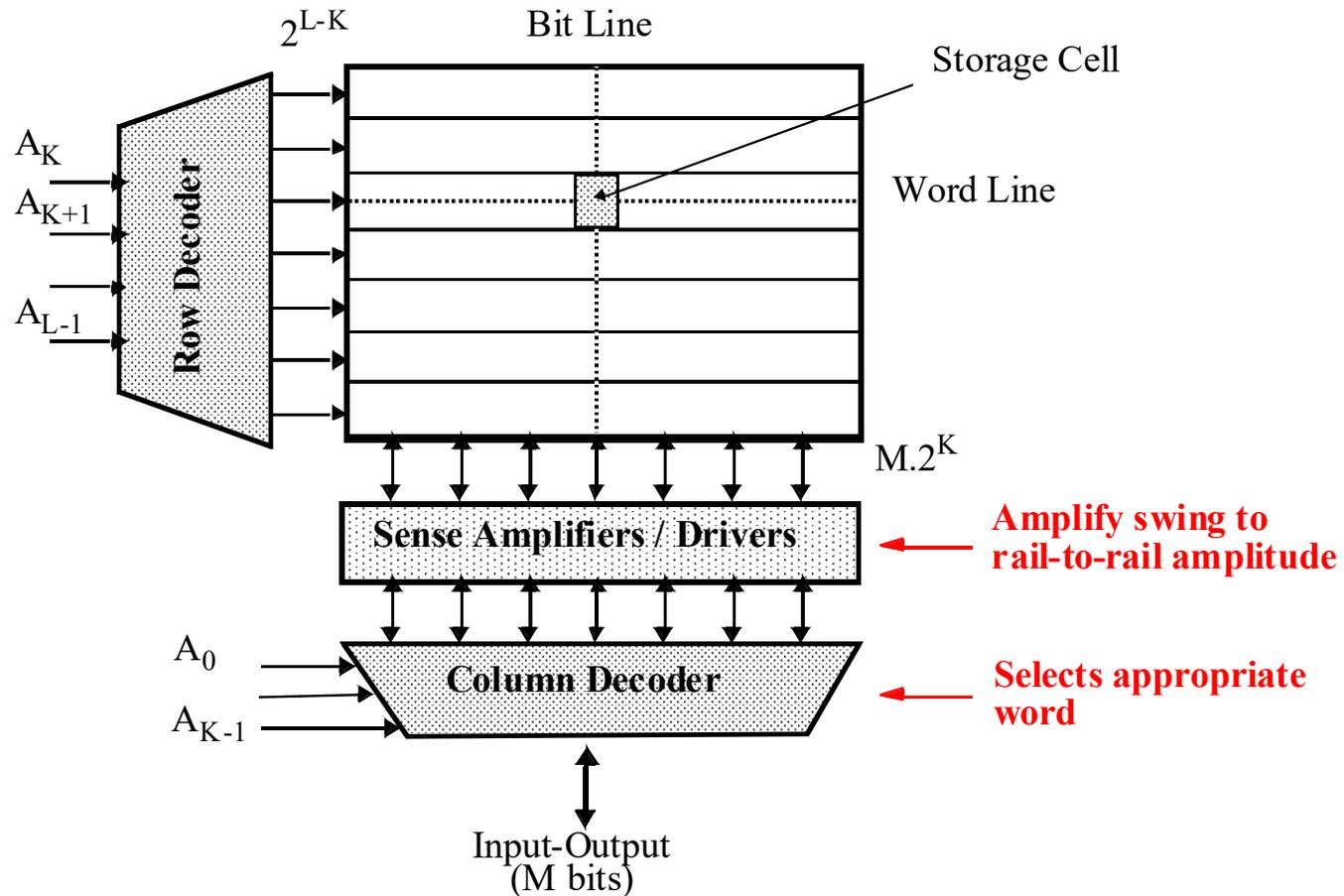Problem: ASPECT RATIO or HEIGHT \gg WIDTH




6T SRAM Cell

 
- ❑ Cell size accounts for most of array size
 - Reduce cell size at expense of complexity
- ❑ 6T SRAM Cell
 - Used in most commercial chips
 - Data stored in cross-coupled inverters
- ❑ Read:
 - Precharge BL, BL'
 - Raise WL
- ❑ Write:
 - Drive data onto BL, BL'
 - Raise WL



6-transistor CMOS SRAM Cell

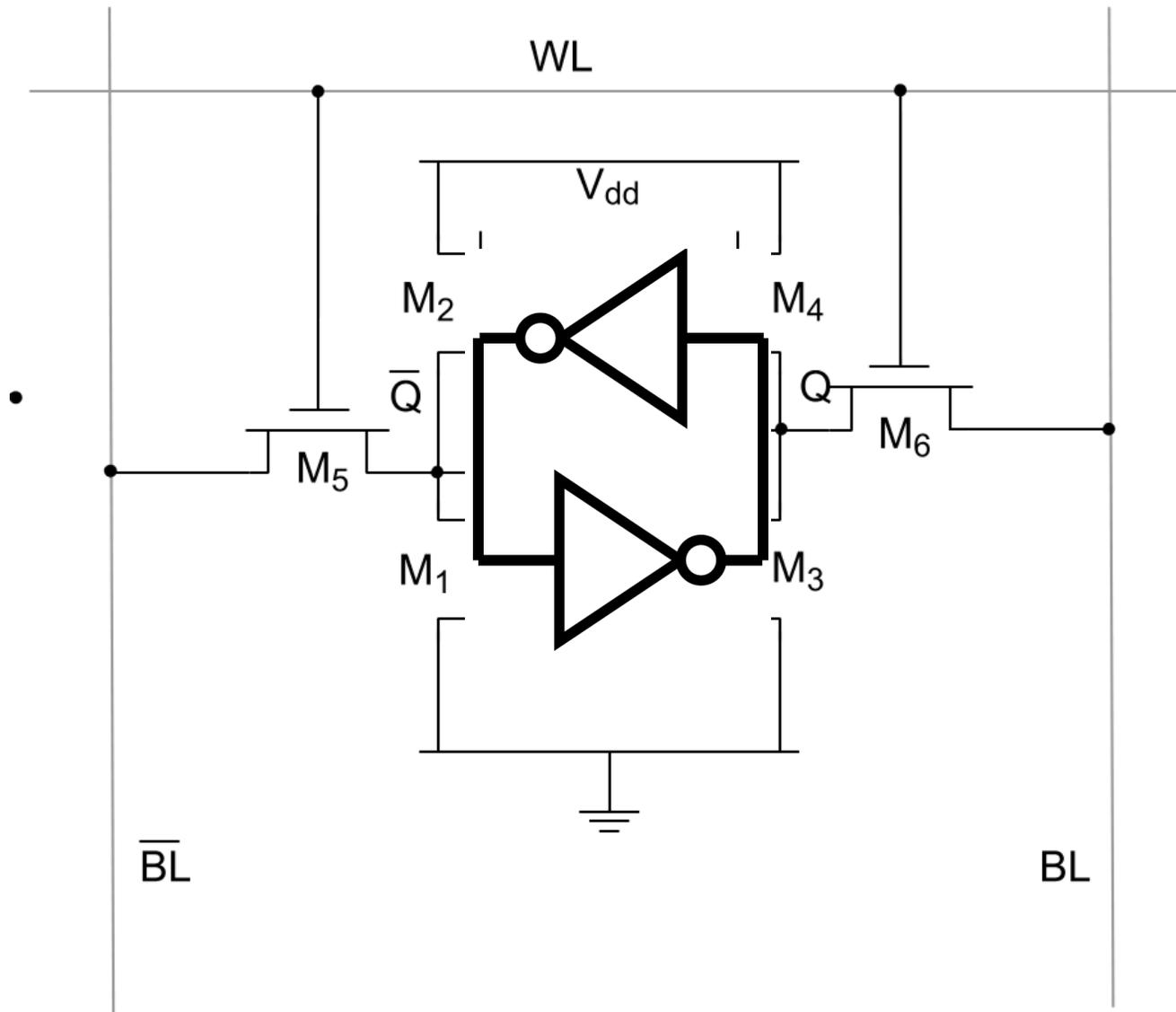


CMOS SRAM Analysis (Read) (preclass 1)

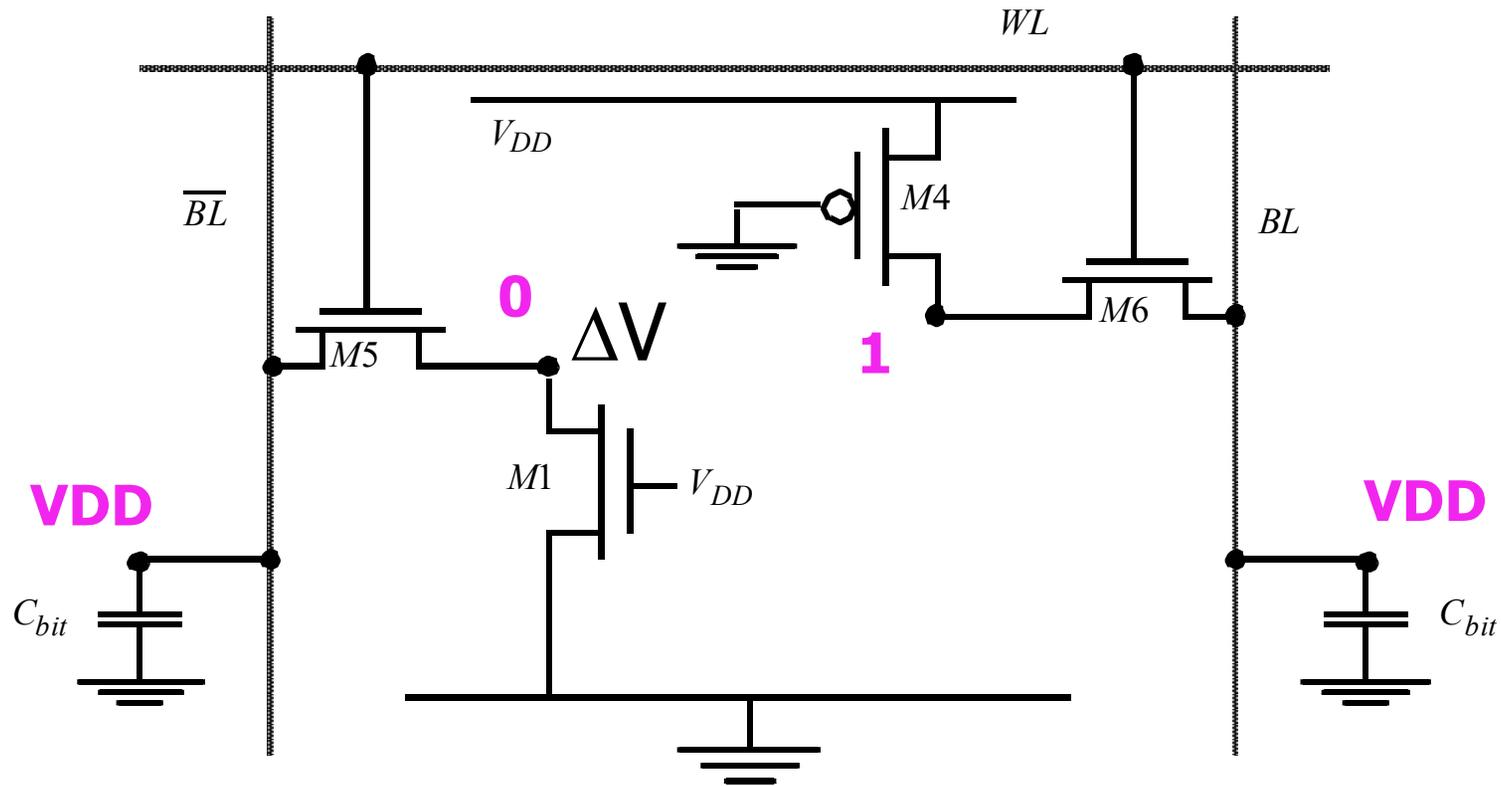


Which two transistors are discharging \overline{BL} to Gnd?
 What regions of operation are the transistors in?
 Write the KCL equation for the two transistors

CMOS SRAM Analysis (Read)

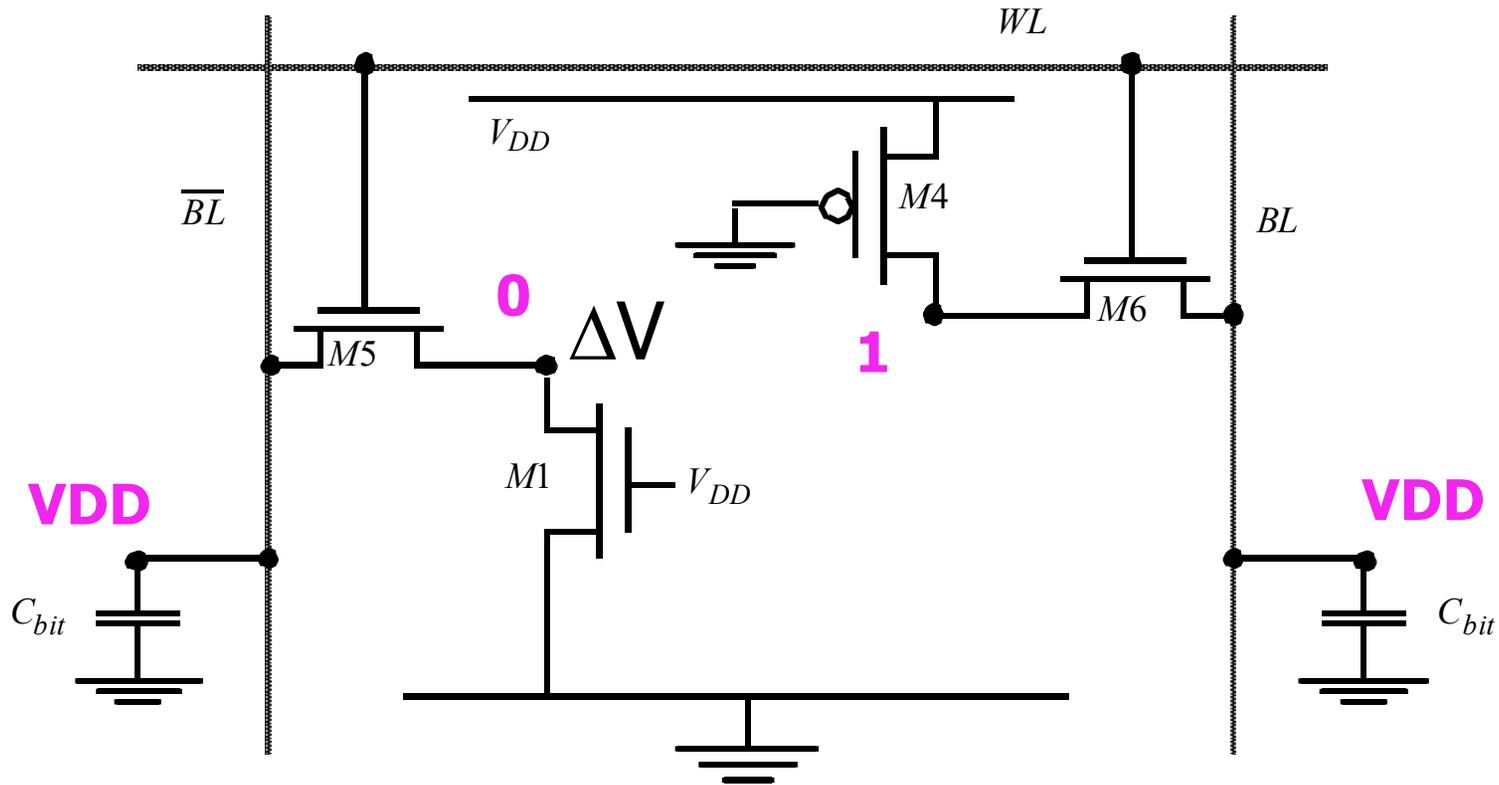

$$\frac{k_{n,M1}}{k_{n,M5}} = \frac{\left(\frac{W}{L}\right)_1}{\left(\frac{W}{L}\right)_5} = \frac{(V_{DD} - \Delta V - V_{Tn})^2}{(V_{DD} - V_{Tn})\Delta V - \frac{\Delta V^2}{2}}$$


CMOS SRAM Analysis (Read)

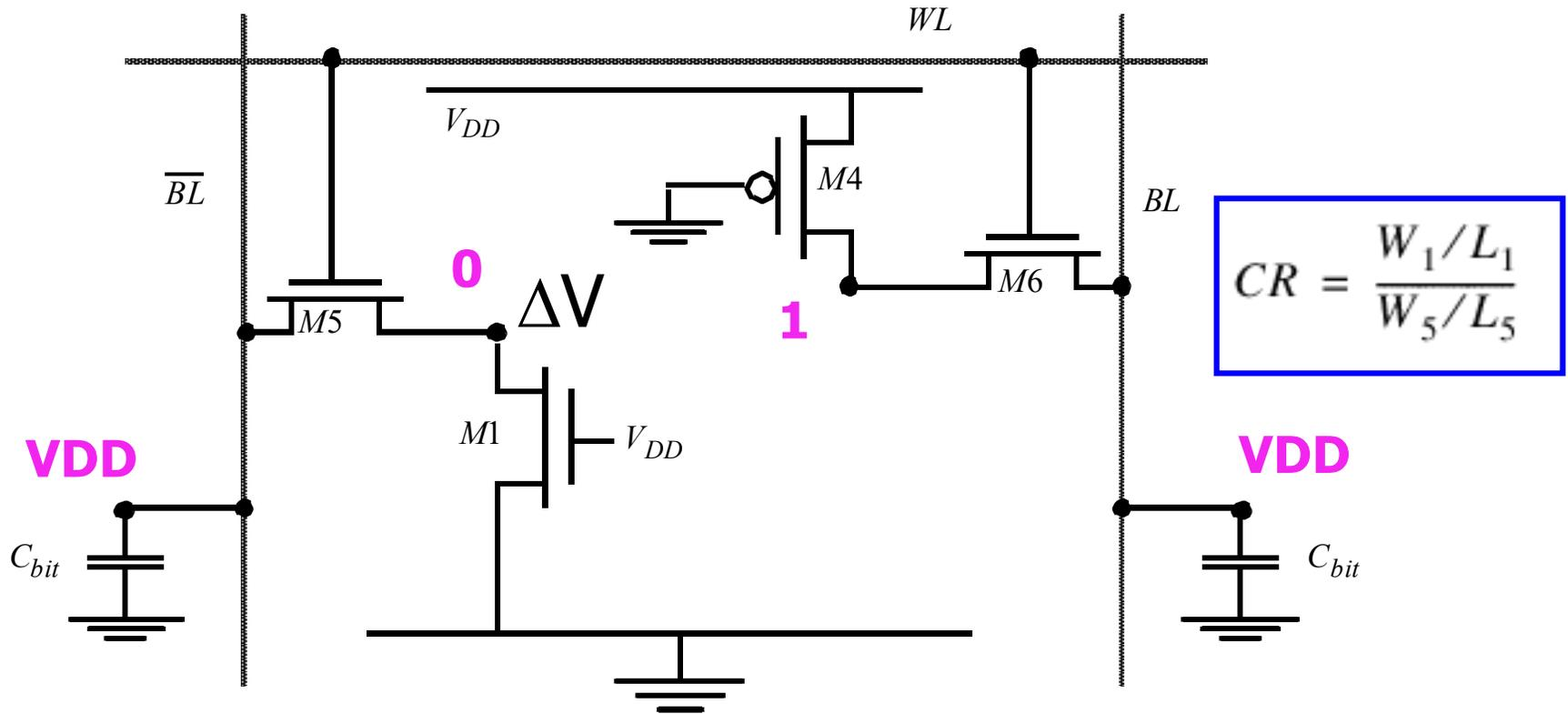

$$\frac{k_{n,M1}}{k_{n,M5}} = \frac{\left(\frac{W}{L}\right)_1}{\left(\frac{W}{L}\right)_5} = \frac{(V_{DD} - \Delta V - V_{Tn})^2}{(V_{DD} - V_{Tn})\Delta V - \frac{\Delta V^2}{2}} \quad \xrightarrow{\Delta V = V_{Tn}} \quad \frac{\left(\frac{W}{L}\right)_1}{\left(\frac{W}{L}\right)_5} = \frac{(V_{DD} - 2V_{Tn})^2}{(V_{DD} - 1.5V_{Tn})V_{Tn}}$$





CMOS SRAM Analysis (Read)

 

$$CR = \frac{W_1/L_1}{W_5/L_5}$$

SRAM Read

 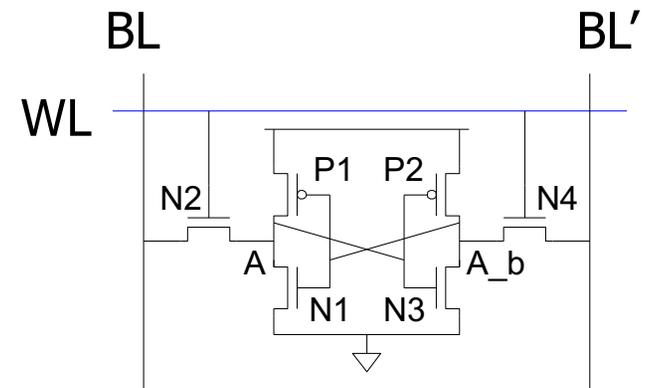- ❑ Precharge both bitlines high
- ❑ Then turn on wordline, WL
- ❑ One of the two bitlines will be pulled down by the cell
- ❑ Ex: $A = 0, A_b = 1$
 - BL discharges, BL' stays high
 - But A bumps up slightly
- ❑ *Read stability*
 - A must not flip
 - $N1 > N2$




6-transistor CMOS SRAM Cell (preclass 2)


Assume 1 is stored
($Q=1$)

Write Operation:

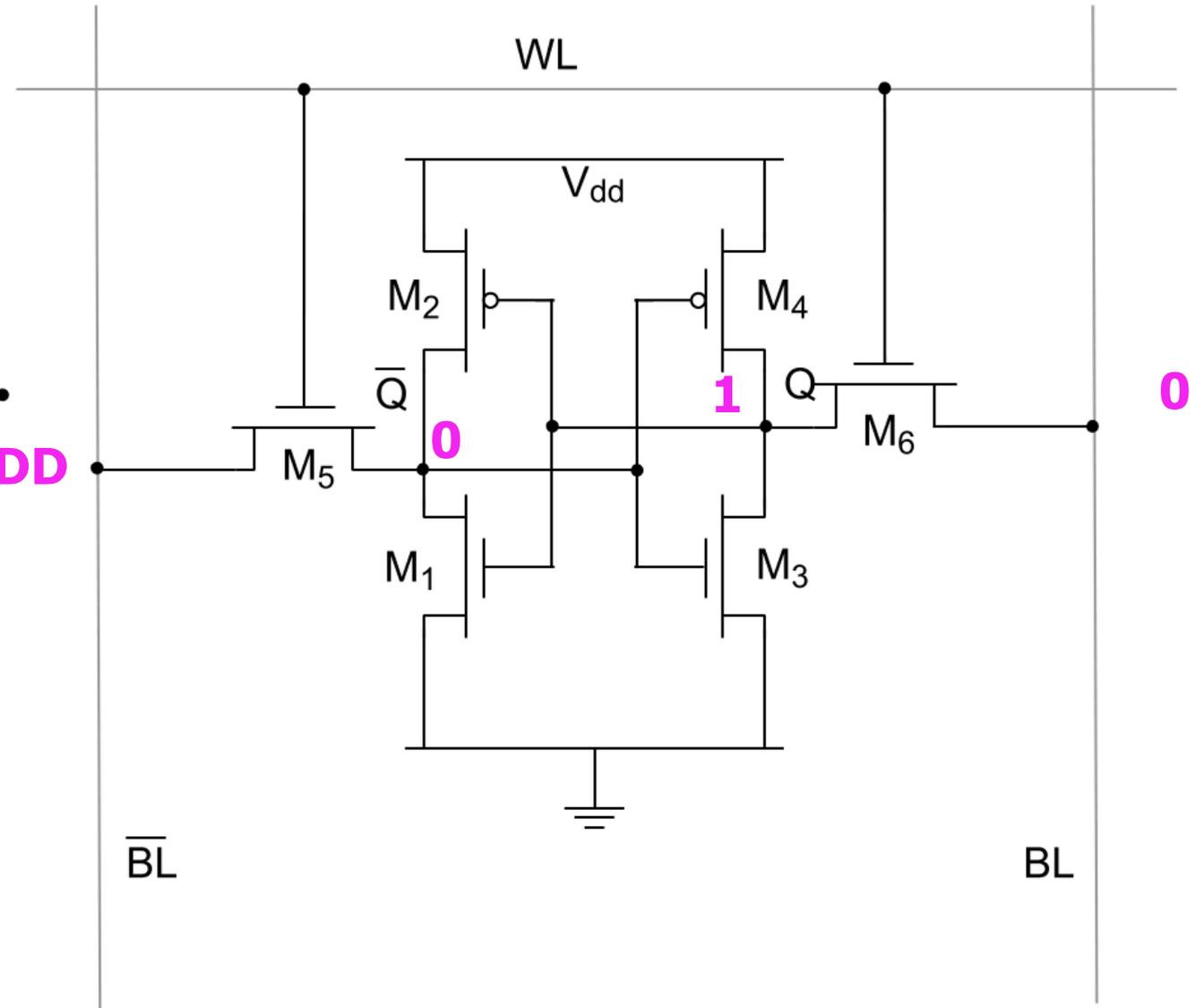- Want to write a 0
- First drive bitlines with input data
- Then wordline goes high (V_{dd})
 - Still driving bitlines




CMOS SRAM Analysis (Write)

 


$$k_{p,M4} (V_{DD} - |V_{Tp}|)^2 = k_{n,M6} \left((V_{DD} - V_{Tn})V_Q - \frac{V_Q^2}{2} \right)$$

CMOS SRAM Analysis (Write)

 

$$\frac{k_{p,M4}}{k_{n,M6}} = \frac{(V_{DD} - V_{Tn})V_Q - \frac{V_Q^2}{2}}{(V_{DD} - |V_{Tp}|)^2}$$

CMOS SRAM Analysis (Write)

 

$$PR = \frac{W_4/L_4}{W_6/L_6}$$


$$\frac{k_{p,M4}}{k_{n,M6}} = \frac{(V_{DD} - V_{Tn})V_Q - \frac{V_Q^2}{2}}{(V_{DD} - |V_{Tp}|)^2}$$

$$V_Q = V_{Tn}$$

$$\frac{k_{p,M4}}{k_{n,M6}} = \frac{(V_{DD} - V_{Tn})V_{Tn} - \frac{V_{Tn}^2}{2}}{(V_{DD} - |V_{Tp}|)^2}$$





CMOS SRAM Analysis (Write)

 

$$PR = \frac{W_4/L_4}{W_6/L_6}$$


SRAM Write

 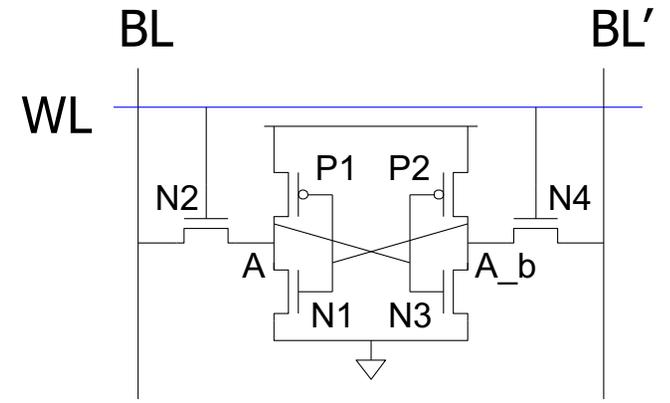- Drive one bitline high, the other low
 - Depending on write data
- Then turn on wordline, WL
- Bitlines overpower cell with new value
- Ex: $A = 0$, $A_b = 1$, $BL = 1$, $BL' = 0$
 - Force A_b low, then A charges high
- *Writability*
 - Must overpower feedback inverter
 - $N4 \gg P2$




SRAM Column Example

read

 


write

 



5T SRAM

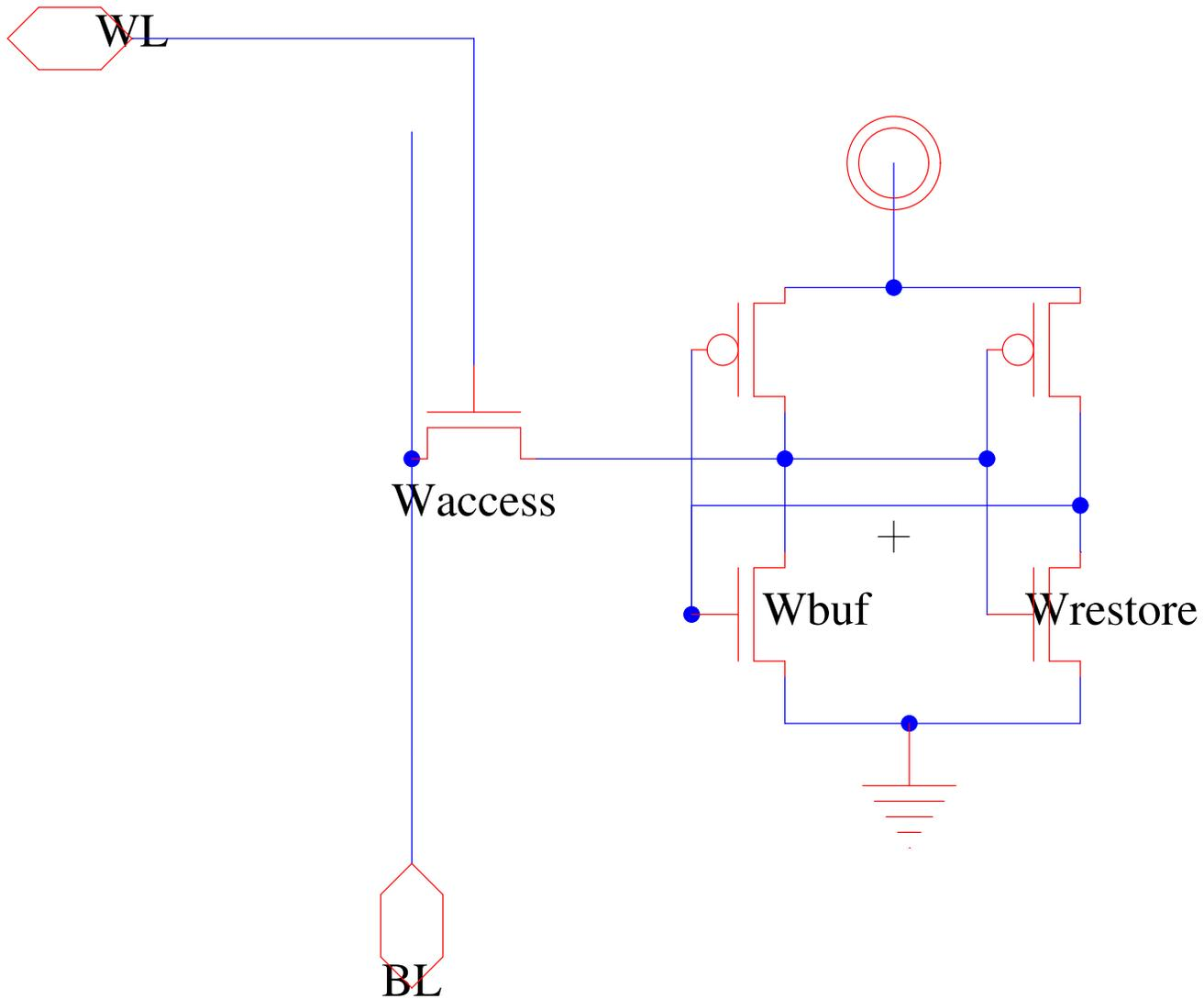



Idea

- 6T SRAM
 - Robust cell when sized carefully
- 5T SRAM
 - More sensitive to sizing than 6T SRAM
 - More next time...



Admin

- Project 2 out - **START NOW!**
 - Work in teams up to 2
 - Milestone due Monday 11/22
 - I will give feedback by Wed (night) 11/24
 - Final report due 12/3