

# ESE370: Circuit-Level Modeling, Design, and Optimization for Digital Systems

---

Lec 29: November 17, 2021  
RAM Core Part 2





# Today

---

- ❑ 6T SRAM
- ❑ 5T SRAM
- ❑ Multiported SRAM
- ❑ DRAM
  
# SRAM Read

- ❑ Precharge both bitlines high
- ❑ Then turn on wordline, WL
- ❑ One of the two bitlines will be pulled down by the cell
- ❑ Ex:  $A = 0, A\_b = 1$ 
  - BL discharges, BL' stays high
  - But A bumps up slightly
- ❑ *Read stability*
  - A must not flip
  - $N1 > N2$




# 6-transistor CMOS SRAM Cell

Assume 1 is stored  
( $Q=1$ )


Write Operation:

 - Want to write a 0 **VDD**
- First drive bitlines with input data
- Then wordline goes high ( $V_{dd}$ )
  - Still driving bitlines






# CMOS SRAM Analysis (Write)

 


$$k_{p,M4} (V_{DD} - |V_{Tp}|)^2 = k_{n,M6} \left( (V_{DD} - V_{Tn})V_Q - \frac{V_Q^2}{2} \right)$$

# CMOS SRAM Analysis (Write)

 

$$\frac{k_{p,M4}}{k_{n,M6}} = \frac{(V_{DD} - V_{Tn})V_Q - \frac{V_Q^2}{2}}{(V_{DD} - |V_{Tp}|)^2}$$

# CMOS SRAM Analysis (Write)

 


$$PR = \frac{W_4/L_4}{W_6/L_6}$$

$$\frac{k_{p,M4}}{k_{n,M6}} = \frac{(V_{DD} - V_{Tn})V_Q - \frac{V_Q^2}{2}}{(V_{DD} - |V_{Tp}|)^2} \quad \xrightarrow{V_Q = V_{Tn}} \quad \frac{k_{p,M4}}{k_{n,M6}} = \frac{(V_{DD} - V_{Tn})V_{Tn} - \frac{V_{Tn}^2}{2}}{(V_{DD} - |V_{Tp}|)^2}$$




# CMOS SRAM Analysis (Write)

 

$$PR = \frac{W_4/L_4}{W_6/L_6}$$

 
# SRAM Write

- Drive one bitline high, the other low
  - Depending on write data
- Then turn on wordline, WL
- Bitlines overpower cell with new value
- Ex:  $A = 0$ ,  $A\_b = 1$ ,  $BL = 1$ ,  $BL' = 0$ 
  - Force  $A\_b$  low, then  $A$  charges high
- *Writability*
  - Must overpower feedback inverter
  - $N4 \gg P2$




# SRAM Column Example


read

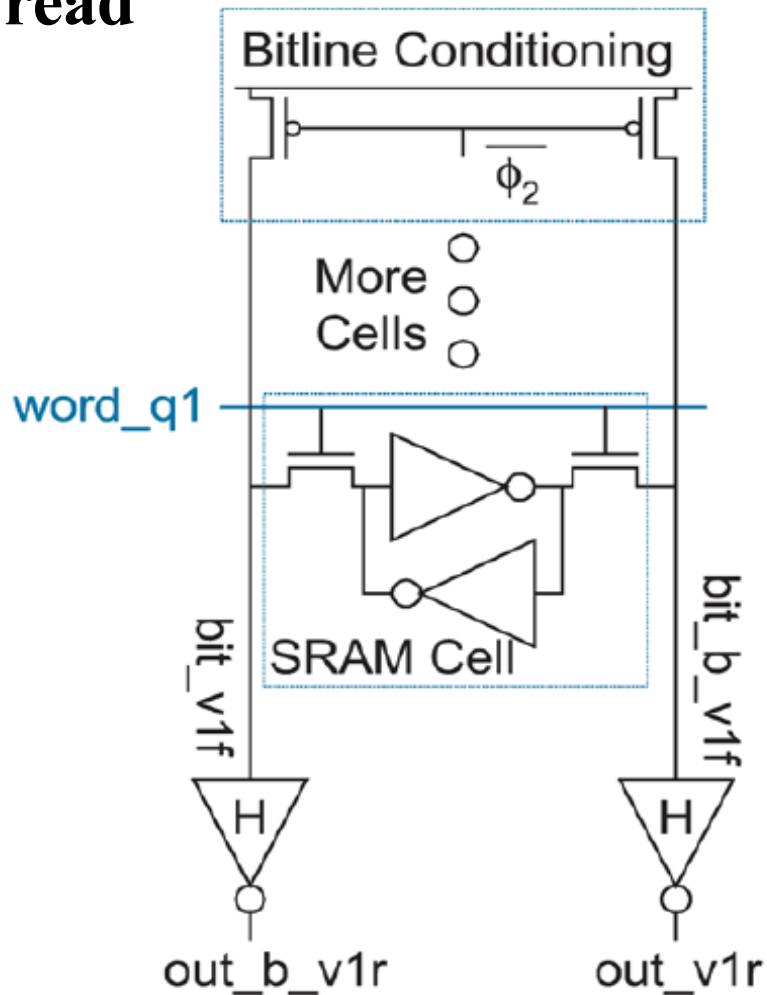

write

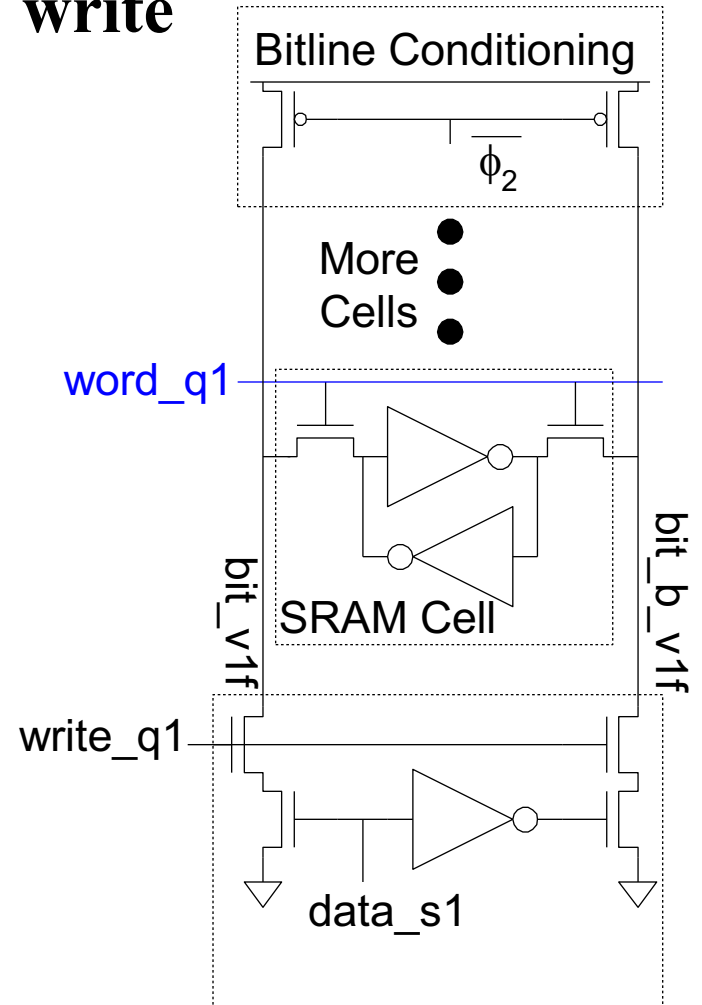


# 5T SRAM

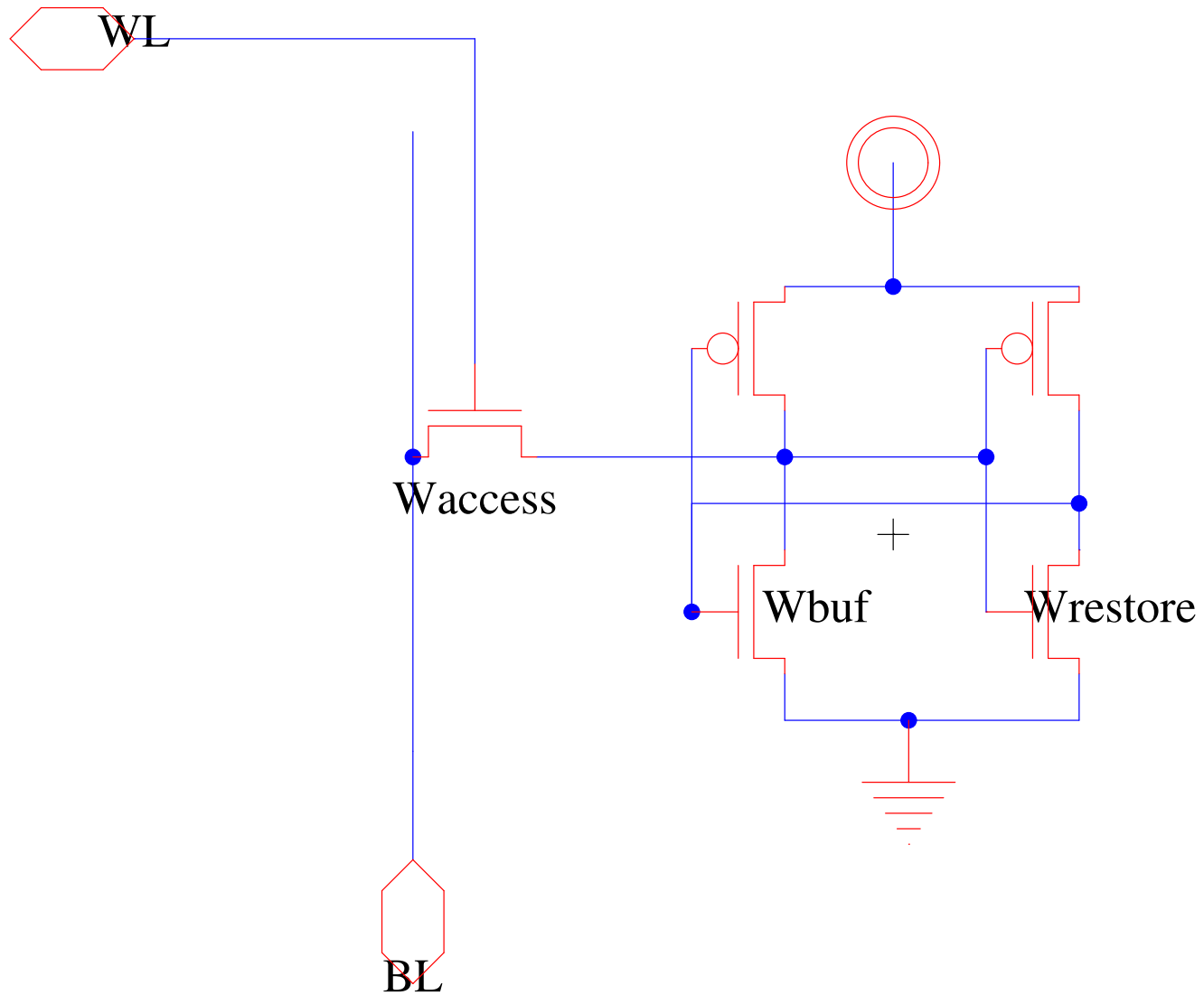

# Charge Sharing (Preclass 1)

Initially

- A @ 1V
- B @ 0V
- $Q_A = 1V * C1 = C1$

 


# Charge Sharing (Preclass 1)

Initially

- A @ 1V
- B @ 0V
- $Q_A = 1V * C1 = C1$

Close switch

 - $Q_{tot} = V_{final} * (C1 + C0)$
- Charge conservation
  - $Q_A = Q_{tot}$
- $C1 = V_{final} * (C1 + C0)$




$$V_{final} = \frac{C1}{C1 + C0}$$
 
# Consider (preclass 2)


□ Read: What happens to voltage at A when WL turns from 0 → 1?

- Assume  $W_{\text{access}}$  large
- $W_{\text{access}} \gg W_{\text{pu}} = 1$
- BL initially 0


 
# Voltage After enable Word Line


- $Q_{BL} = 0$
- $Q_A = (1V)(\gamma 2C_0 + \gamma W_{\text{access}} C_0)$





 
# Voltage After enable Word Line


- $Q_{BL} = 0$
- $Q_A = (1V)(\gamma 2C_0 + \gamma W_{\text{access}} C_0)$
- $100\text{fF} = C_{BL} \gg C_A = (\gamma(2 + W_{\text{access}})C_0)$
- After enable  $W_{\text{access}}$  ( $W_{\text{access}}$  large)
  - Total charge  $Q_{BL} + Q_A$  unchanged
    - Charge conservation
  - Distributed over larger capacitance  $\sim C_{BL}$
  - $V_A = V_{BL} \sim C_A / C_{BL}$



# Simulation: $W_{\text{access}} = 100$

 


## Transient Response

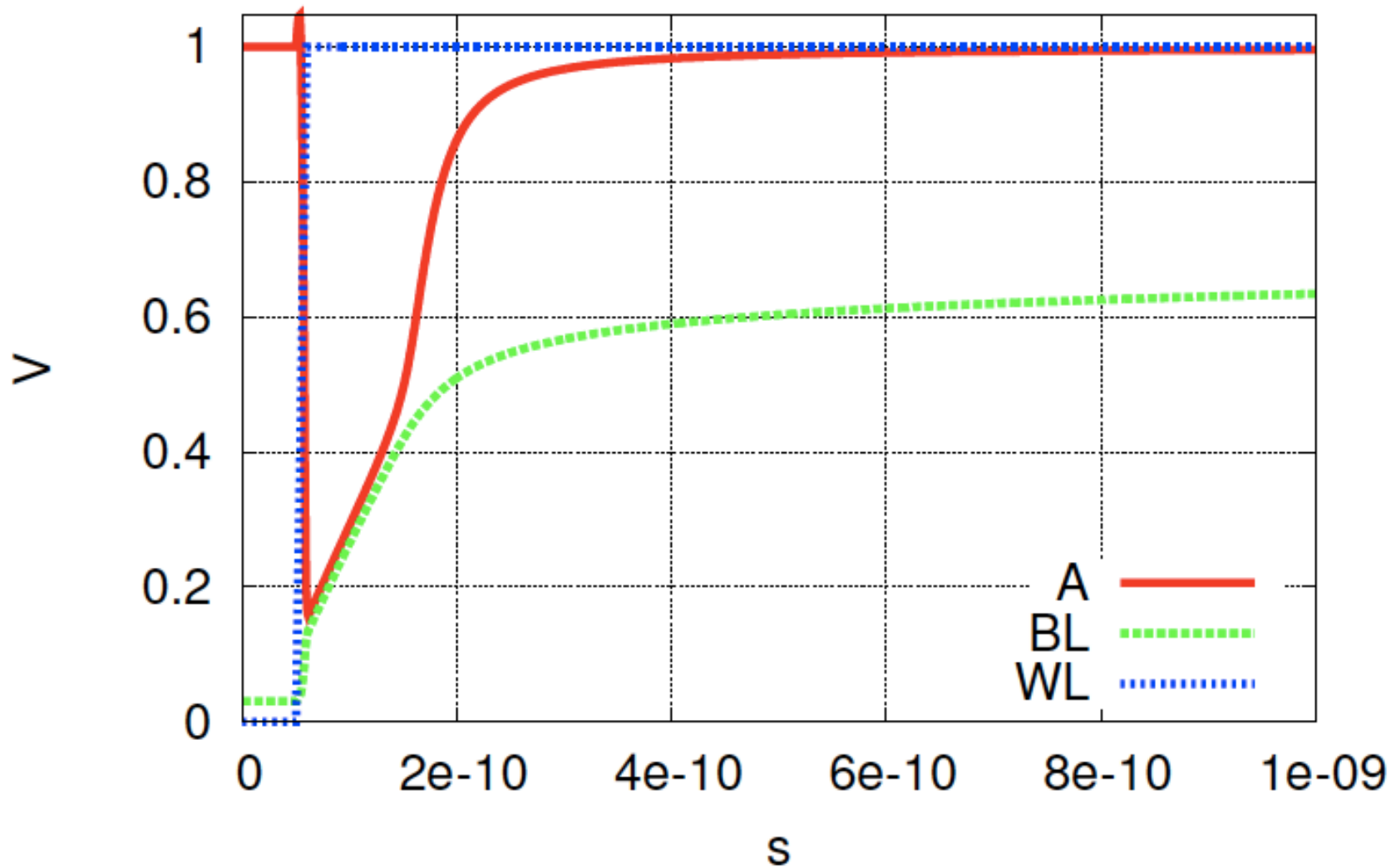

 
# Consider (5T SRAM) (preclass 3)

□ What happens to voltage at A when WL turns from 0 → 1?


- Assume  $W_{\text{access}}$  large
- A initially 1
- BL initially 0



# Simulation $W_{\text{access}} = 20$

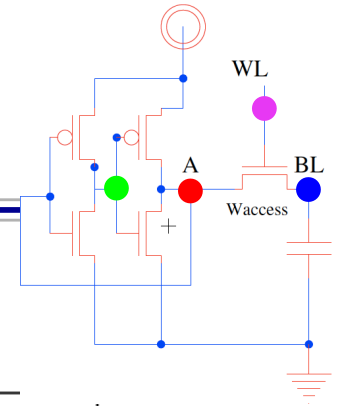


## Transient Response

 


S

# Simulation $W_{\text{access}}=4$

 


## Transient Response

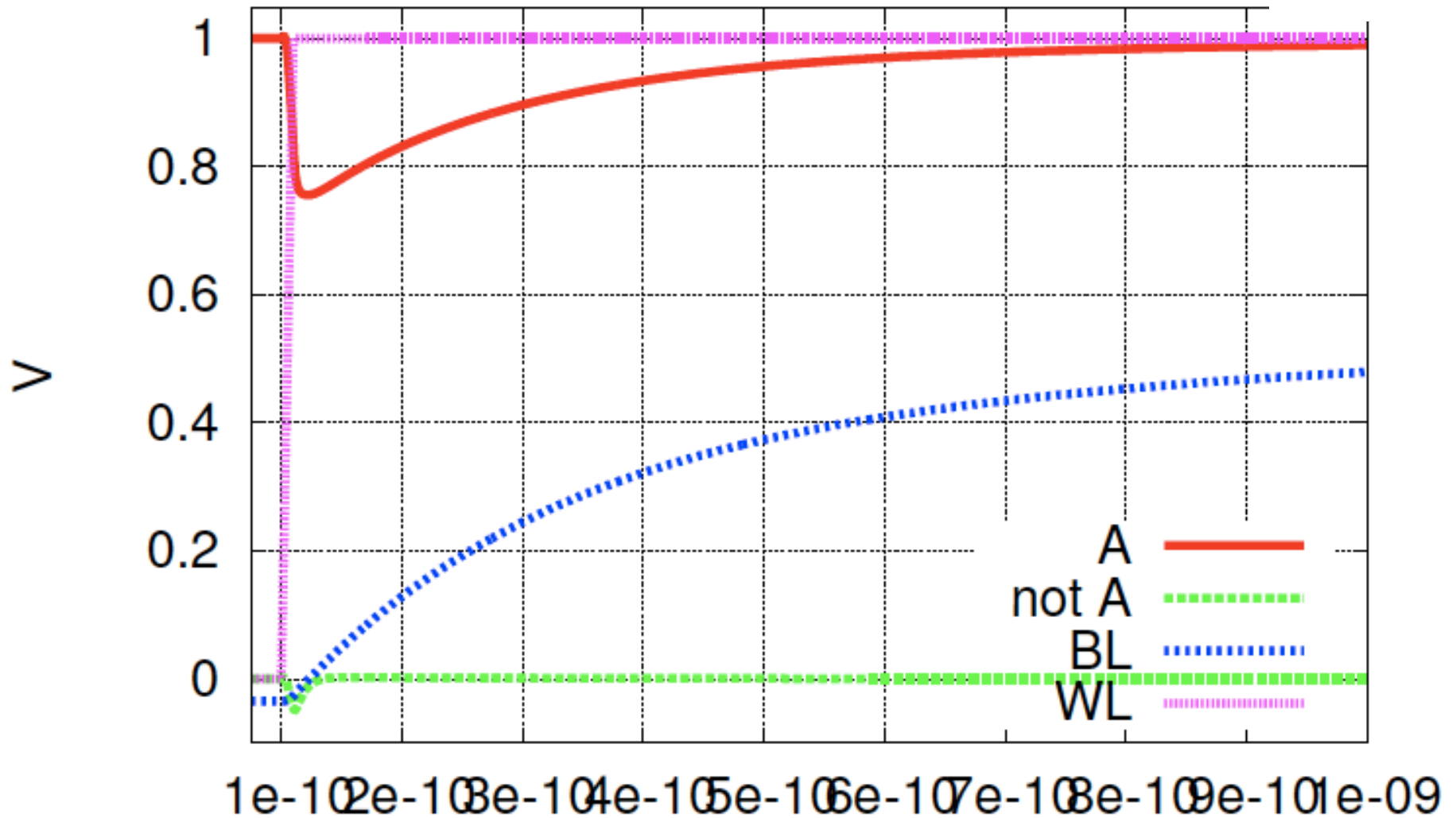

 
# Charge Sharing

- ❑ **Conclude:** charge sharing can lead to read upset
  - Charge redistribution/sharing adequate to flip state of bit





$$W_{\text{access}}=20$$

 

$$W_{\text{access}}=4$$
 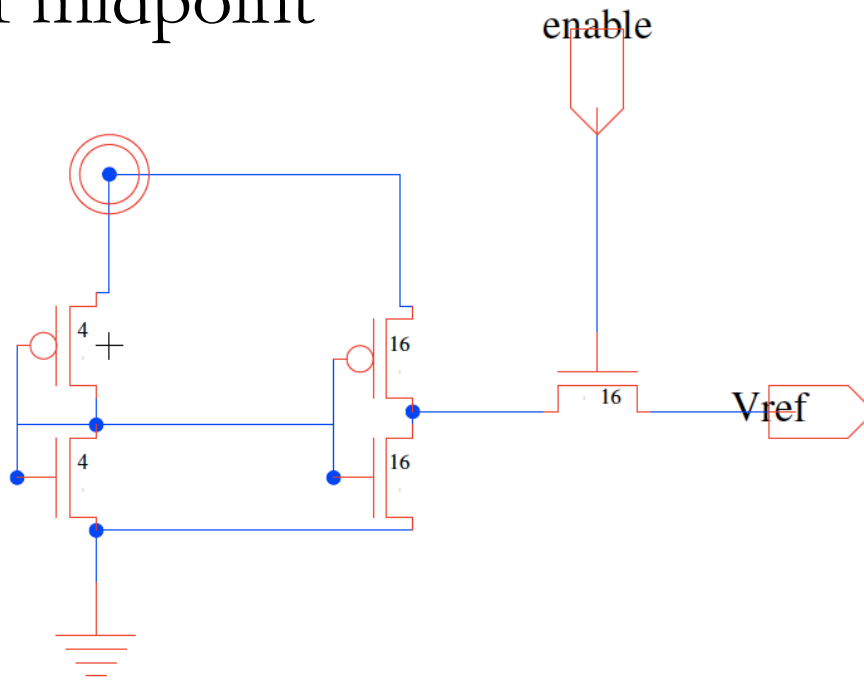
# Charge to middle Voltage


- ❑ Pre-charge bitlines to  $V_{dd}/2$  before begin read operation
- ❑ Now charge sharing doesn't swing to opposite side of midpoint





 
# Compare

□ Both  $W_{\text{access}}=20$ ; vary BL precharge voltage




0 precharge

 


$V_{\text{dd}}/2$  precharge



 
Simulation  $W_{\text{access}}=20$  (precharge  $V_{\text{dd}}/2$ , reading 0)




Transient Response (reading 0)

 

# Simulation $W_{\text{access}}=20$ (with precharge $V_{\text{dd}}/2$ )

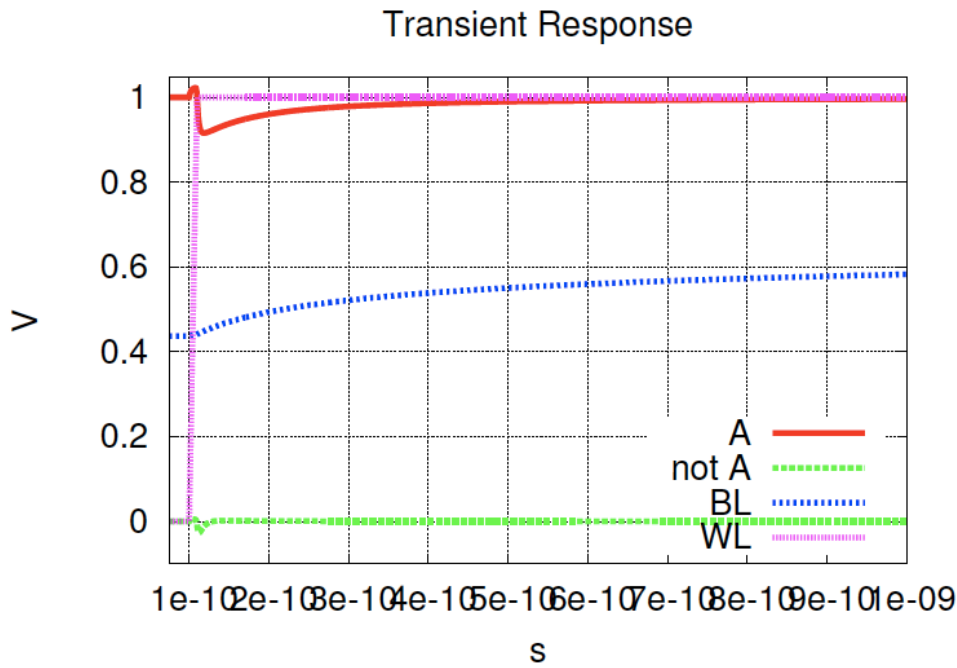


Read 1

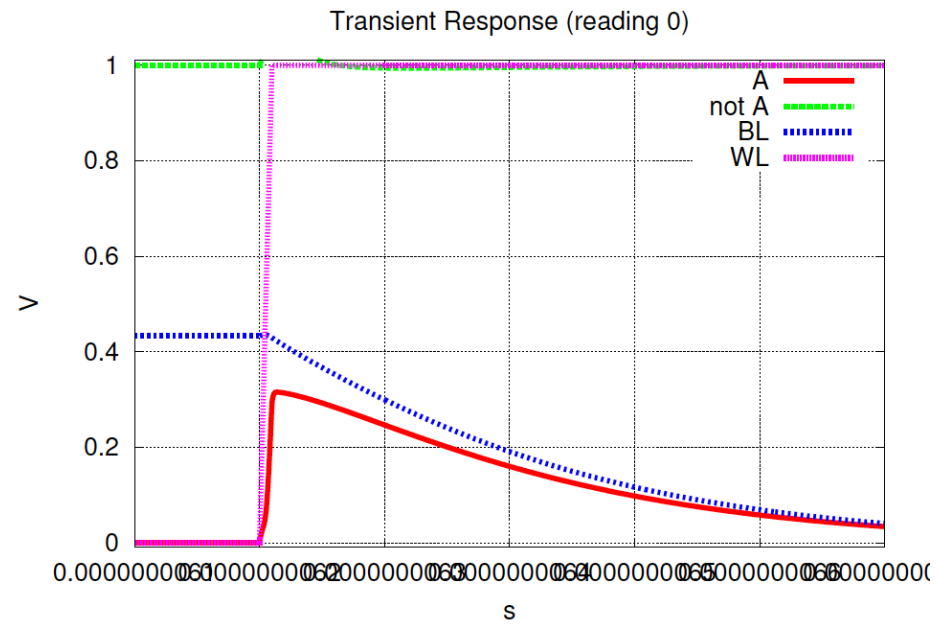

Read 0

 
# Multiple Ports

- ❑ We have considered single-ported SRAM
  - One read or one write on each cycle
- ❑ *Multiported* SRAM are needed for register files
- ❑ Examples:
  - Pipelined ALU register file:
    - add r1,r2,r3
    - $R3 \leftarrow R1 + R2$
    - Requires two reads and one write



 
# Dual-Ported SRAM

- Simple dual-ported SRAM
  - Two independent single-ended reads
  - Or one differential write


 
# Dual-Ported SRAM


- Simple dual-ported SRAM
  - Two independent single-ended reads
  - Or one differential write



- Do two reads and one write by time multiplexing
  - Read during ph1, write during ph2

 
# Multi-Ported SRAM

- ❑ Adding more access transistors hurts read stability
- ❑ Multiported SRAM isolates reads from state node
- ❑ Single-ended bitlines save area


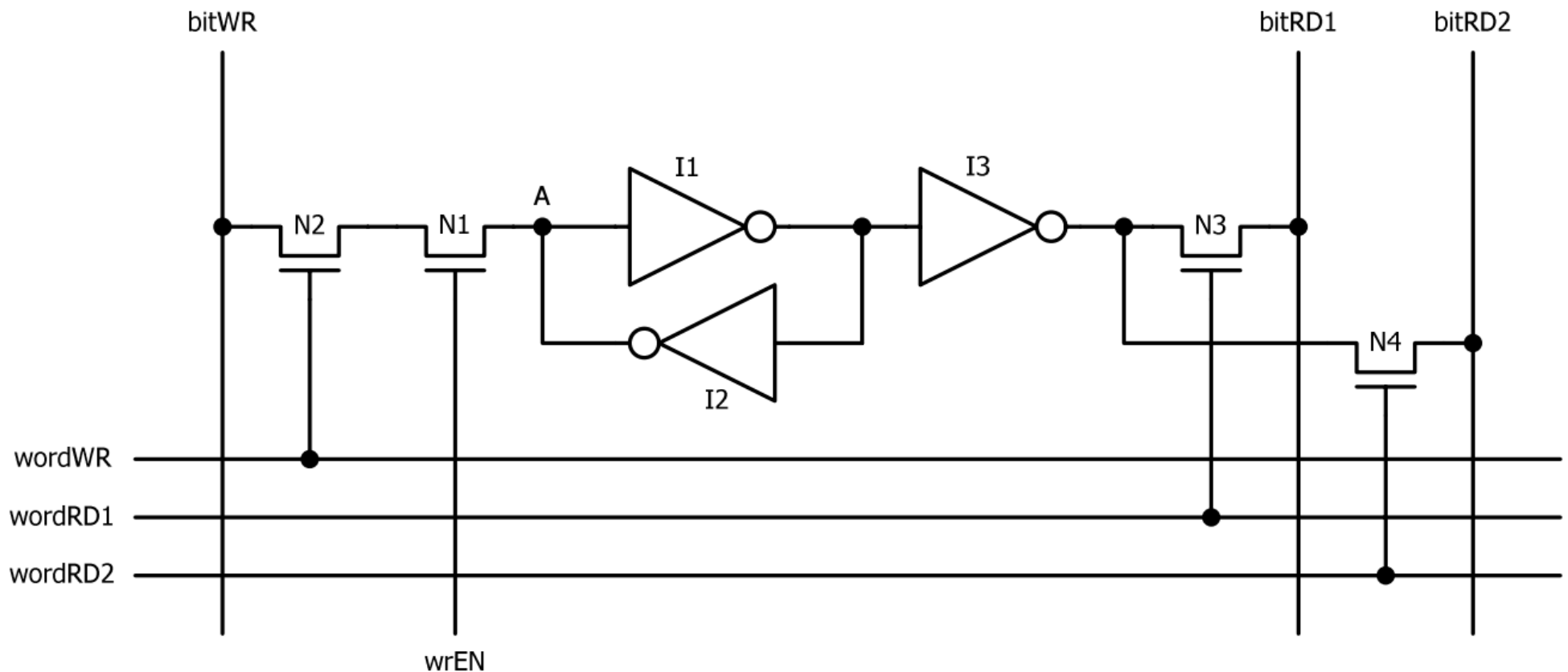
# Register File Cell

- Single-ended 2-read/1-write ports (Slow-write)





# DRAM


---

- ❑ Smaller than SRAM
- ❑ Require data refresh to compensate for leakage




# 3-Transistor DRAM Cell (preclass 4)

- ❑ Cell is inverting on read operation

 


# 3-Transistor DRAM Cell

- Cell is inverting on read operation

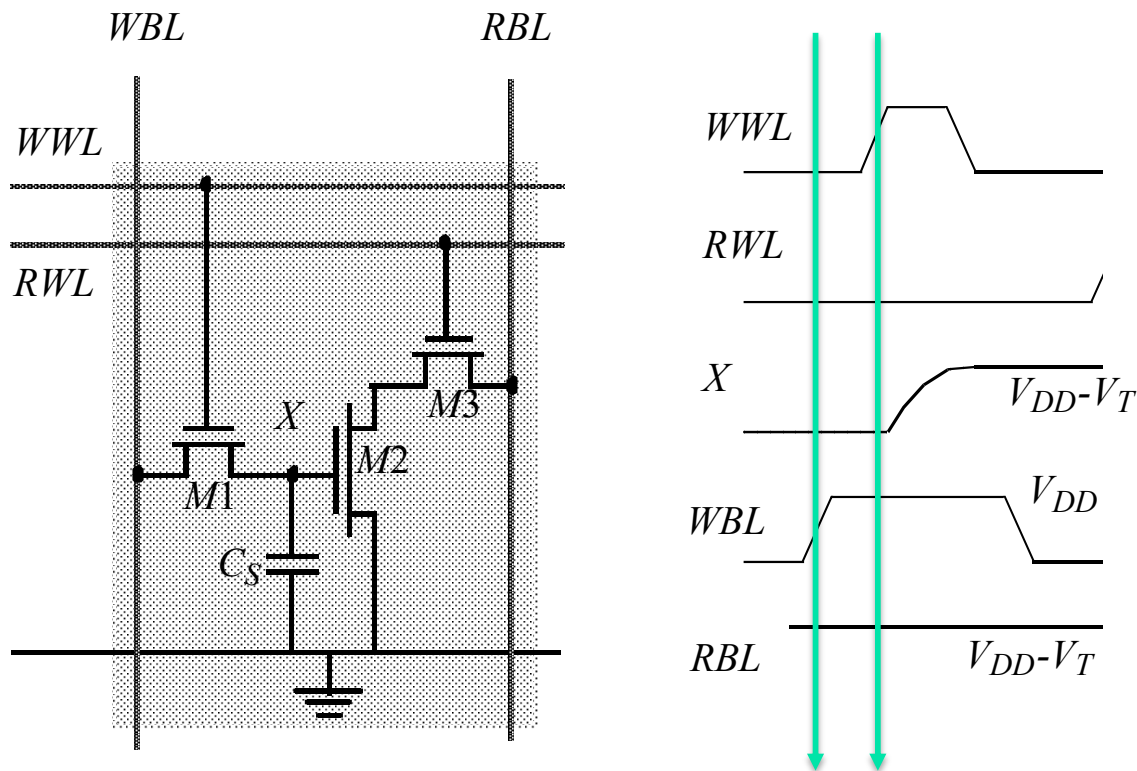


# 3-Transistor DRAM Cell

- Cell is inverting on read operation

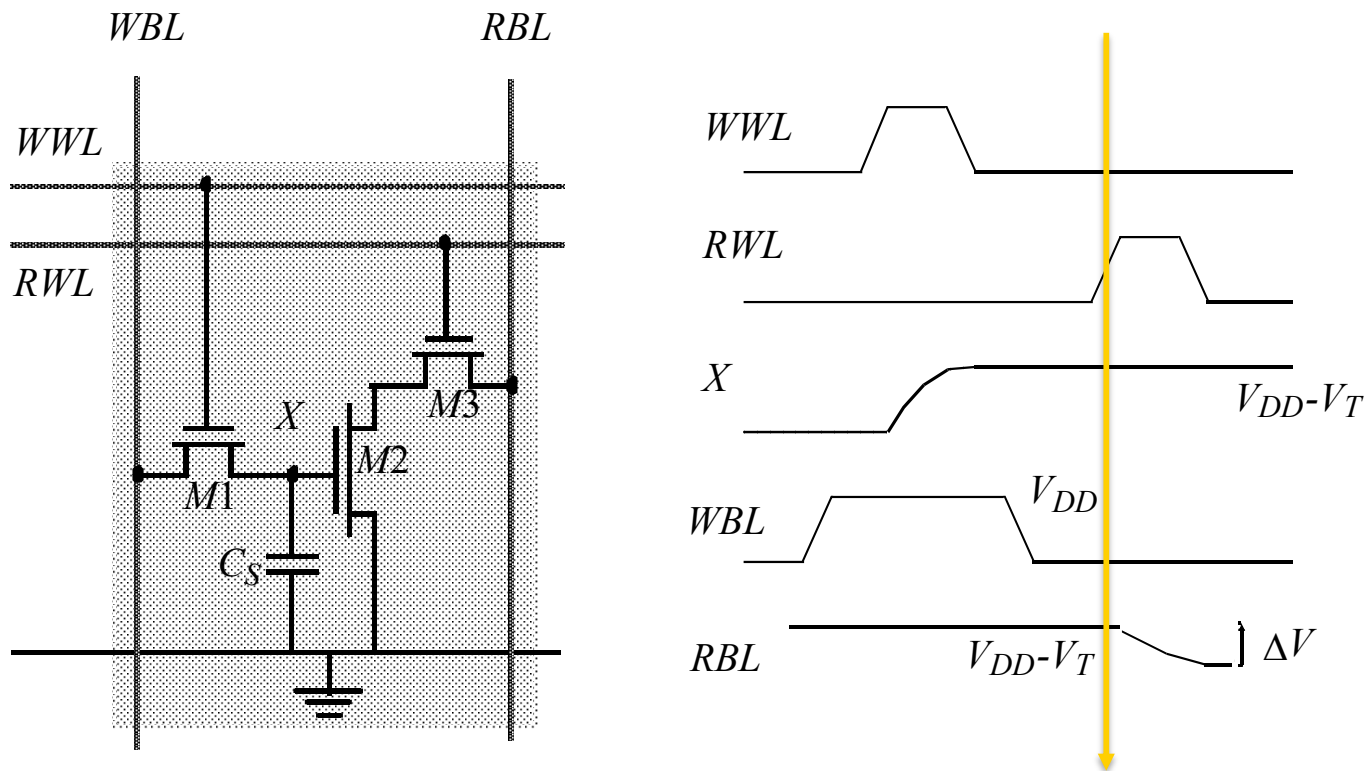


# 3-Transistor DRAM Cell

- Cell is inverting on read operation


 


- No constraints on device ratios
- Reads are non-destructive
- Data stored has a  $V_T$  drop
  - When storing a 1, value at X =  $V_{WWL}-V_{Tn}$

# 1-Transistor DRAM Cell (preclass 5)

 


# 1-Transistor DRAM Cell

  

**Write:  $C_S$  is charged or discharged by asserting WL and BL.**

# 1-Transistor DRAM Cell

 



**Write:**  $C_S$  is charged or discharged by asserting WL and BL.

**Read:** Charge redistribution takes place between bit line and storage capacitance

$$\Delta V = V_{BL} - V_{PRE} = (V_{BIT} - V_{PRE}) \frac{C_S}{C_S + C_{BL}}$$

**Voltage swing is small; typically around 250 mV.**

# 1-Transistor DRAM Cell

  

**Write:**  $C_S$  is charged or discharged by asserting WL and BL.

**Read:** Charge redistribution takes place between bit line and storage capacitance

$$\Delta V = V_{BL} - V_{PRE} = (V_{BIT} - V_{PRE}) \frac{C_S}{C_S + C_{BL}}$$

**Voltage swing is small; typically around 250 mV.**





# DRAM Cell Observations

---

- ❑ 1T DRAM requires a sense amplifier for each bit line, due to charge redistribution read-out
- ❑ DRAM memory cells are single ended in contrast to SRAM cells
- ❑ The read-out of the 1T DRAM cell is destructive; read and refresh operation are necessary for correct operation
- ❑ Unlike 3T cell, 1T cell requires presence of an extra capacitance that must be explicitly included in the design
- ❑ When writing a “1” into a DRAM cell, a threshold voltage is lost. This loss can be circumvented by bootstrapping the word lines to a higher value than  $V_{DD}$ .



# Idea

---

- ❑ Minimize area of repeated cell
  - 6T/5T SRAM
  - Muiltport trade off area for function
  - 1T/3T DRAM helps but slower
- ❑ Compensate with periphery
  - Decoders
  - Bitline (column) drivers
  - Sensing/Amplification (regeneration/restoration)



# Admin

---

- Project 2 out
  - Milestone due Monday 11/22
    - I will give feedback by Wed (night) 11/24
  - Final report due 12/3