

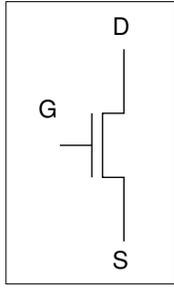
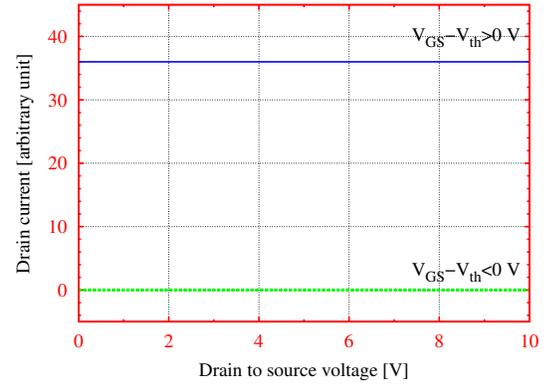




N-type MOSFET

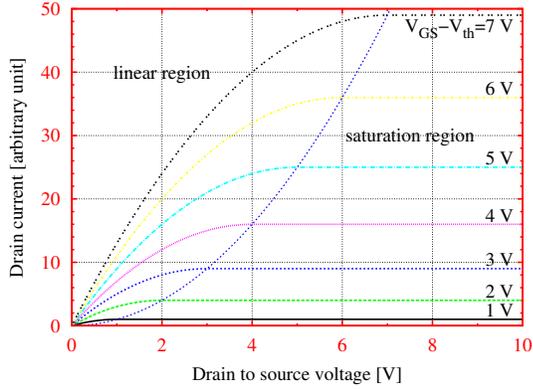

Zero-Order Model

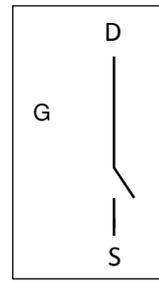

I_{ds} unbounded when $V_{gs} > V_{th}$

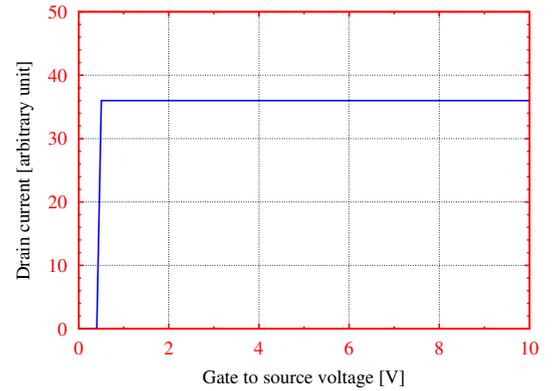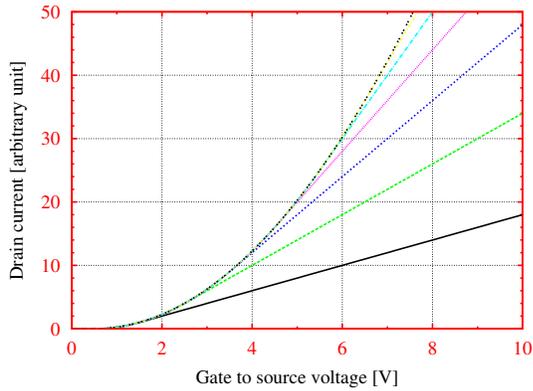

Step at $V_{gs} = V_{th}$


(even this is a simplified approximation)

	NMOS	PMOS
Threshold	$V_{thn} > 0$	$V_{thp} < 0$ $V_{thp} \approx -V_{thn}$
Conduct	positive input $V_{gs} > V_{thn}$	negative input $V_{gs} < V_{thp}$
Drain	most positive terminal	most negative terminal
Source	most negative terminal (source of electrons)	most positive terminal (source of holes)

$$V_{gs} = V_g - V_s \tag{1}$$

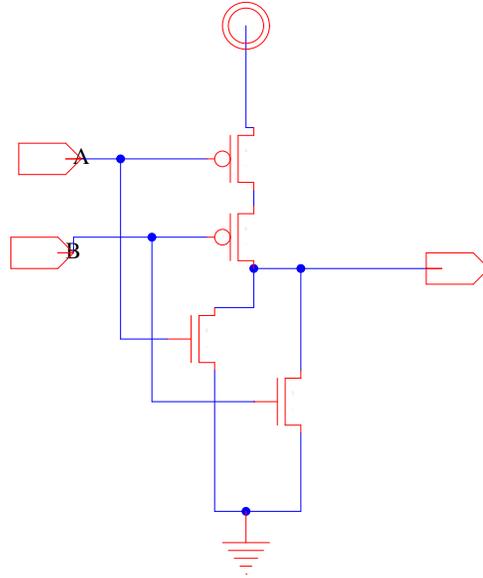1) What function does this circuit implement? (inputs are a and b)

[N.B. crossing wires with no dot are **not** connected.]



2) If $\bar{f} = a + b$, what is f in minimum-sum-of-products form?

[N.B. $\bar{f} = \sim f = /f = (\text{not } f) = f'$]

General form for Static CMOS Gate:

3) Design gate to perform: $f = (\bar{a} + \bar{b}) \cdot \bar{c}$

