

# ESE370: Circuit-Level Modeling, Design, and Optimization for Digital Systems

---

Lec 3: September 10, 2021

Transistor Introduction (first order)






# Today

---

- Basic Digital Gates
- Boolean Logic
  - Basic Algebra
    - DeMorgan's Law
  - Minimum Sum of Products/K-maps
- Cascading Gates
- Transistor first order model
  - For performance estimates (i.e propagation delay!)
  - There are always Rs and Cs!


# Basic Digital Gates

NOT  
 $Y = \bar{X}$

 


X	Y
0	1
1	0

AND  
 $Y = A \cdot B$

 

A	B	Y
0	0	0
0	1	0
1	0	0
1	1	1


OR  
 $Y = A + B$

 

A	B	Y
0	0	0
0	1	1
1	0	1
1	1	1


# Basic Digital Gates

NOT  
 $Y = \bar{X}$

 


X	Y
0	1
1	0

AND  
 $Y = A \cdot B$

 


A	B	Y	Z
0	0	0	1
0	1	0	1
1	0	0	1
1	1	1	0

OR  
 $Y = A + B$

 


A	B	Y	Z
0	0	0	1
0	1	1	0
1	0	1	0
1	1	1	0

NAND  
 $Z = \overline{A \cdot B}$

 


NOR  
 $Z = \overline{A + B}$

 



# Basic Digital Gates

---

 

A	B	C	Z
0	0	0	1
0	0	1	1
0	1	0	1
0	1	1	1
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	0

# Boolean Algebra


□ **TABLE 2-3**  
**Basic Identities of Boolean Algebra**

1. $X + 0 = X$	2. $X \cdot 1 = X$	
3. $X + 1 = 1$	4. $X \cdot 0 = 0$	
5. $X + X = X$	6. $X \cdot X = X$	
7. $X + \bar{X} = 1$	8. $X \cdot \bar{X} = 0$	
9. $\overline{\bar{X}} = X$		
10. $X + Y = Y + X$	11. $XY = YX$	Commutative
12. $X + (Y + Z) = (X + Y) + Z$	13. $X(YZ) = (XY)Z$	Associative
14. $X(Y + Z) = XY + XZ$	15. $X + YZ = (X + Y)(X + Z)$	Distributive
16. $\overline{X + Y} = \bar{X} \cdot \bar{Y}$	17. $\overline{X \cdot Y} = \bar{X} + \bar{Y}$	DeMorgan's



# Combination

---

 

# Boolean Expressions

- Sum-of-products form (SOP)
  - Eg.  $ABC+DEF+GHI$
- Product-of-sums form (POS)
  - Eg.  $(A+B+C)(D+E+F)(G+H+I)$
- Convert between the two with Boolean algebra
  - DeMorgan's Law


$$A + B = \overline{\overline{A} \cdot \overline{B}}$$

$$A \cdot B = \overline{\overline{A} + \overline{B}}$$





# Combination

 



# Canonical Form

---

- Every minterm in your expression has every variable

Row Number	A	B	C	f
0	0	0	0	0
1	0	0	1	0
2	0	1	0	0
3	0	1	1	1
4	1	0	0	0
5	1	0	1	0
6	1	1	0	1
7	1	1	1	1

# Canonical Form



- Every minterm in your expression has every variable

Row Number	A	B	C	f
0	0	0	0	0
1	0	0	1	0
2	0	1	0	0
3	0	1	1	1
4	1	0	0	0
5	1	0	1	0
6	1	1	0	1
7	1	1	1	1

$f(A, B, C) = ABC + ABC\bar{C} + \bar{A}BC$

  
# What is a K(arnaugh)-map?

- ❑ A grid of squares (representing truth table)
- ❑ Each square represents one minterm
- ❑ The minterms are ordered according to Gray code
  - Only one variable changes between adjacent squares
- ❑ Squares on edges are considered adjacent to squares on opposite edges
  - I.e Table wraps around
- ❑ K-maps are clumsy with more than 4 variables




# K-map Examples (Preclass 1)

- 2-variable

 

Eg:  $Z = A'B' + AB' + A'B$

- 3-variable

 

# K-map Examples (Preclass 2)

□ 2-variable

		B	0	1
A	0			
	1			



$$\text{Eg: } Z = A'B' + AB' + A'B$$

□ 3-variable

					BC	00	01	11	10
A	0								
	1								



$$\text{Eg: } Z = A'B'C' + A'B + ABC' + AC$$

# Static CMOS Gate Structure

 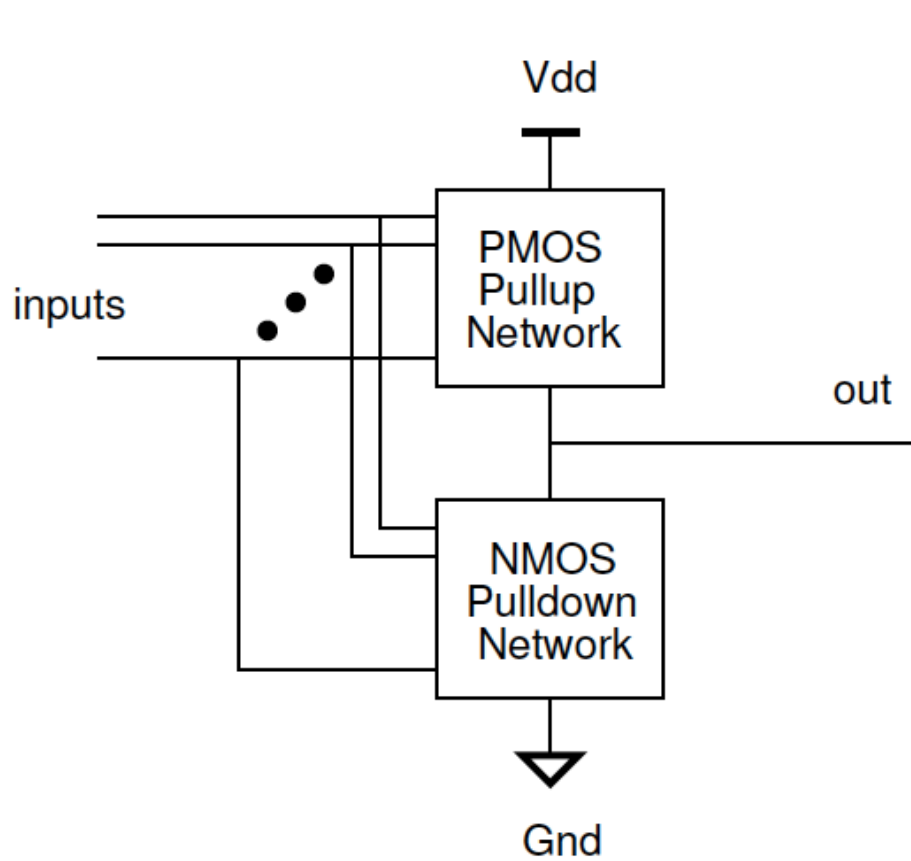
 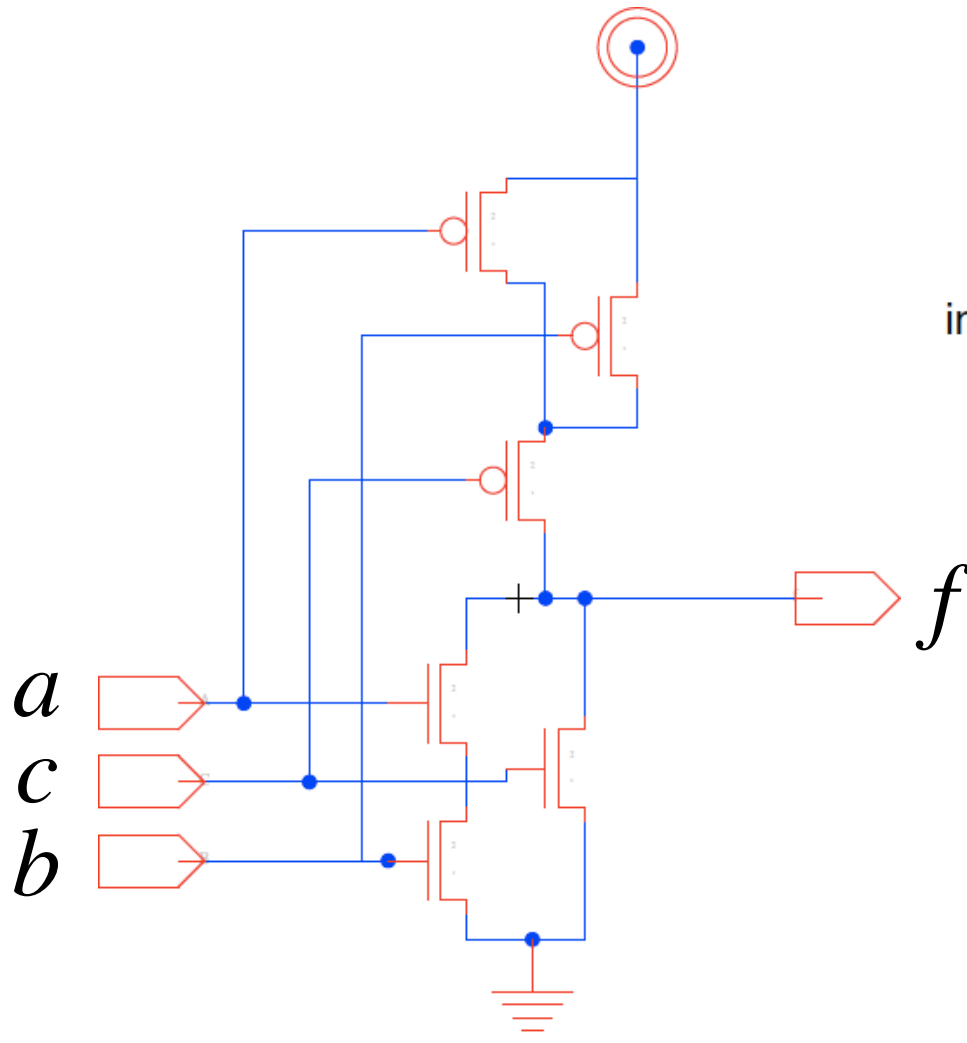
# Gate Design Example

- Design gate to perform:  $f = (\bar{a} + \bar{b}) \cdot \bar{c}$









 
# Inverting Stage

---

- Each stage of Static CMOS gate is inherently inverting



# NAND/NOR Fundamental Gates

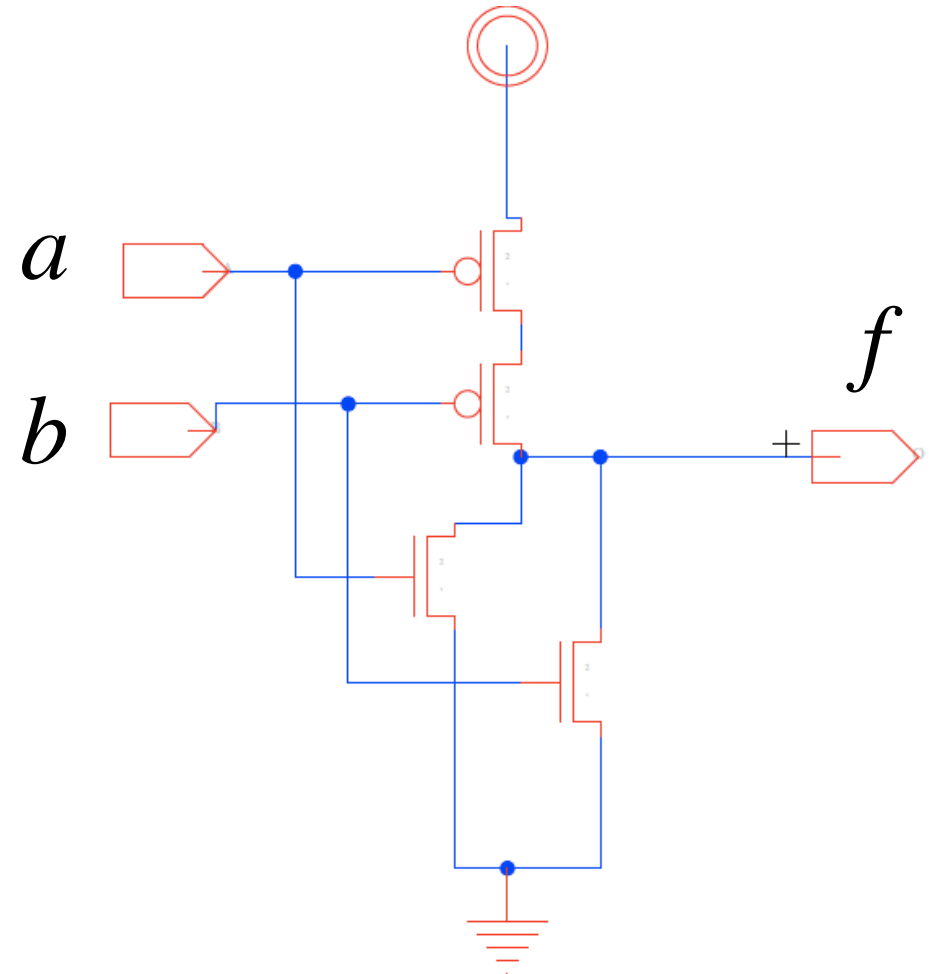 




# How implement OR?

---

# How implement OR?

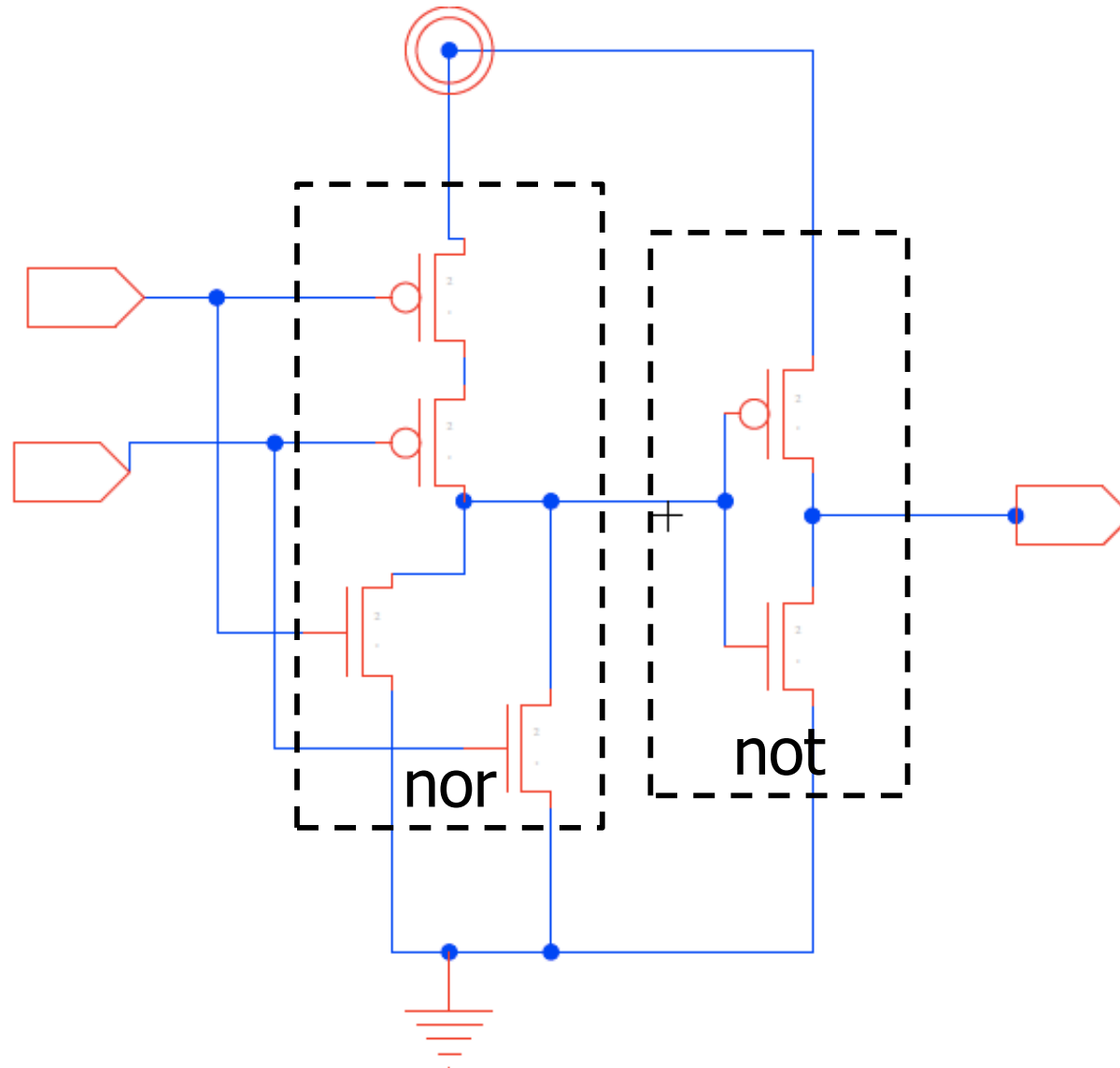



# Cascading Stages

---

- ❑ Can always cascade “stages” to build more complex gates
- ❑ Could simply build nor2 or nand2 at circuit level and assemble arbitrary logic by combining – universality
  - but may not be smallest/fastest/least power



Implement:  $f = a \cdot \bar{b}$

---

□ Pullup?


□ Pulldown?

Hint: use cascading stages

Implement:  $f = a \cdot \bar{b}$

□ Pullup?


□ Pulldown?

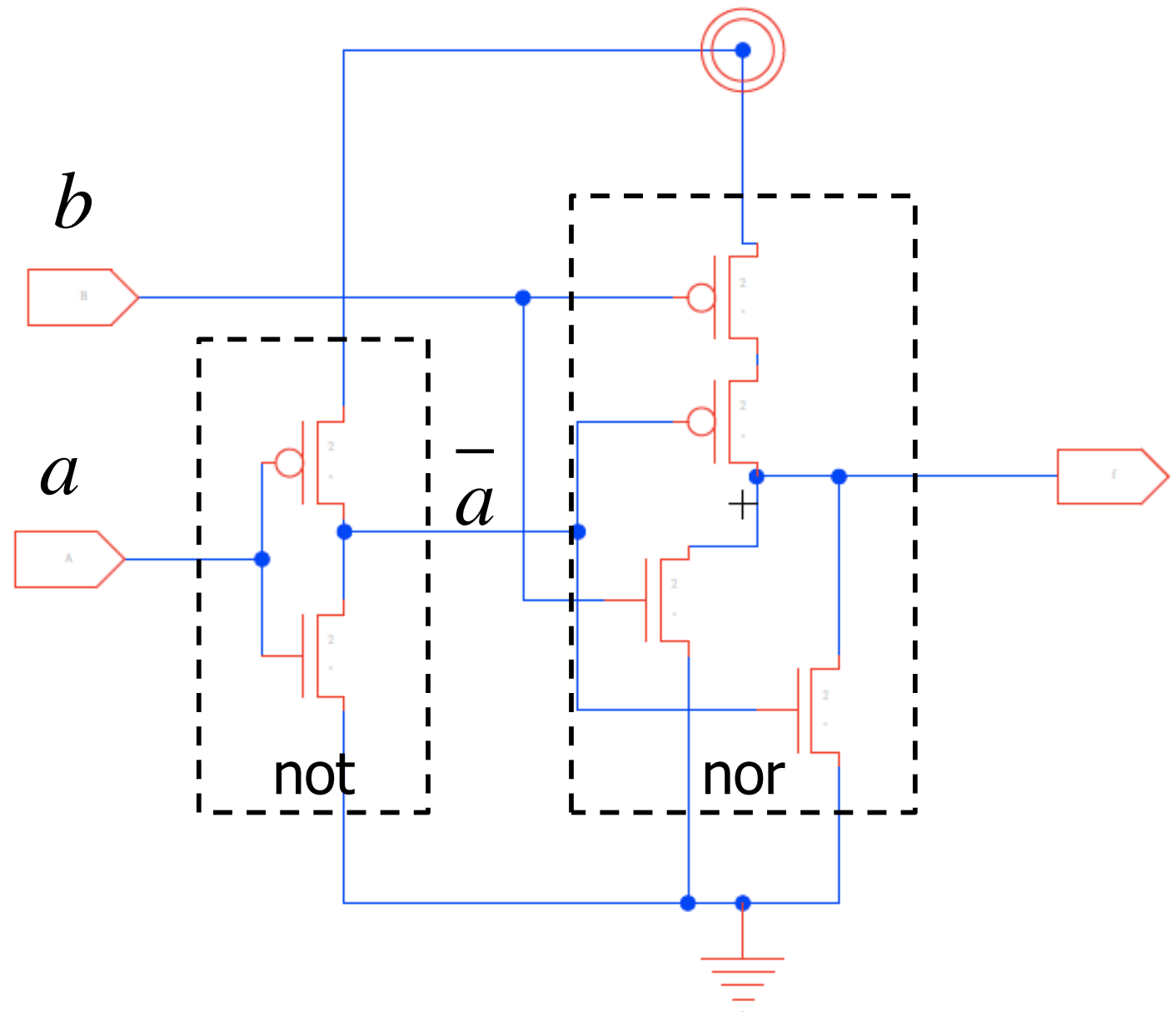
 
# Final Voltage? (Preclass 4)

Assume  $V_{in}$  is 0 for  $t < 0$  and steps to 1V at  $t = 0$ .

What value does  $V_{measure}$  take on as  $t \rightarrow \infty$  ?





 
# Final Voltage?


Assume  $V_{in}$  is 0 for  $t < 0$  and steps to 1V at  $t = 0$ .

What value does  $V_{measure}$  take on as  $t \rightarrow \infty$  ?



 
# Final Voltage?

□ Bonus question: Which one will settle faster?



**A**

 


**B**
 
# Final Voltage?

Assume  $V_{in}$  is 0 for  $t < 0$  and steps to 1V at  $t = 0$ .


What value does  $V_{measure}$  take on as  $t \rightarrow \infty$  ?


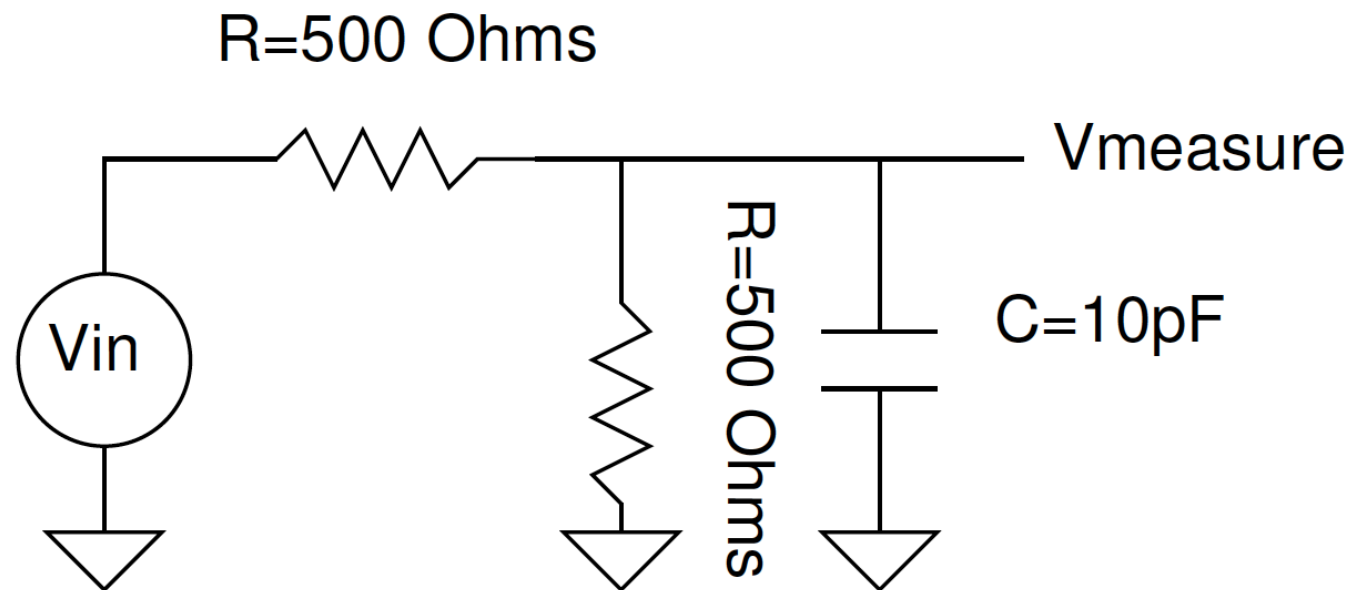
# Final Voltage?

Assume  $V_{in}$  is 0 for  $t < 0$  and steps to 1V at  $t = 0$ .

What value does  $V_{measure}$  take on as  $t \rightarrow \infty$  ?






# Conclude?

---

- DC/*Steady-State*
  - Ignore the capacitors
  - Look like “open circuit”

# MOSFET – Zeroeth Order Model

 

## □ Ideal Switch


$V_{GS} > V_{th} \rightarrow$  switch is closed, conducts

$V_{GS} < V_{th} \rightarrow$  switch is open, does not conduct

## □ Gate draws no current from input

- Loads input capacitively (gate capacitance)


# First Order Model

 

## □ Switch

- Loads gate input capacitively
  - $C_g$
- Has finite drive strength
  - $R_{on}$

# First Order Model

 







## □ Switch

- Loads gate input capacitively
  - $C_g$
- Has finite drive strength
  - $R_{on}$

What do **drive** and **load** mean?



# First Order Model - PMOS

      


$V_{DS}, V_{GS} < 0$



# CMOS Buffer Gate

Stage 1    Stage 2


Vdd

 

# Reminder: Zero-Order Model?

What happens when  $V_{in} = V_{dd} > V_{thn}$ ?


$$V_{GS} = 0 > V_{th,p}$$

 

$$V_{th,p} = -V_{th,n}$$

$$V_{GS} = V_G - V_S$$


$$V_{GS} = -V_{dd} < V_{th,p}$$

 


$$V_{out} = V_{dd}$$

$$V_{GS} = V_G - V_S = V_{dd} > V_{th,n}$$


# CMOS Buffer Gate - First Order

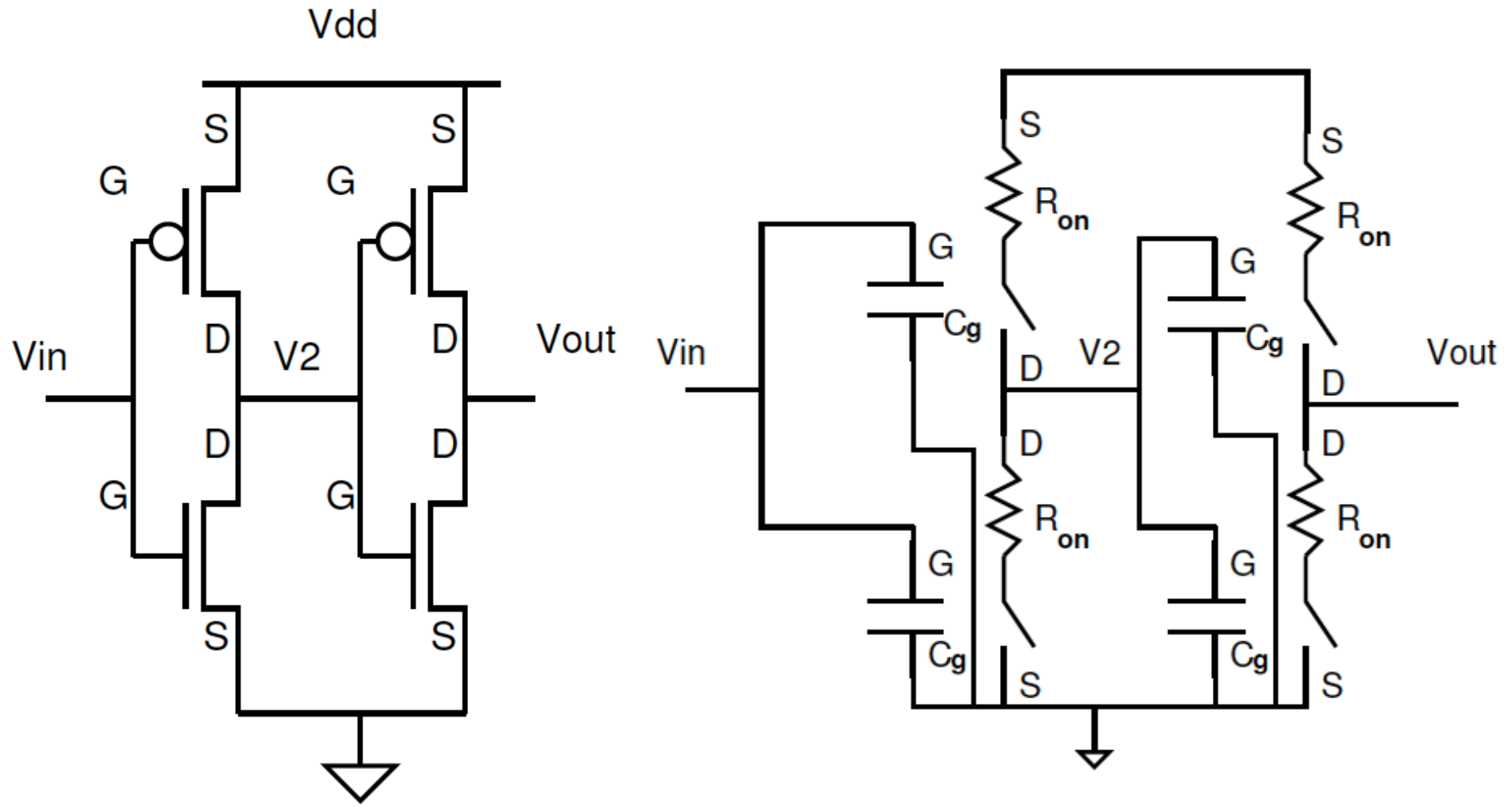


# CMOS Buffer Gate - First Order

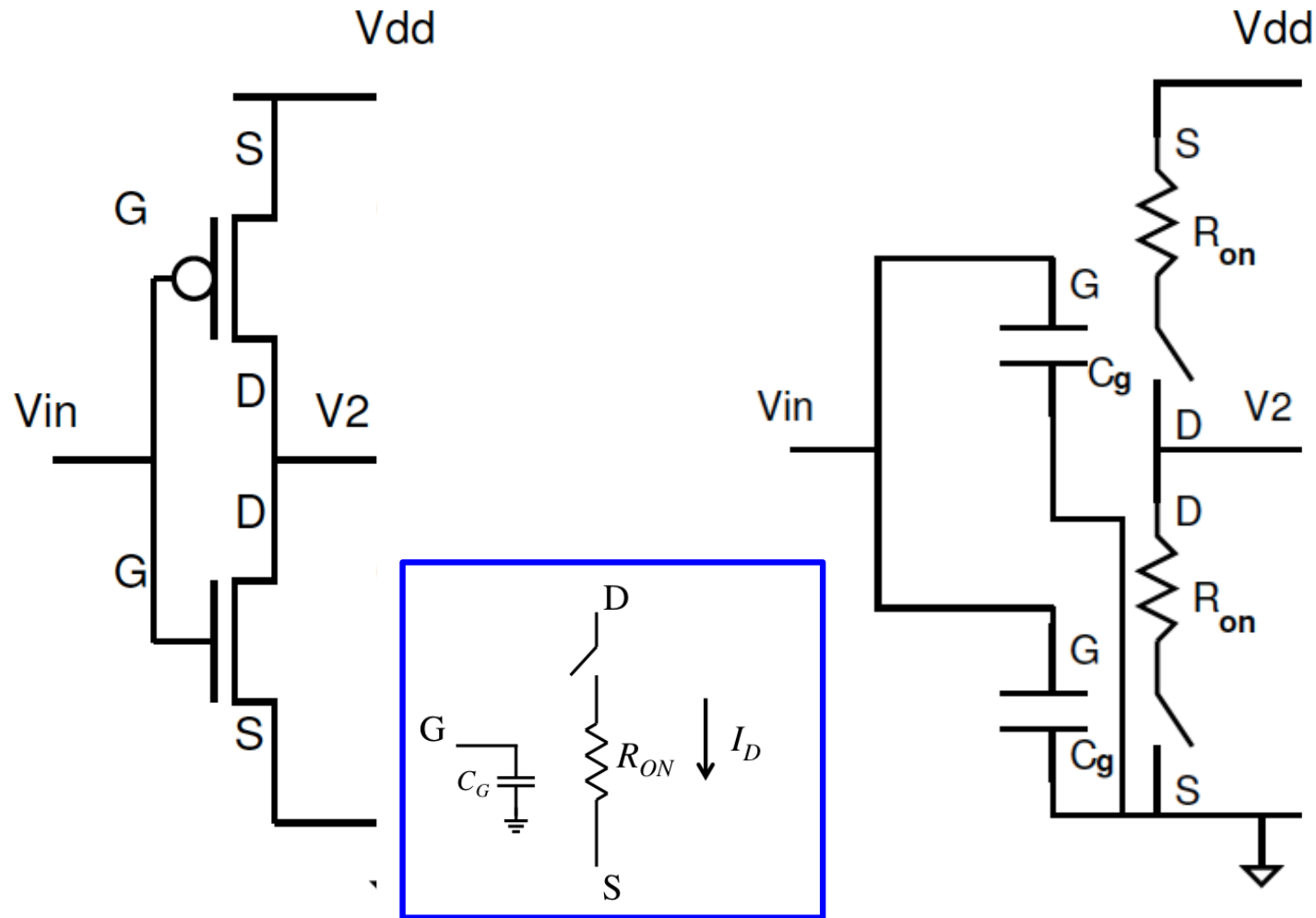


# CMOS Buffer Gate - First Order

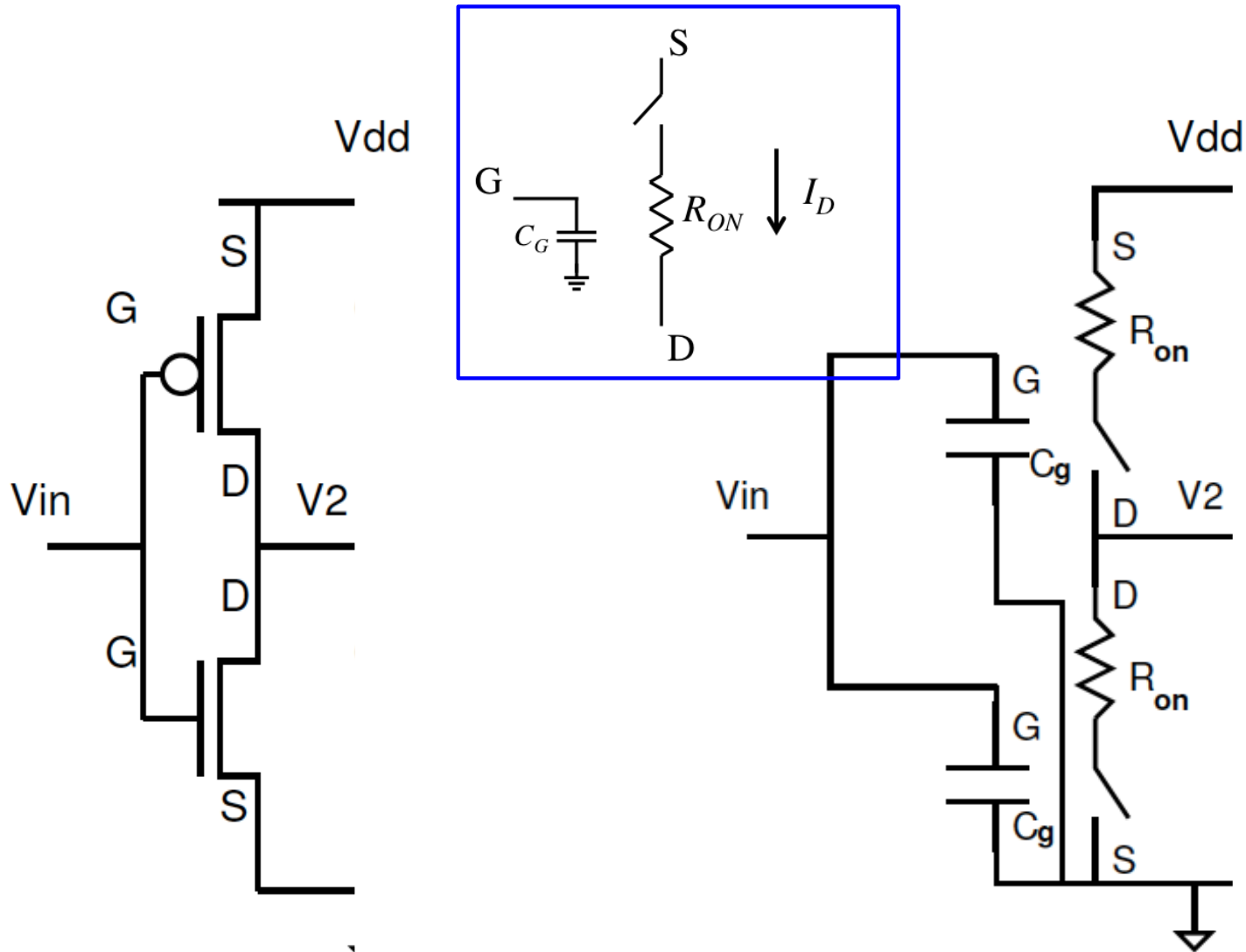

# CMOS Buffer Gate - First Order

 


# Zero-Order Model to Set Switches

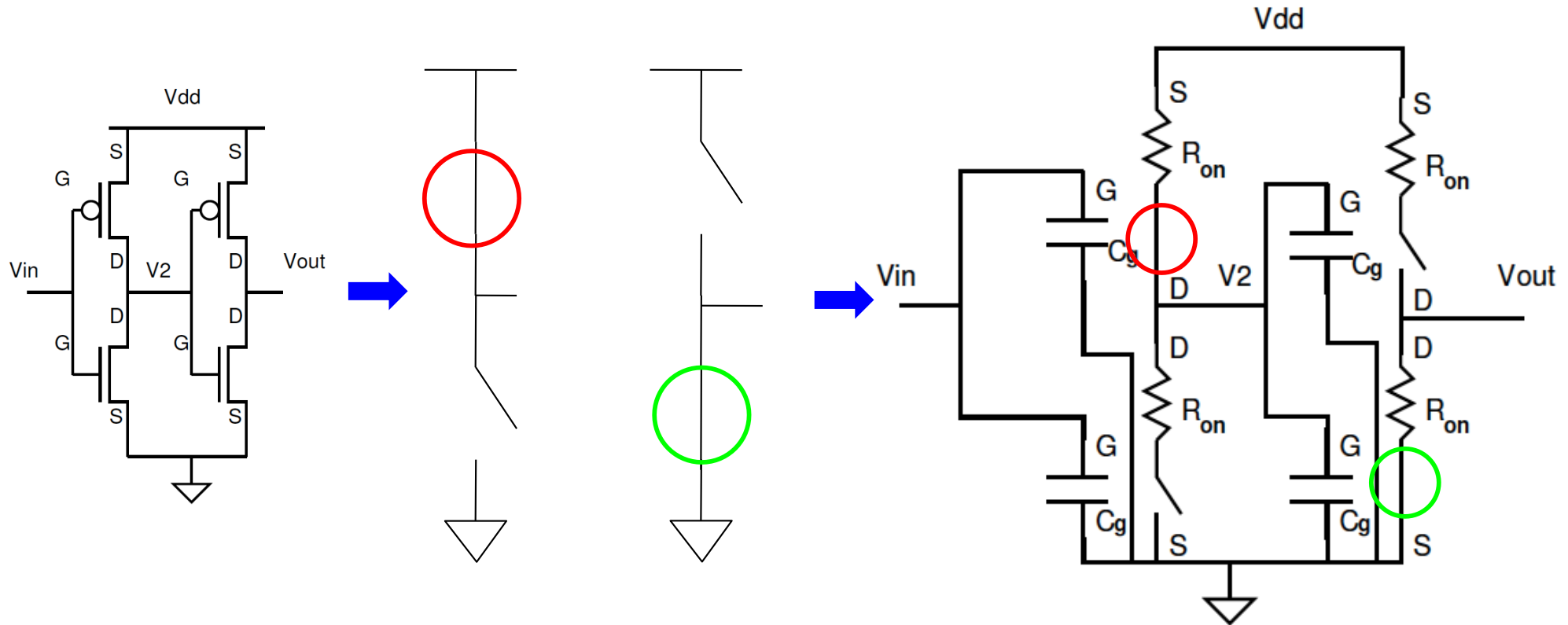

□ What is  $V_{IN}$  for this switch pattern?




# CMOS Buffer Gate - First Order

 

ESE215 problem


- ❑ Leaves an RC Circuit we can analyze

# CMOS Buffer Gate - First Order

 


- Look at intermediary node  $V_2$ 
  - Connected to output of stage 1 and input of stage 2

# CMOS Buffer Gate - First Order

 


- What is equivalent circuit for the gate output of stage 1 driving  $V_2$ ? What is load on the output of stage 1?

# CMOS Buffer Gate - First Order

 


- Stage 1 equivalent circuit for the gate output
- Load on  $V_2$ 
  - Capacitive, input of stage 2

# CMOS Buffer Gate - First Order

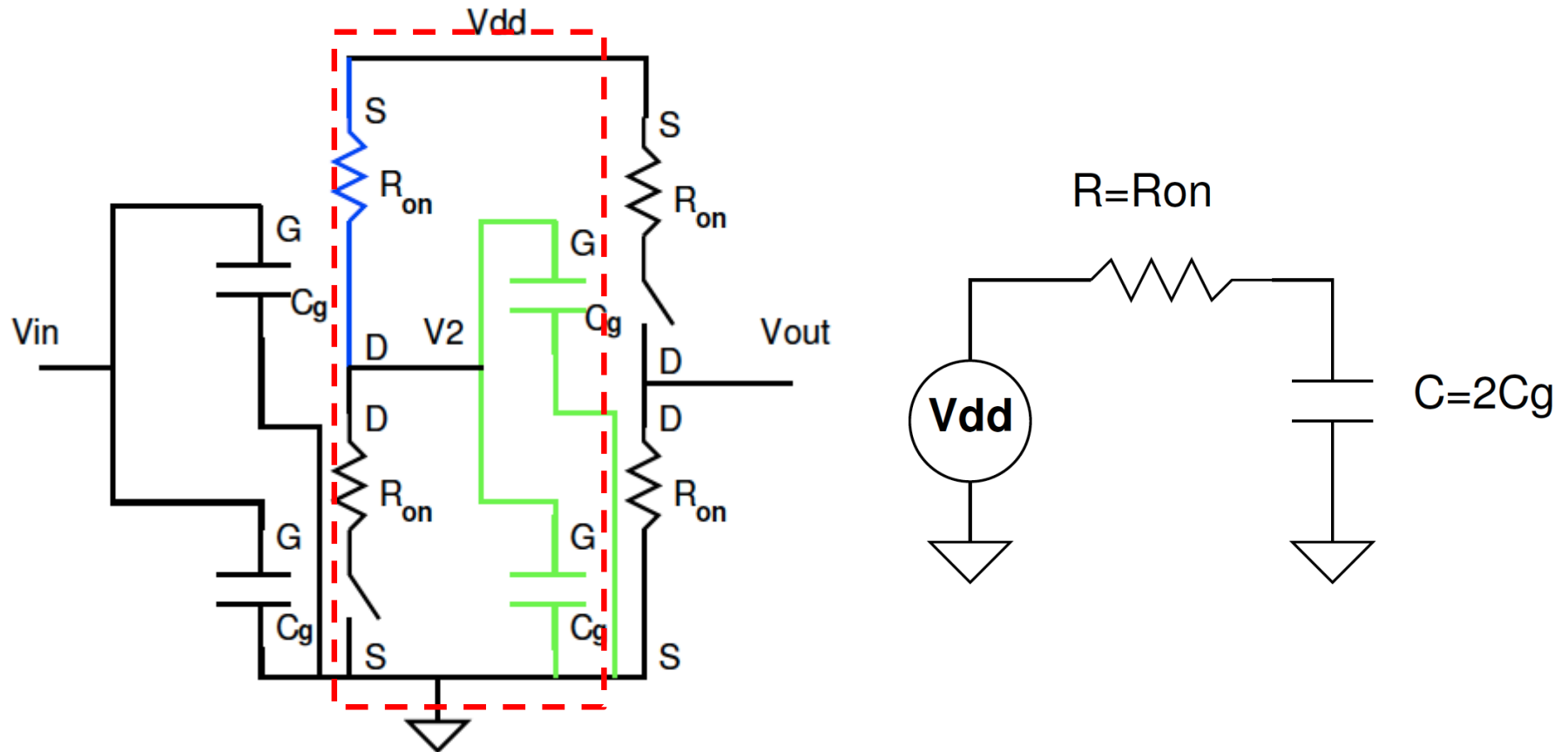


- Stage 1 equivalent circuit for the gate output
- Load on  $V_2$ 
  - Capacitive, input of stage 2

# CMOS Buffer Gate - First Order

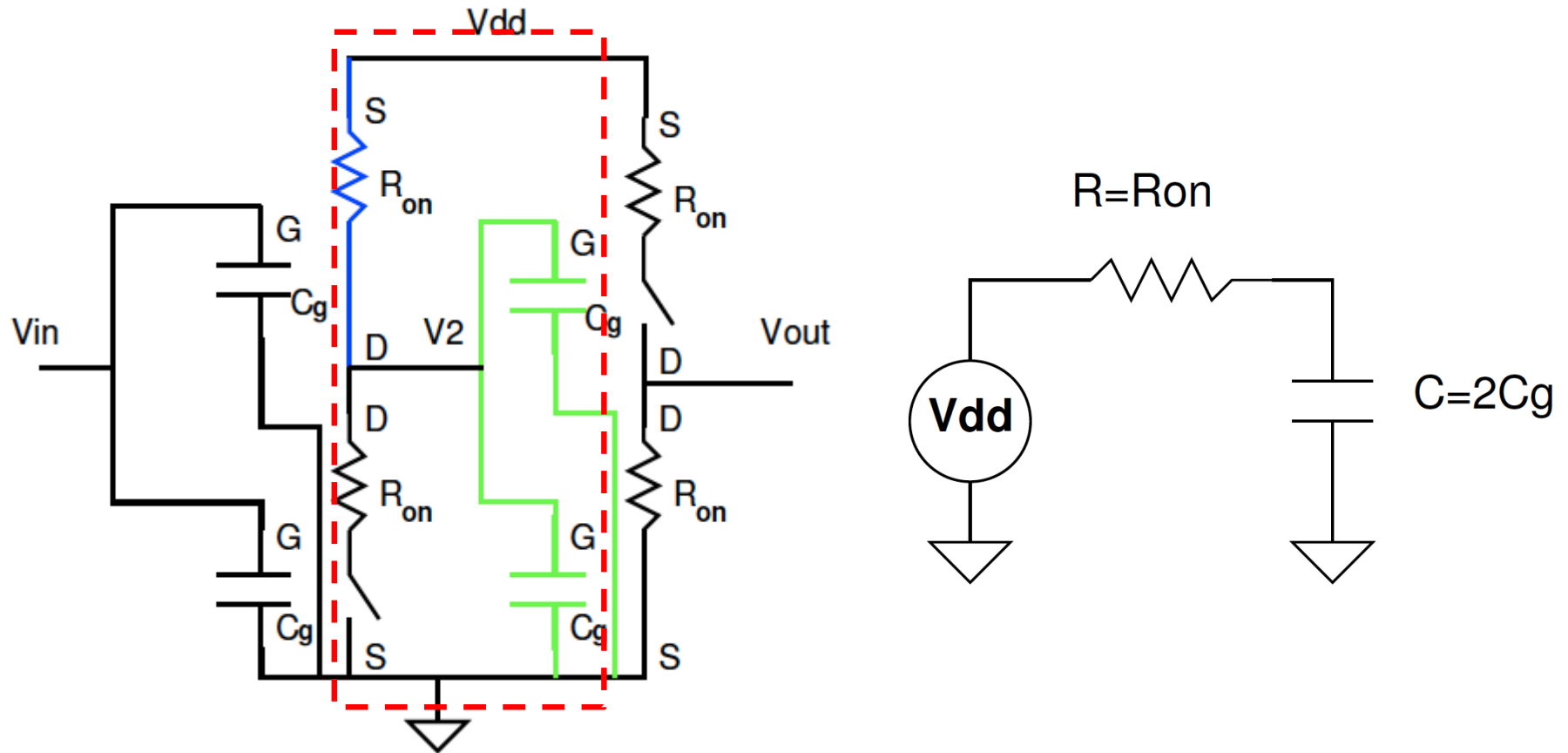

- What is time constant of  $V_2$  when  $V_{in}$  switches from  $V_{DD}$  to 0?

# CMOS Buffer Gate - First Order

 

- What is time constant of  $V_2$  when  $V_{in}$  switches from  $V_{DD}$  to 0?
  - $\tau = 2R_{on}C_g$



# First-Order Model

---


- ❑ Includes settling times/delay
- ❑ Voltage settling with capacitive loads
  - At least some basis for reasoning about delay






# What is still missing?

## IV curve

 


## 1<sup>st</sup> Order

 




# What is still missing?

## IV curve

 

## 1<sup>st</sup> Order

 



# What is still missing?

---

- What happens at intermediate voltages?
  - When the input is not rail-to-rail (not just gnd or  $V_{dd}$  inputs)
- Details of dynamics, including...
  - Input transition is not an ideal step
  - Intermediate drive strengths change with  $V_{GS}$ 
    - Drain resistance changes
- Sub-threshold operation
  - When  $V_{gs} < V_{th}$



# Design: Engineering Control

---

- $V_{th}$ 
  - Process engineer
- Drive strength ( $R_{on}$ )
  - Circuit engineer
  - Control with sizing transistors
- Supply voltages ( $V_{dd}$ )
  - Range set by process engineer
  - Detail use by circuit engineer



# Big Ideas

---

- ❑ MOSFET Transistor as switch
  - With limited drive
- ❑ Purpose-driven simplified modeling
  - Aid reasoning, sanity check, simplify design
- ❑ Analysis methodology
  - Zero order to understand switch state (logic)
  - First-order to get equivalent RC circuit (delay)



# Admin

---

- Diagnostic grades recorded
  - Solutions posted online (pdf in Canvas)
  - Make sure you understand
  - Diagnose what you need to review and study
    - Karnaugh maps (minimum sum of products), RC capacitive settling (time constant), and wire resistive and capacitive properties
- HW 1 due **Tuesday** 9/14 next week
  - Because you need Monday lecture for noise margins
    - Can look at last year's lecture slides if you want to look ahead
  - HW due following **Monday** 9/20