

ESE370: Circuit-Level Modeling, Design, and Optimization for Digital Systems

Lec 32: December 1, 2021
Transmission Line




Next few Lectures

- ❑ Saw in action in lab
- ❑ Where transmission lines arise?
- ❑ General wire formulation
- ❑ Lossless Transmission Line
- ❑ End of Transmission Line?
- ❑ Termination
- ❑ Discuss Lossy
- ❑ Implications

Where Transmission Lines Arise

Transmission Lines

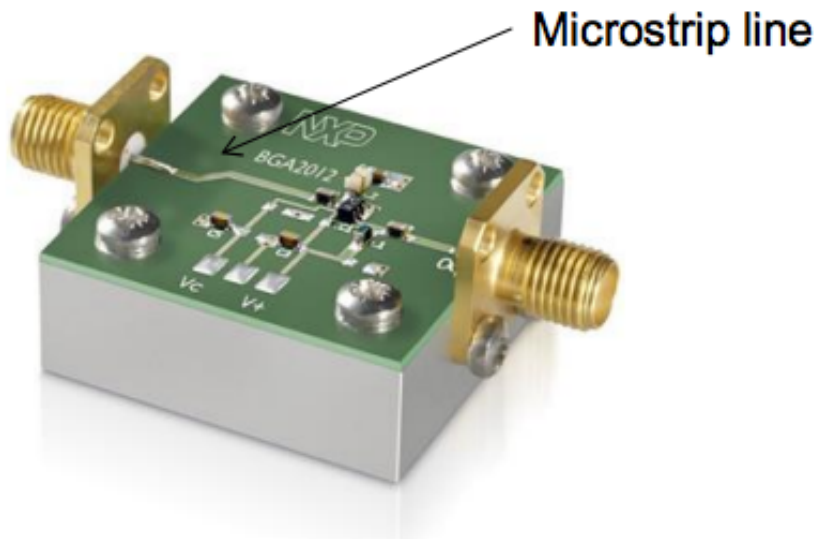- ❑ Cable: coaxial
- ❑ PCB
 - Strip line
 - Microstrip line
- ❑ Twisted Pair (Cat5)





Transmission Lines

- How did the traces behave in lab?
- How does this differ from
 - Ideal equipotential?
 - RC-wire on chip?



Transmission Lines

- This is what long wires/cables look like
 - Aren't an ideal equipotential
 - Signals take time to propagate
 - Maintain shape of input signal
 - Within limits
 - Shape and topology of wiring effects how signals propagate



Transmission Lines

- Need theory/model to support design
 - Reason about behavior
 - Understand what can cause noise
 - Engineer high performance/speed communication

Wire Formulation

From the Way Way Back

- ❑ Problem: A long cable – the trans-atlantic telephone cable – is laid out connecting NY to London. We would like analyze the electrical properties of this cable.
- ❑ For simplicity, assume the cable has a uniform cross-sectional configuration (shown as two wires here)






Trans-Atlantic Cable


- ❑ Can we do it with circuit theory?
- ❑ Fundamental problem with circuit theory is that it assumes that the speed of light is infinite. So all signals are in phase: $V(z) = V(z + \ell)$
- ❑ Consequently, all variations in space are ignored:
 $\partial/\partial z \rightarrow 0$
- ❑ This allows the lumped circuit approximation

Lumped Circuit Properties of Cable

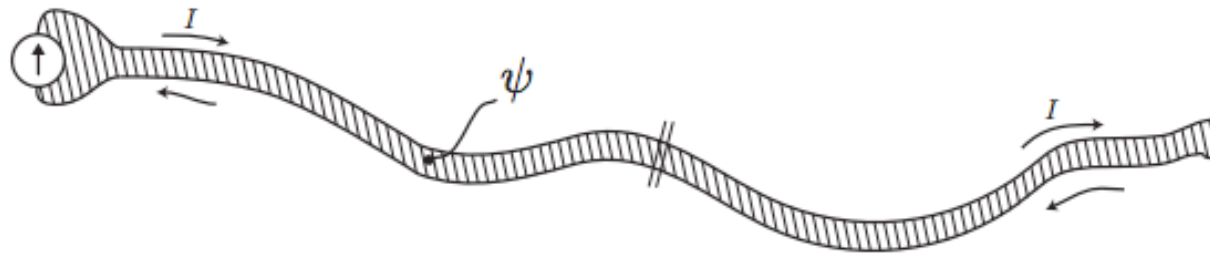- Shorted Line: The long loop has inductance since the magnetic flux ψ is not negligible (long cable) ($\psi = LI$)



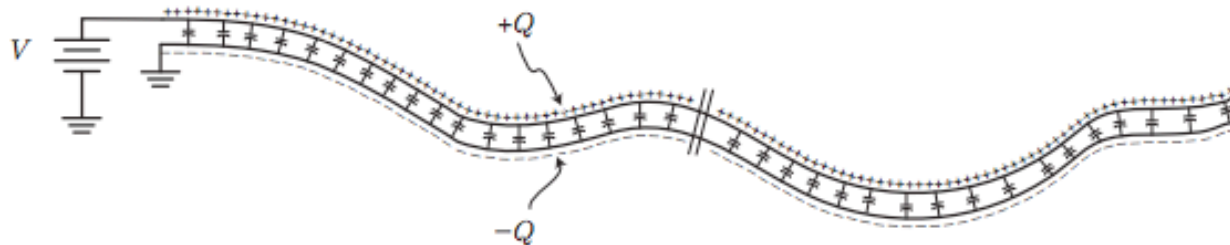
- Open Line: The cable also has substantial capacitance ($Q = CV$)






Wires

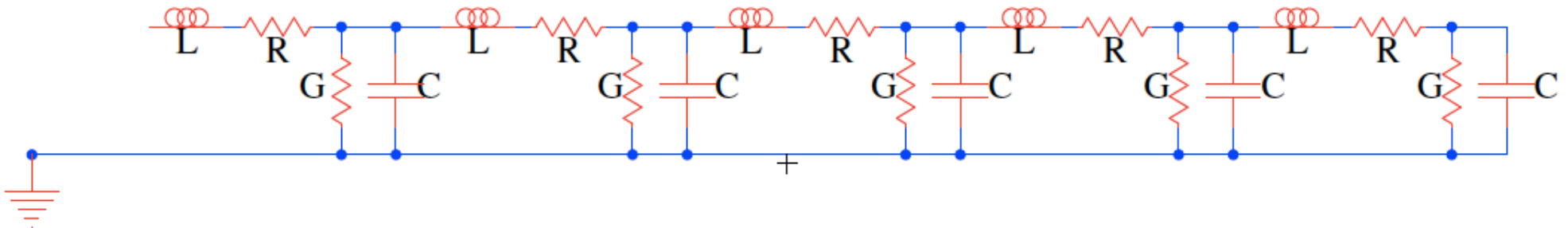- In general, our “wires” have distributed R, L, C components



RC Wire (Preclass 1)

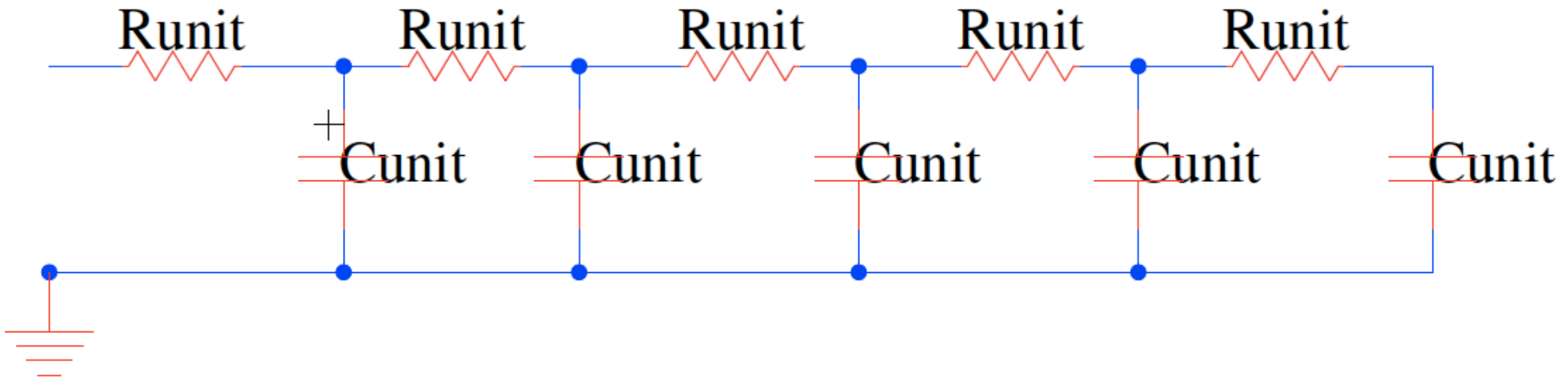
- When R dominates L
 - We have the distributed RC Wires
 - Typical of on-chip wires in ICs
 - What is RC response to step?







Transmission Line

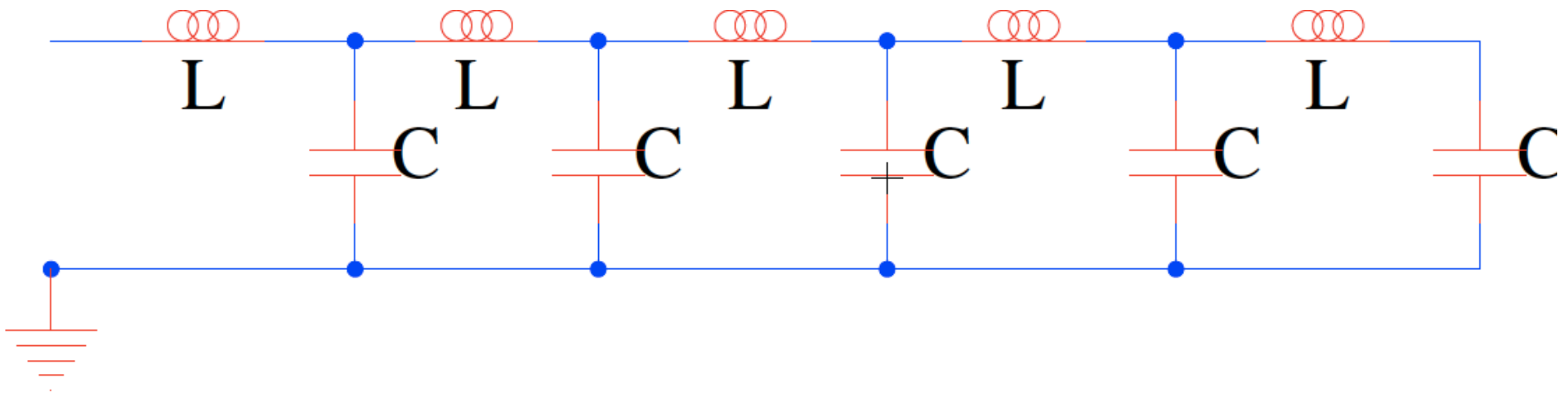- When resistance is negligible
 - Have LC wire = Lossless Transmission Line
 - No energy dissipation (loss) through R's
 - More typical of printed circuit board (PCB) wires and bond wires





Build Intuition from LC (Preclass 2)

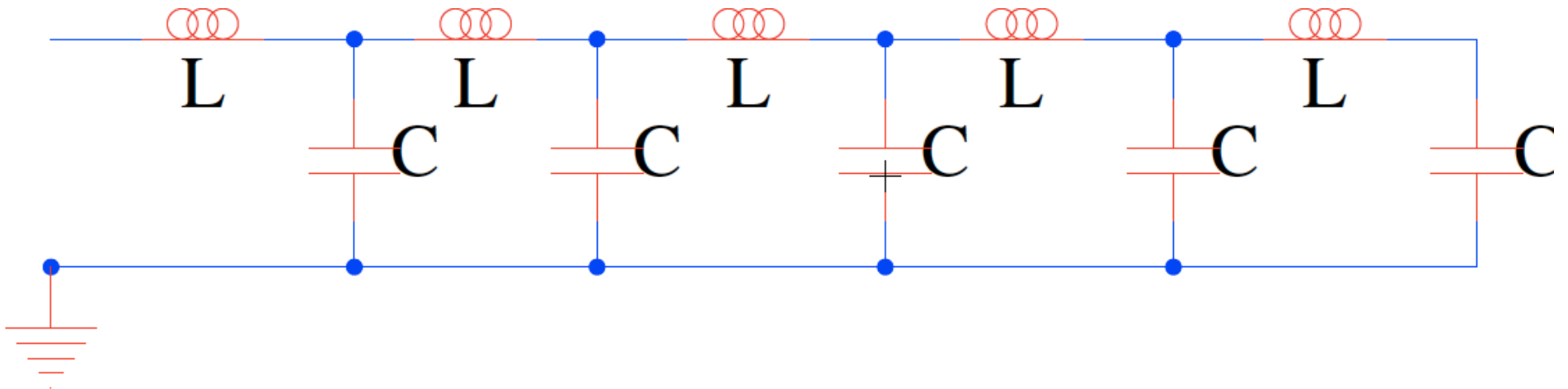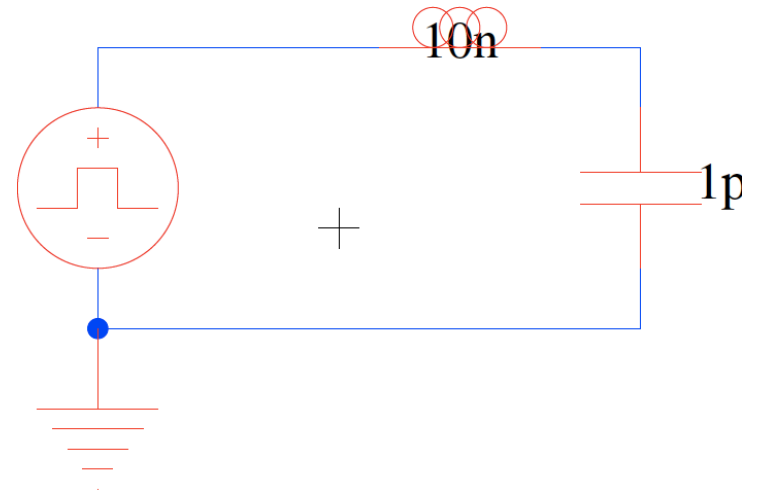- ❑ What did one LC do?
- ❑ What will chain do?



Build Intuition from LC (Preclass 2)

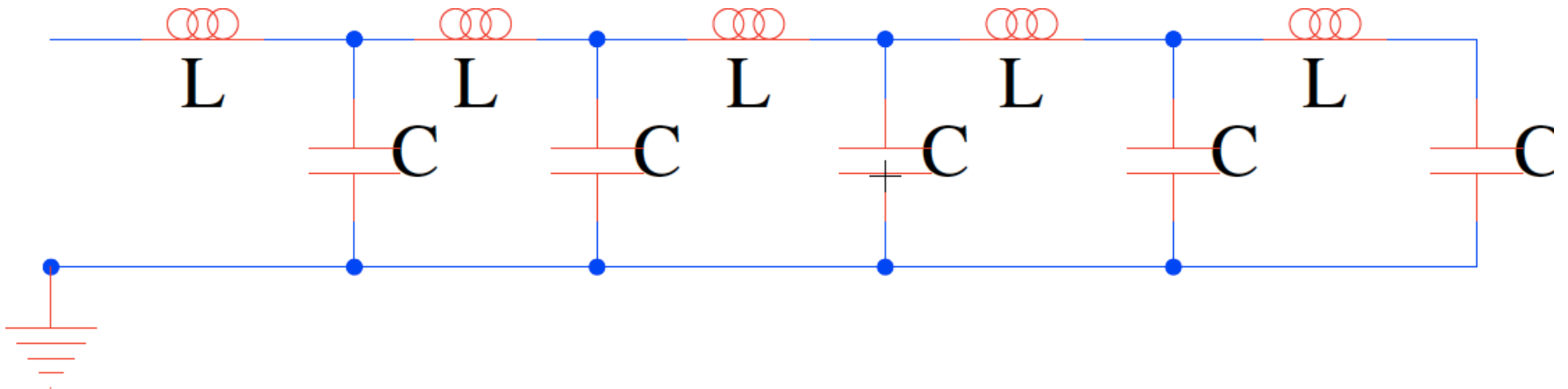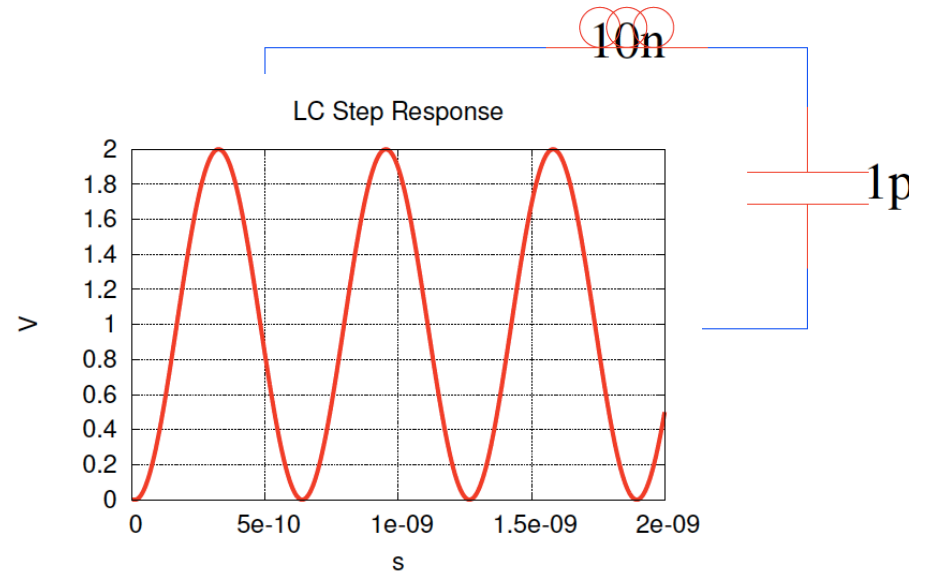- ❑ What did one LC do?
- ❑ What will chain do?






Intuitive: Lossless


- Pulses travel as waves without distortion
 - (up to a characteristic frequency)




SPICE Simulation

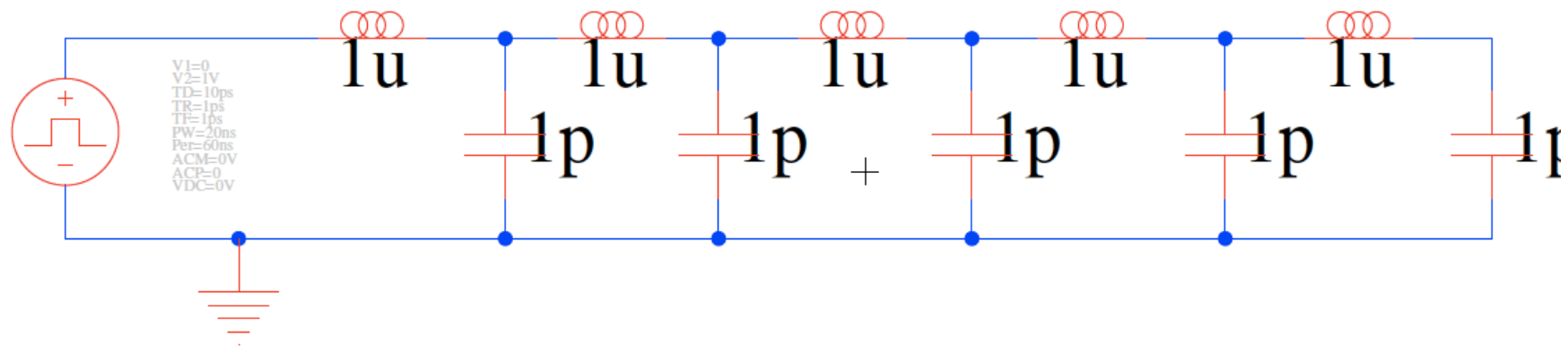

Step Response SPICE

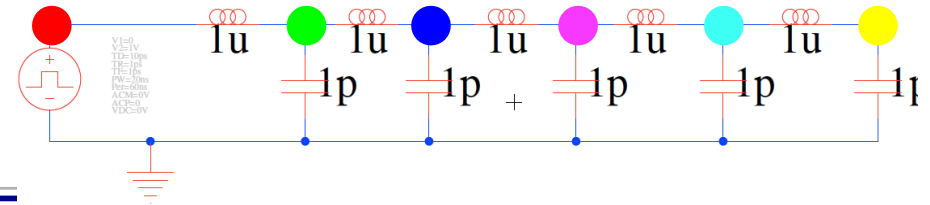


LC Ladder

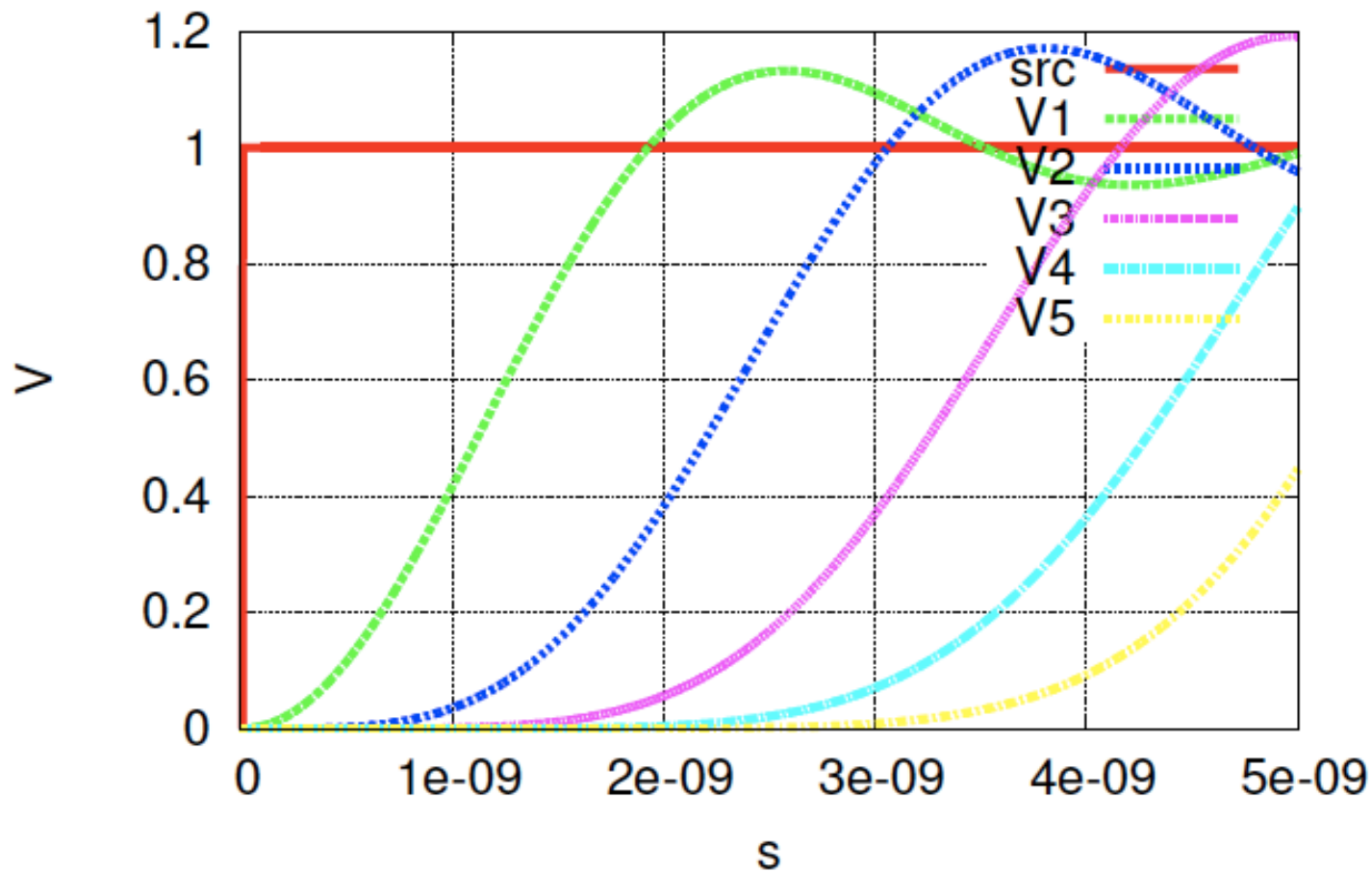




Pulse Response SPICE

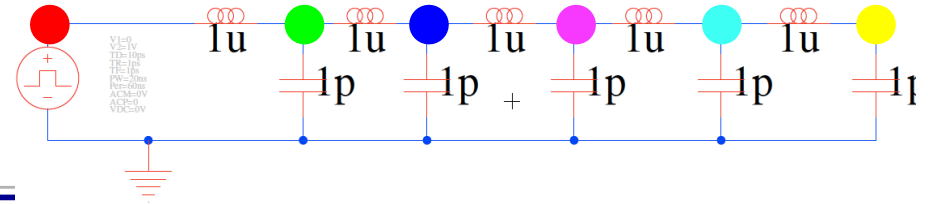


Step Reponse 20 element LC Ladder

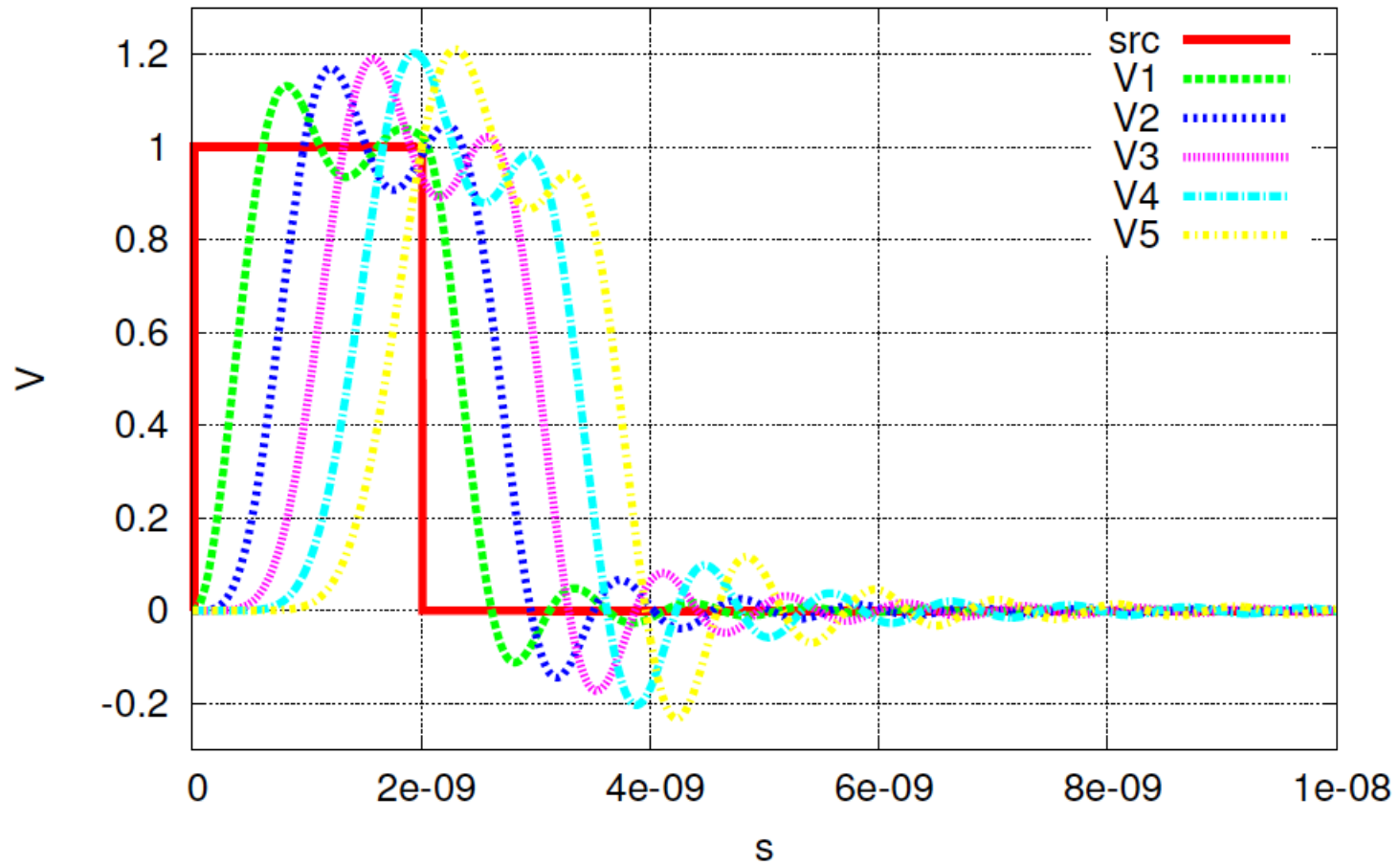




Contrast RC Wire

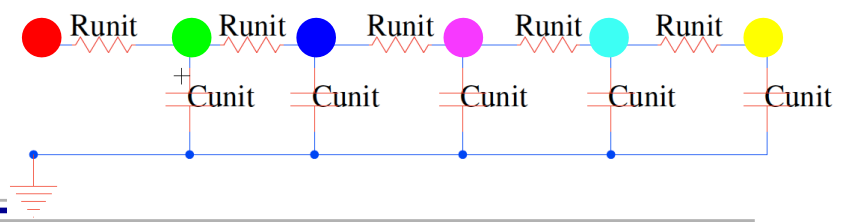


RC Ladder

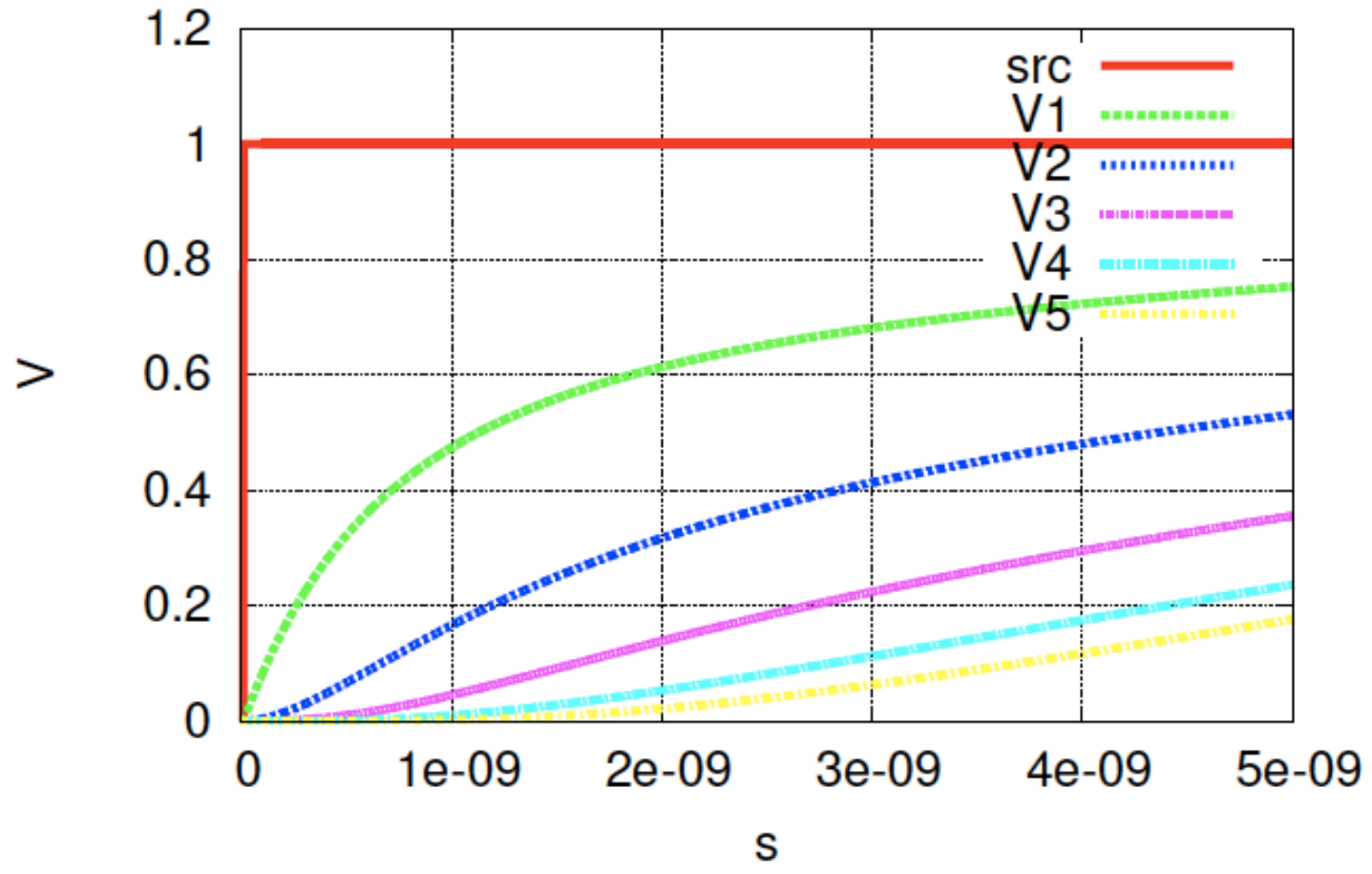




Contrast

LC Ladder

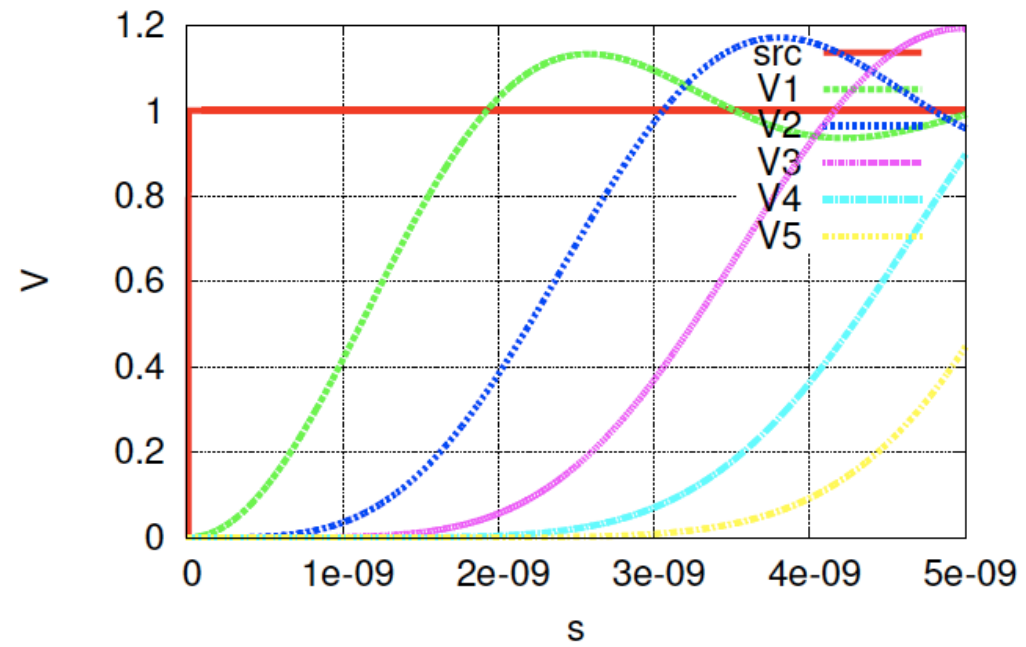

RC Ladder

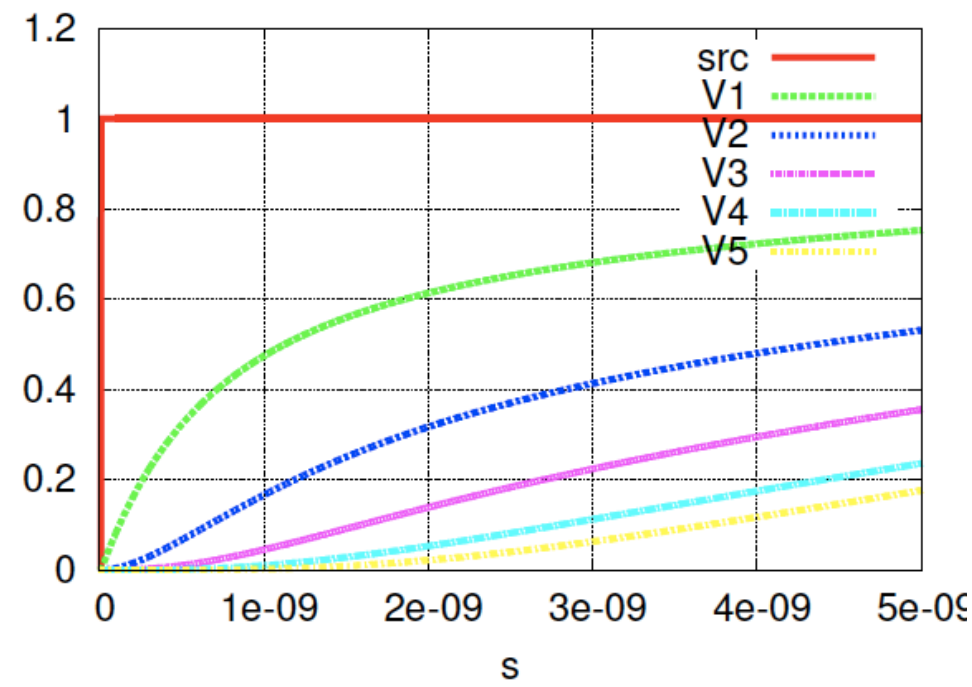




Model

- Now voltage is a function of time **and** position
 - Position along wire – distance from source
- Want to get $V(x,t)$
 - And $I(x,t)$


Setup Relations (Preclass 4)

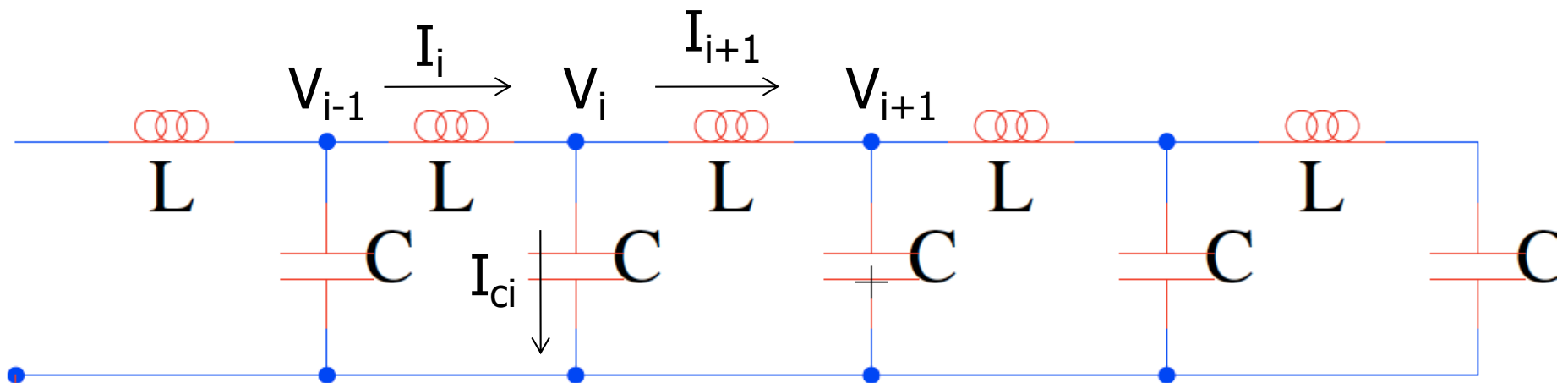- i is a node, x is the distance from source, Δx is distance between nodes
- Position along wire: $x=i \Delta x$
- So $V_i(t) = V(x=i\Delta x, t)$



Setup Relations (Preclass 4)

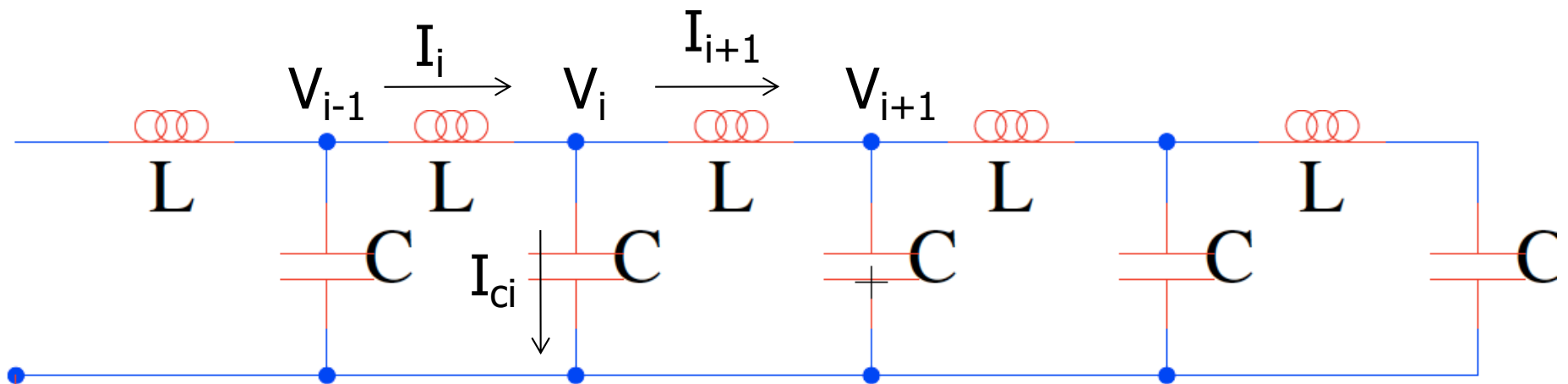- a) KCL @ V_i : $I_i - I_{i+1} =$
- b) $I_{ci} =$
- d) $V_i - V_{i-1} =$



Setup Relations (Preclass 4)

□ a) KCL @ V_i : $I_i - I_{i+1} =$


$$I_i - I_{i+1} = C \frac{dV_i}{dt}$$

□ b) $I_{ci} =$

□ d) $V_i - V_{i-1} =$

$$V_i - V_{i-1} = -L \frac{dI_i}{dt}$$

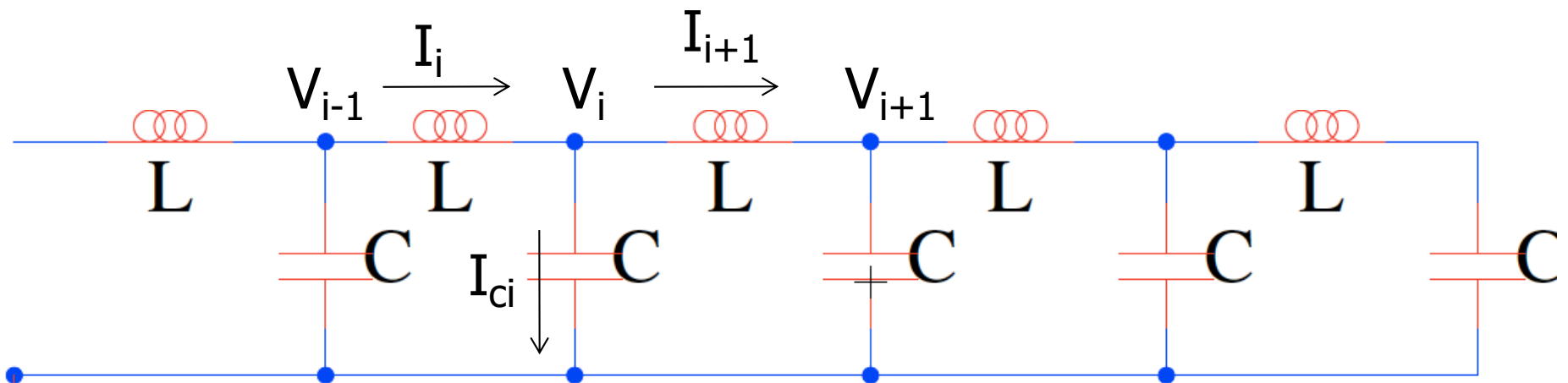- i is a node, but has spatial dimension along the Tline
 - No longer agnostic of wire length
- V_i changes at different positions



Setup Relations (Preclass 4)

□ a) KCL @ V_i : $I_i - I_{i+1} =$


$$I_i - I_{i+1} = C \frac{dV_i}{dt} \Rightarrow -\frac{dI_i}{dx} = C \frac{dV_i}{dt}$$

□ b) $I_{ci} =$

□ d) $V_i - V_{i-1} =$

$$V_i - V_{i-1} = -L \frac{dI_i}{dt} \Rightarrow \frac{dV_i}{dx} = -L \frac{dI_i}{dt}$$

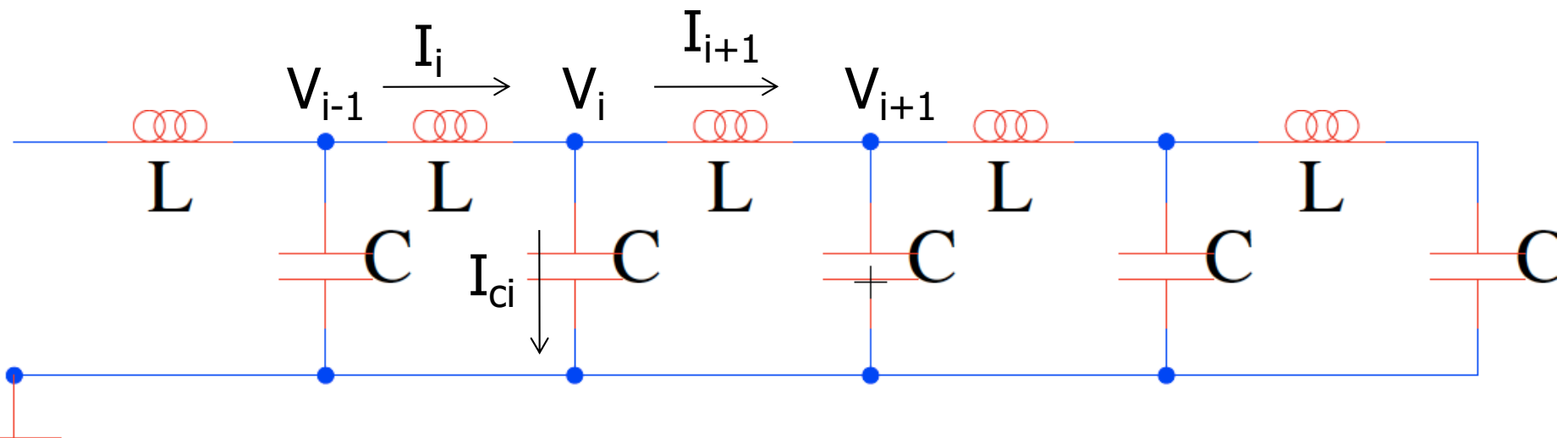- i is a node, but has spatial dimension along the Tline
 - No longer agnostic of wire length
- V_i changes at different positions





Reduce to Single Equation

- Eliminate I ? Differential equation in voltage only.

$$I_i - I_{i+1} = C \frac{dV_i}{dt}$$

- Take derivative with respect to time

$$\frac{dI_i}{dt} - \frac{dI_{i+1}}{dt} = C \frac{d^2V_i}{dt^2}$$



Reduce to Single Equation

$$\frac{dI_i}{dt} - \frac{dI_{i+1}}{dt} = C \frac{d^2 V_i}{dt^2}$$

$$\frac{dV_i}{dx} = -L \frac{dI_i}{dt}$$

□ Eliminate I_s ?



Reduce to Single Equation

$$\frac{dI_i}{dt} - \frac{dI_{i+1}}{dt} = C \frac{d^2 V_i}{dt^2}$$

$$\frac{dV_i}{dx} = -L \frac{dI_i}{dt}$$

$$\frac{dV_{i+1}}{dx} = -L \frac{dI_{i+1}}{dt}$$

□ Eliminate I_s ?

Reduce to Single Equation

$$\frac{dI_i}{dt} - \frac{dI_{i+1}}{dt} = C \frac{d^2V_i}{dt^2}$$

$$\frac{dV_i}{dx} = -L \frac{dI_i}{dt}$$

$$\frac{dV_{i+1}}{dx} = -L \frac{dI_{i+1}}{dt}$$

□ Eliminate Is ?

$$\frac{dI_i}{dt} - \frac{dI_{i+1}}{dt} = C \frac{d^2V_i}{dt^2}$$

$$-\frac{1}{L} \frac{dV_i}{dx} - \left(-\frac{1}{L} \frac{dV_{i+1}}{dx} \right) = C \frac{d^2V_i}{dt^2}$$

$$\frac{dV_{i+1}}{dx} - \frac{dV_i}{dx} = LC \frac{d^2V_i}{dt^2}$$

$$\frac{d^2V_i}{dx^2} = LC \frac{d^2V_i}{dt^2}$$



Implication

- Wave equation:

$$\frac{\partial^2 V}{\partial x^2} = LC \frac{\partial^2 V}{\partial t^2}$$

- Solution:

$$V(x, t) = A + Be^{x-wt}$$

- What is w ?



Implication

- Wave equation:

$$\frac{\partial^2 V}{\partial x^2} = LC \frac{\partial^2 V}{\partial t^2}$$

- Solution:

$$V(x, t) = A + Be^{x-wt}$$

- What is w ?

$$Be^{x-wt} = LCw^2 Be^{x-wt}$$


$$w = \sqrt{\frac{1}{LC}}$$

w is the rate of propagation



Propagation Rate in Example

- $L=1\mu\text{H}$
- $C=1\text{pF}$
- What is w ?

$$w = \frac{1}{\sqrt{LC}}$$

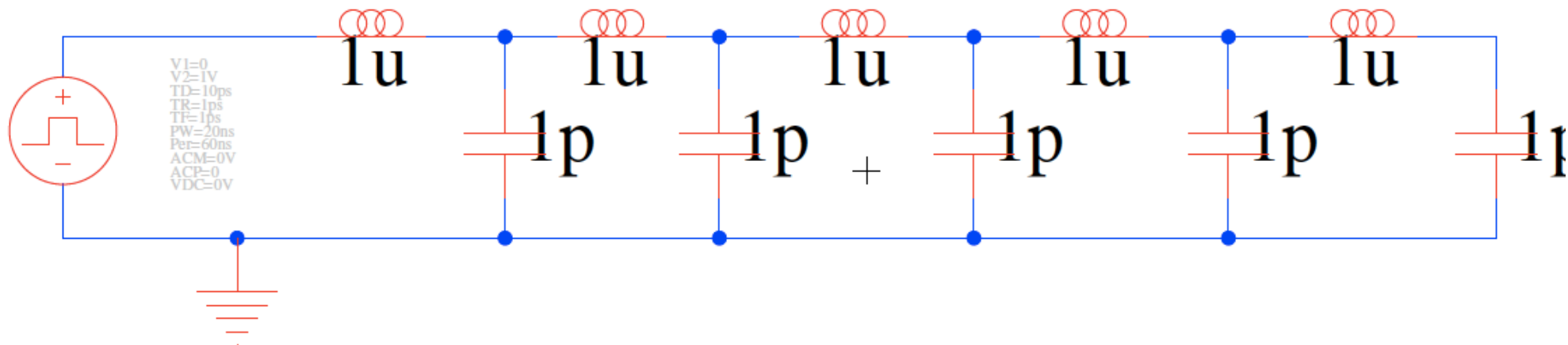


Signal Propagation

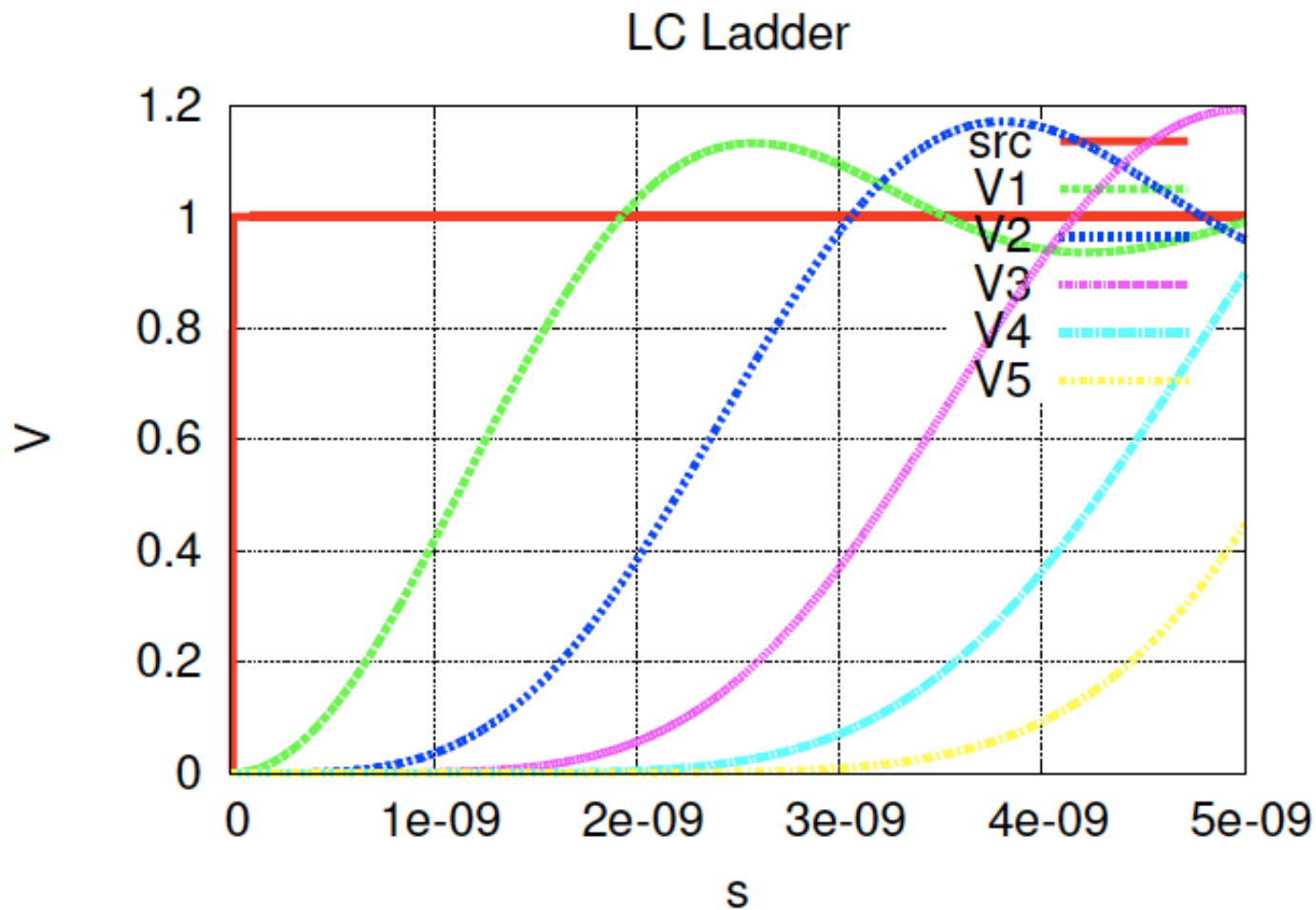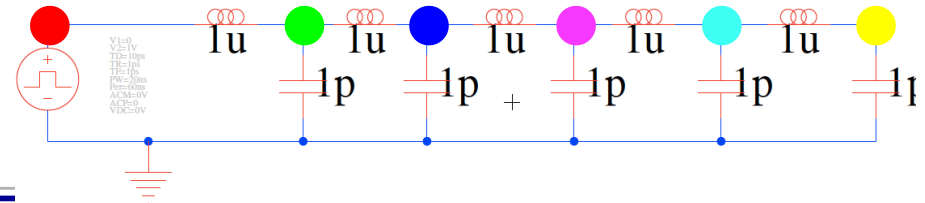




Signal Propagation

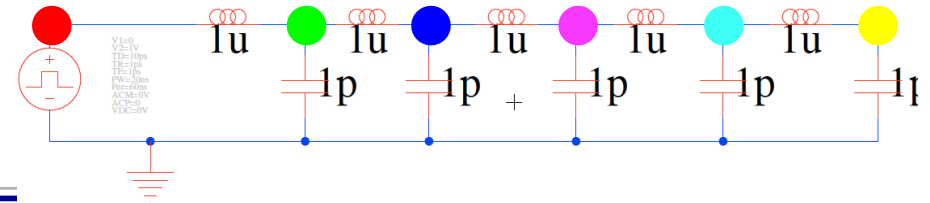


Delay linear in length

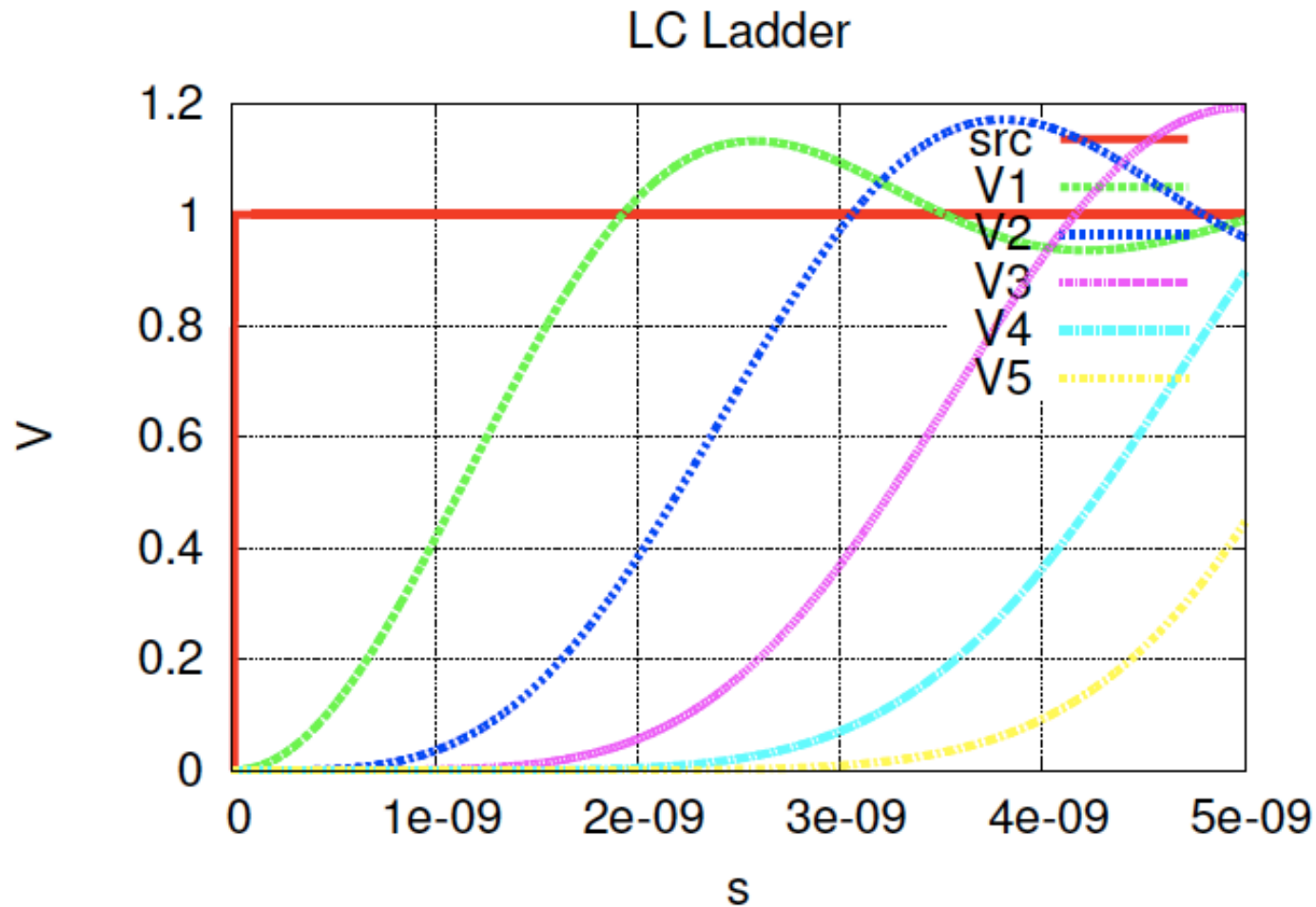




Contrast RC Wire

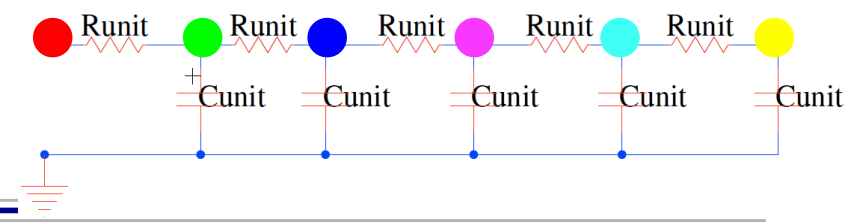

RC wire delay quadratic
in length

RC Ladder

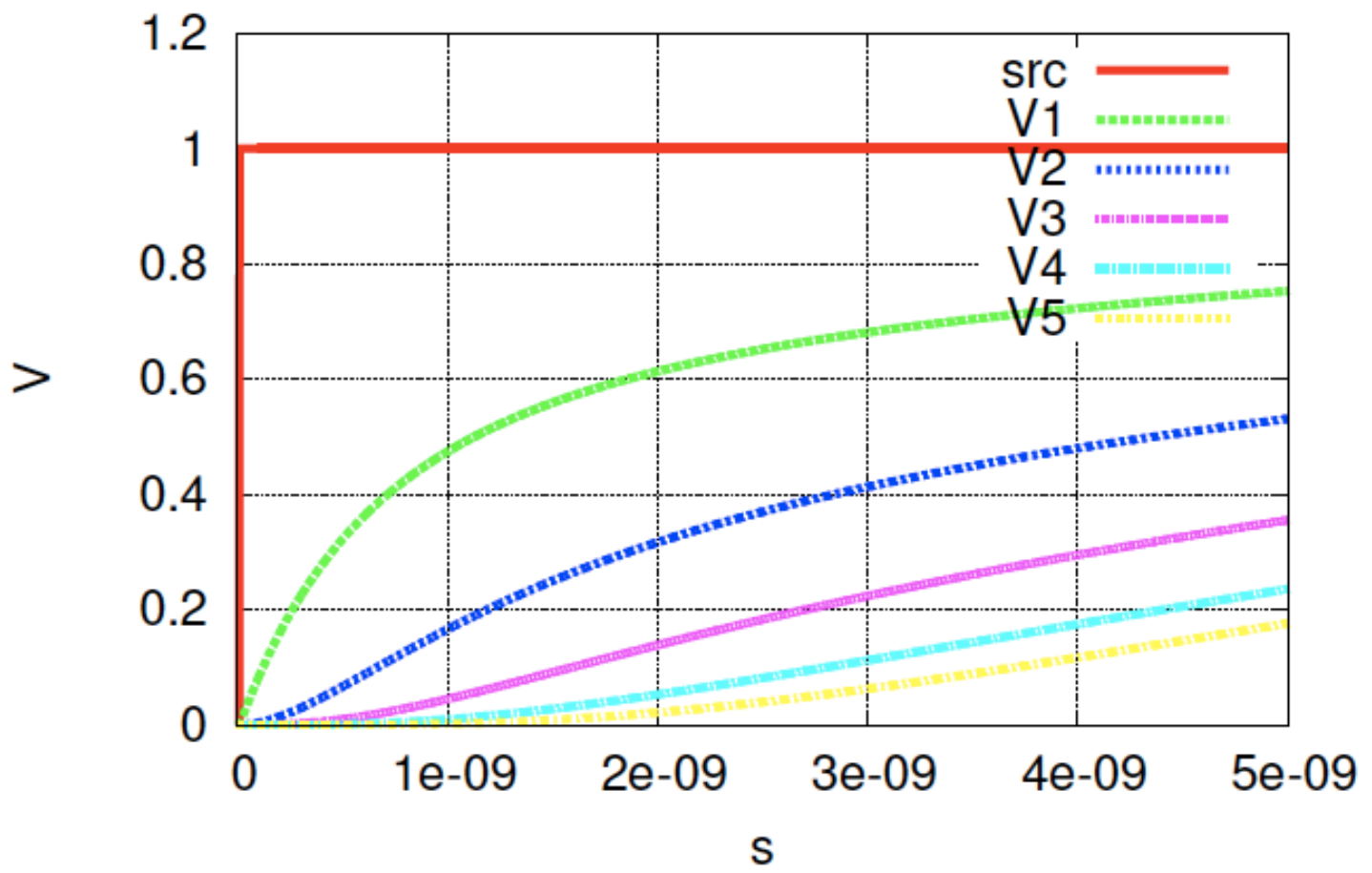



Propagation

- Solution:

$$V(x, t) = A + Be^{x-wt}$$

- Rate of propagation, w :

$$w = \sqrt{\frac{1}{LC}}$$

- Previously:

$$CL = \epsilon\mu$$



Propagation

- Solution:

$$V(x, t) = A + Be^{x-wt}$$

- Rate of propagation, w :

$$w = \sqrt{\frac{1}{LC}}$$

- Previously:

$$CL = \epsilon\mu$$

$$w = \sqrt{\frac{1}{\epsilon\mu}} = \sqrt{\frac{1}{\epsilon_0\epsilon_r\mu_0\mu_r}}$$

$$c^2 = \frac{1}{\epsilon_0\mu_0} \Rightarrow$$

$$w = \frac{c}{\sqrt{\epsilon_r\mu_r}}$$




Longer LC (open)

- ❑ 40 Stages
- ❑ $L=100\text{nH}$
- ❑ $C=1\text{pF}$

$$w = \frac{1}{\sqrt{LC}} = \frac{c_0}{\sqrt{\epsilon_r \mu_r}}$$


Stage delay? How long to propagate?

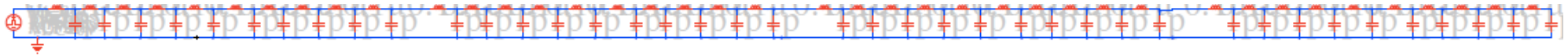

Reflection Teaser: Pulse Travel RC


□ V1,V3,V4,V5,V6 about 10 stages apart

40 stage LC Ladder (open)

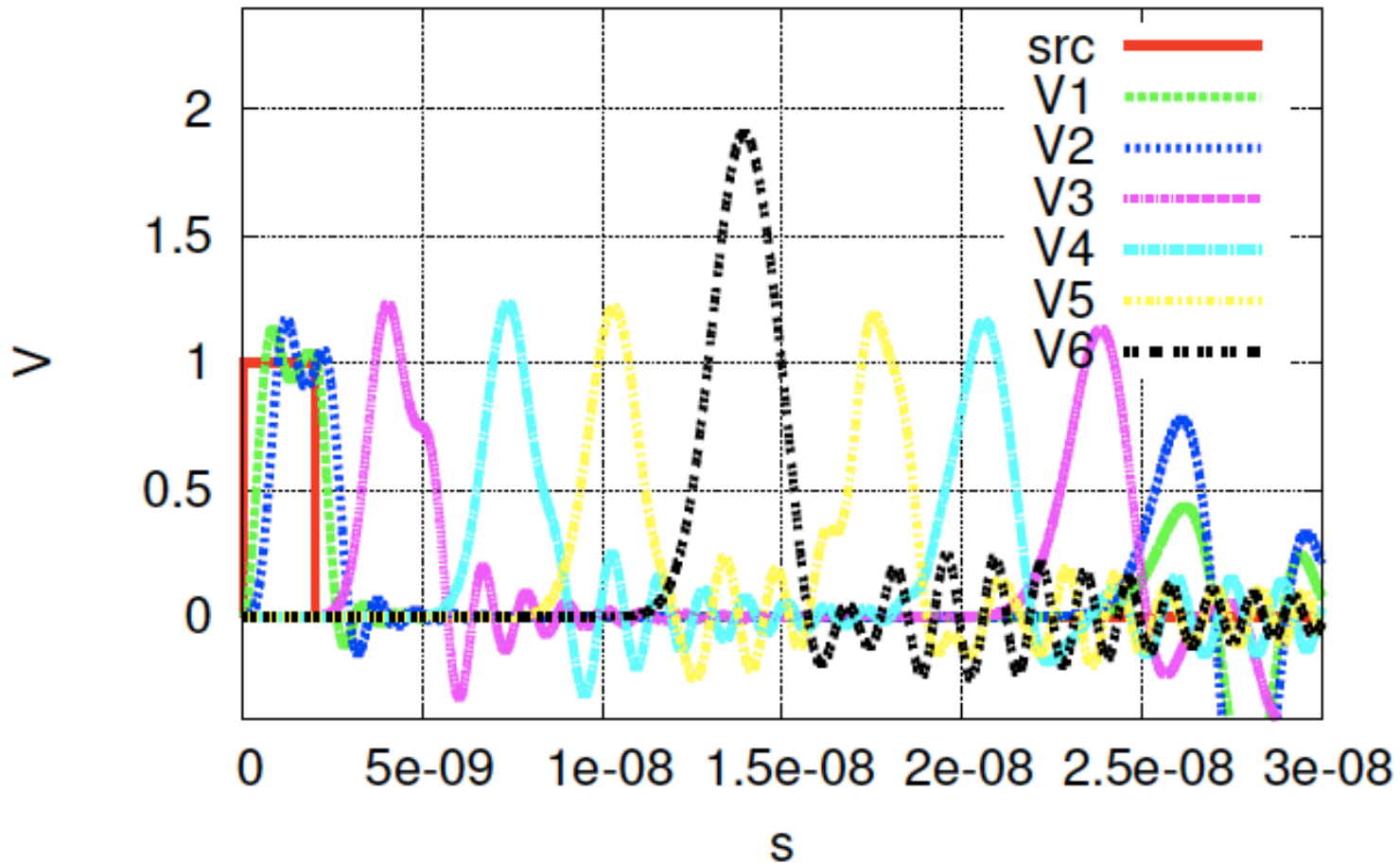

Wire “Resistance”

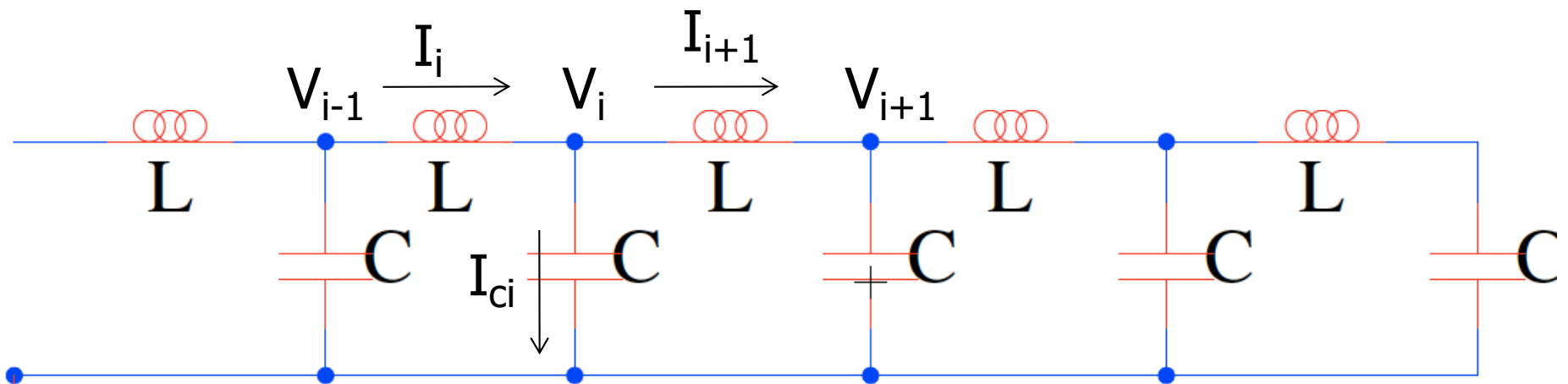- What is the resistance at V_i ?
 - Q needed to charge C to V_i ?
 - I_i given velocity w ?
 - $R = V_i/I_i$?




Wire “Resistance”

- $Q = CV_i$
- $I_i = dQ/dt$
- Moving at rate w
- $I_i = wCV_i$
- $R = V_i/I_i = 1/(wC)$

$$w = \frac{1}{\sqrt{LC}}$$


$$R = \frac{\sqrt{LC}}{C}$$

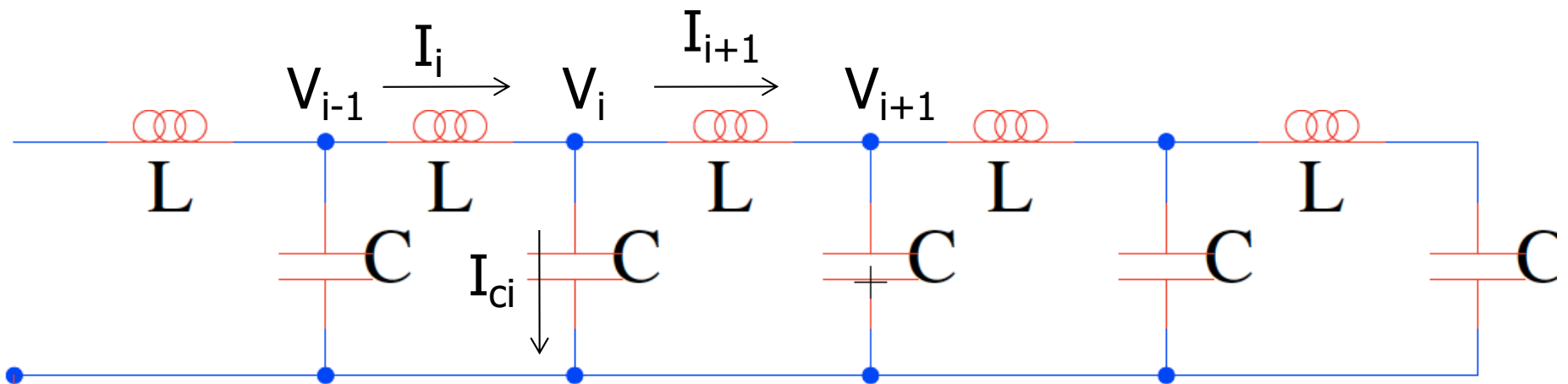

Characteristic Impedance

□ $Z_0 = R$

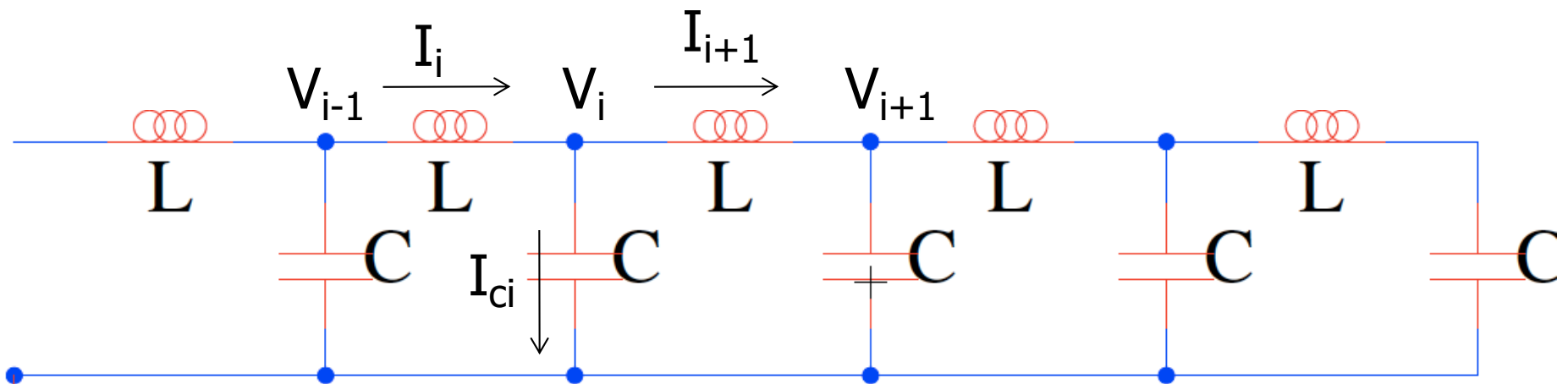
$$R = \frac{\sqrt{LC}}{C} = \sqrt{\frac{L}{C}} = Z_0$$





Impedance

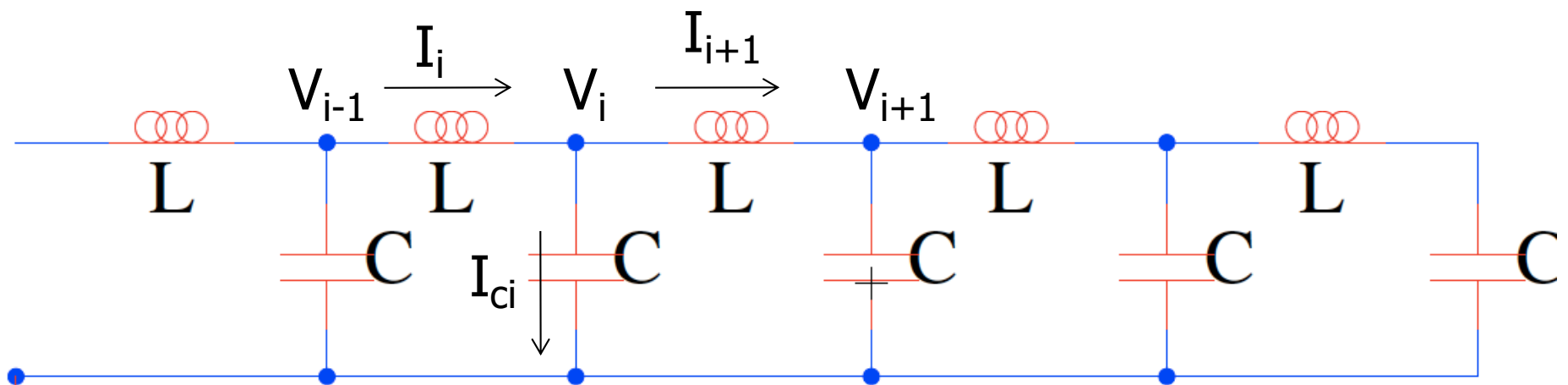- Assuming infinitely long wire, how does the impedance look at V_i , V_{i+1} , V_{i+2} ?






Impedance

- Assuming infinitely long wire, how does the impedance look at V_i , V_{i+1} , V_{i+2} ?

$$Z_0 = \sqrt{\frac{L}{C}}$$

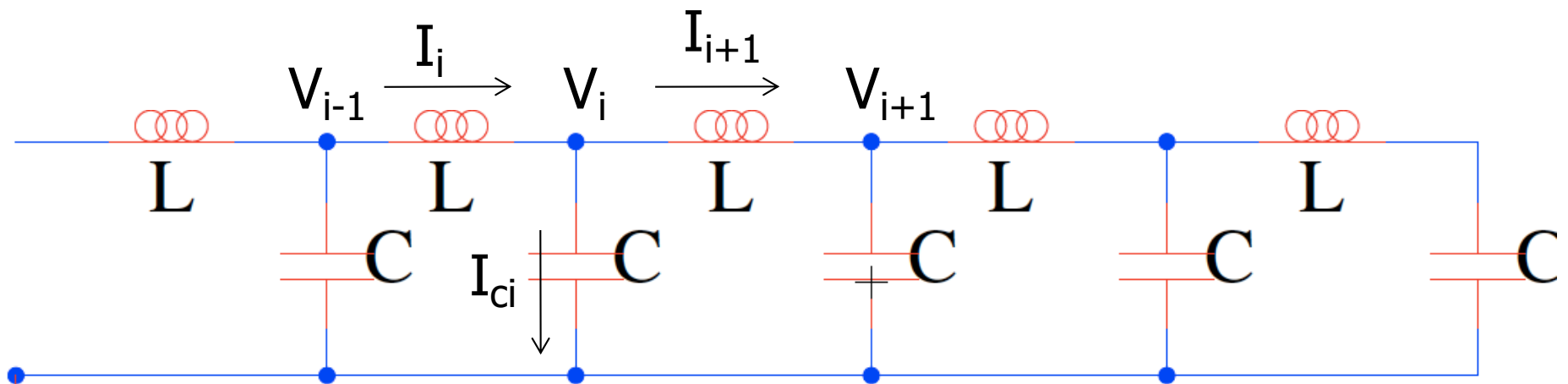



Impedance


- Transmission lines have a characteristic impedance

$$Z_0 = \sqrt{\frac{L}{C}}$$

Infinite Lossless Transmission Line

- Transmission line looks like resistive load

$$Z_0 = \sqrt{\frac{L}{C}}$$

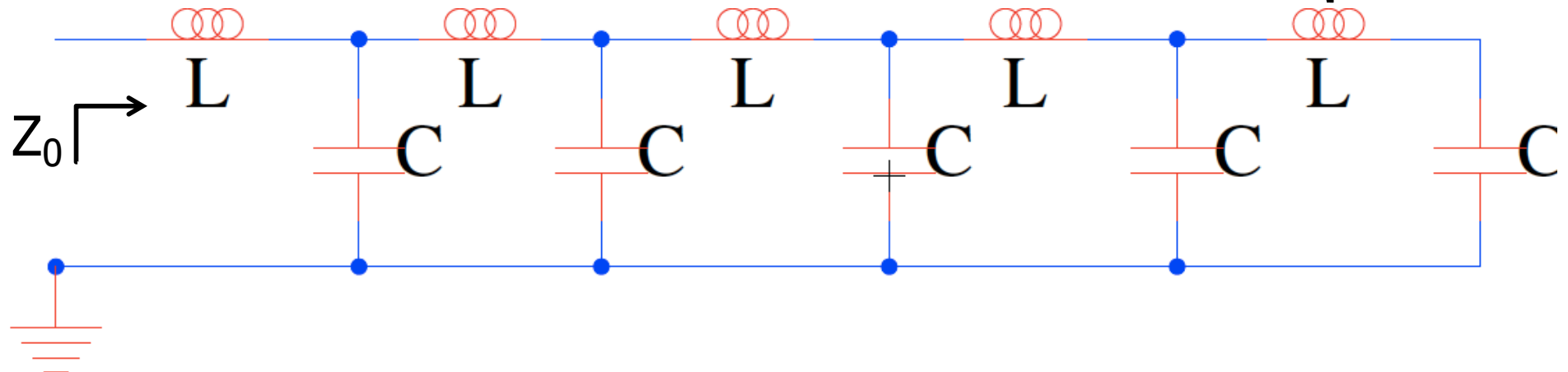

- Input waveform travels down line at velocity
 - Without distortion

$$w = \frac{1}{\sqrt{LC}}$$



Idea

- Signal propagates as wave down transmission line
 - Delay linear in wire length, if resistance negligible
 - Rate of propagation
 - Characteristic impedance

$$w = \frac{1}{\sqrt{LC}} = \frac{c}{\sqrt{\epsilon_r \mu_r}}$$

$$Z_0 = \sqrt{\frac{L}{C}}$$



Admin

- ❑ Project 2 due Friday 12/3
- ❑ HW 7 out on Friday
 - Due 12/10