

ESE370: Circuit-Level Modeling, Design, and Optimization for Digital Systems

Lec 33: December 3, 2021
Transmission Lines Termination



Transmission Line Agenda

- ~~See in action in lab~~
- ~~Where transmission lines arise?~~
- ~~General wire formulation~~
- ~~Lossless Transmission Line~~
- ~~Impedance~~
- End of Transmission Line?
 - Open, short, matched
- Termination
- Discuss Lossy
- Implications



Reminder: Propagation

- Signal propagates as wave down transmission line
 - Delay linear in wire length, if resistance negligible
 - Solution:

$$V(x, t) = A + Be^{x-wt}$$


- Rate of propagation (characteristic frequency), w :

$$w = \sqrt{\frac{1}{LC}} = \frac{c}{\sqrt{\epsilon_r \mu_r}}$$

Infinite Lossless Transmission Line

- Transmission line looks like resistive load

$$Z_0 = \sqrt{\frac{L}{C}}$$

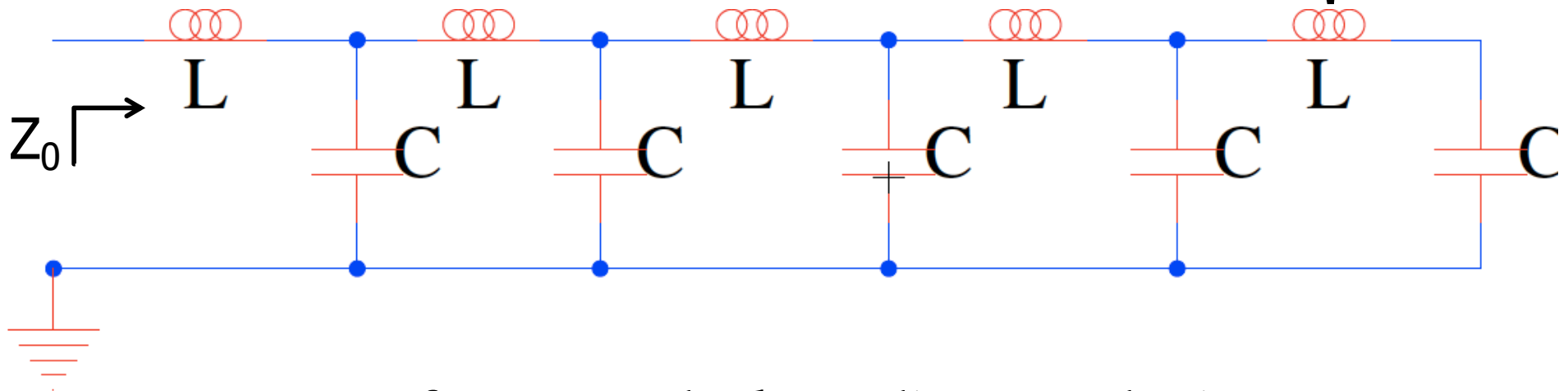

- Input waveform travels down line at velocity
 - Without distortion

$$w = \frac{1}{\sqrt{LC}}$$




End of Line


- What happens at the end of the transmission line?
 - Short Circuit
 - Terminate with $R=Z_0$
 - Open Circuit

- What did the reflections look like in each case in lab?


Open

 


LC Ladder

 


Short

 


LC Ladder (short)

 

Terminate $R=Z_0$

 

LC Ladder

 


Longer LC (open)

- ❑ 40 Stages
- ❑ $L=100\text{nH}$
- ❑ $C=1\text{pF}$

$$w = \frac{1}{\sqrt{LC}} = \frac{c_0}{\sqrt{\epsilon_r \mu_r}}$$



Stage delay? How long to propagate?

 

- ❑ Drive with 2ns Pulse
- ❑ No termination (open circuit)
 - What reflection do we expect?



Pulse Travel RC

□ V1,V3,V4,V5,V6 about 10 stages apart

  

Analyze End of Line

  
- Incident Wave, Reflected Wave, Transverse Wave



Source: https://en.wikipedia.org/wiki/Reflection_coefficient


Analyze End of Line

 - Incident wave $V_i = I_i \times Z_0$
- @ $T - \delta$ V_i is voltage on line
- V_t is what goes forward
 - Voltage seen by end of line at T
- V_r is the reflected voltage that starts moving back towards source at $T + \delta$




Analyze End of Line (Preclass 1)

 - Incident wave $V_i = I_i \times Z_0$
- KCL @ end of line
- KVL @ end of line
- $V = IR$ relationships?
 - Which resistances go with each V ?
- Relate all three V 's using R, Z_0




Analyze End of Line (Preclass 1a)

 - Incident wave $V_i = I_i \times Z_0$
- KCL @ end of line
 - KCL: $I_i = I_r + I_t$




Analyze End of Line (Preclass 1a)

 - Incident wave $V_i = I_i \times Z_0$
- KCL: $I_i = I_r + I_t$
- KVL @ end of line
 - KVL: $V_i + V_r = V_t$




Analyze End of Line (Preclass 1b)

 - ❑ Incident wave $V_i = I_i \times Z_0$
- ❑ KCL: $I_i = I_r + I_t$
- ❑ KVL: $V_i + V_r = V_t$
- ❑ $V = IR$ relationships?
 - Which resistances go with each V ?
 - $V_r = I_r \times Z_0 \rightarrow I_r = V_r / Z_0$
 - $V_t = I_t \times R \rightarrow I_t = V_t / R$
 - $V_i = I_i \times Z_0 \rightarrow I_i = V_i / Z_0$



Analyze End of Line

 - Incident wave $V_i = I_i \times Z_0$
- KCL: $I_i = I_r + I_t$
- KVL: $V_i + V_r = V_t$
- $V_r = I_r \times Z_0 \rightarrow I_r = V_r / Z_0$
- $V_t = I_t \times R \rightarrow I_t = V_t / R$
- $V_i = I_i \times Z_0 \rightarrow I_i = V_i / Z_0$



$$\frac{V_i}{Z_0} = \frac{V_r}{Z_0} + \frac{V_t}{R}$$

Analyze End of Line (Preclass 1c)

□ $V_i + V_r = V_t$ $\frac{V_i}{Z_0} = \frac{V_r}{Z_0} + \frac{V_t}{R}$

□ Eliminate V_t

Analyze End of Line (Preclass 1c)

□ $V_i + V_r = V_t$ $\frac{V_i}{Z_0} = \frac{V_r}{Z_0} + \frac{V_t}{R}$

□ Eliminate V_t

$$\frac{V_i}{Z_0} = \frac{V_r}{Z_0} + \frac{V_i + V_r}{R}$$

$$RV_i = RV_r + Z_0(V_i + V_r)$$

$$V_i(R - Z_0) = V_r(R + Z_0)$$

$$V_r = \left(\frac{R - Z_0}{R + Z_0} \right) V_i \text{ Reflection coefficient}$$



Analyze End of Line

□ $V_i + V_r = V_t$


$$V_i + V_i \left(\frac{R - Z_0}{R + Z_0} \right) = V_t$$

$$V_i \left(1 + \frac{R - Z_0}{R + Z_0} \right) = V_t$$

$$V_i \left(\frac{2R}{R + Z_0} \right) = V_t$$

Reflection


 
- Sanity check with previous
 - Short
 - Matched
 - Open



$$V_i \left(\frac{R - Z_0}{R + Z_0} \right) = V_r$$

Pulse Travel RC


□ V1,V3,V4,V5,V6 about 10 stages apart

  




Visualization

- <https://tinyurl.com/y2jortrq>

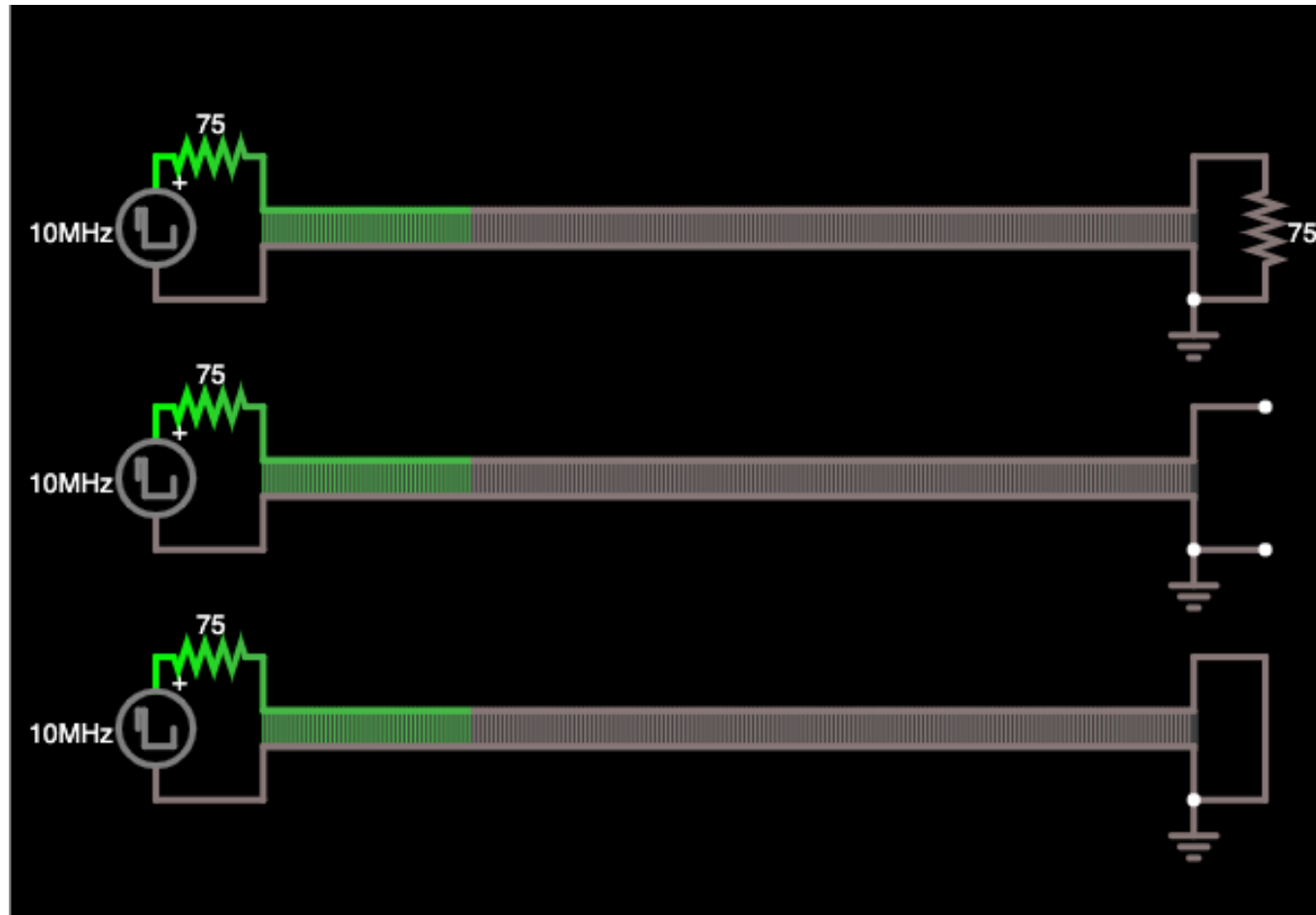

 

Back to Source



Back at Source? (Preclass 2)

- What happens at source?
 - Depends on how it's terminated
 - Looks like a sink end now




$$R \neq Z_0$$

- What happens?
 - 75 Ω termination on 50 Ω line


Transmission Line Symbol

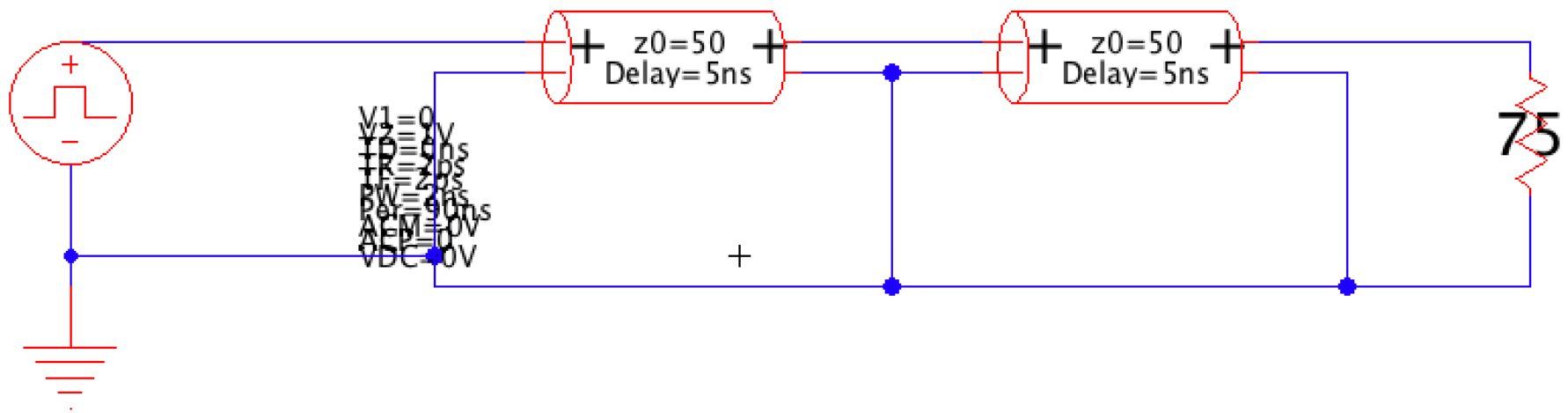- ❑ Specify delay of full Tline and characteristic impedance
- ❑ Need reference




Simulation (Preclass 3)

 
- For these, with direct drive from voltage source
 - Source looks like short circuit (not typical of CMOS)
 - Source cannot be changed



50Ω line, 75Ω termination

 


Mismatch Termination

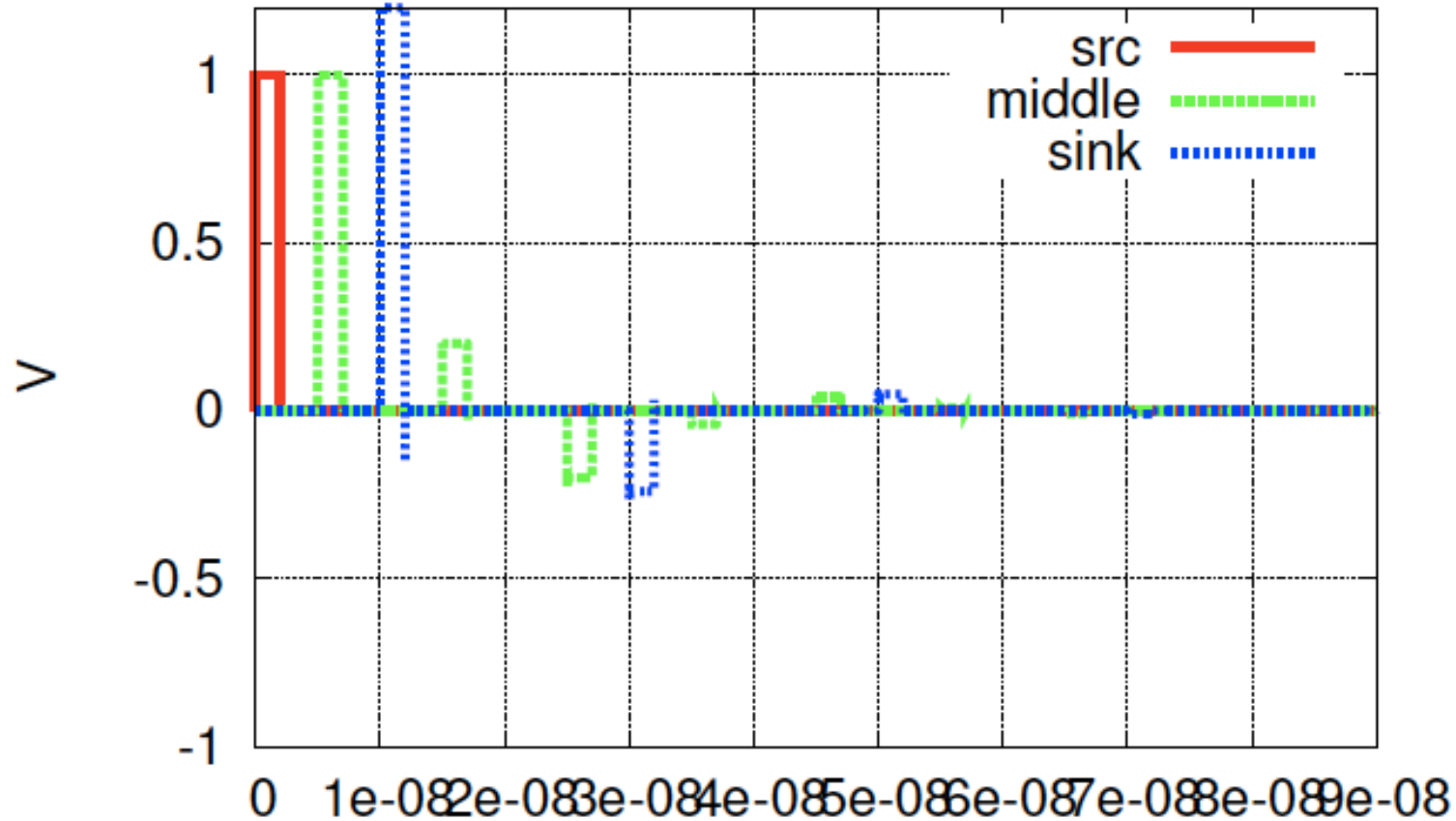


$$V_r = V_i \left(\frac{R - Z_0}{R + Z_0} \right) = V_i \left(\frac{75 - 50}{75 + 50} \right) = 0.2V_i$$

Source Series Termination


□ What happens here?

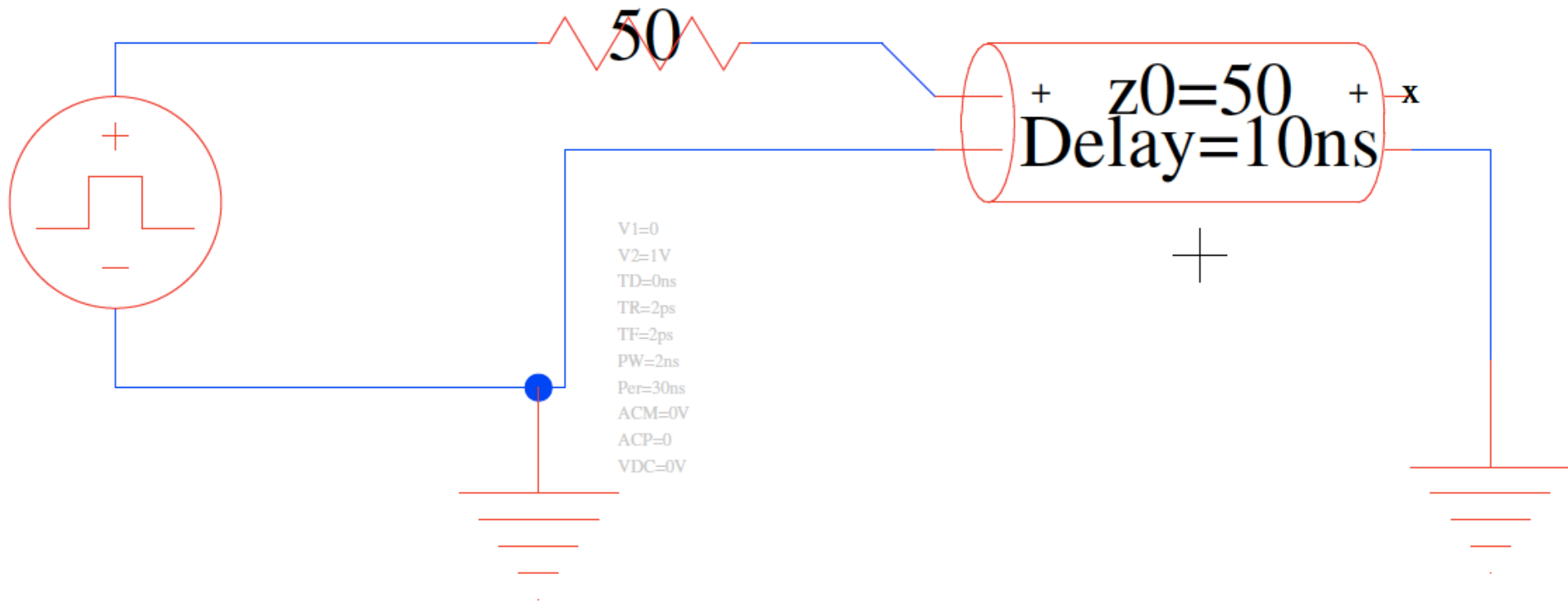

Simulation


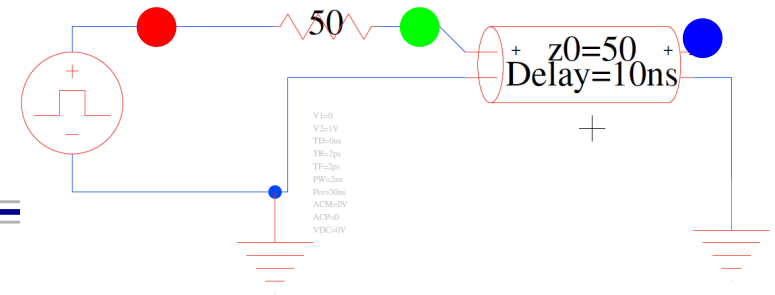


Series Terminated Transmission Line

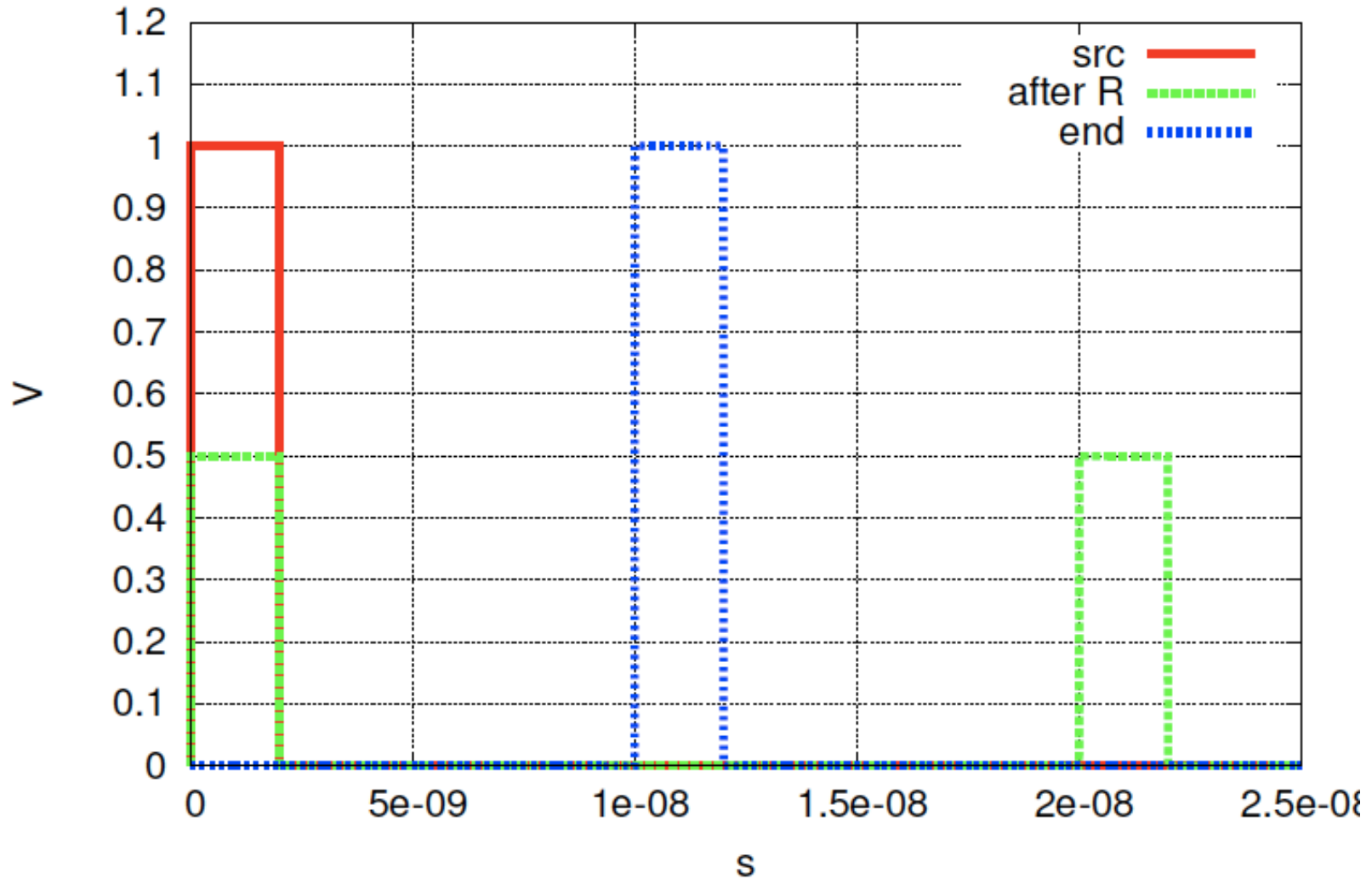

Series Termination

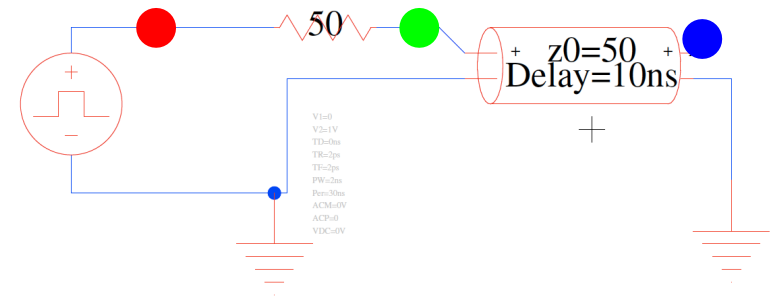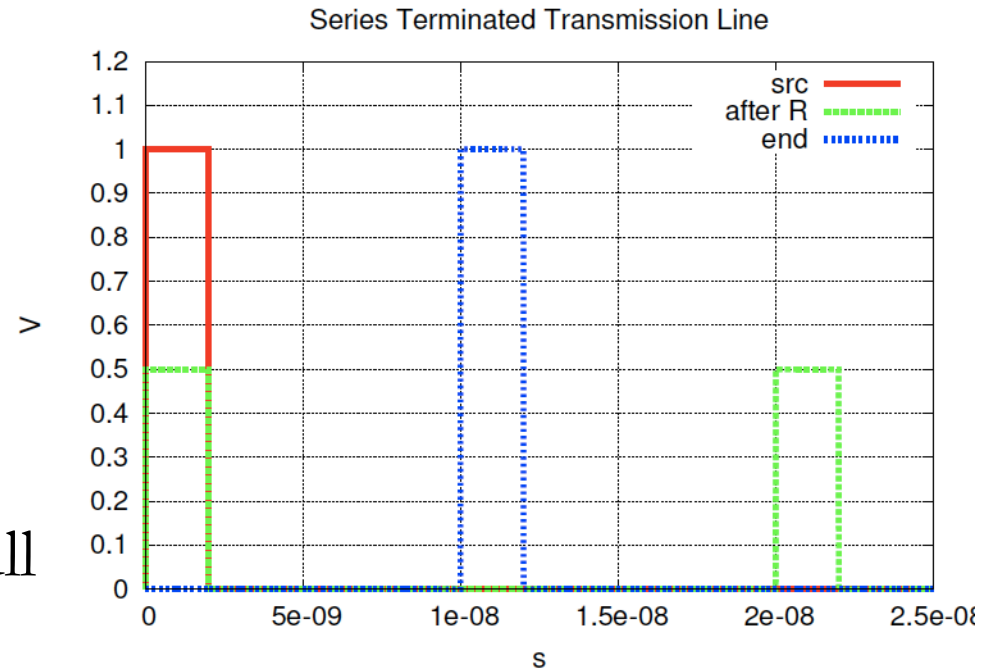
- ❑ $R_{\text{series}} = Z_0$
- ❑ Initial voltage divider
 - Half voltage pulse propagates down Tline
- ❑ End of line open circuit
 - Sees single transition to full voltage (full reflection)
- ❑ Reflection returns to source and sees termination $R_{\text{series}} = Z_0$
- ❑ No further reflections






Termination Cases

- Termination in parallel at Sink

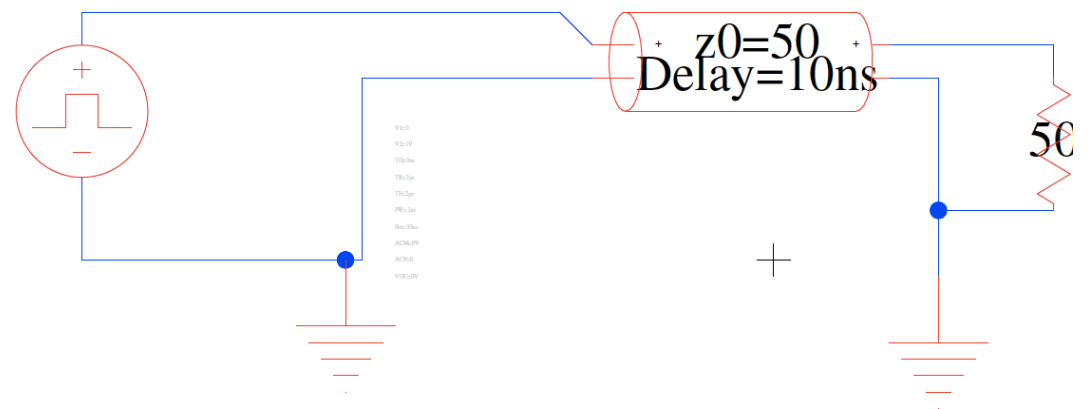


- Termination in series at Source

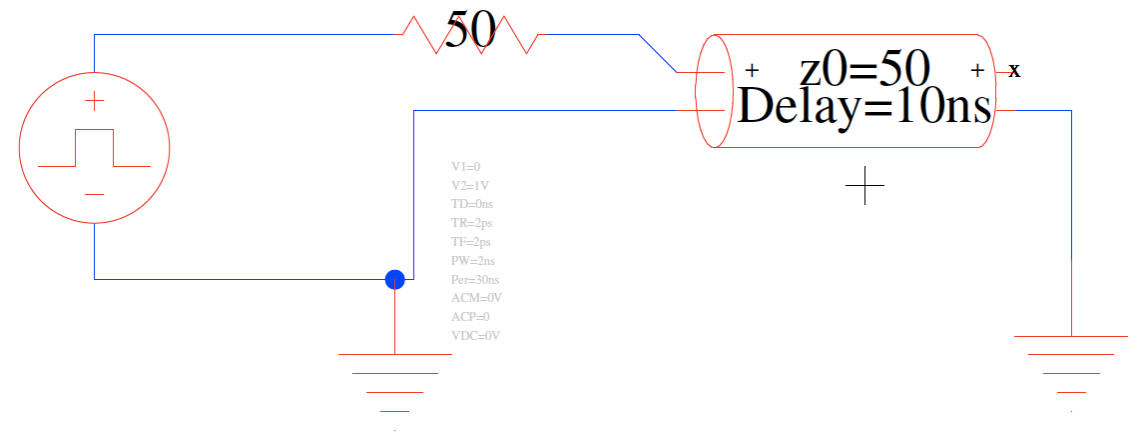


CMOS Driver / Receiver

 - Driver: What does a CMOS driver look like at the source?
 - $I_{d,sat} = 1200\mu\text{A}/\mu\text{m}$ @ 45nm, $V_{dd} = 1\text{V}$
- Receiver: What does a CMOS inverter look like at the sink?



CMOS Driver

 
- Driver: What does a CMOS driver look like at the source?
- $I_{d,sat} = 1200\mu\text{A}/\mu\text{m}$ @ 45nm, $V_{dd} = 1\text{V}$
- Min size:
 - $I_{drive} = 1200\mu\text{A}/\mu\text{m} * 45\text{nm} = 54\mu\text{A}$
 - $R_{out} = V_{dd}/I_{drive} = 18\text{k}\Omega$



CMOS Driver

□ Driver: What does a CMOS driver look like at the source?

 - $I_{d,sat} = 1200\mu\text{A}/\mu\text{m}$ @ 45nm, $V_{dd} = 1\text{V}$
- Min size:
 - $I_{drive} = 1200\mu\text{A}/\mu\text{m} * 45\text{nm} = 54\mu\text{A}$
 - $R_{out} = V_{dd}/I_{drive} = 18\text{k}\Omega$
- $W = 370$
 - $I_{drive} = 1200\mu\text{A}/\mu\text{m} * 45\text{nm} * 370 = 20\text{mA}$
 - $R_{out} = V_{dd}/I_{drive} = 50\Omega$



Idea

- Signal propagates as wave down transmission line
 - Delay linear in wire length
 - Speed
 - Impedance
- Behavior at end of line depends on termination
- Both src and sink are “ends” with reflections



$$w = \frac{1}{\sqrt{LC}} = \frac{c_0}{\sqrt{\epsilon_r \mu_r}}$$

$$Z_0 = \sqrt{\frac{L}{C}}$$

$$V_r = V_i \left(\frac{R - Z_0}{R + Z_0} \right)$$

Tline Examples (Preclass 4)

□ Will start with these next lecture

  



Admin

□ Proj 2

- EXTENDED: due Sunday 12/5 @ midnight
- No late days allowed

□ HW 7

- Due Friday 12/10
- Out now