

# ESE370: Circuit-Level Modeling, Design, and Optimization for Digital Systems

---

Lec 34: December 6, 2021

Transmission Lines

Implications



# Transmission Line Agenda

---


- ~~See in action in lab~~
- ~~Where transmission lines arise?~~
- ~~General wire formulation~~
- ~~Lossless Transmission Line~~
- ~~Impedance~~
- ~~End of Transmission Line?~~
  - ~~Open, short, matched~~
- Physical Geometry
- Discuss Lossy
- Implications/Effects

# Reminder: Transmission Line

- Data travels as waves
- Line has Impedance
- May reflect at end of line

$$w = \frac{1}{\sqrt{LC}} = \frac{c_0}{\sqrt{\epsilon_r \mu_r}}$$

$$Z_0 = \sqrt{\frac{L}{C}}$$

 


$$V_i \left( \frac{R - Z_0}{R + Z_0} \right) = V_r$$

$$V_i \left( \frac{2R}{R + Z_0} \right) = V_t$$


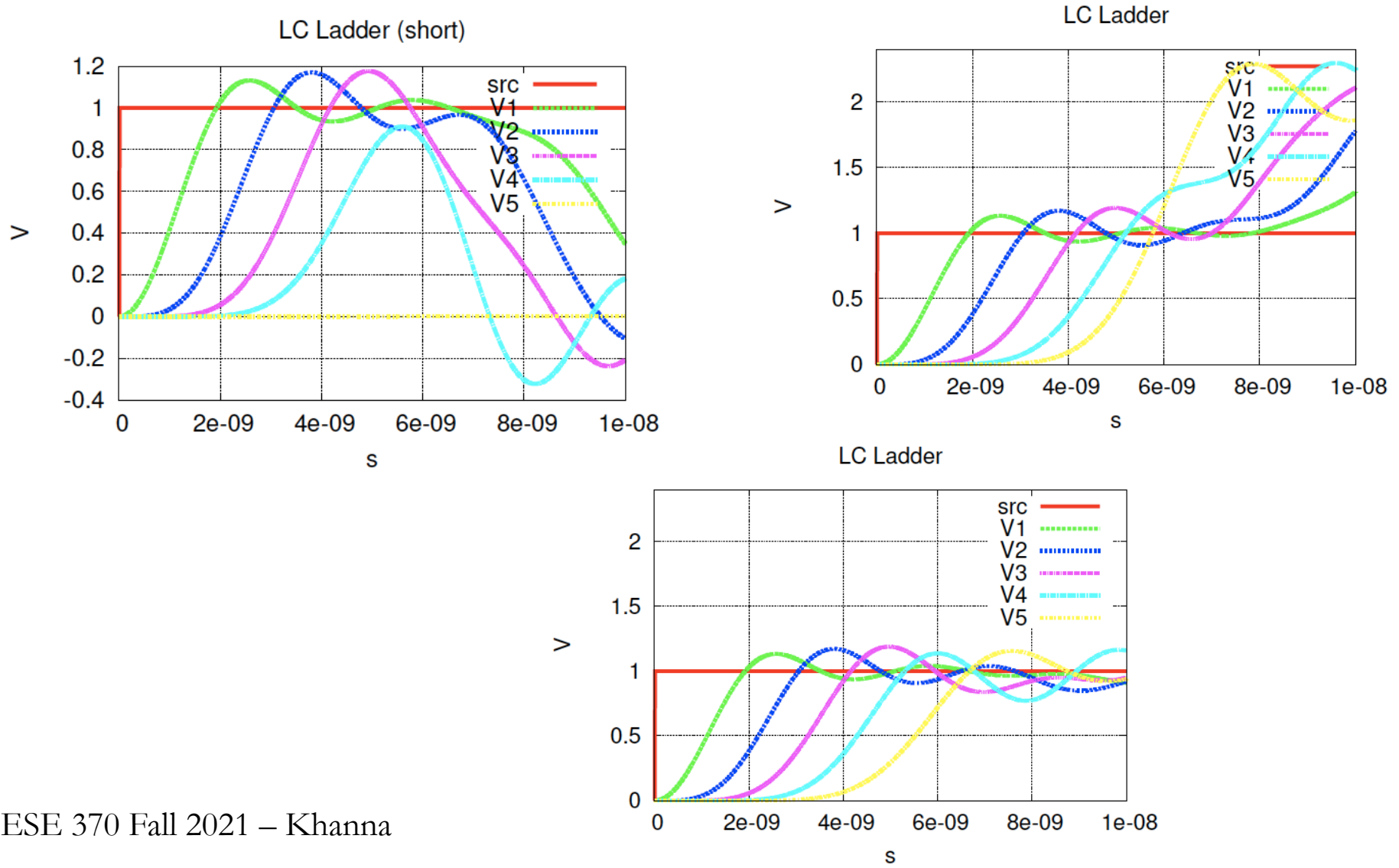
# Reminder: End of Line


□ What happens at the end of the transmission line?






# Termination Cases

- Termination in parallel at Sink

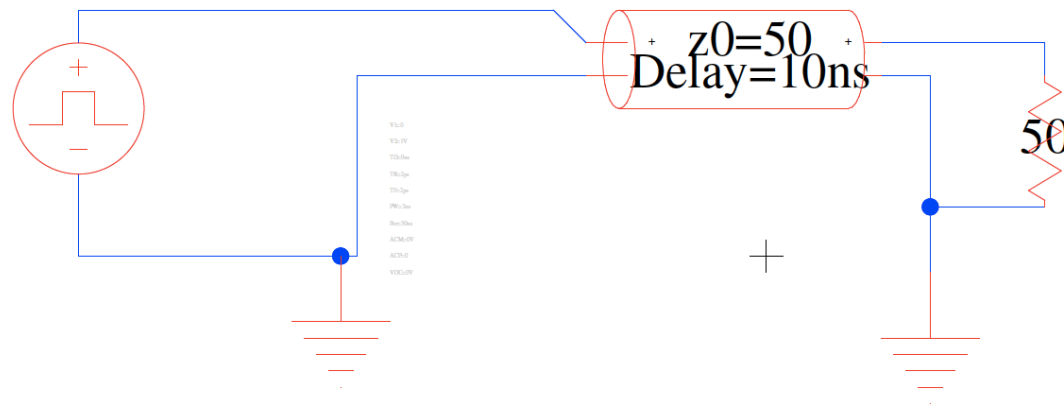

- Termination in series at Source

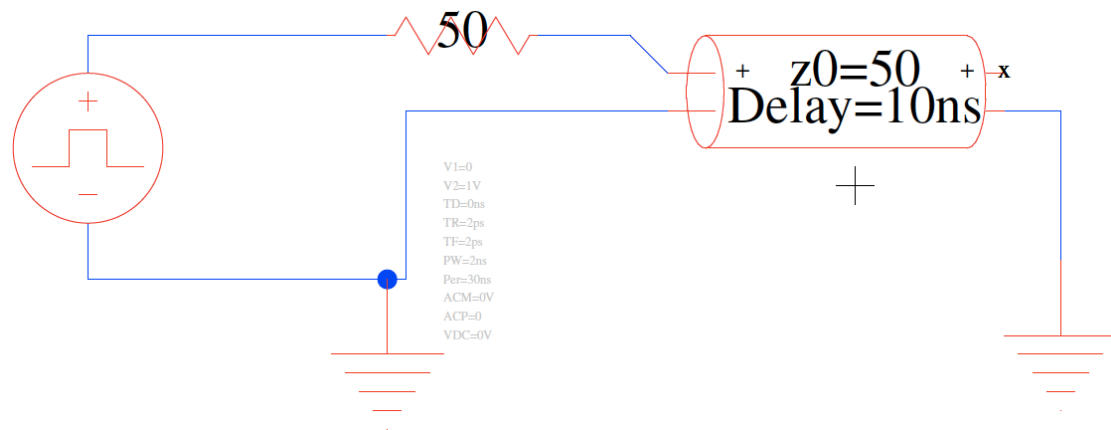


# Transmission Lines Specifics

---

Characteristics arise from their geometry
 
# Coaxial Cable

- ❑ Inner core conductor: radius  $r$
- ❑ Insulator: out to radius  $R$
- ❑ Outer core shield (ground)



$$L = \left( \frac{\mu}{2\pi} \right) \ln \left( \frac{R}{r} \right) \quad Z_0 = \left( \frac{1}{2\pi} \right) \left( \sqrt{\frac{\mu}{\epsilon}} \right) \ln \left( \frac{R}{r} \right)$$



- ❑ RG-58  $Z_0 = 50\Omega$  – networking
- ❑ RG-59  $Z_0 = 75\Omega$  – video
- ❑ HDMI  $Z_0 = 100\Omega$  – video



# Printed Circuit Board

## □ Stripline

- Trace between ground planes

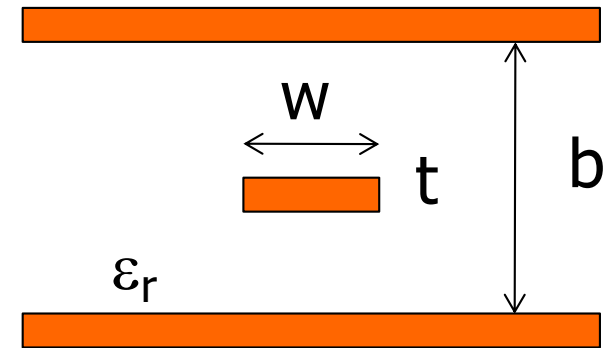
 


$$Z_0 = \left(\frac{1}{4}\right) \left(\sqrt{\frac{\mu}{\epsilon}}\right) \ln\left(\frac{1 + W/b}{t/b + W/b}\right)$$


  
# Printed Circuit Board

- Microstrip line
  - Trace over single supply plane



$$Z_0 = \left( \frac{1}{2\pi} \right) \left( \sqrt{\frac{\mu}{(0.475\epsilon_r + 0.67)\epsilon_0}} \right) \ln \left( \frac{4h}{0.536W + 0.67t} \right)$$



# Twisted Pair

---

- Category 5 ethernet cable
  - $Z_0=100\Omega$
  - $w=0.64c_0$



# Implications

---

(you should be able to reason about this)



## Example (Preclass 2)

---

- ❑ 25 meter category-5e cable ( $Z_0=100\Omega$ ,  $w=0.64c$ )
  - $c = 3 \times 10^8$  m/s
- ❑ Supporting 1Gb/s ethernet
  - 4 pairs at 250Mb/s
- ❑ a) Time to send data from one end to the other?
- ❑ b) Time between bits at 250Mb/s?
- ❑ c) Bits on each pair in the cable?



# Pipeline Bits

---

- For properly terminated transmission line
  - Do not need to wait for bits to arrive at sink
  - Can stick new bits onto wire



# Limits to Bit Pipelining (Preclass 3)


---

- What limits? (why only 250Mb/s)

# Limits to Bit Pipelining (Preclass 3)
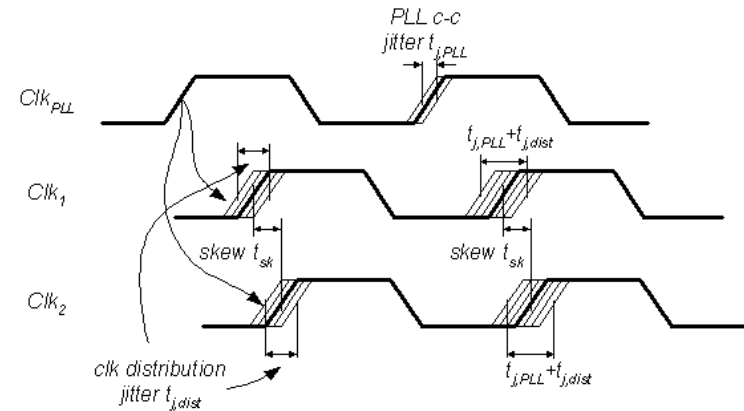
## □ What limits? (why only 250Mb/s)

- Risetime/signal distortion
- Clocking
  - Skew
  - Jitter
- For bus
  - Wire length differences between lines





 
# Eye Diagrams

---



- ❑ Watch bits over line on scope
  - Look at distortion
  - “open” eye clean place to sample
    - Consistent timing of transitions
    - Well defined high/low voltage levels




  
# Construct Eye Diagram

- ❑ Generate an input bit sequence pattern that contains all possible combinations of  $B$  bits (e.g.,  $B=3$  or  $4$ ), so a sequence of  $2^{B*B}$  bits. (Otherwise, a random sequence of comparable length is fine.)
- ❑ Transmit the corresponding discrete time sequence  $x[n]$  over the channel ( $2^{B*B*N}$  samples, if there are  $N$  samples/bit)





- ❑ Instead of one long plot of  $y[n]$ , plot the response as an eye diagram:
  - a. break the plot up into short segments, each containing  $K*N$  samples, starting at sample  $0, K*N, 2K*N, 3K*N, \dots$  (e.g.,  $K=2$  or  $3$  # bits at a time)
  - b. plot all the short segments on top of each other


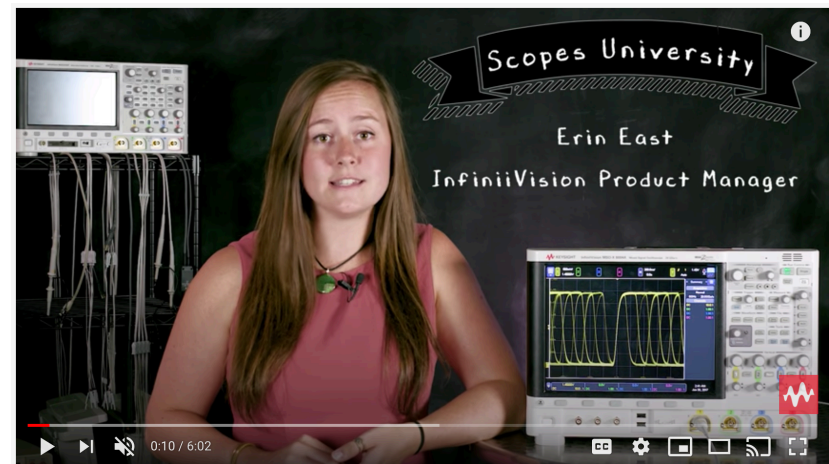 
# Eye Diagrams

- ❑ Watch bits over line on scope
  - Look at distortion
  - “open” eye clean place to sample
    - Consistent timing of transitions
    - Well defined high/low voltage levels





<https://www.youtube.com/watch?v=mnugUjaMN70>



  
# Eye Diagrams

- ❑ Watch bits over line on scope
  - Look at distortion
  - “open” eye clean place to sample
    - Consistent timing of transitions
    - Well defined high/low voltage levels




# Interpretation of Eye Diagram

 



# Bad “eye”

---

 







# Receiver Deconvolution

---

 



# Receiver Deconvolution

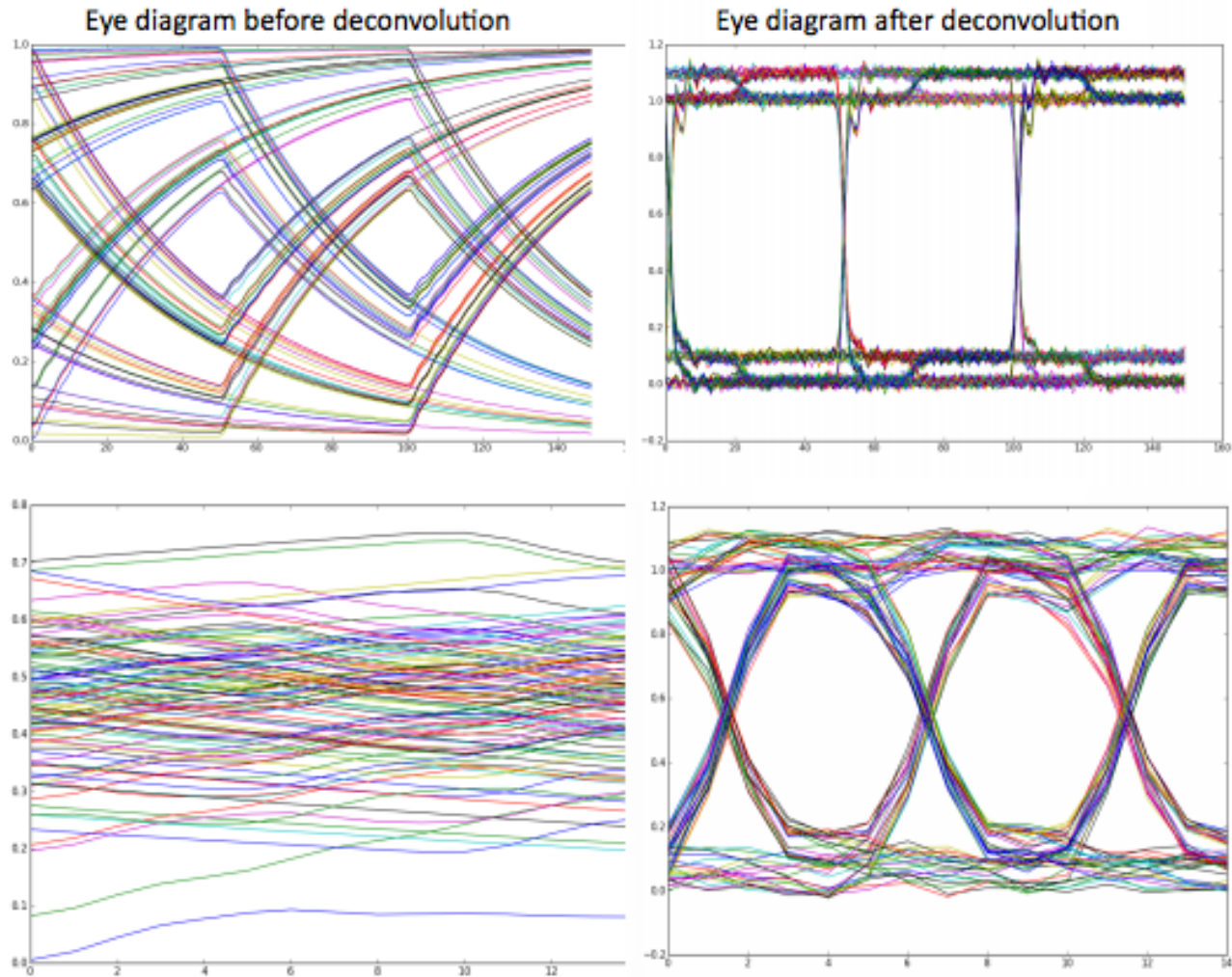



# Termination / Mismatch



---

- ❑ Wires do look like these transmission lines
- ❑ We are terminating them in some way when we connect to chip (gate)
  - Need to be deliberate about how terminate, if we care about high performance



  
# Where is Mismatch?

- ❑ Vias
- ❑ Wire corners
- ❑ Branches
- ❑ Connectors
- ❑ Board-to-cable
- ❑ Cable-to-cable



 
# Lossless Transmission Line

- What prevents us from having a 500km cat-5 cable?


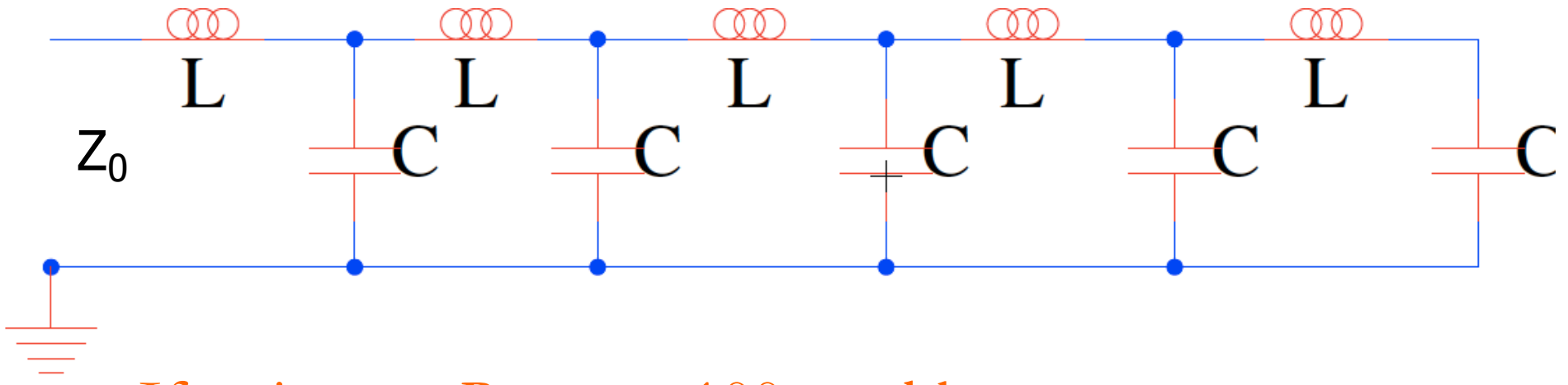
# Lossless Transmission Line


- How to measure resistance across a cable?



- If resistance  $R$  across 100m cable, what is resistance across 200m cable?
 
# Lossy Transmission Line (Preclass 4)

- How do addition of R's change?
  - Concretely, discretely think about  $R=0.2\Omega$  every meter on  $Z_0=100\Omega$ 
    - what does each R do? Voltage impact?




# Lossy Transmission Line

- Each  $R$  is a mismatched termination

$$V_t = V_i \left( \frac{2(R + Z_0)}{(R + Z_0) + Z_0} \right)$$

- Each  $R$  is a voltage divider

 
$$V_{i+1} = V_t \left( \frac{Z_0}{R + Z_0} \right)$$


 
# Lossy Transmission Line

$$V_{i+1} = V_i \left( \frac{2(R + Z_0)}{(R + Z_0) + Z_0} \right) \left( \frac{Z_0}{R + Z_0} \right)$$


$$V_{snk} = V_{src} \left( \left( \frac{2(R + Z_0)}{(R + Z_0) + Z_0} \right) \left( \frac{Z_0}{R + Z_0} \right) \right)^N$$


 
# Lossy Transmission Line (Preclass 4)


- How long before drop voltage by half?  
R=0.2Ω every meter on Z<sub>0</sub>=100Ω

$$V_{snk} = V_{src} \left( \left( \frac{2(R + Z_0)}{(R + Z_0) + Z_0} \right) \left( \frac{Z_0}{R + Z_0} \right) \right)^N$$


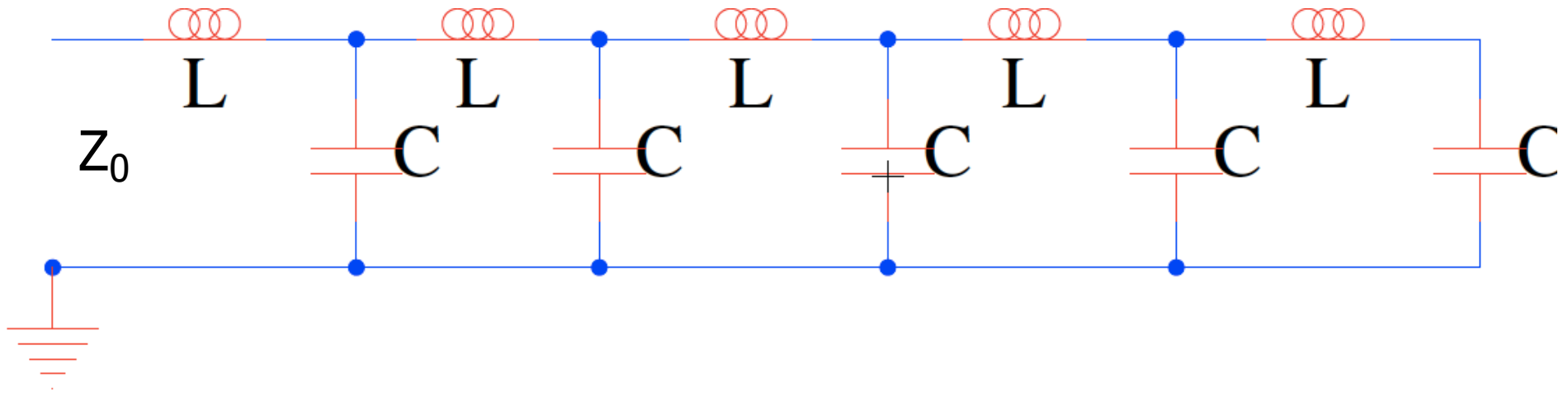
# Lossless Transmission Line

- What prevents us from having a 500km cat-5 cable?
  - Not actually lossless!






# More Examples...

---

Time Permitting
 
# Impedance Change (Preclass 5)

- What happens if there is an impedance change in the wire?  $Z_0=75\Omega$ ,  $Z_1=50\Omega$ 
  - What reflections and transmission do we get?



# $Z_0=75, Z_1=50$ (Preclass 5)


□ At junction:

■ Reflects

■  $V_r = (50-75)/(50+75)V_i = -0.2V_i$

■ Transmits

■  $V_t = (100/(50+75))V_i = 0.8V_i$

 

$$V_i \left( \frac{R - Z_0}{R + Z_0} \right) = V_r$$

$$V_i \left( \frac{2R}{R + Z_0} \right) = V_t$$

# Impedance Change $Z_0=75$ , $Z_1=50$ (Preclass 5)


At junction:

Reflects


$$V_r = -0.2V_i$$

Transmits


$$V_t = 0.8V_i$$

 


Mismatch Transmission Line

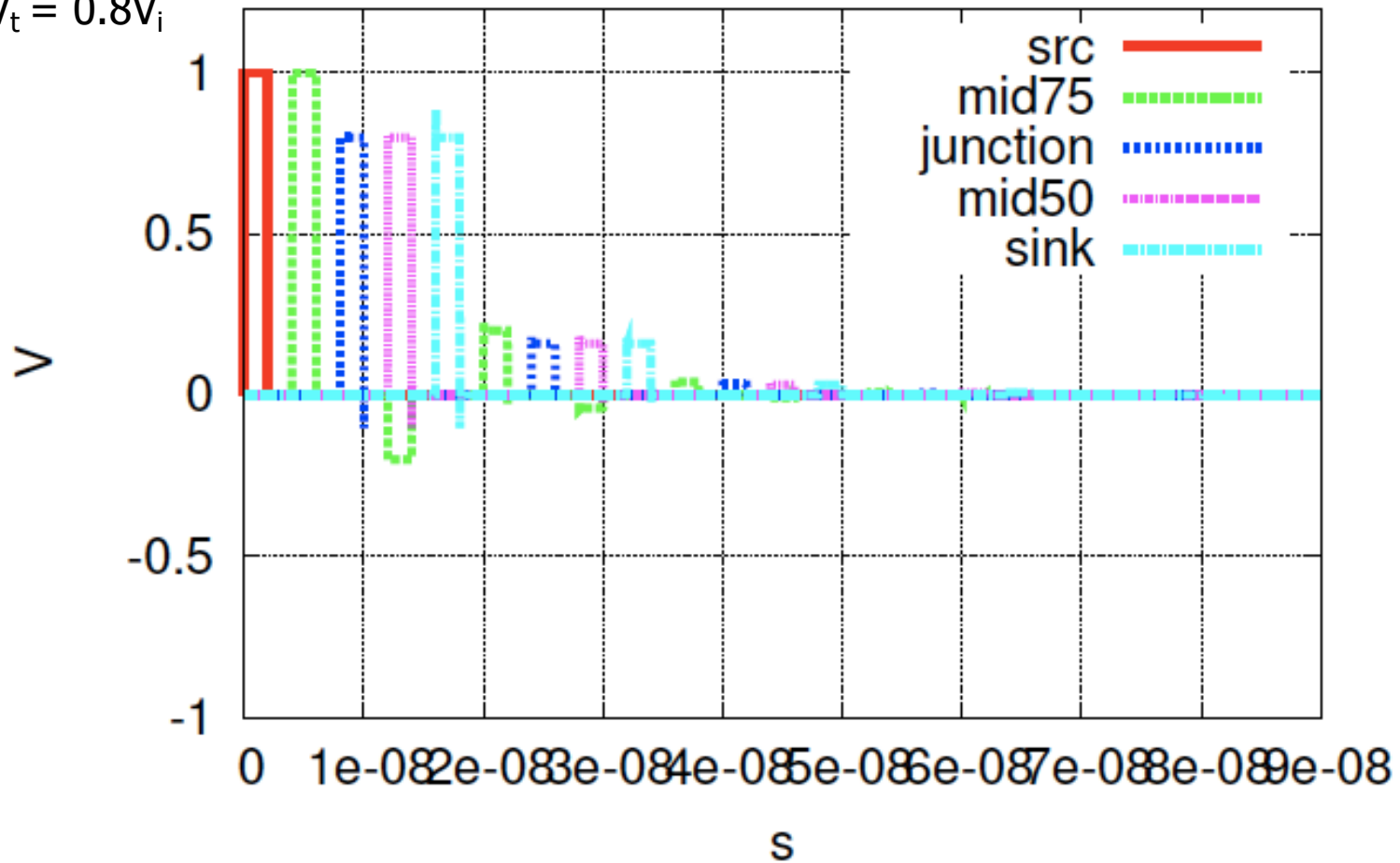

# What happens at branch?

 


Assume all  $50\Omega$

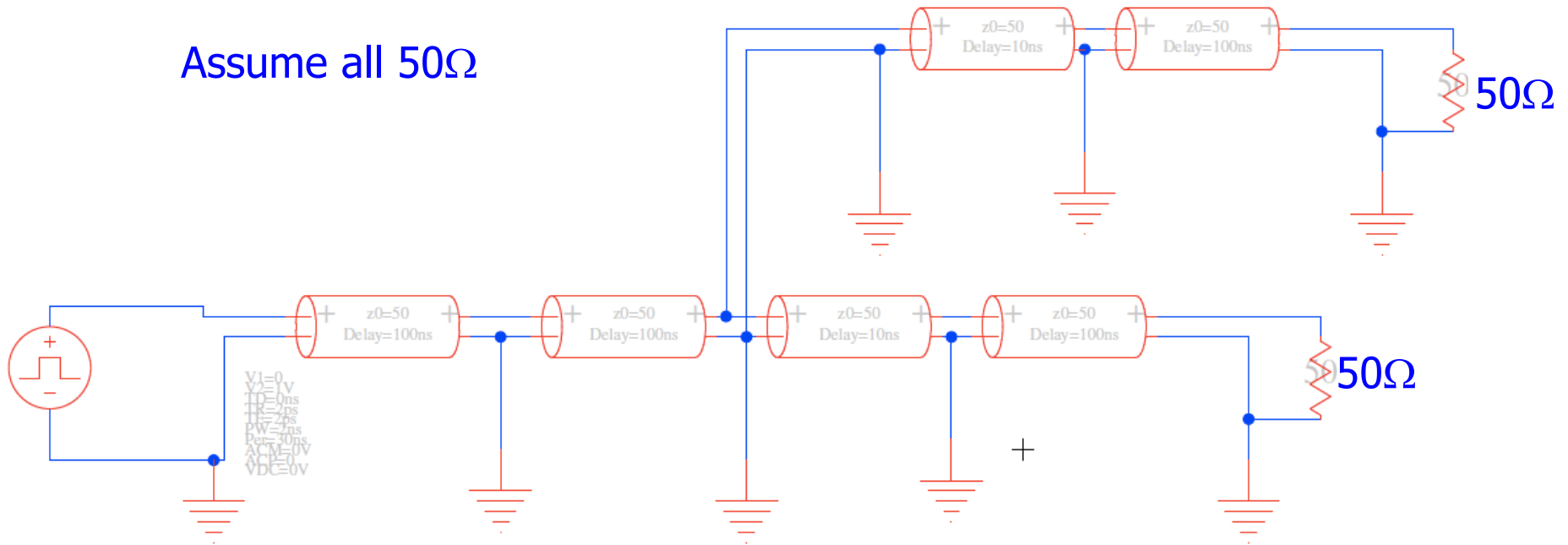


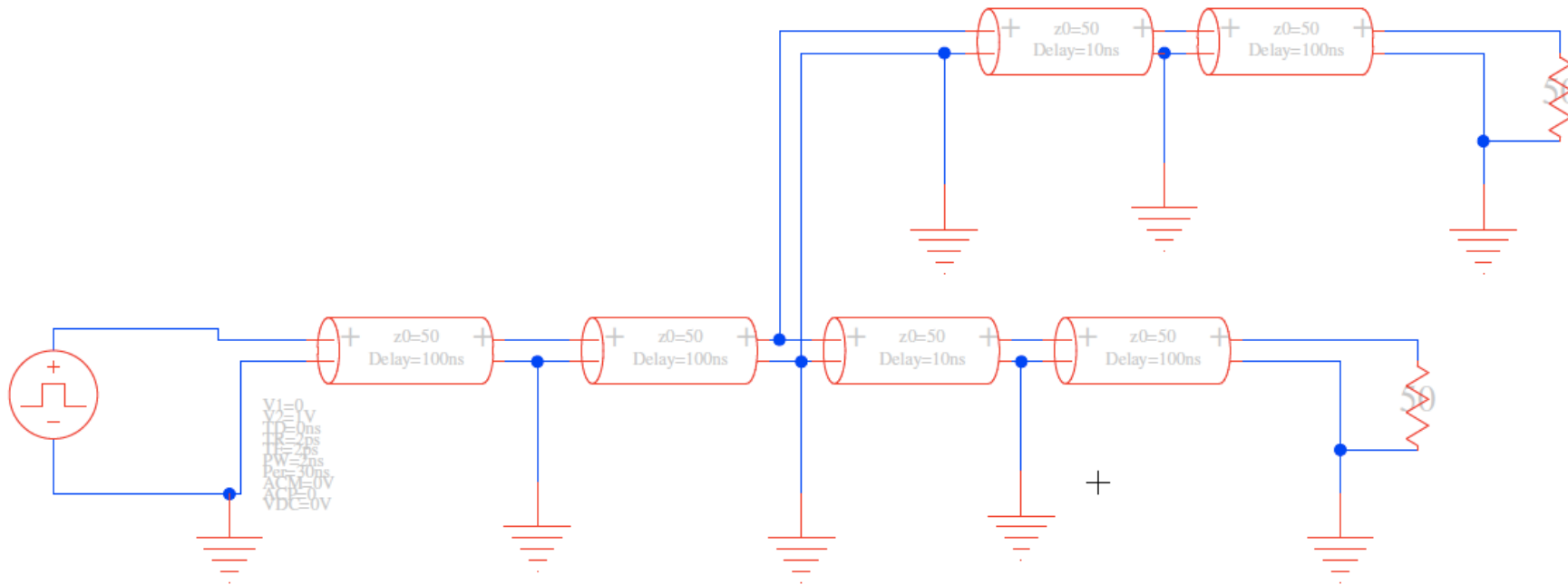
# Branch

- Transmission line sees two  $Z_0$  in parallel
  - Looks like  $Z_0/2$



$$Z_0 = 50, Z_1 = 25$$


□ At junction:

■ Reflects

■  $V_r = (25 - 50) / (25 + 50) V_i = -0.33 V_i$

■ Transmits

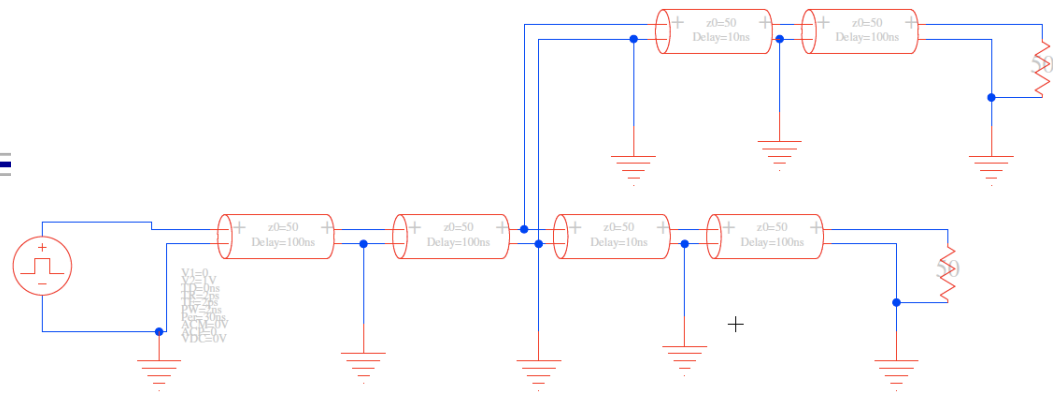■  $V_t = (50 / (25 + 50)) V_i = 0.67 V_i$




$$V_i \left( \frac{R - Z_0}{R + Z_0} \right) = V_r$$

$$V_i \left( \frac{2R}{R + Z_0} \right) = V_t$$
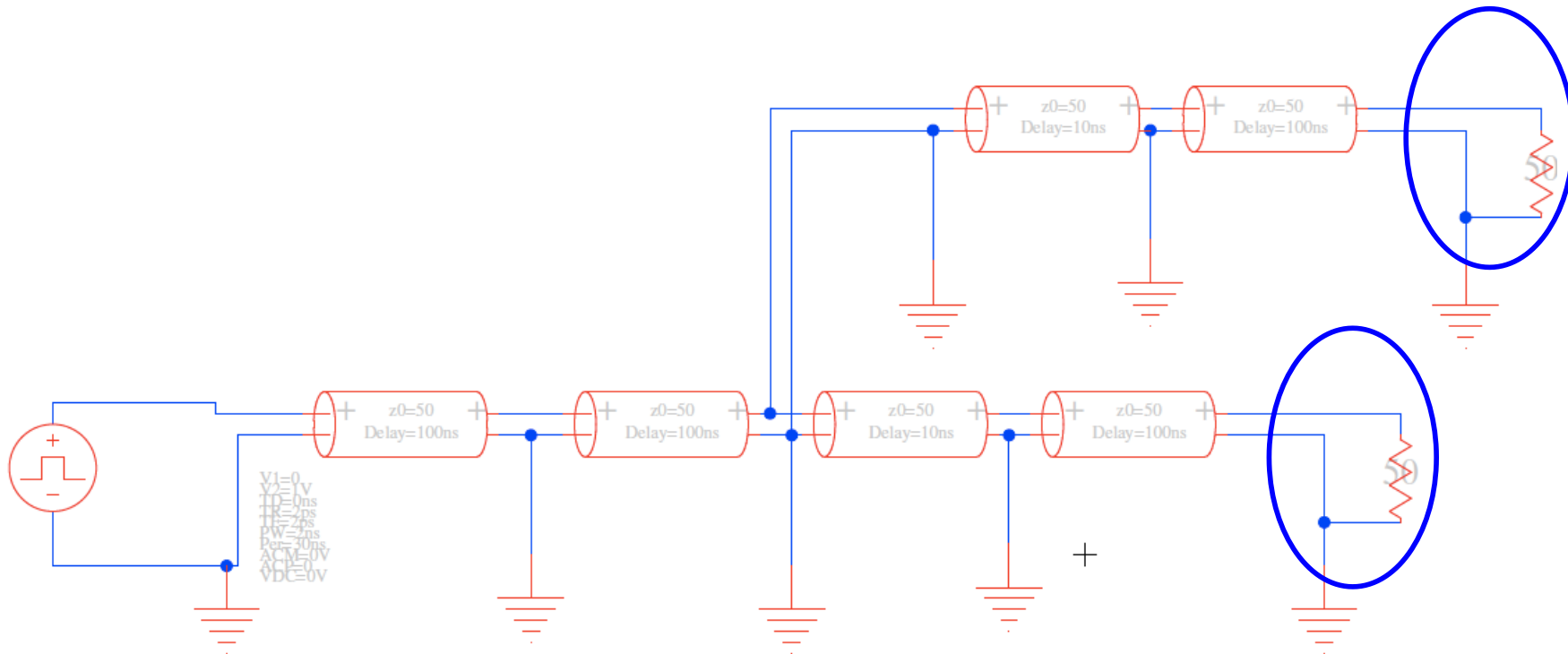
# End of Branch


- ❑ What happens at end?
- ❑ If ends in matched, parallel termination
  - No further reflections







# Branch Simulation

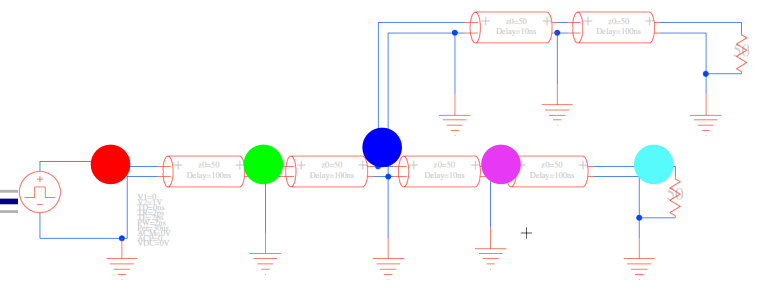

At junction:


Reflects

$$V_r = -0.33V_i$$

Transmits


$$V_t = 0.67V_i$$

### Branch Line Termination

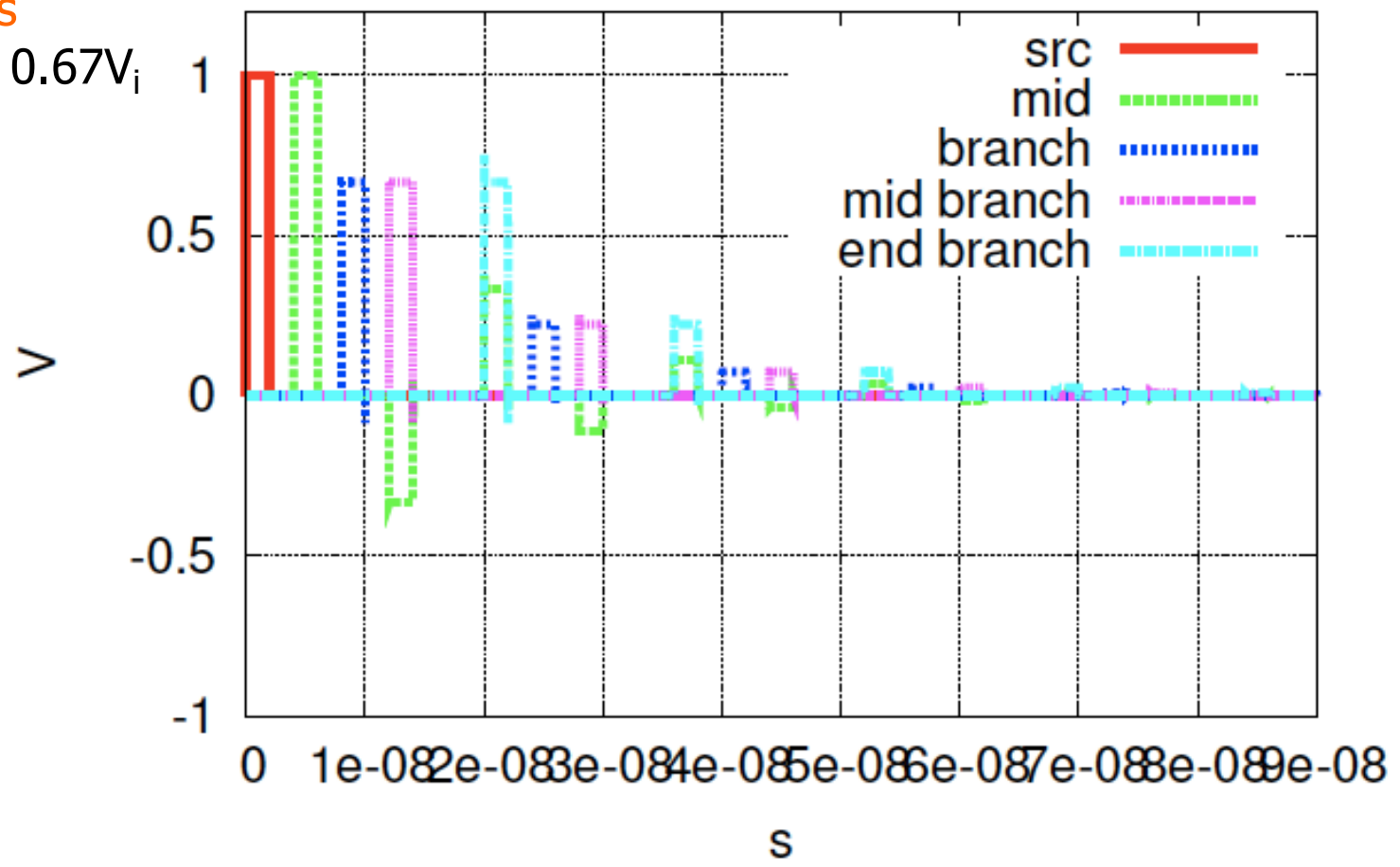

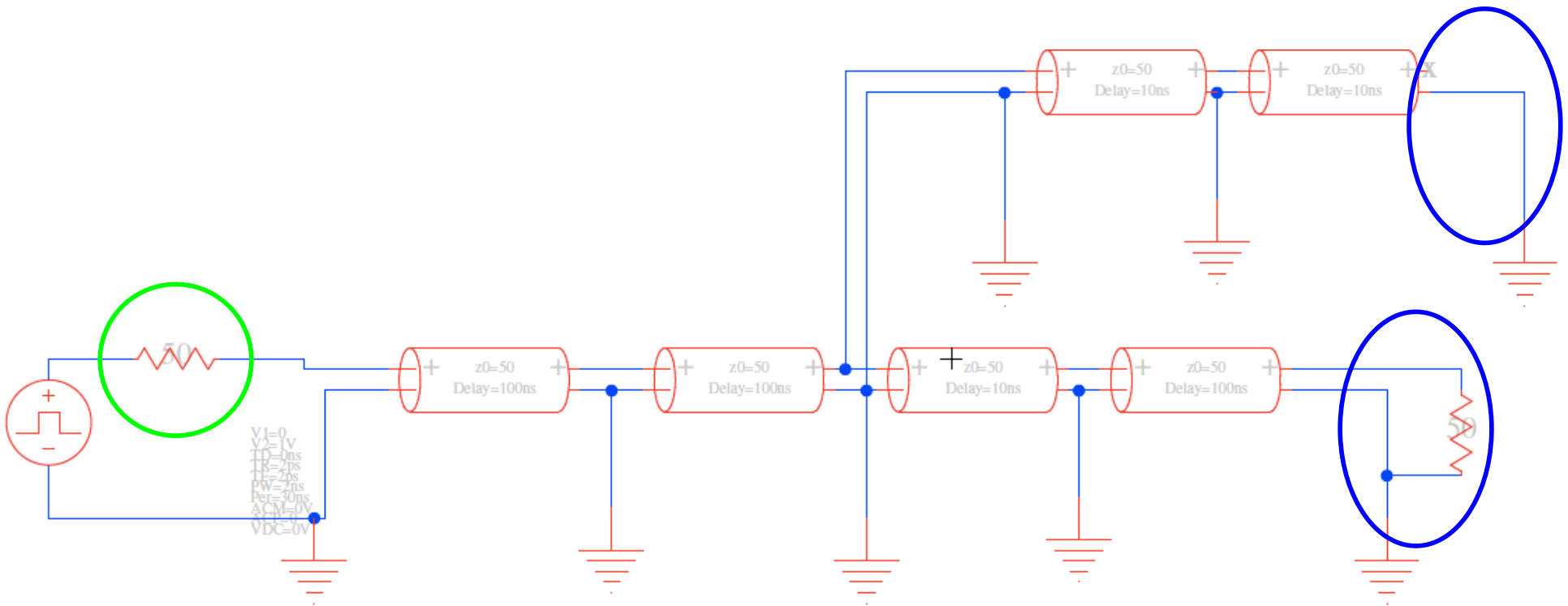
# Branch with Open Circuit?

- ❑ What happens if branch open circuit?
- ❑ And source termination?



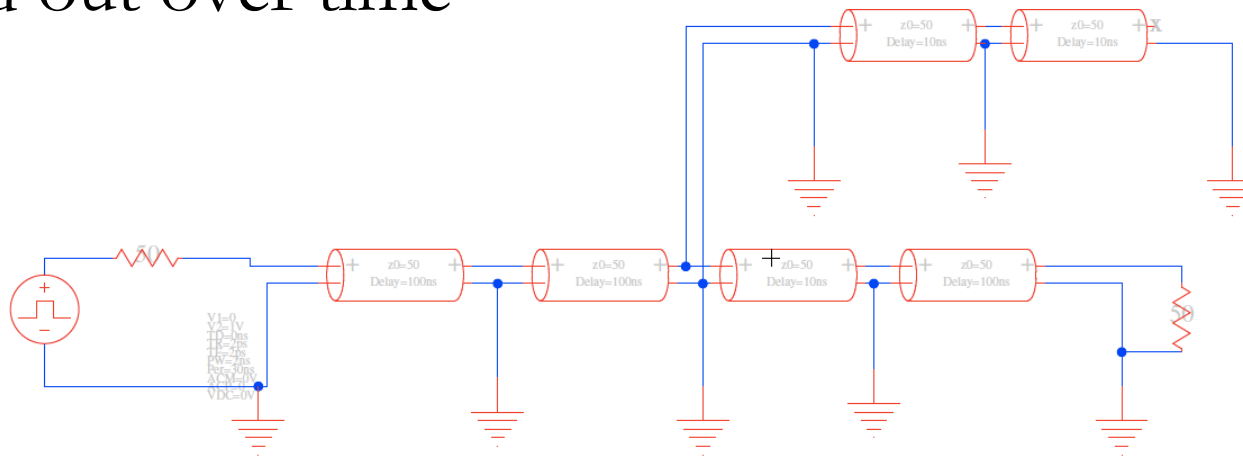
# Branch with Open Circuit

- ❑ Reflects at end of open-circuit stub
- ❑ Reflection returns to branch
  - ...and encounters branch again
  - Send transmission pulse to both
    - Source and other branch
- ❑ Sink sees original pulse as multiple smaller pulses spread out over time






# Open Branch Simulation

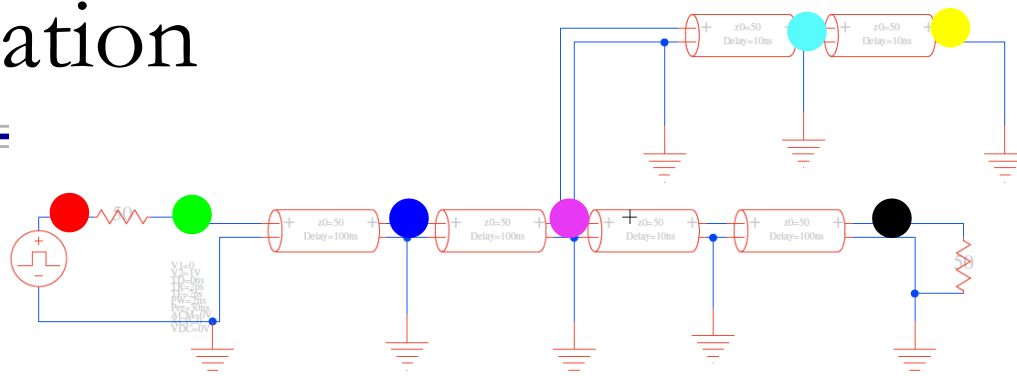


Branch Open Line

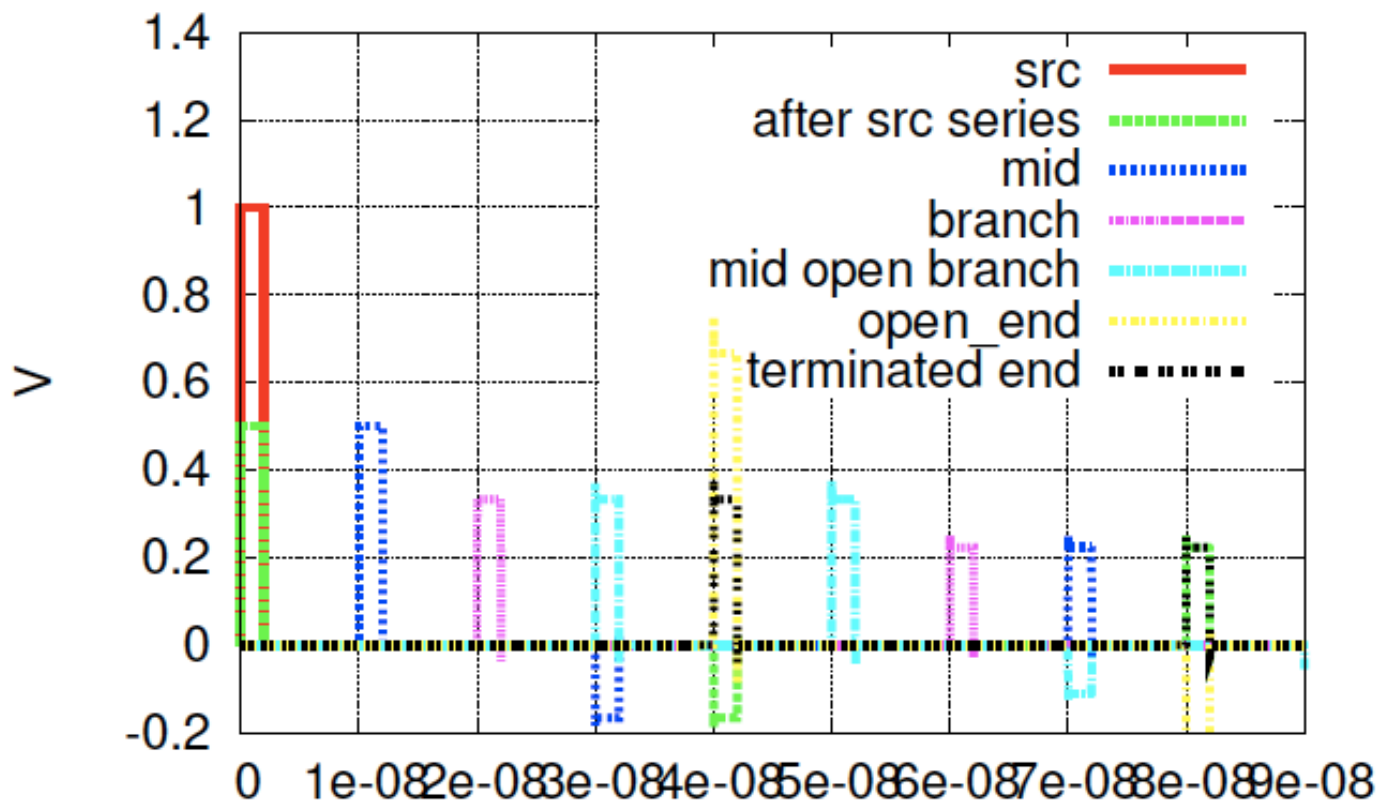




# Open Branch Simulation

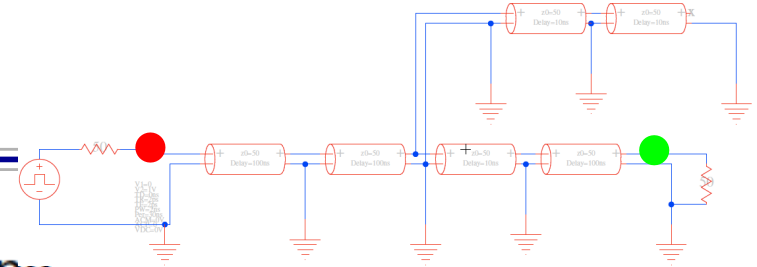


Branch Open Line

 


 
# Bus


- ❑ Common to have many modules on a bus
  - E.g. PCI slots
  - DIMM slots for memory
- ❑ High speed → bus lines are trans. lines





# Multi-drop Bus

- ❑ Ideal
  - Open circuit, no load


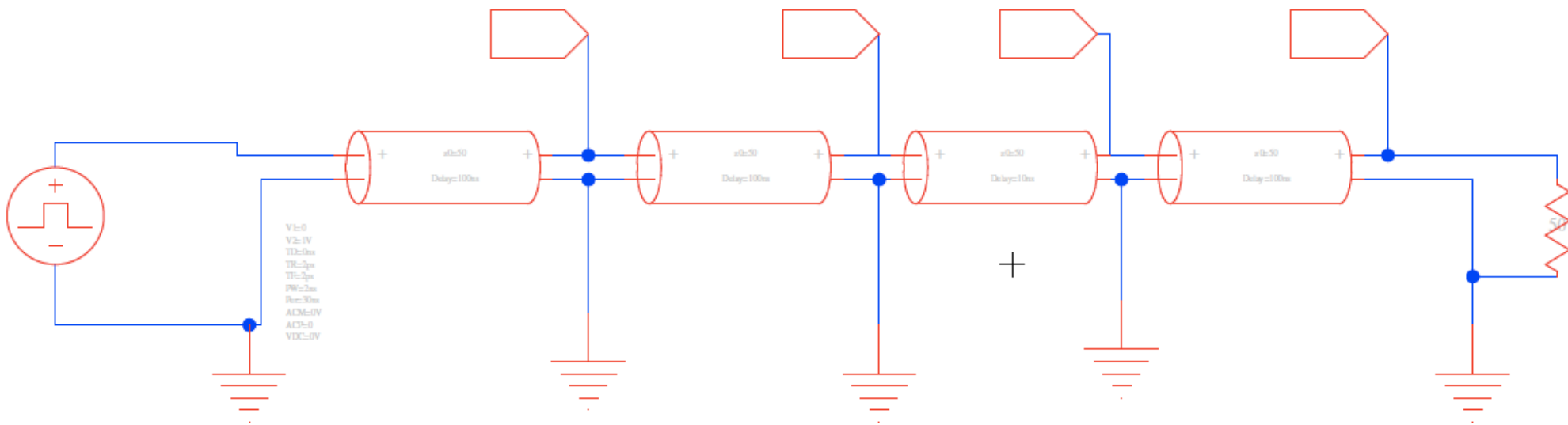




# Multi-Drop Bus

- Impact of capacitive load (stub) at drop?
  - If tight/regular enough, change  $Z$  of line

$$Z_0 = \sqrt{\frac{L}{C}}$$

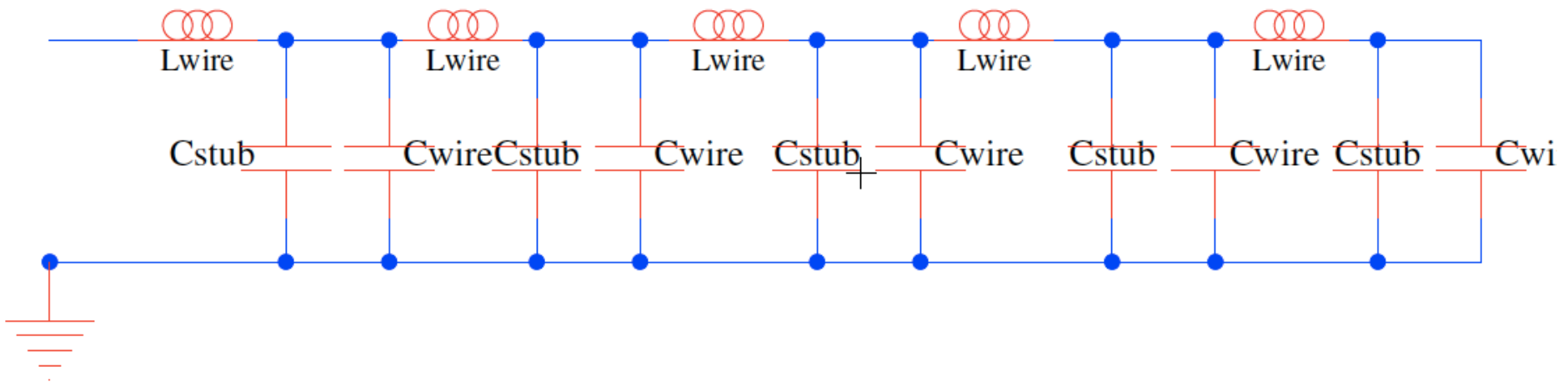 





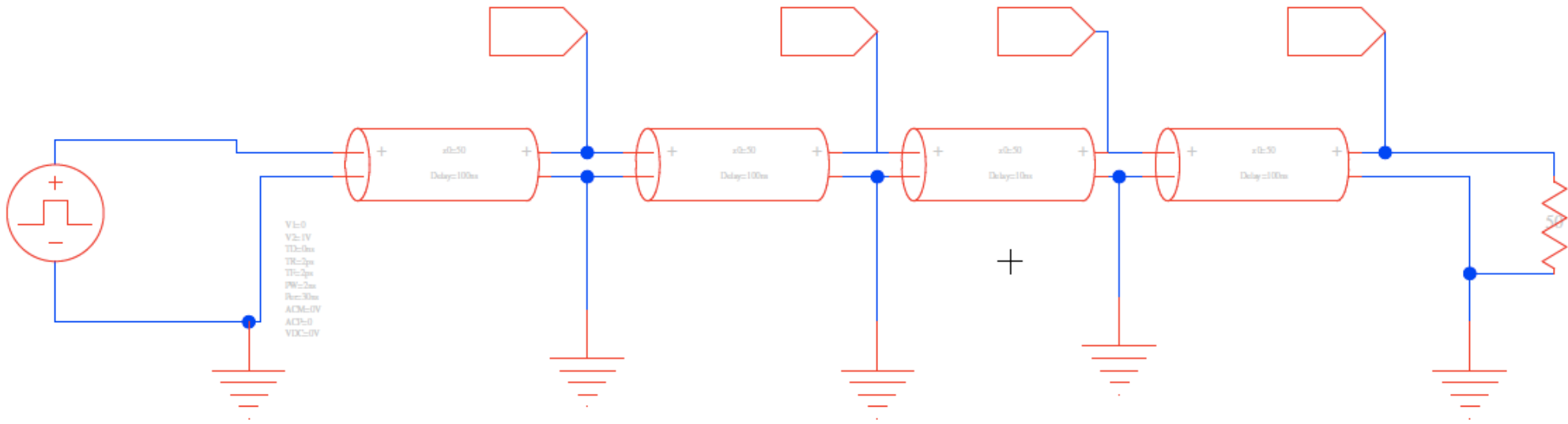
# Multi-Drop Bus

- ❑ Long wire stub?
- Looks like branch
  - may produce reflections





# Transmission Line Noise

---

- ❑ Frequency limits
- ❑ Imperfect termination
- ❑ Mismatched segments/junctions/vias/connectors
- ❑ Loss due to resistance in line
  - Limits length



# Idea

---

- Transmission lines
  - high-speed
  - high throughput
  - long-distance signaling
- Termination
- Signal quality losses

$$w = \frac{1}{\sqrt{LC}} = \frac{c_0}{\sqrt{\epsilon_r \mu_r}}$$

$$Z_0 = \sqrt{\frac{L}{C}}$$

$$V_r = V_i \left( \frac{R - Z_0}{R + Z_0} \right)$$



# Admin

---

- ❑ Friday HW 7 due
- ❑ Final (F 12/17)
  - 12-2pm in Moore 212
  - Cumulative: Lec 1 – 35
    - Big Idea slides from each lecture
  - Finals 2010—2020 online
  - Friday lecture review
  - TA review session before exam
    - TBD, watch Piazza. Maybe a poll.