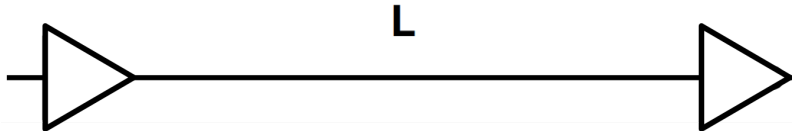


Assume:

- $R_u=60K\Omega$ per 1mm length of wire; $C_u=0.16pF$ per 1mm length of wire
- $R_{wire} = L \times R_u$; $C_{wire} = L \times C_u$;
- $R_0=25K\Omega$; $C_0=0.01fF$
- velocity saturated; $\gamma = C_{diff}/C_{gate} = 1$
- initial, minimum size buffer has $W_p = W_n = 1$

1. What is the delay of an unbuffered wire of length $L=1mm$ driven and loaded by a minimum size buffer ($W_p = 1, W_n = 1$)? Draw the equivalent RC network and write a symbolic equation.



• Symbolic Equation:

2. What is the delay of a length $L = 1mm$, when we add N evenly spaced buffers to the wire.

Wire of Length	Delay (ns)	Number in 1mm	Total Delay for 1mm (ns)
1mm		1	
0.5mm		2	
0.1mm		10	
0.01mm		100	
0.001mm		1000	

3. What is the delay of a length L , when we add N evenly spaced buffers to the wire.

• Symbolic Equation:

4. How many buffers do we use to minimize delay?

• Symbolic Equation:

• Number of buffers to minimize delay on 1mm wire:

• Delay at this buffer count:

• Optimum segment length between buffers:

5. How should we size the buffers?

- Symbolic Equation:
- W to minimize delay:
- Delay of 1mm wire at optimal buffer size: