
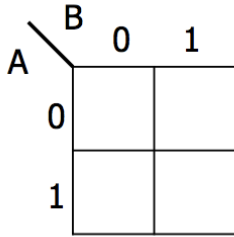


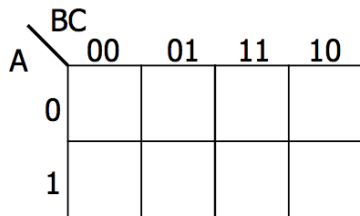
- Simplify the boolean expression  $Z = \bar{A} \cdot \bar{B} + A \cdot \bar{B} + \bar{A} \cdot B$  to the minimum sum of products with the 2-variable K-map:



- Simplify the boolean expression  $Z = \bar{A} \cdot \bar{B} \cdot \bar{C} + \bar{A} \cdot B + A \cdot B \cdot \bar{C} + A \cdot C$  to the minimum sum of products with the 3-variable K-map:




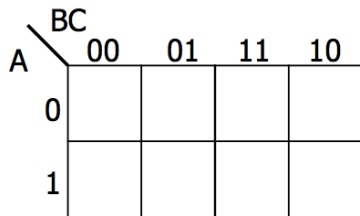- Extra practice for outside of class:  
Simplify the boolean expression  $Z = A \cdot B \cdot C + A \cdot B \cdot \bar{C} + \bar{A} \cdot B \cdot C$  to the minimum sum of products with the 3-variable K-map:







Simplify the truth table to the minimum sum of products with the 4-variable K-map:

A	B	C	D	Z
0	0	0	0	1
0	0	0	1	1
0	0	1	0	1
0	0	1	1	1
0	1	0	0	1
0	1	0	1	1
0	1	1	0	1
0	1	1	1	1
1	0	0	0	0
1	0	0	1	1
1	0	1	0	0
1	0	1	1	1
1	1	0	0	0
1	1	0	1	0
1	1	1	0	0
1	1	1	1	0

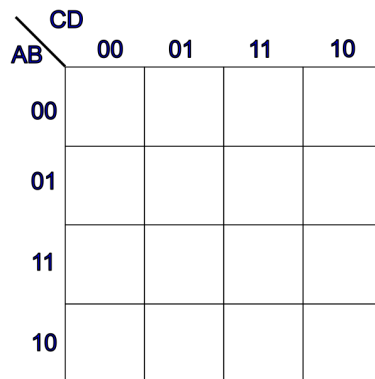


Assume  $V_{in}$  is 0 for  $t < 0$  and steps to 1V at  $t = 0$ .


4. What value does  $V_{measure}$  take on as  $t \rightarrow \infty$  ?


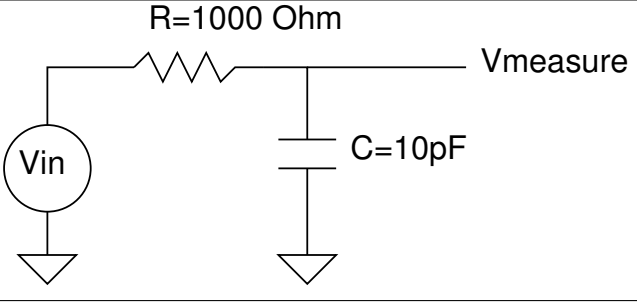
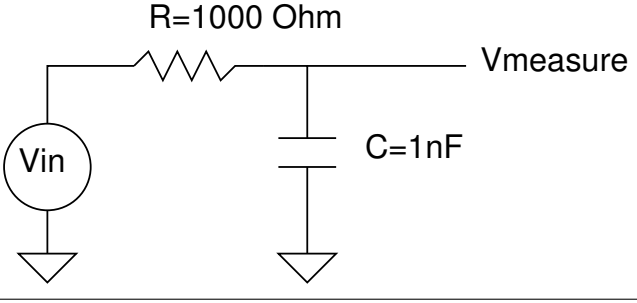
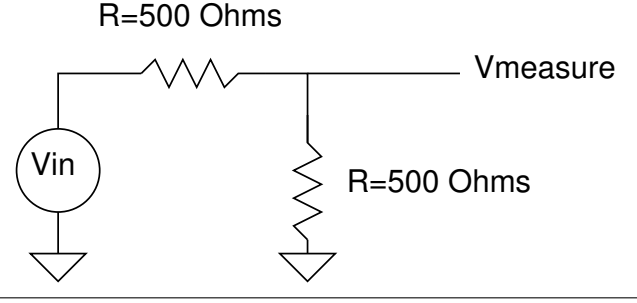
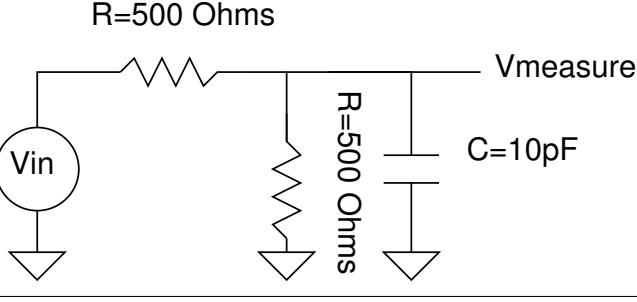
N-type MOSFET

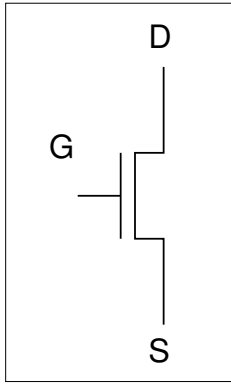



Zero-Order Model

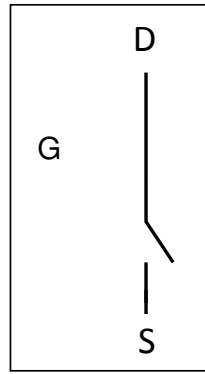

First-Order Model

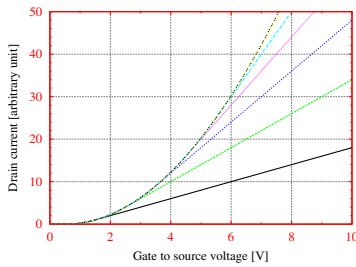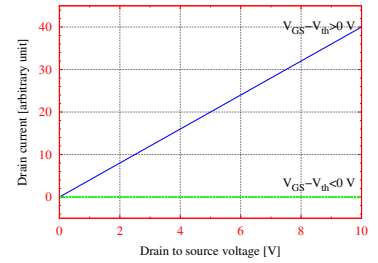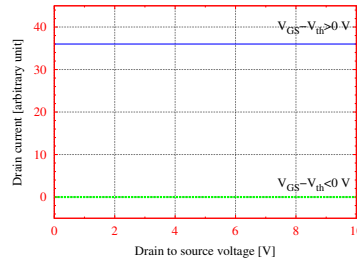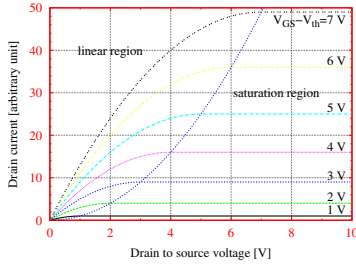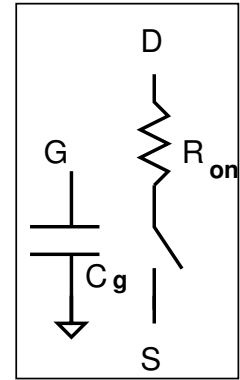

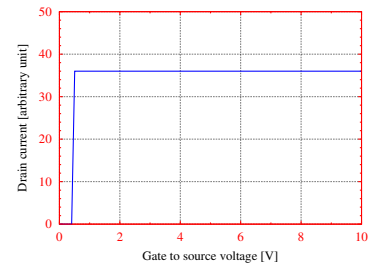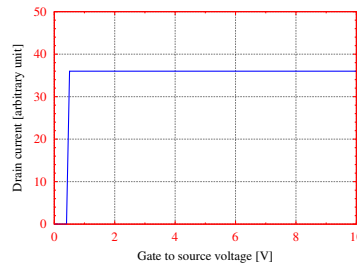$I_{ds}$  unbounded when  $V_{gs} > V_{th}$



(even this is a simplified approximation)

Step at  $V_{gs} = V_{th}$

Reminder:

	NMOS	PMOS
Threshold	$V_{thn} > 0$	$V_{thp} < 0$ $V_{thp} \approx -V_{thn}$
Conduct	positive input $V_{gs} > V_{thn}$	negative input $V_{gs} < V_{thp}$
Drain	most positive terminal	most negative terminal
Source	most negative terminal (source of electrons)	most positive terminal (source of holes)

$$V_{gs} = V_g - V_s \tag{1}$$