
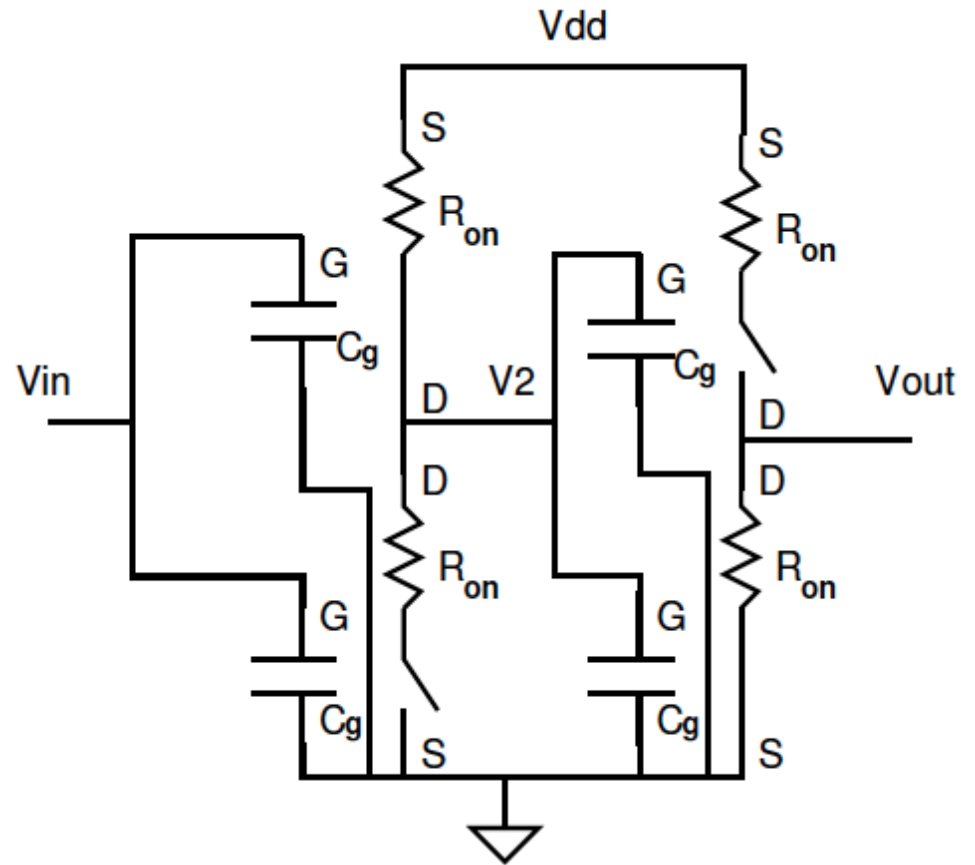


ESE370: Circuit-Level Modeling, Design, and Optimization for Digital Systems

Lec 5: September 15, 2021
Delay and RC Response


Delay is RC Charging

 

Gate Delay is RC Charging

Strategy:

 - ❑ Use zero-order model to understand switch state
- ❑ Break into output/input stages
- ❑ For each stage
 - Understand R_{drive}
 - Understand C_{load}






Today

- ❑ RC Charging
 - RC Step Response Curve
- ❑ What is the C?
 - Capacitive **load** on logic gate output node
- ❑ What is the R?
 - Equivalent **output resistance** on the current path **driving** the output node
- ❑ Approximating and Measuring Delay
 - Tau estimate!


90% Rise Time? (preclass 1ab)

 

What is final $V_{measure}$?


What is time constant, τ ?

Governing Equations? (KCL)

 

- KCL @ $V_{measure}$
 - Kirchoff's Current Law
 - Sum of all currents into a node = 0
 - Current entering a node = current exiting a node
 - $I_R = I_C$

Governing Equations? (KCL)

 


$$I_R = I_C$$

$$\frac{V_R}{R} = C \frac{dV_C}{dt}$$

$$\frac{V_{in} - V_{measure}}{R} = C \frac{dV_{measure}}{dt}$$

Governing Equations? (KCL)

 

$$I_R = I_C$$

$$\frac{V_R}{R} = C \frac{dV_C}{dt}$$


$$\frac{V_{in} - V_{measure}}{R} = C \frac{dV_{measure}}{dt}$$

$$0 = \frac{dV_{measure}}{dt} + \frac{1}{RC} V_{measure} - \frac{V_{in}}{RC}$$

$$V_{measure} = V_{in} \left(1 - \left(e^{-t/RC} \right) \right)$$

$$\tau = RC$$

What does look like?

 

$$V_{measure} = V_{in} \left(1 - \left(e^{-t/RC} \right) \right)$$


Shape of Curve (preclass 1c)

t (in ps)	$e^{-t/RC}$	$1-e^{-t/RC}$
0		
0.1		
1		
2		
2.3		

$$V_{in} = 1$$

$$V_{measure} = V_{in} \left(1 - \left(e^{-t/RC} \right) \right)$$

Rise Time: 10—90%

 

$$t_{\text{rise}} \approx 2.2\text{ps} \approx 2.2\tau$$

Shape of Curve (preclass 1d)


t (in ps)	$e^{-t/RC}$	$1-e^{-t/RC}$
0		
0.1		
1		
2		
2.3		

$$V_{in}=1$$

$$V_{measure} = V_{in} \left(1 - \left(e^{-t/RC} \right) \right)$$


At what time is $V_{measure}$ 50% of its value?

Delay Time: 50% (in)—50% (out)

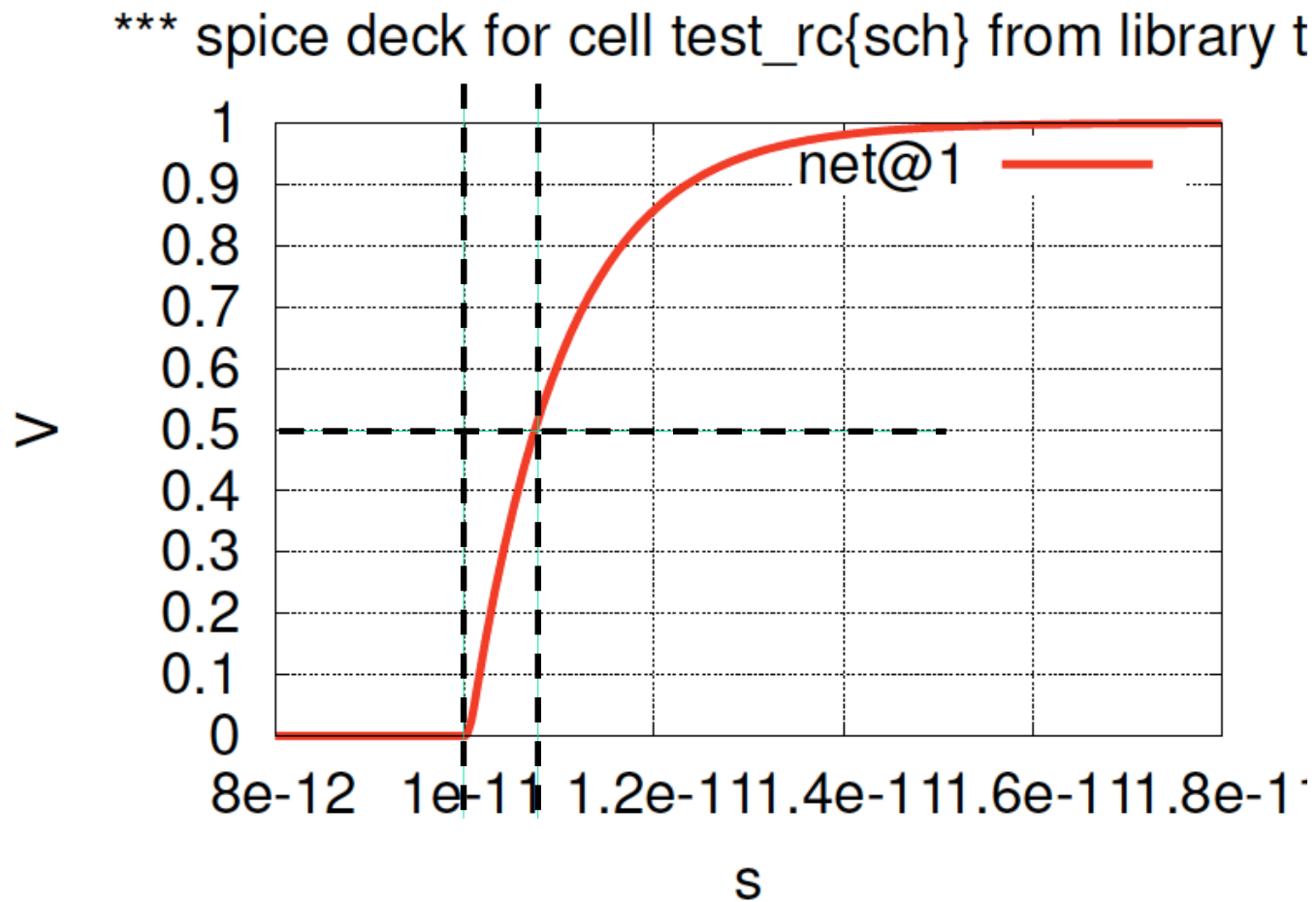


$$t_{\text{PLH}} \approx .69\text{ps} \approx .69\tau$$

Propagation Delay Definitions

 

$$V_{50\%} = V_{OL} + 0.5 [V_{OH} - V_{OL}] = 0.5 [V_{OL} + V_{OH}]$$

Rise/Fall Times

 


$$V_{10\%} = V_{OL} + 0.1 [V_{OH} - V_{OL}]$$

$$V_{90\%} = V_{OL} + 0.9 [V_{OH} - V_{OL}]$$

Delay Time: 50% (in)—50% (out)

 *** spice deck for cell test_rc{sch} from library t




$$t_{\text{PLH}} \approx .69\text{ps} \approx .69\tau$$

Voltage Waveform at Output/Input Node

R_{drive} from
looking into
output stages


C_{load} from
looking into
input stages

 

Voltage Waveform at Output/Input Node

R_{drive} from
looking into
output stages
and wires

 C_{load} from
looking into
input stages
and wires



What is C?



Capacitance

- Wire
- Fanout -- Total gate load
 - Logical Gate
 - MOSFET gate




Fanout

- Number of things to which a gate output connects


Fanout in Circuit

- Output routed to many gate inputs

 


Fanout in Circuit (preclass 2)

- ❑ Maximum fanout?
- ❑ Second?
- ❑ Min?

 


MOSFET Capacitance

- “load of 1”?
 - Capacitive

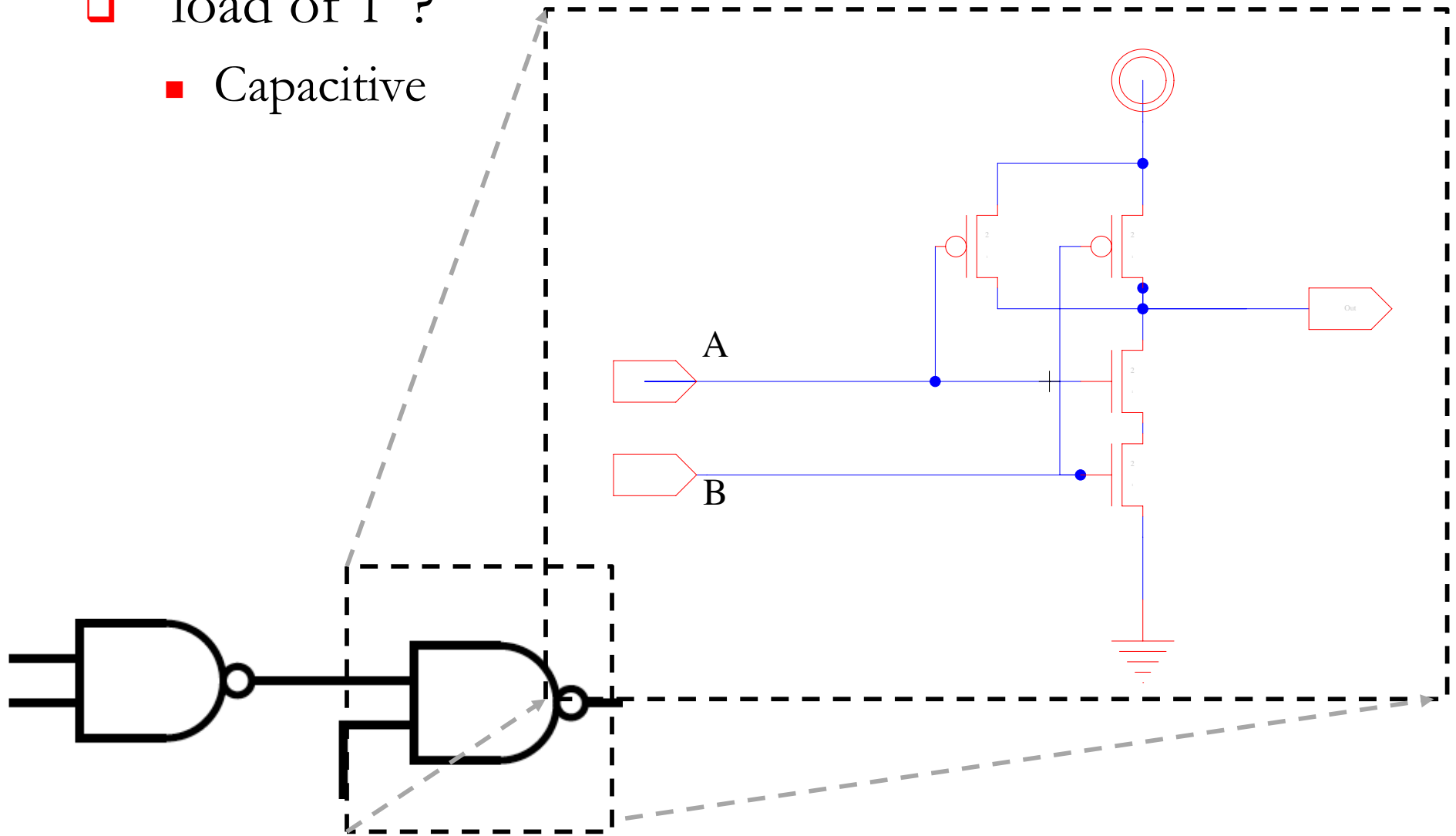

MOSFET Capacitance

- “load of 1”?
- Capacitive

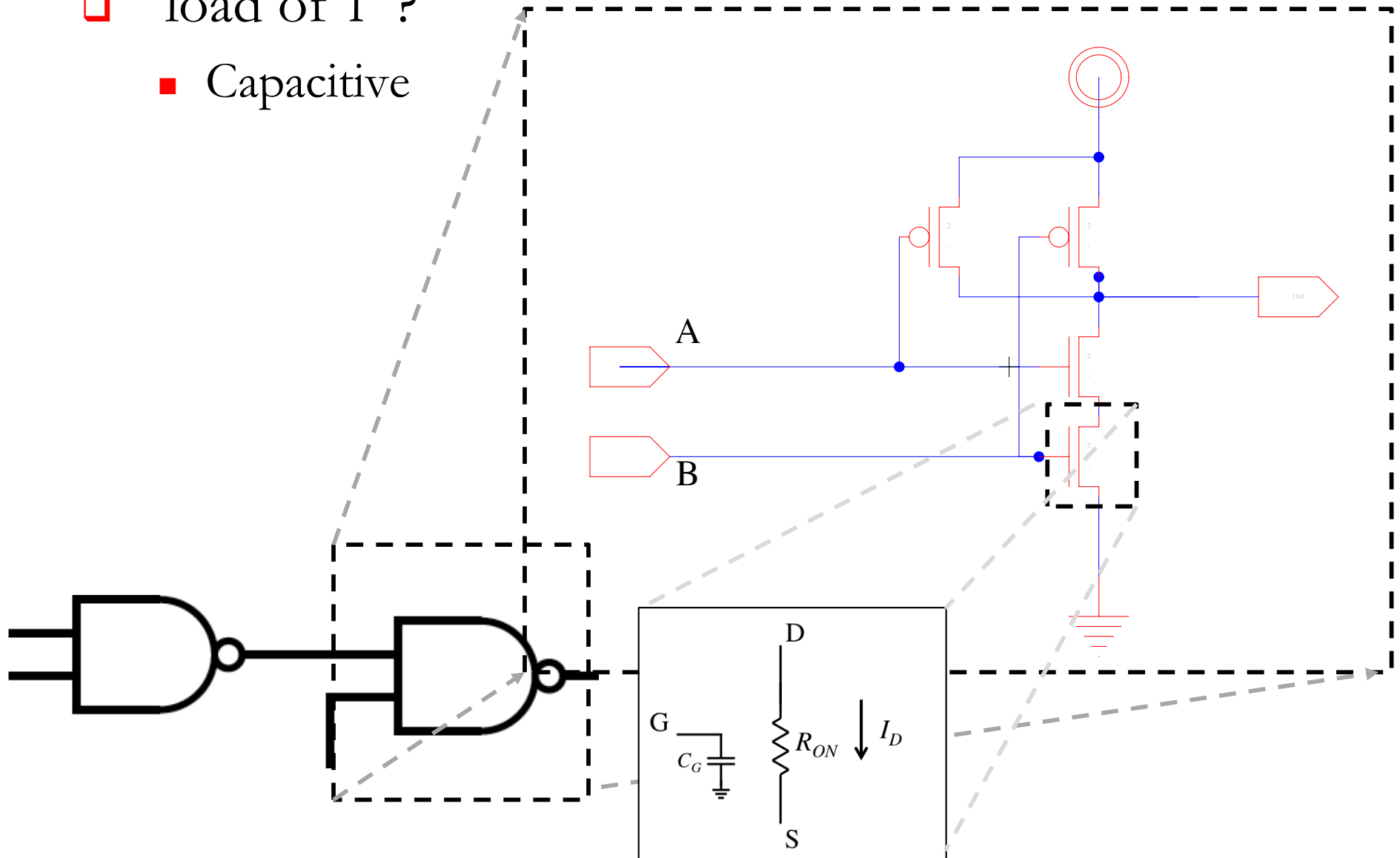




Lumped Capacitive Load

$$C_{load} = \sum_{i \in fanout} C_{G_i} + \sum_{i \in wires} C_{w_i}$$


What is R?

Resistance

 

- Wire resistance
 - From supply (V_{DD} or Gnd) to transistor source
 - From transistor output to gate it is driving
- Transistor equivalent resistance (R_{on})


Equivalent Resistance

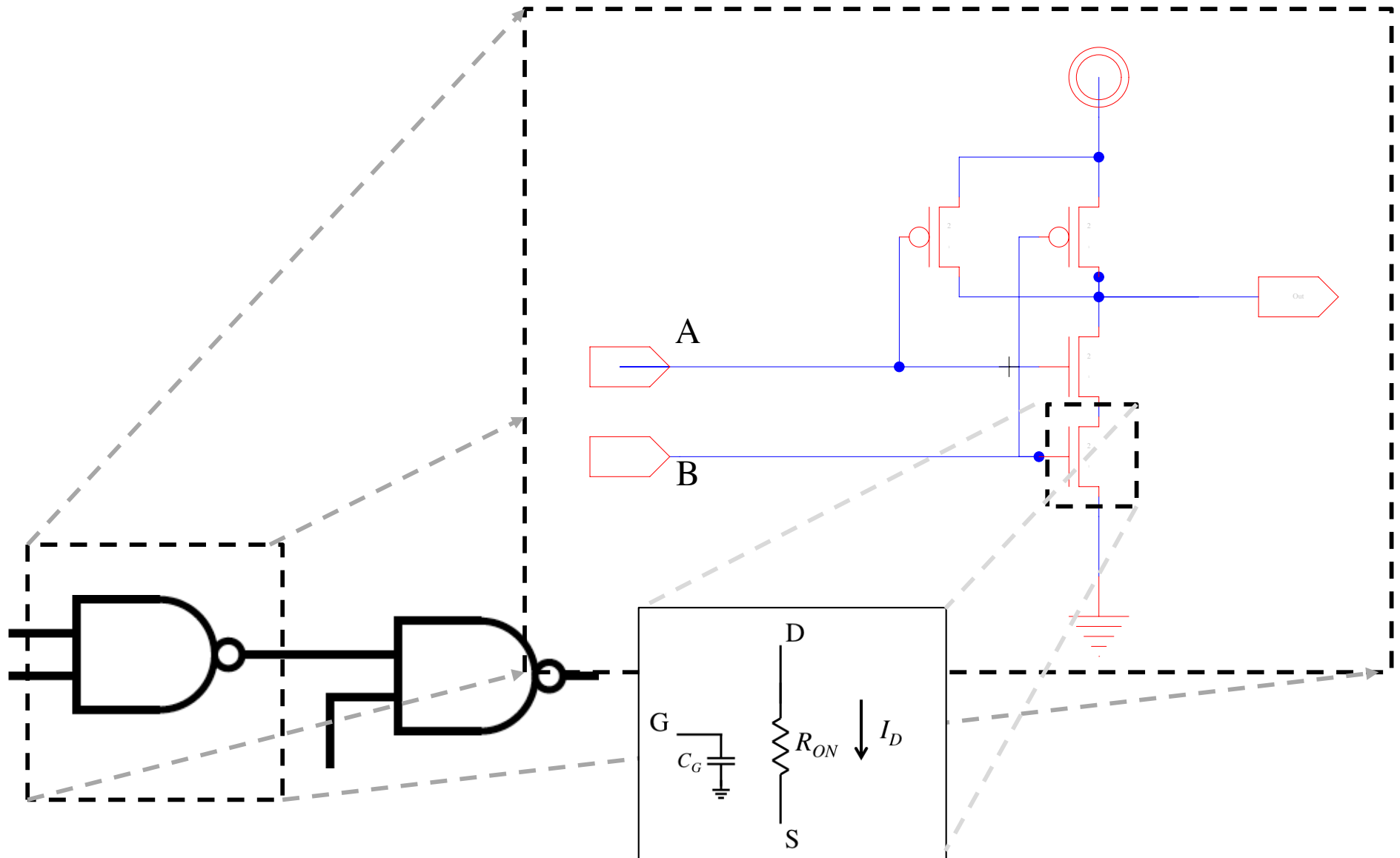

Equivalent Resistance (prelcass 3)

□ What resistances might transistors contribute?

 - How many cases?
- Assume $R_{on} = R_{on,p} = R_{on,n}$




Equivalent Resistance (prelcass 3)

□ What resistances might transistors contribute?

- How many cases?
- Assume $R_{on} = R_{on,p} = R_{on,n}$

Input	Rout
00	
01	
10	
11	

 


Rise/Fall Times

□ Rise and Fall time may differ

- Why?
- What is worst case?
- What is best case?

Input	Out
00	
01	
10	
11	

 



Lumped Resistive Source


$$R_{drive} = R_{tr,net} + \sum_{i \in wires} R_{w_i}$$

$R_{tr,net}$ = transistor network resistance = parallel and series combination of R_{tr}

Voltage Waveform at Output/Input Node


R_{drive} from
output stages
and wires

C_{Load} from
input stages
and wires

 

Measuring Delay

Measuring Gate Propagation Delay

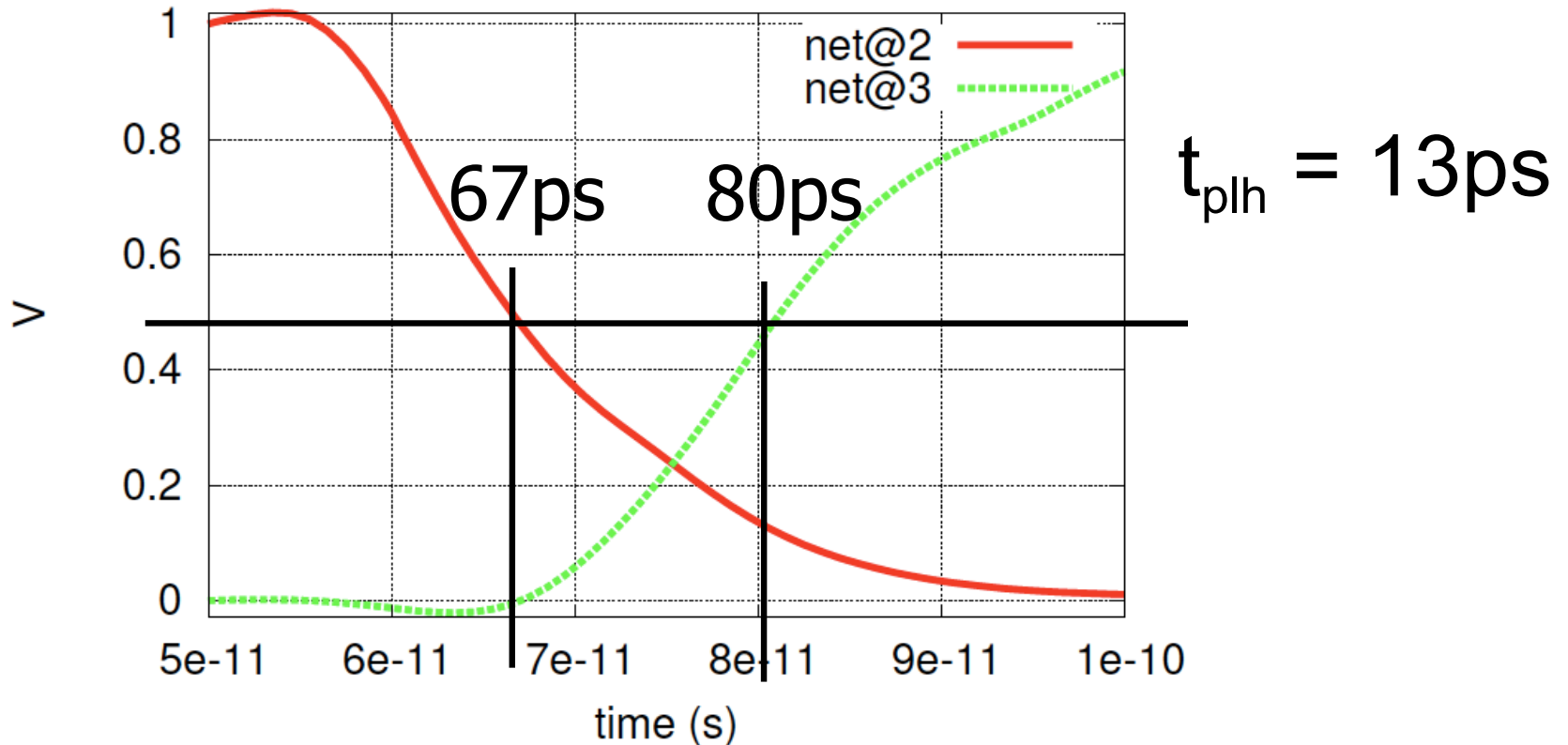

- ❑ Next stage starts to switch before first finishes
- ❑ Measure from 50% of input swing to 50% of output swing



Characterizing Gate/Technology


- Delay measure of a logic gate will be
 - Function of load on logic gate
 - Function of input signal rise time
 - Which, in turn, may be a function of input loading from the driving logic gate



Delay vs. Risetime

1ps input rise


fast rise

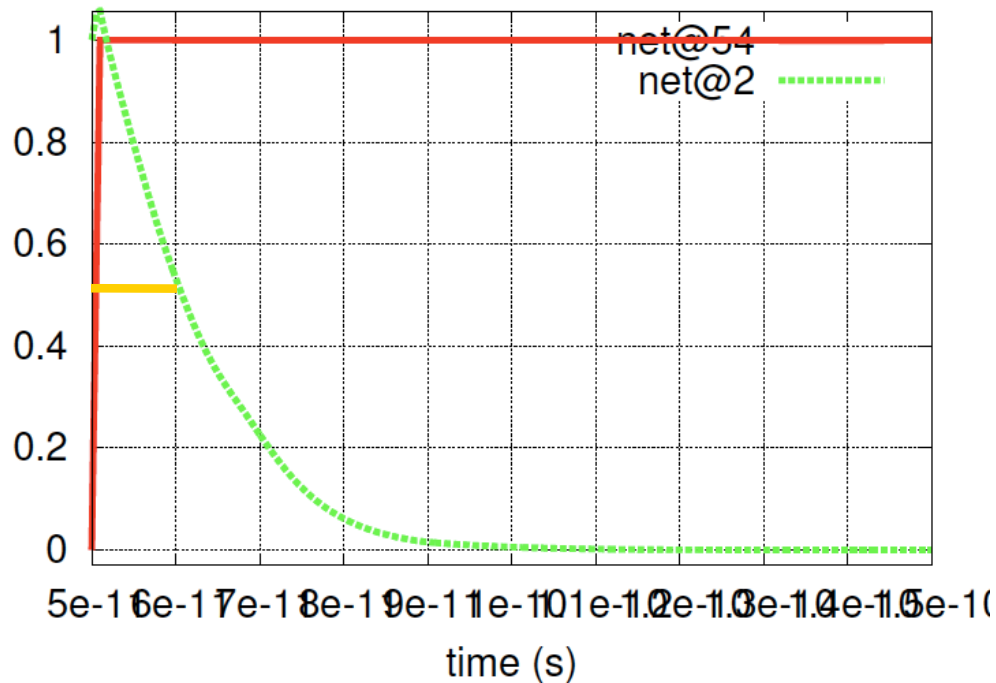

10ps delay

100ps input rise

slow rise

 

20ps delay

- If we didn't know the input rise time, we wouldn't know what a 13ps delay meant




Characterizing Gate/Technology

- Delay measure will be
 - Function of load on gate
 - Function of input signal rise time
 - Which, in turn, may be a function of input loading
- Want to understand typical delay times
 - Allows us to compare designs with a (somewhat) normalized delay metric


Standard Measurement for Characterization

 - ❑ Drive with a gate
 - **Not** an ideal source
 - Input rise time typically would see in circuit
- ❑ Measure loaded gate
 - Typical loading – FO4




Not realistic measurement

HW2 Measurement Setup

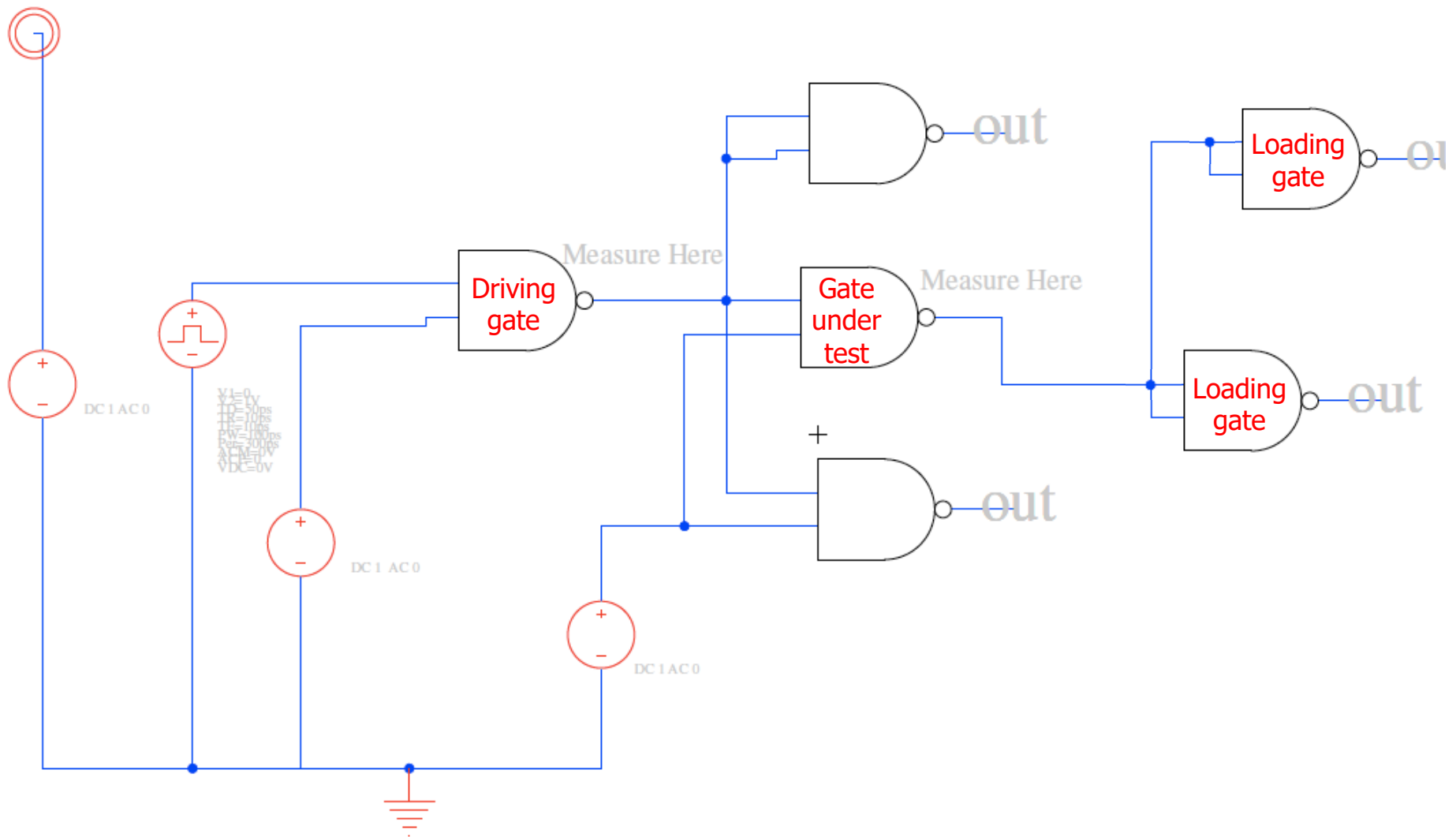


Measurement for Characterization

 - Drive with a gate
 - **Not** an ideal source (how does delay change if drive is ideal?)
 - Input rise time typically would see in circuit
- Measure loaded gate
 - Typical loading – FO4




Measurement for Characterization



 
- Drive with a gate
 - **Not** an ideal source
 - Input rise time typically would see in circuit
- Measure loaded gate
 - Typical loading – FO4 (how does delay change if gate is unloaded?)




Ring Oscillator (If time)

 



Ring Oscillator (If time)

   


Ring Oscillator (If time)

 

  $C_{load,1} = C_{load,2} = C_{load,3}$ and **INV1 = INV2 = INV3** = SYM INV



Ring Oscillator (If time)

 

$$T = \tau_{PHL2} + \tau_{PLH3} + \tau_{PHL1} + \tau_{PLH2} + \tau_{PHL3} + \tau_{PLH1} = 6\tau_p$$

$$f = \frac{1}{T} = \frac{1}{6\tau_p} = \frac{1}{2n\tau_p} \rightarrow \tau_p = \frac{1}{2nf}$$



Admin

- ❑ HW 2 due 9/20
 - If you haven't started, start now!
 - Office hours on every weekday
- ❑ Setup Spice Work Flow
 - access to electric, setup for spice, run ngspice
 - See tool guides on website
 - <https://www.seas.upenn.edu/~ese370/#tools>
 - read spice style guide on webpage:
 - https://www.seas.upenn.edu/~ese370/fall2021/handouts/spice_style_guide.pdf