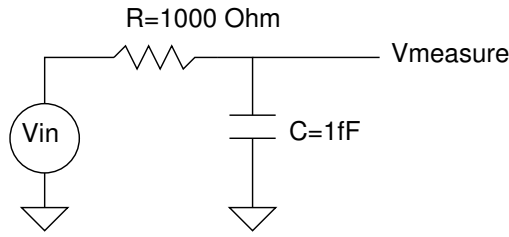


1. Assume V_{in} is 0 for $t < 0$ and steps to 1V at $t = 0$. The circuit is then allowed to achieve steady-state.




- a) What is the final value of $V_{measure}$?
- b) What is the time constant, τ ?
- c) How many seconds does it take before $V_{measure}$ reaches 90% of the final value? Use the table below and $e = 2.72$.

t (in ps)	$e^{-t/\tau}$	$1-e^{-t/\tau}$
0		
0.1		
1		
2		
2.3		


- d) At what time does $V_{measure}$ reach 50% of its value? Use $\ln(0.5) = -0.69$.

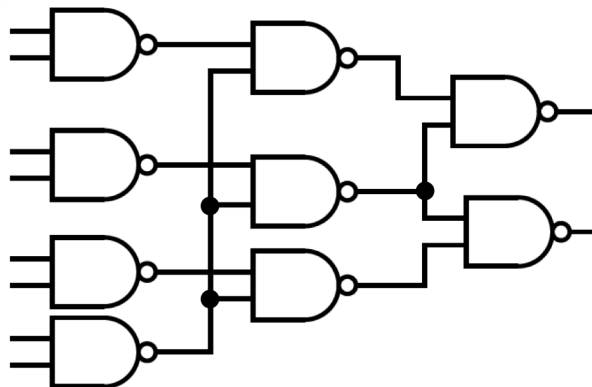2. Assume each gate puts a load of 1 on each of its two inputs. (All intersecting wires are **not** connected)



What is the load on the most heavily loaded gate output?	
What is the load on the least heavily loaded gate output?	

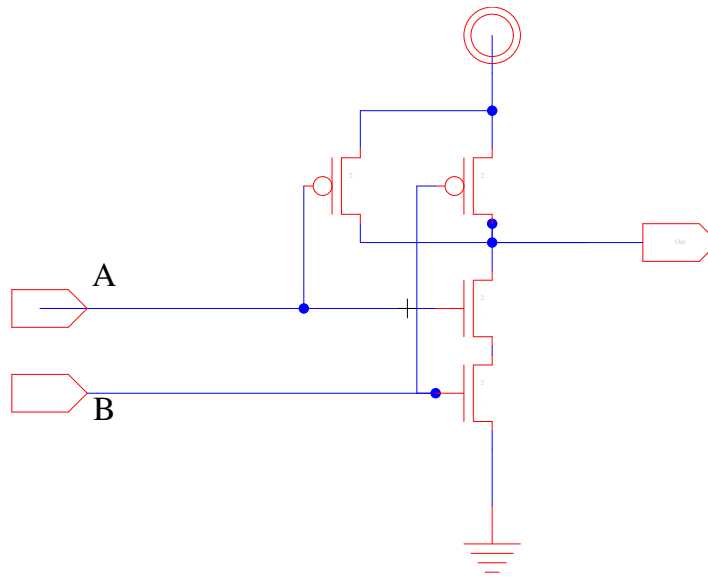3. Assuming $R_{on,p}=R_{on,n}=R_{on}$, what are all the possible equivalent resistance values of the gate output stage?



Hint: How many cases are there? What is the resistance for each of the cases?

Case	Resistance