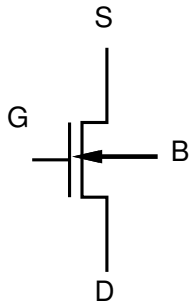


- How many capacitance values might we need to represent a 4-terminal transistor?
(fourth terminal is body)




Hint: How many terminal pairs are there?

Terminal Pair	Capacitance

Use in class for notes to summarize cases and capacitances.

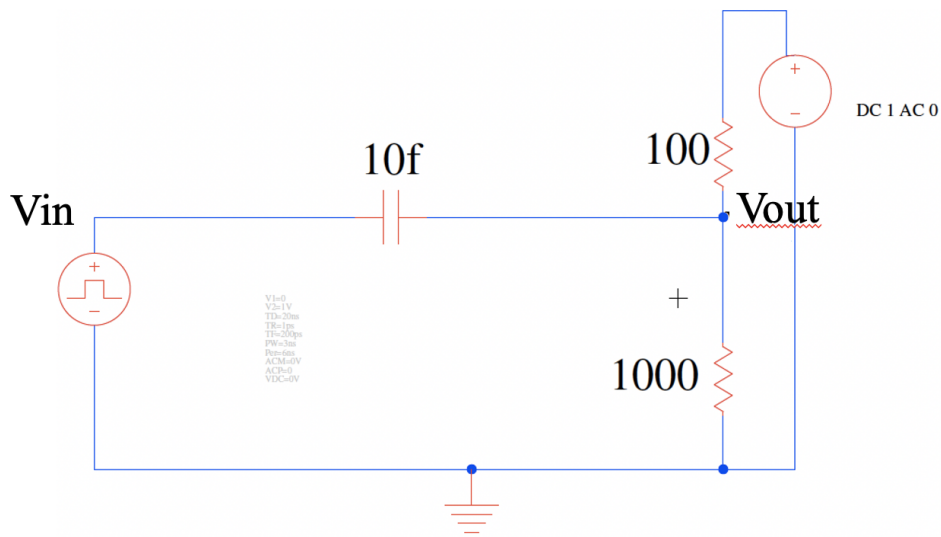- Assuming a step input from 0 to 1V by the pulse generator on the left, what does the voltage on V_{out} as a function of time look like?



Hints: What is the initial voltage? What is the steady-state voltage as $t \rightarrow \infty$?