

**University of Pennsylvania**  
**Department of Electrical and System Engineering**  
**Circuit-Level Modeling, Design, and Optimization for Digital Systems**

ESE370, Fall 2021

Midterm 1

Friday, October 1

---


- 4 problems with weights indicated.
- Parts within a problem will not be weighted equally.
- Calculators allowed.
- Closed book = No text or notes allowed.

<b>Name:</b> <a href="#">Answers</a>
--------------------------------------

Grade:


Q1	
Q2	
Q3	
Q4	
Total	<a href="#">Mean: 92.4, Stdev: 7.2</a>

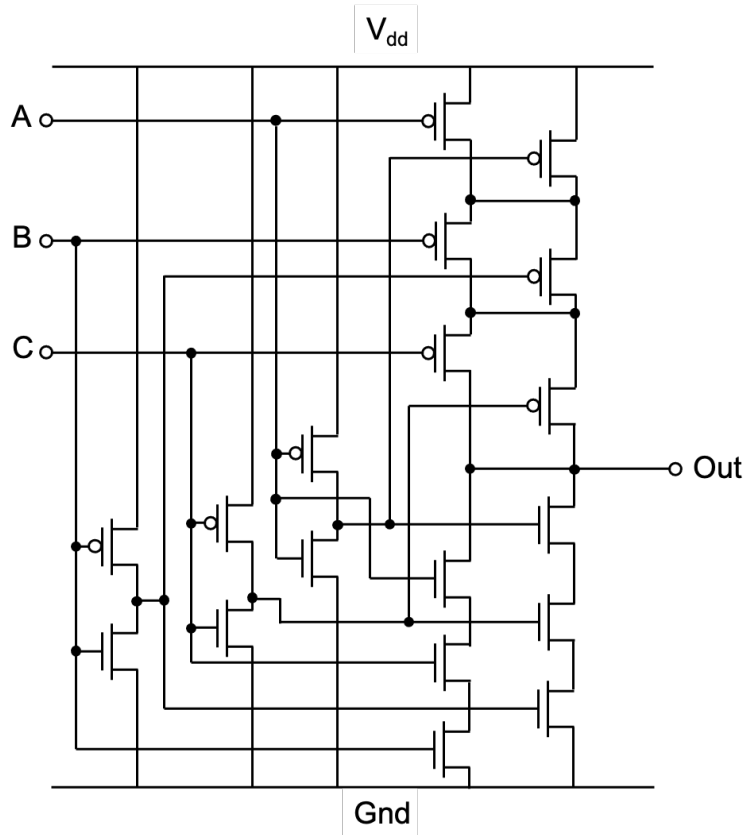1. (25 points) Identify if the following circuits are CMOS, why or why not, and their functions. [Show your work for partial credit consideration.]




(a)

CMOS? (circle one)	Yes	No
(if CMOS) Function (Out)		
(if not CMOS) Why not?	Short from Vdd to Gnd for A=B=C=1	

 


CMOS? (circle one)	Yes      No
(if CMOS) Function (Out)	$\overline{Out} = A \cdot B \cdot C + \overline{A} \cdot \overline{B} \cdot \overline{C}$
(if not CMOS) Why not?	

 

(c)

CMOS? (circle one)	Yes	No
(if CMOS) Function (Out)		
(if not CMOS) Why not?	Short from Vdd to Gnd when A=1, B=C=0	

 2. (25 points) Consider the following circuit:



Assume:

- all transistors are same size.
- all on transistors have resistance  $R_{on}$ .
- all transistors have total gate capacitance  $C_g$ .

- (a) Identify the output function.

$$Out = \bar{A} \cdot \bar{B} + \bar{D}$$

- (b) Lowest resistance driving output?

Case:  $A=B=C=D=0$

Resistance:  $\frac{10}{11}R_{on}$

- (c) Highest resistance driving output?

Case:  $A=B=0, C=D=1$

Resistance:  $2R_{on}$

- (d) Lowest capacitance of an input?

Which:  $C$

Capacitance:  $C_g$

- (e) Highest capacitance of an input?

Which:  $B, D$

Capacitance:  $3C_g$


- (f) Worst-case 10-90 rise time for one of these gates driving a single input of another of these gates?

Case: with  $B=0, C=D=1, A:1 \rightarrow 0$

Rise Time Expression:  $2.2 * 2R_{on} * 3C_g = 13.2R_{on}C_g$

[Show calculation for partial credit consideration.]

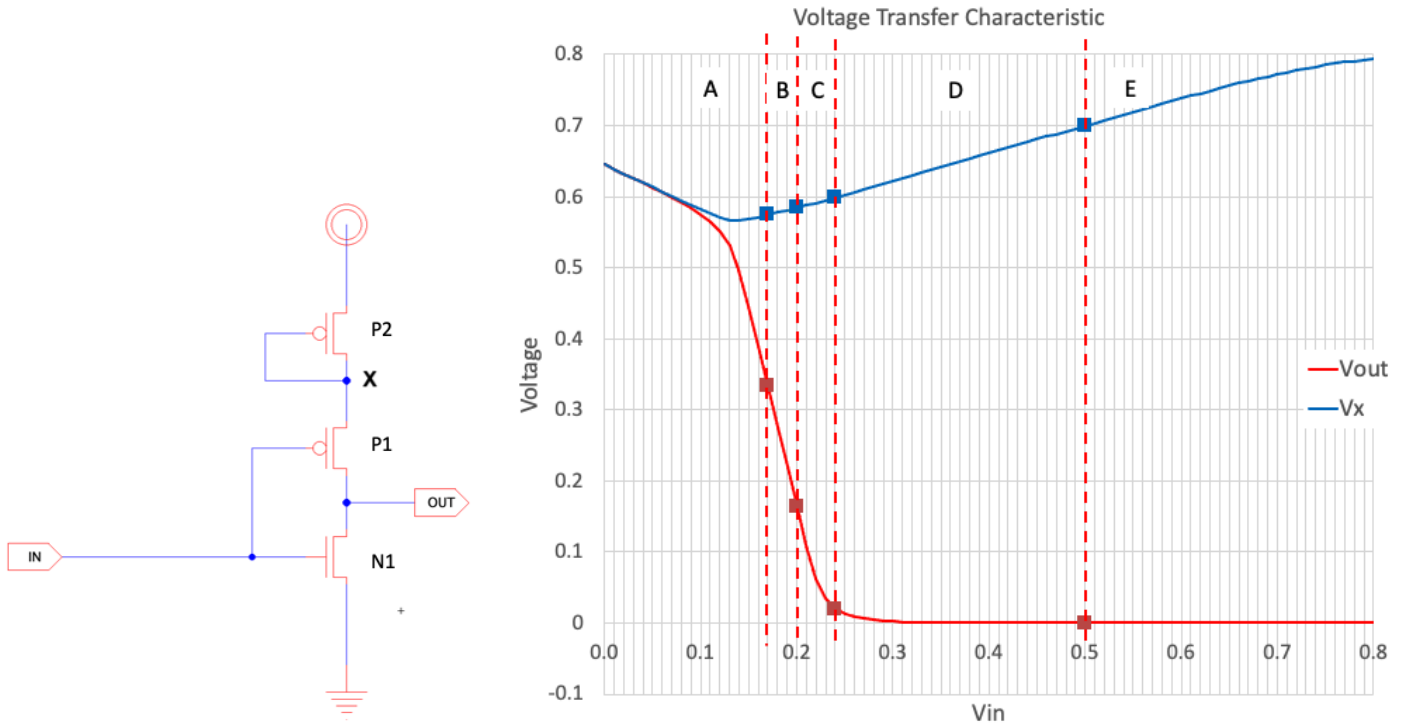3. (25 points) Consider the following circuit and its voltage transfer characteristic as well as the voltage at node X. Assume  $V_{dd} = 800mV$  and  $V_{thn} = -V_{thp} = 200mV$ .



For the regions A-E labeled on the transfer function, identify the region of operation of the nMOS and both pMOS devices. Fill out the table below.

	N1	P1	P2
A	Subthreshold	Linear	Saturation*
B	Subthreshold	Saturation	Saturation
C	Saturation	Saturation	Saturation
D	Linear	Saturation	Saturation*
E	Linear	Subthreshold	Saturation*

Subthreshold and Saturation were both accepted.

For reference on the next page are the transistor current models and additional work space if needed:

NMOS:

$V_{GS}$	$V_{DS}$	Mode	$I_{DS}$
$\geq V_{thn}$	$< V_{GS} - V_{thn}$	Linear	$\mu_n C_{ox} \frac{W}{L} \cdot \left( (V_{GS} - V_{thn}) \cdot V_{DS} - \frac{V_{DS}^2}{2} \right)$
	$\geq V_{GS} - V_{thn}$	Saturation	$\frac{1}{2} \mu_n C_{ox} \frac{W}{L} \cdot (V_{GS} - V_{thn})^2$
$< V_{th}$		Subthreshold	0

PMOS:

$V_{GS}$	$V_{DS}$	Mode	$I_{DS}$
$\leq V_{thp}$	$> V_{GS} - V_{thp}$	Linear	$\mu_p C_{ox} \frac{W}{L} \cdot \left( (V_{GS} - V_{thp}) \cdot V_{DS} - \frac{V_{DS}^2}{2} \right)$
	$\leq V_{GS} - V_{thp}$	Saturation	$\frac{1}{2} \mu_n C_{ox} \frac{W}{L} \cdot (V_{GS} - V_{thp})^2$
$> V_{th}$		Subthreshold	0



4. (25 points) For this problem we consider a new technology that is not necessarily MOS. You can assume  $V_{dd} = 1V$ . We are told there are two "gates" available to us:

- $P$ -gate: 1-input gate where:

$$V_{out} = \begin{cases} 1 - 0.5V_{in} & V_{in} < 0.3 \\ 1.6 - 2.5V_{in} & 0.3 \leq V_{in} < 0.6 \\ 0.25 - 0.25V_{in} & 0.6 \leq V_{in} \end{cases} \quad (1)$$

- $Q$ -gate: 2-input gate where:  $V_{out} = |V_A - V_B|$


- (a) What logical function does the restoring  $P$ -gate perform? Identify the noise margins that will provide restoration for this gate.

Function: Inverter

$V_{OH}$	850mV
$V_{IH}$	600mV
$V_{IL}$	300mV
$V_{OL}$	100mV
$NM_L$	200mV
$NM_H$	250mV

- (b) What logical function does the non-restoring Q-gate perform and is it restoring? Draw a combination of P and Q gates that will serve as a restoring gate that performs the same logic function and identify the noise margins that will provide restoration for this new gate.

Function: XOR

 

$V_{OH}$	750mV
$V_{IH}$	600mV
$V_{IL}$	300mV
$V_{OL}$	150mV
$NM_L$	150mV
$NM_H$	150mV

$V_{IL}$  and  $V_{IH}$  are the inflection points of the P-gates. The outputs of each P-gate will be  $> 0.85$  or  $< 0.1$ . The worst-case low output will be when the P-gate outputs are 1 and 0.85, thus  $V_{OL} = 0.15$ ; the worst-case high output will be when the P-gate outputs are 0.1 and 0.85,  $V_{OH} = 0.75$