

ESE370: Circuit-Level Modeling, Design, and Optimization for Digital Systems

Lec 10: February 27, 2023
Energy and Power Tradeoffs



1

Previously

- Three components of power
 - Static
 - Dynamic
 - Short circuit
- $P_{tot} = P_{static} + P_{dyn} + P_{sc}$

Penn ESE 3700 Spring 2023 - Li

2

Switching


Dynamic Power



3

Switching Currents

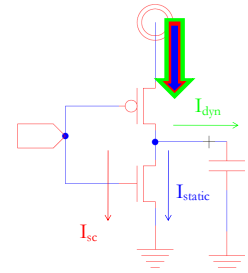- $I_{total}(t) = I_{static}(t) + I_{switch}(t)$
- $I_{switch}(t) = I_{sc}(t) + I_{dyn}(t)$



Penn ESE 3700 Spring 2023 - Li


4

Charging

- $I_{dyn}(t)$ – why is it changing?
 - $I_{ds} = f(V_{ds}, V_{gs})$
 - and V_{gs}, V_{ds} changing

$$I_{DS} \approx v_{sat} C_{OX} W \left(V_{GS} - V_T - \frac{V_{DSAT}}{2} \right)$$

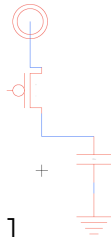
$$I_{DS} = \mu_n C_{OX} \left(\frac{W}{L} \right) \left[(V_{GS} - V_T) V_{DS} - \frac{V_{DS}^2}{2} \right]$$



Penn ESE 3700 Spring 2023 - Li

5

Switching Energy – focus on $I_{dyn}(t)$

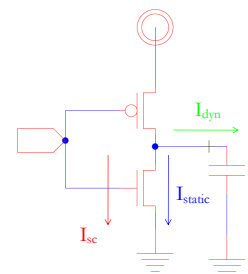

Penn ESE 3700 Spring 2023 - Li

6

Switching (Dynamic)


- CMOS circuit switching output from 0→1
 - Spends energy CV_{dd}^2 charging load
 - CV_{dd}^2 energy is pulled from the energy source

$$Q = \int I(t) dt = CV$$

$$E = \int P(t) dt$$

$$E = V_{dd} \int I(t) dt$$

$$E = CV_{dd}^2$$

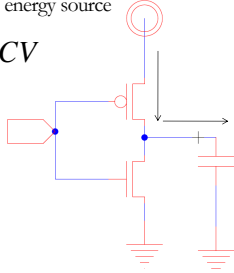

Penn ESE 3700 Spring 2023 - Li

7

Switching Power

- Every time output switches 0→1 pay:
 - $E = CV^2$
- $P_{dyn} = (\# 0 \rightarrow 1 \text{ trans}) \times CV^2 / \text{time}$

Penn ESE 3700 Spring 2023 - Li

8

Charging Power

- $P_{dyn} = (\# 0 \rightarrow 1 \text{ trans}) \times CV^2 / \text{time}$
- Often like to think about switching frequency
- Useful to consider per clock cycle
 - Frequency $f = 1/\text{clock-period} = \text{clock-cycles}/\text{time}$
- $P_{dyn} = (\# 0 \rightarrow 1 \text{ trans}/\text{clock-cycle}) CV^2 f$

Penn ESE 3700 Spring 2023 - Li

9

Data Dependent Activity


- Consider an 8b counter
 - How often do each of the following switch?
 - Low bit?
 - High bit?
- Assuming random inputs
 - Activity at output of nand2?
 - Activity at output of xor2?

Penn ESE 3700 Spring 2023 - Li

10

Gate Output Switching (random inputs)

Output states

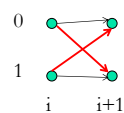

$$P(\text{out}_i \neq \text{out}_{i+1}) = P(\text{out}_i = 0) * P(\text{out}_{i+1} = 1) + P(\text{out}_i = 1) * P(\text{out}_{i+1} = 0)$$


Probability of output switch of nand2?
Probability of output switch of xor2?

Penn ESE 3700 Spring 2023 - Li

11

Gate Output Switching (random inputs)

Output states

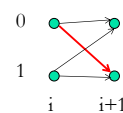

$$P(\text{out}_i \rightarrow \text{out}_{i+1} = 0 \rightarrow 1) = P(\text{out}_i = 0) * P(\text{out}_{i+1} = 1)$$

Penn ESE 3700 Spring 2023 - Li

12

Dynamic Power

- $P_{\text{dyn}} = (\#0 \rightarrow 1 \text{ trans/clock-cycle}) CV^2 f$
- Let $a = \text{activity factor}$
 - $a = \text{average } \# \text{tran}_{0 \rightarrow 1} / \text{clock}$
 - $a = \text{probability of } \# \text{tran}_{0 \rightarrow 1}$
- $P_{\text{dyn}} = aCV^2 f$

Penn ESE 3700 Spring 2023 - Li

13

Activity Factor

- Let $a = \text{activity factor}$
 - $a = \text{average } \# \text{tran}_{0 \rightarrow 1} / \text{clock}$
 - $a = \text{probability of } \# \text{tran}_{0 \rightarrow 1}$

$$a = p(\text{out}_i = 0)p(\text{out}_{i+1} = 1)$$

$$a = \frac{N_0}{2^N} \frac{N_1}{2^N} = \frac{N_0(2^N - N_0)}{2^{2N}}$$

Penn ESE 3700 Spring 2023 - Li

14

Switching


Short Circuit Power



15

Short Circuit Power

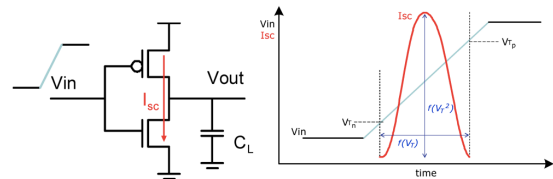- Between V_{TN} and $V_{dd} - V_{TP}$
 - Both N and P devices conducting




Penn ESE 3700 Spring 2023 - Li

16

Short Circuit Power

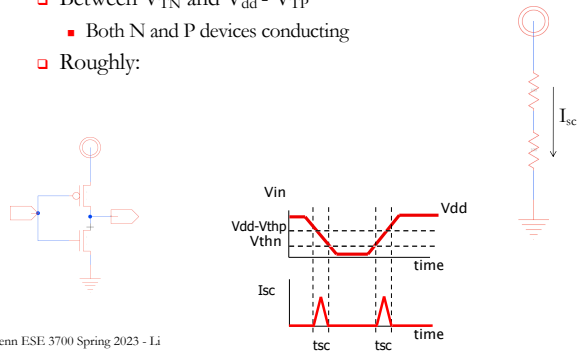- Between V_{TN} and $V_{dd} - V_{TP}$
 - Both N and P devices conducting
- Roughly:




Penn ESE 3700 Spring 2023 - Li

17

Peak Current

- I_{peak} around $V_{dd}/2$
 - If $|V_{TN}| = |V_{TP}|$ and sized equal rise/fall
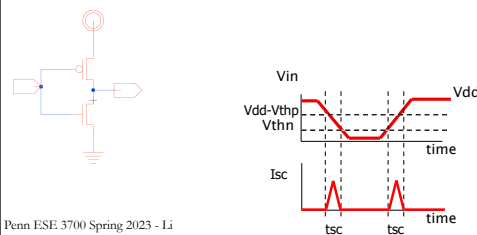
$$I_{DS} \approx v_{\text{sat}} C_{OX} W \left(V_{GS} - V_T - \frac{V_{DSAT}}{2} \right)$$



Penn ESE 3700 Spring 2023 - Li

18

Peak Current

- I_{peak} around $V_{dd}/2$
 - If $|V_{TN}| = |V_{TP}|$ and sized equal rise/fall

$$I_{DS} \approx v_{sat} C_{OX} W \left(V_{GS} - V_T - \frac{V_{DSAT}}{2} \right)$$

$$\int I(t) dt \approx I_{peak} \times t_{sc} \times \left(\frac{1}{2} \right)$$

Penn ESE 3700 Spring 2023 - Li

19

Peak Current

- I_{peak} around $V_{dd}/2$
 - If $|V_{TN}| = |V_{TP}|$ and sized equal rise/fall

$$I_{DS} \approx v_{sat} C_{OX} W \left(V_{GS} - V_T - \frac{V_{DSAT}}{2} \right)$$

$$\int I(t) dt \approx I_{peak} \times t_{sc} \times \left(\frac{1}{2} \right)$$

$$E = V_{dd} \times I_{peak} \times t_{sc} \times \left(\frac{1}{2} \right)$$

Penn ESE 3700 Spring 2023 - Li

20

Short Circuit Energy

- Make it look like switching an equivalent capacitance, C_{SC}

$$E = V_{dd} \times \left(I_{peak} \times t_{sc} \times \frac{1}{2} \right)$$

$$E = C_{SC} V_{dd}^2$$

Penn ESE 3700 Spring 2023 - Li

21

Short Circuit Energy

- Make it look like switching an equivalent capacitance, C_{SC}

$$E = V_{dd} \times \left(I_{peak} \times t_{sc} \times \frac{1}{2} \right)$$

$$E = C_{SC} V_{dd}^2$$

$$C_{SC} = \frac{I_{peak} t_{sc}}{2V_{dd}}$$

Penn ESE 3700 Spring 2023 - Li

22

Short Circuit Energy

- Every time switch ($0 \rightarrow 1$ and $1 \rightarrow 0$)
 - Also dissipate short-circuit energy: $E = C_{sc} V^2$
 - C_{sc} “fake” capacitance (for accounting)

Penn ESE 3700 Spring 2023 - Li

23

Total Power

- $P_{tot} = P_{static} + P_{sc} + P_{dyn}$
- $P_{dyn} + P_{sc} = \alpha C_{load} V^2 f + 2\alpha C_{sc} V^2 f$
- $P_{tot} \approx \alpha (C_{load} + 2C_{sc}) V^2 f + V I_s' (W/L) e^{-V_t/(nkT/q)}$



Penn ESE 3700 Spring 2023 - Li

24

Preclass 1 (Done in last lecture)

Device	V_{gs}	I_d
NMOS	$V_{gs} < V_{thn}$	$(3 \times 10^{-7}) e^{-\frac{V_{gs}-V_{thn}}{40mV}}$
	$V_{gs} > V_{thn}$	$1.8 \times 10^{-4} (V_{gs} - V_{thn})^2$
PMOS	$V_{gs} > V_{thp}$	$(3 \times 10^{-7}) e^{-\frac{V_{gs}-V_{thp}}{40mV}}$
	$V_{gs} < V_{thp}$	$-1.8 \times 10^{-4} (V_{gs} - V_{thp})^2$

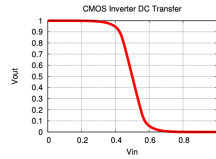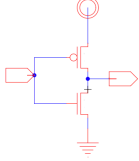Consider an inverter using the pmos and nmos devices described above:



Penn ESE 3700 Spring 2023 - Li

25

Preclass 1

V_{in}	I_{static}	$I_{dynamic}$	I_{sc}
0V			
140mV			
400mV			
500mV			
600mV			
860mV			
1V			

Penn ESE 3700 Spring 2023 - Li

26

Design Tradeoffs



27

Reduce Dynamic Power?


- $P_{dyn} = aCV^2 f$
- How do we reduce dynamic power?

Penn ESE 3700 Spring 2023 - Li


28

Reduce Activity Factor

Tree

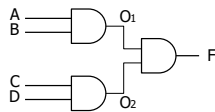

Chain

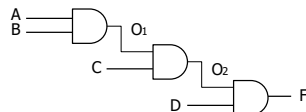

$$a = p(\text{out}_i = 0)p(\text{out}_{i+1} = 1)$$


$$a = \frac{N_0}{2^N} \frac{N_1}{2^N} = \frac{N_0(2^N - N_0)}{2^{2N}}$$

Penn ESE 3700 Spring 2023 - Li


29

Reduce Activity Factor

Tree

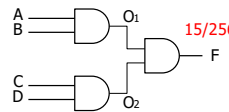

Chain

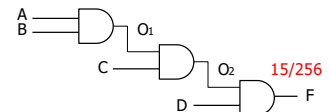


$$a = p(\text{out}_i = 0)p(\text{out}_{i+1} = 1)$$

$$a = \frac{N_0}{2^N} \frac{N_1}{2^N} = \frac{N_0(2^N - N_0)}{2^{2N}}$$

Penn ESE 3700 Spring 2023 - Li

30

Reduce Activity Factor

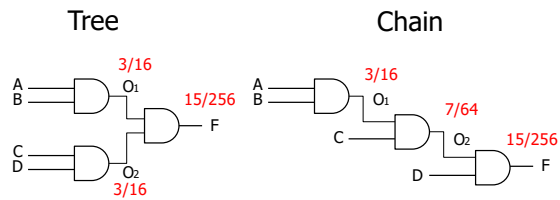

$$a = p(\text{out}_i = 0)p(\text{out}_{i+1} = 1)$$

$$a = \frac{N_0}{2^N} \frac{N_1}{2^N} = \frac{N_0(2^N - N_0)}{2^{2N}}$$

Penn ESE 3700 Spring 2023 - Li

31

Reduce V_{dd} (Preclass 2)

$$\square V_{dd}=520\text{mV}, V_{thn}=|V_{thp}|=300\text{mV}$$

V_{in}	I_{static}	$I_{dynamic}$	I_{sc}
0V			
140mV			
260mV			
380mV			
520mV			

Penn ESE 3700 Spring 2023 - Li

32

Reduce V_{dd} (Preclass 2)

$$\square V_{dd}=520\text{mV}, V_{thn}=|V_{thp}|=300\text{mV}$$

V_{in}	I_{static}	$I_{dynamic}$	I_{sc}
0V	180pA	39.6uA	
140mV	6nA	14.4uA	
260mV	111nA		
380mV	6nA	14.4uA	
520mV	180pA	39.6uA	

Penn ESE 3700 Spring 2023 - Li

33

Reduce V_{dd}

□ What happens as reduce V ?

- Energy?
 - Static
 - Switching
- Delay?

Penn ESE 3700 Spring 2023 - Li

34


Reduce V_{dd} :

$$\square \tau_{gd}=Q/I=(CV)/I$$

$$\square I_d=(\mu C_{ox}/2)(W/L)(V_{gs}-V_{TH})^2$$

□ τ_{gd} impact?
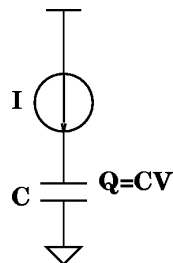
$$\square \tau_{gd} \propto \frac{1}{V}$$



Penn ESE 3700 Spring 2023 - Li

35

Reduce V_{dd} :

$$\square \tau_{gd}=Q/I=(CV)/I$$


$$\square I_d=(\mu C_{ox}/2)(W/L)(V_{gs}-V_{TH})^2$$

□ τ_{gd} impact?

$$\square \tau_{gd} \propto \frac{1}{V}$$

□ Ignoring leakage:

$$E \propto V^2$$

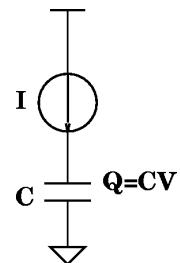

Penn ESE 3700 Spring 2023 - Li

36

Reduce V_{dd} :

- $\tau_{gd} = Q/I = (CV)/I$
- $I_d = (\mu C_{ox}/2)(W/L)(V_{gs} - V_{TH})^2$
- τ_{gd} impact?
- $\tau_{gd} \propto \frac{1}{V}$
- Ignoring leakage:
 $E \propto V^2$
 $E\tau^2 \approx Const$

Penn ESE 3700 Spring 2023 - Li

37

Reduce V_{dd} : Velocity Saturation

- $\tau_{gd} = Q/I = (CV)/I$
- $I_d = (v_{sat} C_{ox})(W)(V_{gs} - V_{TH} - V_{DSAT}/2)$
- τ_{gd} impact?

Penn ESE 3700 Spring 2023 - Li

38

Reduce V_{dd} (Preclass 3)

- $V_{thn} = |V_{thp}| = 300mV, V_{in} = V_{dd}$, estimate $E\tau$

V_{dd}	I_{dyn}	$\tau/(\tau@V_{dd}=1)$	$E_{switch}/(E_{switch}@V_{dd}=1)$	$E\tau$
1V				
700mV				
500mV				
350mV				
260mV				

Penn ESE 3700 Spring 2023 - Li

39

Reduce V_{dd} (Preclass 3)

- $V_{thn} = |V_{thp}| = 300mV, V_{in} = V_{dd}$, estimate $E\tau$

V_{dd}	I_{dyn}	$\tau/(\tau@V_{dd}=1)$	$E_{switch}/(E_{switch}@V_{dd}=1)$	$E\tau$
1V	126uA	1	1	1
700mV	72uA	1.225	0.49	.6
500mV	36uA	1.75	0.25	.437
350mV	9uA	4.9	0.12	.588
260mV	111nA	295	0.07	20.6

Penn ESE 3700 Spring 2023 - Li

40

Increase V_{th} (Preclass 4)

- What is impact of increasing threshold on
 - Delay?
 - Leakage?
- $V_{dd} = 1V, V_{in} = V_{dd}$

$V_{thn} = -V_{thp}$	I_{dyn}	$\tau/(\tau@V_{th}=300mV)$	I_{static}	$I_{static}/(I_{static}@V_{th}=300mV)$
300mV				
460mV				
600mV				

Penn ESE 3700 Spring 2023 - Li

41

Increase V_{th} (Preclass 4)

- What is impact of increasing threshold on
 - Delay?
 - Leakage?
- $V_{dd} = 1V, V_{in} = V_{dd}$

$V_{thn} = -V_{thp}$	I_{dyn}	$\tau/(\tau@V_{th}=300mV)$	I_{static}	$I_{static}/(I_{static}@V_{th}=300mV)$
300mV	126uA	1	180pA	1
460mV	97uA	1.3	3.6pA	0.02
600mV	72uA	1.75	108fA	0.0006

Penn ESE 3700 Spring 2023 - Li

42

Big Ideas

- Three components of power
 - Static
 - Dynamic
 - Short-circuit
- $P_{tot} = P_{static} + P_{dyn} + P_{sc}$
- Tradeoff (knobs: V_{dd} , V_{th} , α , etc.)
 - Speed
 - Switching energy
 - Leakage energy
 - Want to look at the energy-delay product for optimality
- Energy-Delay tradeoff: $E\tau^2$, $E\tau$

Penn ESE 3700 Spring 2023 - Li

43

Admin

- HW 5 due Friday 2/24
- Proj 1 release Friday 2/24
 - Design 8-bit adder (baseline design)
 - Due four weeks on Friday 3/24

Penn ESE 3700 Spring 2023 - Li

44

Acknowledgement

- Prof. André DeHon (University of Pennsylvania)
- Prof. Tania Khanna (University of Pennsylvania)

Penn ESE 3700 Spring 2023 - Li

45