

ESE370: Circuit-Level Modeling, Design, and Optimization for Digital Systems

Lec 11: March 1, 2023
Ratioed Logic and Design-Space Exploration



1

Today

- Ratioed Logic
 - Break all the rules... (lose our nice properties)
 - Not rail-to-rail signals, steady-state-current...
 - Correctness

Penn ESE 3700 Spring 2023 - Li

2

Ratioed Logic



3

Previously

- Restoration and Noise Margins
 - Allows for gate abstraction
- CMOS Gates
 - Drive outputs rail-to-rail
 - Only one PDN/PUN turned on in steady state
 - Only subthreshold leakage current in steady state

Penn ESE 3700 Spring 2023 - Li

4

Today


- Ratioed Gates
 - Break all the rules... (nice properties)
 - No rail-to-rail outputs, steady-state-current is not subthreshold...
 - Logic correctness
 - Performance
 - Power implications

Penn ESE 3700 Spring 2023 - Li

5

Idea

 - Building both pull-up and pull-down can be expensive – many gates
- Seems wasteful to build logic function twice
 - Once in pullup, once in pulldown
 - Large gate capacitance




Penn ESE 3700 Spring 2023 - Li

6

Idea

 - Maybe only need to build one
- Build NFET pulldown
 - Exploit high N mobility
 - traditional




Penn ESE 3700 Spring 2023 - Li

7

Ratioed Inverter

 
- Does this work?
 - What is V_{out} for $V_{in}=Gnd$?
 - What is V_{out} for $V_{in}=V_{dd}$?



Penn ESE 3700 Spring 2023 - Li

8

Ratioed Inverter in 22nm

 


Penn ESE 3700 Spring 2023 - Li

9

Ratioed Inverter (Preclass 1)

 
- How do we need to size N to make it “work”?
 - $V_{DD}=0.8$



Penn ESE 3700 Spring 2023 - Li

10


Ratioed Inverter in 22nm

 

Penn ESE 3700 Spring 2023 - Li


11

DC Transfer Function

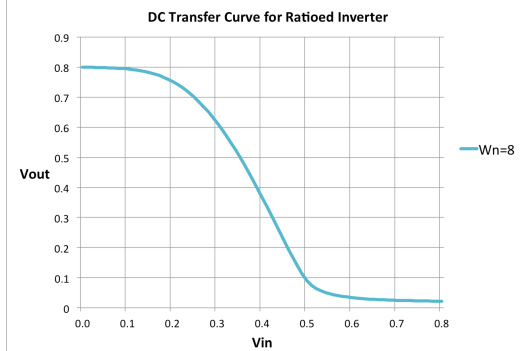

Penn ESE 3700 Spring 2023 - Li

12

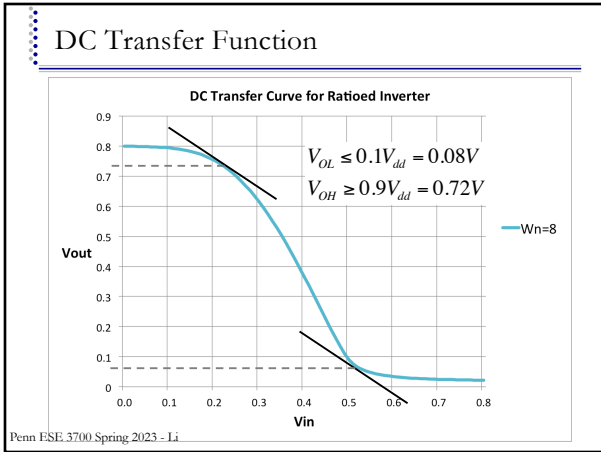


13

Ratioed Inverter (Preclass 1)


- How do we need to size P to make it work?
 - $V_{DD}=0.8$

Penn ESE 3700 Spring 2023 - Li

14

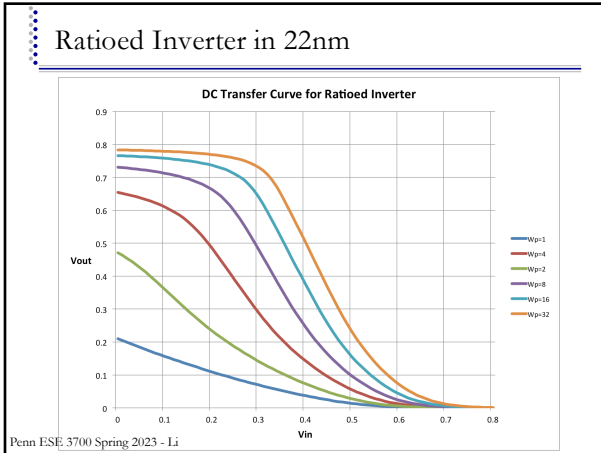

15

 

16

P vs. N

- Conclusion:** still prefer N to P for ratioed logic

DC Transfer Curve for Ratioed Inverter

Wp=1, Wp=4, Wp=8, Wp=16, Wp=32

Penn ESE 3700 Spring 2023 - Li

17

Noise Margin Tradeoff

- What is impact of increasing noise margin?
 - On size
 - On input capacitance

DC Transfer Curve for Ratioed Inverter


Wp=1, Wp=4, Wp=8, Wp=16, Wp=32

Penn ESE 3700 Spring 2023 - Li

18

Size for $R_0/2$ drive?

 - How do we size for $R_0/2$ drive?
 - (assume $R_{0p}=R_{0n}$ for CMOS)



Penn ESE 3700 Spring 2023 - Li


19

Size for $R_0/2$ drive? (Preclass 2)

- How do we size for $R_0/2$ drive?
 - (assume $R_{0p}=R_{0n}$ for CMOS)

$$R_{drive} = \frac{R_{op}}{W_p} = \frac{R_0}{W_p} = \frac{R_0}{2}$$

$$\Rightarrow W_p = 2$$

 

Penn ESE 3700 Spring 2023 - Li

20

Size for $R_0/2$ drive?


- How do we size for $R_0/2$ drive? What is C_{in} ?
 - (assume $R_{0p}=R_{0n}$ for CMOS)

$$R_{drive} = \frac{R_{op}}{W_p} = \frac{R_0}{W_p} = \frac{R_0}{2}$$

$$\Rightarrow W_p = 2$$

$$W_n > 8W_p$$

$$\Rightarrow W_n = 16$$

 


Penn ESE 3700 Spring 2023 - Li

21

Static Power

 - I_{static} ?
- Input low-Output high?
 - I_{leak}
- Input high-Output low?
 - I_{pmos_on}
 - $\sim V_{dd}/(R_0/2)$ -- for our sample case



Penn ESE 3700 Spring 2023 - Li

22

Total Power

$$P_{tot} \approx a(C_{load} + 2C_{sc})V^2f$$

Penn ESE 3700 Spring 2023 - Li

23

Total Power

$$P_{tot} \approx a(C_{load} + 2C_{sc})V^2f$$

$$+ p(V_{out=low})V^2/R_{pon}$$

$$+ p(V_{out=high})VI_s(W/L)e^{-Vt/(nkT/q)}$$

$p(V_{out=low})$ – probability the output is low

$p(V_{out=high})$ – probability the output is high

$$p(V_{out=high})=1-p(V_{out=low})$$

Penn ESE 3700 Spring 2023 - Li

24

Compare Static CMOS

For $R_{drive} = R_0/2$ inverter (assume $R_{0p} = R_{0n}$ for CMOS)


- Total Transistor Width?
- Input capacitance load?

Penn ESE 3700 Spring 2023 - Li

25

How do we size for $R_0/2$ drive?

- 2-input nand?

 

Penn ESE 3700 Spring 2023 - Li


26

How do we size for $R_0/2$ drive?

- 2-input nand?

$$R_{drive} = \frac{R_{op}}{W_p} = \frac{R_0}{W_p} = \frac{R_0}{2}$$

$$\Rightarrow W_p = 2$$

 

Penn ESE 3700 Spring 2023 - Li

27

How do we size for $R_0/2$ drive?

- 2-input nand? What is C_{in} ?


$$R_{drive} = \frac{R_{op}}{W_p} = \frac{R_0}{W_p} = \frac{R_0}{2}$$

$$\Rightarrow W_p = 2$$

$$R_{drive,pdn} = \frac{2R_0}{W_n} = \frac{R_0}{W_n/2}$$

$$W_n/2 > 8W_p$$

$$\Rightarrow W_n = 32$$

 


Penn ESE 3700 Spring 2023 - Li

28

How do we size for $R_0/2$ drive?

- 2-input nor?

 

Penn ESE 3700 Spring 2023 - Li

29

How do we size for $R_0/2$ drive?


- 2-input nor? What is C_{in} ?

$$R_{drive} = \frac{R_{op}}{W_p} = \frac{R_0}{W_p} = \frac{R_0}{2}$$

$$\Rightarrow W_p = 2$$

$$W_n > 8W_p$$

$$\Rightarrow W_n = 16$$

 


Penn ESE 3700 Spring 2023 - Li

30

How do we size for $R_0/2$ drive? (Preclass 3)

 
- k-input nor?
- What is the input capacitance for k-input nor?



Penn ESE 3700 Spring 2023 - Li

31

 Which Implementation is faster in ratioed logic?



Penn ESE 3700 Spring 2023 - Li

32

Design Space Exploration



33

Design Problem

- Function: Identify equivalence of two 32bit inputs
- Optimize: Minimize total energy
- Assumptions: Match case uncommon
 - I.e. Most of the time, the inputs won't be matched
- Deliberately focus on Energy to complement project
 - ...but will still talk about delay

Last page of preclass

Penn ESE 3700 Spring 2023 - Li

34

Idea: Design Space Explore

- Identify options
 - All the knobs you can turn
- Explore space systematically
- Formulate continuum where possible
 - i.e. formulate trends and tradeoffs quantitatively

Penn ESE 3700 Spring 2023 - Li

35

Problem Solvable (preclass 4.1)

- Is it feasible?
 - First, make sure we have a solution so we know our main goal is optimization
- How do we decompose the problem?

Penn ESE 3700 Spring 2023 - Li

36


Problem Solvable (preclass 4.2)

- Is it feasible?
 - First, make sure we have a solution so we know our main goal is optimization
- How do we decompose the problem?
- What look like built out of nand2 gates and inverters?

Penn ESE 3700 Spring 2023 - Li

37

Nand2 and inverter implementation

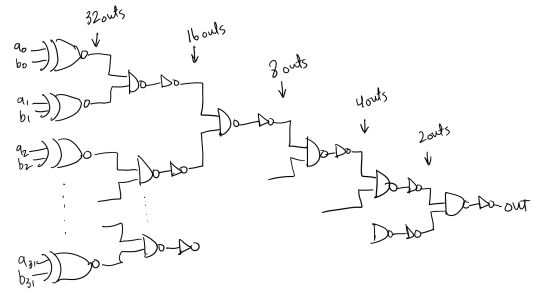

Penn ESE 3700 Spring 2023 - Li

38

Single Gate Match Condition (preclass 4.3)

- Design a single gate for match comparison

Penn ESE 3700 Spring 2023 - Li

39

Total Power

- Static CMOS:
 - $P_{tot} \approx a(C_{load} + 2C_{sc})V^2f + VT_s(W/L)e^{-V_t/(nkT/q)}$
- Ratioed Logic:
 - $P_{tot} \approx a(C_{load} + 2C_{sc})V^2f$
 $+ p(V_{out=low})V^2/R_{pon}$
 $+ (1-p(V_{out=low}))VT_s(W/L)e^{-V_t/(nkT/q)}$
- What can we do to reduce power?

Penn ESE 3700 Spring 2023 - Li

40

Knobs (preclass 4.4)

- What are the options and knobs we can turn?

Penn ESE 3700 Spring 2023 - Li

41


Design Space Dimensions

- Topology
 - (A) Gate choice, logical optimization
 - (B) Fanin, fanout, (C) Serial vs. parallel
- Gate style / logic family
 - (D) CMOS, Ratioed (N load, P load)
- (E) Transistor Sizing
- (F) Vdd
- (G) Vth

Penn ESE 3700 Spring 2023 - Li

42

Gate

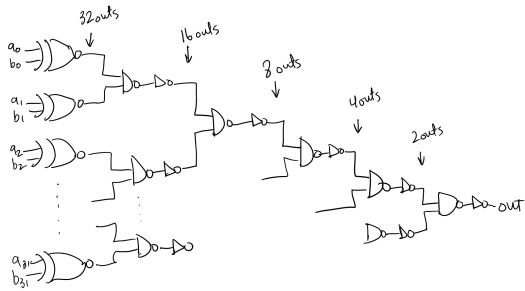


Penn ESE 3700 Spring 2023 - Li

43

Gate Choice

□ (A) What gates might we build?

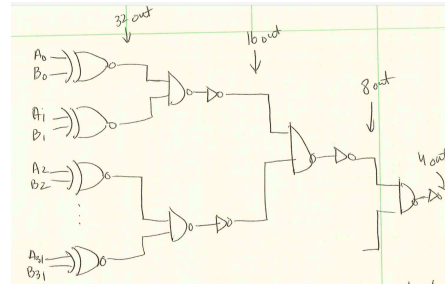


Penn ESE 3700 Spring 2023 - Li

44

Gate Choice

□ (A) What gates might we build?

 


Penn ESE 3700 Spring 2023 - Li

45

Gate Fan-in

□ (B) High fan-in?

 


Penn ESE 3700 Spring 2023 - Li

46

Gate Topology

□ (C) Serial-Parallel?

 

Penn ESE 3700 Spring 2023 - Li

47

(D) Logic Family

□ Considerations for each logic family?

- CMOS
- Ratioed with PMOS load
- Ratioed with NMOS load

□ Ratioed Logic

- Reduced C_{loads} result in lower switching power (P_{dyn} ↓)
- Increased static power

Penn ESE 3700 Spring 2023 - Li

48

(E) Sizing

- How do we want to size gates?
 - Sizing transistors up will reduce delay →
 - Reduces short circuit power

$$E = V_{dd} \times \left(I_{peak} \times t_{sc} \times \left(\frac{1}{2} \right) \right)$$

- Increases dynamic power

Penn ESE 3700 Spring 2023 - Li

49


(F) Reduce Vdd

- What happens as reduce V?

- Energy?
 - Dynamic ↓
 - Static ↓
- Switching Delay? ↑

- $\tau_{gd} = Q/I = (CV)/I$
- $I_d = (\mu C_{OX}/2)(W/L)(V_{gs} - V_{TH})^2$
- τ_{gd} impact?
- $\tau_{gd} \propto 1/V$

- Limit on Vdd?

 

Penn ESE 3700 Spring 2023 - Li


50

(G) Increase V_{th}

- What is impact of increasing threshold on

- Dynamic Energy? ↓
- Leakage Energy? ↓
- Delay? ↑

 - $\tau_{gd} = Q/I = (CV)/I$
- $I_{ds} = (v_{sat} C_{OX})(W)(V_{gs} - V_{TH} - V_{DSAT}/2)$



Penn ESE 3700 Spring 2023 - Li

51

Ideas

- There are other logic disciplines
- You have the tools to analyze
- Ratioed Logic
 - Tradeoff noise margin for
 - Reduced area? Capacitive load?
 - Dissipates non-leakage static power in one input case
- We know many things we can do to our circuits
- Design space is large
- Systematically identify dimensions
- Identify continuum (trends) tuning when possible
- Watch tradeoffs ...but don't over-tune

Penn ESE 3700 Spring 2023 - Li

52

Admin

- Project 1 out now
 - Design 8-bit ripple-carry adder
 - You already know how to do this
 - Refresh yourself on binary addition of 2 bits
 - Work **individually**
 - Full Report due F 3/24
- No in-class lecture (3/13)
 - Monday (after spring break)
 - Work on your project

Penn ESE 3700 Spring 2023 - Li

53

Acknowledgement

- Prof. André DeHon (University of Pennsylvania)
- Prof. Tania Khanna (University of Pennsylvania)

Penn ESE 3700 Spring 2023 - Li

54