

ESE370: Circuit-Level Modeling, Design, and Optimization for Digital Systems

Lec 12: March 15, 2023
 Design Space Exploration (con't)
 Pass Transistor Logic



1

Today

- Pass Transistor Logic
- Pass Transistor Circuit
 - $C_{diff} > 0$
 - Output levels
 - Cascading
 - Series pass transistors?
 - Delay

Penn ESE 3700 Spring 2023 - Li

2


Pass Transistor Logic



3

Pass Transistor Logic (Preclass 1)

- What does this do?

 


Penn ESE 3700 Spring 2023 - Li

4

Identify Function (Preclass 2)

- What function is this?

 


Penn ESE 3700 Spring 2023 - Li

5

Area

- Compare PT with CMOS circuit?

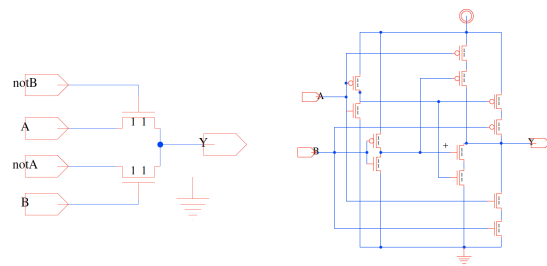


Penn ESE 3700 Spring 2023 - Li

6

Output

- Is this a regenerating/restoring gate?

 


Penn ESE 3700 Spring 2023 - Li

7

Output


 
- What does output look like (DC transfer)?
 - (B=1, notB=0, sweep A, notA=CMOS inv(A))



Penn ESE 3700 Spring 2023 - Li

8

Pass TR transfer (B=1)

  


Penn ESE 3700 Spring 2023 - Li

9

XOR Output


- Reasonable Input to CMOS Inverter?

 

Penn ESE 3700 Spring 2023 - Li

10

Pass Transistor xor2 with inv restore

 

Penn ESE 3700 Spring 2023 - Li

11

Required to use?


- What should we add to make suitable comparison with CMOS?

Penn ESE 3700 Spring 2023 - Li

12

Restore Output

 - What should we add to make suitable comparison with CMOS?




Penn ESE 3700 Spring 2023 - Li

13

Restore Output


- Area? (compare to CMOS)

 

Penn ESE 3700 Spring 2023 - Li

14


Chain Together

 

Penn ESE 3700 Spring 2023 - Li

15

Analyze Stage

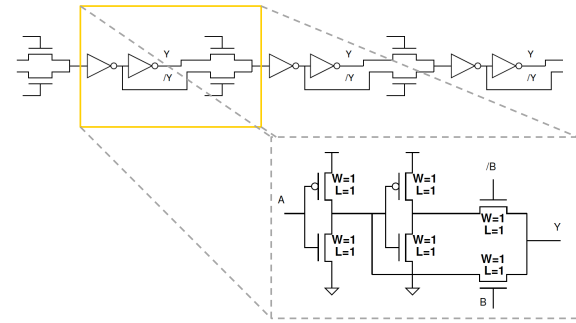


Penn ESE 3700 Spring 2023 - Li

16

Impact of Capacitance

 - $C_{GS} = C_{GCS} + C_{GSO}$
- $C_{GD} = C_{GCD} + C_{GDO}$
- $C_{GB} = C_{GCB}$
- $C_{SB} = C_{diff}$
- $C_{DB} = C_{diff}$



Penn ESE 3700 Spring 2023 - Li

17


Contact/Diffusion Capacitance

- C_j – diffusion depletion
- C_{jsw} – sidewall capacitance
- L_S – length of diffusion

$$C_{diff} = C_j L_S W + C_{jsw} (2L_S + W)$$

$$\text{Define: } C_{diff0} \approx \gamma C_0$$

 
$$C_{diff} \approx W C_{diff0} = W \cdot \gamma C_0$$



Penn ESE 3700 Spring 2023 - Li

18

First Order Model

 

Switch

- Loads **all terminals** capacitively
 - Draw no steady-state current for a CMOS gate
 - Does not impact steady-state output voltage
 - Impacts Settling time/Delay
- Has finite drive strength
 - Could form voltage divider with resistive load
 - Impacts Settling time/Delay

Penn ESE 3700 Spring 2023 - Li

19

First Order Delay

- R_0 = Resistance of minimum size NMOS device
- C_0 = gate capacitance of minimum size NMOS device
- C_{diff0} = diffusion capacitance on minimum size NMOS
 - $C_{diff0} = \gamma C_0$
- $R_{drive} = R_0/W$
- $C_g = WC_0$
- $C_{diff} = WC_{diff0} = \gamma WC_0$


Penn ESE 3700 Spring 2023 - Li

20

Inverter Delay

Delay driving another (min size) inverter?

 
- Include $C_{diff} = \gamma C_g = \gamma WC_0$



Penn ESE 3700 Spring 2023 - Li

21

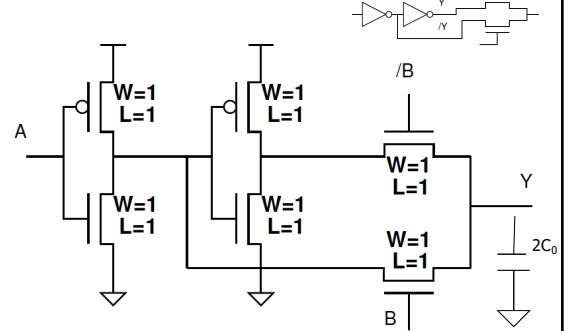Delay $A=1, B=0, C_{diff0} = \gamma C_0$ (Preclass 3)




Penn ESE 3700 Spring 2023 - Li

22

Delay $A=1, B=0, C_{diff0} = \gamma C_0$ (Preclass 3)

What's the equivalent RC circuit?

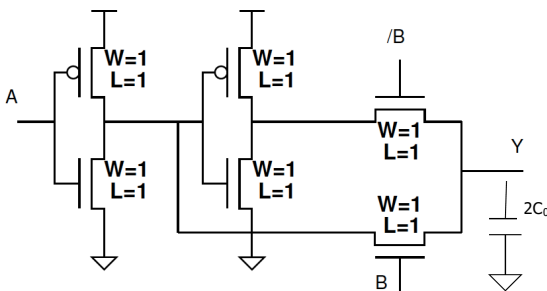


Penn ESE 3700 Spring 2023 - Li

23

Delay $A=1, B=0, C_{diff0} = \gamma C_0$ (Preclass 3)

What's the equivalent RC circuit?

 

Penn ESE 3700 Spring 2023 - Li

24

Delay A=1, B=0, $C_{diff0}=\gamma C_0$? (Preclass 3)

- What's the equivalent RC circuit?

Penn ESE 3700 Spring 2023 - Li

25

Delay A=1, B=0, $C_{diff0}=\gamma C_0$? (Preclass 3)

- What's the equivalent RC circuit?
 - Delay from A to Y?

Penn ESE 3700 Spring 2023 - Li

26

Delay A=1, B=1, $C_{diff0}=\gamma C_0$? (Preclass 3)

Penn ESE 3700 Spring 2023 - Li

27

Delay A=1, B=1, $C_{diff0}=\gamma C_0$? (Preclass 3)

- What's the equivalent RC circuit?

Penn ESE 3700 Spring 2023 - Li

28

Delay A=1, B=1, $C_{diff0}=\gamma C_0$? (Preclass 3)

- What's the equivalent RC circuit?

Penn ESE 3700 Spring 2023 - Li

29

Bonus

- What does this do?


A	B	Y
0	0	
0	1	
1	0	
1	1	

Penn ESE 3700 Spring 2023 - Li

30

Bonus

What does this do?

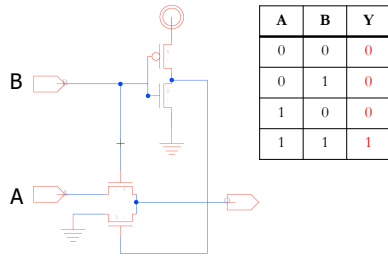

A	B	Y
0	0	0
0	1	0
1	0	0
1	1	1

More examples in the text

Penn ESE 3700 Spring 2023 - Li

31


Cascading Pass Transistors



32

Chain without Inverters

What if we did this?

 


Penn ESE 3700 Spring 2023 - Li

33

Chain without Inverters

Extract key path

 

Penn ESE 3700 Spring 2023 - Li


34

Voltage of Chain (Preclass 4)

What is voltage at output?

$$V_{dd}=1V$$

$$V_{thn}=-V_{thp}=0.3V$$

 

Penn ESE 3700 Spring 2023 - Li


35

Voltage of Chain (Preclass 4)

What is voltage at output?

$$V_{dd}=1V$$

$$V_{thn}=-V_{thp}=0.3V$$

 


Penn ESE 3700 Spring 2023 - Li

36

How compare (Preclass 4)


Compare

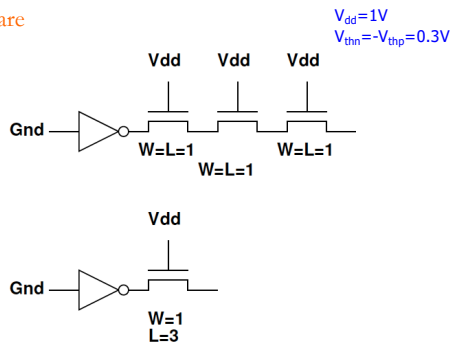

Penn ESE 3700 Spring 2023 - Li

37

DC Analysis – chain of 3 vs length of 3

 


Penn ESE 3700 Spring 2023 - Li

38

Conclude

 
- Can chain any number of pass transistors and only drop a single V_{th}



Penn ESE 3700 Spring 2023 - Li

39


Transient

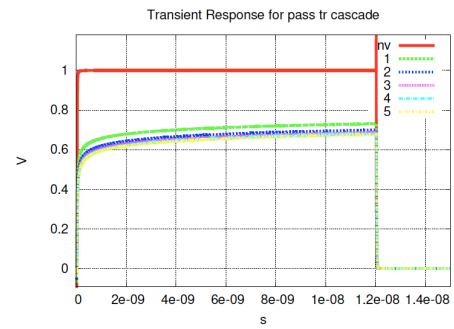

Penn ESE 3700 Spring 2023 - Li

40

Transient: Zoomed Closeup

 


Penn ESE 3700 Spring 2023 - Li

41

Capacitance

 - What is output capacitance per stage?
 - I.e. What is the capacitance at output y?




Penn ESE 3700 Spring 2023 - Li

42

Delay Setup

- What does RC circuit look like?

 


Penn ESE 3700 Spring 2023 - Li

43

Gate Cascade? (Preclass 5)

- What are the voltages?

$$V_{dd}=1V$$
$$V_{thn}=-V_{thp}=0.3V$$

 


Penn ESE 3700 Spring 2023 - Li

44

Conclude

 - Cannot cascade degraded inputs into **gates**.



Penn ESE 3700 Spring 2023 - Li

45

Idea

- There are other circuit disciplines
- Can use pass transistors for logic
 - Even chains of pass transistors
 - Mostly gives area win, sometimes gives delay win
 - Will talk more about delay on Wednesday
- Do not cascade as easily as CMOS

Penn ESE 3700 Spring 2023 - Li

46

Admin

- Project 1 out now
 - Design 8-bit ripple-carry adder
 - You already know how to do this
 - Refresh yourself on binary addition of 2 bits
 - Work **individually**
 - Full Report due F 3/24
 - **Can't pass the class if you don't turn in projects**
 - Can't do project last minute

Penn ESE 3700 Spring 2023 - Li

47

Logic Types

- CMOS Gates
 - Dual pull-down and pull-up networks, only one enabled at a time
 - Performance of gate is strong function of the fanin of gate
 - Techniques to improve performance include sizing, input reordering, and buffering (staging)
- Ratioed Gates
 - Have active pull-down (-up) network connected to load device
 - Reduced gate complexity at expense of static power asymmetric transfer function
 - Techniques to improve performance include sizing to improve noise margins and reduce static power
- Pass Gates
 - Implement logic gate as switch network for reduced area and load capacitance
 - Long cascades of switches result in quadratic increase in delay
 - Also suffer from reduced noise margins (V_T drop)
 - Use level-restoring buffers to improve noise margins

Penn ESE 3700 Spring 2023 - Li

□ Dynamic logic ... coming up soon

48

Acknowledgement

- Prof. André DeHon (University of Pennsylvania)
- Prof. Tania Khanna (University of Pennsylvania)

Penn ESE 3700 Spring 2023 - Li