

ESE370: Circuit-Level Modeling, Design, and Optimization for Digital Systems

Lec 13: March 20, 2023

Distributed RC Wire and Elmore Delay






Today

- Estimate delay in RC Network
 - Elmore delay calculation
- Apply to wire delay
- Apply to pass transistor circuits
- Apply to CMOS gates


Distributed RC (setup)




What is response? (Preclass 1)

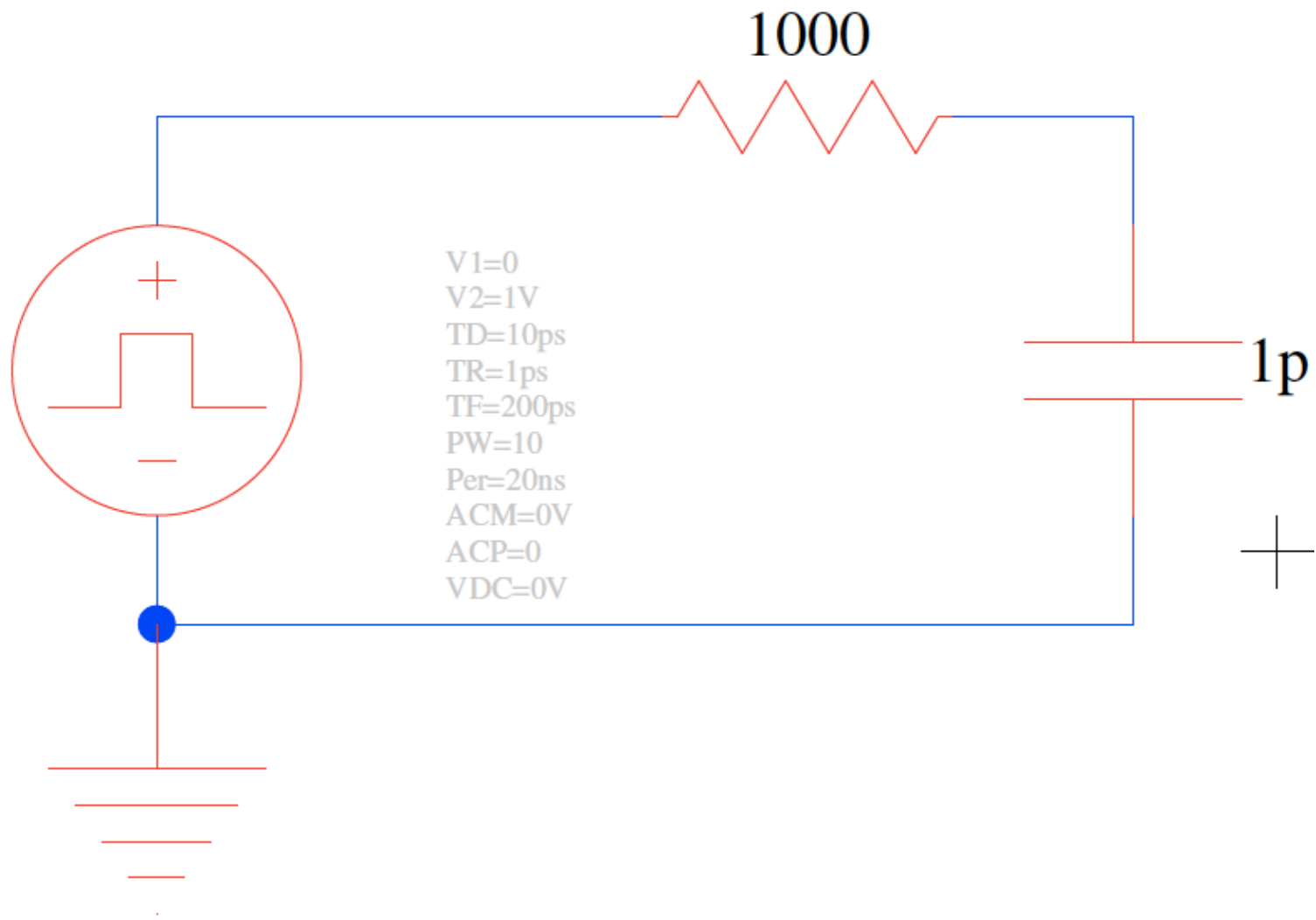

What is response? (Preclass 1)

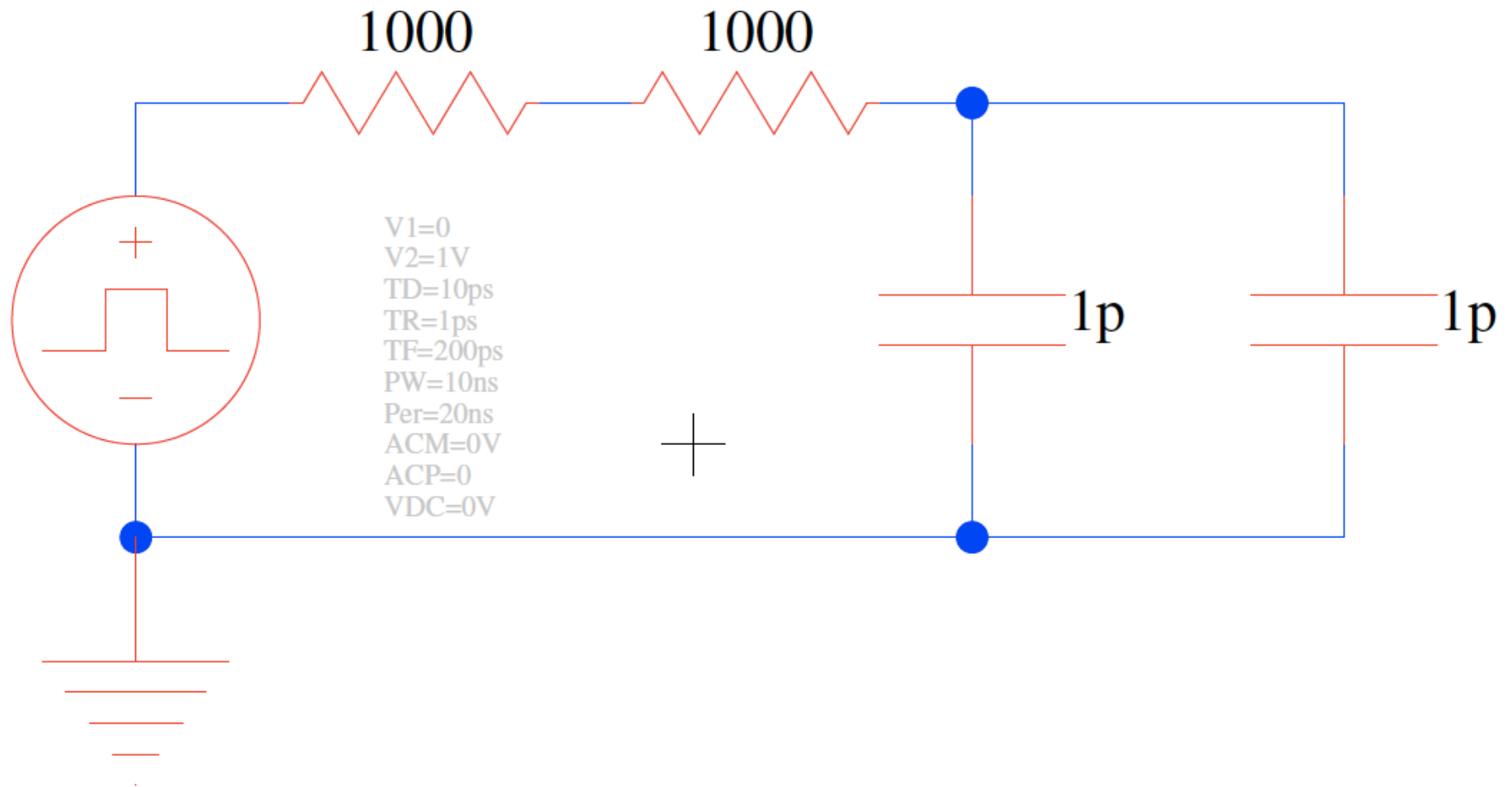


What is response? (Preclass 1)

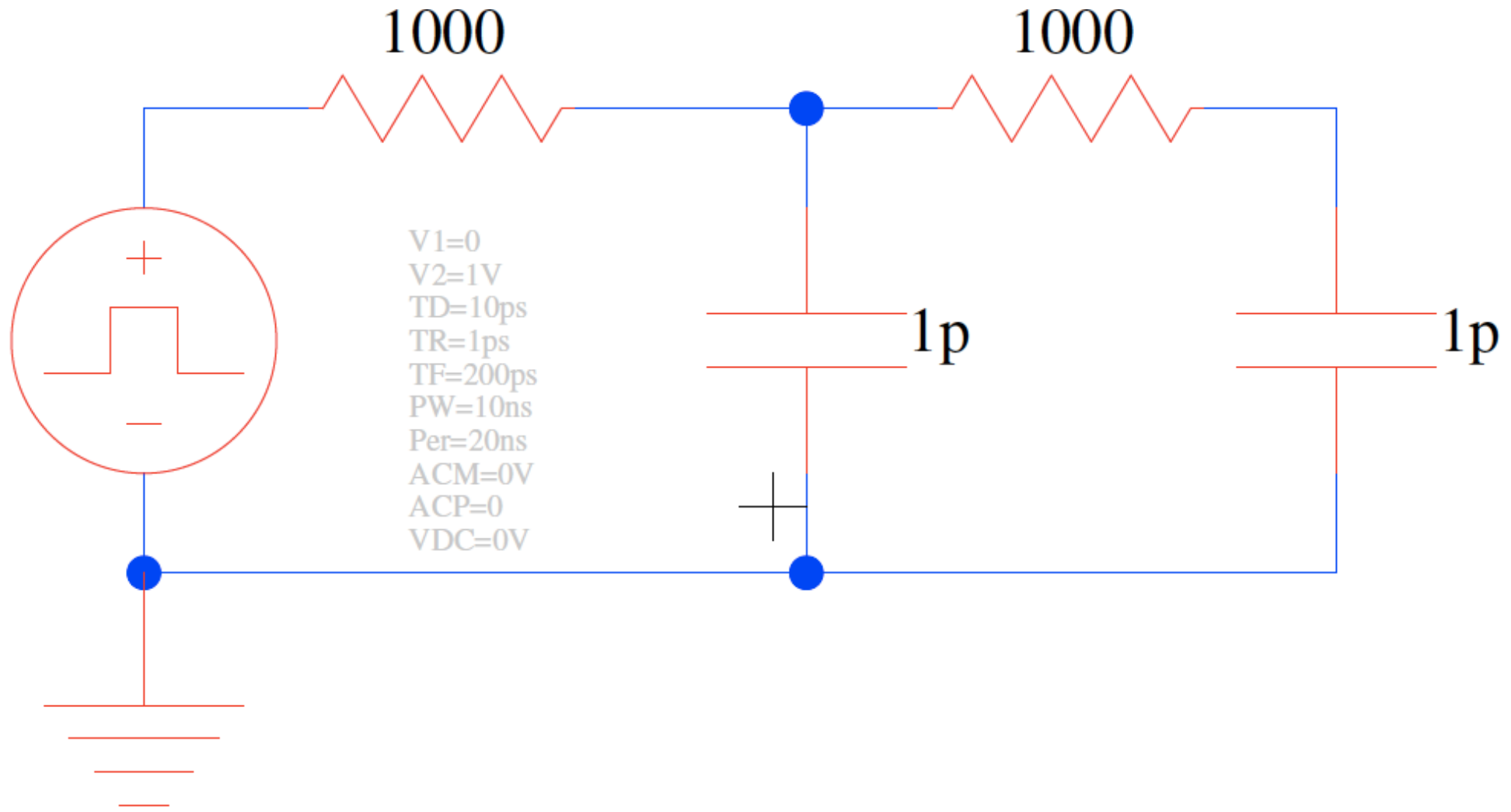




SPICE Response

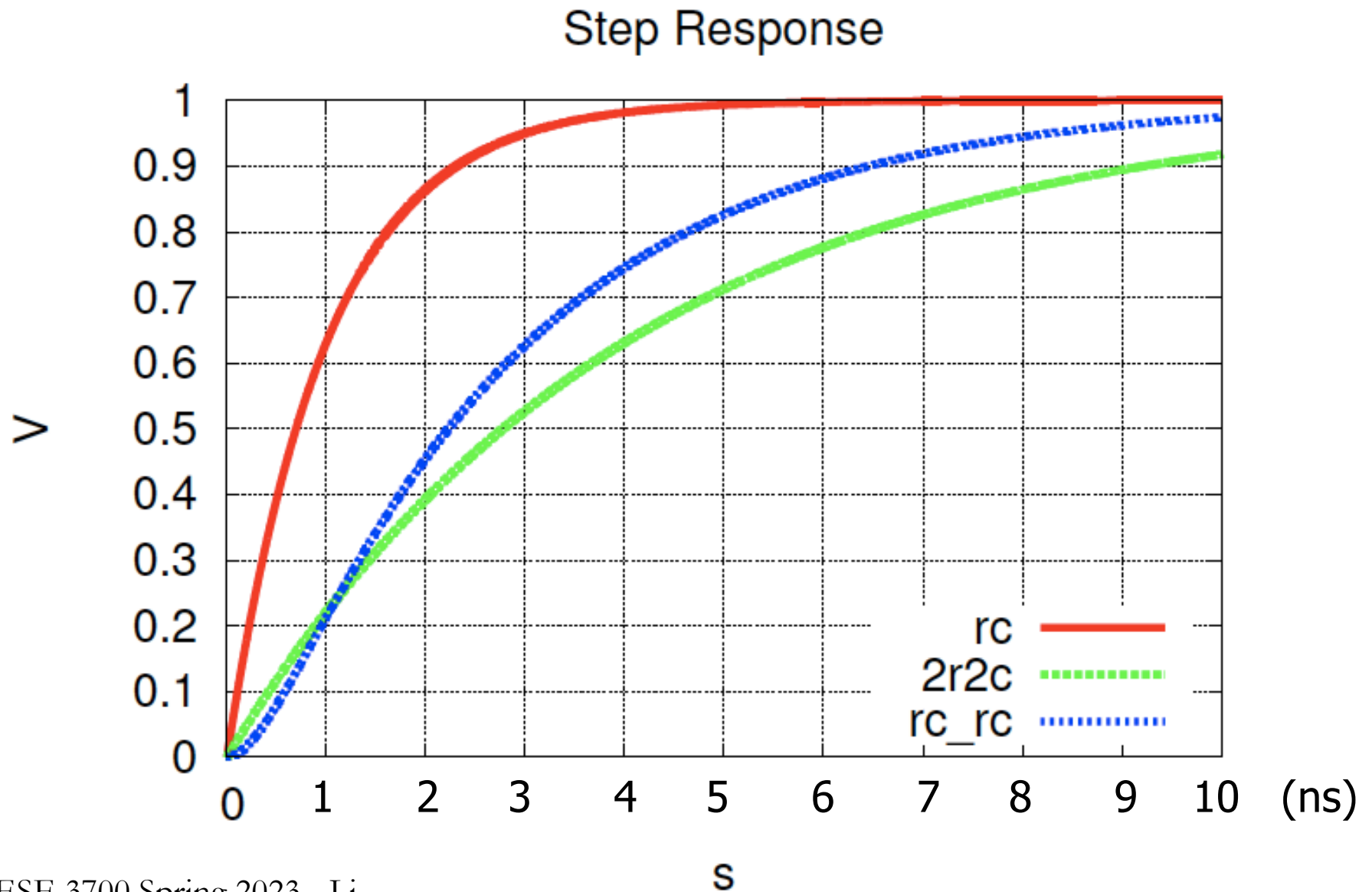





SPICE Response

 


Intuition

 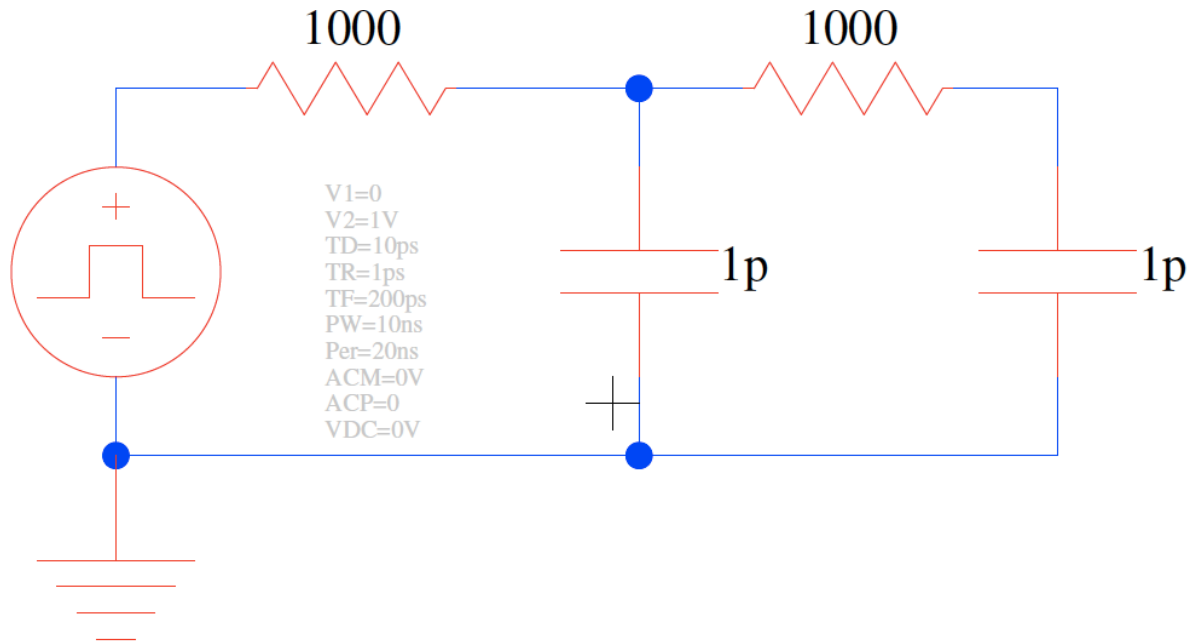- Look at series of R's on path
 - Must move $Q=V(\Sigma C)$ across each R



Elmore Delay: Distributed RC network

 - The delay from source s to node 5
 - $N =$ number of nodes in circuit




Elmore Delay: Distributed RC network

- The delay from source s to node 5
 - N = number of nodes in circuit

$$R_{5k} = \sum R_j \Rightarrow (R_j \in [\text{path}(s \rightarrow 5) \cap \text{path}(s \rightarrow k)])$$

$$\tau_{D5} = \sum_{k=1}^N C_k R_{5k}$$

 


Elmore Delay: Distributed RC network

- The delay from source s to node 5
 - N = number of nodes in circuit

$$R_{5k} = \sum R_j \Rightarrow (R_j \in [path(s \rightarrow 5) \cap path(s \rightarrow k)])$$

$$\tau_{D5} = \sum_{k=1}^N C_k R_{5k}$$

 


Elmore Delay: Distributed RC network

- The delay from source s to node 5
 - N = number of nodes in circuit

$$R_{5k} = \sum R_j \Rightarrow (R_j \in [\text{path}(s \rightarrow 5) \cap \text{path}(s \rightarrow k)])$$

$$\tau_{D5} = \sum_{k=1}^N C_k R_{5k}$$

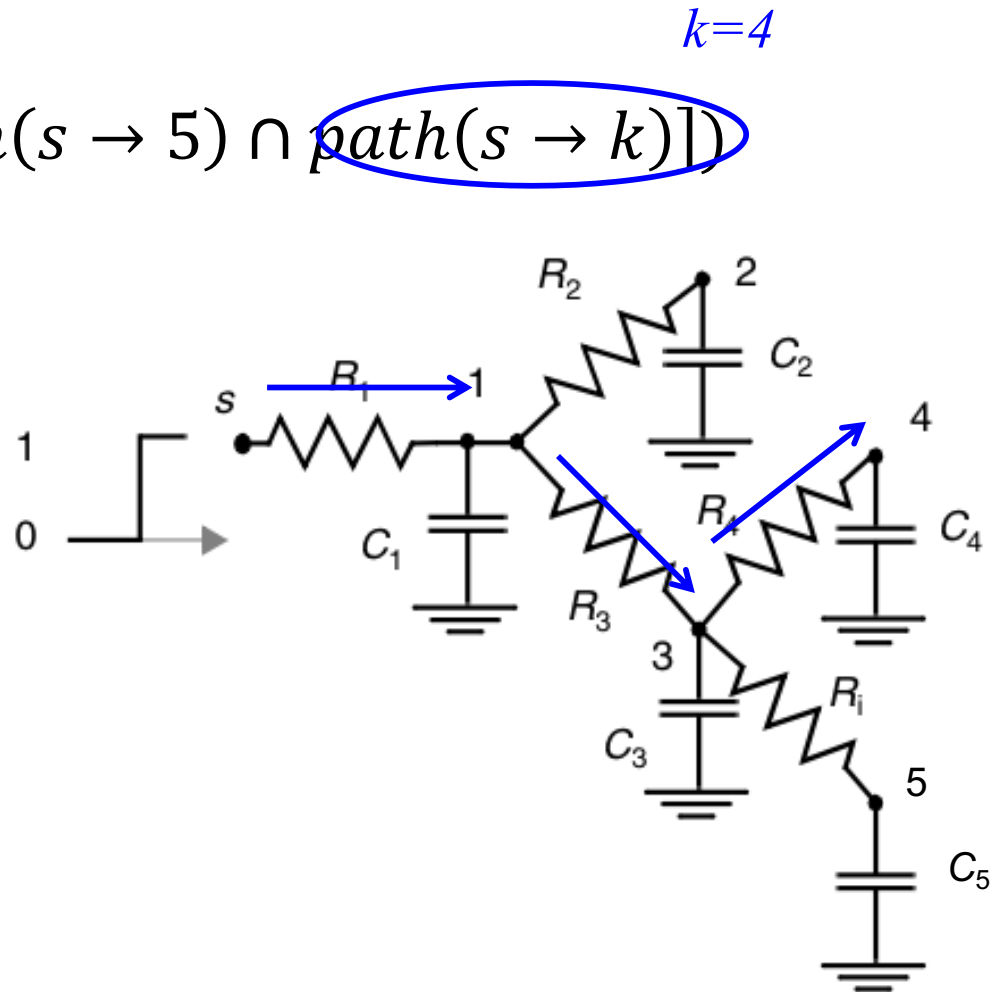


Elmore Delay: Distributed RC network

- The delay from source s to node 5
 - N = number of nodes in circuit

$$R_{5k} = \sum R_j \Rightarrow (R_j \in [\text{path}(s \rightarrow 5) \cap \text{path}(s \rightarrow k)])$$

$$\tau_{D5} = \sum_{k=1}^N C_k R_{5k}$$

 


Elmore Delay: Distributed RC network

□ The delay from source s to node 5

■ N = number of nodes in circuit

$$R_{5k} = \sum R_j \Rightarrow (R_j \in [\text{path}(s \rightarrow 5) \cap \text{path}(s \rightarrow k)])$$

$$\tau_{D5} = \sum_{k=1}^N C_k R_{5k}$$

 


Elmore Delay: Distributed RC network

- The delay from source s to node 5
 - N = number of nodes in circuit

$$R_{5k} = \sum R_j \Rightarrow (R_j \in [\text{path}(s \rightarrow 5) \cap \text{path}(s \rightarrow k)])$$
 
$$\tau_{D5} = \sum_{k=1}^N C_k R_{5k} = ?$$




Elmore Delay: Distributed RC network

- The delay from source s to node 5
 - N = number of nodes in circuit

$$R_{5k} = \sum R_j \Rightarrow (R_j \in [path(s \rightarrow 5) \cap path(s \rightarrow k)])$$
 
$$\tau_{D5} = \sum_{k=1}^N C_k R_{5k} = ?$$




Elmore Delay: Practice



- The delay from source s to node O
 - N = number of nodes in circuit

$$R_{Ok} = \sum R_j \Rightarrow (R_j \in [\text{path}(s \rightarrow O) \cap \text{path}(s \rightarrow k)])$$
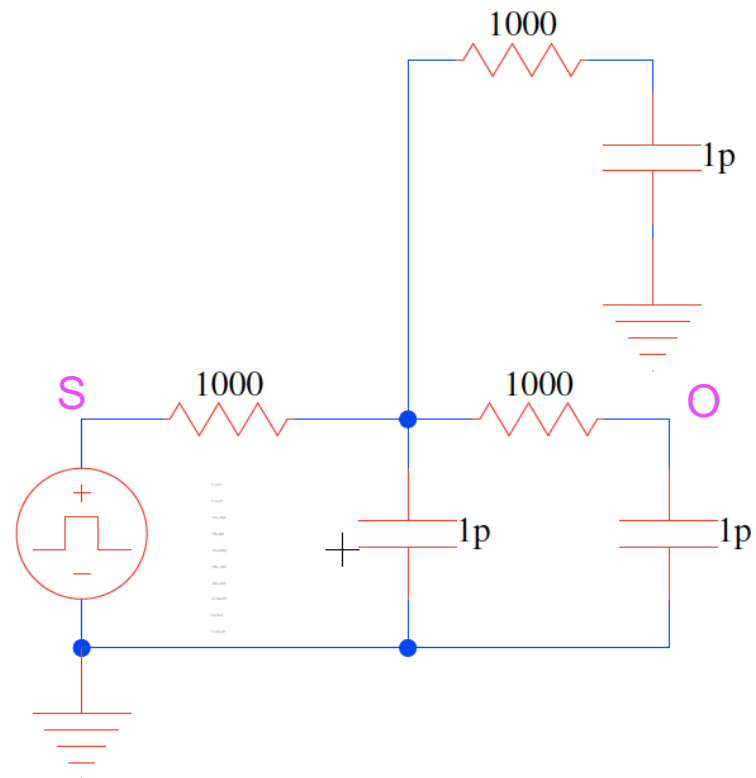
$$\tau_{DO} = \sum_{k=1}^N C_k R_{Ok} = ?$$





Previously: Equivalent RC

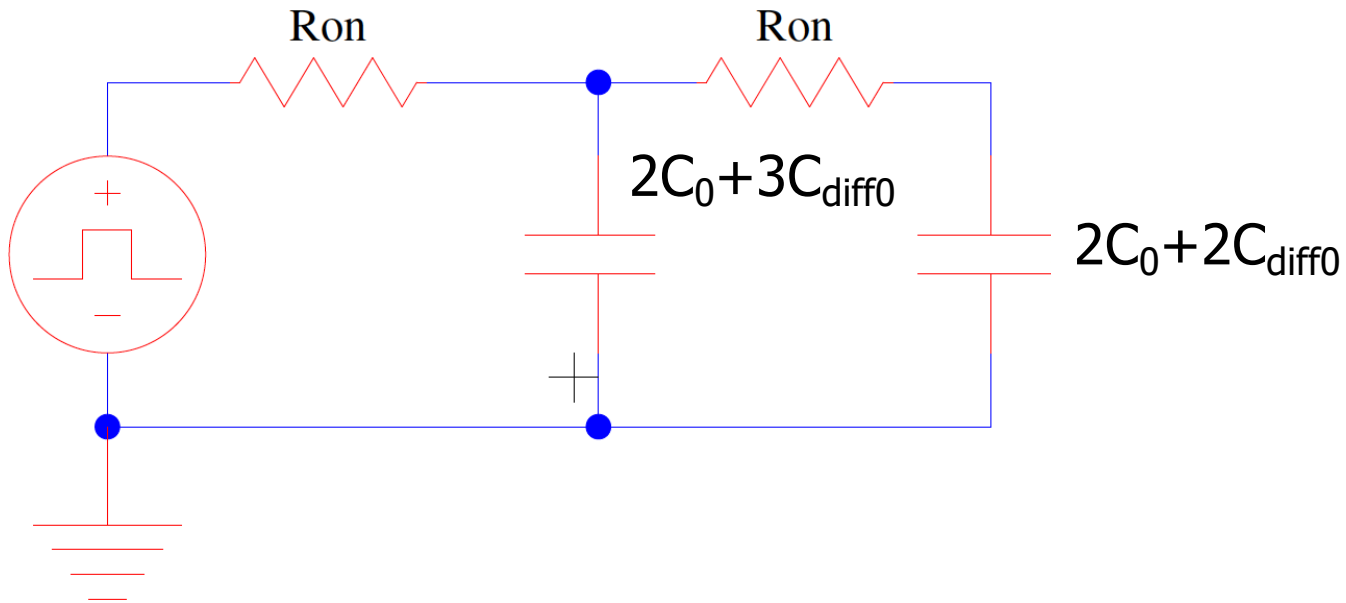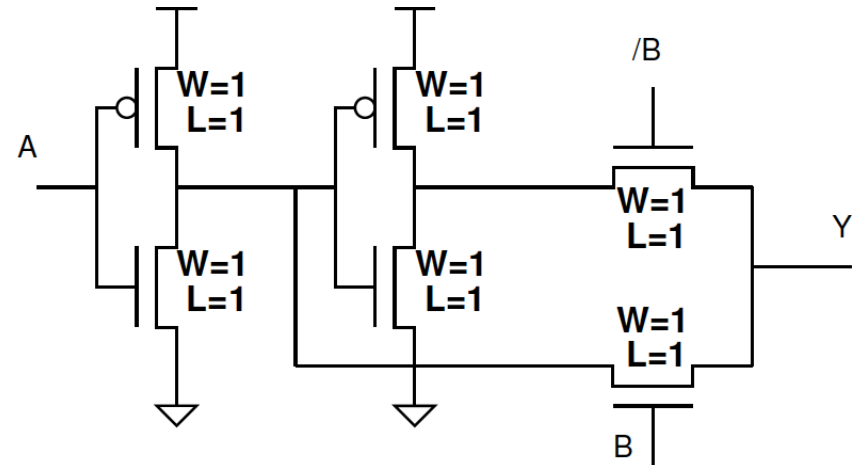



What is response?

  


Elmore Delay: Practice (preclass 1)

- The delay from source s to node i
 - N = number of nodes in circuit


$$R_{ik} = \sum R_j \Rightarrow (R_j \in [path(s \rightarrow i) \cap path(s \rightarrow k)])$$

$$\tau_{Di} = \sum_{k=1}^N C_k R_{ik}$$

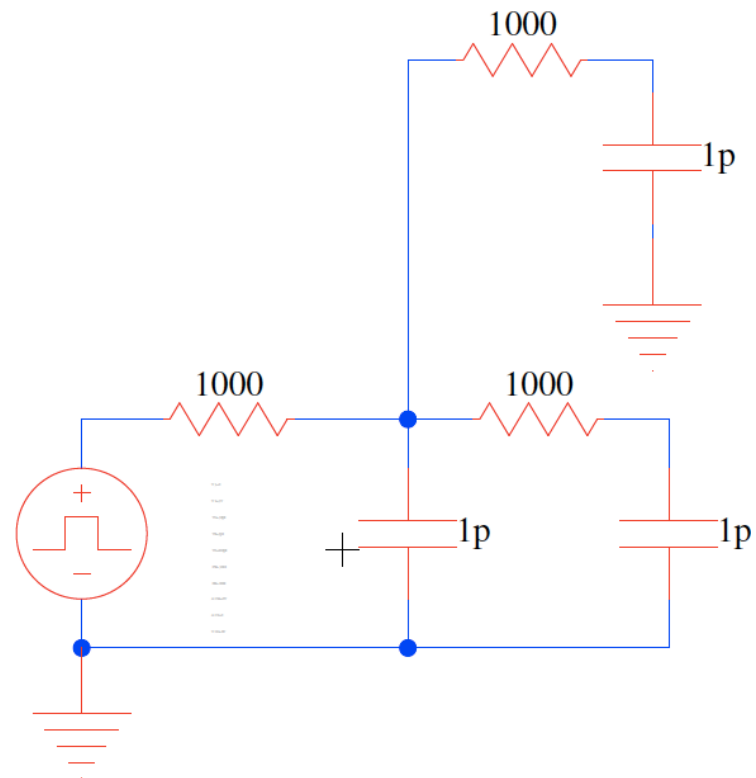



Apply (preclass 1)

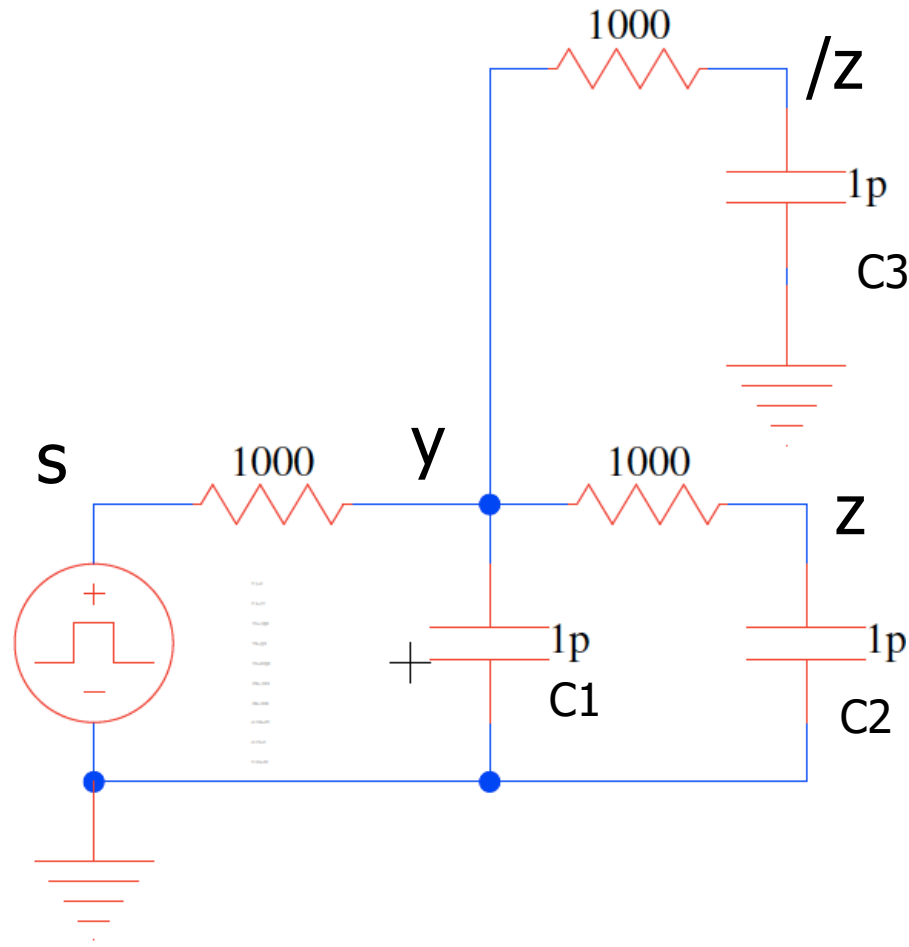- What is Elmore delay?
 - $S \rightarrow Z$






SPICE Response

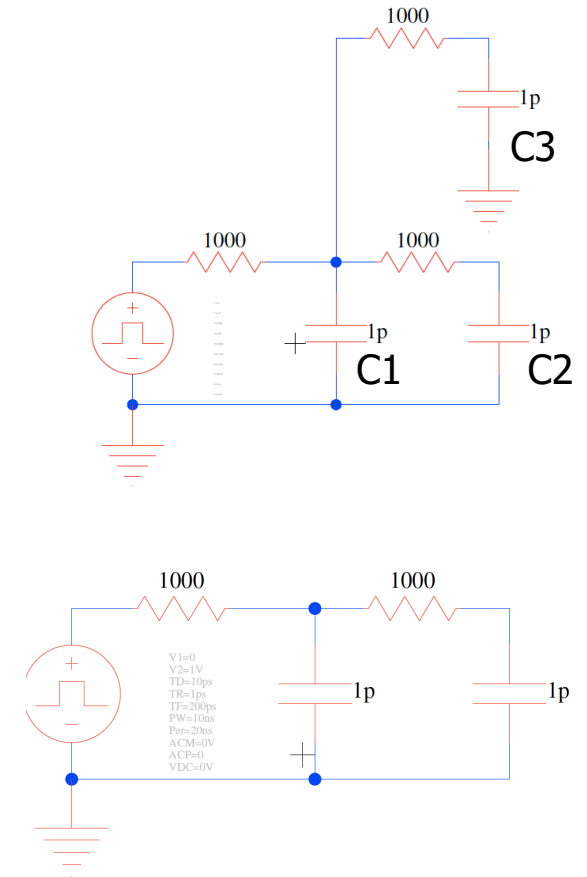 

Elmore Delay: Special Ladder Case

- For each resistor C_k in path
 - Compute $R_{k,k} =$ sum of all R s upstream of C_k
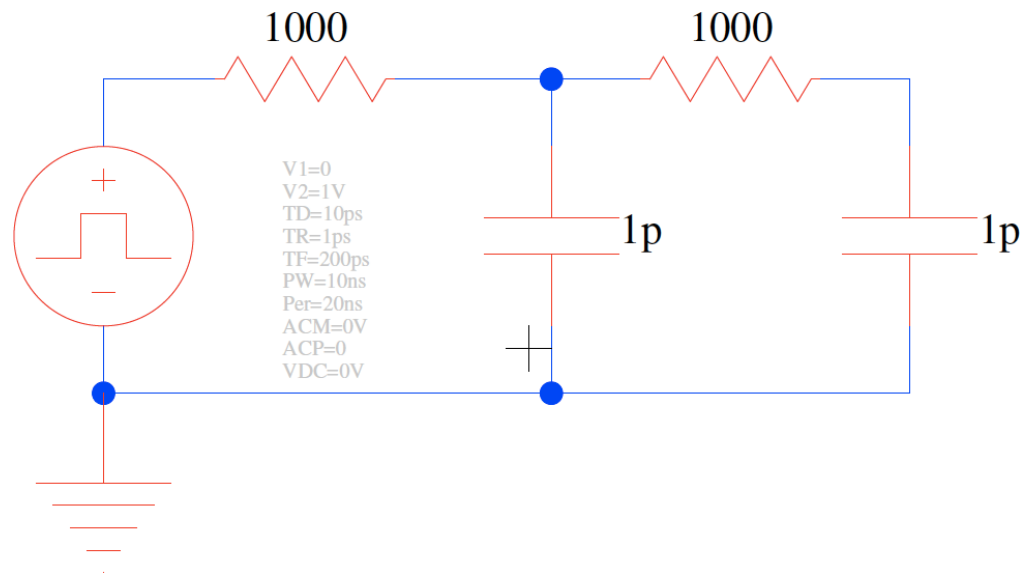
$$\tau_{DN} = \sum_{k=1}^N C_k \sum_{j=1}^k R_j = \sum_{k=1}^N C_k R_{kk}$$




Elmore Delay: Special Ladder Case

- For each resistor C_k in path
 - Compute $R_{k,k} =$ sum of all R s upstream of C_k

$$\tau_{DN} = \sum_{k=1}^N C_k \sum_{j=1}^k R_j = \sum_{k=1}^N C_k R_{kk}$$

$$C_1 * (R_1) + C_2 * (R_1 + R_2)$$

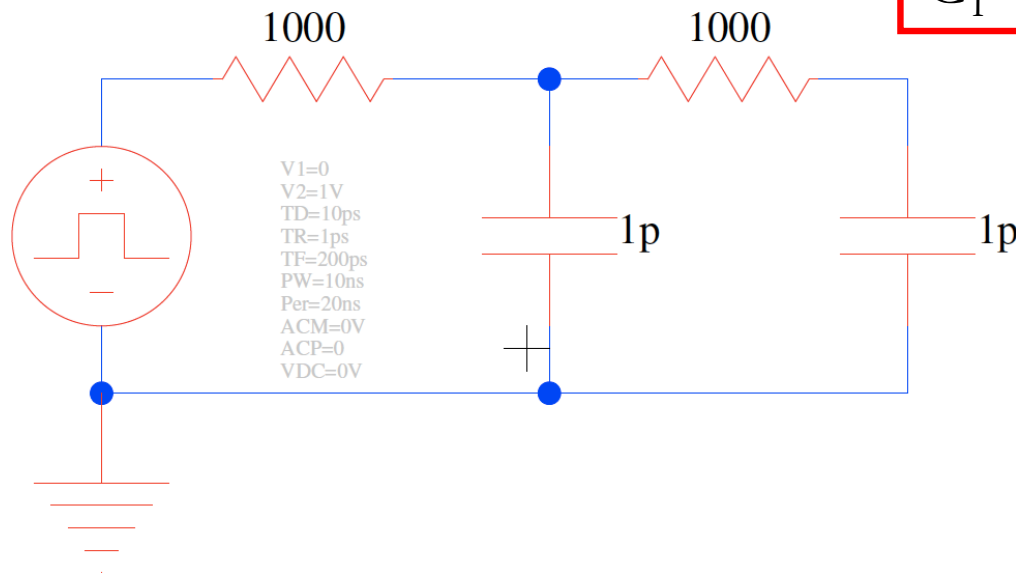


Elmore Delay: Special Ladder Case

- For each resistor C_k in path
 - Compute $R_{k,k} =$ sum of all R s upstream of C_k

$$\tau_{DN} = \sum_{k=1}^N C_k \sum_{j=1}^k R_j = \sum_{k=1}^N C_k R_{kk}$$

$$C_1 * (R_1) + C_2 * (R_1 + R_2)$$

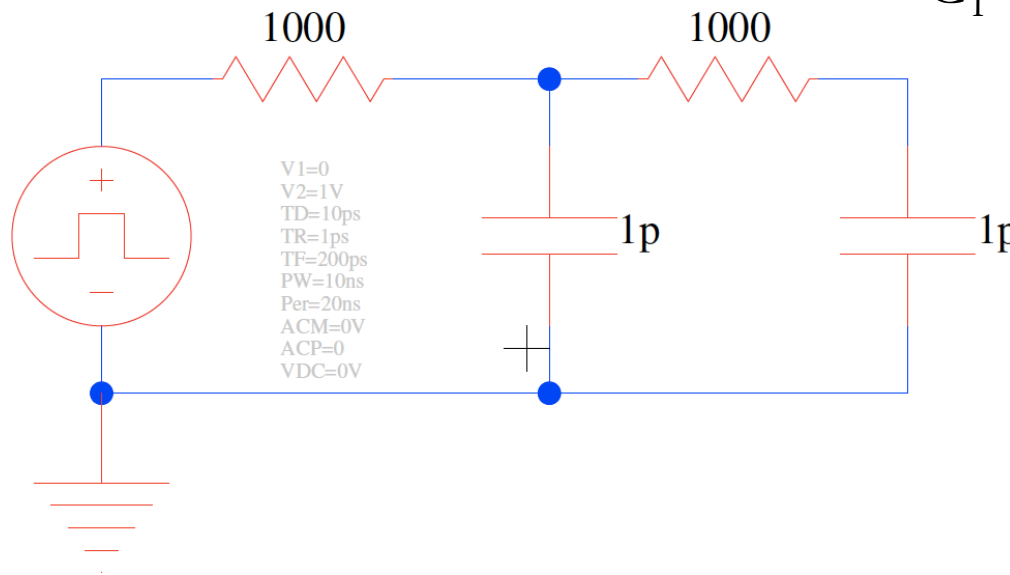

$$=3RC$$


$$=3ns$$

Compare KCL: Setup

□ Equations from KCL?

$$\text{@}V_1: \frac{V_S - V_1}{R_1} = \frac{V_1 - V_2}{R_2} + C_1 \frac{dV_1}{dt}$$
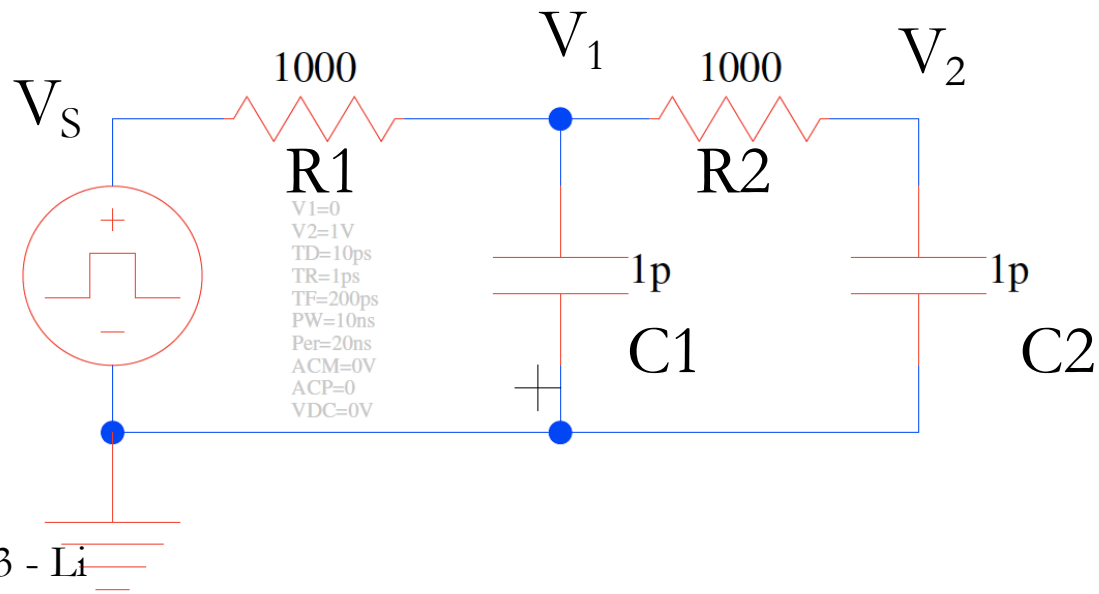
$$\text{@}V_2: \frac{V_1 - V_2}{R_2} = C_2 \frac{dV_2}{dt}$$



Compare KCL: Math

@ V_1 :

$$\frac{V_S - V_1}{R_1} = \frac{V_1 - V_2}{R_2} + C_1 \frac{dV_1}{dt}$$

$$\frac{V_S}{R_1} = \frac{V_1}{R_1} + \frac{V_1}{R_2} - \frac{V_2}{R_2} + C_1 \frac{dV_1}{dt}$$

$$V_S = V_1 \left(1 + \frac{R_1}{R_2} \right) - \frac{R_1 V_2}{R_2} + R_1 C_1 \frac{dV_1}{dt}$$

@ V_2 :

$$\frac{V_1 - V_2}{R_2} = C_2 \frac{dV_2}{dt}$$

$$\frac{V_1}{R_2} = \frac{V_2}{R_2} + C_2 \frac{dV_2}{dt}$$

$$V_1 = V_2 + R_2 C_2 \frac{dV_2}{dt}$$

$$\frac{dV_1}{dt} = \frac{dV_2}{dt} + R_2 C_2 \frac{d^2 V_2}{dt^2}$$



Compare KCL: Math

$$V_S = V_1 \left(1 + \frac{R_1}{R_2} \right) - \frac{R_1}{R_2} V_2 + R_1 C_1 \frac{dV_1}{dt}$$

$$V_S = \left(V_2 + R_2 C_2 \frac{dV_2}{dt} \right) \left(1 + \frac{R_1}{R_2} \right) - \frac{R_1}{R_2} V_2 + R_1 C_1 \left(\frac{dV_2}{dt} + R_2 C_2 \frac{d^2 V_2}{dt^2} \right)$$

$$V_S = V_2 + \left(R_2 C_2 \left(1 + \frac{R_1}{R_2} \right) + R_1 C_1 \right) \frac{dV_2}{dt} + R_1 C_1 R_2 C_2 \frac{d^2 V_2}{dt^2}$$

$$V_S = V_2 + (R_2 C_2 + R_1 C_2 + R_1 C_1) \frac{dV_2}{dt} + R_1 C_1 R_2 C_2 \frac{d^2 V_2}{dt^2}$$



Compare KCL: Math

$$R_1 = R_2 = R$$

$$C_1 = C_2 = C$$

$$V_s = V_2 + (R_2 C_2 + R_1 C_2 + R_1 C_1) \frac{dV_2}{dt} + R_1 C_1 R_2 C_2 \frac{d^2 V_2}{dt^2}$$

$$V_s = V_2 + 3RC \frac{dV_2}{dt} + R^2 C^2 \frac{d^2 V_2}{dt^2}$$



Compare KCL: Math

$$R_1 = R_2 = R$$

$$C_1 = C_2 = C$$

$$V_S = V_2 + (R_2 C_2 + R_1 C_2 + R_1 C_1) \frac{dV_2}{dt} + R_1 C_1 R_2 C_2 \frac{d^2 V_2}{dt^2}$$

$$V_S = V_2 + 3RC \frac{dV_2}{dt} + R^2 C^2 \frac{d^2 V_2}{dt^2}$$

$$V_2 = A(1 + e^{-\alpha t}) \rightarrow$$

$$V_S = A(1 + e^{-\alpha t}) - 3RC \cdot \alpha A e^{-\alpha t} + R^2 C^2 \cdot \alpha^2 A e^{-\alpha t}$$



Compare KCL: Math

$$V_2 = A(1 + e^{-\alpha t}) \rightarrow$$

$$V_S = A(1 + e^{-\alpha t}) - 3RC \cdot \alpha A e^{-\alpha t} + R^2 C^2 \cdot \alpha^2 A e^{-\alpha t}$$

$$t = \infty \rightarrow V_2 = V_S = A$$



Compare KCL: Math

$$V_2 = A(1 + e^{-\alpha t}) \rightarrow$$

$$V_S = A(1 + e^{-\alpha t}) - 3RC \cdot \alpha A e^{-\alpha t} + R^2 C^2 \cdot \alpha^2 A e^{-\alpha t}$$

$$t = \infty \rightarrow V_2 = V_S = A$$

$$V_S = V_S(1 + e^{-\alpha t}) - 3RC \cdot \alpha V_S e^{-\alpha t} + R^2 C^2 \cdot \alpha^2 V_S e^{-\alpha t}$$

$$0 = e^{-\alpha t} - 3RC \cdot \alpha e^{-\alpha t} + R^2 C^2 \cdot \alpha^2 e^{-\alpha t}$$

$$0 = e^{-\alpha t} (1 - 3RC\alpha + R^2 C^2 \cdot \alpha^2)$$

$$0 = 1 - 3RC\alpha + R^2 C^2 \cdot \alpha^2$$


Compare KCL: Math

$$V_2 = V_s(1 + e^{-\alpha t})$$

$$0 = 1 - 3RC\alpha + R^2C^2 \cdot \alpha^2$$

$$\alpha = \frac{3RC \pm \sqrt{9(RC)^2 - 4(RC)^2}}{2(RC)^2} = \frac{3RC \pm \sqrt{5}RC}{2(RC)^2} = \frac{3 \pm \sqrt{5}}{2RC}$$
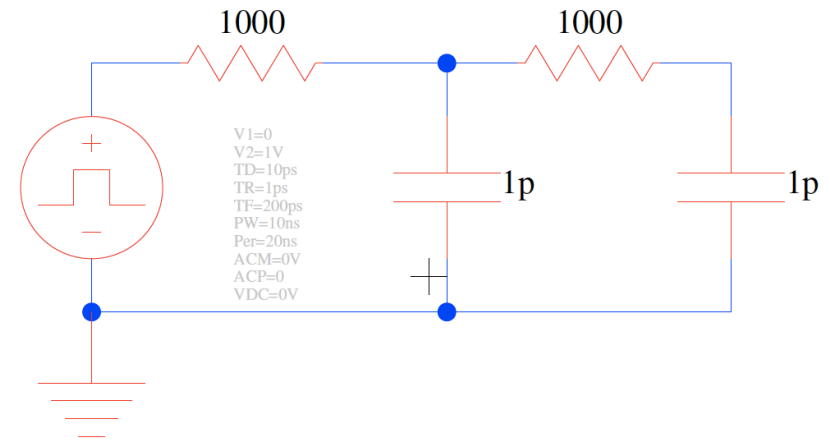
$$\rightarrow \tau = \frac{2}{3 \pm \sqrt{5}} RC \approx 2.6RC$$




Compare KCL: Math

$$V_2 = V_s(1 + e^{-\alpha t})$$

$$0 = 1 - 3RC\alpha + R^2C^2 \cdot \alpha^2$$

$$\alpha = \frac{3RC \pm \sqrt{9(RC)^2 - 4(RC)^2}}{2(RC)^2} = \frac{3RC \pm \sqrt{5}RC}{2(RC)^2} = \frac{3 \pm \sqrt{5}}{2RC}$$
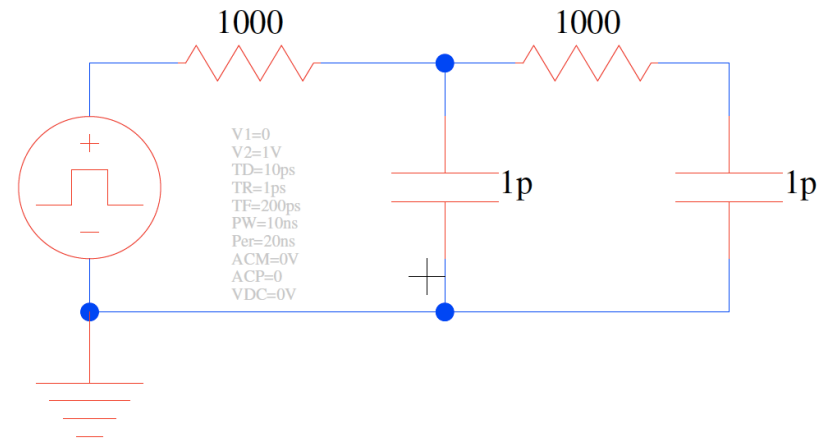
$$\rightarrow \tau = \frac{2}{3 \pm \sqrt{5}} RC \approx 2.6RC$$



$$= 3RC$$
$$= 3\text{ns}$$

Elmore Delay: Distributed RC network

□ The delay from source to node i

■ N = number of nodes in circuit

$$R_{ik} = \sum R_j \Rightarrow (R_j \in [\text{path}(s \rightarrow i) \cap \text{path}(s \rightarrow k)])$$

$$\tau_{Di} = \sum_{k=1}^N C_k R_{ik}$$


□ Special ladder case

$$\tau_{DN} = \sum_{k=1}^N C_k \sum_{j=1}^k R_j = \sum_{k=1}^N C_k R_{kk}$$

Wire Delay



Wire Resistance

 


$$R = \frac{\rho L}{A}$$

$$R = \frac{10^{-7} \Omega \cdot m \cdot 100 \mu m}{1 \mu m \cdot 1 \mu m} = 10 \Omega$$




Wire Capacitance

$$C = \epsilon_d \frac{A}{d}$$

 

Wire as Distributed RC Ladder

 
- Measure wire length in units
 - Say λ
 - Each λ unit has C_{unit} , R_{unit}
 - Unit capacitance and resistance of wire of length λ





Wire Delay

- Delay of Wire N units long:

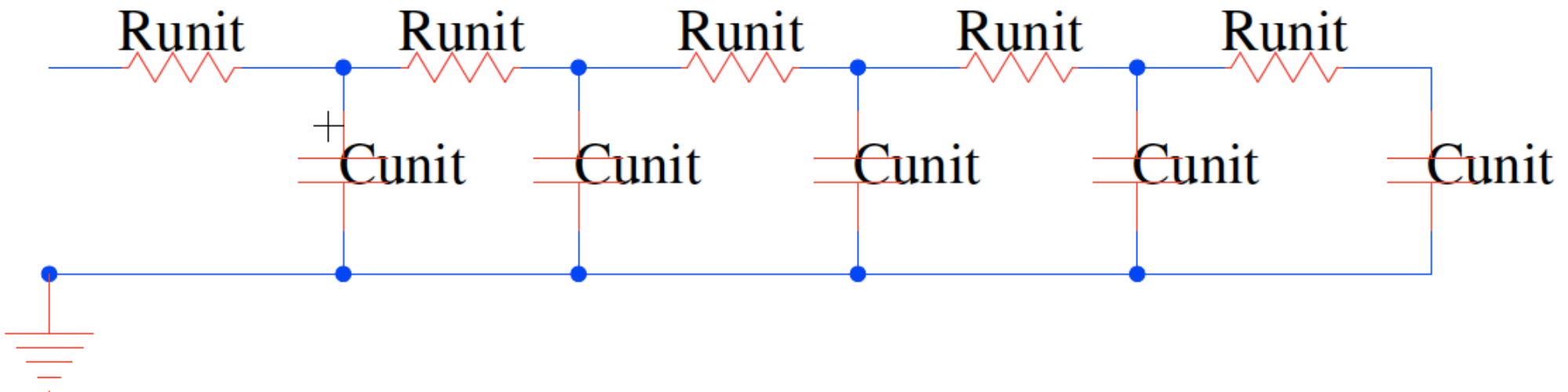




Wire Delay

□ Delay of Wire N units long:

$$R_{\text{unit}} C_{\text{unit}}$$

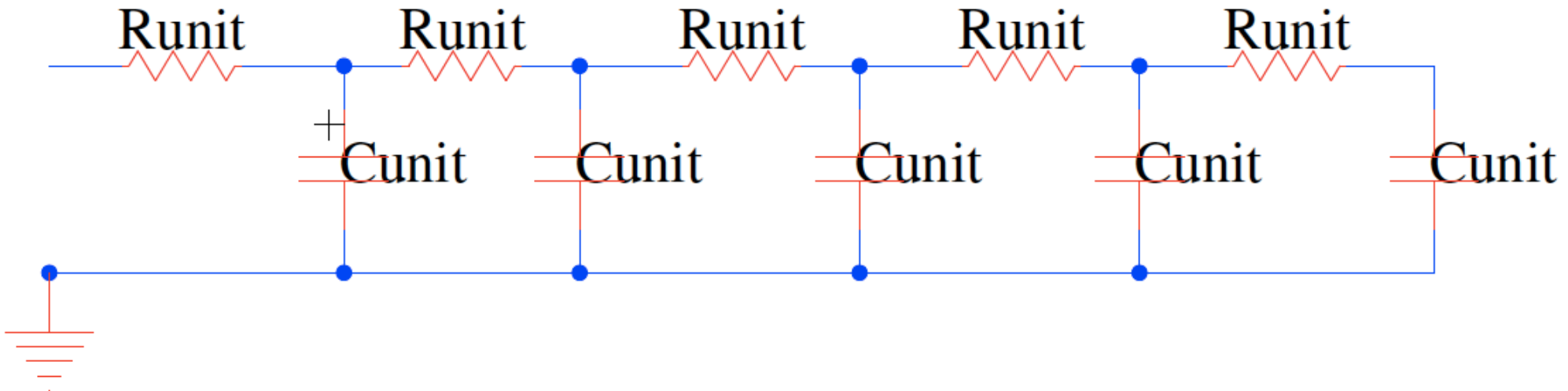




Wire Delay

□ Delay of Wire N units long:
 
$$R_{\text{unit}}C_{\text{unit}} + 2R_{\text{unit}}C_{\text{unit}}$$






Wire Delay

□ Delay of Wire N units long:
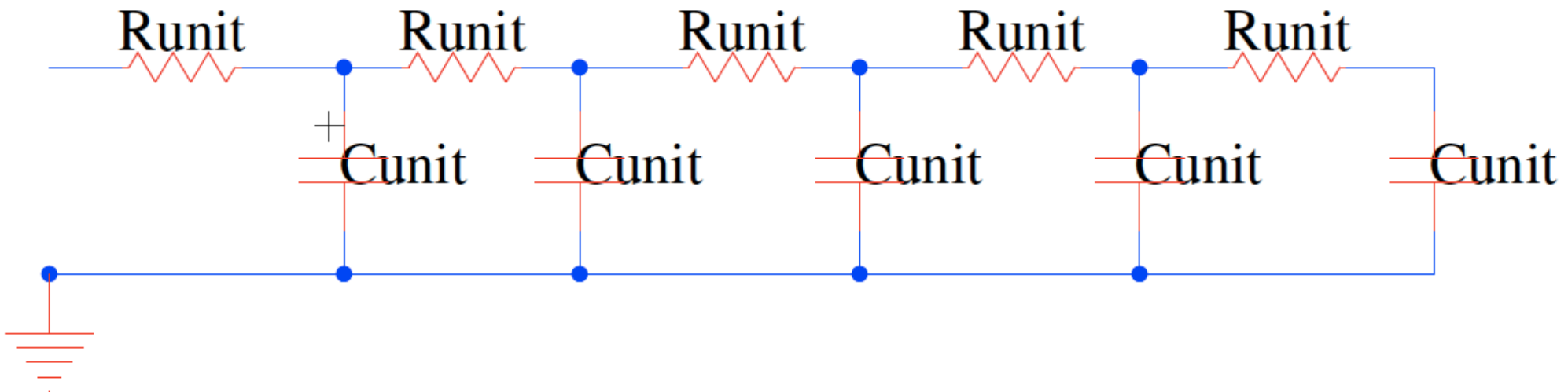
$$\begin{aligned} & R_{\text{unit}} C_{\text{unit}} \\ & + 2R_{\text{unit}} C_{\text{unit}} \\ & + 3R_{\text{unit}} * C_{\text{unit}} + \dots + NR_{\text{unit}} * C_{\text{unit}} \\ & = (R_{\text{unit}} * C_{\text{unit}}) * (N + (N-1) + (N-2) + \dots + 1) \end{aligned}$$





Sum of integers (preclass 2)

- What's the sum of the integer 1 to N?

$$\sum_{k=0}^N k =$$



Sum of integers

- What's the sum of the integer 1 to N?

$$\sum_{k=0}^N k = \frac{N(N+1)}{2} \approx \frac{N^2}{2}$$

Wire Delay (preclass 3)

□ Delay of Wire N units long:


$$R_{\text{unit}} * (N * C_{\text{unit}})$$

$$+ R_{\text{unit}} * ((N-1) * C_{\text{unit}})$$

$$+ R_{\text{unit}} * (N-2) * C_{\text{unit}} + \dots + R_{\text{unit}} * C_{\text{unit}}$$

$$= (R_{\text{unit}} * C_{\text{unit}}) * (N + N-1 + N-2 + \dots + 1)$$
 
$$\sim R_{\text{unit}} C_{\text{unit}} * N^2 / 2$$




Lumped RC Wire? (preclass 4)

- What would the delay be if we treated the wire as lumped R and C?

$$R_{\text{wire}} = N \times R_{\text{unit}}$$
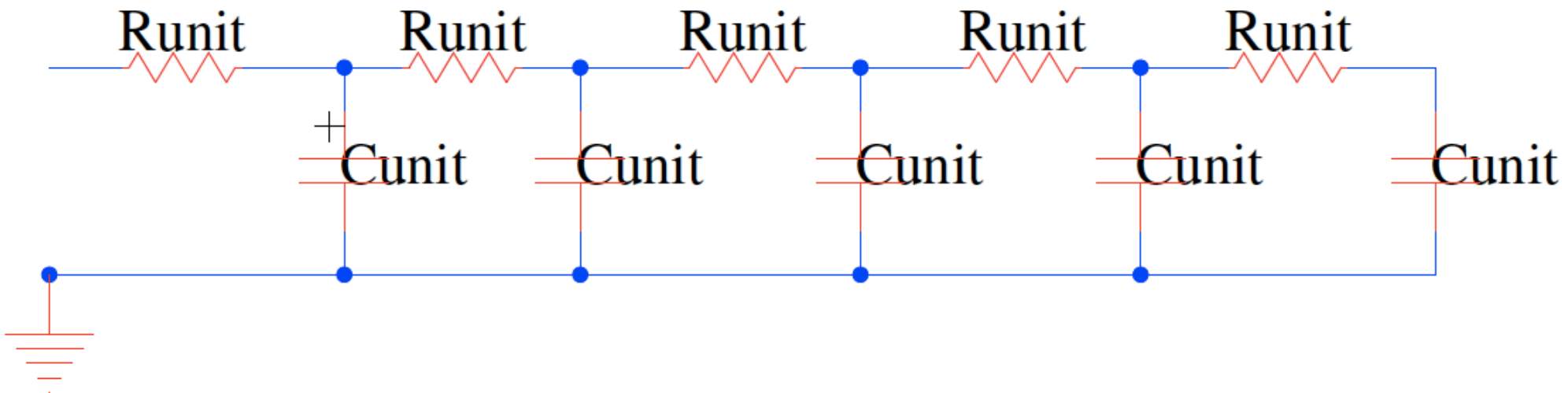
$$C_{\text{wire}} = N \times C_{\text{unit}}$$





Wire Delay

- ❑ $R_{\text{wire}} = N * R_{\text{unit}}$
- ❑ $C_{\text{wire}} = N * C_{\text{unit}}$
- ❑ Lumped RC wire delay = $R_{\text{unit}} * C_{\text{unit}} * N^2$
- ❑ Distributed RC Wire delay = $R_{\text{unit}} * C_{\text{unit}} * N^2 / 2$

- ❑ Distributed has half the delay of lumped RC product
- ❑ Delay is quadratic in length of wire in both cases



Apply to Gates

Pass Transistor and CMOS




Pass Transistor XOR

□ Delay when $A=B=1$?

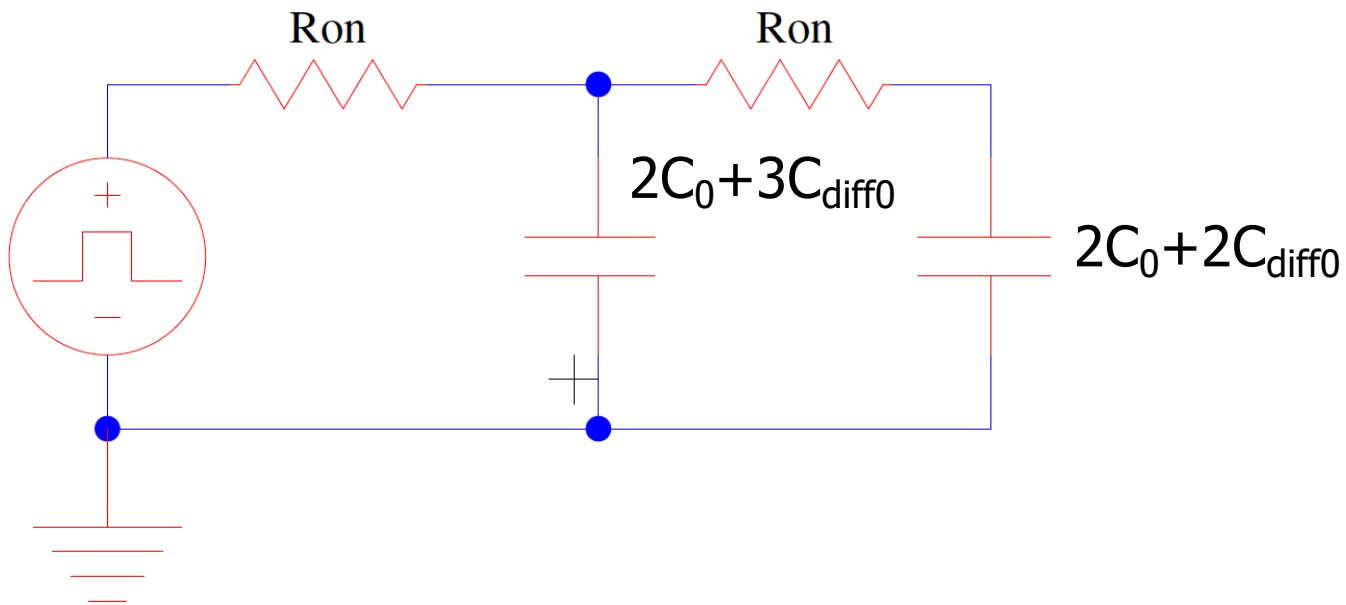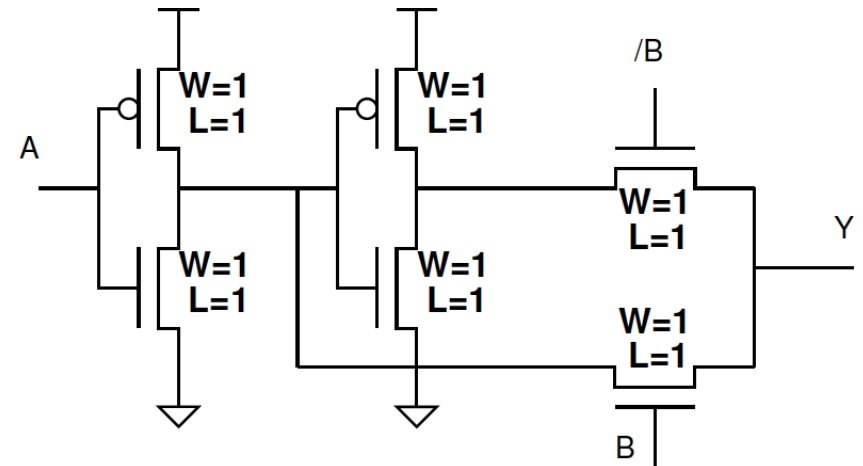

Pass Transistor XOR (preclass 5)

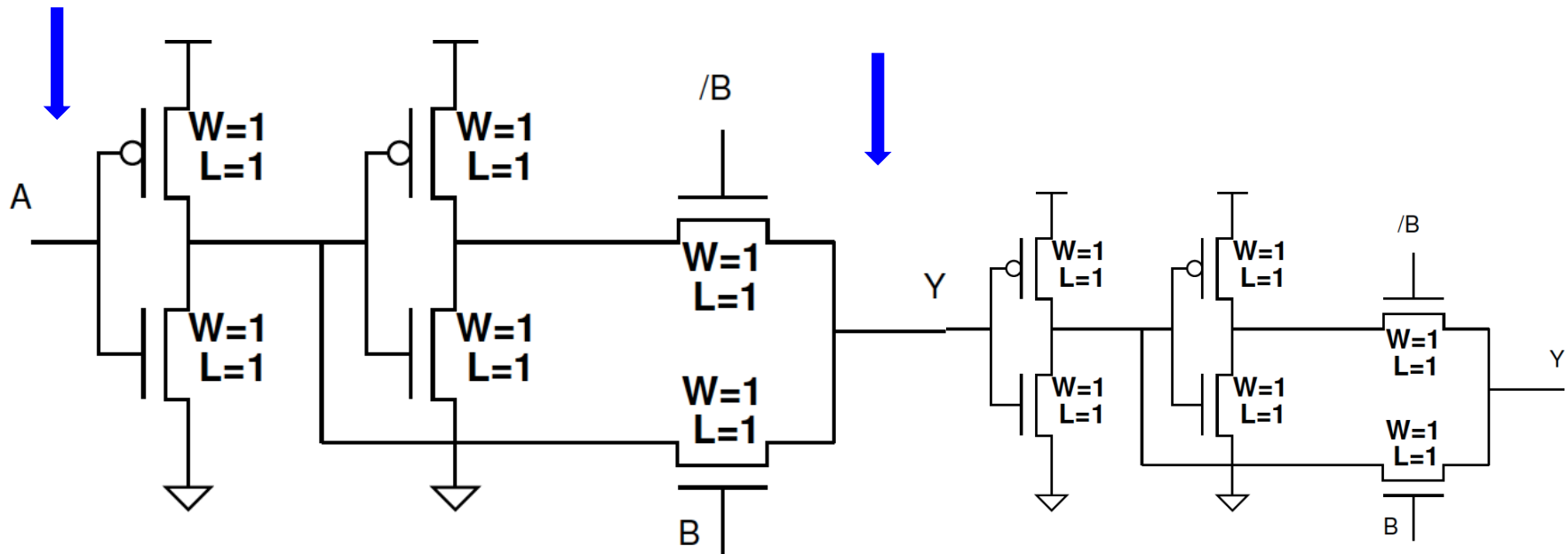
- Delay when $A=1, B=0$?
 - Start with equivalent RC circuit



Unbuffered (preclass 6)

□ Circuit → Delay?

■ 2 stages

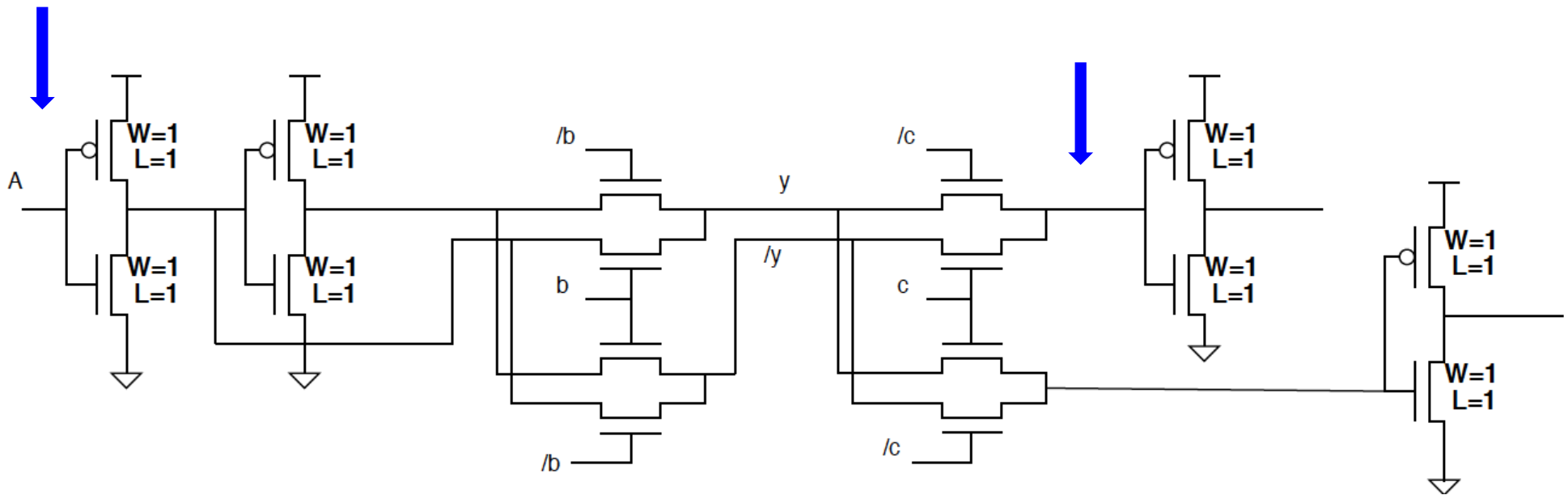




Unbuffered (preclass 7)

□ Circuit → Delay?


■ 3 stages

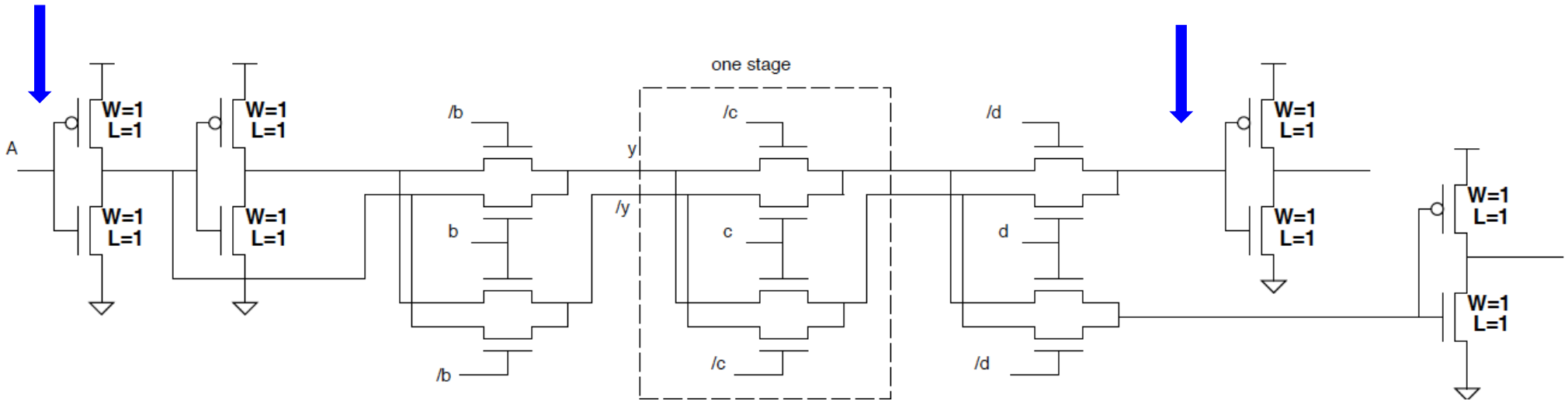




Unbuffered (preclass 8)

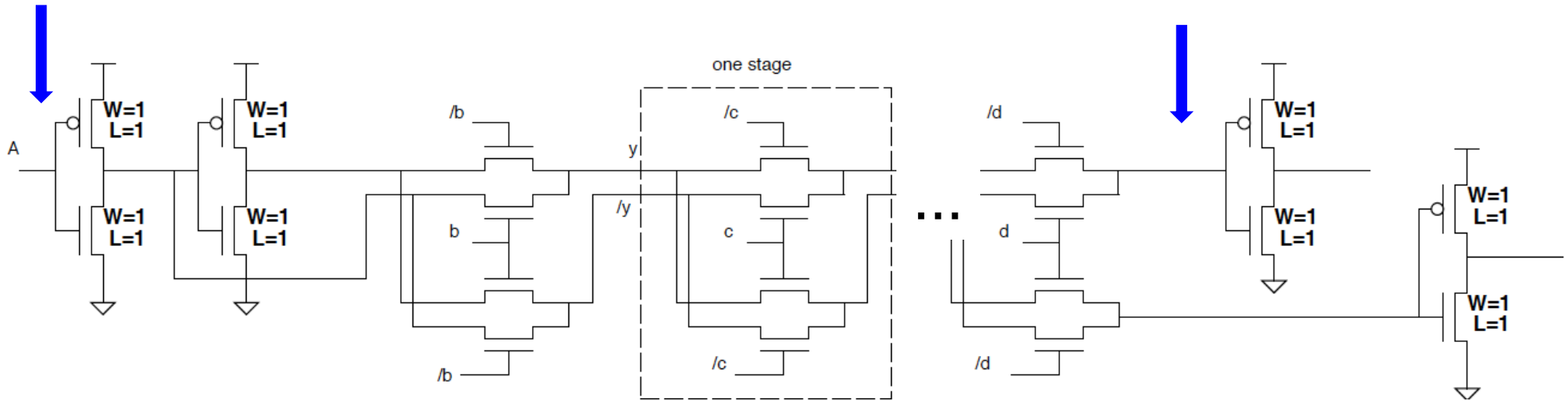- Delay as a function of number of stages, k ?





CMOS XOR (preclass 9)

- Delay with $C_{diff} > 0$?


 


Review: Two-Input NOR Gate (NOR2)

 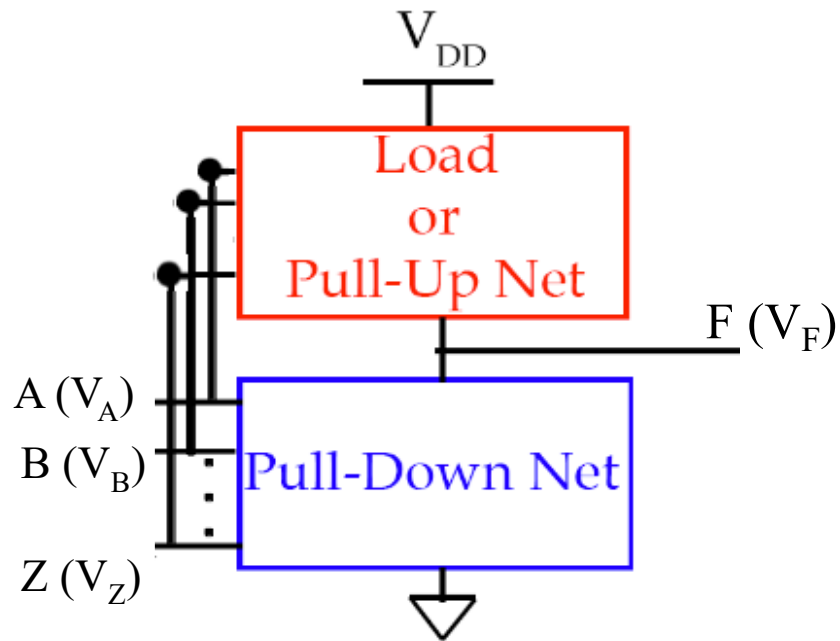

- ❑ Worst case delay of NOR2?
 - Minimum size, Loaded with itself

NOR2 Transfer Curve

  

3 VTC Cases

$$V_1 = 0 \text{ V}; V_2 = 0 \rightarrow V_{DD}$$

$$V_1 = 0 \rightarrow V_{DD}; V_2 = 0$$


$$V_1 \text{ and } V_2 = 0 \rightarrow V_{DD} \text{ simultaneously}$$

Switching Threshold Voltage:

$$V_1 = V_2 = V_{out} = V_t$$


NOR2 Delay (preclass 10)

- Worst case delay for Pull-up?

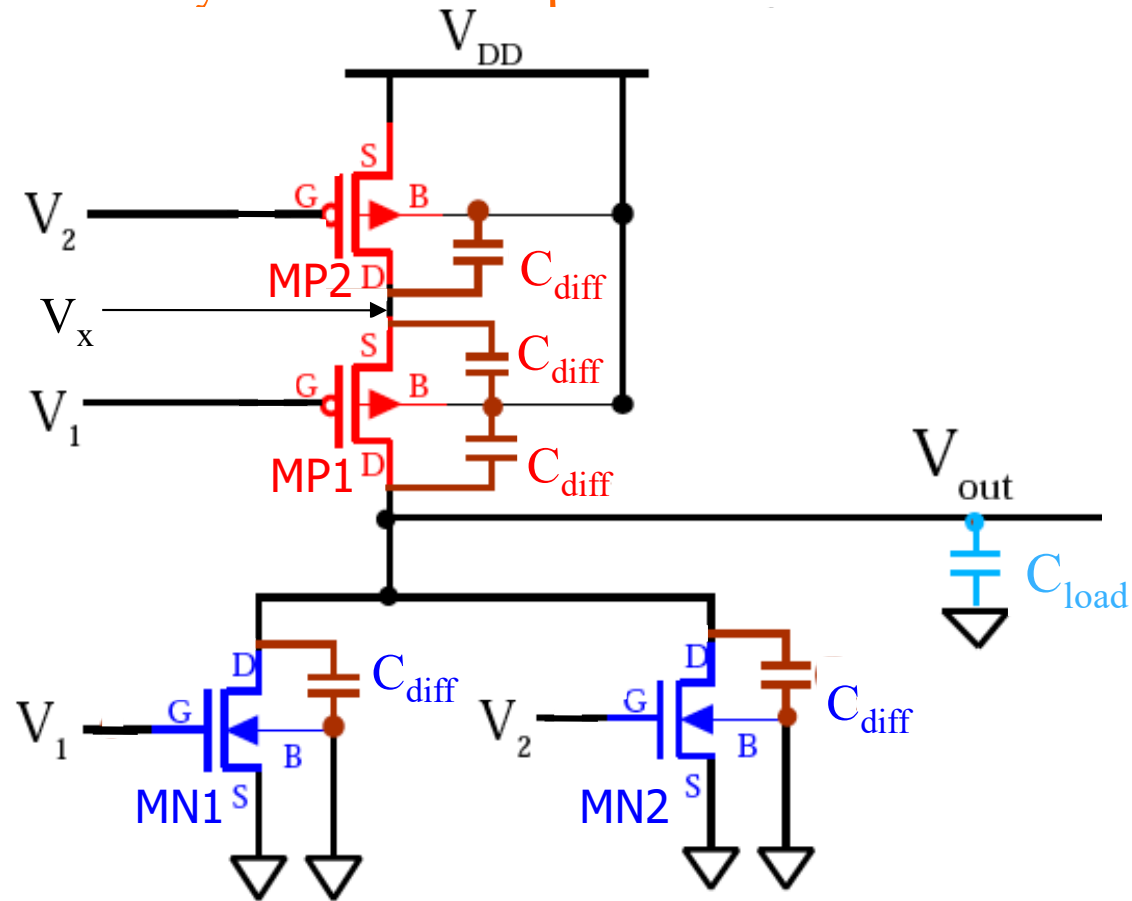

NOR2 Delay

- Worst case delay for Pull-up?

 

Worst Case for Pull-up $\rightarrow V_1 = 0, V_2 = V_{DD} \rightarrow 0$ @ $t=0$ & $V_x \approx V_{out} = 0 \rightarrow V_{DD}$


NOR2 Delay

□ Worst case delay for Pull-up?

$$C_{\text{load-NR2}} \approx 2C_{\text{diff}} + 3C_{\text{diff}} + C_{\text{load}}$$

$$R_{\text{EQV}} = R_{p2} + R_{p1}$$


Lumped Model

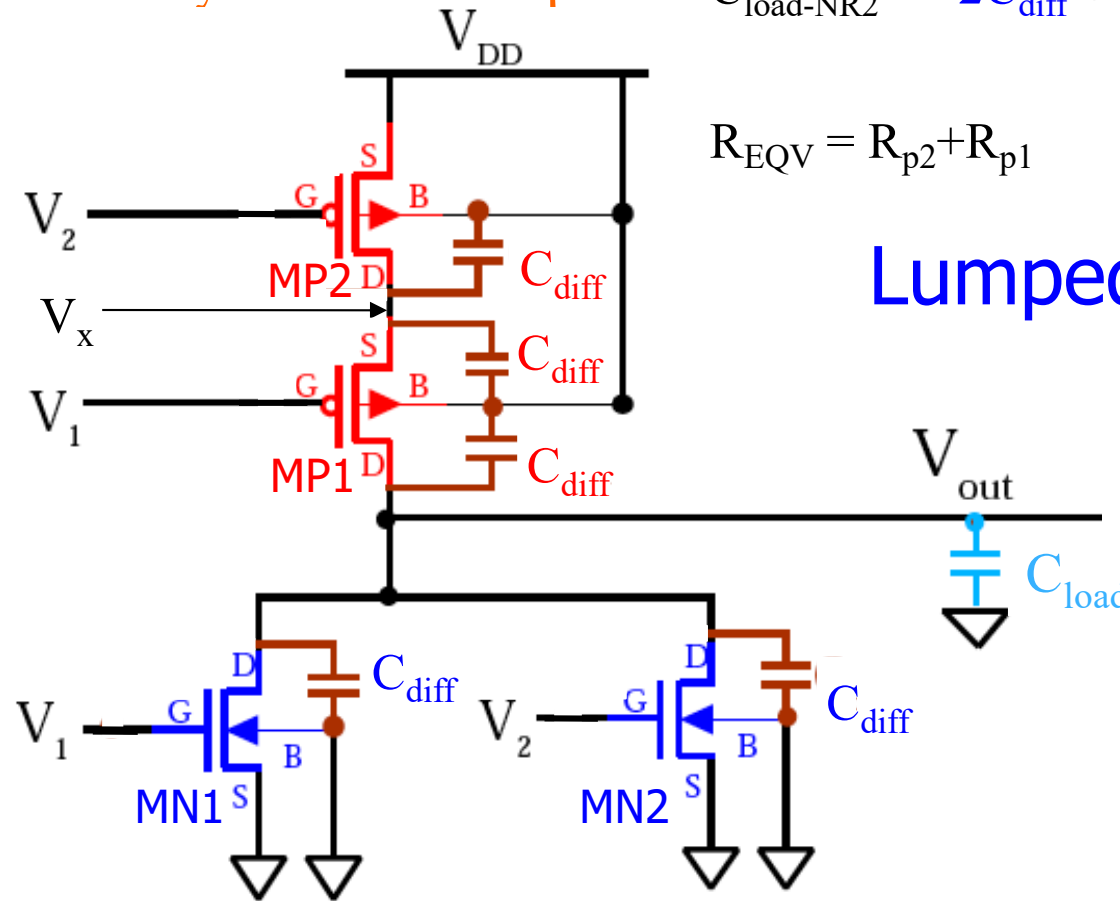

Worst Case for Pull-up $\rightarrow V_1 = 0, V_2 = V_{DD} \rightarrow 0$ @ $t=0$ & $V_x \approx V_{out} = 0 \rightarrow V_{DD}$

NOR2 Delay

□ Worst case delay for Pull-up?

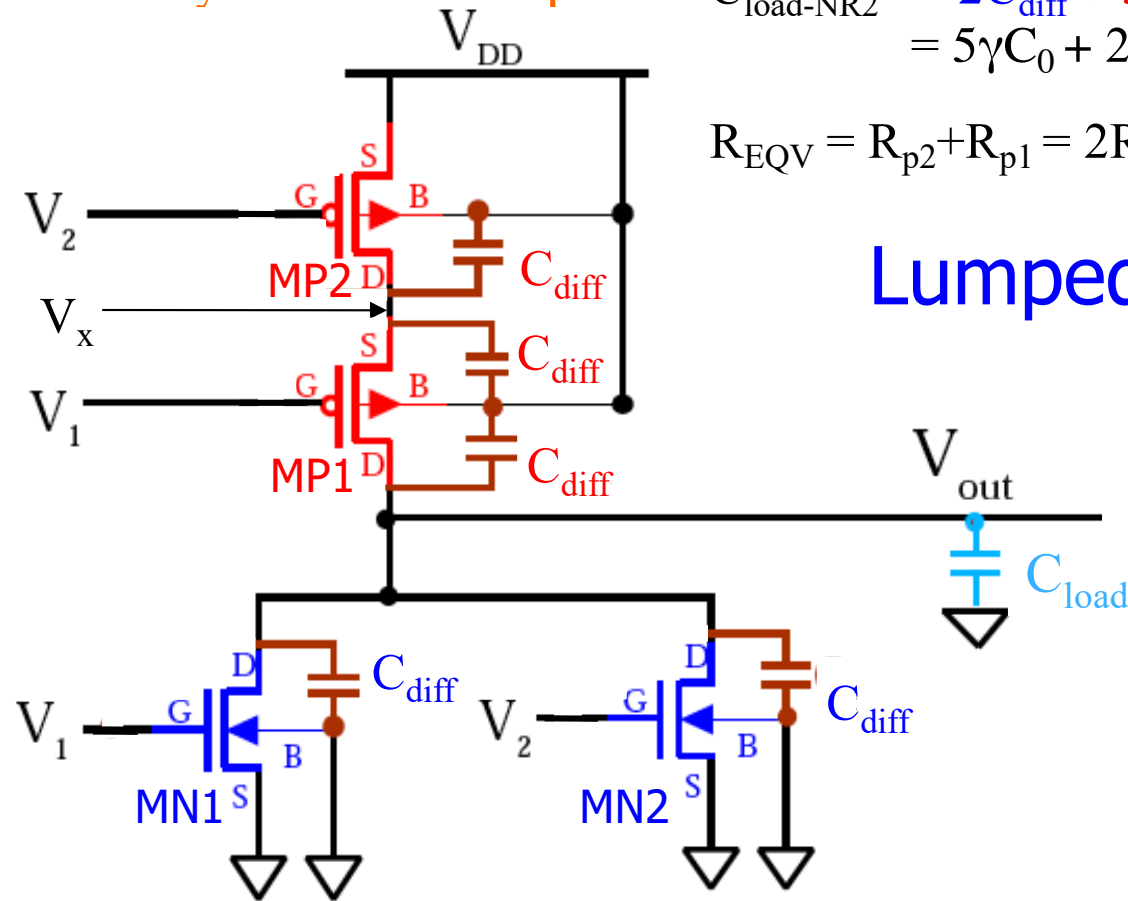

$$C_{\text{load-NR2}} \approx 2C_{\text{diff}} + 3C_{\text{diff}} + C_{\text{load}} = 5\gamma C_0 + 2C_0$$

$$R_{\text{EQV}} = R_{p2} + R_{p1} = 2R_0$$


Lumped Model

Worst Case for Pull-up $\rightarrow V_1 = 0, V_2 = V_{DD} \rightarrow 0$ @ $t=0$ & $V_x \approx V_{\text{out}} = 0 \rightarrow V_{DD}$

$$\text{delay} = (5\gamma C_0 + 2C_0)(2R_0) = (10\gamma + 4)\tau$$

NOR2 Delay

□ Worst case delay?

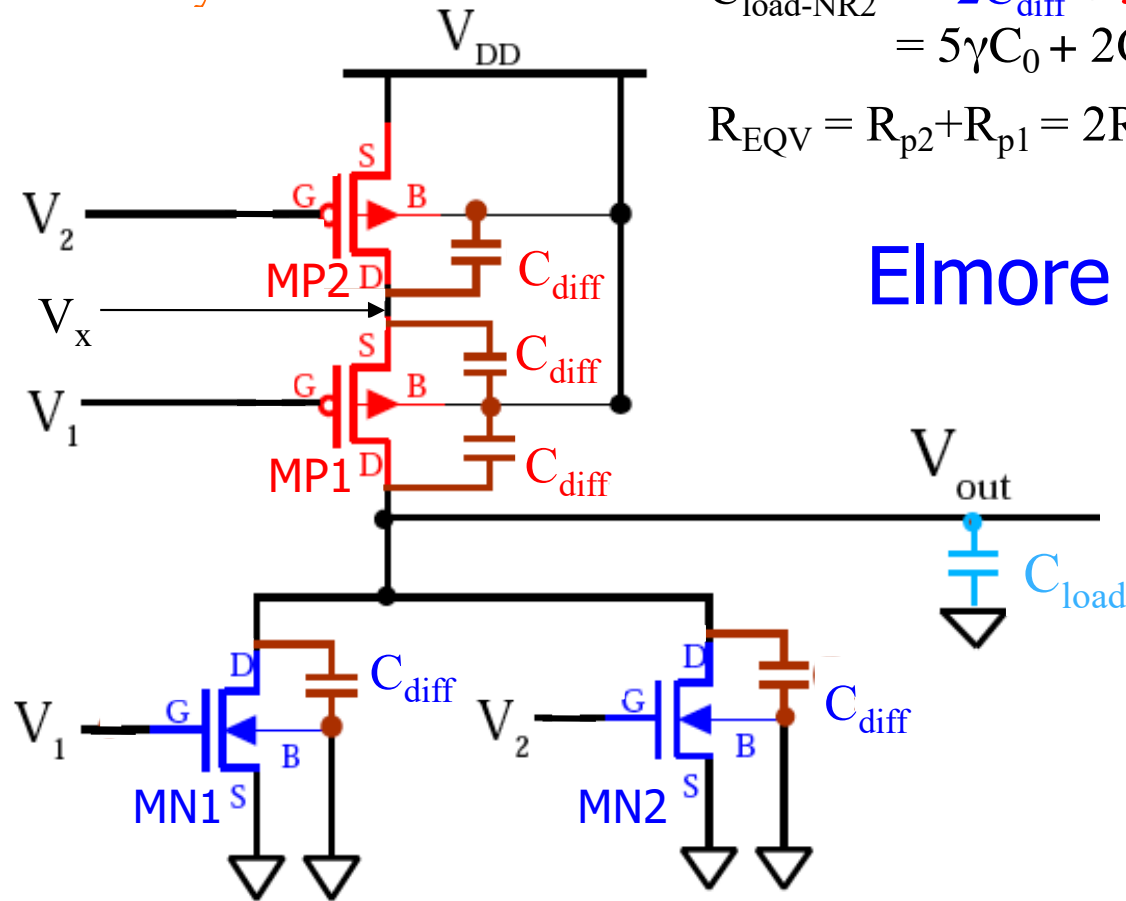

$$C_{\text{load-NR2}} \approx 2C_{\text{diff}} + 3C_{\text{diff}} + C_{\text{load}} = 5\gamma C_0 + 2C_0$$


$$R_{\text{EQV}} = R_{p2} + R_{p1} = 2R_0$$

Elmore Model?

Worst Case for Pull-up $\rightarrow V_1 = 0, V_2 = V_{DD} \rightarrow 0$ @t=0 & $V_x \approx V_{\text{out}} = 0 \rightarrow V_{DD}$

NOR2 Delay

Worst case delay?

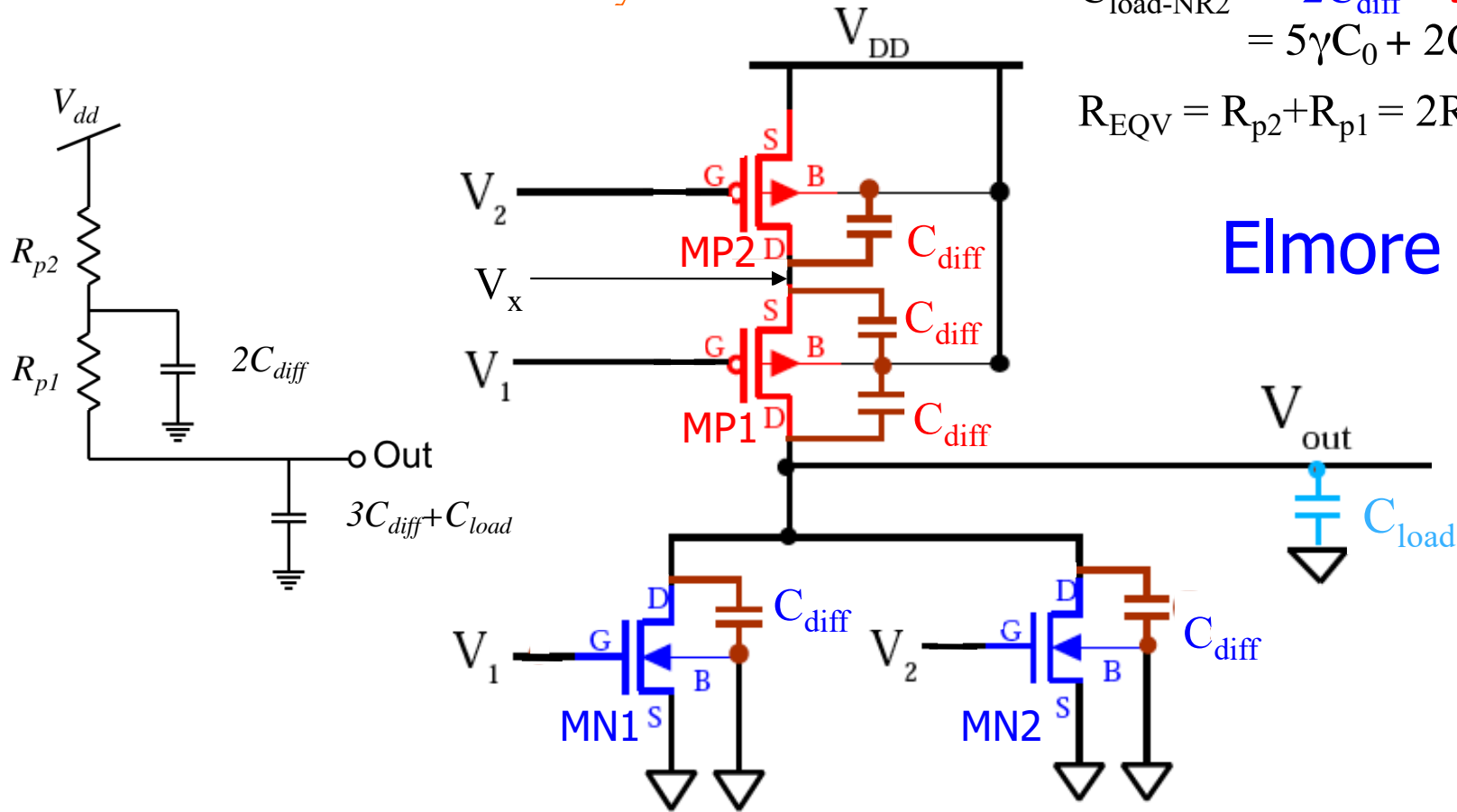

$$C_{\text{load-NR2}} \approx 2C_{\text{diff}} + 3C_{\text{diff}} + C_{\text{load}} = 5\gamma C_0 + 2C_0$$


$$R_{\text{EQV}} = R_{p2} + R_{p1} = 2R_0$$

Elmore Model?

Worst Case for Pull-up $\rightarrow V_1 = 0, V_2 = V_{DD} \rightarrow 0$ @t=0 & $V_x \approx V_{\text{out}} = 0 \rightarrow V_{DD}$

NOR2 Delay

□ Worst case delay?

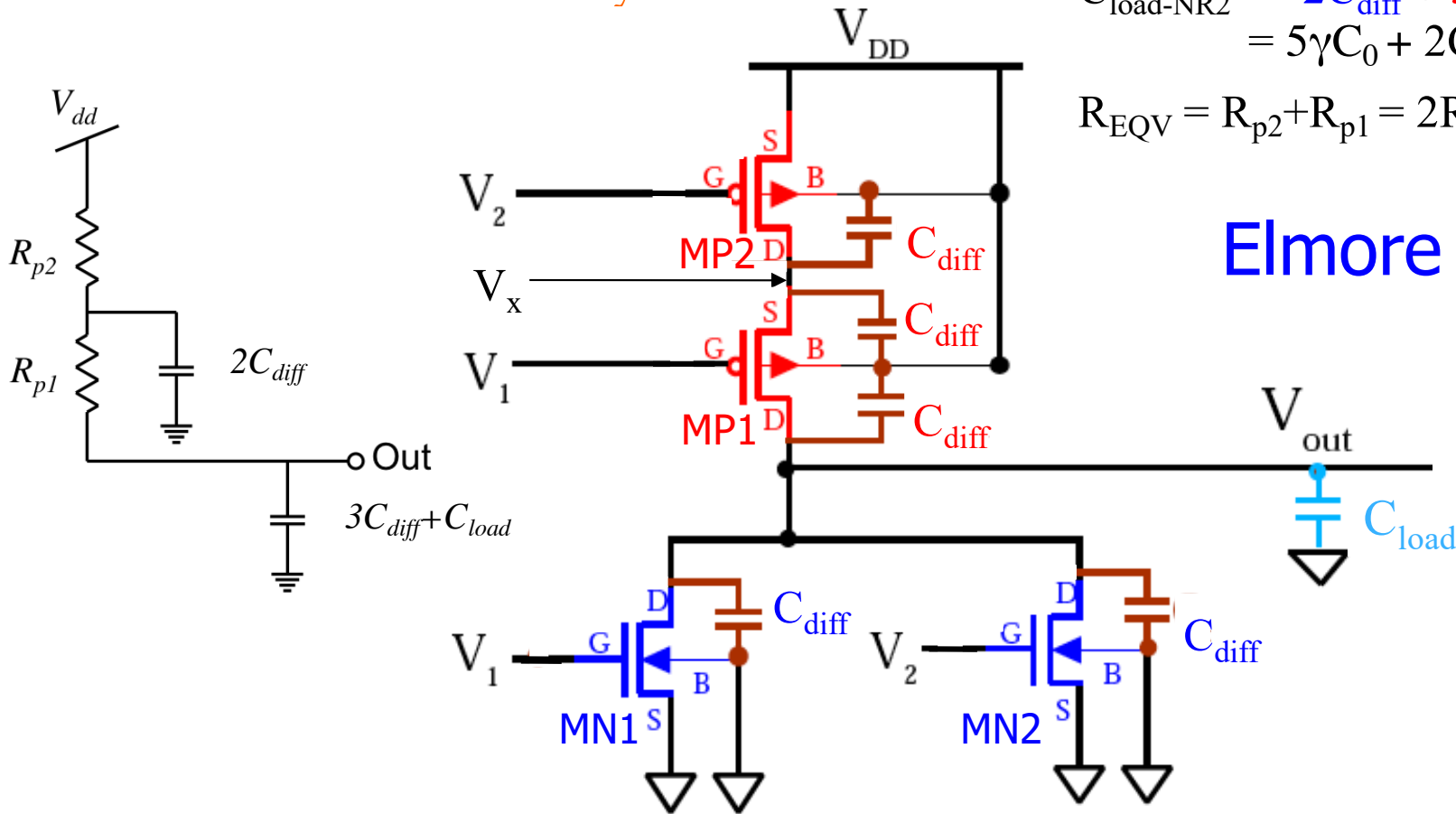

$$C_{load-NR2} \approx 2C_{diff} + 3C_{diff} + C_{load} = 5\gamma C_0 + 2C_0$$

$$R_{EQV} = R_{p2} + R_{p1} = 2R_0$$


Elmore Model?

Worst Case for Pull-up $\rightarrow V_1 = 0, V_2 = V_{DD} \rightarrow 0$ @ $t=0$ & $V_x \approx V_{out} = 0 \rightarrow V_{DD}$

$$\text{delay} = (2C_{diff})(R_{p2}) + (3C_{diff} + C_{load})(R_{p1} + R_{p2}) = (8\gamma + 4)\tau$$


NOR2 Delay

□ Worst case delay Pull-down?

 

NOR2 Delay


- Worst case delay Pull-down?

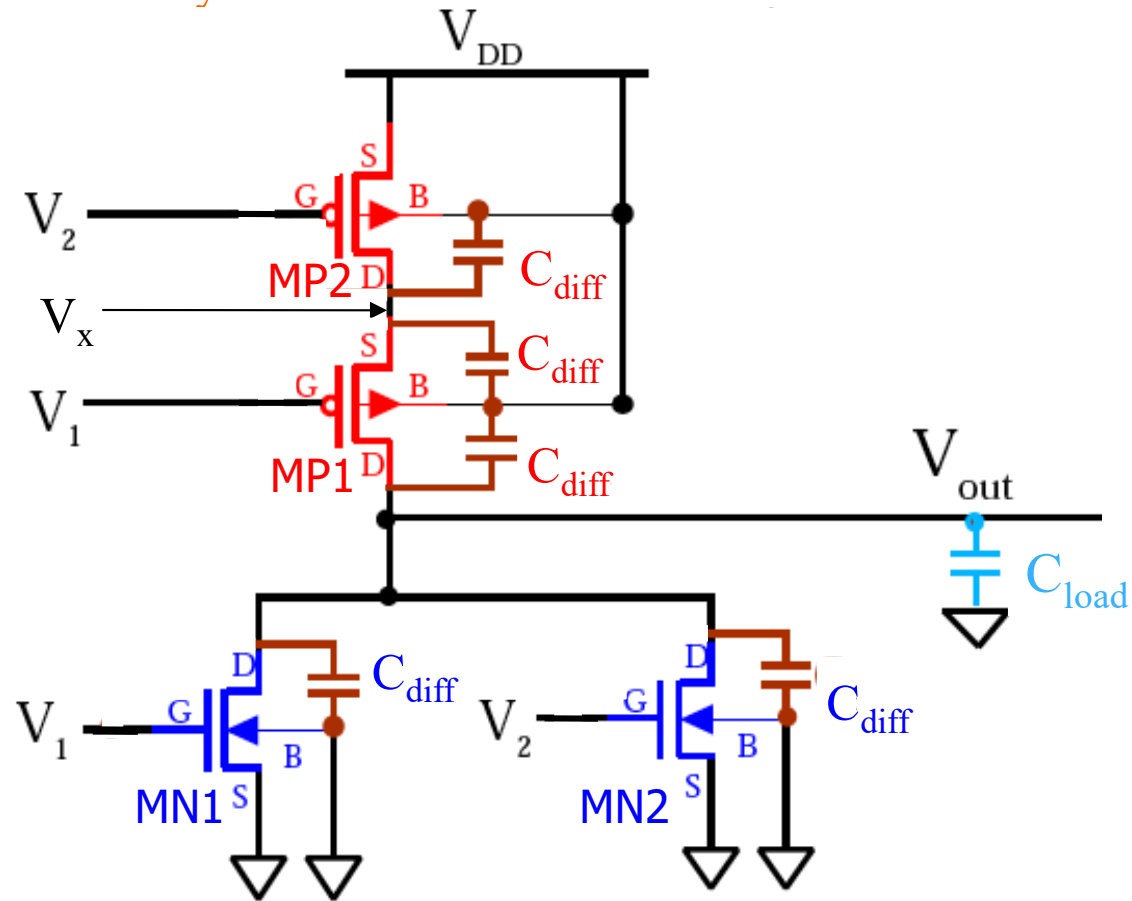

Worst case for Pull-down $\rightarrow V_1 = 0, V_2 = 0 \rightarrow V_{DD} @ t=0$ & $V_x \approx V_{out} = V_{DD} \rightarrow 0$

NOR2 Delay


- Worst case delay Pull-down?

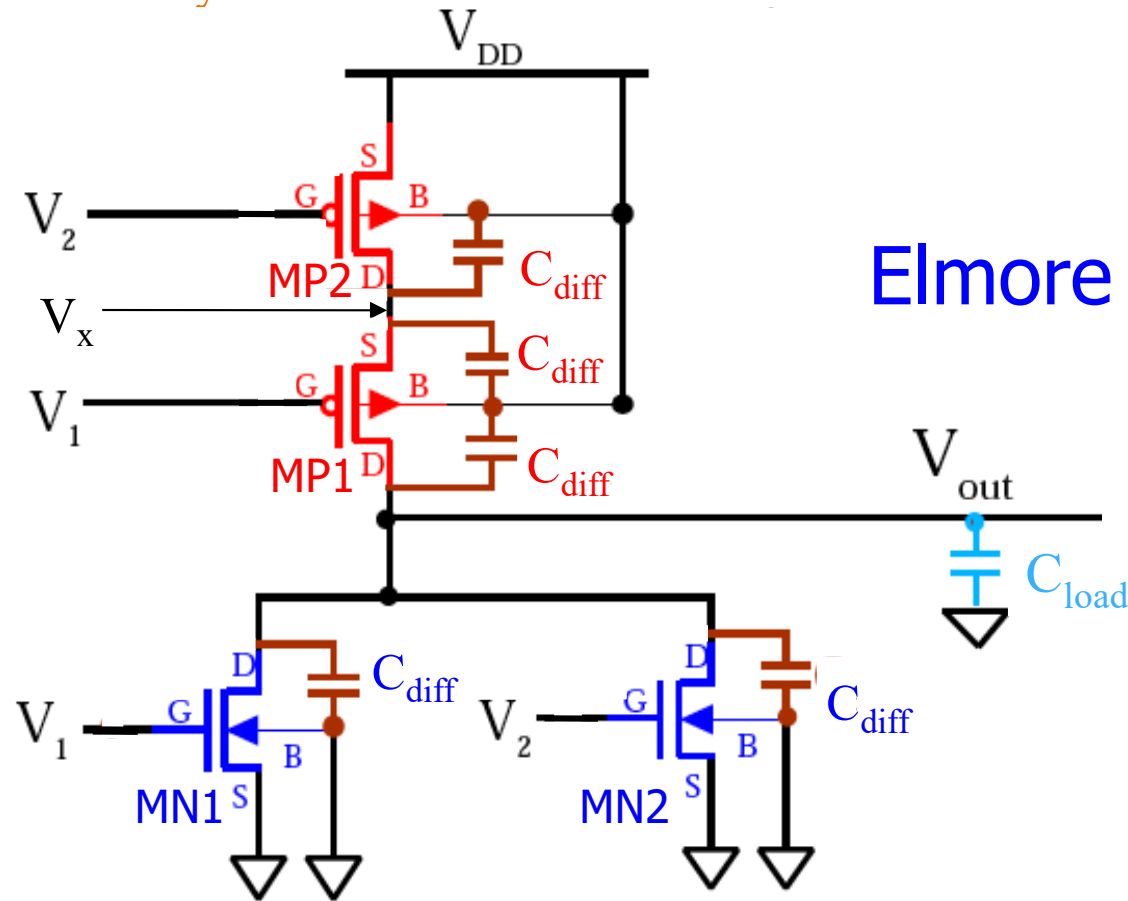

Worst case for Pull-down $\rightarrow V_1 = 0, V_2 = 0 \rightarrow V_{DD} @ t=0$ & $V_x \approx V_{out} = V_{DD} \rightarrow 0$

NOR2 Delay

Worst case delay Pull-down?

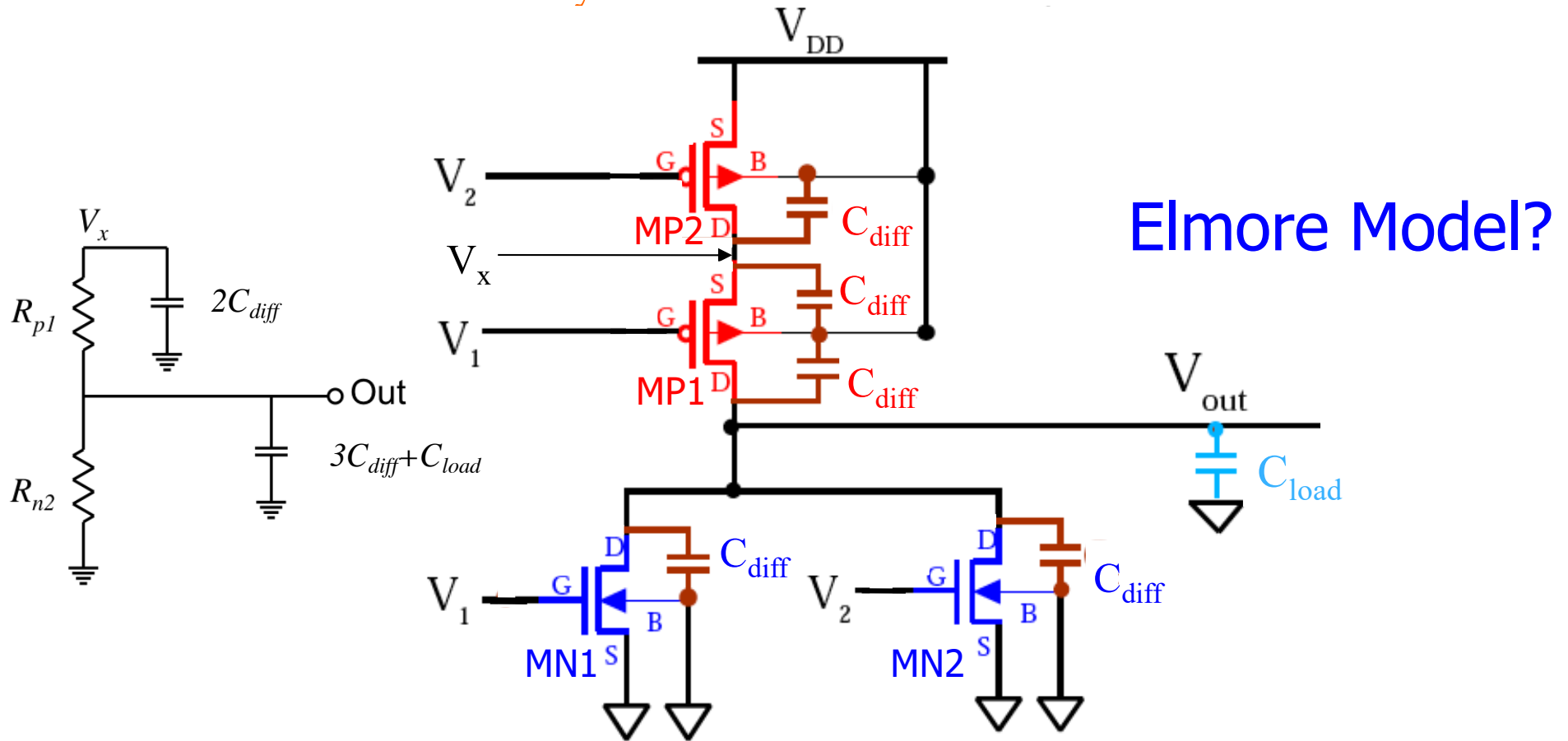


Worst case for Pull-down $\rightarrow V_1 = 0, V_2 = 0 \rightarrow V_{DD} @ t=0$ & $V_x \approx V_{out} = V_{DD} \rightarrow 0$


$$\text{delay} = (2C_{diff})(R_{p1} + R_{n2}) + (3C_{diff} + C_{load})(R_{n2}) = (7\gamma + 2)\tau$$




NAND2 Delay (preclass 11)

 

Parasitic Caps for NAND2 (worst case)

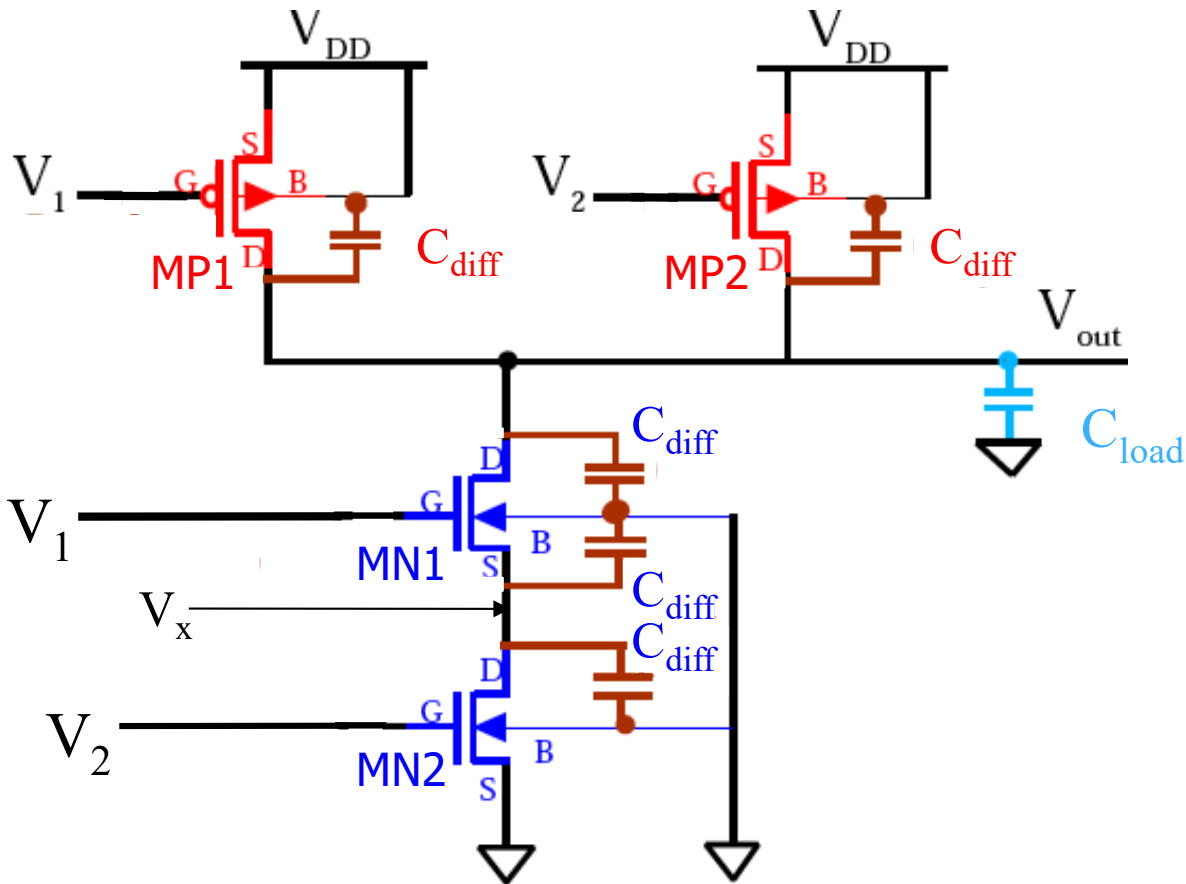


Parasitic Caps for NAND2 (worst case)

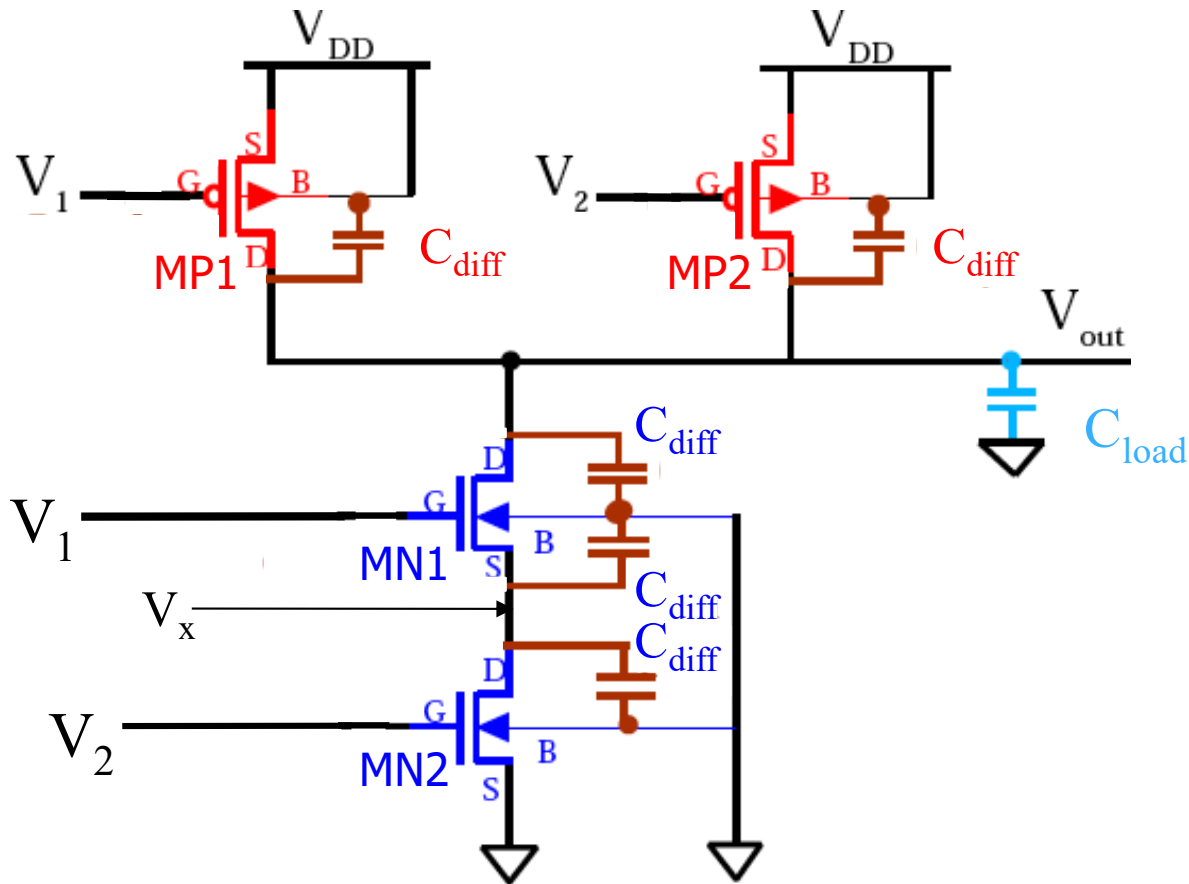


Worst case for Pull-up →

Parasitic Caps for NAND2 (worst case)

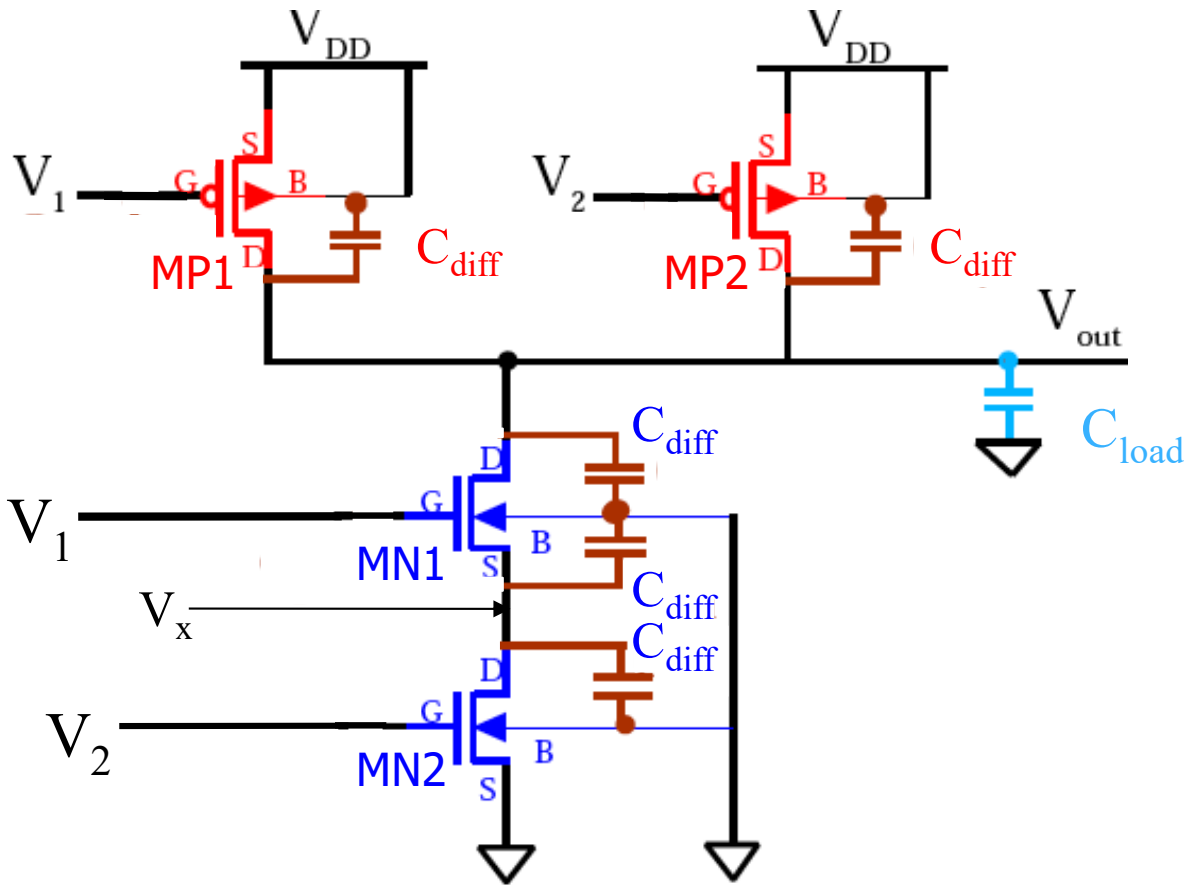


Worst case for Pull-up $\rightarrow V_1 = V_{DD}, V_2 = V_{DD} \rightarrow 0$ @ $t=0$ & $V_x \approx V_{out} = 0 \rightarrow V_{DD}$

Parasitic Caps for NAND2 (worst case)

 

Worst case for pull down →

Parasitic Caps for NAND2 (worst case)

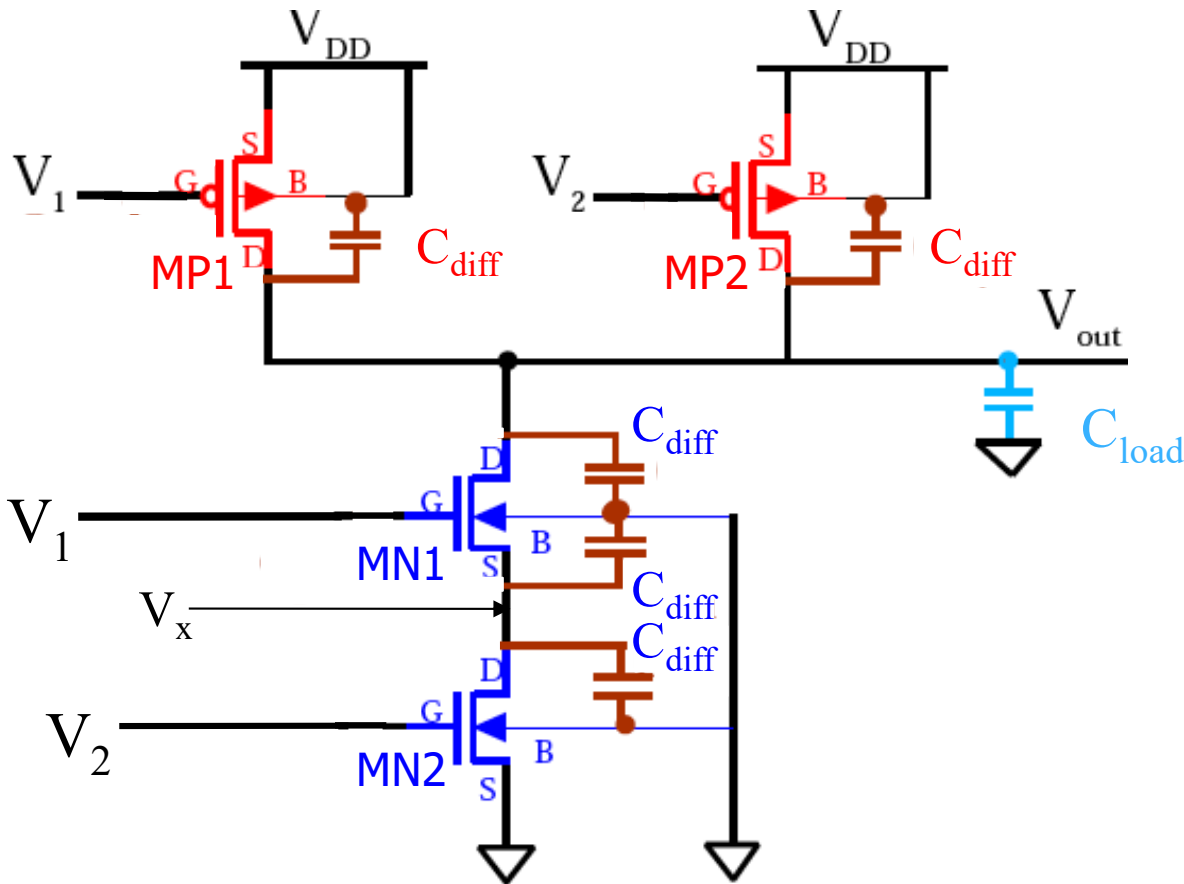

Worst case for pull down $\rightarrow V_1 = V_{DD}, V_2 = 0 \rightarrow V_{DD} @ t=0$ & $V_x \approx V_{out} = V_{DD} \rightarrow 0$



Logic Types

- ❑ CMOS Gates
 - Dual pull-down and pull-up networks, only one enabled at a time
 - Performance of gate is strong function of the fanin of gate
 - Techniques to improve performance include sizing, input reordering, and buffering (staging)
- ❑ Ratioed Gates
 - Have active pull-down (-up) network connected to load device
 - Reduced gate complexity at expense of static power asymmetric transfer function
 - Techniques to improve performance include sizing to improve noise margins and reduce static power
- ❑ Pass Gates
 - Implement logic gate as switch network for area and often delay win
 - Long cascades of switches result in quadratic increase in delay
 - Also suffer from reduced noise margins (V_T drop)
 - Use level-restoring buffers to improve noise margins
- ❑ Dynamic logic ... next time



Idea

- ❑ Elmore delay calculation allows us to estimate delay for distributed RC network
 - Necessary for pass transistors
- ❑ Wires are distributed RC
 - Half delay lumped calculation
 - Still quadratic in length



Admin

- Project 1
 - Final report due **Friday 3/24** midnight



Acknowledgement

- ❑ Prof. André DeHon (University of Pennsylvania)
- ❑ Prof. Tania Khanna (University of Pennsylvania)