

ESE370: Circuit-Level Modeling, Design, and Optimization for Digital Systems

Lec 18: April 12, 2023
Memory Core






Today

- Memory Array examples
- Memory
 - Memory core
 - 6T SRAM
- Project 2 is on this


Array-Structured Memory Architecture

 Problem: ASPECT RATIO or HEIGHT \gg WIDTH




6T SRAM Cell

 
- ❑ Cell size accounts for most of array size
 - Reduce cell size at expense of complexity
- ❑ 6T SRAM Cell
 - Used in most commercial chips
 - Data stored in cross-coupled inverters
- ❑ Read:
 - Precharge BL, BL'
 - Raise WL
- ❑ Write:
 - Drive data onto BL, BL'
 - Raise WL



6-transistor CMOS SRAM Cell

 

6-transistor CMOS SRAM Cell

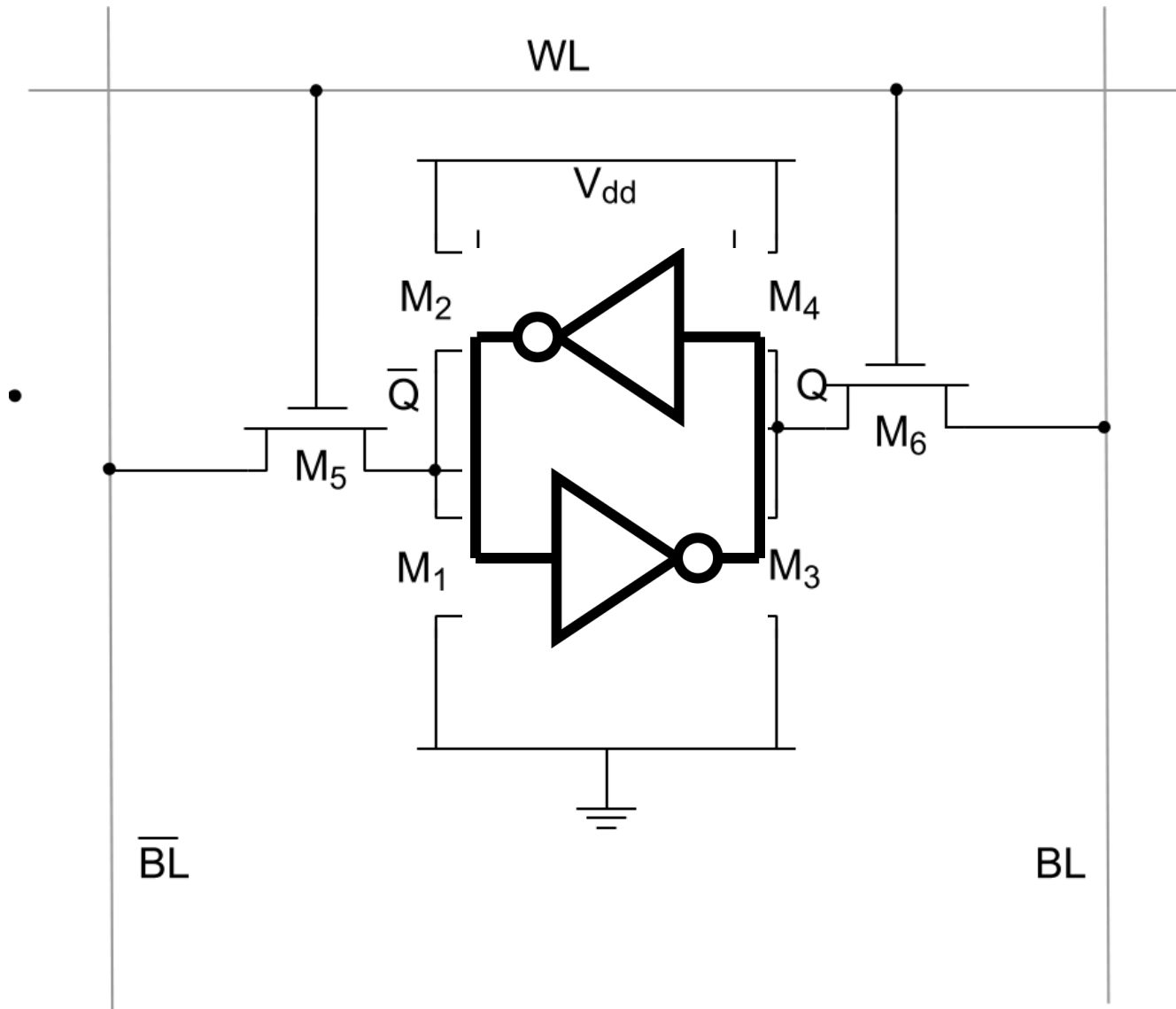


6-transistor CMOS SRAM Cell (preclass 1)


Assume 1 is stored (Q=1)

Read Operation:

 - First bitlines get **VDD**
- Then wordline goes high (Vdd)
 - Precharge disconnected




CMOS SRAM Analysis (Read) (preclass 1)

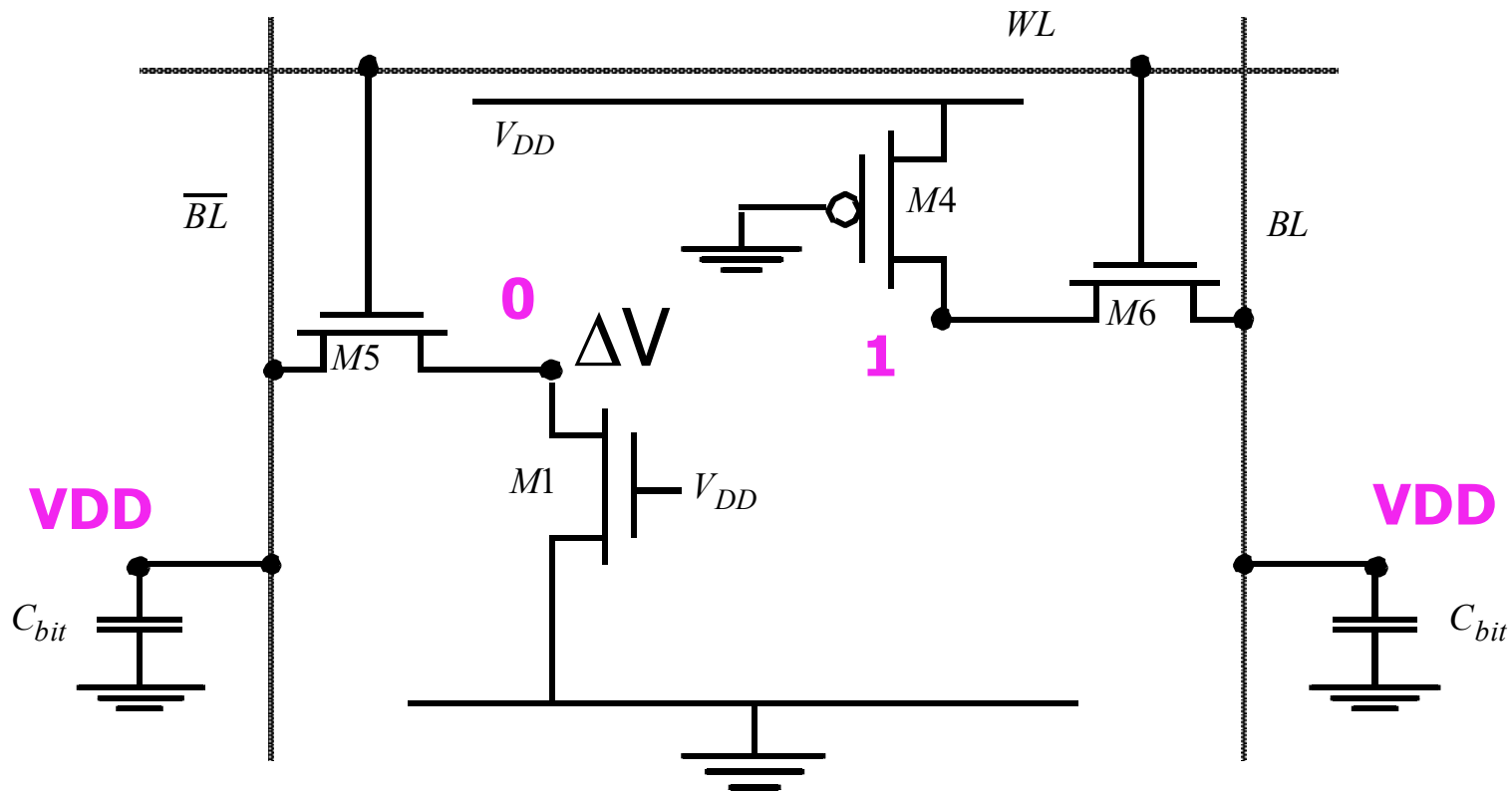


Which two transistors are discharging \overline{BL} to Gnd?
 What regions of operation are the transistors in?
 Write the KCL equation for the two transistors

CMOS SRAM Analysis (Read)

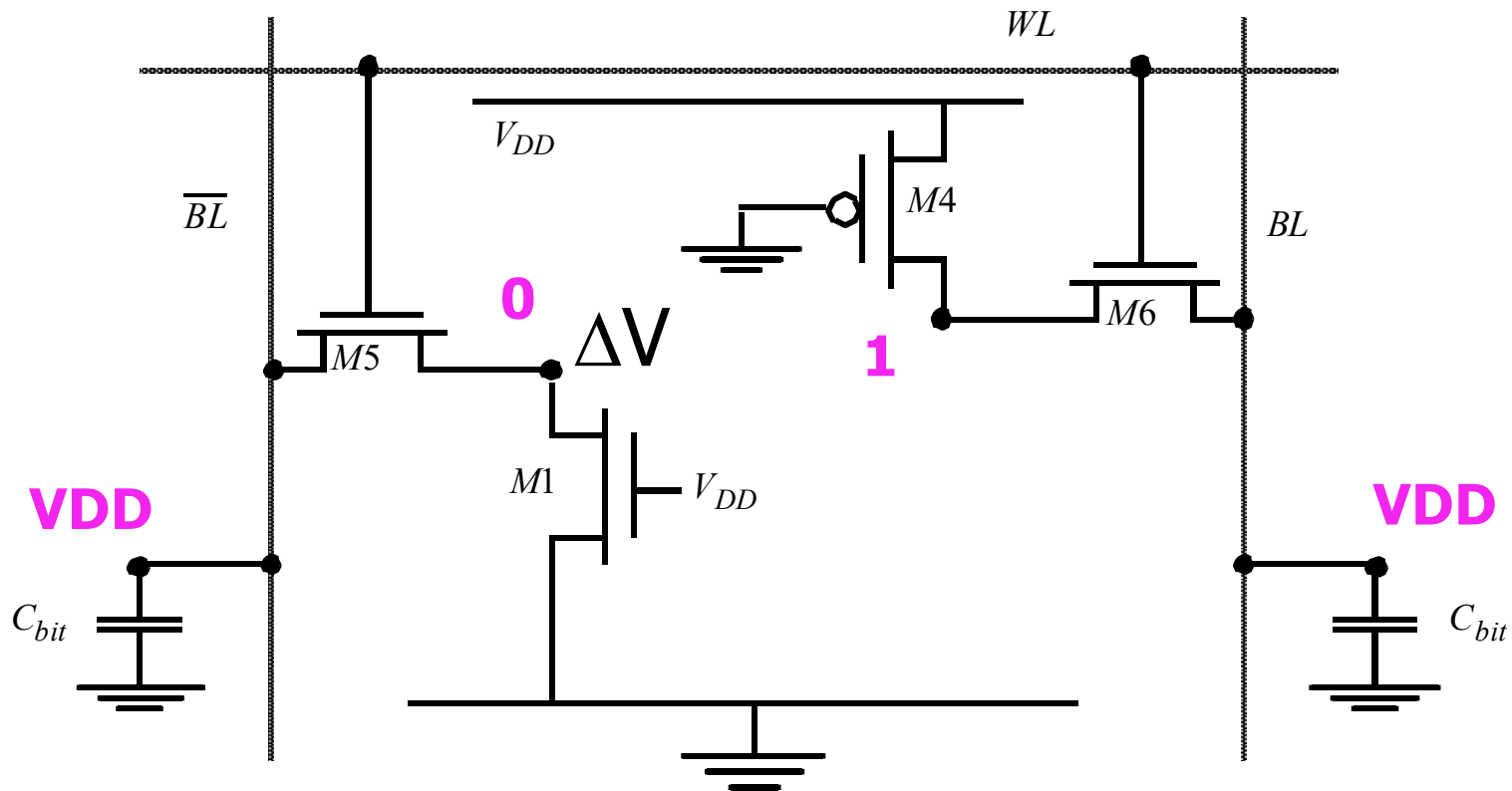


$$k_{n,M5} (V_{DD} - \Delta V - V_{Tn})^2 = k_{n,M1} \left((V_{DD} - V_{Tn}) \Delta V - \frac{\Delta V^2}{2} \right)$$

CMOS SRAM Analysis (Read)

 

$$\frac{k_{n,M1}}{k_{n,M5}} = \left(\frac{W}{L}\right)_1 = \frac{(V_{DD} - \Delta V - V_{Tn})^2}{(V_{DD} - V_{Tn})\Delta V - \frac{\Delta V^2}{2}}$$


CMOS SRAM Analysis (Read)

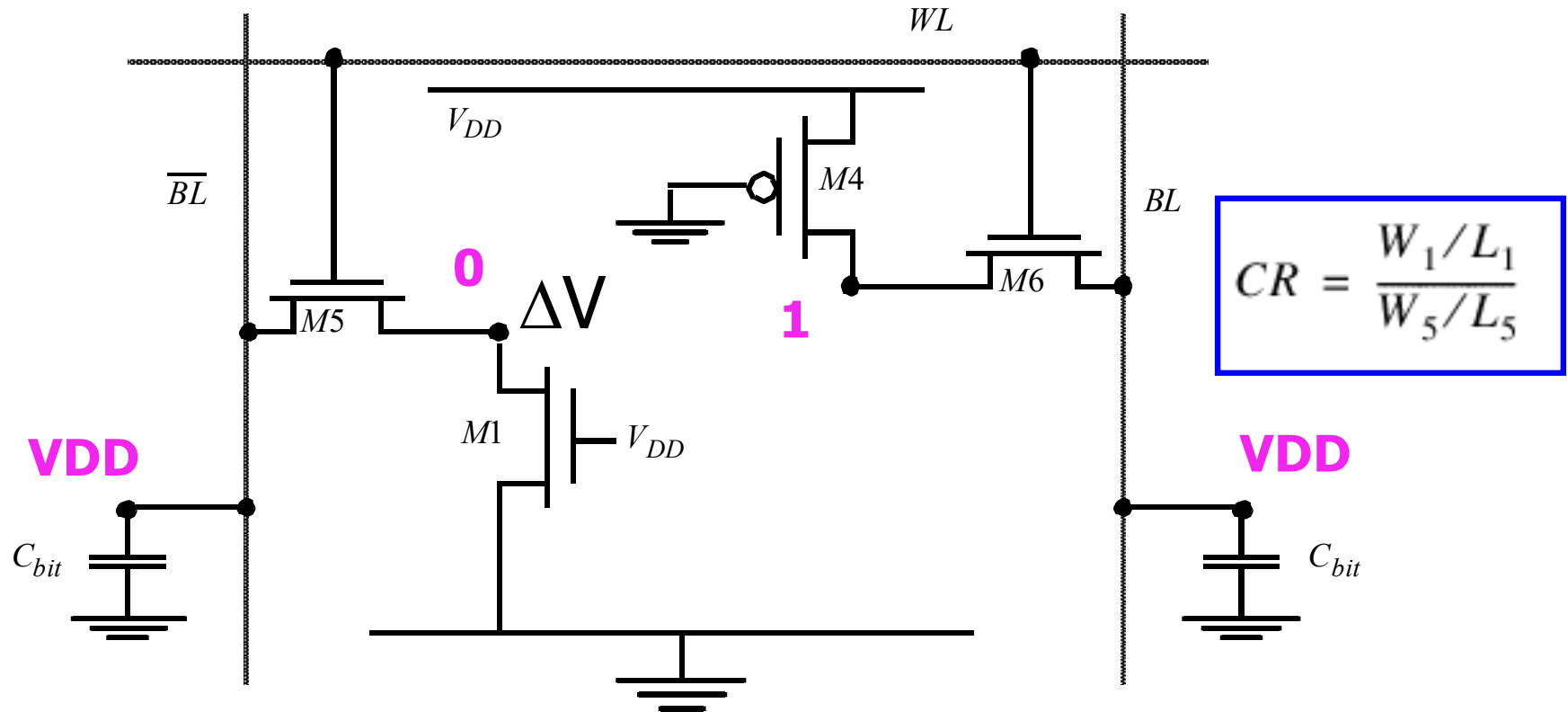

$$\frac{k_{n,M1}}{k_{n,M5}} = \frac{\left(\frac{W}{L}\right)_1}{\left(\frac{W}{L}\right)_5} = \frac{(V_{DD} - \Delta V - V_{Tn})^2}{(V_{DD} - V_{Tn})\Delta V - \frac{\Delta V^2}{2}}$$

$$\xrightarrow{\Delta V = V_{Tn}} \frac{\left(\frac{W}{L}\right)_1}{\left(\frac{W}{L}\right)_5} = \frac{(V_{DD} - 2V_{Tn})^2}{(V_{DD} - 1.5V_{Tn})V_{Tn}}$$



CMOS SRAM Analysis (Read)

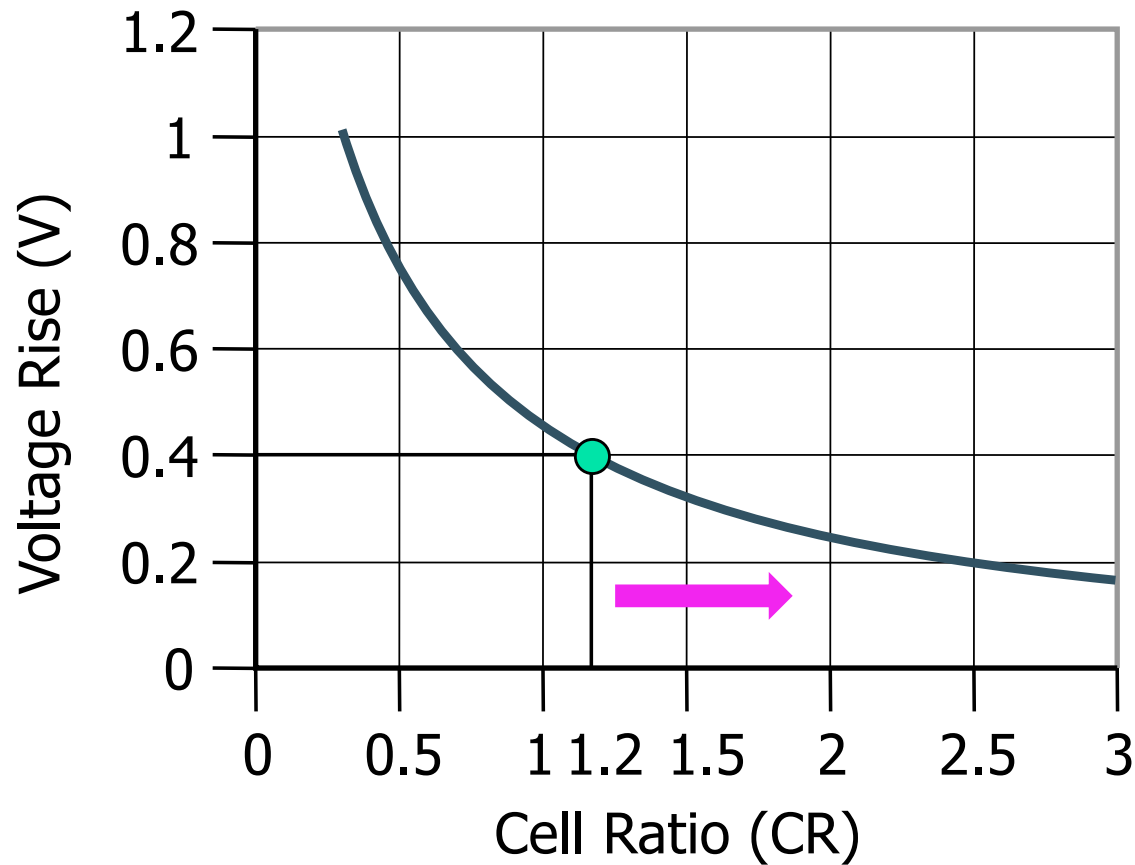

$$CR = \frac{W_1/L_1}{W_5/L_5}$$

SRAM Read

 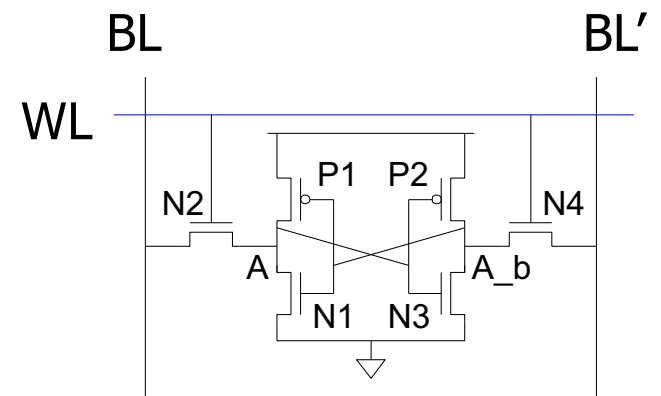- ❑ Precharge both bitlines high
- ❑ Then turn on wordline, WL
- ❑ One of the two bitlines will be pulled down by the cell
- ❑ Ex: $A = 0, A_b = 1$
 - BL discharges, BL' stays high
 - But A bumps up slightly
- ❑ *Read stability*
 - A must not flip
 - $N1 > N2$




6-transistor CMOS SRAM Cell (preclass 2)


Assume 1 is stored (Q=1)

Write Operation:

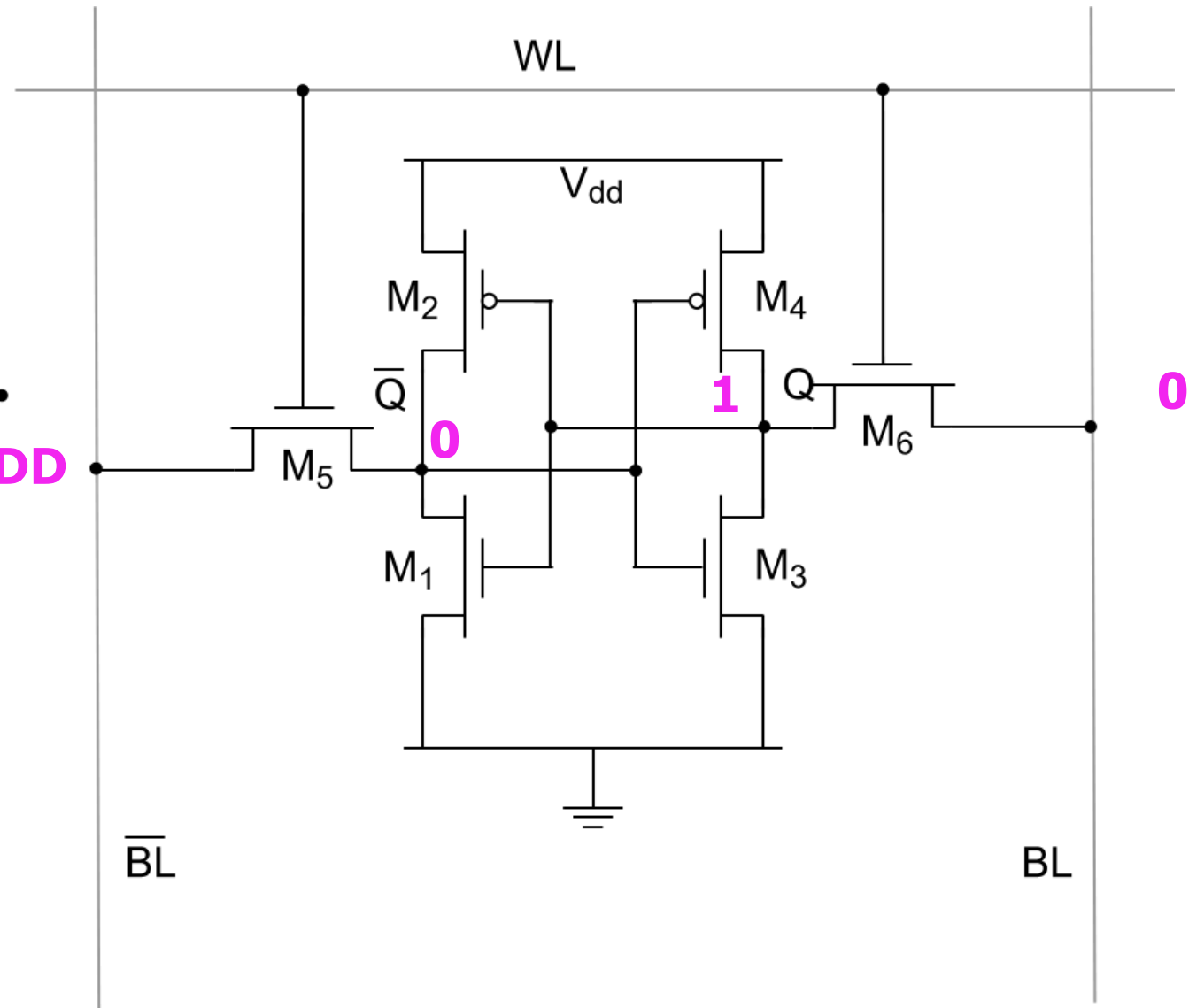- Want to write a 0 **VDD**
- First drive bitlines with input data
- Then wordline goes high (Vdd)
 - Still driving bitlines




CMOS SRAM Analysis (Write) (preclass 2)

 


- Which transistor discharges Q to Gnd?
- Which transistor must it overpower?
- What regions of operation are the transistors in?
- Write the KCL equation for the two transistors

CMOS SRAM Analysis (Write)

 


$$k_{p,M4} (V_{DD} - |V_{Tp}|)^2 = k_{n,M6} \left((V_{DD} - V_{Tn})V_Q - \frac{V_Q^2}{2} \right)$$

CMOS SRAM Analysis (Write)

 

$$\frac{k_{p,M4}}{k_{n,M6}} = \frac{(V_{DD} - V_{Tn})V_Q - \frac{V_Q^2}{2}}{(V_{DD} - |V_{Tp}|)^2}$$

CMOS SRAM Analysis (Write)

 


$$PR = \frac{W_4/L_4}{W_6/L_6}$$

$$\frac{k_{p,M4}}{k_{n,M6}} = \frac{(V_{DD} - V_{Tn})V_Q - \frac{V_Q^2}{2}}{(V_{DD} - |V_{Tp}|)^2}$$

$$V_Q = V_{Tn}$$

$$\frac{k_{p,M4}}{k_{n,M6}} = \frac{(V_{DD} - V_{Tn})V_{Tn} - \frac{V_{Tn}^2}{2}}{(V_{DD} - |V_{Tp}|)^2}$$


CMOS SRAM Analysis (Write)

 

$$PR = \frac{W_4/L_4}{W_6/L_6}$$


SRAM Write

 - Drive one bitline high, the other low
 - Depending on write data
- Then turn on wordline, WL
- Bitlines overpower cell with new value
- Ex: $A = 0$, $A_b = 1$, $BL = 1$, $BL' = 0$
 - Force A_b low, then A charges high
- *Writability*
 - Must overpower feedback inverter
 - $N4 \gg P2$




SRAM Column Example

read

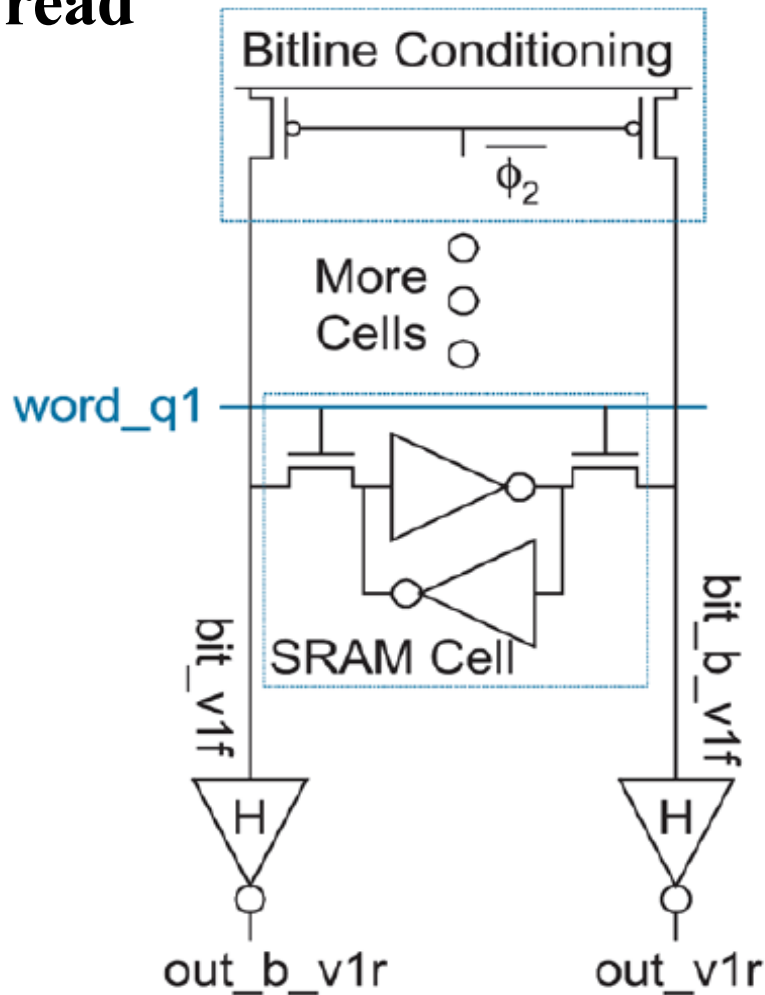


write

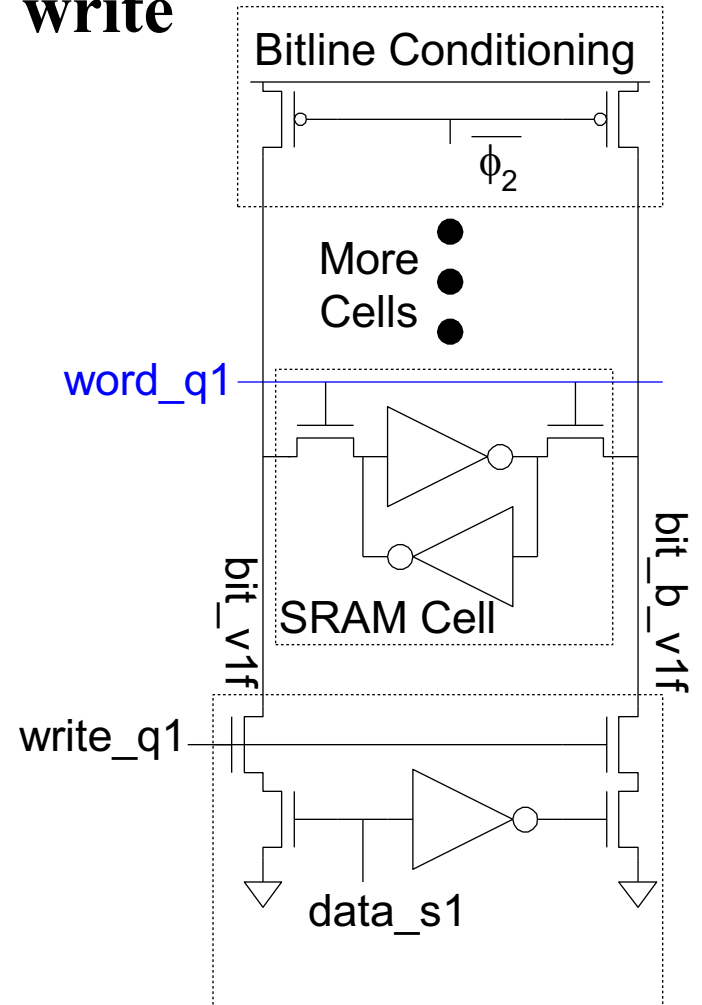


Multiple Ports

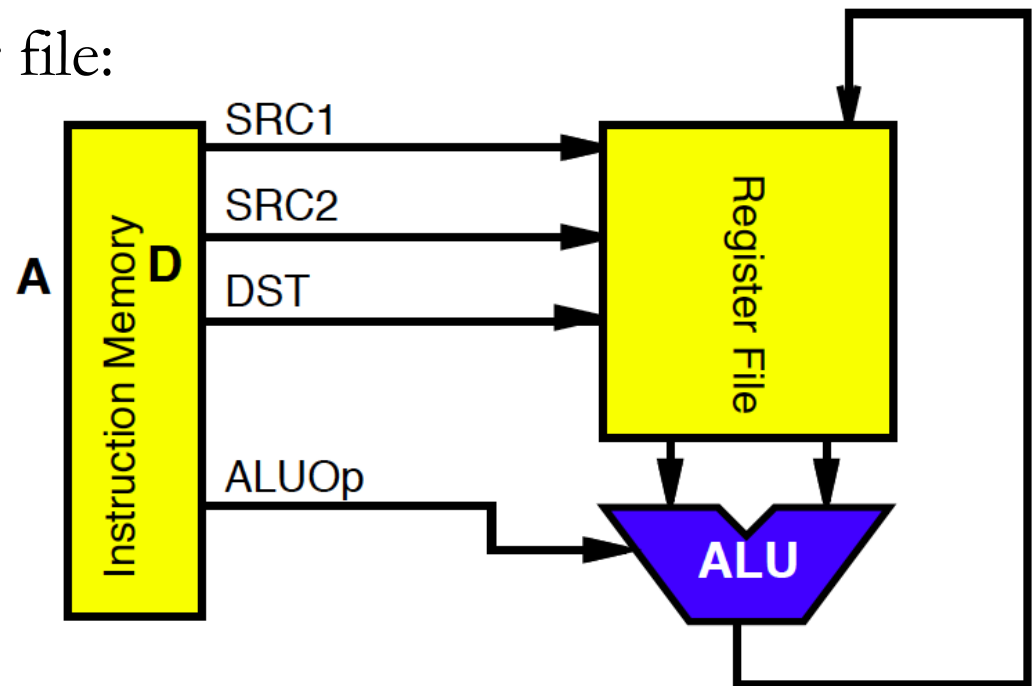- ❑ We have considered single-ported SRAM
 - One read or one write on each cycle
- ❑ *Multiported* SRAM are needed for register files
- ❑ Examples:
 - Pipelined ALU register file:
 - `add r1,r2,r3`
 - $R3 \leftarrow R1 + R2$
 - Requires two reads and one write




Multi-Ported SRAM

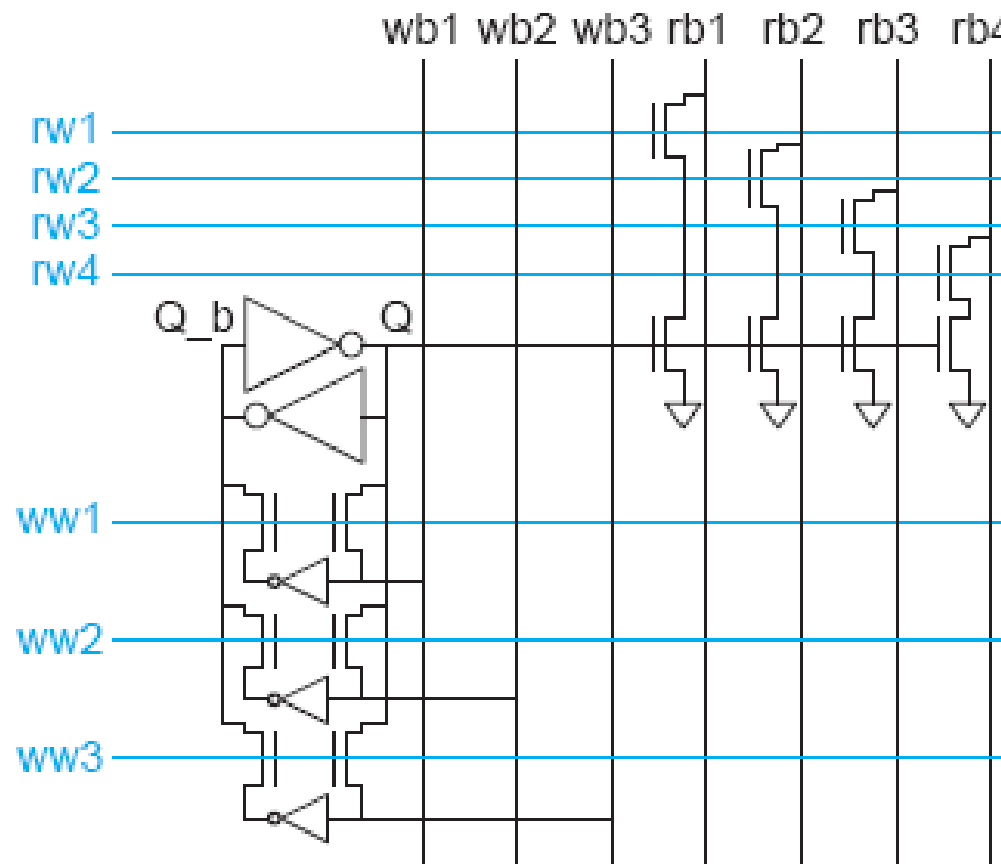- ❑ Adding more access transistors hurts read stability
- ❑ Multiported SRAM isolates reads from state node
- ❑ Single-ended bitlines save area




Register File Cell

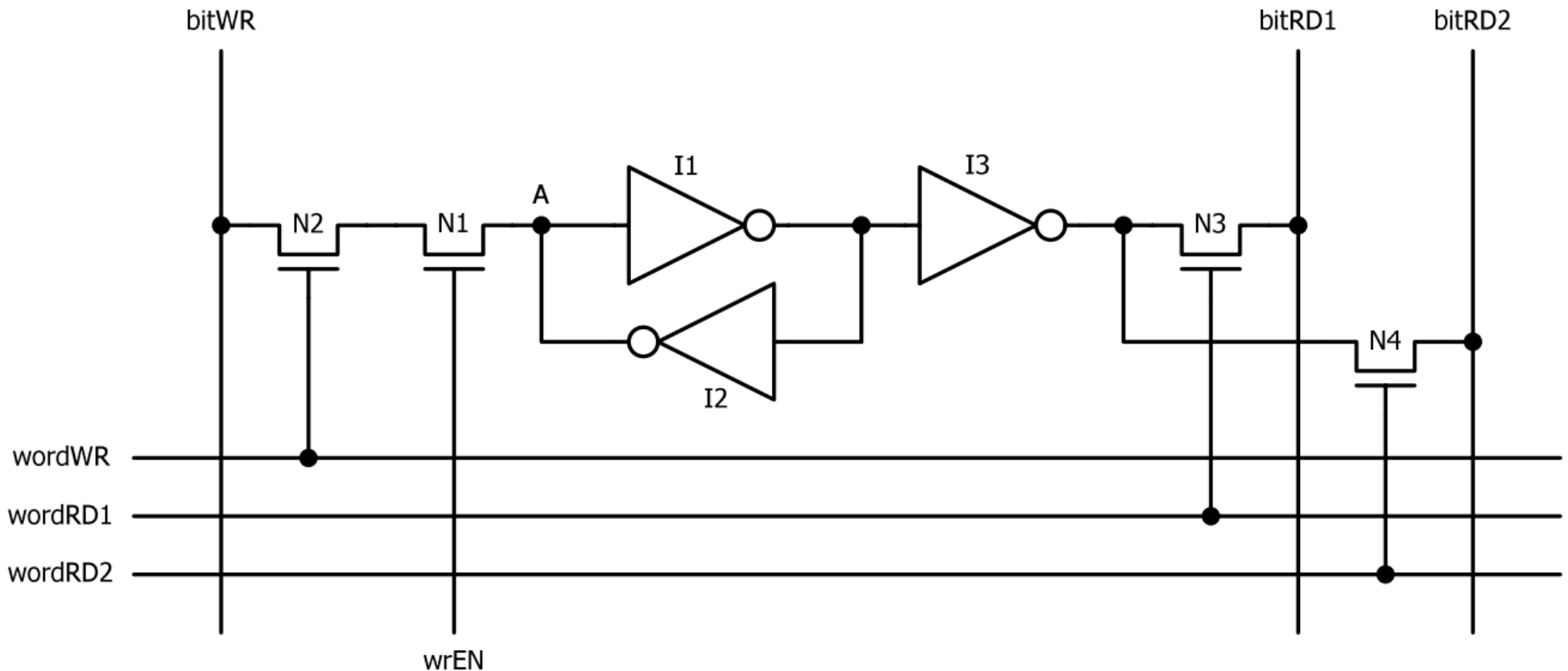- Single-ended 2-read/1-write ports (Slow-write)



Register File Cell

- Single-ended Read/Dual-ended Write

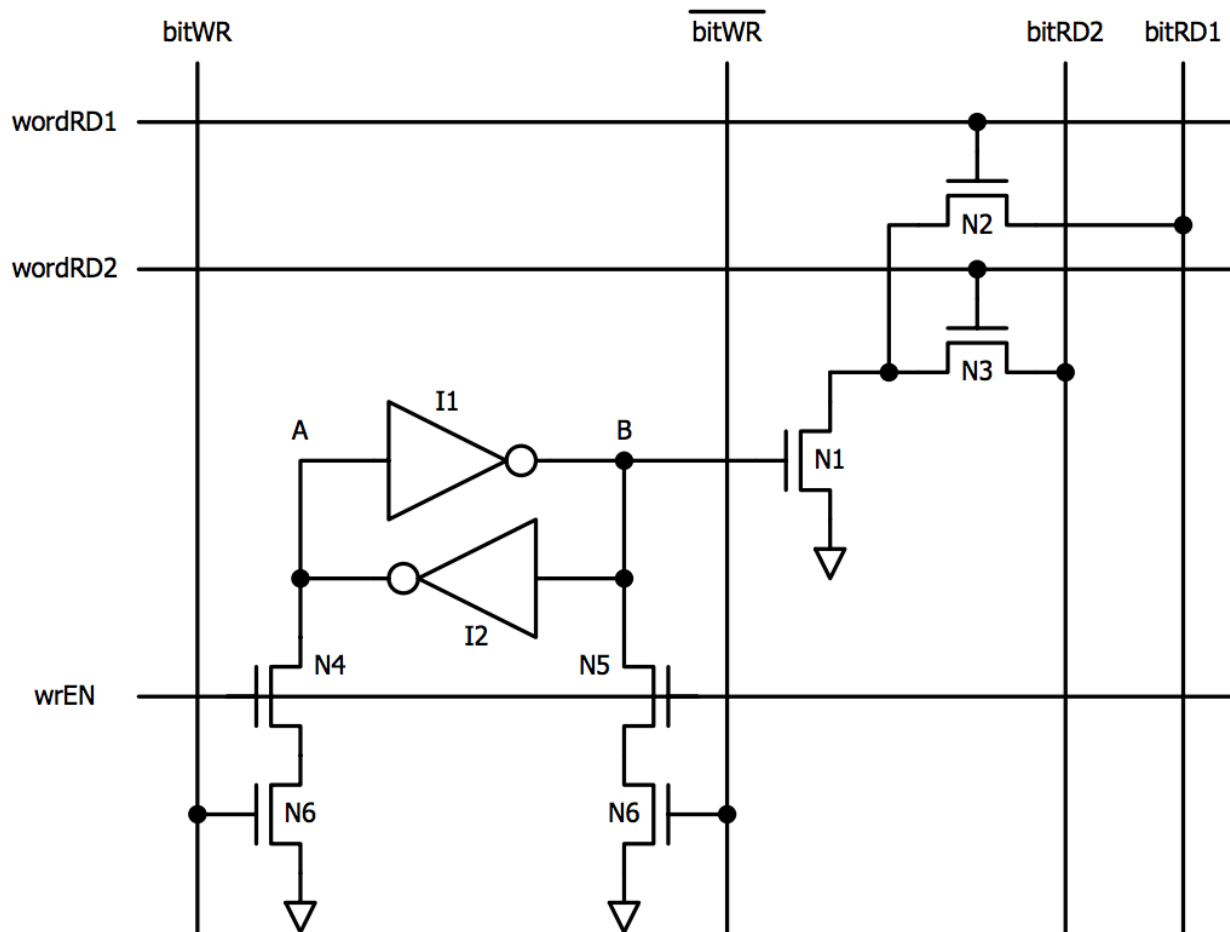






DRAM

- ❑ Smaller than SRAM
- ❑ Require data refresh to compensate for leakage

1-Transistor DRAM Cell

 


1-Transistor DRAM Cell

  

Write: C_S is charged or discharged by asserting WL and BL.

1-Transistor DRAM Cell

 



Write: C_S is charged or discharged by asserting WL and BL.

Read: Charge redistribution takes place between bit line and storage capacitance

$$\Delta V = V_{BL} - V_{PRE} = (V_{BIT} - V_{PRE}) \frac{C_S}{C_S + C_{BL}}$$

Voltage swing is small; typically around 250 mV.

1-Transistor DRAM Cell

  

Write: C_S is charged or discharged by asserting WL and BL.

Read: Charge redistribution takes place between bit line and storage capacitance

$$\Delta V = V_{BL} - V_{PRE} = (V_{BIT} - V_{PRE}) \frac{C_S}{C_S + C_{BL}}$$

Voltage swing is small; typically around 250 mV.



DRAM Cell Observations

- ❑ 1T DRAM requires a sense amplifier for each bit line, due to charge redistribution read-out
- ❑ DRAM memory cells are single ended in contrast to SRAM cells
- ❑ The read-out of the 1T DRAM cell is destructive; read and refresh operation are necessary for correct operation
- ❑ 1T cell requires presence of an extra capacitance that must be explicitly included in the design
- ❑ When writing a “1” into a DRAM cell, a threshold voltage is lost. This loss can be circumvented by bootstrapping the word lines to a higher value than V_{DD} .



Big Idea

- ❑ 6T SRAM
 - Robust cell when sized carefully
- ❑ 5T SRAM
 - More sensitive to sizing than 6T SRAM
- ❑ Minimize area of repeated cell
 - 6T/5T SRAM
 - Multiport trade off area for function
 - 1T/3T DRAM helps but slower
- ❑ Compensate with periphery
 - Decoders
 - Bitline (column) drivers
 - Sensing/Amplification (regeneration/restoration)



Admin

- Project 2 out - **START NOW!**
 - Work in teams up to 2
 - Final report due 4/26



Acknowledgement

- ❑ Prof. André DeHon (University of Pennsylvania)
- ❑ Prof. Tania Khanna (University of Pennsylvania)