

# ESE370: Circuit-Level Modeling, Design, and Optimization for Digital Systems

---

Lec 19: April 19, 2023

Crosstalk






# Today

---


- Crosstalk
  - Characterization
    - Magnitude
  - Avoiding
    - Design practices
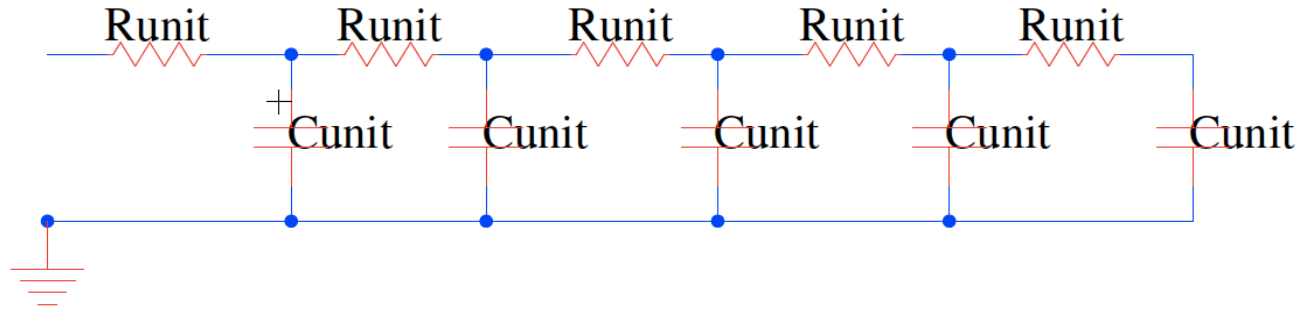
# Capacitance

- There are capacitors everywhere
- We already talked about
  - Wires modeled as a distributed RC network



 - Parasitic capacitances between terminals on transistor





# Capacitance Everywhere

---

- Potentially a capacitor between any two conductors
  - On the chip
  - On the package
  - On the board
- All wires
  - Package pins
  - PCB traces (what you did in lab)
  - Cable wires
  - Bit/word lines



# Capacitance...


---

- ❑ ...decreases with conductor separation
- ❑ ...increases with size
- ❑ ...depends on dielectric

$$C = \epsilon_r \epsilon_0 \frac{A}{d}$$
 
# Wire Capacitance

- ❑ Changes in voltage on one wire may couple through parasitic capacitance to an adjacent wire





# Crosstalk

---

- A wire has high capacitance to its neighbor.
  - When the neighbor switches from 1- $\rightarrow$  0 or 0- $\rightarrow$ 1, the wire tends to switch too.
  - Called capacitive *coupling* or *crosstalk*.
- Crosstalk effects
  - Noise on non-switching wires
  - Increased delay on switching wires

# Qualitative

---







 
# Undriven Wire

---

- ❑ What happens to undriven wire?
- ❑ Where do we have undriven wires?





 
# Driven Wire

---

- What happens to a driven “neighbor” wire?
  - One wire switches
  - Neighbors driven but not switch
  - What happens to neighbors?





# Clocked Logic

---

- ❑ CMOS driven lines
- ❑ Clocked logic
  - Willing to wait to settle/evaluate
  
- ❑ Impact is on delay
  - May increase delay of transitions


# Quantitative

---




# Isolated Wire RC

$$R = \frac{\rho L}{A}$$

 


$$C = \epsilon_d \frac{A}{d}$$


 


# Isolated Wire RC

$$R = \frac{\rho L}{A}$$

 


$$C = \epsilon_d \frac{A}{d}$$

  


# Wire step response (preclass 1)

- Step response for isolated wire?

 
 
# Undriven Adjacent Wire (preclass 2)


- $V_1$  transitions from 0 to  $V$ 
  - How big is the noise on  $V_2$ ?




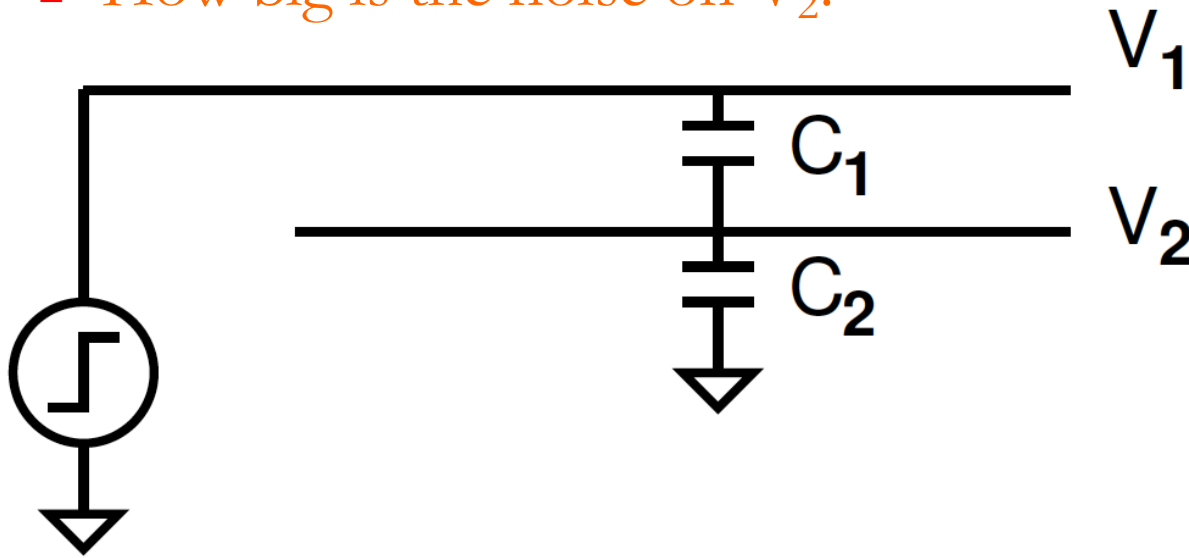
# Undriven Adjacent Wire

- $V_1$  transitions from 0 to  $V$ 
  - How big is the noise on  $V_2$ ?




$$I(t) = C \frac{dV(t)}{dt}$$

# Undriven Adjacent Wire

□  $V_1$  transitions from 0 to  $V$

■ How big is the noise on  $V_2$ ?

 


$$I(t) = C \frac{dV(t)}{dt}$$

# Undriven Adjacent Wire

□  $V_1$  transitions from 0 to  $V$

■ How big is the noise on  $V_2$ ?

$$I(t) = C \frac{dV(t)}{dt}$$

 



$$C_1 \frac{d(V_1(t) - V_2(t))}{dt} = C_2 \frac{dV_2(t)}{dt}$$

$$C_1 \frac{dV_1(t)}{dt} = (C_1 + C_2) \frac{dV_2(t)}{dt}$$


$$C_1 V_1(t) = (C_1 + C_2) V_2(t)$$

$$V_2(t) = \frac{C_1}{C_1 + C_2} V_1(t)$$

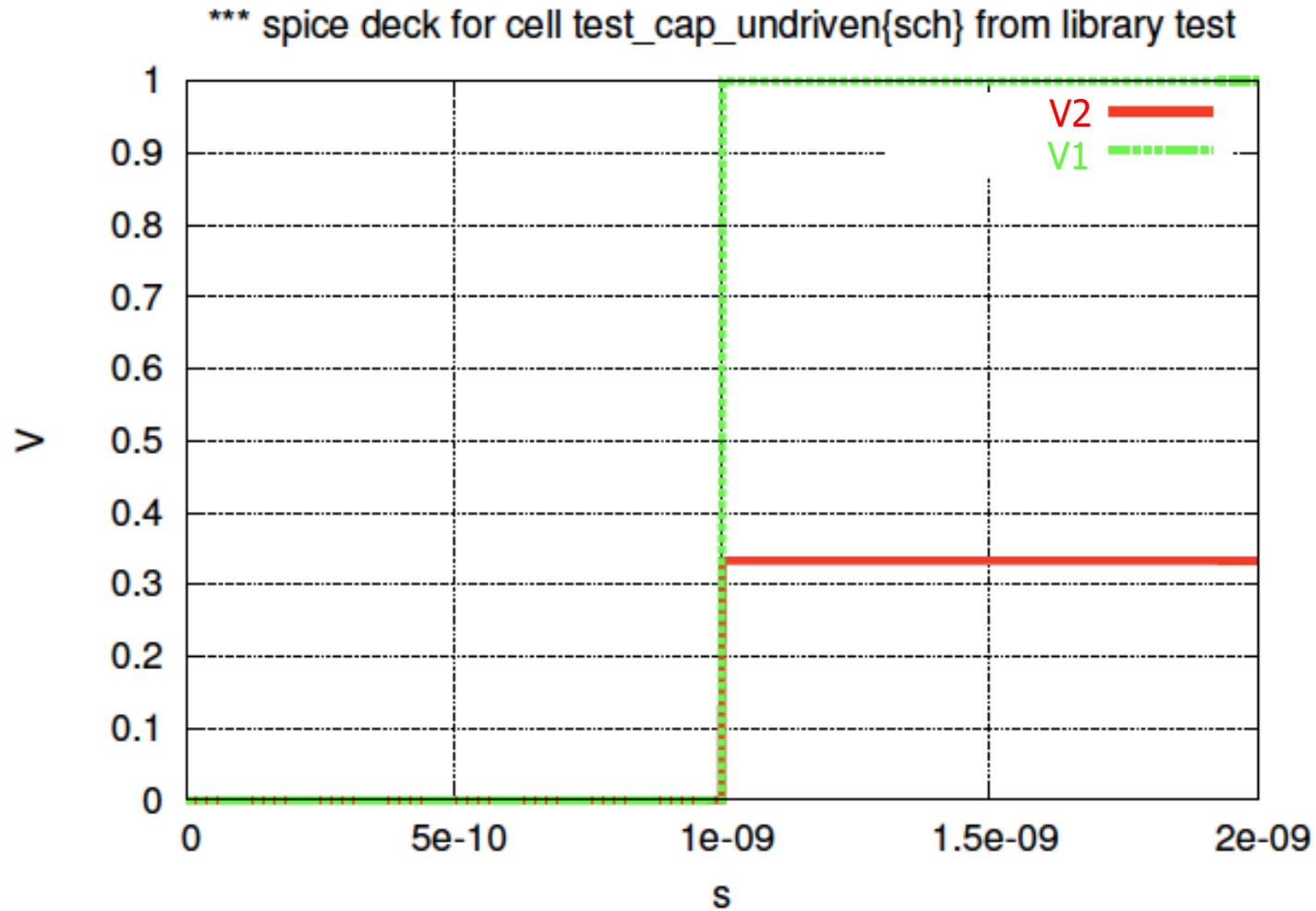 
SPICE  $C_1=10\text{pF}$ ,  $C_2=20\text{pF}$



 SPICE  $C_1=10\text{pF}$ ,  $C_2=20\text{pF}$




 \*\*\* spice deck for cell test\_cap\_undriven{sch} from library test


 
# Good (?) Capacitance


- High capacitance to ground plane ( $C_2$ )
  - Limits node swing from adjacent conductors



$$V_2 = \left( \frac{C_1}{C_1 + C_2} \right) V_1$$

 
# Driven Adjacent Wire (preclass 2)

- What happens when neighbor line is driven?



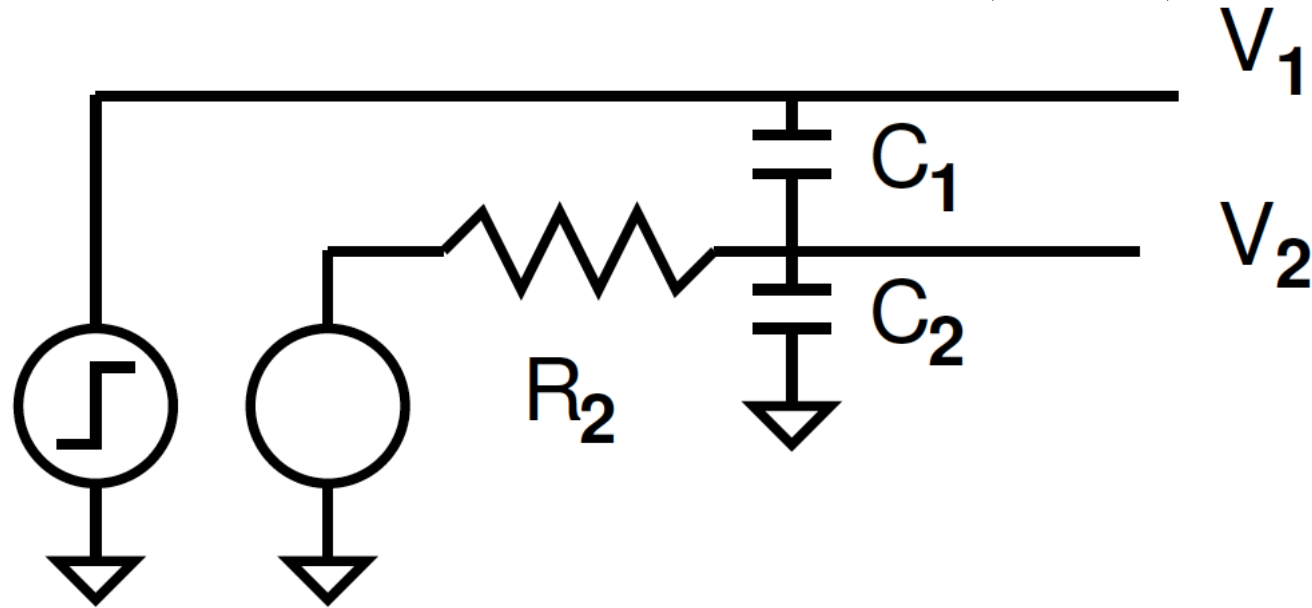
# Driven Adjacent Wire

- What happens when neighbor line is driven?
  - Recovers with time constant:  $R_2(C_1 + C_2)$







 
Spice:  $R_2=1\text{K}$ ,  $C_1=10\text{pF}$ ,  $C_2=20\text{pF}$



 \*\*\* spice deck for cell test\_cap\_undriven{sch} from library



  Spice:  $R_2=1\text{K}$ ,  $C_1=10\text{pF}$ ,  $C_2=20\text{pF}$




# Magnitude of Noise on Driven Line (preclass 3)

- Magnitude of diversion depends on relative time constants

- $\tau_1 \ll \tau_2$


- $\tau_1 \gg \tau_2$

- $\tau_1 \sim \tau_2$

 

 
# Magnitude of Noise on Driven Line

- Magnitude of diversion depends on relative time constants
  - $\tau_1 \ll \tau_2$ 
    - full diversion, then recover
  - $\tau_1 \gg \tau_2$ 
    - Drive capacitor ( $C_2$ ) faster than line 1 can change
      - little noise
  - $\tau_1 \sim \tau_2$ 
    - Somewhere in between





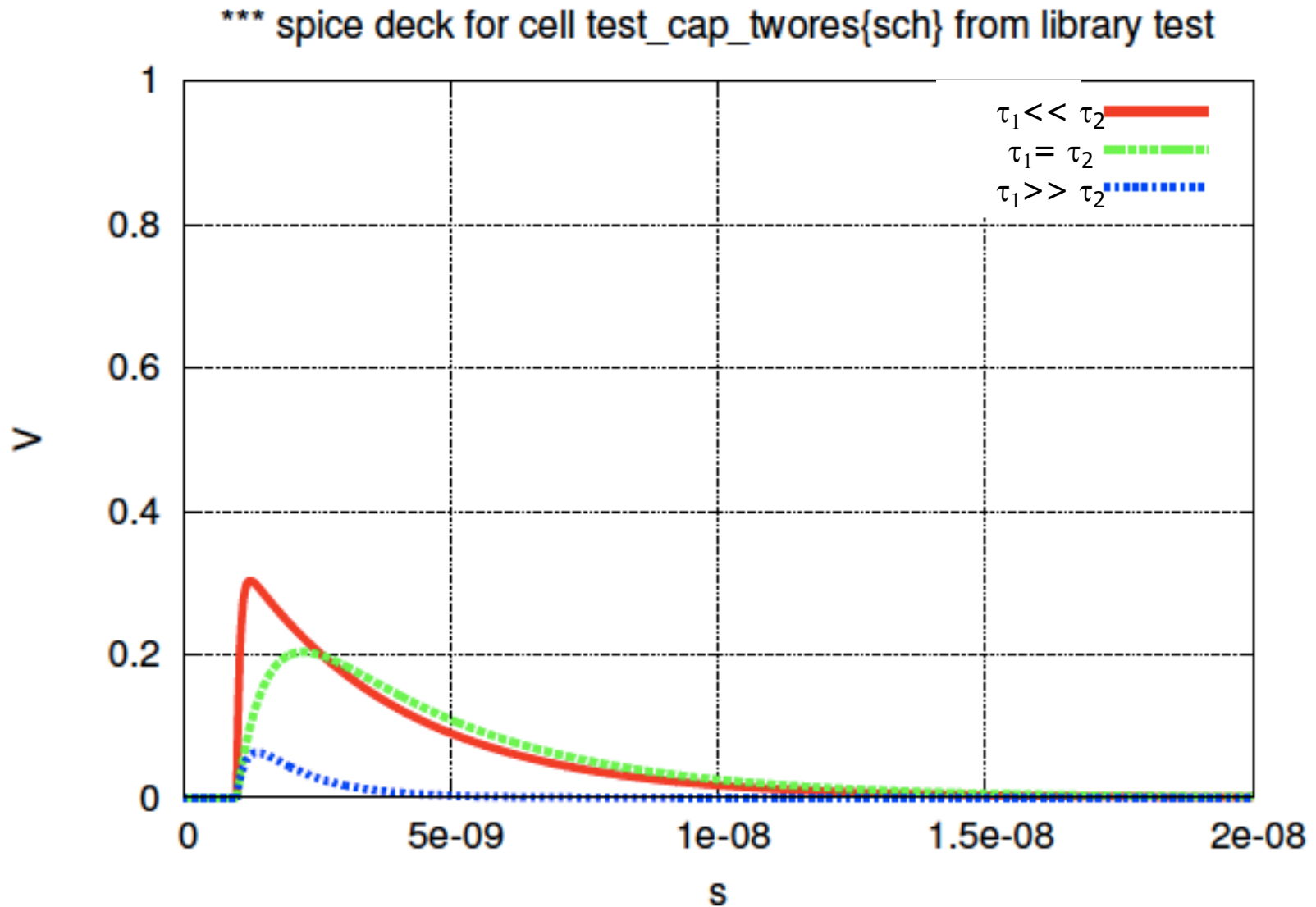
# Spice: $C_1=1\text{pF}$ , $C_2=2\text{pF}$



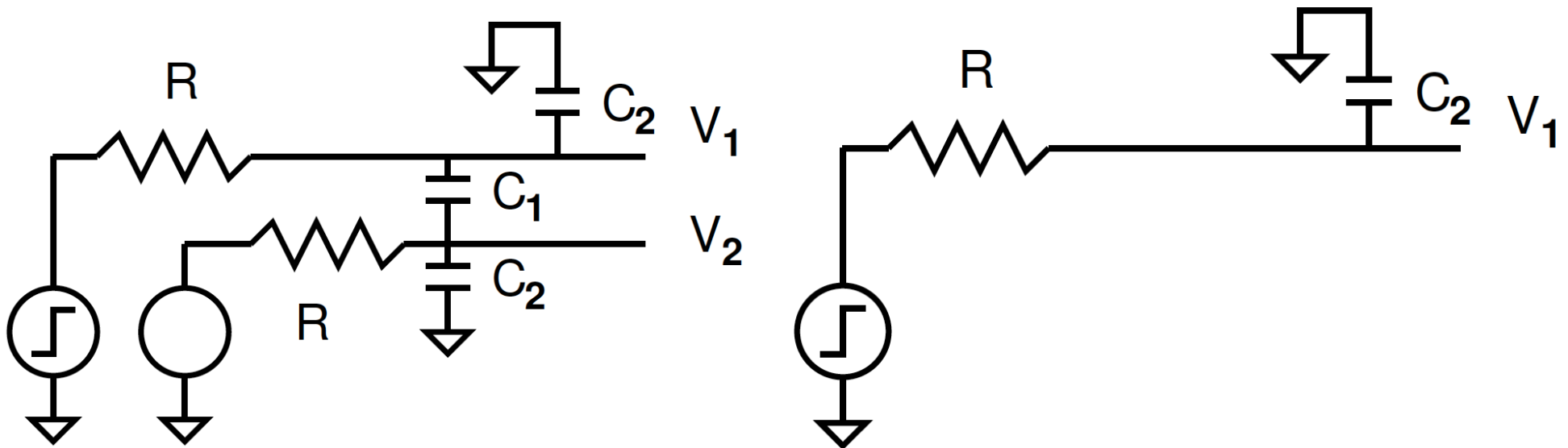
# Switching Line with Finite Drive

- What impact does the presence of the neighbour line have on the **switching** line?
  - All previous questions were about noise on non-switching wire
  - Finite drive ( $R$ )



 
# Simultaneous Transition

- What happens if lines transition in opposite directions?


 
# Simultaneous Transition


- What happens if lines transition in opposite directions?
  - Must charge  $C_1$  by  $2V$
  - Or looks like  $2C_1$  between wires





 
# Simultaneous Transition

- What happens if lines transition in same direction?


 
# Simultaneous Transition

- What happens if lines transition in same direction?
  - Looks like no coupling capacitor!




# Where Does it Arise?

---




# Interconnect Cross Section

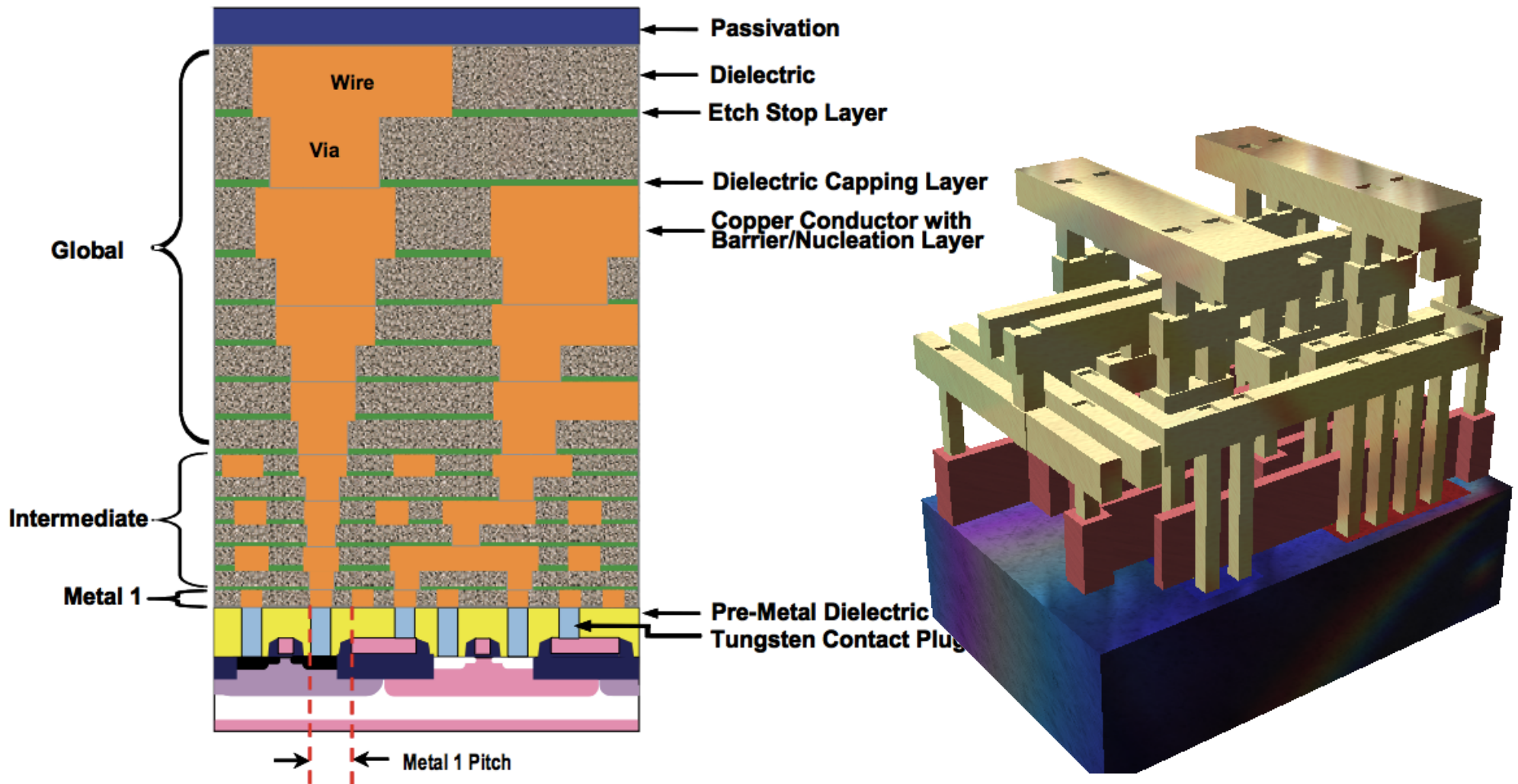



# Standard Cell Area

 



 
# Wires


---

- Will be capacitively coupled to many adjacent wires of varying degrees


 
# Rowhammer Attack

- ❑ Smaller and higher density DRAMs leads to increase electromagnetic interactions between memory cells
- ❑ Rapid wordline switching can affect adjacent words causing them to flip





# Noise Implications

---

- ❑ *So what* if we have noise?
- ❑ If the noise is less than the noise margin, nothing happens
- ❑ Static CMOS logic will eventually settle to correct output even if disturbed by large noise spikes
  - But glitches cause extra delay
  - Also cause extra power from false transitions
- ❑ Dynamic logic never recovers from glitches
  - Can't correct mid-cycle, need precharge nodes
- ❑ Memories and other sensitive circuits also can produce the wrong result







# Wire Engineering

---

- ❑ Goal: achieve delay, area, power goals with acceptable noise
- ❑ Degrees of freedom:
 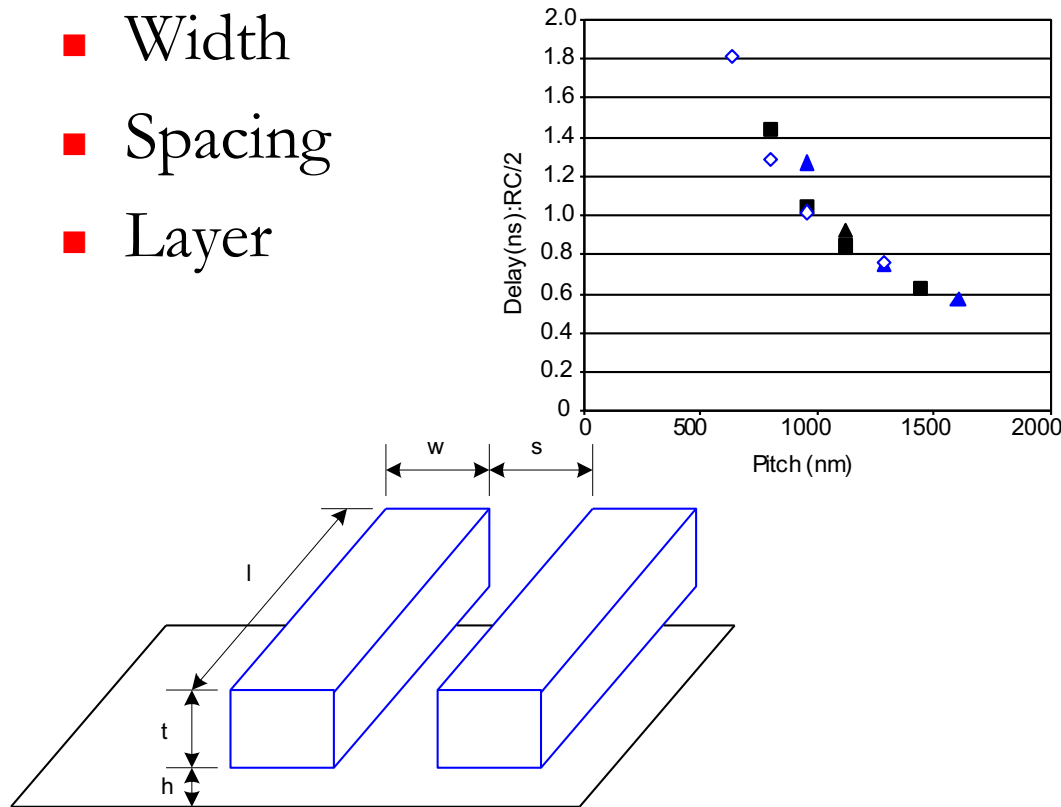
# Wire Engineering






- Goal: achieve delay, area, power goals with acceptable noise
- Degrees of freedom:
  - Width
  - Spacing
  - Layer





     
# Wire Engineering

- Goal: achieve delay, area, power goals with acceptable noise
- Degrees of freedom:
  - Width
  - Spacing
  - Layer
  - Shielding


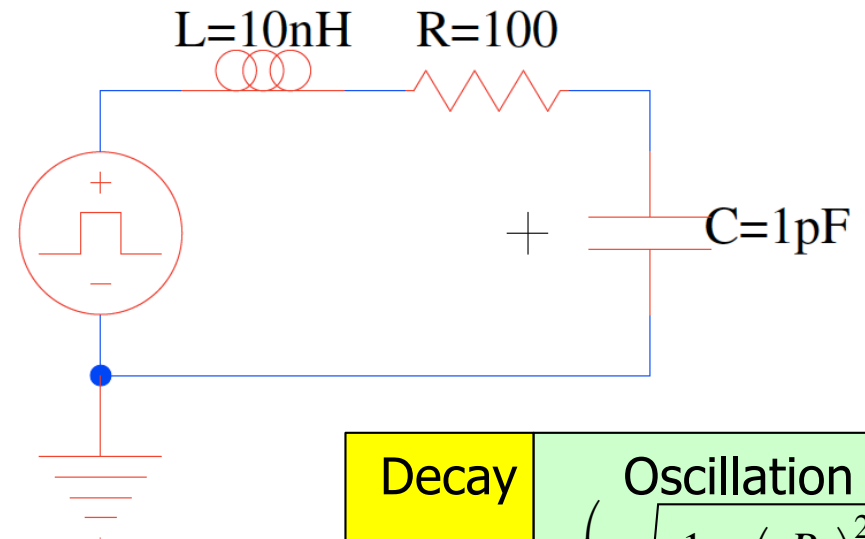
# Idea

- ❑ Long wires are inductive
  - **Avoid** them
  - Especially on power supplies
- ❑ Bypass capacitors help
- ❑ Capacitance is everywhere
  - Especially between adjacent wires
- ❑ Will get “noise” from crosstalk
- ❑ Clocked and driven wires
  - Slow down transitions
- ❑ Undriven wires voltage changed
- ❑ Can cause spurious transitions



$$V_2 = V_s + B e^{\left(-\frac{R}{2L}\right)t} e^{\left(j\sqrt{\frac{1}{LC} - \left(\frac{R}{2L}\right)^2}\right)t}$$

Decay	Oscillation
-------	-------------



# Admin

---

- Project 2
  - Final report due Friday 4/26
- Final Exam
  - Date: 5/3 (W)
  - Location: TBD
  - Time: 3:00pm -5:00pm



# Acknowledgement

---

- ❑ Prof. André DeHon (University of Pennsylvania)
- ❑ Prof. Tania Khanna (University of Pennsylvania)