

ESE370: Circuit-Level Modeling, Design, and Optimization for Digital Systems

Lec 2: January 18, 2023

Transistor Introduction and
Gates from Transistors





Today


- ❑ Transistors – MOSFET
- ❑ Zero-th order transistor model
 - Good enough for [what?]
- ❑ Basic Digital Gates
- ❑ Boolean Logic
 - Basic Algebra
 - Minimum Sum of Products/K-maps
- ❑ How to construct static CMOS gates
 - Gate function identification (preclass)
 - CMOS gate structure
 - Pullup/pulldown networks

Transistor

- ❑ Electrical switch to conduct electricity
 - Instead of physically connecting conducting materials to conduct electricity, apply a voltage to conduct



MOSFET

 


$$V_{GS} = V_G - V_S$$

$$V_{DS} = V_D - V_S$$

$$I_D = f(V_{DS}, V_{GS})$$


- Metal Oxide Semiconductor Field Effect Transistor
 - Primary **active** component for the term
 - Three terminal device
 - Voltage at gate controls conduction between two other terminals (source, drain)

MOSFET – IV Characteristics

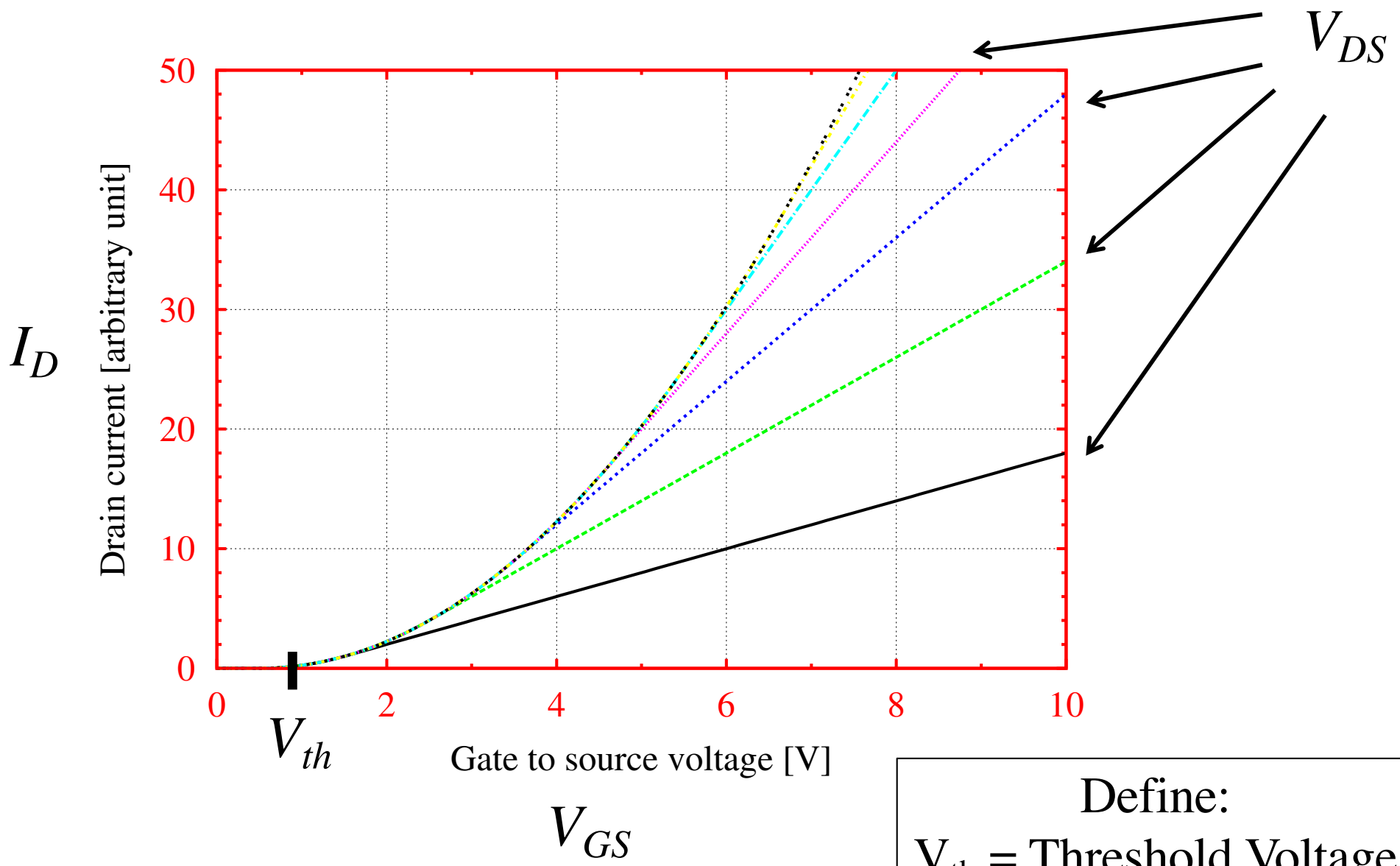


Define:
 $V_{th} = \text{Threshold Voltage}$


MOSFET – IV Characteristics

 

MOSFET – IV Characteristics

 

MOSFET – Zeroeth Order Model

 

□ Ideal Switch



$V_{GS} > V_{th} \rightarrow$ switch is closed, conducts

$V_{GS} < V_{th} \rightarrow$ switch is open, does not conduct

□ Gate draws no current from input


- Loads input capacitively (gate capacitance)

MOSFET – Zeroeth Order Model

 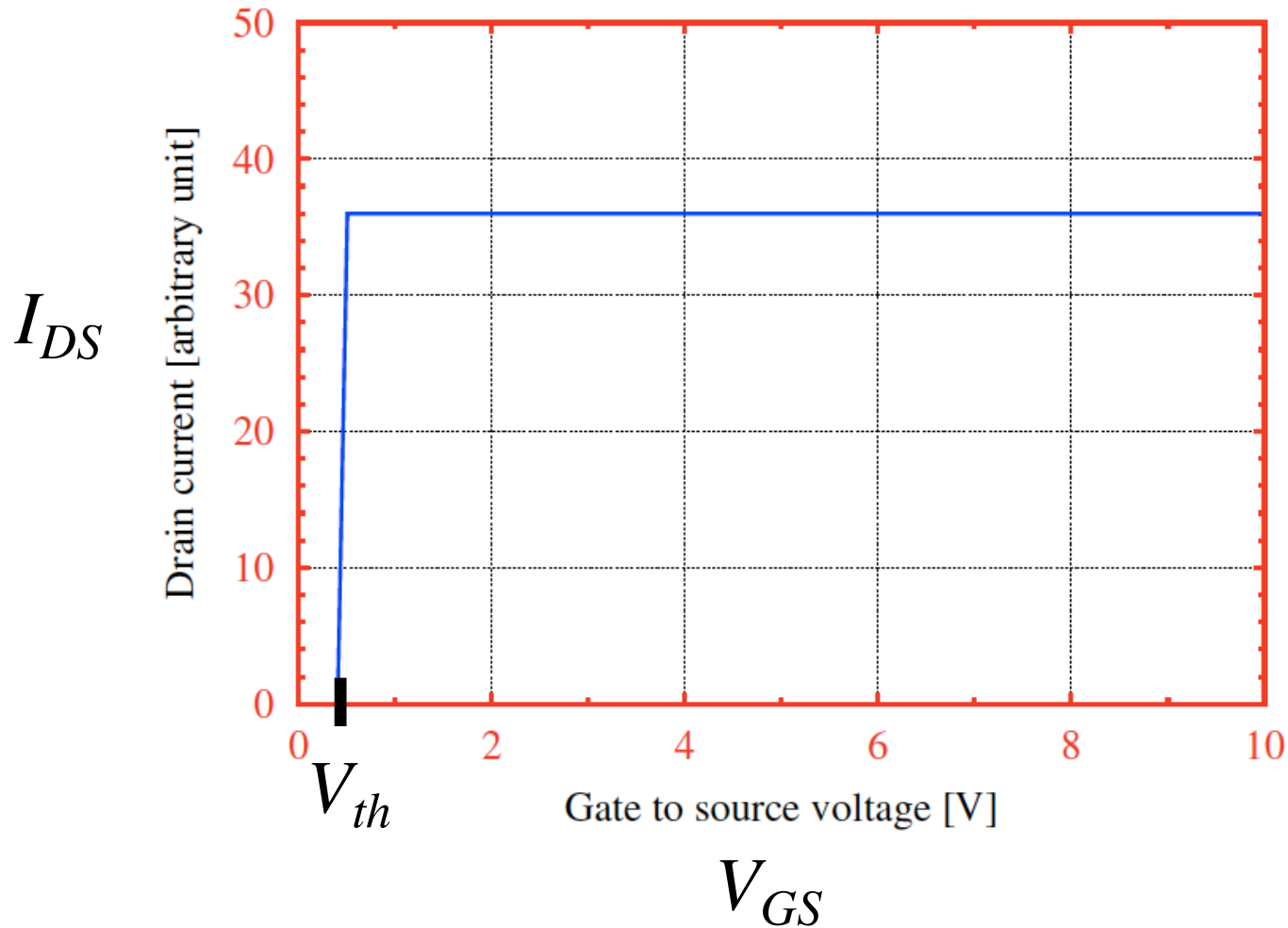

MOSFET - Symmetric

 
- ❑ Switch turned on for positive V_{GS}
 - Which side is drain or source?



MOSFET – N-Type

- Switch turned on for positive V_{GS}

$$V_D > V_S$$

 


$V_{th,n} > 0$
 $V_{GS} > V_{th,n}$
to conduct

MOSFET – N-Type, P-Type

□ Switch turned on for
positive V_{GS}


$$V_D > V_S$$

 

$V_{th,n} > 0$
 $V_{GS} > V_{th,n}$
to conduct

□ Switch turned on for
negative V_{GS}


$$V_S > V_D$$

 

MOSFET – N-Type, P-Type

□ Switch turned on for positive V_{GS}


$$V_D > V_S$$

 

$V_{th,n} > 0$
 $V_{GS} > V_{th,n}$
to conduct

□ Switch turned on for negative V_{GS}

$$V_S > V_D$$

 


$V_{th,p} < 0$
 $V_{GS} < V_{th,p}$
to conduct

MOSFET – N-Type, P-Type

□ Switch turned on for positive V_{GS}


$$V_D > V_S$$

 

$V_{th,n} > 0$
 $V_{GS} > V_{th,n}$
to conduct

□ Switch turned on for negative V_{GS}

$$V_S > V_D$$

 



$|V_{th,p}| > 0$
 $|V_{GS}| > |V_{th,p}|$
to conduct



Apply zero-order model

Note S, D annotation on this slide (won't be labeled in future)

Why is it this way?


 
 




Apply zero-order model?

What happens when $V_{in} = V_{dd} > V_{thn}$?
   
$$V_{th,p} = -V_{th,n}$$
$$V_{GS} = V_G - V_S$$








Apply zero-order model?

What happens when $V_{in} = V_{dd} > V_{thn}$?
   
$$V_{th,p} = -V_{th,n}$$
$$V_{GS} = V_G - V_S$$







Apply zero-order model?

What happens when $V_{in} = V_{dd} > V_{thn}$?
  
$$V_{th,p} = -V_{th,n}$$
$$V_{GS} = V_G - V_S$$






$$V_{GS} = V_G - V_S = V_{dd} > V_{th,n}$$



Apply zero-order model?

What happens when $V_{in} = V_{dd} > V_{thn}$?
   
$$V_{th,p} = -V_{th,n}$$
$$V_{GS} = V_G - V_S$$






$$V_{GS} = V_G - V_S = V_{dd} > V_{th,n}$$

Apply zero-order model?

What happens when $V_{in} = V_{dd} > V_{thn}$?

$$V_{th,p} = -V_{th,n}$$

$$V_{GS} = V_G - V_S$$

   

$$V_{GS} = V_G - V_S = V_{dd} > V_{th,n}$$




Apply zero-order model?

What happens when $V_{in} = V_{dd} > V_{thn}$?

$$V_{GS} = 0 > V_{th,p}$$

$$V_{th,p} = -V_{th,n}$$

$$V_{GS} = V_G - V_S$$

   

$$V_{GS} = V_G - V_S = V_{dd} > V_{th,n}$$

Apply zero-order model?


What happens when $V_{in} = V_{dd} > V_{thn}$?

$$V_{GS} = 0 > V_{th,p}$$

$$|V_{GS}| = 0 < |V_{th,p}|$$

$$V_{th,p} = -V_{th,n}$$

$$V_{GS} = V_G - V_S$$

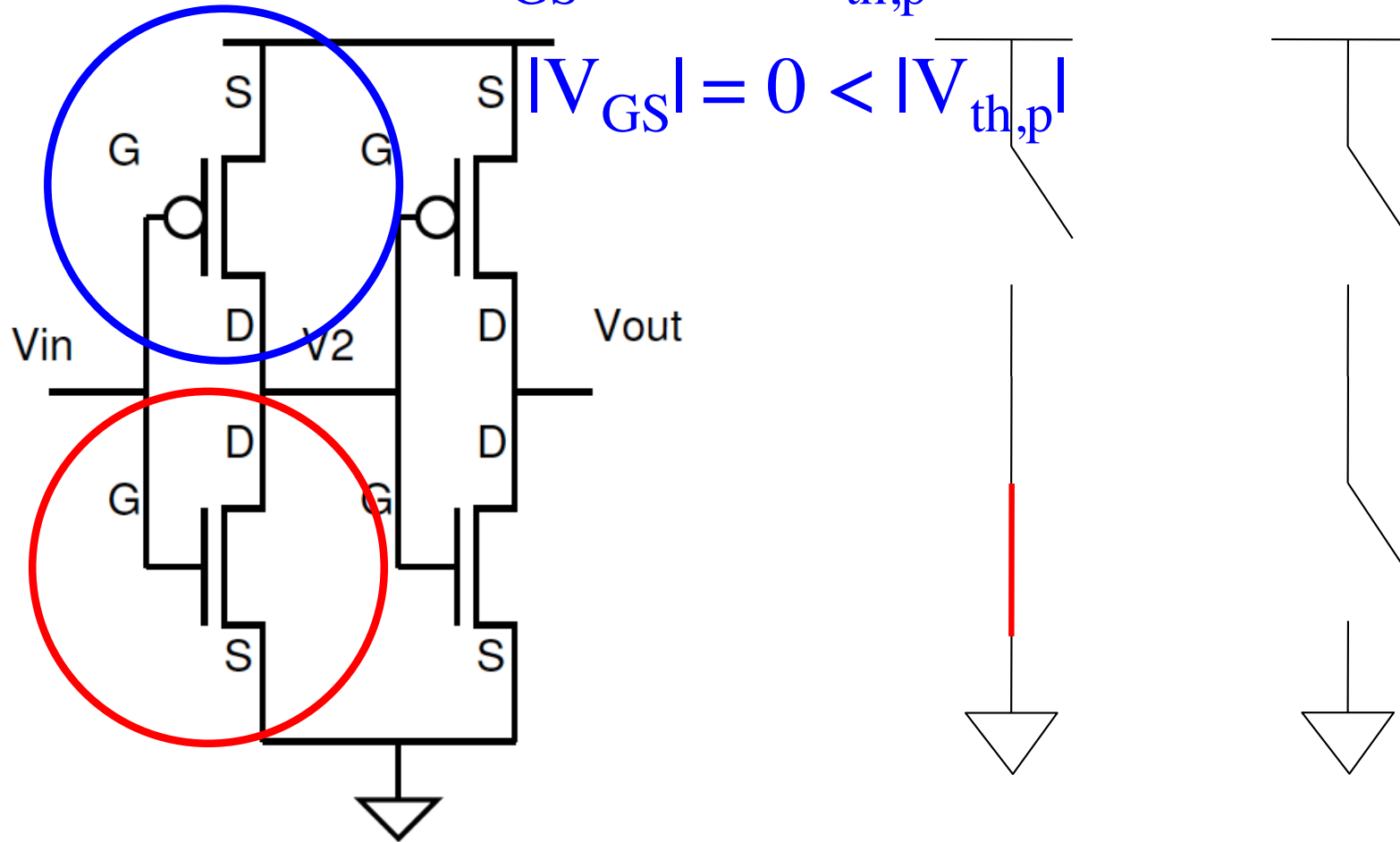

$$V_{GS} = V_G - V_S = V_{dd} > V_{th,n}$$




Apply zero-order model?

What happens when $V_{in} = V_{dd} > V_{thn}$?

$$V_{dd} \quad |V_{GS}| = 0 < |V_{th,p}|$$

$$V_{th,p} = -V_{th,n}$$

$$V_{GS} = V_G - V_S$$

   



$$V_{GS} = V_G - V_S = V_{dd} > V_{th,n}$$

Apply zero-order model?

What happens when $V_{in} = V_{dd} > V_{thn}$?

$$V_{dd} \quad |V_{GS}| = 0 < |V_{th,p}|$$
  
$$\begin{aligned} V_{th,p} &= -V_{th,n} \\ V_{GS} &= V_G - V_S \end{aligned}$$





$$V_{GS} = V_G - V_S = V_{dd} > V_{th,n}$$

Apply zero-order model?

What happens when $V_{in} = V_{dd} > V_{thn}$?

$$V_{dd} \quad |V_{GS}| = 0 < |V_{th,p}|$$
  
$$\begin{aligned} V_{th,p} &= -V_{th,n} \\ V_{GS} &= V_G - V_S \end{aligned}$$





$$V_{GS} = V_G - V_S = V_{dd} > V_{th,n}$$

Apply zero-order model?

What happens when $V_{in} = V_{dd} > V_{thn}$?

$$V_{dd} \quad |V_{GS}| = 0 < |V_{th,p}|$$
  
$$\begin{aligned} V_{th,p} &= -V_{th,n} \\ V_{GS} &= V_G - V_S \end{aligned}$$



$$V_{GS} = 0 < V_{th,n}$$



$$V_{GS} = V_G - V_S = V_{dd} > V_{th,n}$$

Apply zero-order model?

What happens when $V_{in} = V_{dd} > V_{thn}$?

$$V_{dd} \quad |V_{GS}| = 0 < |V_{th,p}|$$
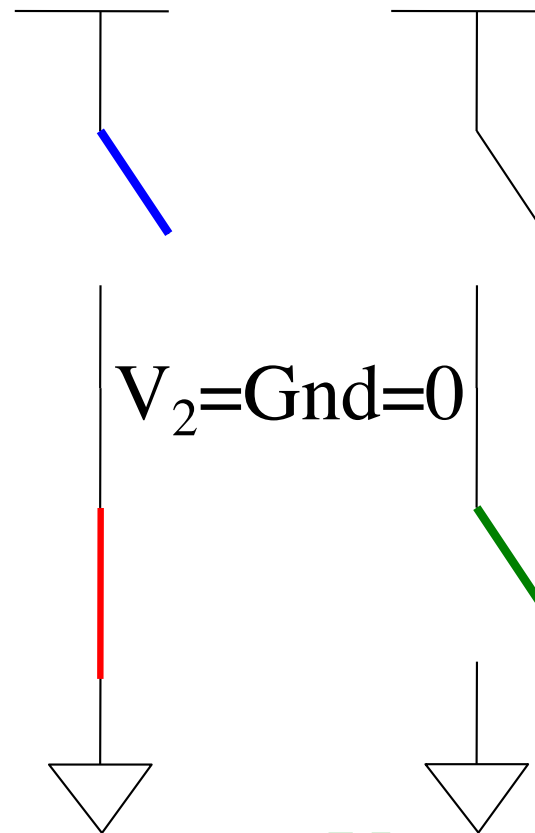 
$$\begin{aligned} V_{th,p} &= -V_{th,n} \\ V_{GS} &= V_G - V_S \end{aligned}$$



$$V_{GS} = 0 < V_{th,n}$$



$$V_{GS} = V_G - V_S = V_{dd} > V_{th,n}$$

Apply zero-order model?

What happens when $V_{in} = V_{dd} > V_{thn}$?

$$V_{dd} \quad |V_{GS}| = 0 < |V_{th,p}|$$
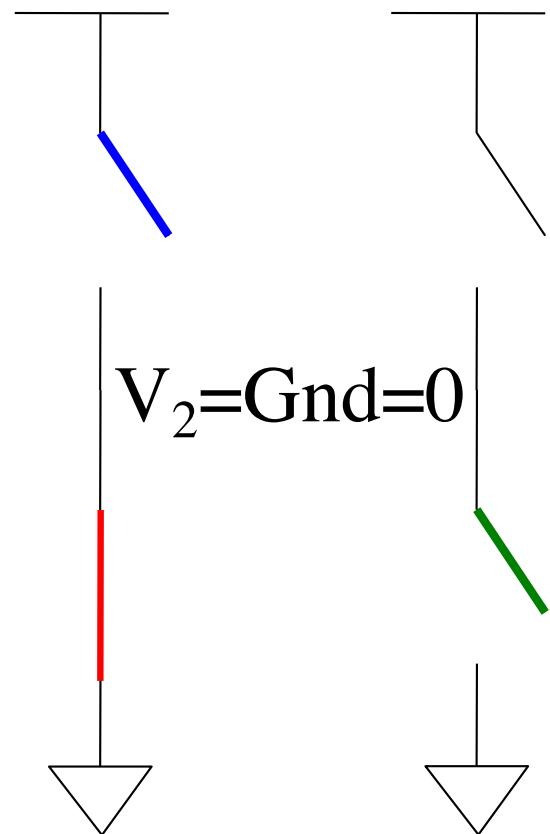 
$$\begin{aligned} V_{th,p} &= -V_{th,n} \\ V_{GS} &= V_G - V_S \end{aligned}$$



$$V_{GS} = 0 < V_{th,n}$$

$$V_{GS} = V_G - V_S = V_{dd} > V_{th,n}$$



Apply zero-order model?

What happens when $V_{in} = V_{dd} > V_{thn}$?

$$V_{th,p} = -V_{th,n}$$

$$V_{GS} = V_G - V_S$$

$$V_{dd} \quad |V_{GS}| = 0 < |V_{th,p}|$$

  



$$V_{GS} = V_G - V_S = V_{dd} > V_{th,n}$$

Apply zero-order model?

What happens when $V_{in} = V_{dd} > V_{thn}$?

$$V_{dd} \quad |V_{GS}| = 0 < |V_{th,p}|$$
  
$$\begin{aligned} V_{th,p} &= -V_{th,n} \\ V_{GS} &= V_G - V_S \end{aligned}$$



$$V_{GS} = V_G - V_S = V_{dd} > V_{th,n}$$



Apply zero-order model?

What happens when $V_{in} = V_{dd} > V_{thn}$?

$$V_{dd} \quad |V_{GS}| = 0 < |V_{th,p}|$$

$$V_{th,p} = -V_{th,n}$$

$$V_{GS} = V_G - V_S$$

  


$$V_{out} = V_{dd}$$

$$V_{GS} = V_G - V_S = V_{dd} > V_{th,n}$$




Apply zero-order model?

What happens when $V_{in} = 0$?

 
 
$$V_{th,p} = -V_{th,n}$$
$$V_{GS} = V_G - V_S$$





Convince yourself that $V_{out} = 0$.



Zeroeth Order Model

- Allows us to reason (mostly) at logic level about steady-state functionality of typical gate circuits before worrying about performance (speed, power, etc.) details

What is missing in Zeroeth Order Model?

  


- ❑ Delay
 - Parasitic capacitances and resistances
- ❑ Dynamics
- ❑ Zeroeth Order captures behaviour if our circuit is **not**:
 - Capacitively loaded, acyclic (if there are Loops)

Digital Logic




Basic Digital Gates

NOT
 $Y = \bar{X}$

 


X	Y
0	1
1	0

AND
 $Y = A \cdot B$

 

A	B	Y
0	0	0
0	1	0
1	0	0
1	1	1


OR
 $Y = A + B$

 

A	B	Y
0	0	0
0	1	1
1	0	1
1	1	1


Basic Digital Gates

NOT
 $Y = \bar{X}$

 


X	Y
0	1
1	0

AND
 $Y = A \cdot B$

 


A	B	Y	Z
0	0	0	1
0	1	0	1
1	0	0	1
1	1	1	0

OR
 $Y = A + B$

 


A	B	Y	Z
0	0	0	1
0	1	1	0
1	0	1	0
1	1	1	0

NAND
 $Z = \overline{A \cdot B}$

 


NOR
 $Z = \overline{A + B}$

 



Basic Digital Gates

 

A	B	C	Z
0	0	0	1
0	0	1	1
0	1	0	1
0	1	1	1
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	0




Boolean Algebra

□ **TABLE 2-3**
Basic Identities of Boolean Algebra

1.	$X + 0 = X$	2.	$X \cdot 1 = X$	
3.	$X + 1 = 1$	4.	$X \cdot 0 = 0$	
5.	$X + X = X$	6.	$X \cdot X = X$	
7.	$X + \bar{X} = 1$	8.	$X \cdot \bar{X} = 0$	
9.	$\overline{\bar{X}} = X$			
10.	$X + Y = Y + X$	11.	$XY = YX$	Commutative
12.	$X + (Y + Z) = (X + Y) + Z$	13.	$X(YZ) = (XY)Z$	Associative
14.	$X(Y + Z) = XY + XZ$	15.	$X + YZ = (X + Y)(X + Z)$	Distributive
16.	$\overline{X + Y} = \bar{X} \cdot \bar{Y}$	17.	$\overline{X \cdot Y} = \bar{X} + \bar{Y}$	DeMorgan's



Combination

 

Boolean Expressions


- Sum-of-products form (SOP)
 - Eg. $ABC+DEF+GHI$
- Product-of-sums form (POS)
 - Eg. $(A+B+C)(D+E+F)(G+H+I)$
- Convert between the two with Boolean algebra
 - DeMorgan's Law

$$A + B = \overline{\overline{A} \cdot \overline{B}}$$

$$A \cdot B = \overline{\overline{A} + \overline{B}}$$



Combination

 



Canonical Form

- Every minterm in your expression has every variable

Row Number	A	B	C	f
0	0	0	0	0
1	0	0	1	0
2	0	1	0	0
3	0	1	1	1
4	1	0	0	0
5	1	0	1	0
6	1	1	0	1
7	1	1	1	1

Canonical Form



- Every minterm in your expression has every variable

Row Number	A	B	C	f
0	0	0	0	0
1	0	0	1	0
2	0	1	0	0
3	0	1	1	1
4	1	0	0	0
5	1	0	1	0
6	1	1	0	1
7	1	1	1	1

$f(A, B, C) = ABC + ABC\bar{C} + \bar{A}BC$

What is a K(arnaugh)-map?

  - ❑ A grid of squares (representing truth table)
- ❑ Each square represents one minterm
- ❑ The minterms are ordered according to **Gray code**
 - Only one variable changes between adjacent squares
- ❑ Squares on edges are considered adjacent to squares on opposite edges
 - I.e Table wraps around
- ❑ K-maps are clumsy with more than 4 variables



K-map Examples (Preclass 1)

- 2-variable

		B	
		0	1
A	0		
	1		

Eg: $Z = A'B' + AB' + A'B$

- 3-variable

		BC			
		00	01	11	10
A	0				
	1				

K-map Examples (Preclass 2)

- 2-variable

		B	0	1
A	0			
	1			

Eg: $Z = A'B' + AB' + A'B$


- 3-variable

				BC	00	01	11	10
A	0							
	1							

Eg: $Z = A'B'C' + A'B + ABC' + AC$


CMOS Gates

How to construct static CMOS gates

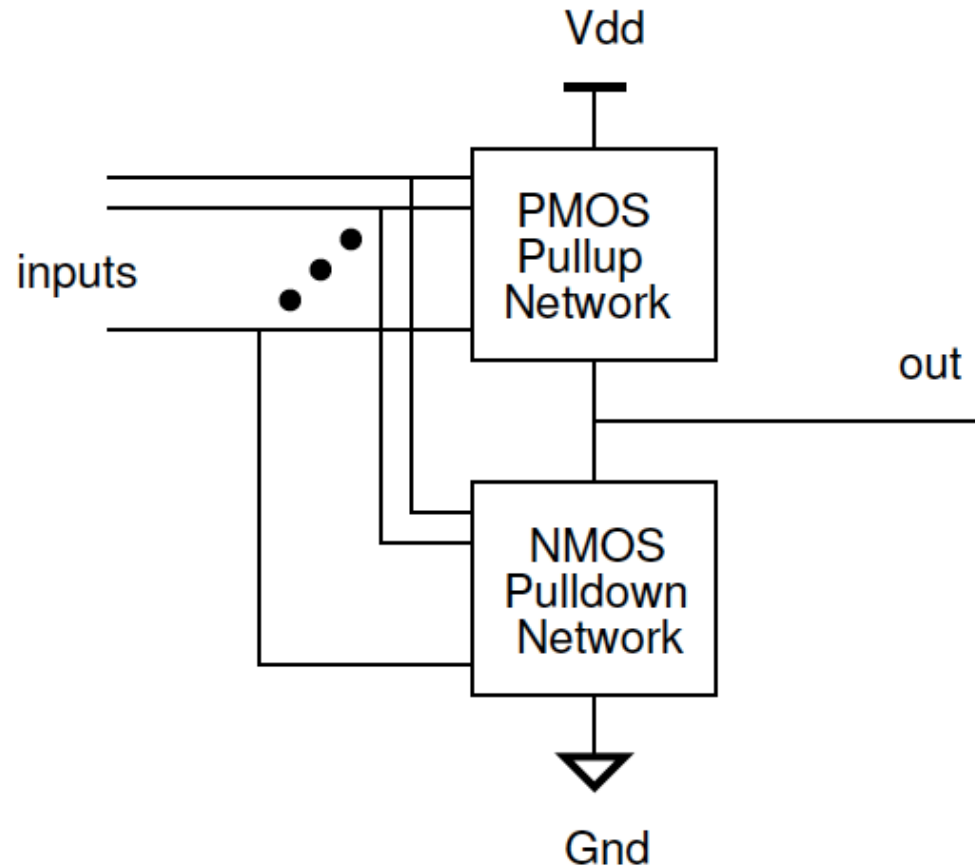


- Complementary Metal Oxide Semiconductor

What gate is this? Preclass 3

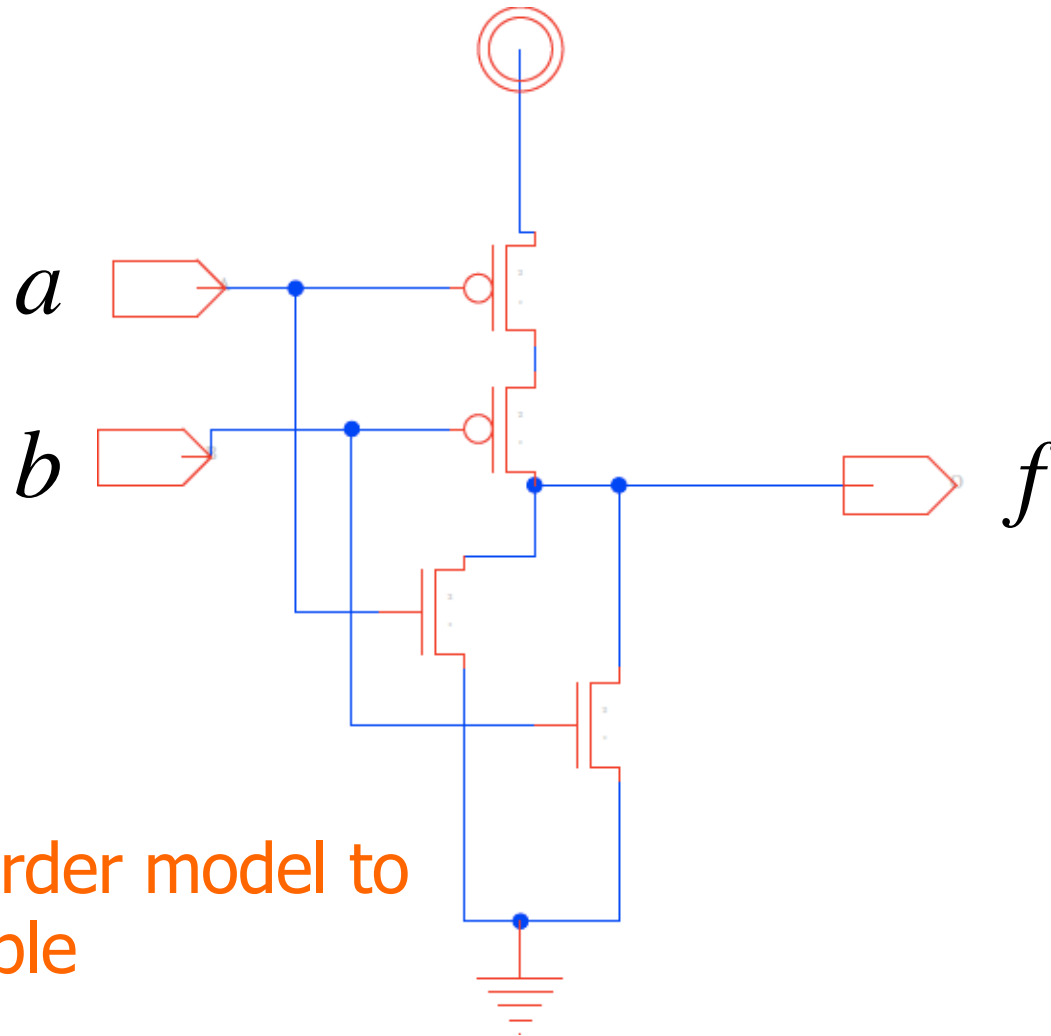


Hint: use zero order model to make a truth table

What gate is this?

 


What gate is this? Preclass 4

 


What is f in minimum-sum-of-products form?



What gate is this?

 

What gate is this?

 

Static CMOS Gate Structure

  




CMOS

- ❑ Complementary Metal Oxide Semiconductor
- ❑ Uses *complementary* transistors
 - NMOS, PMOS
- ❑ Pull-down and pull-up networks are *complements* of each other
 - Only one network active (on) at a time to charge or discharge output to V_{dd} or Gnd respectively

Static CMOS Gate Structure

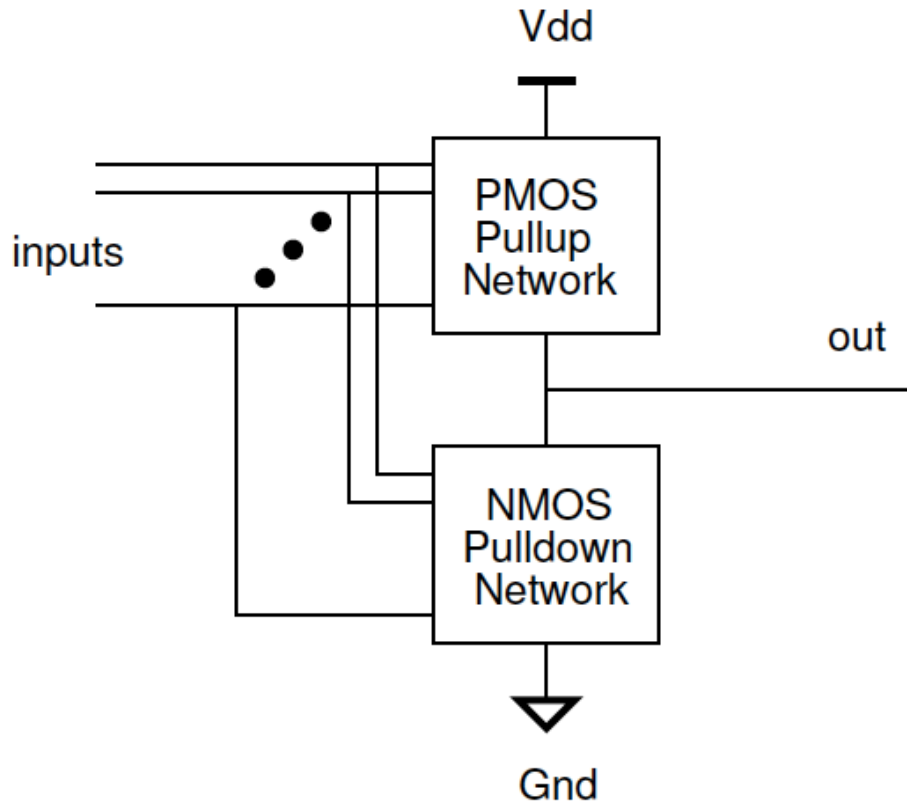


- ❑ Drives rail-to-rail
 - Power rails are V_{dd} and Gnd
 - output is V_{dd} or Gnd
- ❑ Input connects to gates
 - load is capacitive
- ❑ Once output node is charged doesn't use energy (no static current)
- ❑ Output actively driven

Gate Design Example Preclass 5

□ Design gate to perform: $f = (\bar{a} + \bar{b}) \cdot \bar{c}$


□ Strategy:

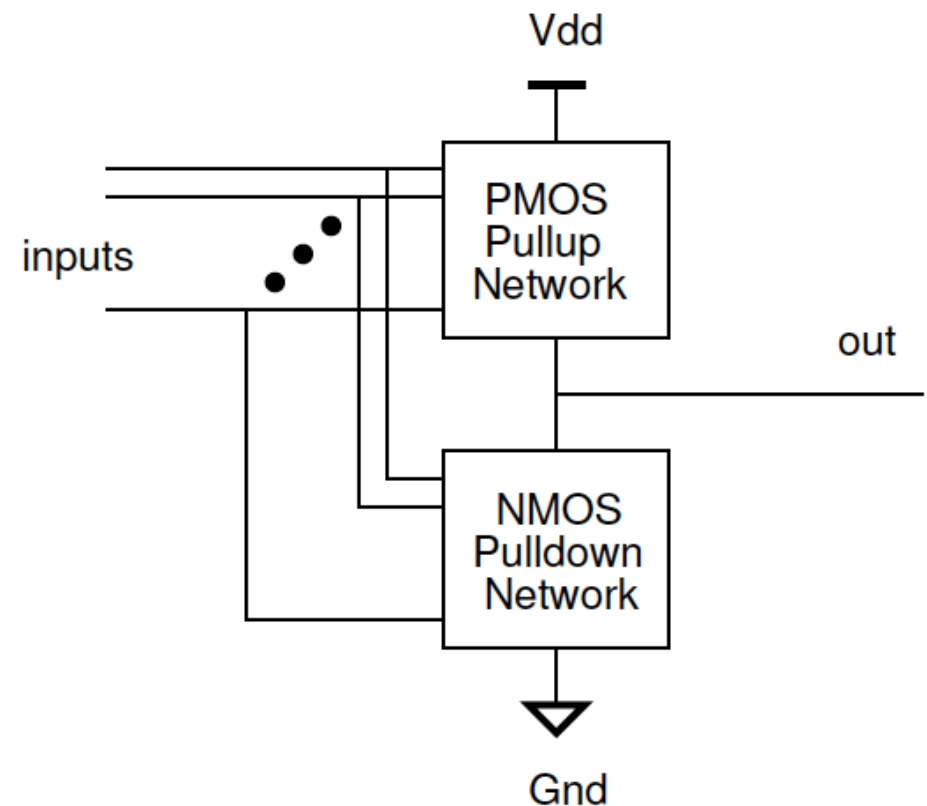1. Use static CMOS structure
2. Design PMOS pullup for f
3. Use DeMorgan's Law to determine f'
4. Design NMOS pulldown for f'




Gate Design Example

 - Design gate to perform: $f = (\bar{a} + \bar{b}) \cdot \bar{c}$
- PMOS Pullup for f ?




Gate Design Example

 - Design gate to perform: $f = (\bar{a} + \bar{b}) \cdot \bar{c}$
- What is f' ?
 - DeMorgan's Law





Gate Design Example

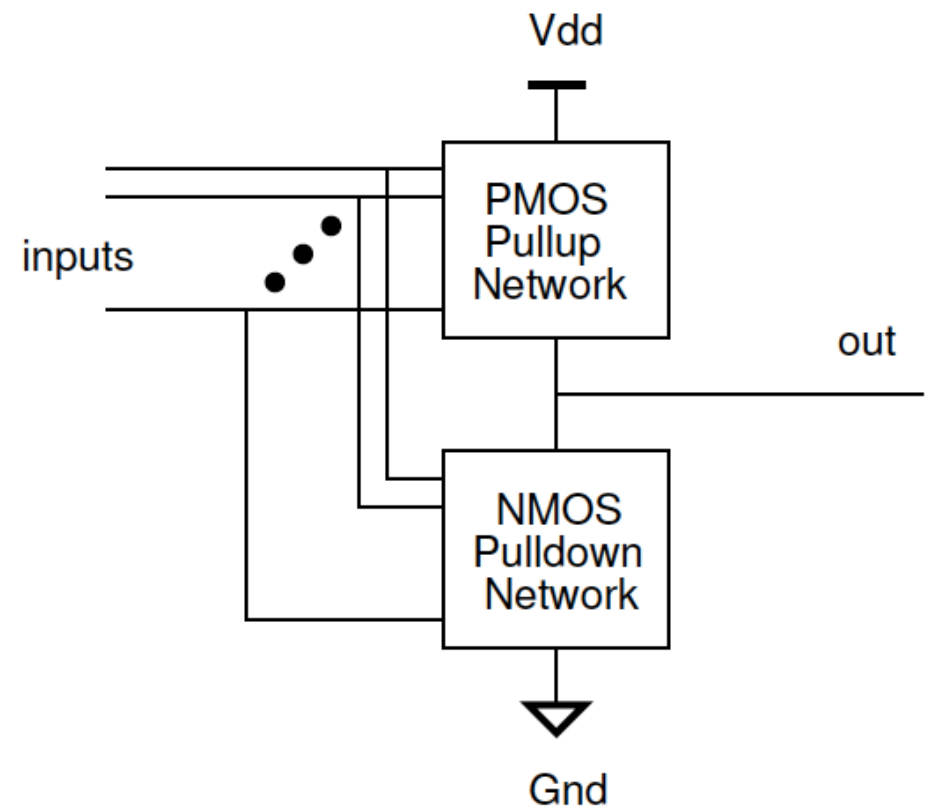- Design gate to perform: $f = (\bar{a} + \bar{b}) \cdot \bar{c}$
- Design NMOS pulldown for f'



Gate Design Example

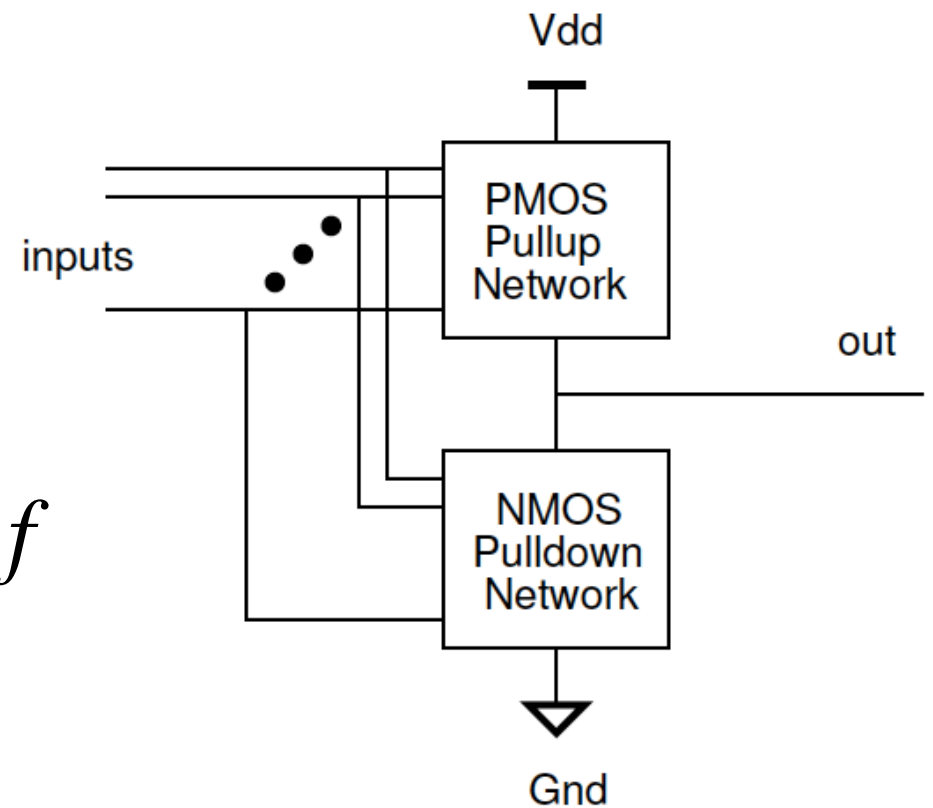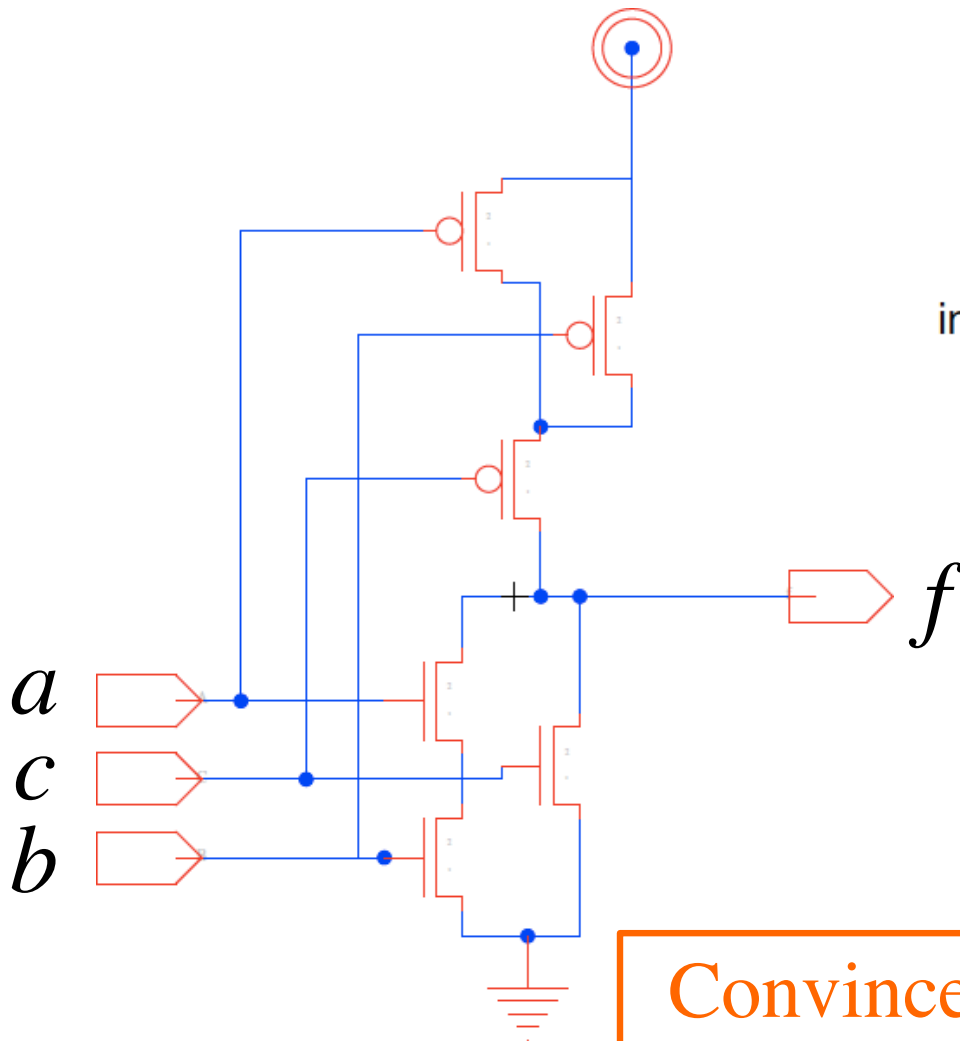- Design gate to perform: $f = (\bar{a} + \bar{b}) \cdot \bar{c}$




Convince yourself with a truth table.





Inverting Stage

 - ❑ Each stage of Static CMOS gate is inherently inverting



NAND/NOR Fundamental Gates

  




How implement OR?



How implement OR?

 



Cascading Stages

- ❑ Can always cascade “stages” to build more complex gates
- ❑ Could simply build nor2 or nand2 at circuit level and assemble arbitrary logic by combining – universality
 - but may not be smallest/fastest/least power

Implement: $f = a \cdot \bar{b}$

□ Pullup?


□ Pulldown?

Hint: use cascading stages

Implement: $f = a \cdot \bar{b}$

□ Pullup?

□ Pulldown?

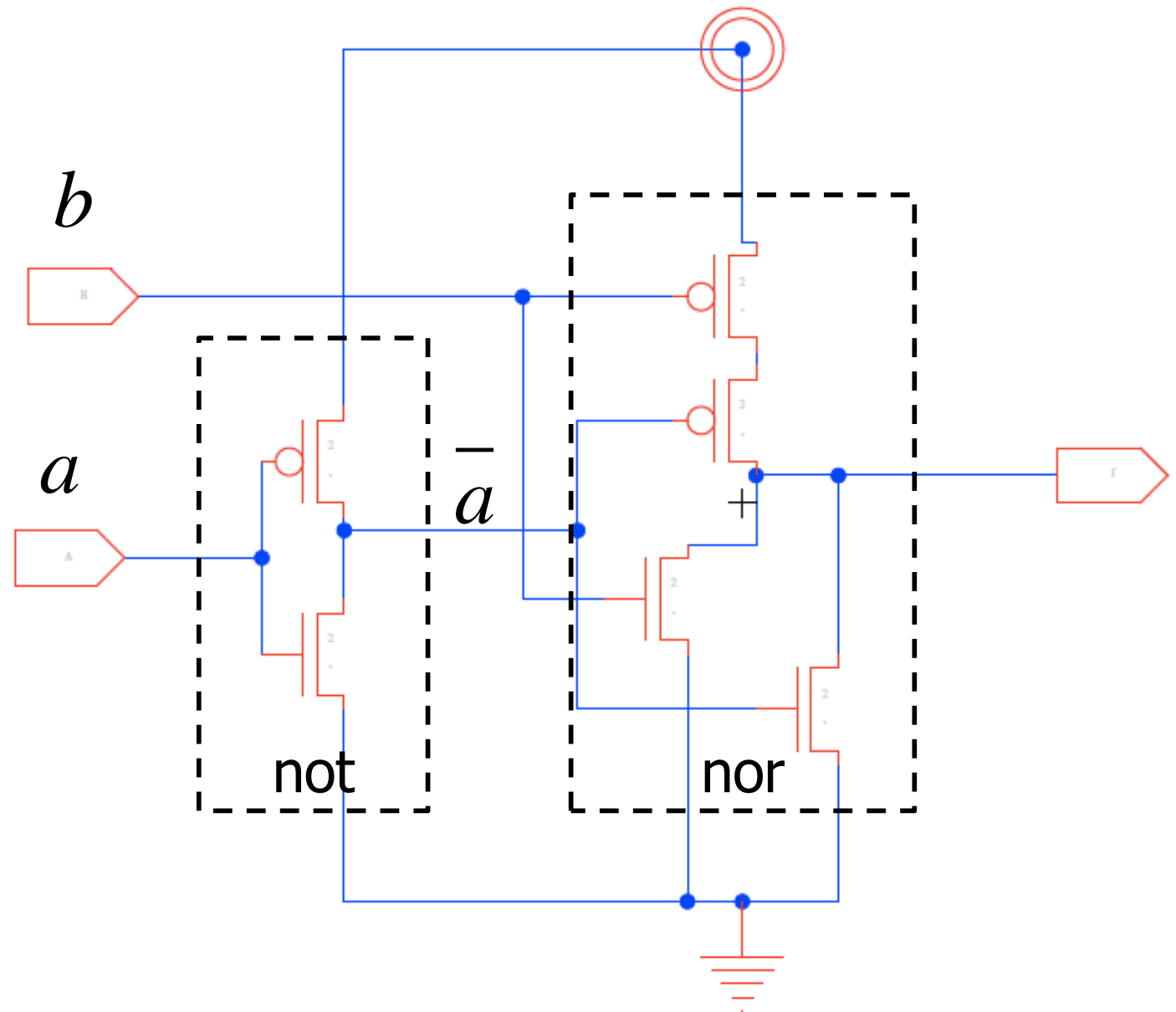




Big Idea

- ❑ MOSFET Transistor as switch
- ❑ Functionality-driven simplified modeling (Zero order)
 - Aid reasoning
 - Sanity check
 - Simplify design
- ❑ CMOS Gate Design
 - Complementary pull-up and pull-down networks

Big Idea

□ Systematic construction of any gate from transistors

 1. Use static CMOS structure
2. Design PMOS pullup for f
3. Use DeMorgan's Law to determine f'
4. Design NMOS pulldown for f'





Admin

- ❑ HW 1 out – due 1/27
 - Will take time to learn Electric CAD tool, start early
- ❑ Monday (1/23) – no lecture, Lab in Detkin
- ❑ Wednesday (1/25) regular physical lecture in LRSM 112B
- ❑ TA office hours announced on Ed Discussion (Mon- Friday)



Acknowledgement

- ❑ Prof. André DeHon (University of Pennsylvania)
- ❑ Prof. Tania Khanna (University of Pennsylvania)