

 


$W_p = 1$

 

$W_n = 1$

 

1. Size  $W_n$  or  $W_p$  for correct operation with  $V_{ol} \leq 0.1V_{dd}$  and  $V_{oh} \geq 0.9V_{dd}$ .

	$W_p$	$W_n$	$C_{in}$ in multiples of $C_0$
	1		
		1	

2. Size for  $R_0/2$  worst-case drive (Assume  $R_{p0} = R_{n0}$ ):

	$W_p$	$W_n$	$C_{in}$ in multiples of $C_0$

3. For a k-input NOR gate, sized for worst-case  $R_{drive} = \frac{R_0}{2}$  (Assume  $R_{p0} = R_{n0}$ ):

	Ratioed Gate	CMOS
What is $C_{in}$ as a function of $k$ ?		

4. For what  $k$  does the ratioed gate present lower input capacitive load?

5. Our design example for today will be to design a circuit to detect when two 32b values match with the minimum energy.

$$Out = (A[31 : 0] == B[31 : 0]) \quad (1)$$

- Assume the match condition is relatively uncommon.
- This is a wakeup circuit for some larger computation. The rest of the computation is powered down to save energy. Maybe this is a battery powered device waiting for a password.

- (a) How would you decompose this problem into sub-pieces?
- (b) How would you perform the match operation using nand2 gates and inverters?
- (c) Design a single gate that takes in two inputs and has one output at the transistor level that you could use to perform the match condition.
- (d) List and briefly explain five things in the design space you could explore to look for a good solution? (Said another way: what “knobs” are available for you to turn and “choices” are available for you to make?)
