

Today's Question: How do we drive a large load


(e.g. $C_{load} = 4 \times 10^4 C_0$) with minimum delay?

Detail buffer count and sizing.

Assume:

- velocity saturated sizing for gate drive; inverter sizing is: $W_n=2, W_p=2$
- Start with $C_{diff} = 0$ case (for simplicity)

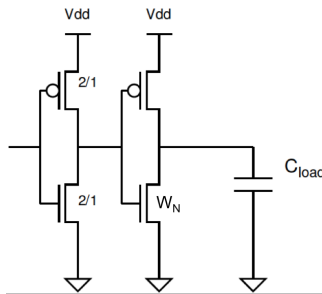1. If we had one inverter stage to size, how should it be sized?




(a) Write delay equation from $R_0/2$ drive through driving C_{load} .

(b) Symbolic expression for delay-minimizing W_N .

(c) Concrete size, W_N , for $C_{load} = 4 \times 10^4 C_0$.

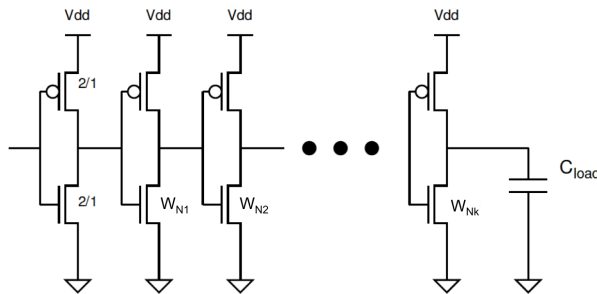2. If we had k inverter stages to size, how should the each be sized?




(a) Write delay equation.

(b) Symbolic expression for delay-minimizing W_{Ni} .

(c) Symbolic expression for total delay using solution above.

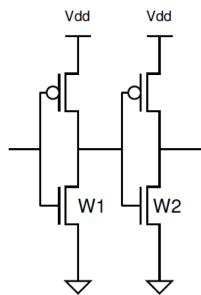3. If $C_{diff} = \gamma C_{gate}$, what is the stage delay for a $W1$ inverter driving a $W2$ inverter?



4. How does optimal stages and buffering change if we include $C_{diff} = \gamma C_{gate}$?

(a) Write delay equation.

(b) Symbolic expression for delay-minimizing W_{Ni} .

(c) Compare with $C_{diff} = 0$ ($\gamma = 0$) case above.

(d) Symbolic expression for total delay.

(e) What is the optimal stage size relation when $\gamma \geq 0$?

(f) For what γ are the following the optimal ρ ?


(Hint: solve for γ in terms of ρ)

ρ	γ
3	
4	

Assume:

- $R_u=60K\Omega$ per 1mm length of wire; $C_u=0.16pF$ per 1mm length of wire
- $R_{wire} = L \times R_u$; $C_{wire} = L \times C_u$;
- $R_0=25K\Omega$; $C_0=0.01fF$
- velocity saturated; $\gamma = C_{diff}/C_{gate} = 1$
- initial, minimum size buffer has $W_p = W_n = 1$

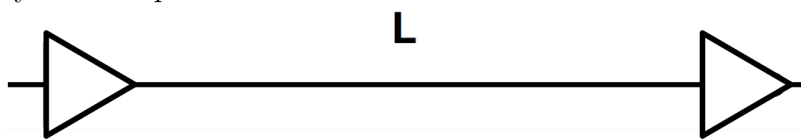5. What is the delay of an unbuffered wire of length $L=1mm$ driven and loaded by a minimum size buffer ($W_p = 1, W_n = 1$)? Draw the equivalent RC network and write a symbolic equation.



• Symbolic Equation:

6. What is the delay of a length $L = 1mm$, when we add N evenly spaced buffers to the wire.

Wire of Length	Delay (ns)	Number in 1mm	Total Delay for 1mm (ns)
1mm		1	
0.5mm		2	
0.1mm		10	
0.01mm		100	
0.001mm		1000	

7. What is the delay of a length L , when we add N evenly spaced buffers to the wire.

• Symbolic Equation:

8. How many buffers do we use to minimize delay?

• Symbolic Equation:

• Number of buffers to minimize delay on 1mm wire:

• Delay at this buffer count:

• Optimum segment length between buffers:

9. How should we size the buffers?

• Symbolic Equation:

• W to minimize delay:

• Delay of 1mm wire at optimal buffer size: